

Switch-Mode Power Concepts

Robert V. White

Embedded Power Labs

Highlands Ranch, Colorado

bob.white@embeddedpowerlabs.com

Seminar Agenda

Part I

- Energy Storage
- Switch Mode Conversion Principle
- The Buck Converter
- Selected Other Topologies

Part II

- Review Of Feedback
- Buck Converter Controller Design Example
- Overview Of Current Mode Control

Seminar Goal

- Goal: Teach You The Operating And Control Principles Of Switch Mode Converters
- Not A Goal: Teach Detailed Design
- Teaching Approach: “Follow The Energy”
 - Understand In Each Switching State Where Energy Is Flowing, Being Stored, And Being Released

Seminar Mechanics

- Part I: 90 Minutes (9:30 – 11:00)
- Break: 30 Minutes (11:00 – 11:30)
- Part II: 90 Minutes (11:30 – 13:00)

- Ask Questions At Any Time

Survey Forms!

Supplementary Material

This Presentation
Plus Appendices

On The USB Flash Drive


Lab Videos And
Simulation Files

Available For Download At:
[www.embeddedpowerlabs.com/
APEC2023.html](http://www.embeddedpowerlabs.com/APEC2023.html)
Only Available Until 30 April 2023


Simulation Files Can Be Run With Either Of Two Free Simulators:
SIMPLIS Elements or Microchip's MPLAB® Mindi™

Switch Mode Regulator Building Blocks

Switch Mode Converter

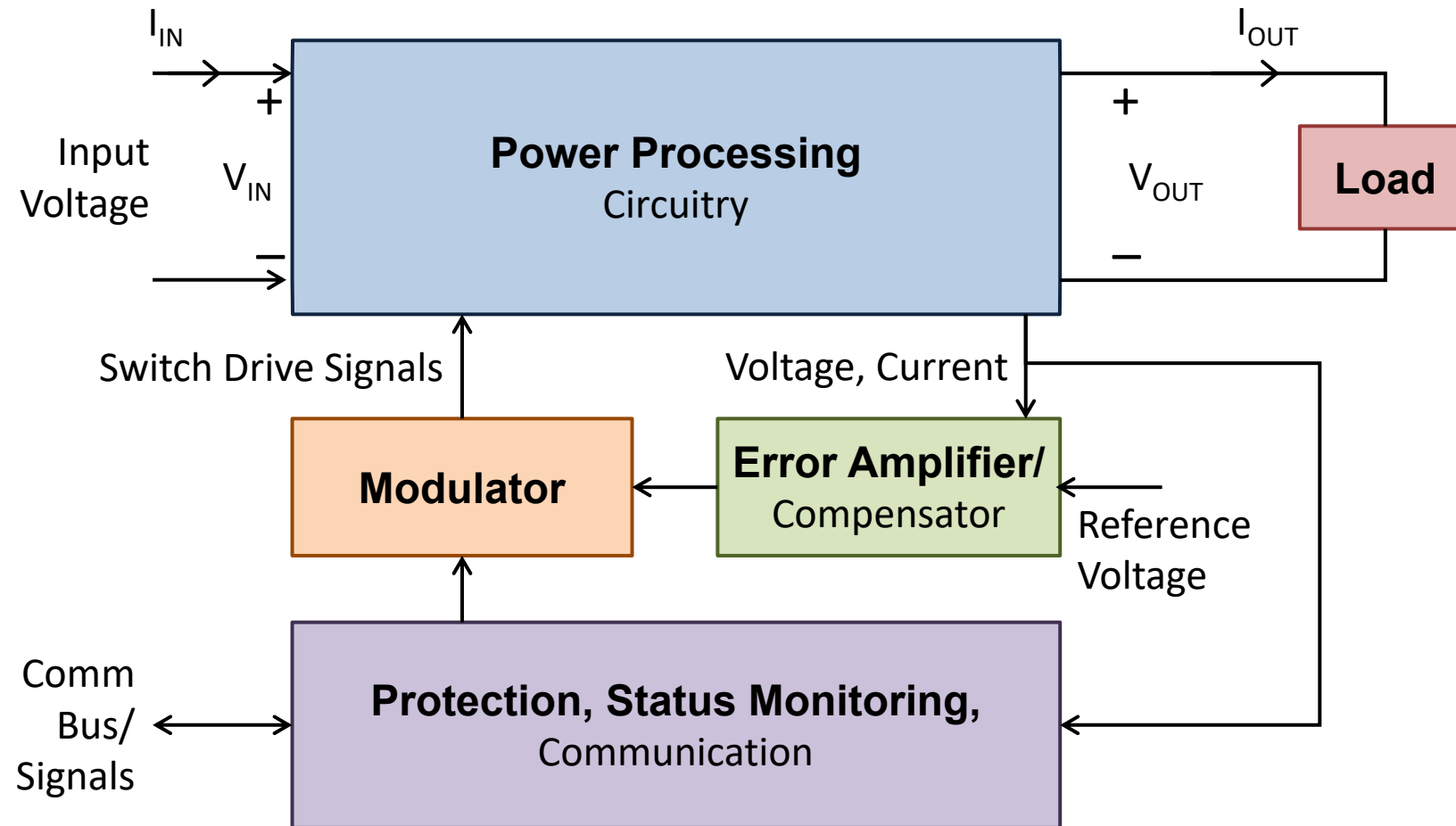


Switch Mode Converter

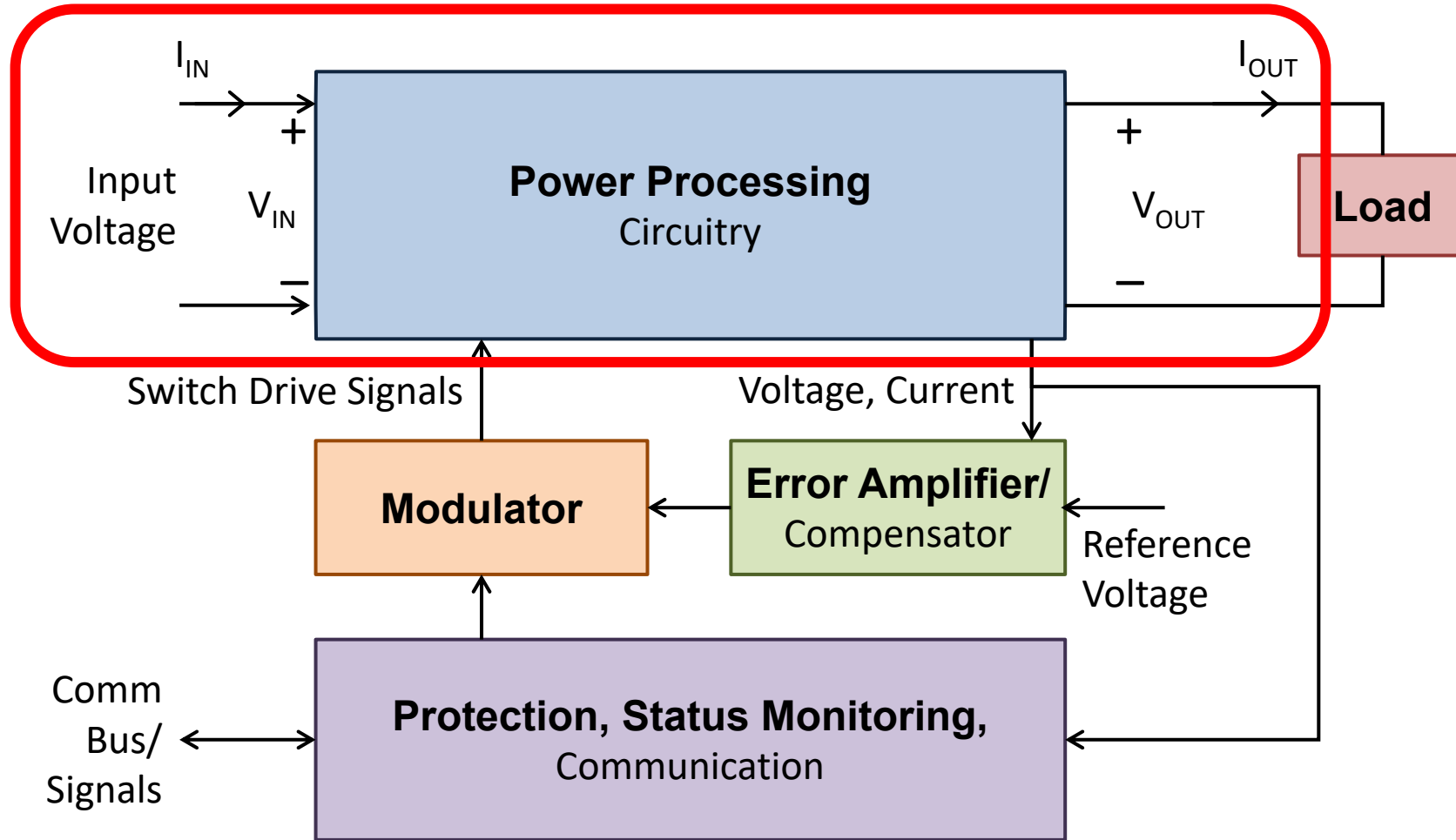


Switch Mode Converter

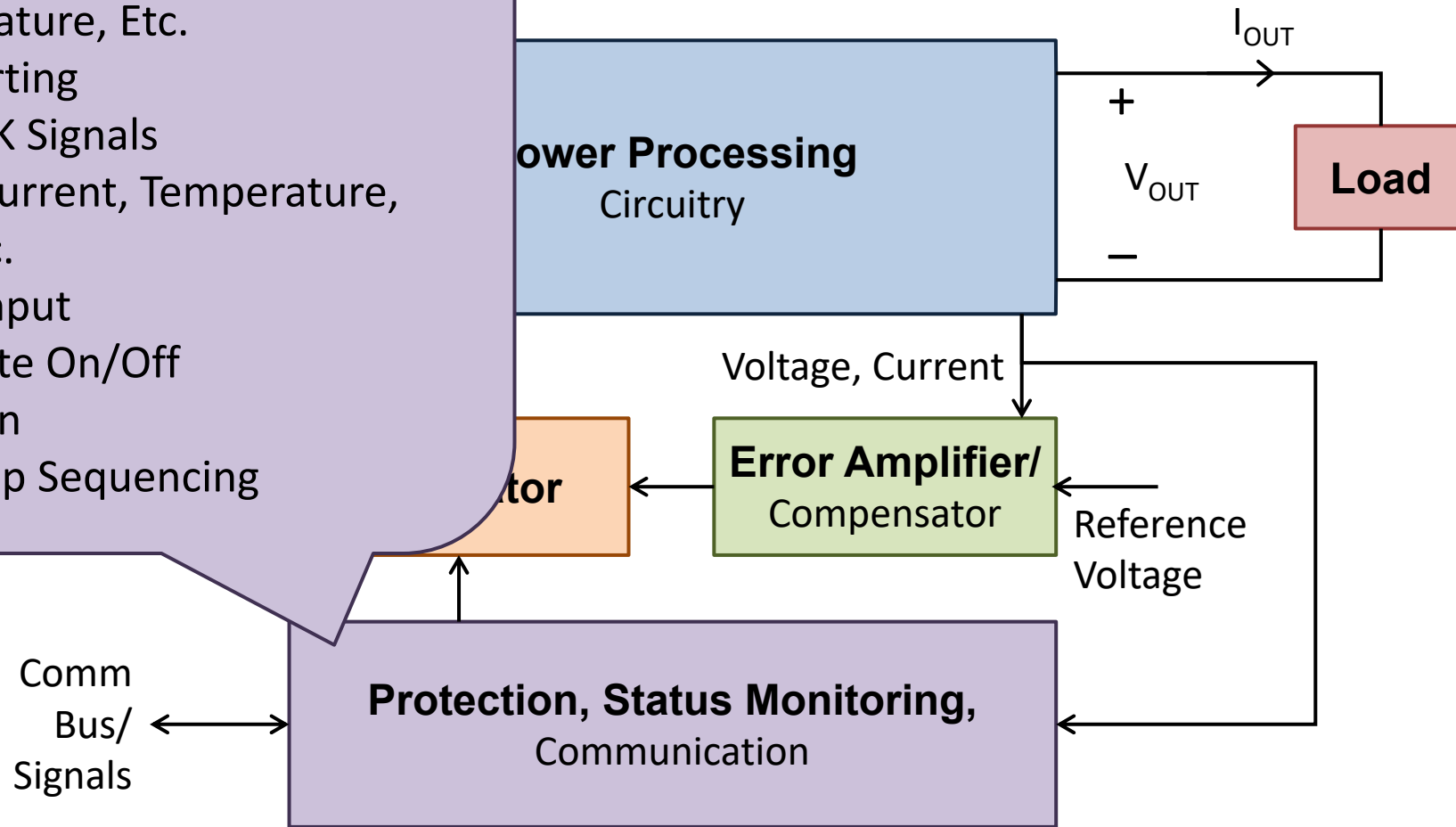
- Overcurrent, Overvoltage, Overtemperature, Etc.
- Status Reporting
 - OK/Not OK Signals
 - Voltage, Current, Temperature, Power, etc.
- Command Input
 - e.g. Remote On/Off
- Configuration
 - e.g. Startup Sequencing




Switch Mode Converter

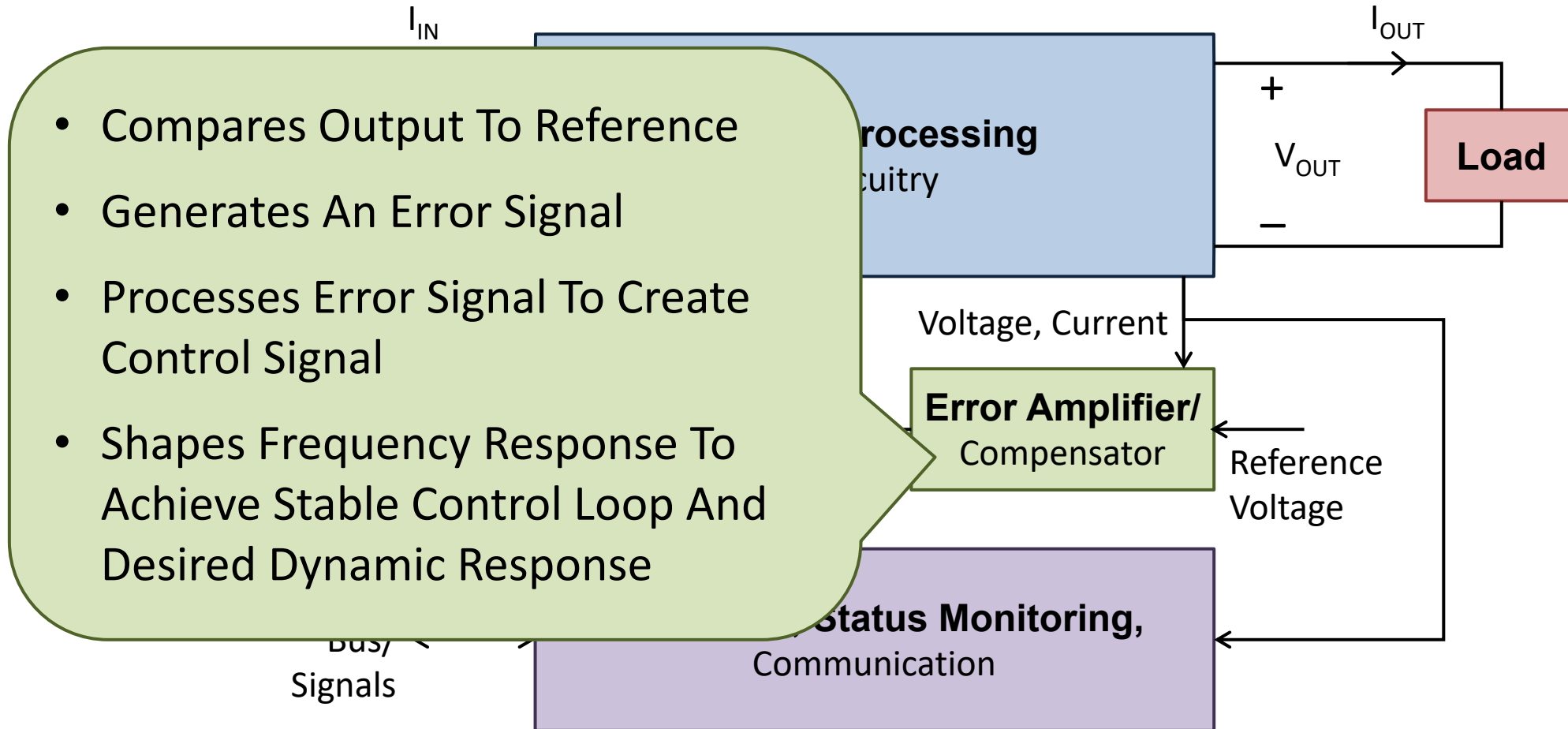

Switch Mode Converter

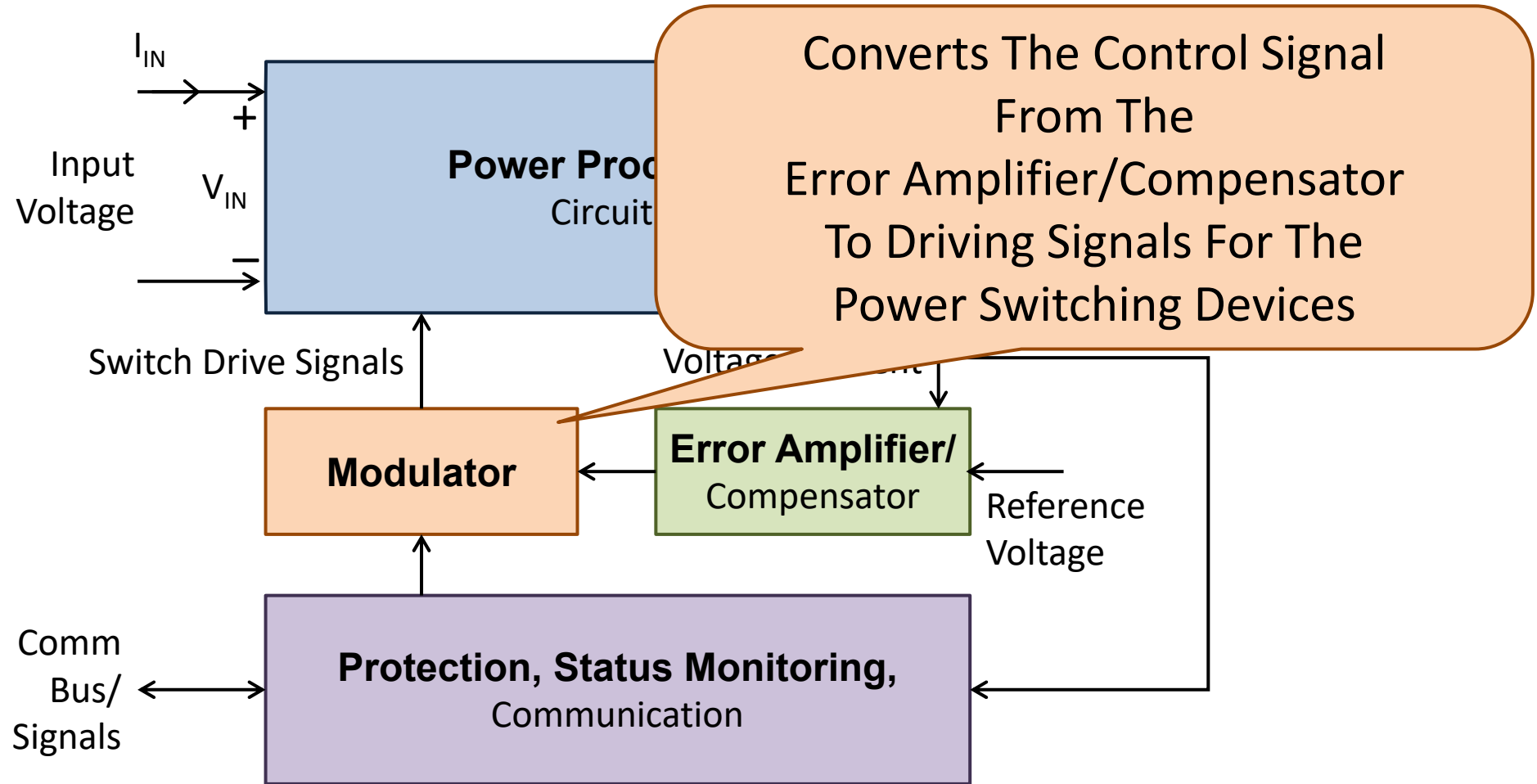


Switch Mode Converter

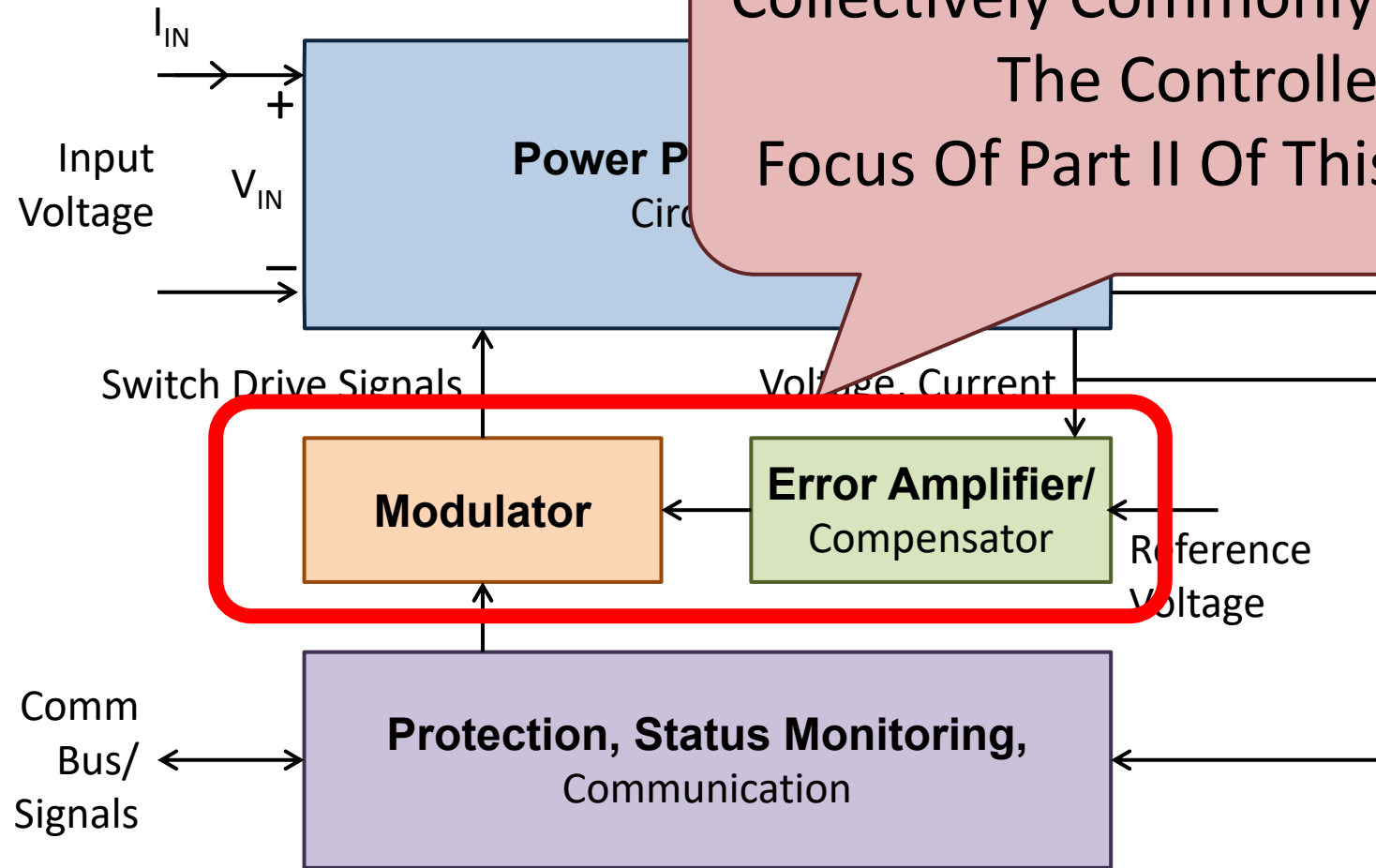


Collectively Commonly Known As
The Controller
Focus Of Part II Of This Seminar

Switch Mode Concepts


Switch Mode Concept

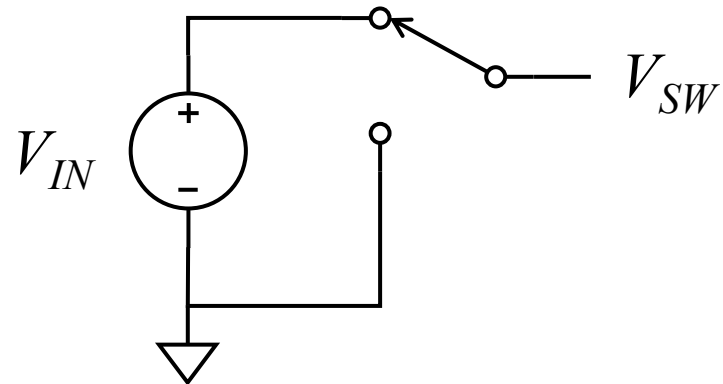

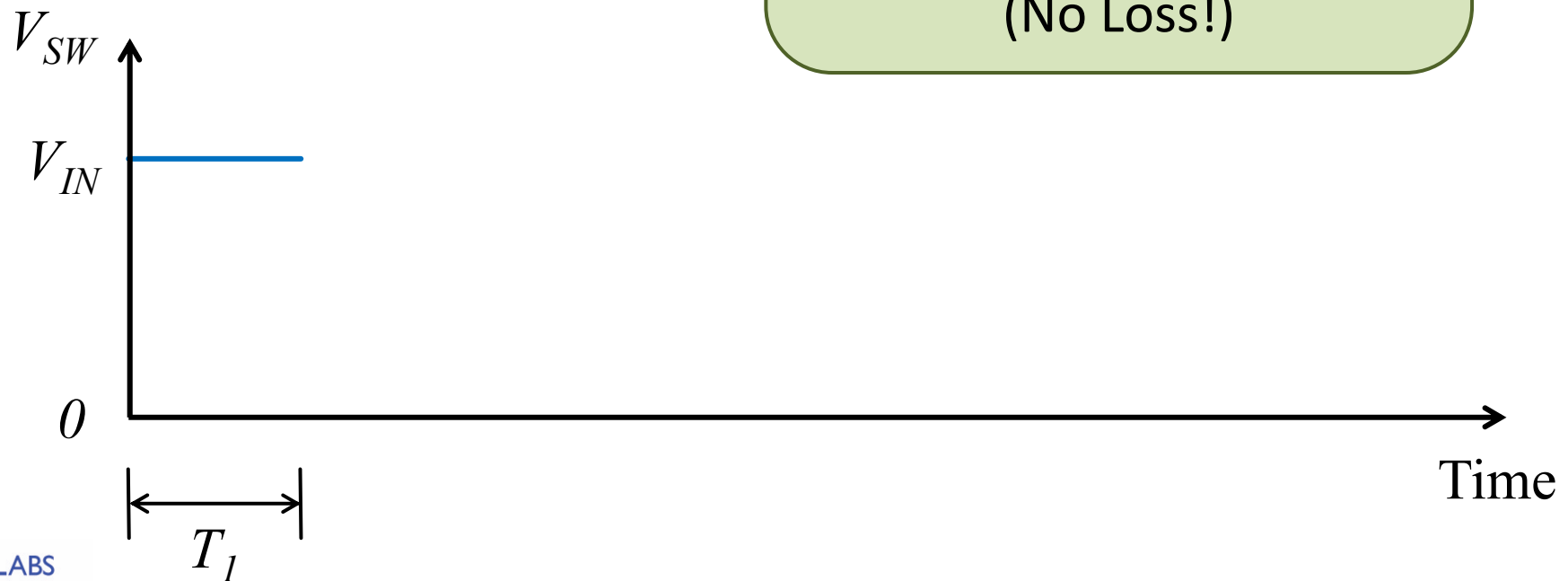
Delivering
Voltage And Power
From Input To Output
With 100% Efficiency
(No Loss!)





Switch Mode Concept

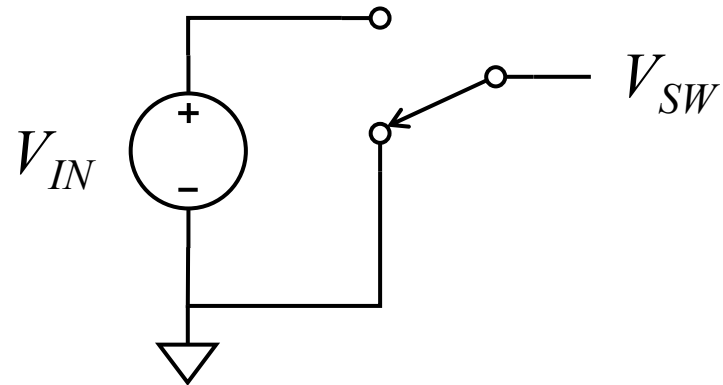


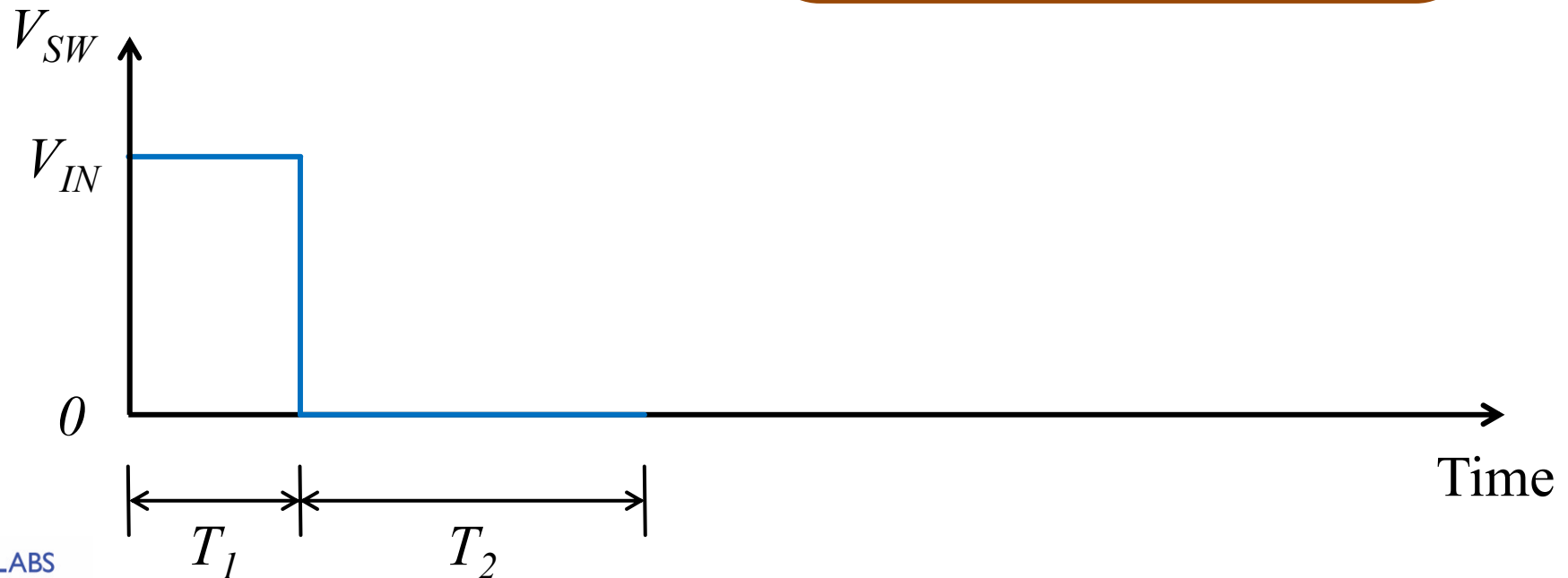
No Voltage Or Power
From Input To Output
But Also No Loss





Switch Mode Concept

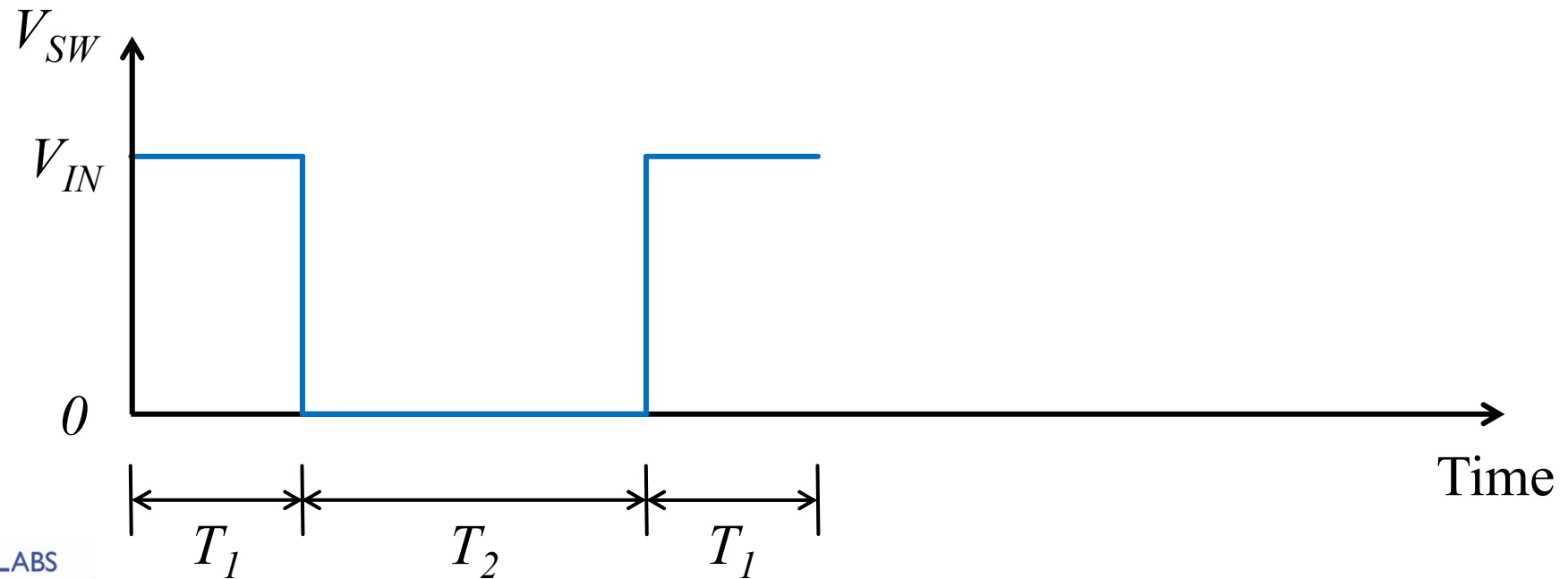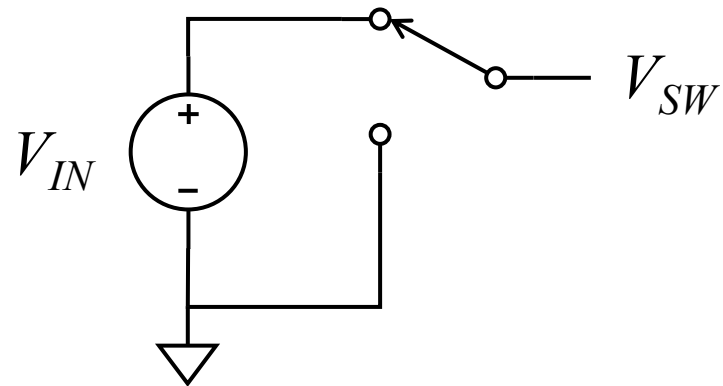

Switch Mode Concept

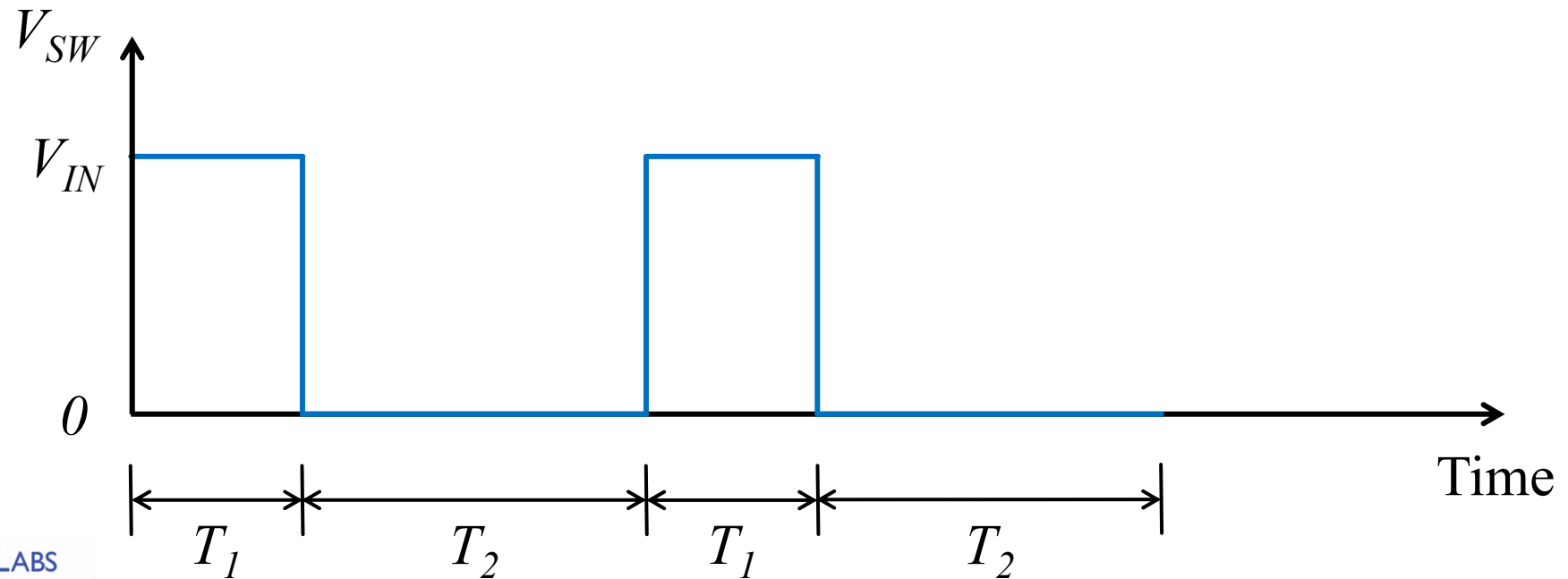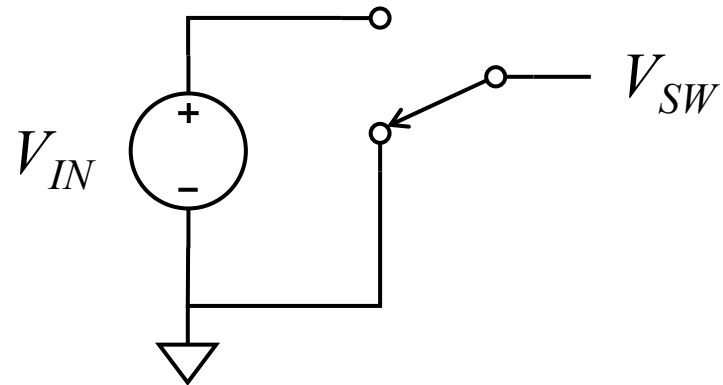


Switch Mode Concept

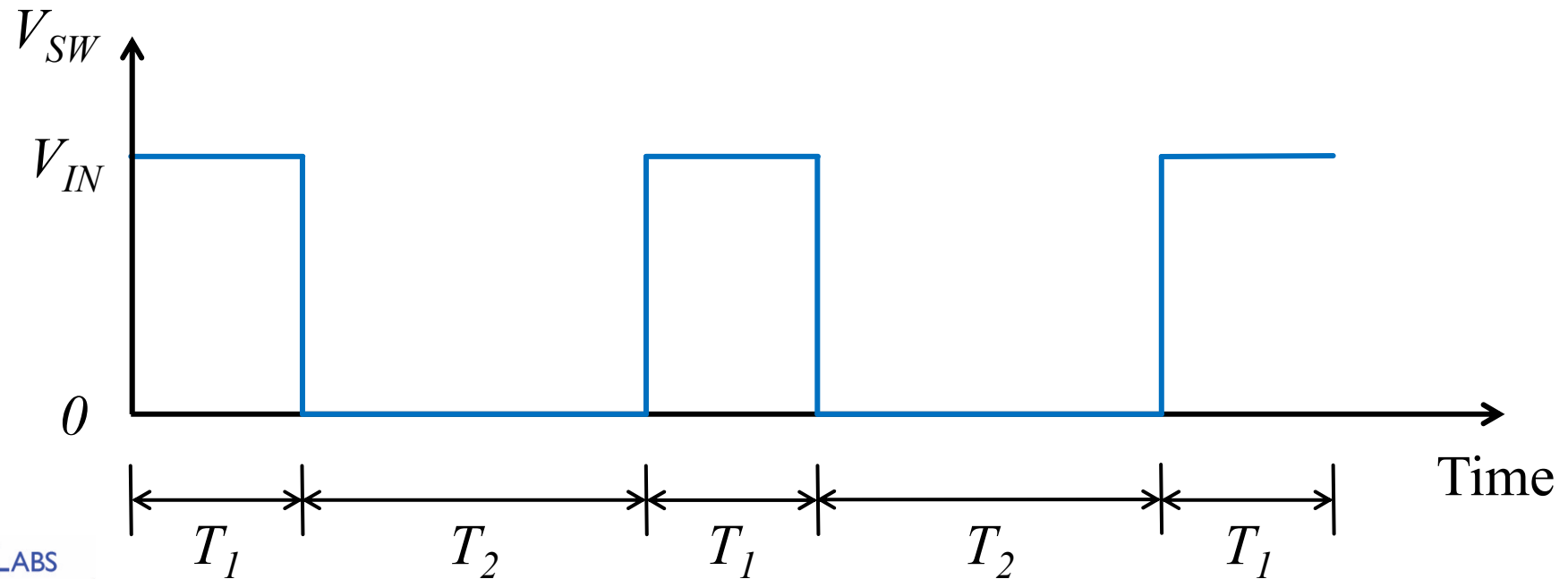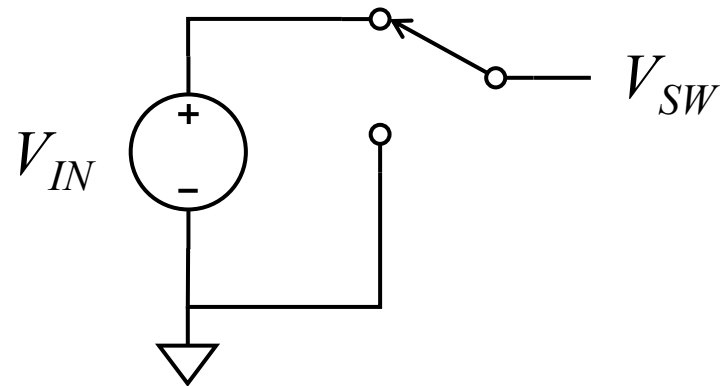

Terminology


Switching Period: $T_{SW} = T_{ON} + T_{OFF}$

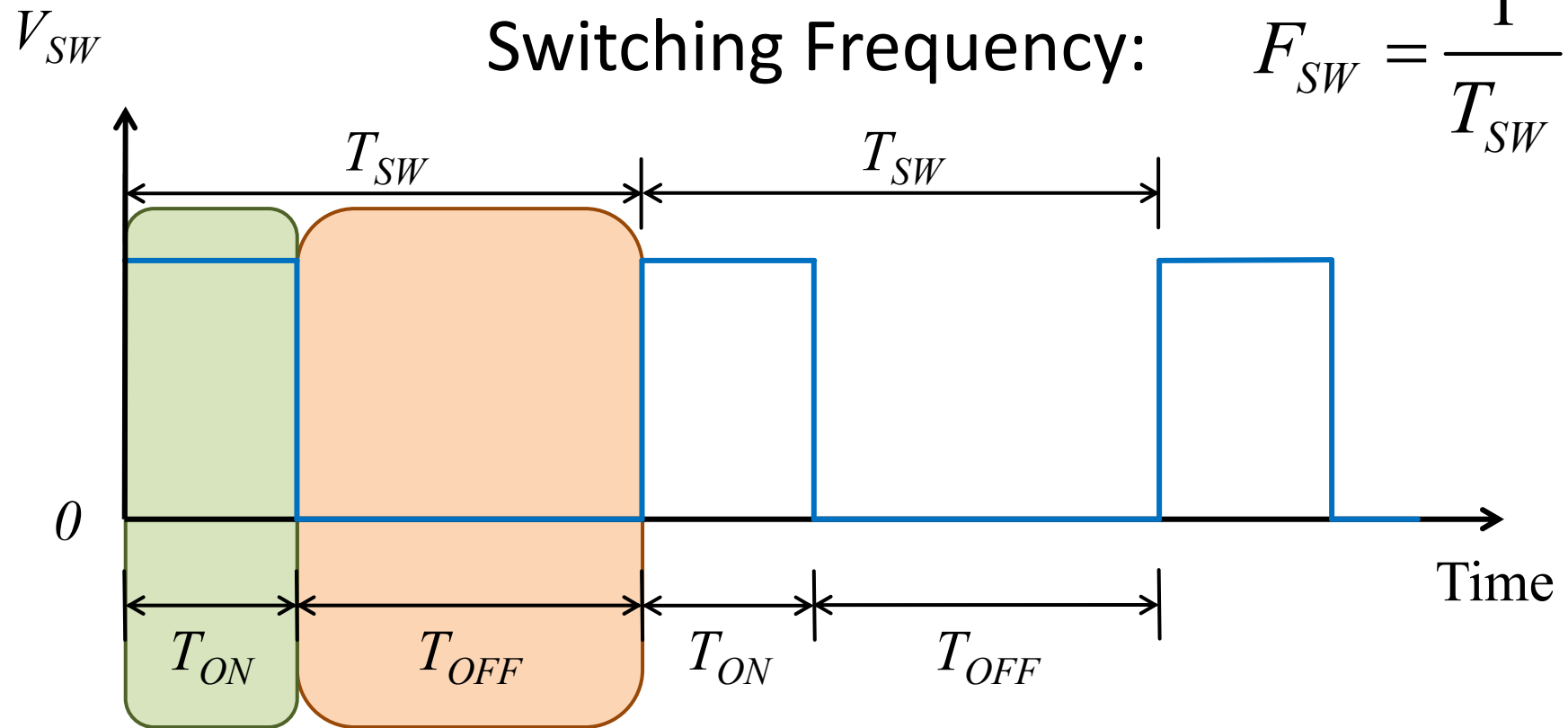Switching Frequency: $F_{SW} = \frac{1}{T_{SW}}$




Terminology

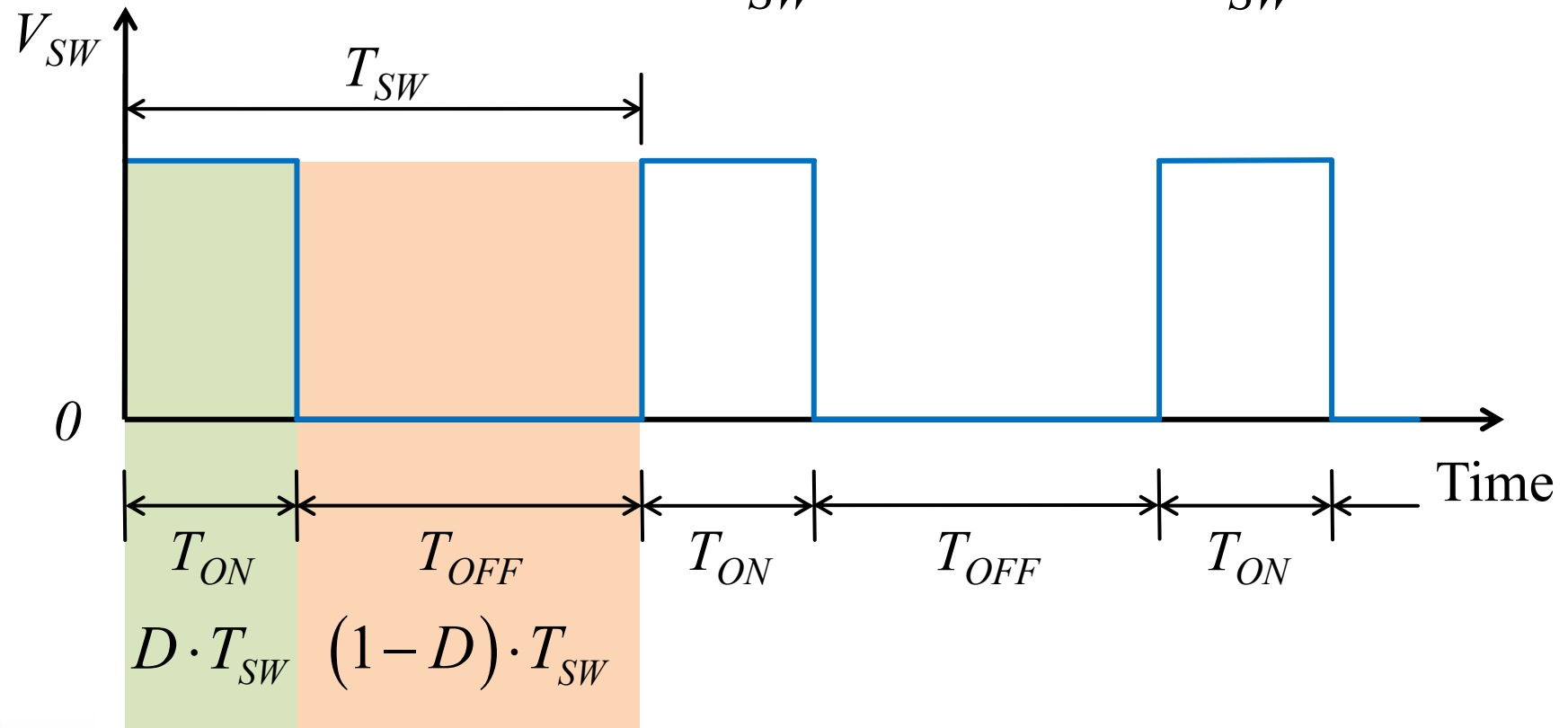Duty Cycle: $D = \frac{T_{ON}}{T_{SW}}$ $D' = \frac{T_{OFF}}{T_{SW}} = 1 - D$



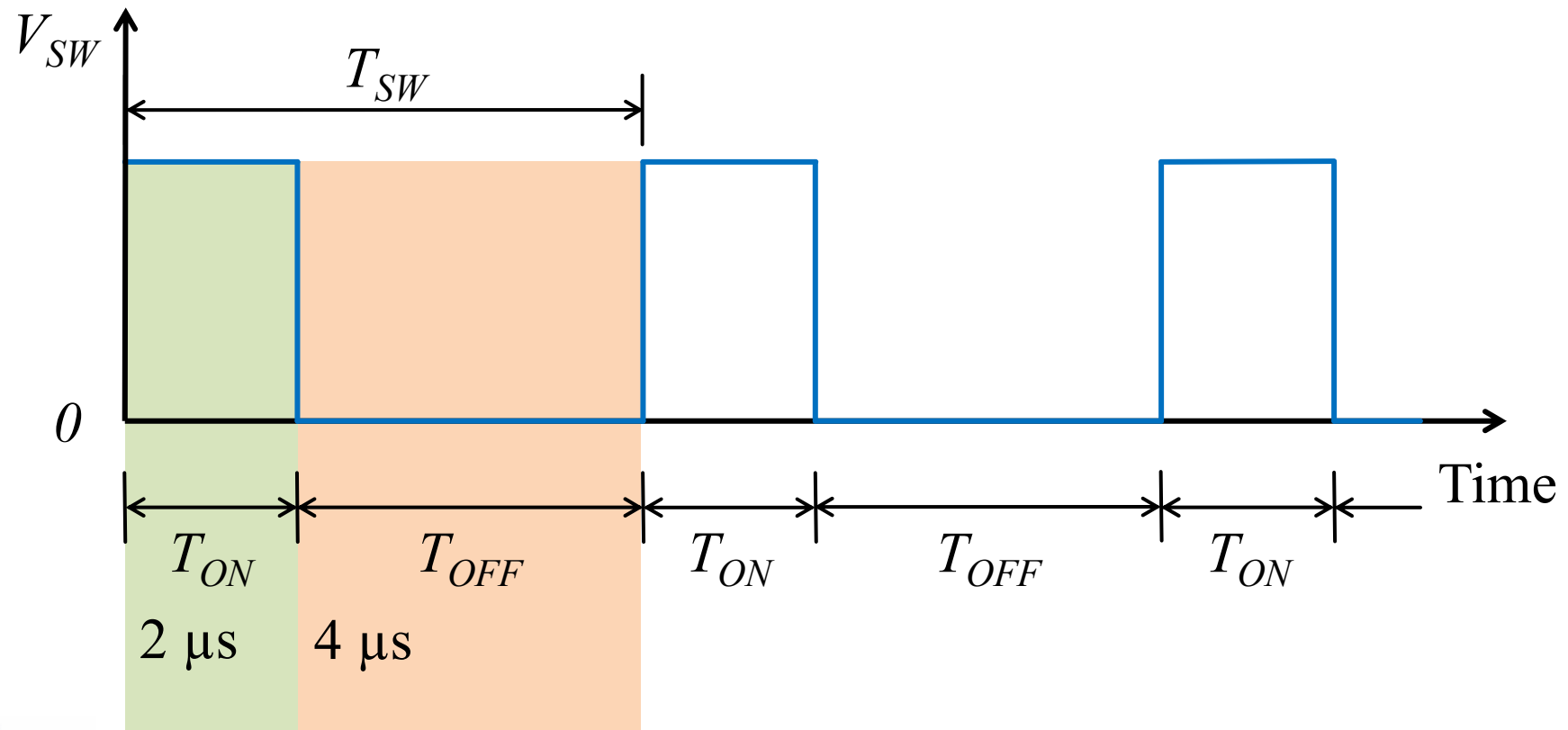Example


$$T_{SW} = T_{ON} + T_{OFF} = 2 \mu\text{s} + 4 \mu\text{s} = 6 \mu\text{s}$$
$$F_{SW} = \frac{1}{T_{SW}} = \frac{1}{6 \mu\text{s}} = 166.7 \text{ kHz}$$




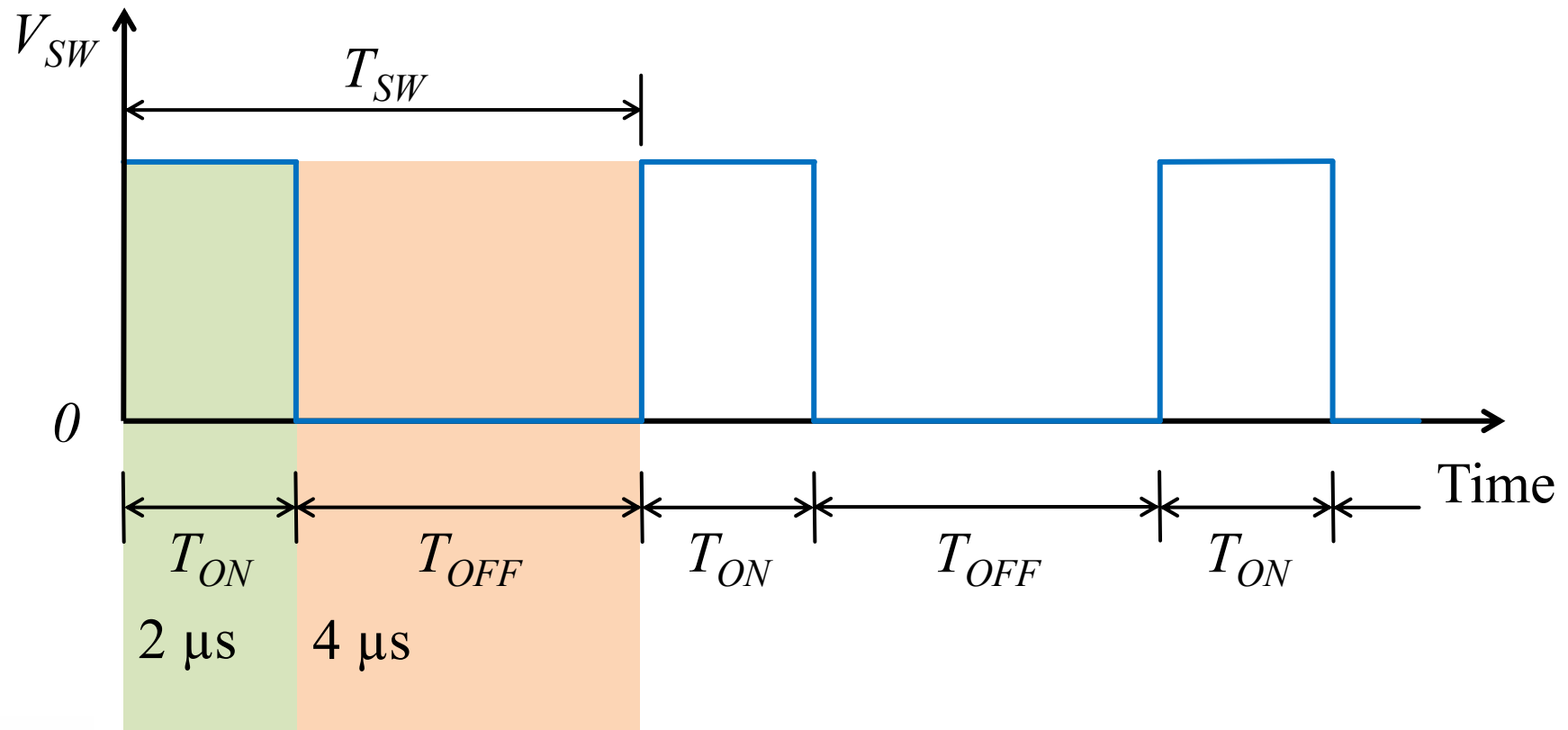
Example

$$D = \frac{T_{ON}}{T_{SW}} = \frac{2 \mu s}{6 \mu s} = \frac{1}{3} = 0.333$$


$$D' = \frac{T_{OFF}}{T_{SW}} = \frac{4 \mu s}{6 \mu s} = \frac{2}{3} = 0.667$$




Switch Mode Concept

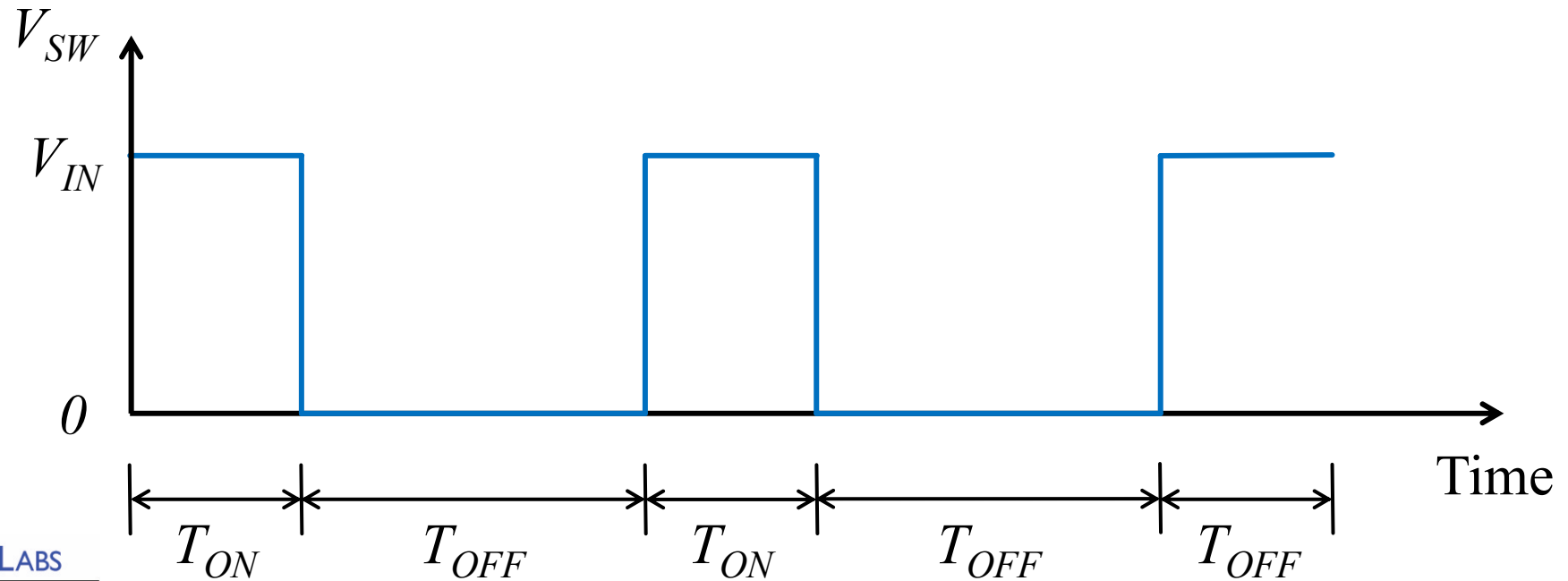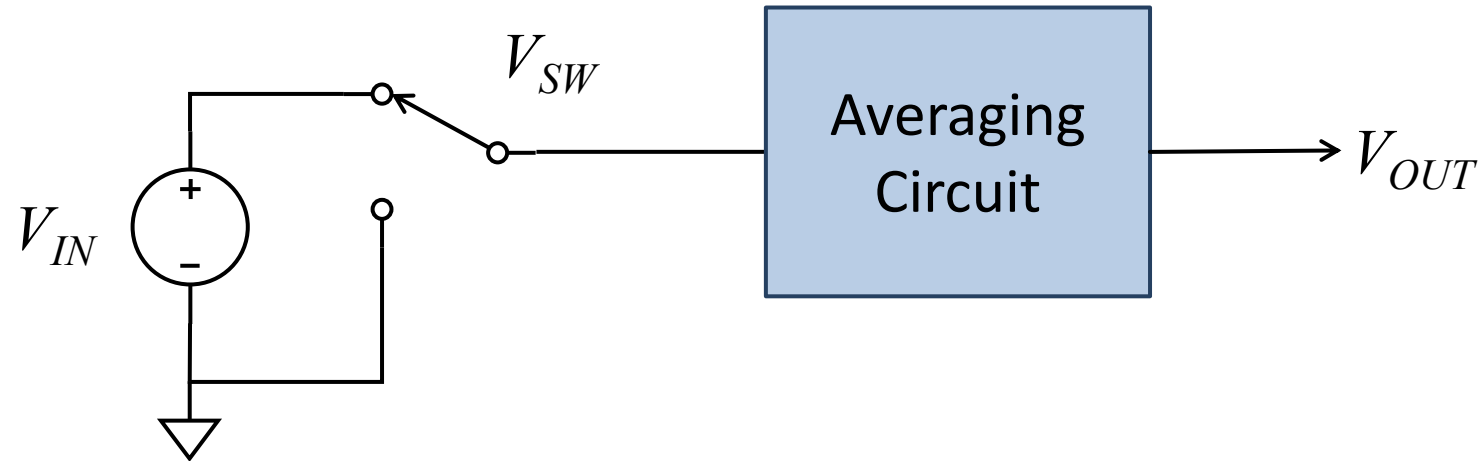


Switch Mode Concept

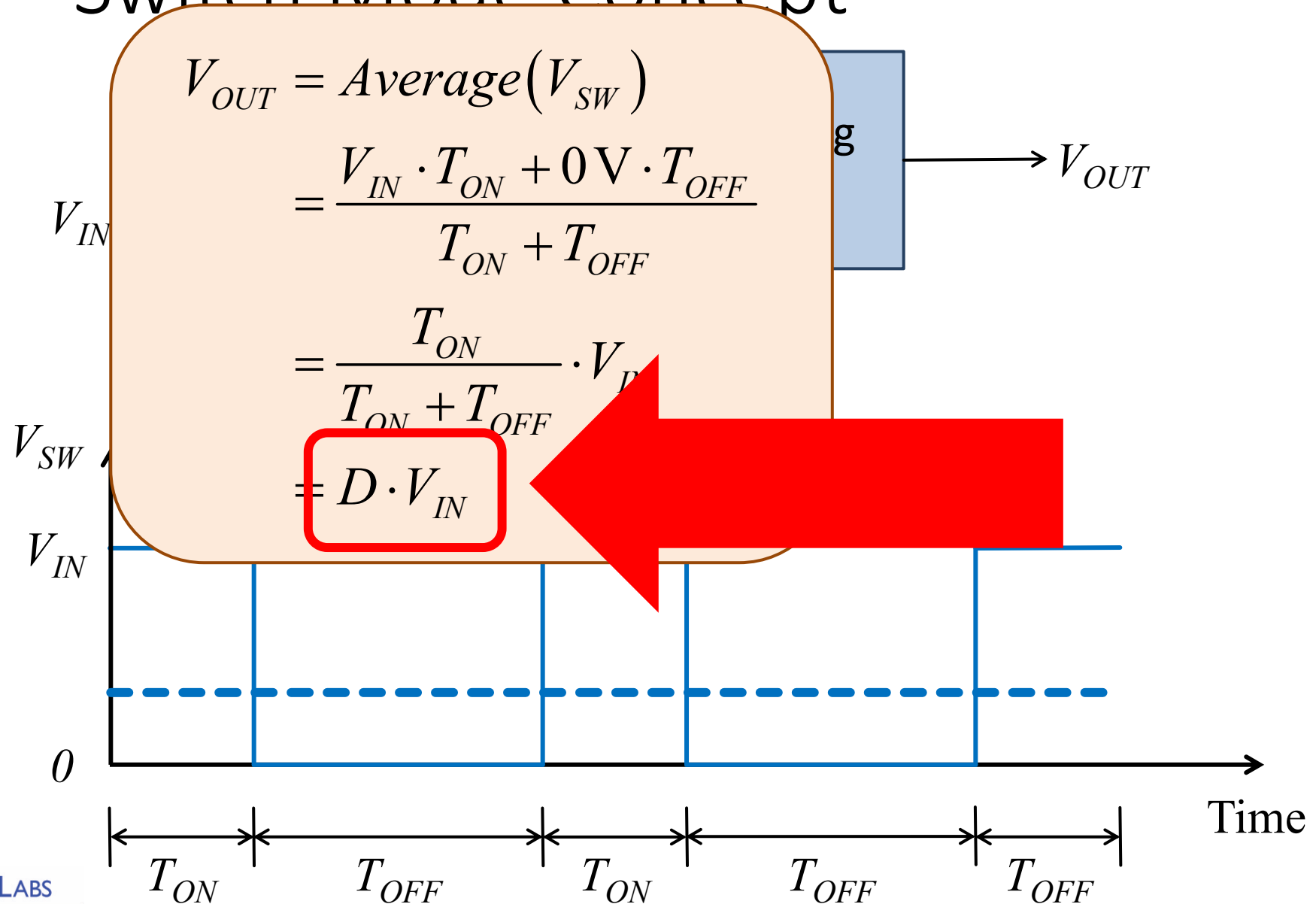

Example

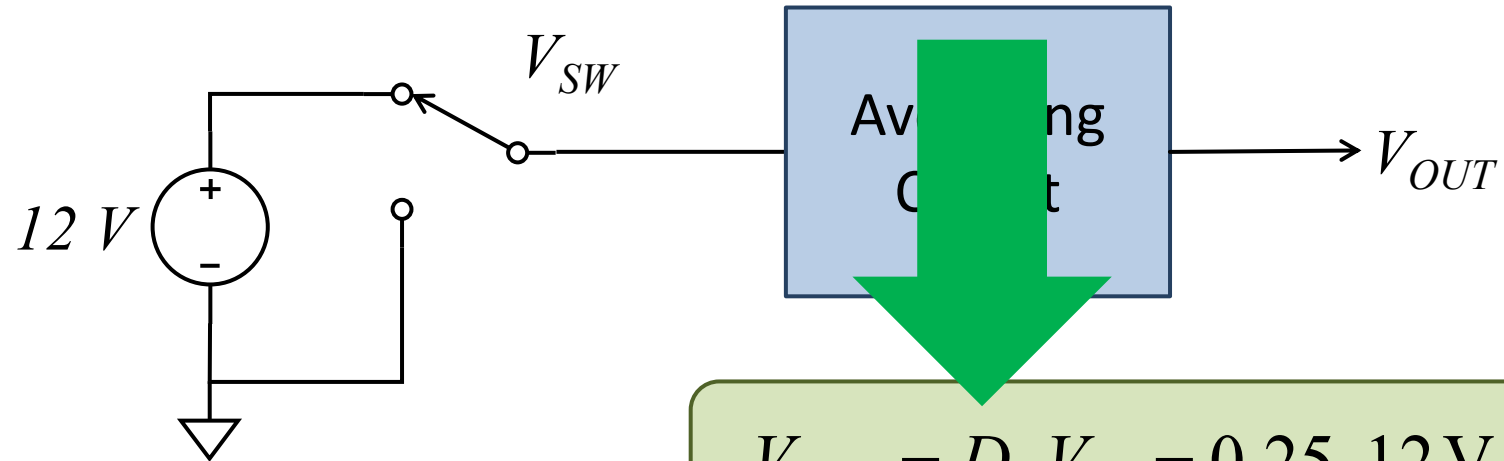

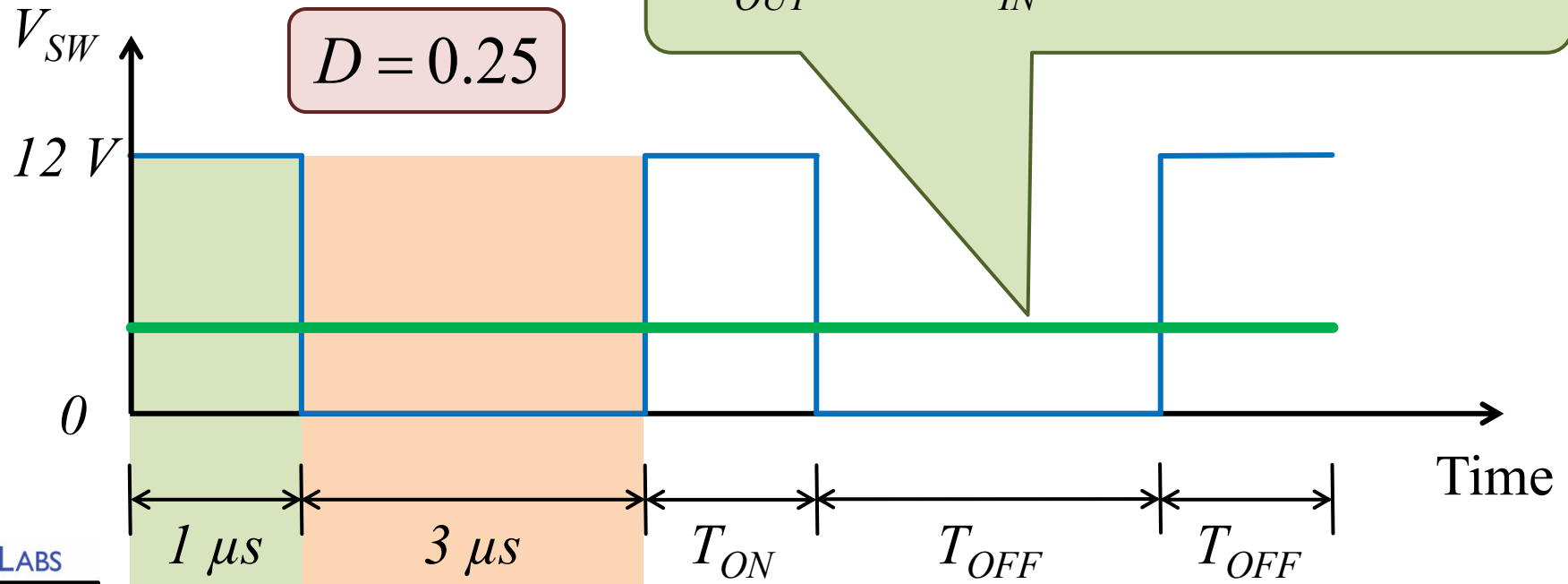$V_{OUT} = D \cdot V_{IN} = 0.25 \cdot 12V = 3V$




Energy Storage Requirement

This Averaging Circuit Must Be Able To Store And Release Energy

During The Off Time The Averaging Circuit Is Delivering Energy To The Load

But No Energy Is Available At The Averaging Circuit Input!



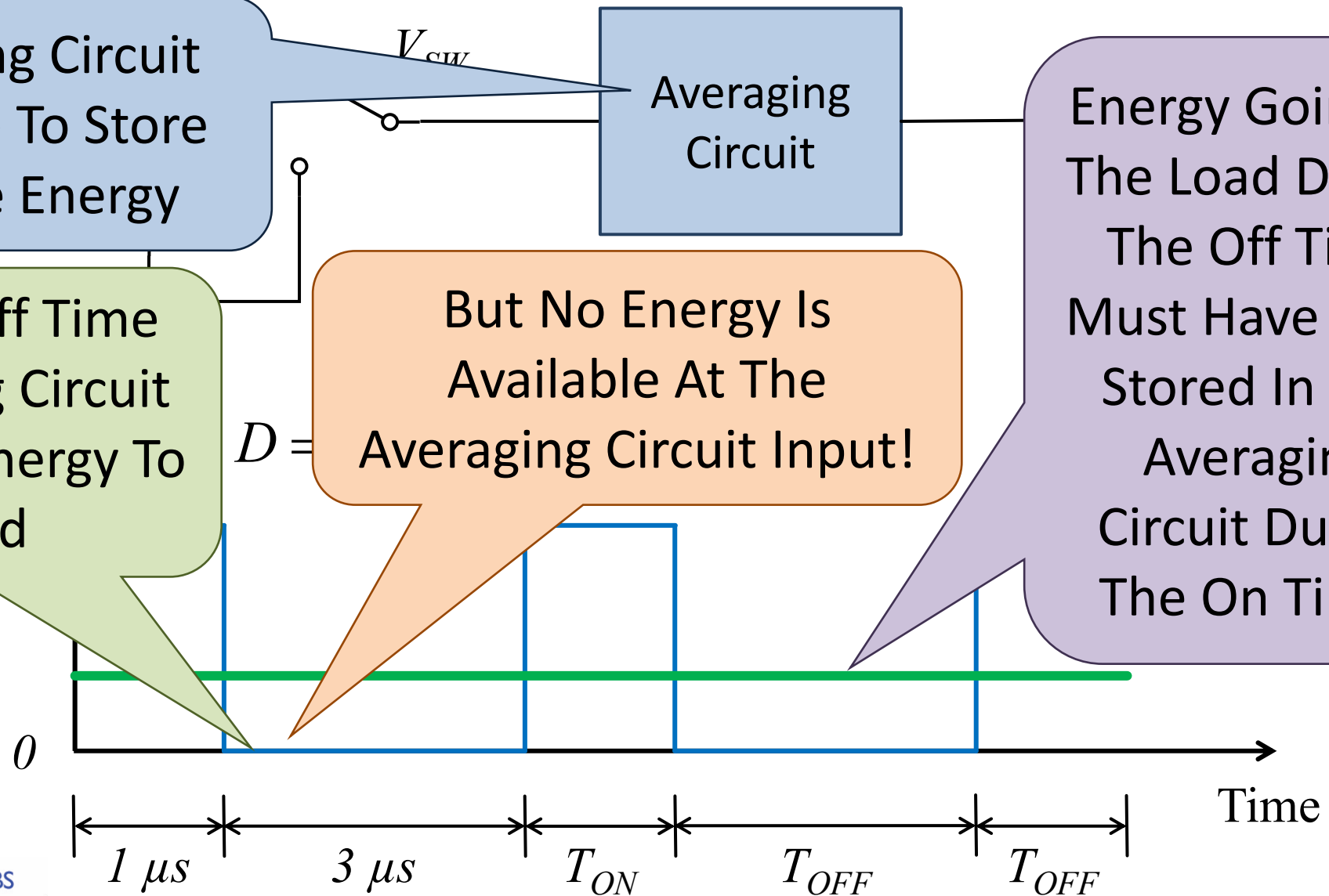
Energy Going To The Load During The Off Time Must Have Been Stored In The Averaging Circuit During The On Time!




Power Conversion Components

Building Blocks


- Switches To Control The Flow Of Energy

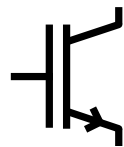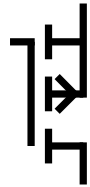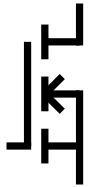


- Containers To Store Energy

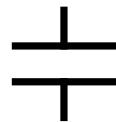


- Transformers

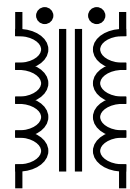


Energy Storage: Capacitor

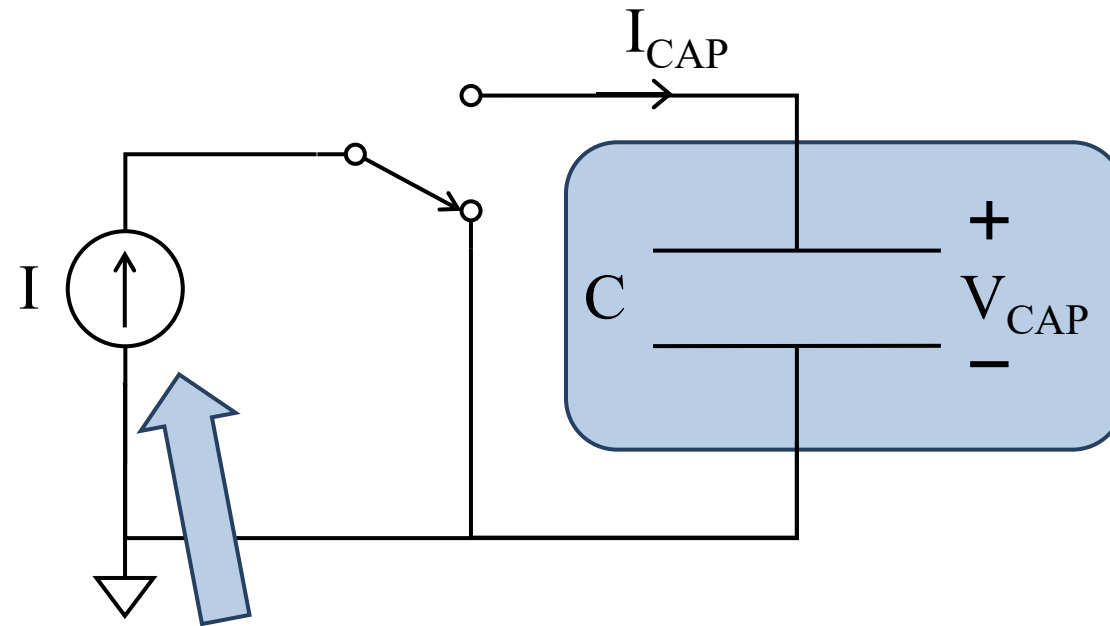



Energy Storage: Capacitor

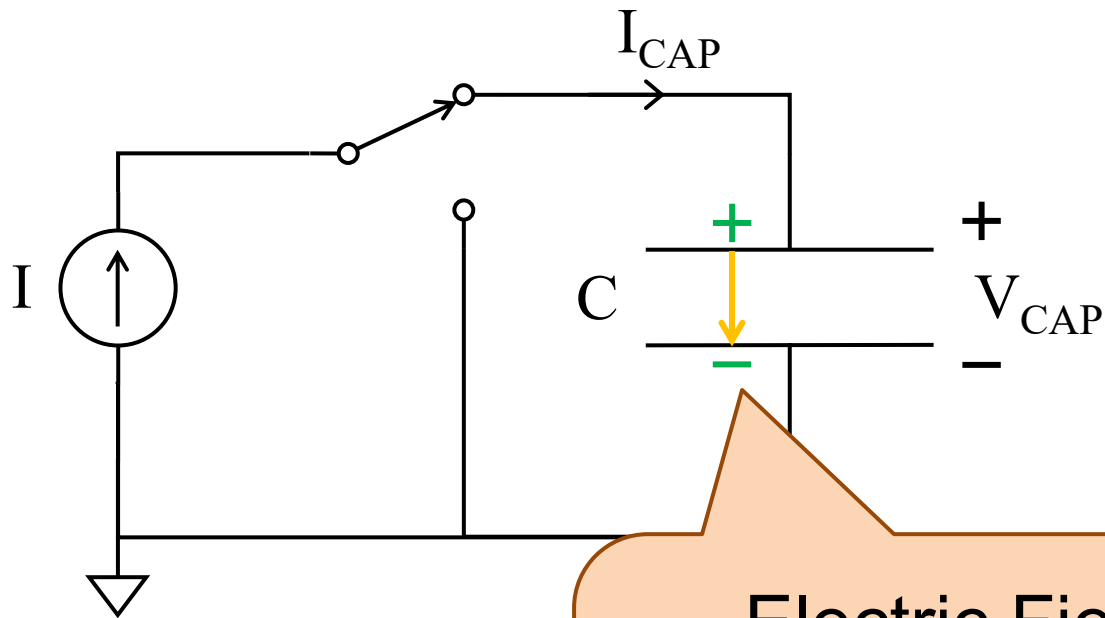


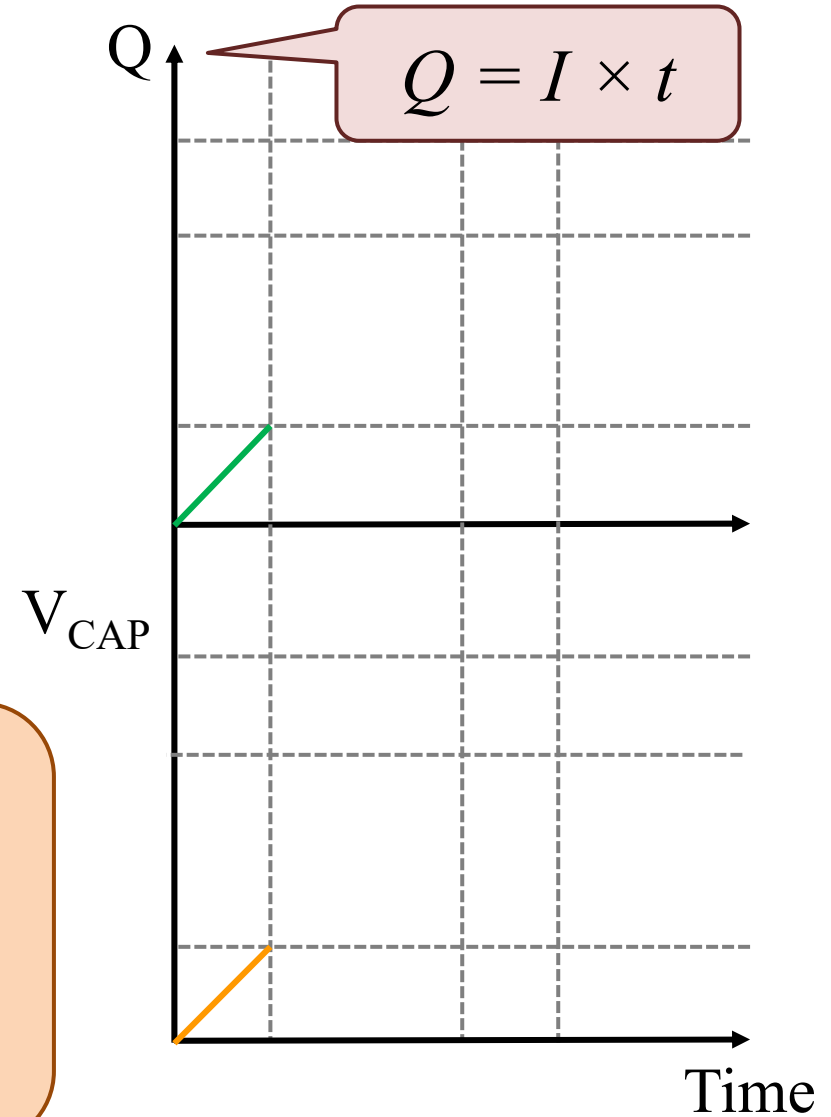
Electric Field Develops From Positive Charge To Negative Charge



Energy Storage: Capacitor

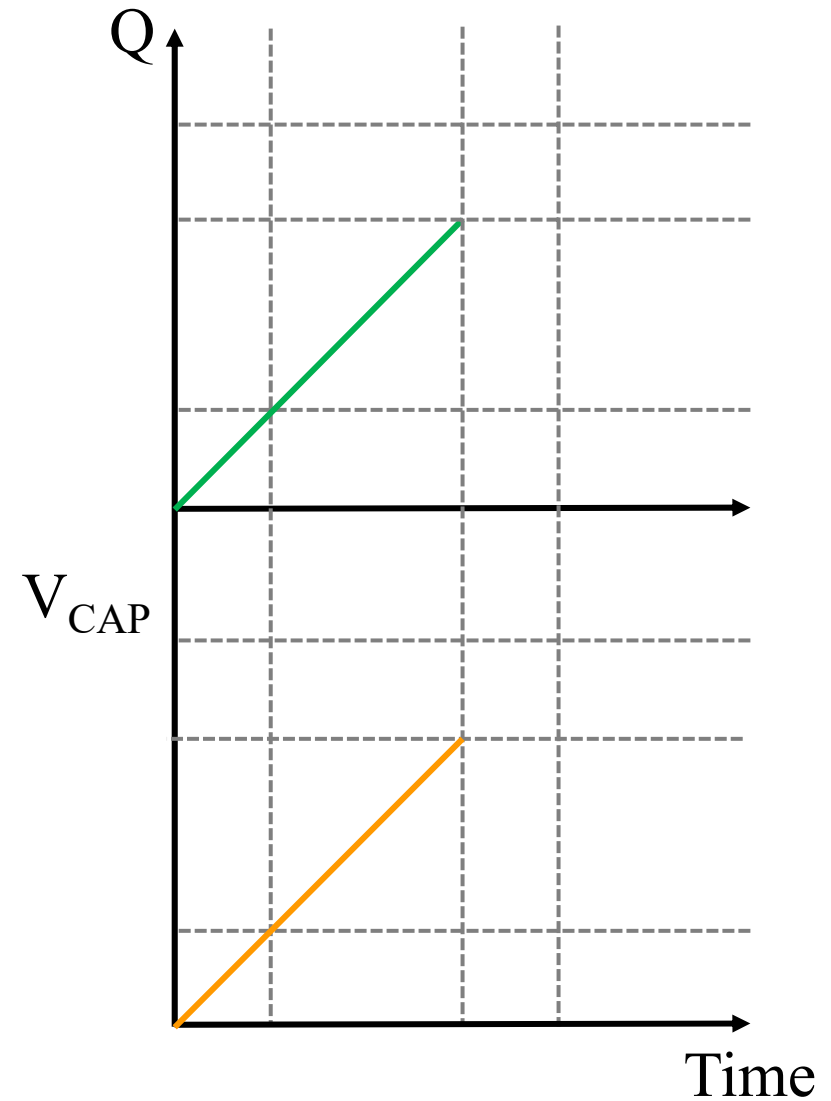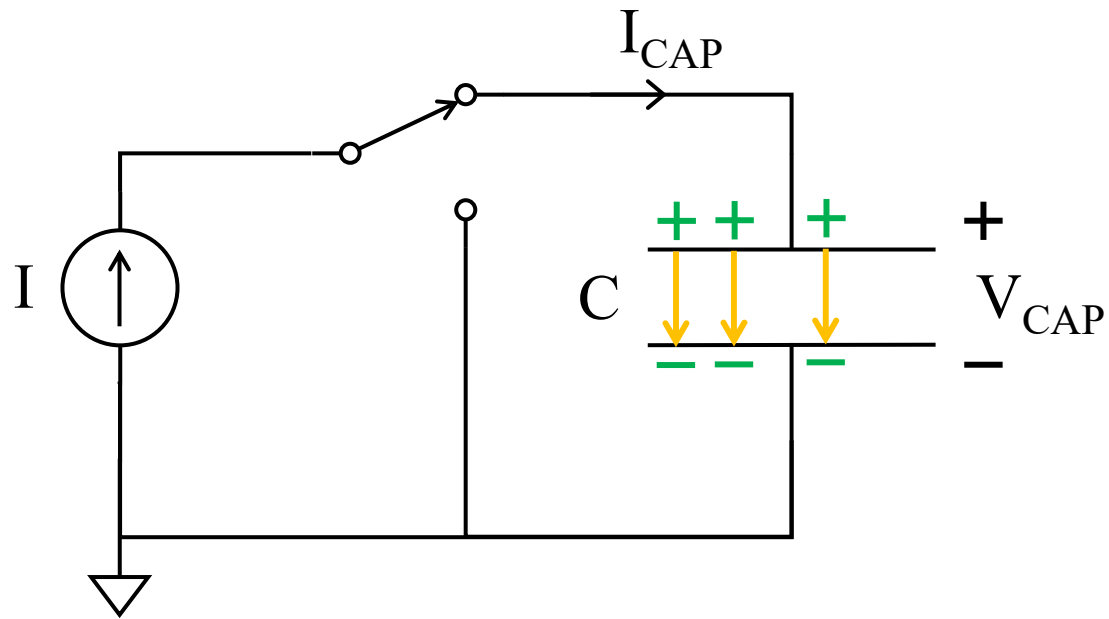

Energy Storage: Capacitor

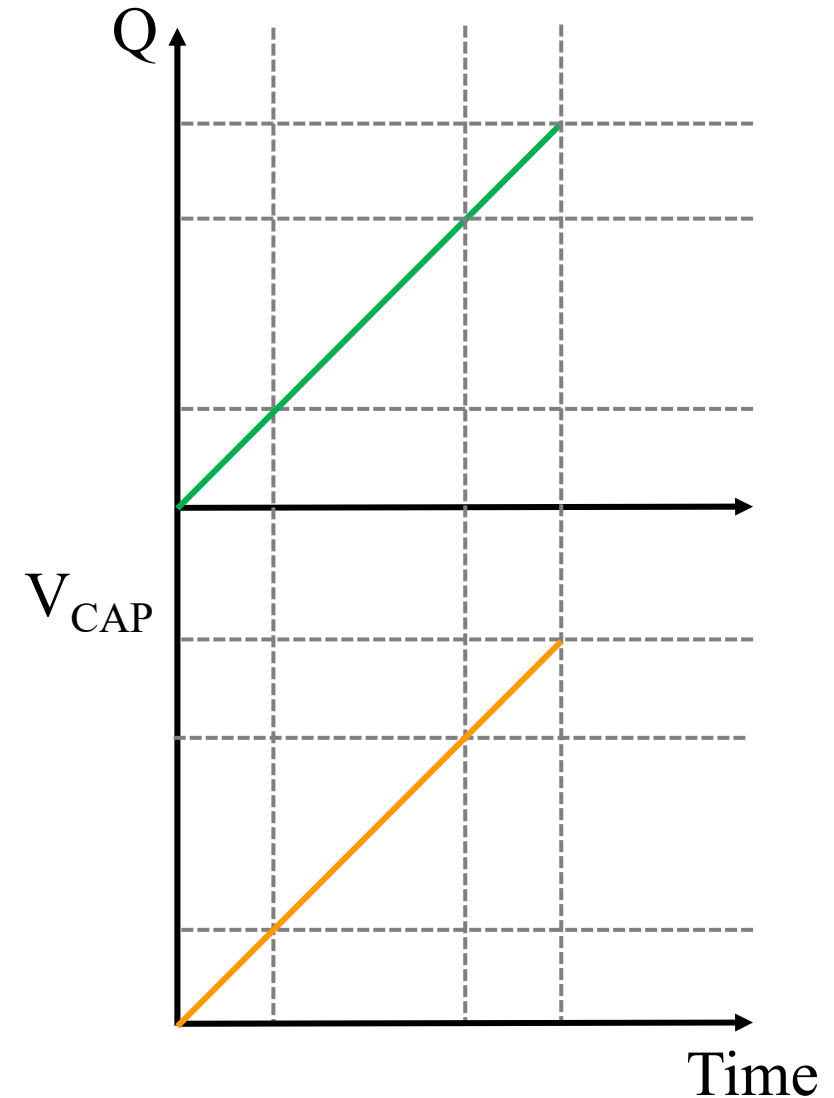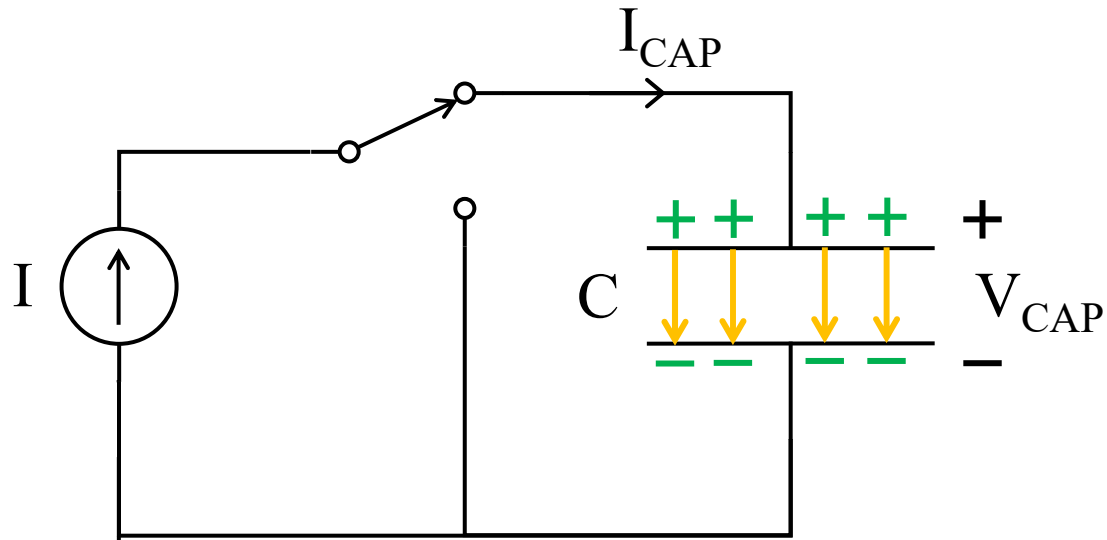


$$Q = C \cdot V$$

$$E = \frac{1}{2} \cdot C \cdot V$$


$$I = \frac{dQ}{dt} = \frac{d(C \cdot V)}{dt} = C \cdot \frac{dV}{dt}$$

Energy Storage: Capacitor

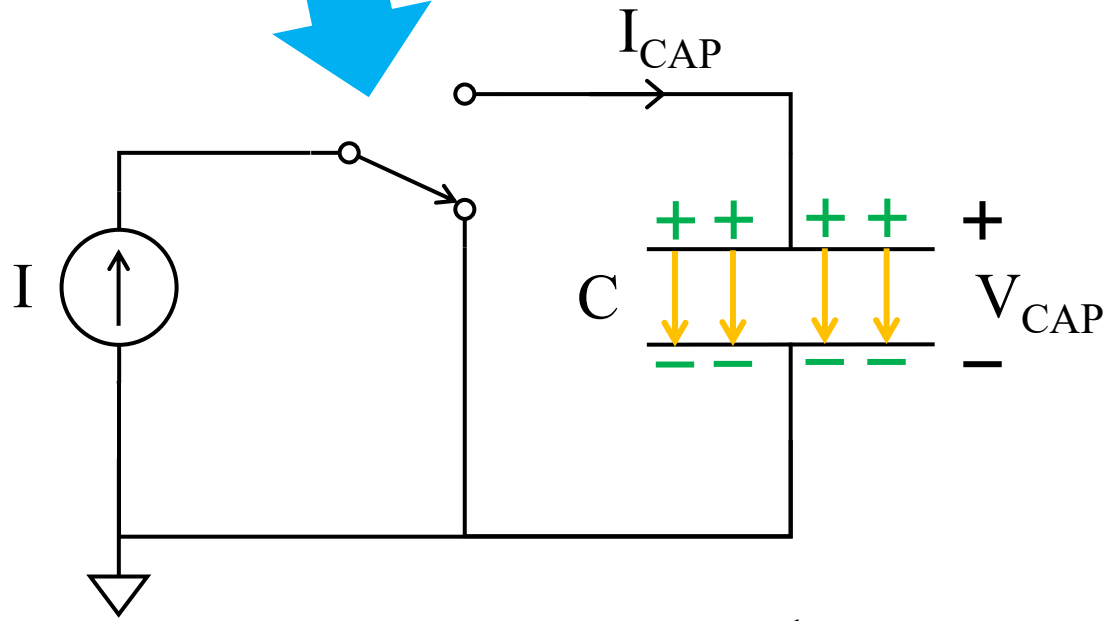


$$Q = C \cdot V \quad E = \frac{1}{2} \cdot C \cdot V^2$$

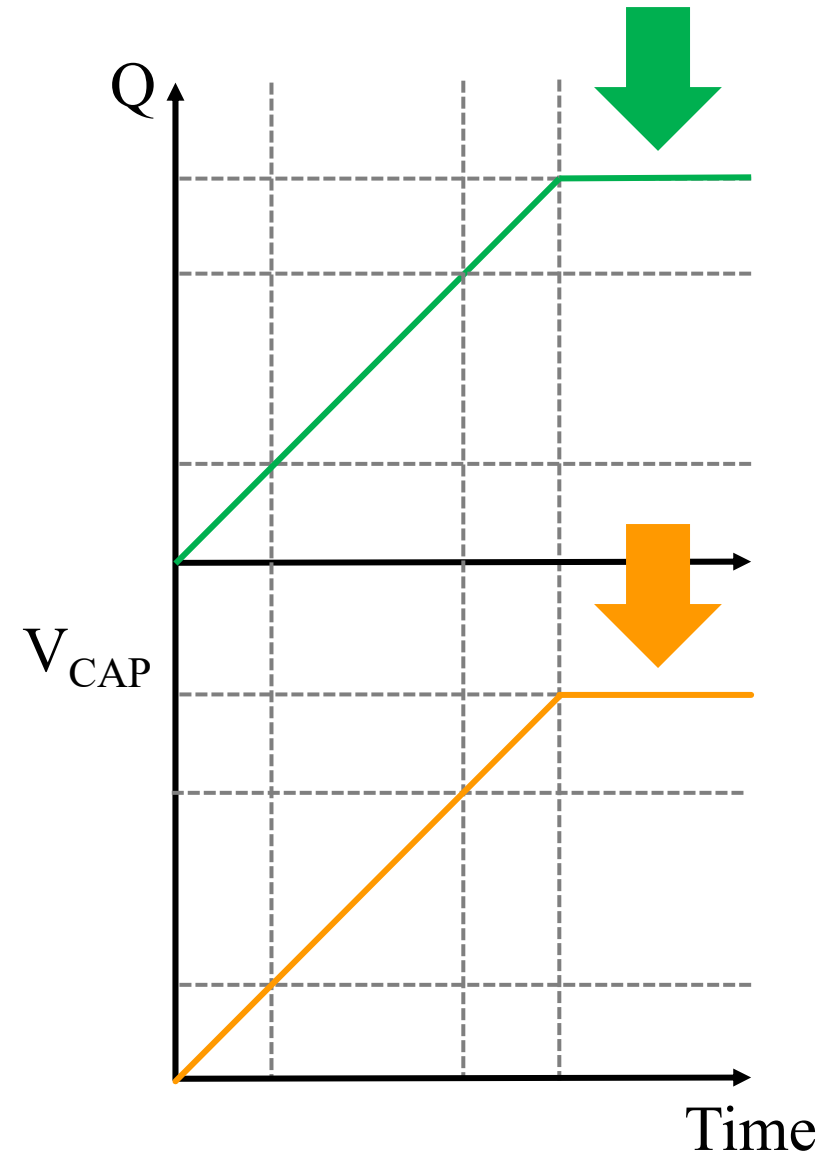
$$I = \frac{dQ}{dt} = \frac{d(C \cdot V)}{dt} = C \cdot \frac{dV}{dt}$$




Energy Storage: Inductor

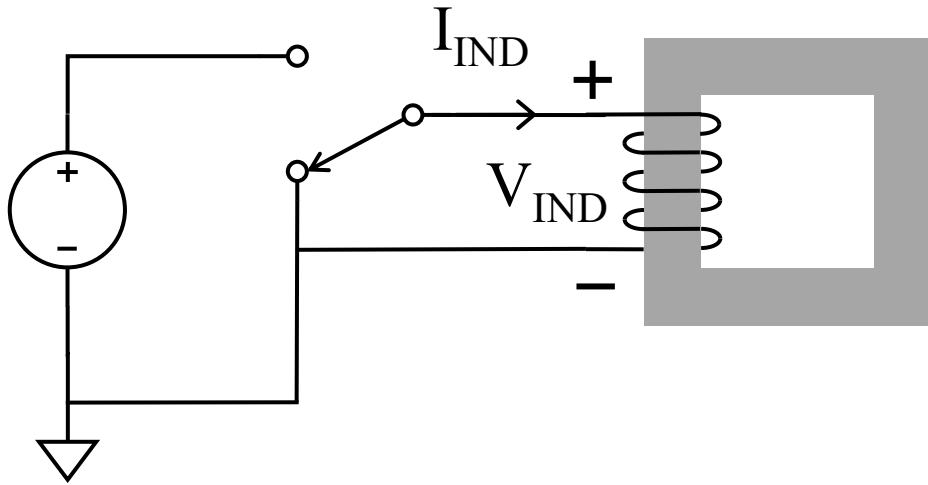



Energy Storage: Inductor

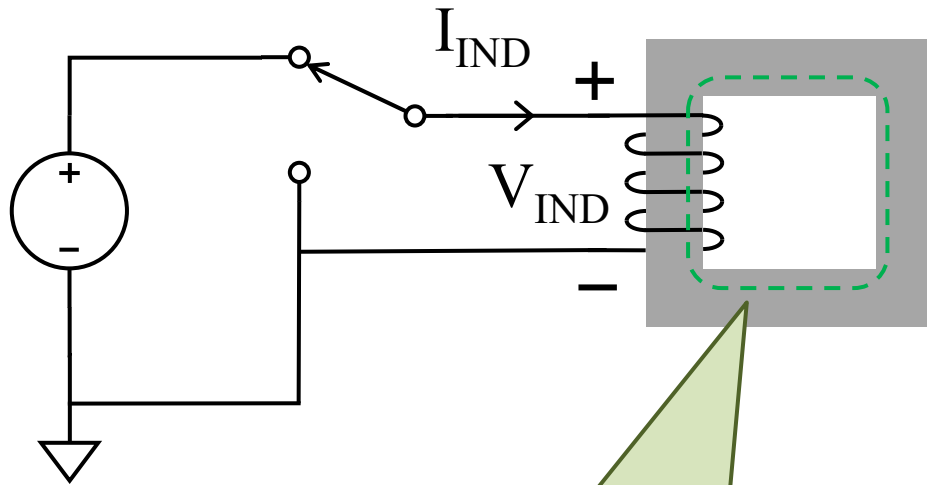


Magnetic Field
Develops In
The Core

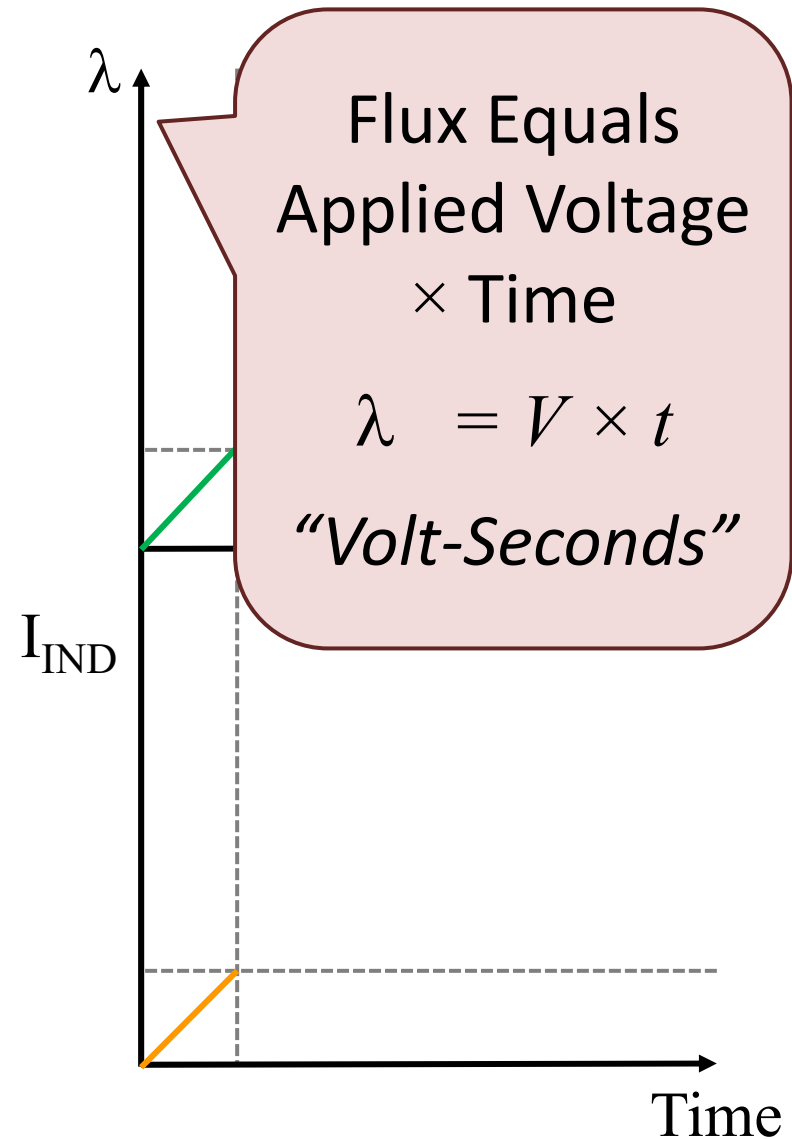

Energy Storage: Inductor

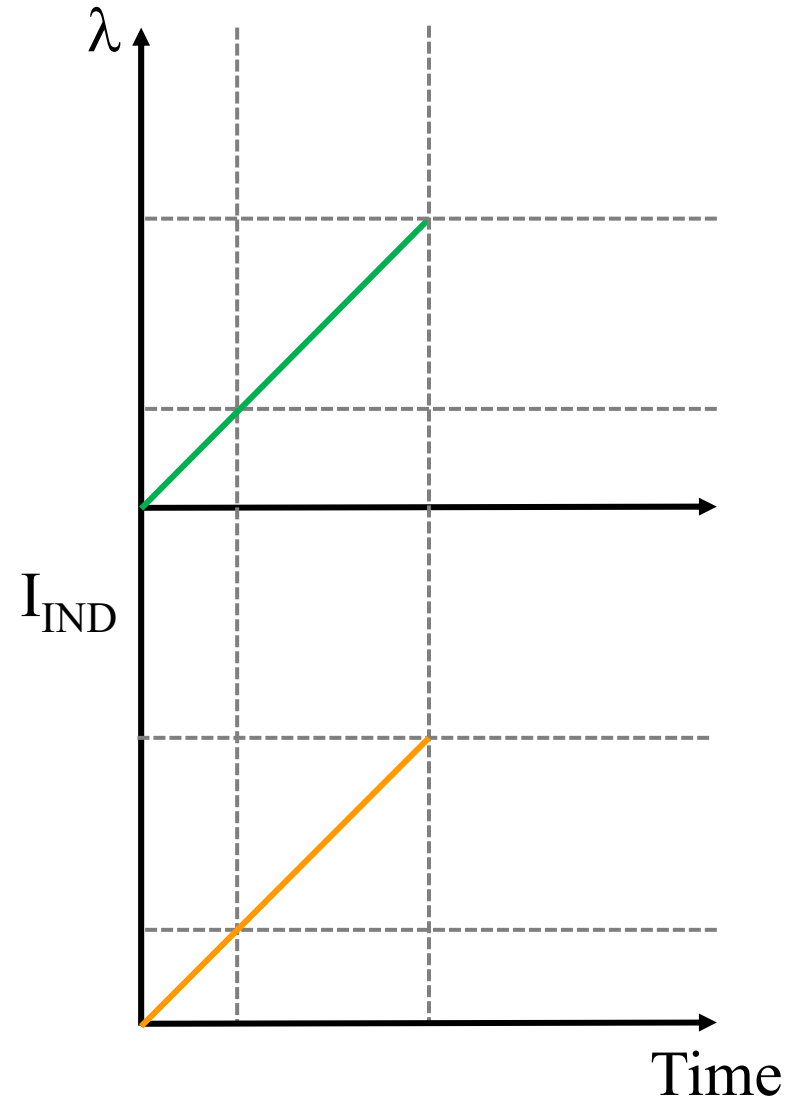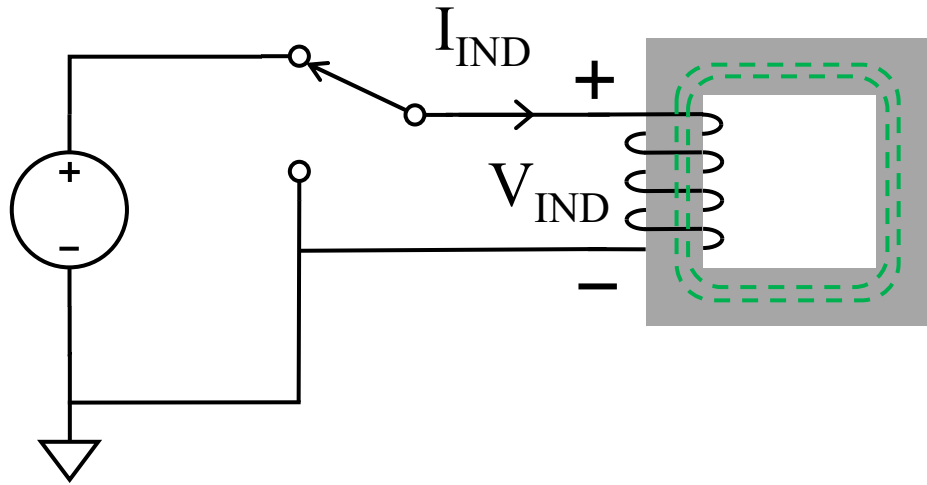


Energy Storage: Inductor

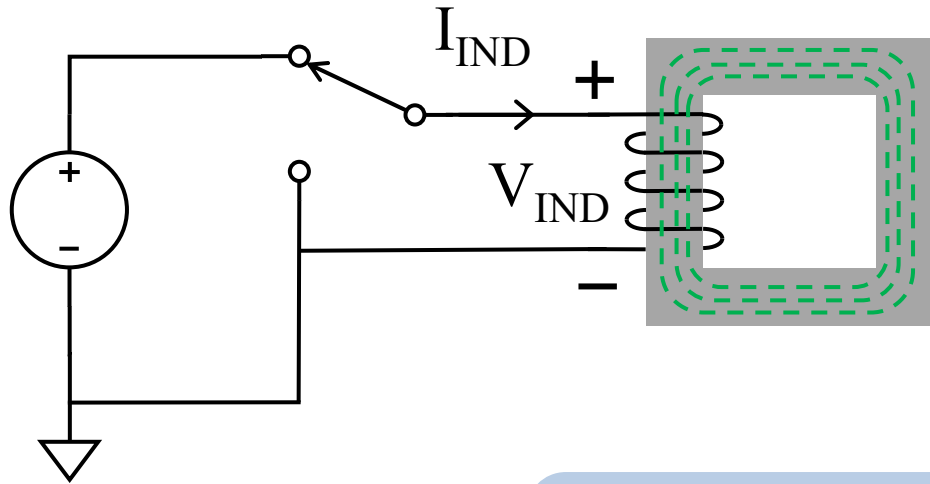


$$\lambda = L \cdot I$$

$$E = \frac{1}{2} \cdot L \cdot I^2$$
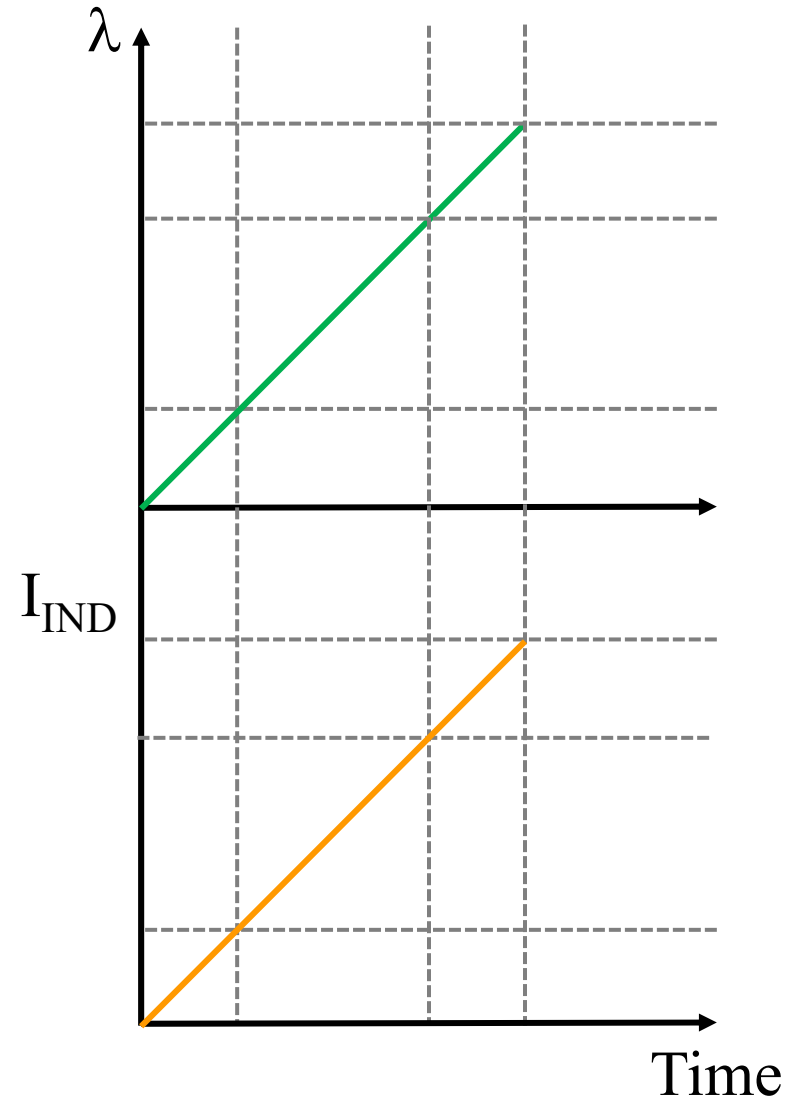
$$V = \frac{d\lambda}{dt} = \frac{d(L \cdot I)}{dt} = L \cdot \frac{dI}{dt}$$




Energy Storage: Inductor

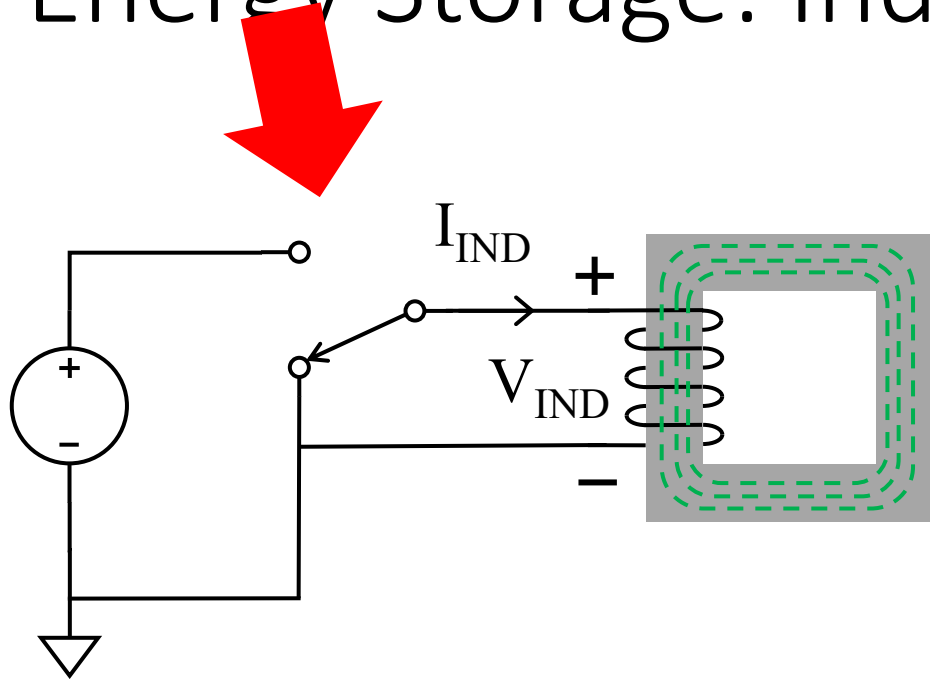


$$\lambda = L \cdot I \quad E = \frac{1}{2} \cdot L \cdot I^2$$
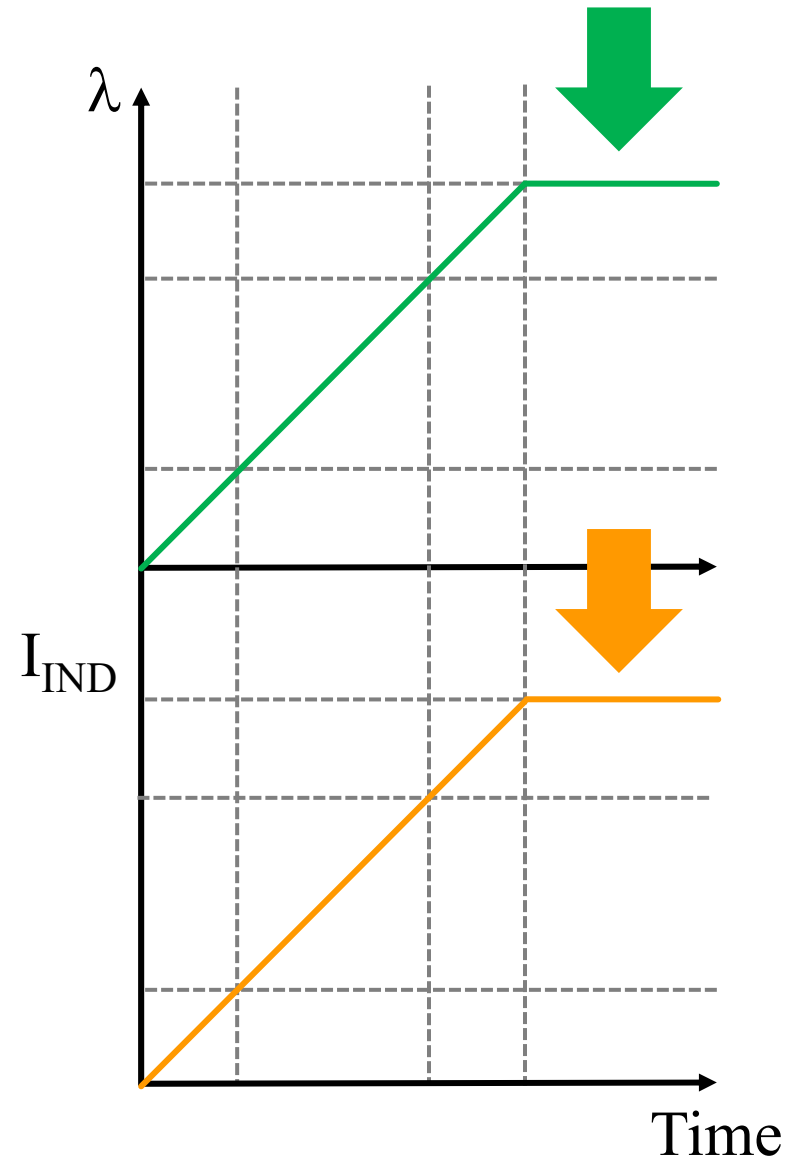
$$V = \frac{d\lambda}{dt} = \frac{d(L \cdot I)}{dt} = L \cdot \frac{dI}{dt}$$




Energy Storage: Inductor

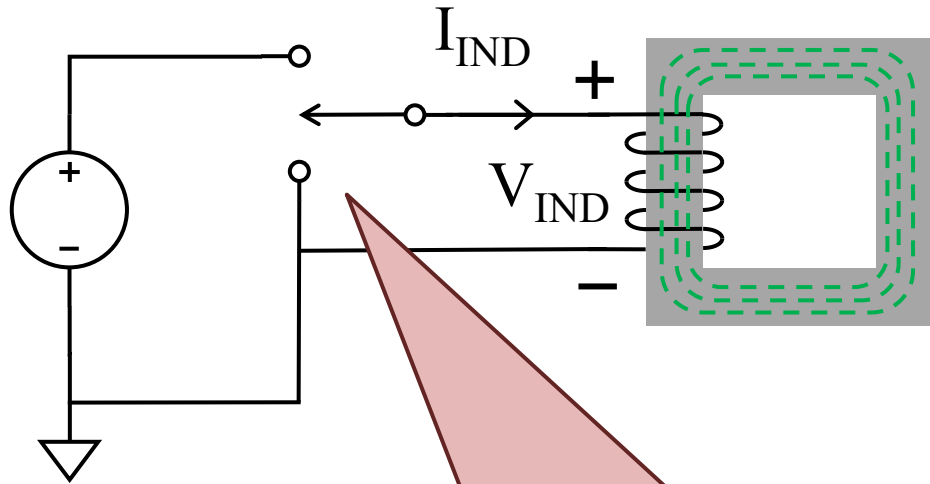



$$\lambda = L \cdot i$$

$$V = \frac{d\lambda}{dt}$$




What Happens
If The Switch
Is Opened?

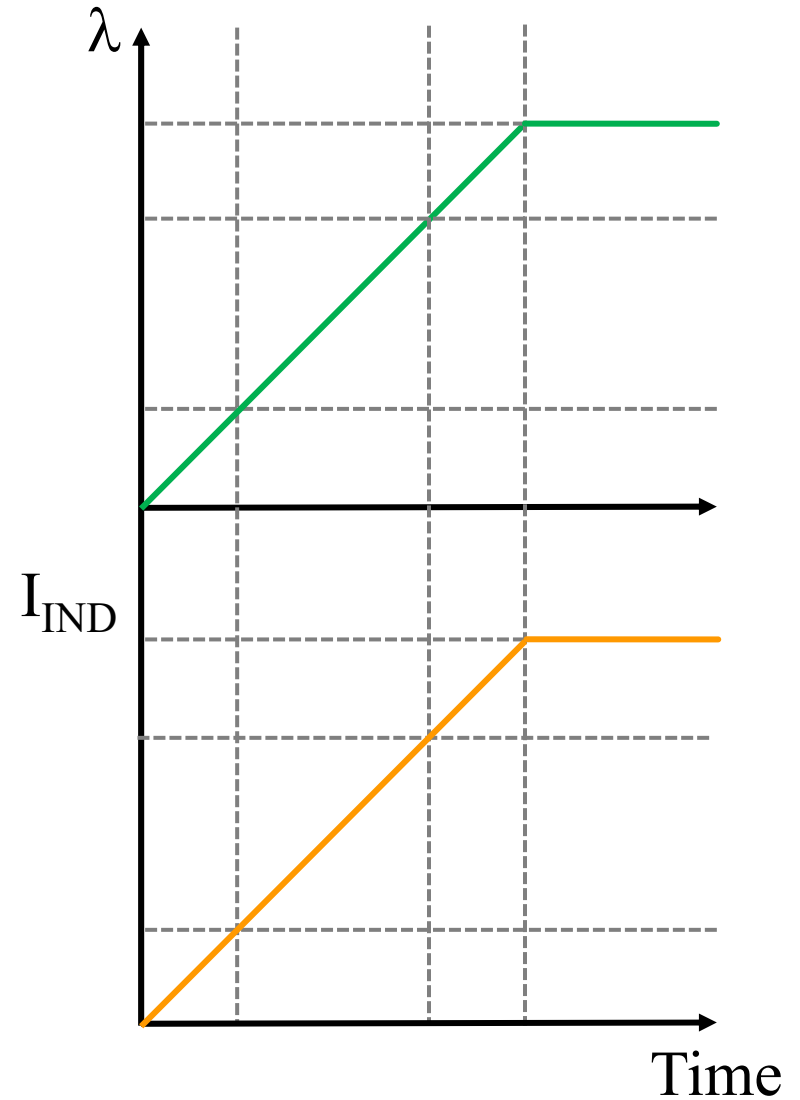


Energy Storage: Inductor

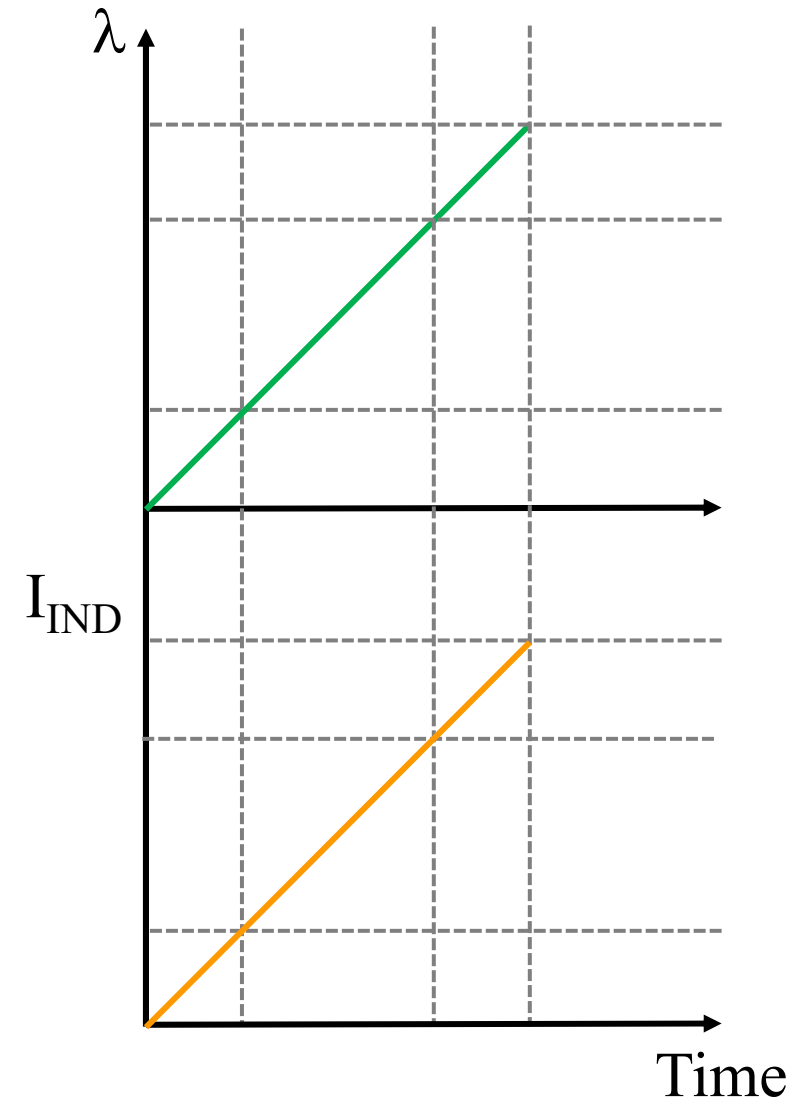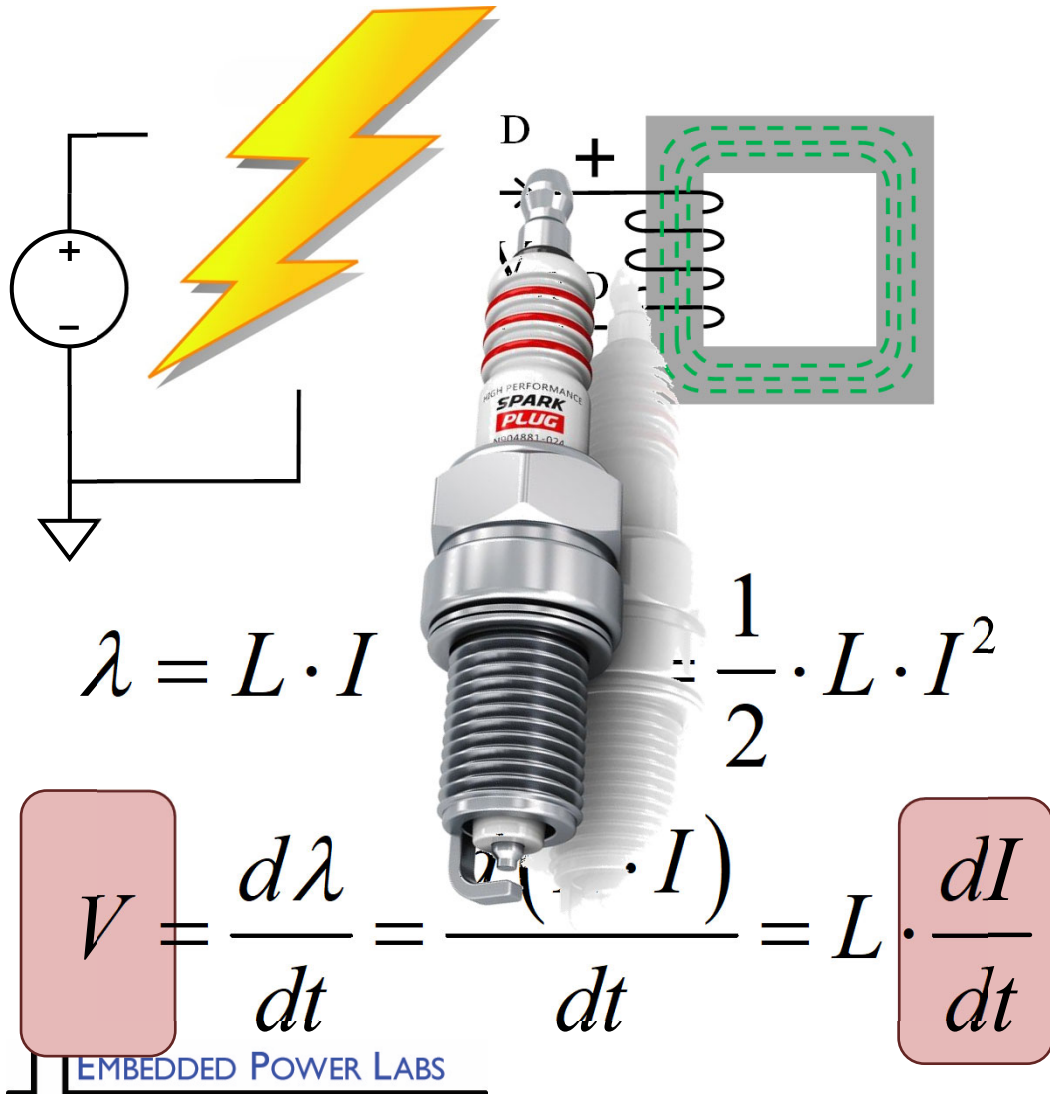

Inductor Ripple Current

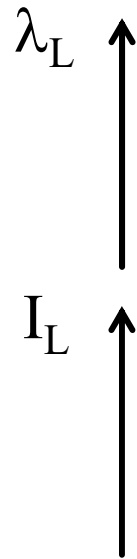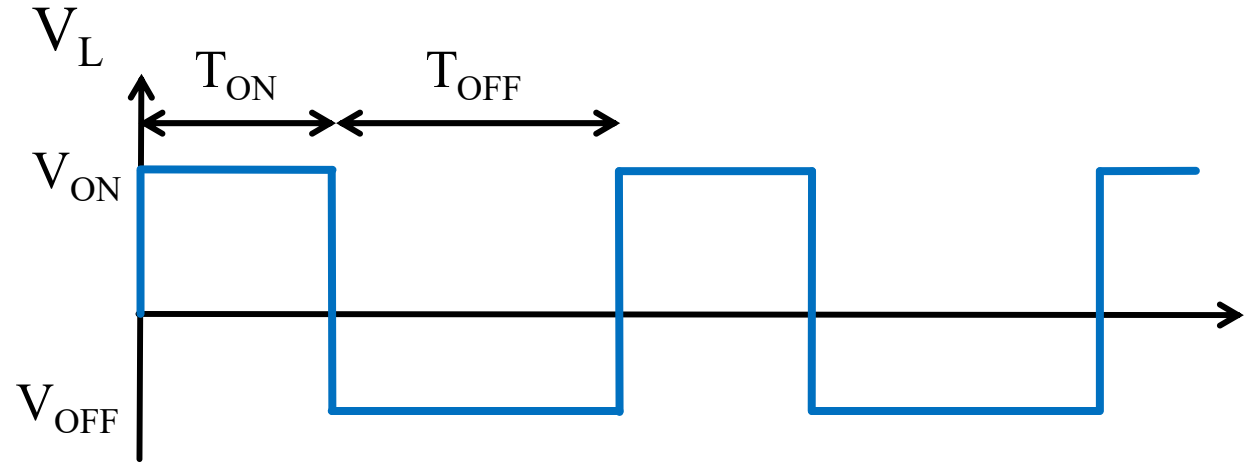
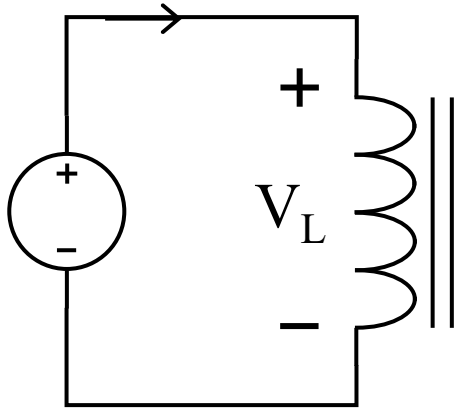


Inductor Ripple Current

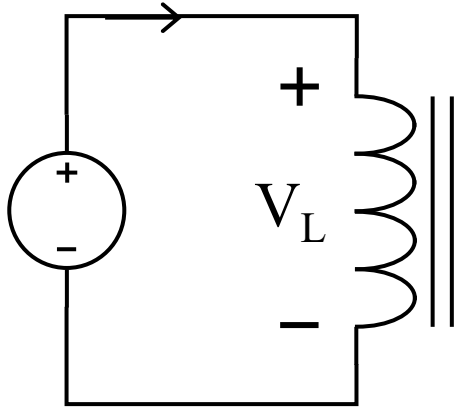


$$V_{ON} \cdot T_{ON} \Rightarrow \Delta\lambda_{ON}$$

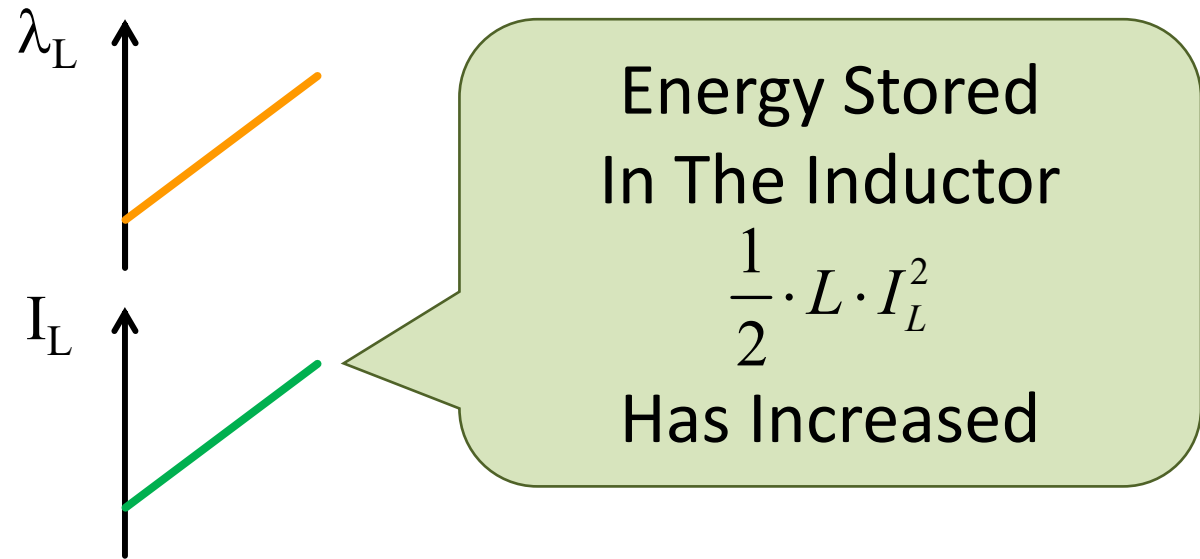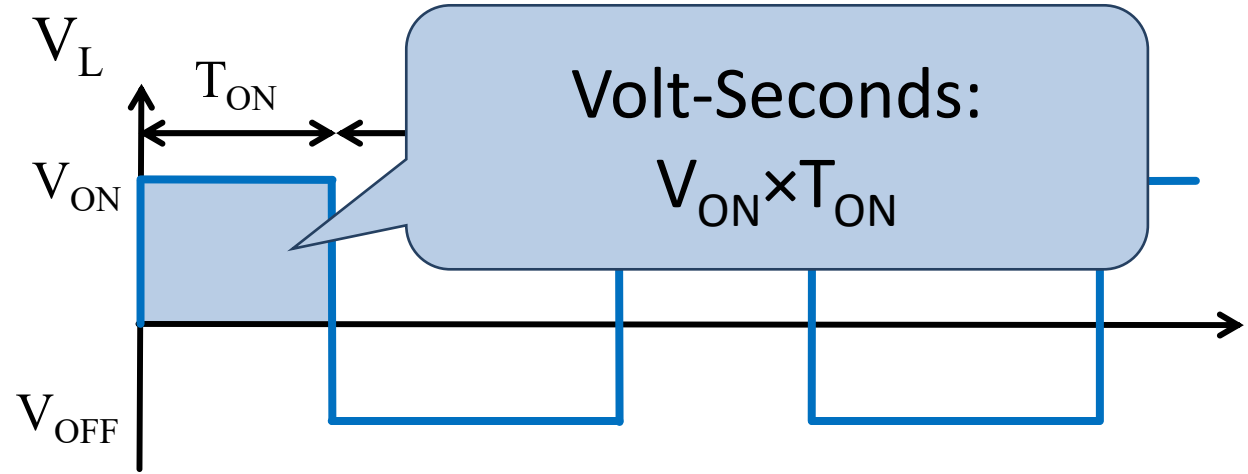
$$\Delta\lambda_{ON} \Rightarrow L \cdot \Delta I_{ON}$$



Inductor Ripple Current

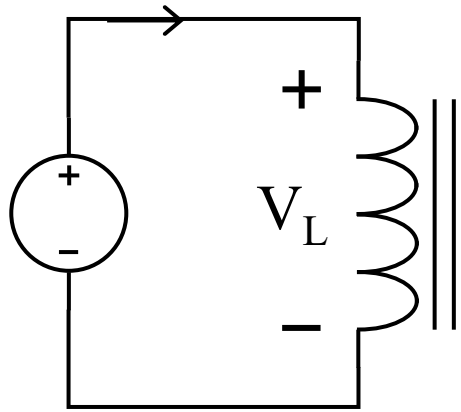


Volt-Seconds:
 $V_{OFF} \times T_{OFF}$

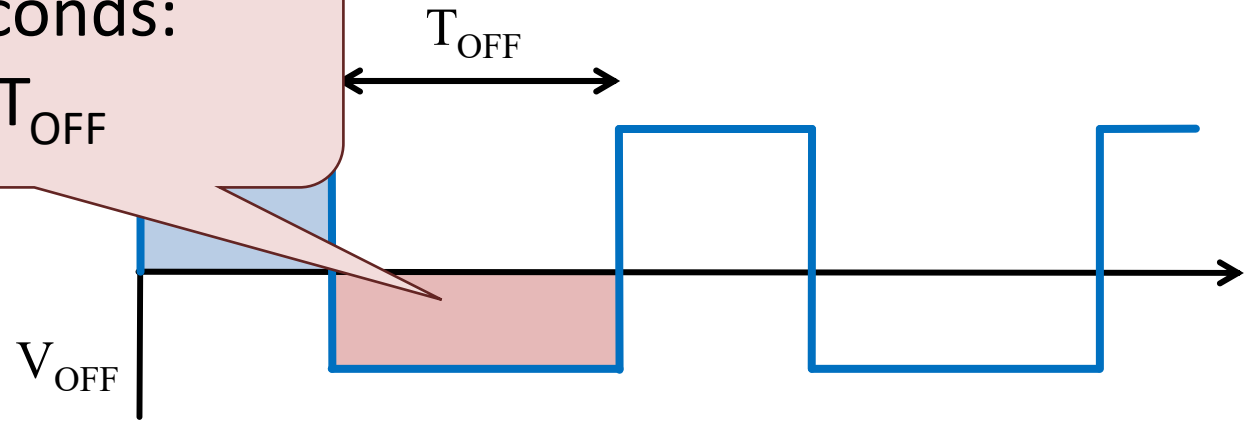




$$V_{OFF} \cdot T_{OFF} \Rightarrow \Delta \lambda_{OFF}$$
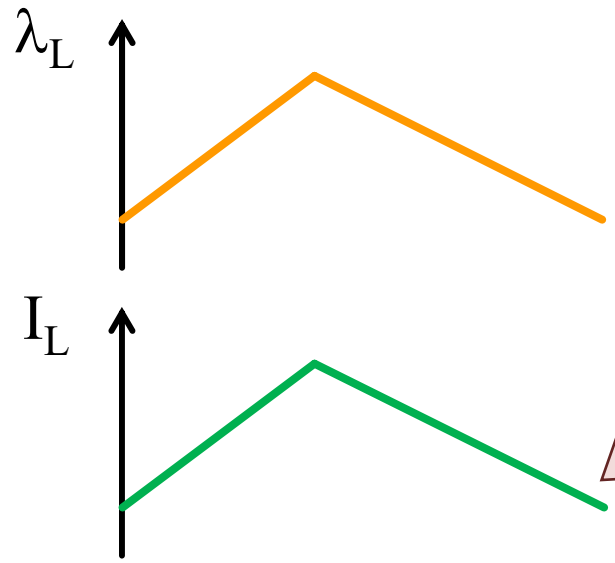
$$\Delta \lambda_{OFF} \Rightarrow L \cdot \Delta I_{OFF}$$





Energy Stored
In The Inductor
 $\frac{1}{2} \cdot L \cdot I_L^2$
Has Decreased


Inductor Ripple Current

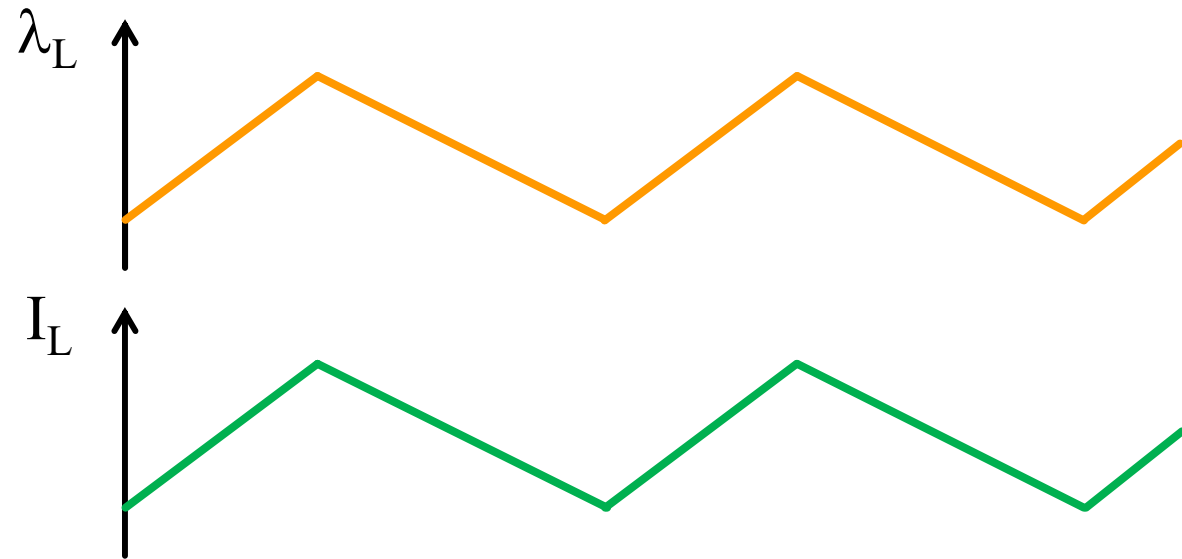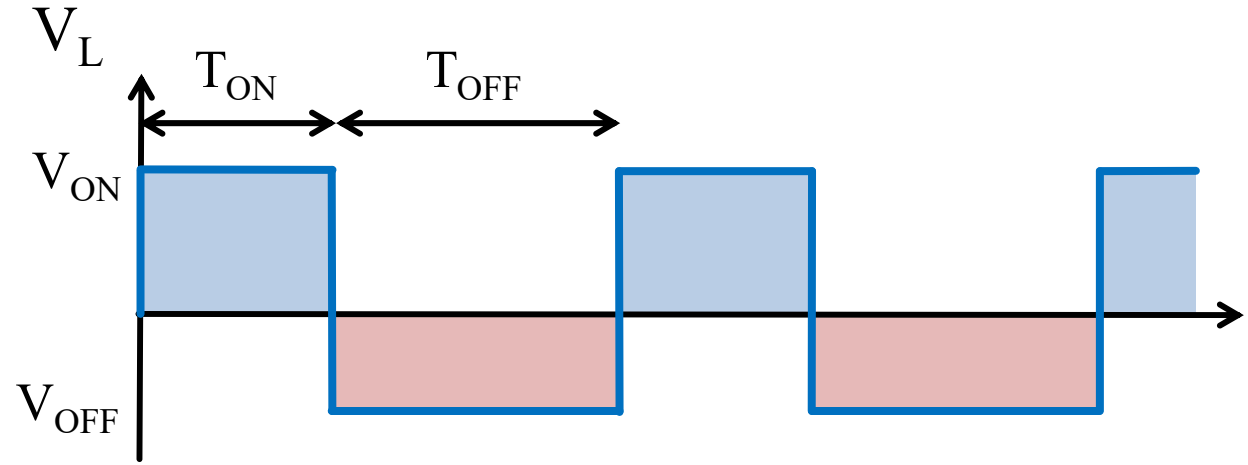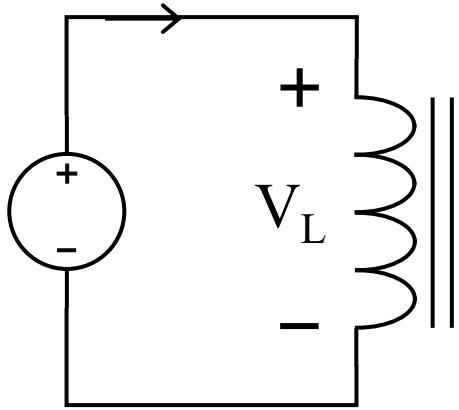



Inductor Ripple Current

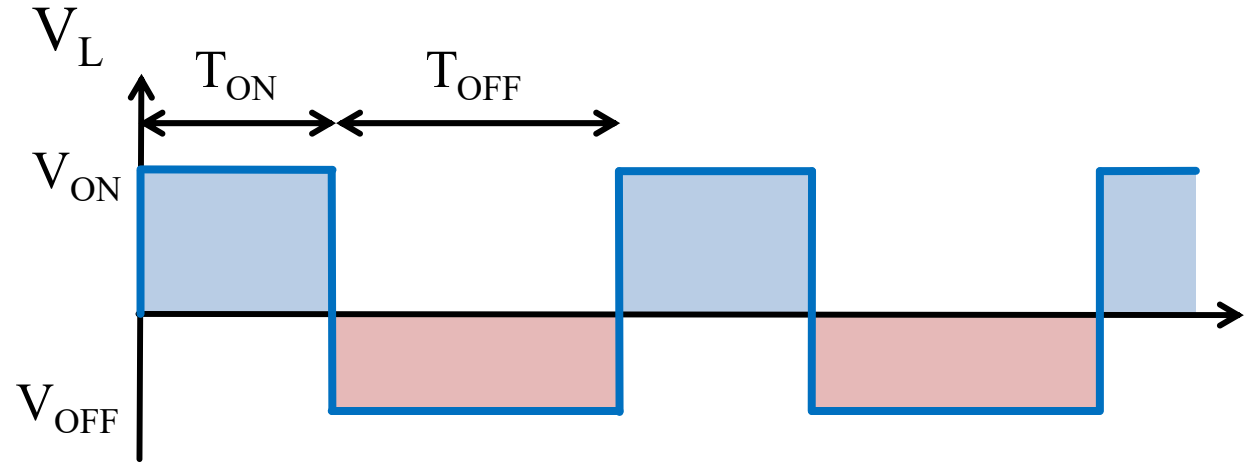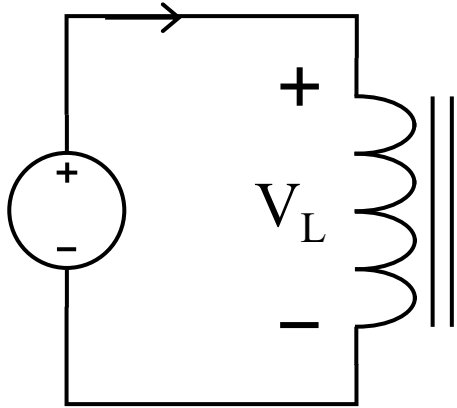

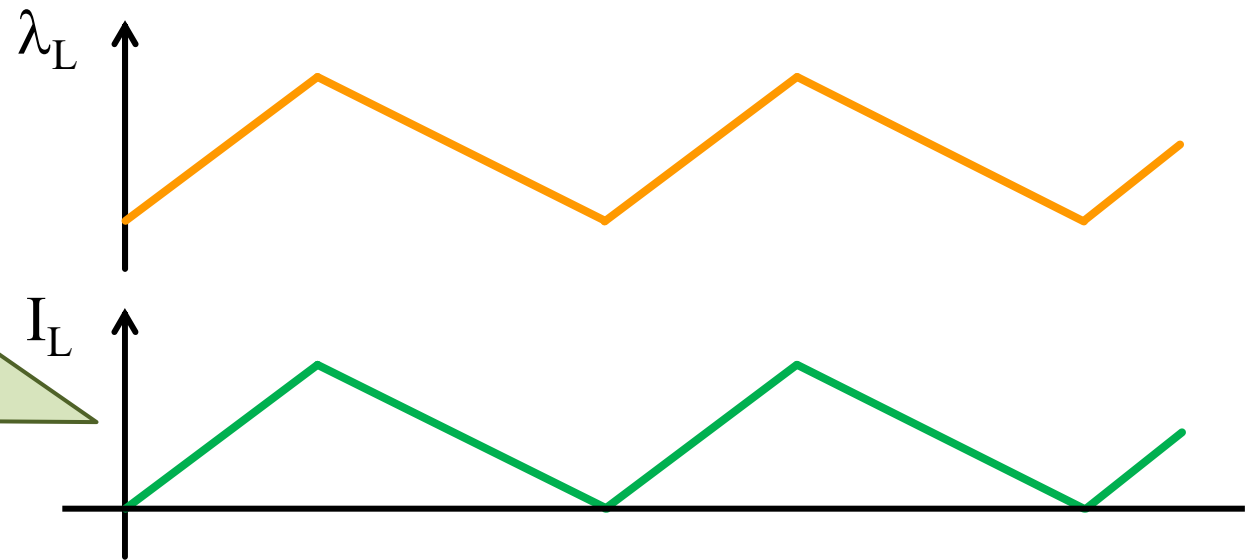In Steady State: Starting Value = Final Value




Inductor Ripple Current

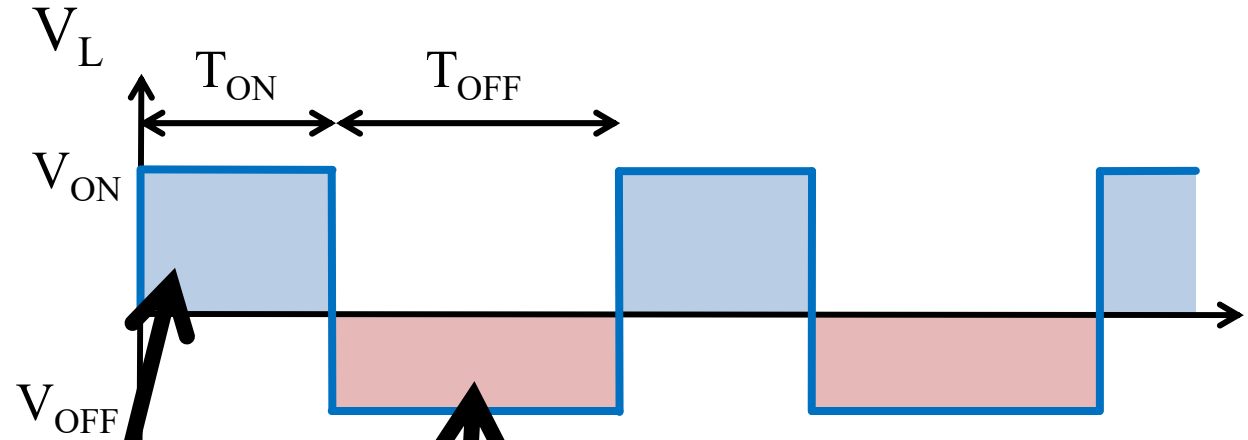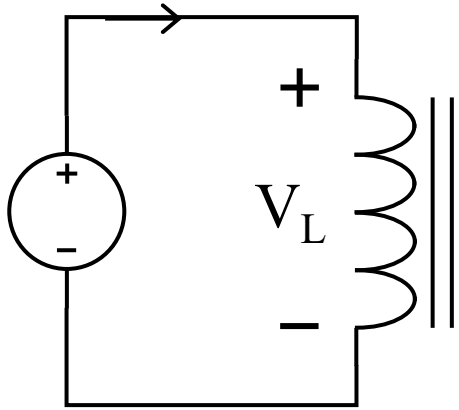

$$V_{ON} \cdot T_{ON} + V_{OFF} \cdot T_{OFF} = 0$$

Inductor Volt-Second Balance

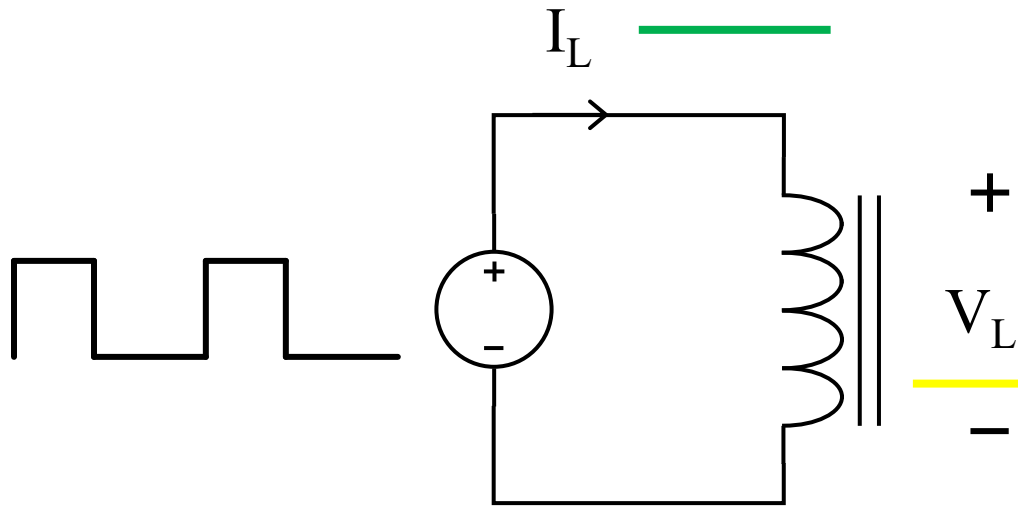Video Lab 1: Inductor Voltage And Current



Video Lab 1: Inductor Voltage And Current



$$V_{PLUS} = 9.00 \text{ V}$$

$$T_{PLUS} = 2.5 \mu\text{s}$$

$$V_{NEG} = -3.00 \text{ V}$$

$$T_{NEG} = 7.5 \mu\text{s}$$

$$V_{PLUS} \cdot T_{PLUS} + V_{NEG} \cdot T_{NEG}$$
$$9.00 \text{ V} \cdot 2.5 \mu\text{s} + (-3.00 \text{ V}) \cdot 7.5 \mu\text{s}$$

$$22.5 \text{ V}\cdot\mu\text{s} - 22.5 \text{ V}\cdot\mu\text{s}$$



$$0 \text{ V}\cdot\mu\text{s}$$

Video Lab 1: Inductor Voltage And Current




$$V = L \cdot \frac{di}{dt}$$
$$L = \frac{V \cdot dt}{di}$$
$$= \frac{9.00 \text{ V} \cdot 2.5 \mu\text{s}}{512 \text{ mA}}$$
$$= 43.9 \mu\text{H}$$

Capacitor Ripple Voltage

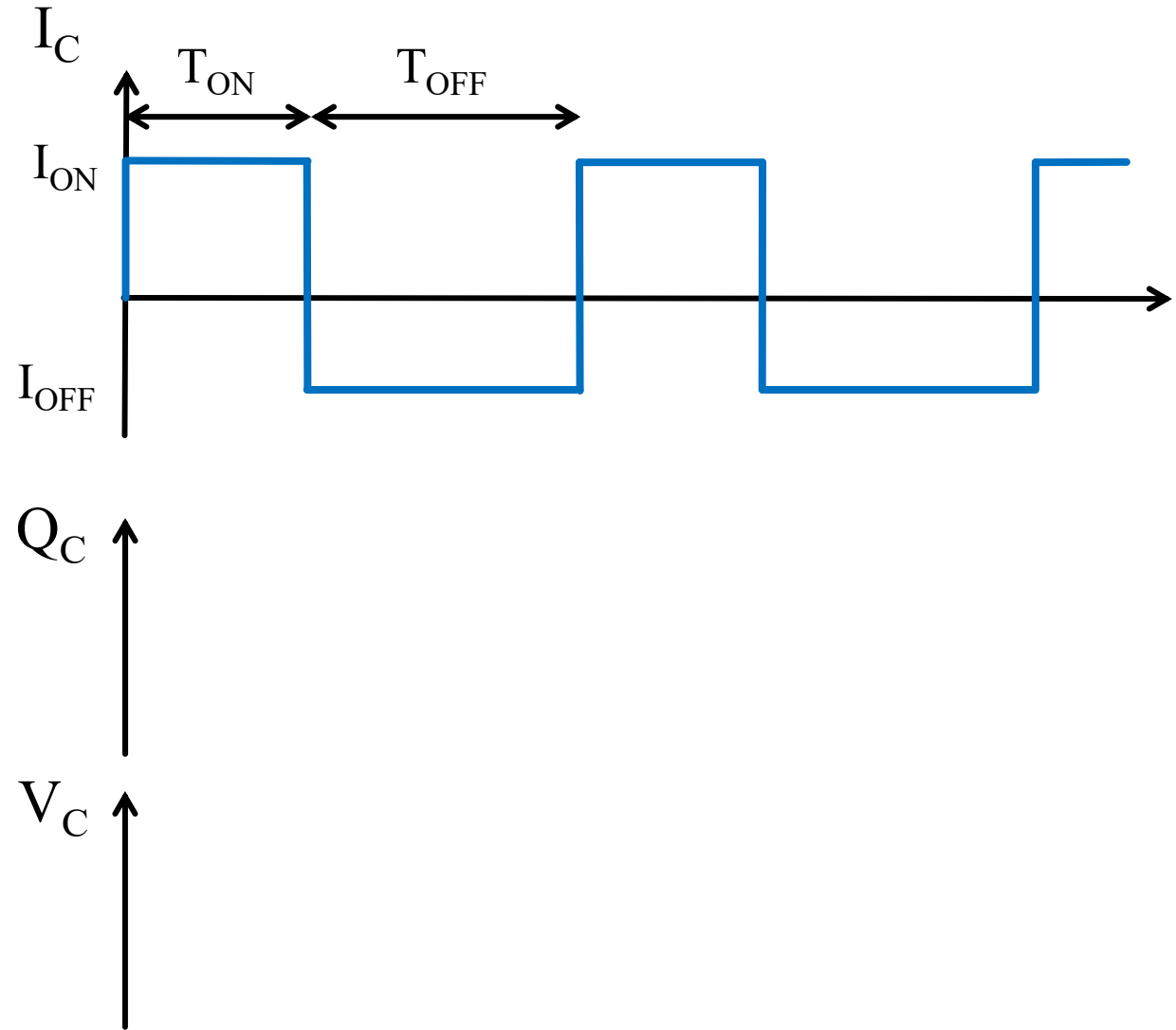
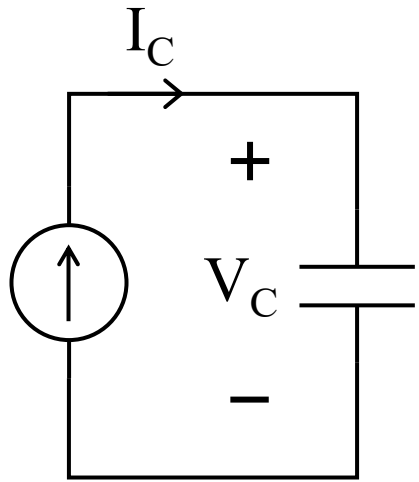


Capacitor Ripple Voltage

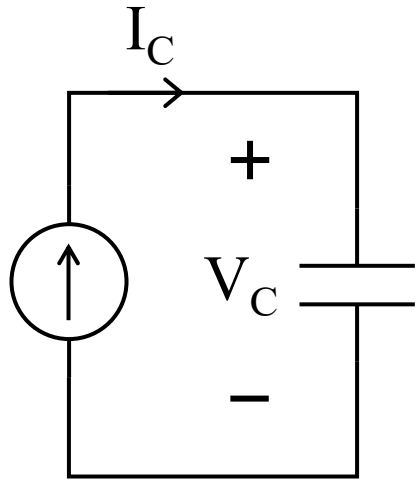


$$I_{ON} \cdot T_{ON} \Rightarrow \Delta Q_{ON}$$
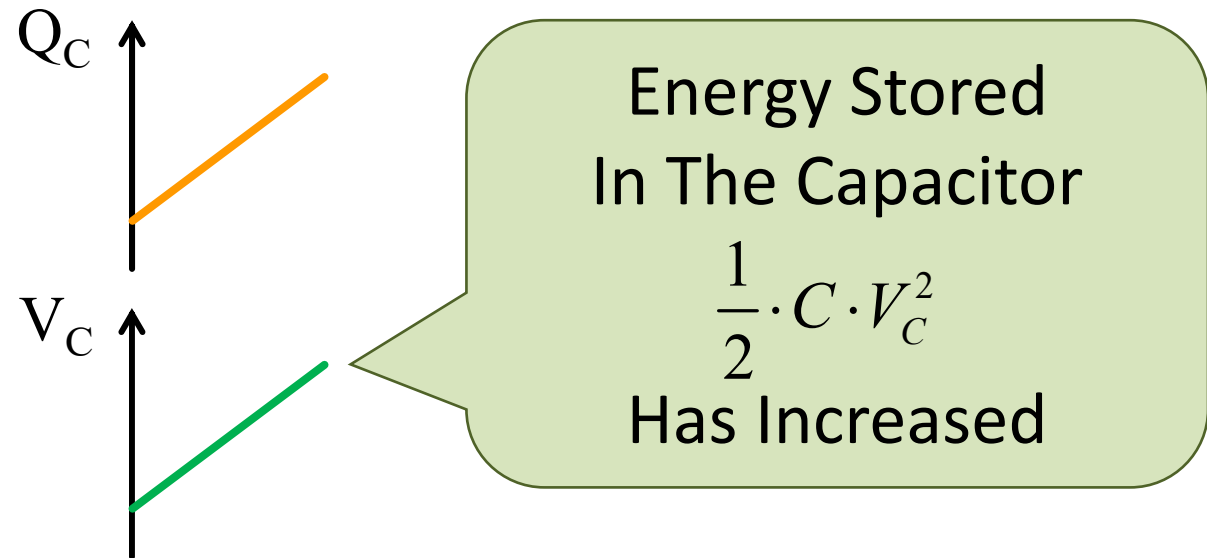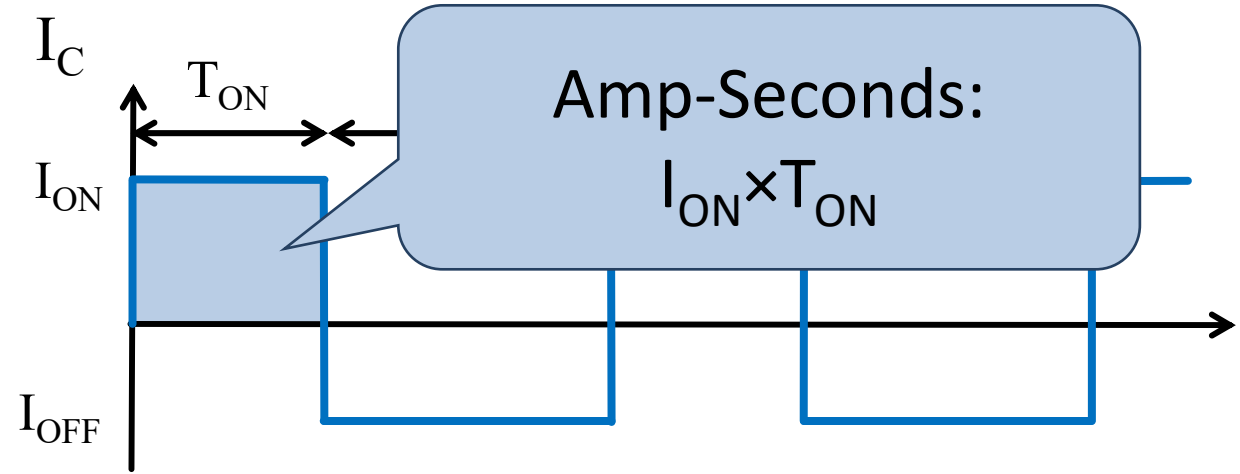
$$\Delta Q_{ON} \Rightarrow C \cdot \Delta V_{ON}$$




Capacitor Ripple Voltage

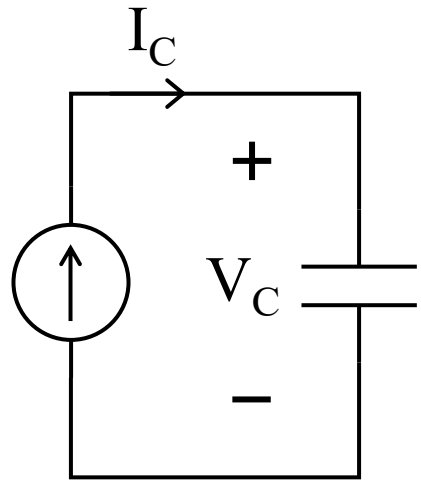


Amp-Seconds:

$$I_{OFF} \times T_{OFF}$$

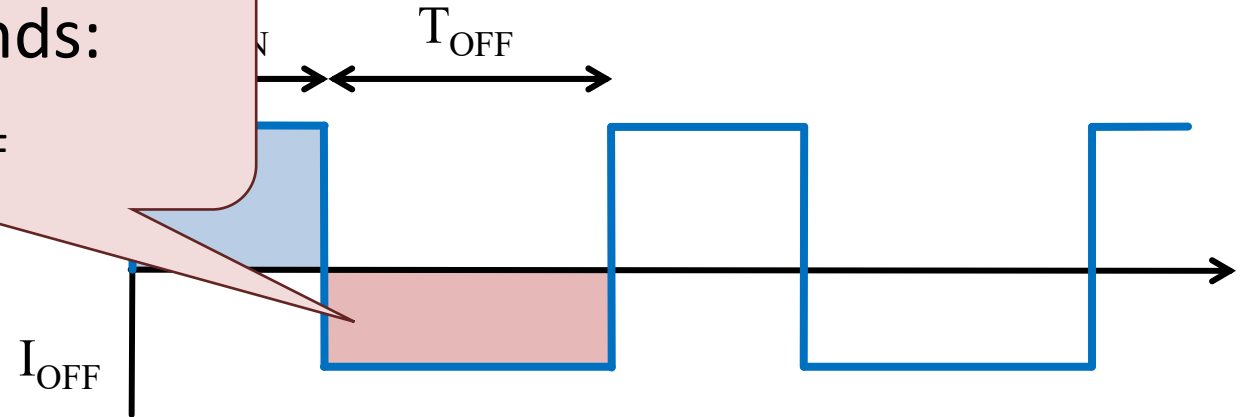

$$I_{OFF} \cdot T_{OFF} \Rightarrow \Delta Q_{OFF}$$
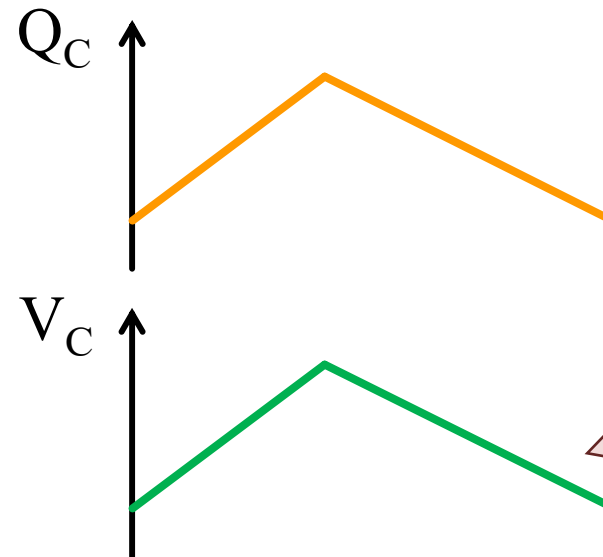
$$\Delta Q_{OFF} \Rightarrow C \cdot \Delta V_{OFF}$$






Energy Stored
In The Capacitor



$$\frac{1}{2} \cdot C \cdot V_C^2$$

Has Decreased


Capacitor Ripple Voltage

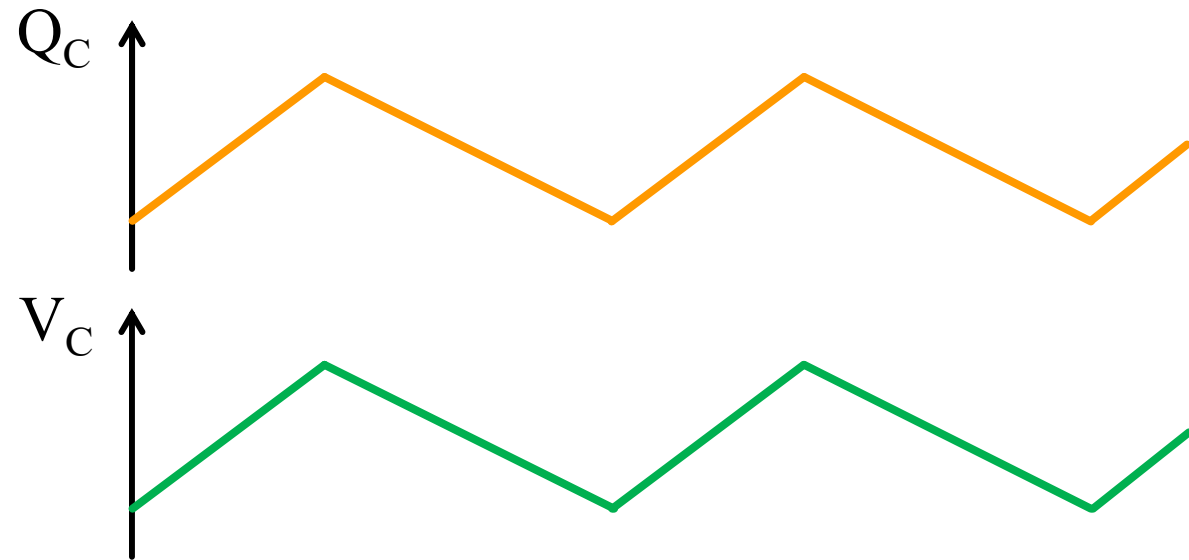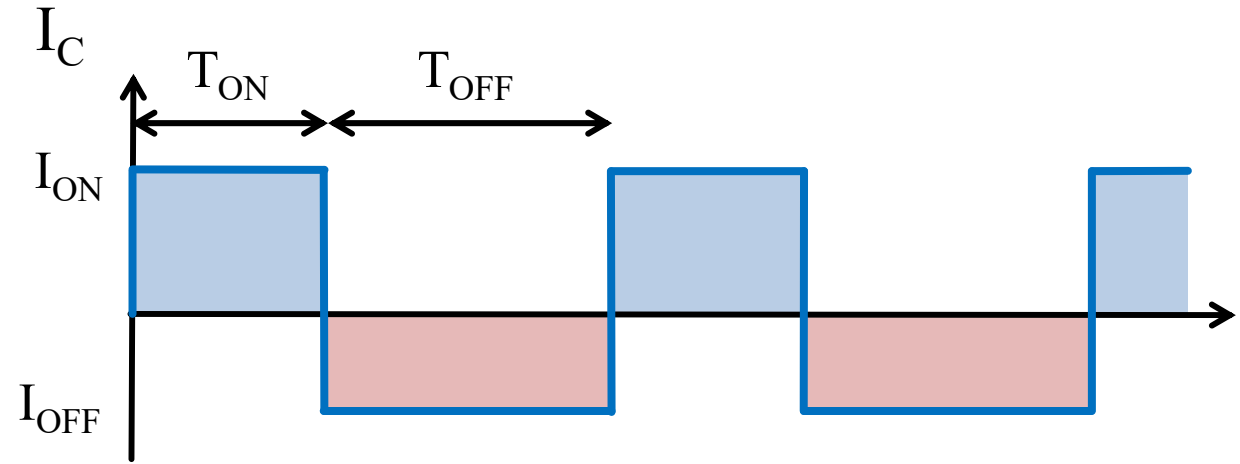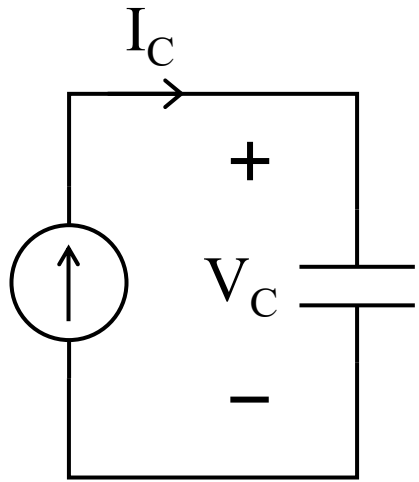



Capacitor Ripple Voltage

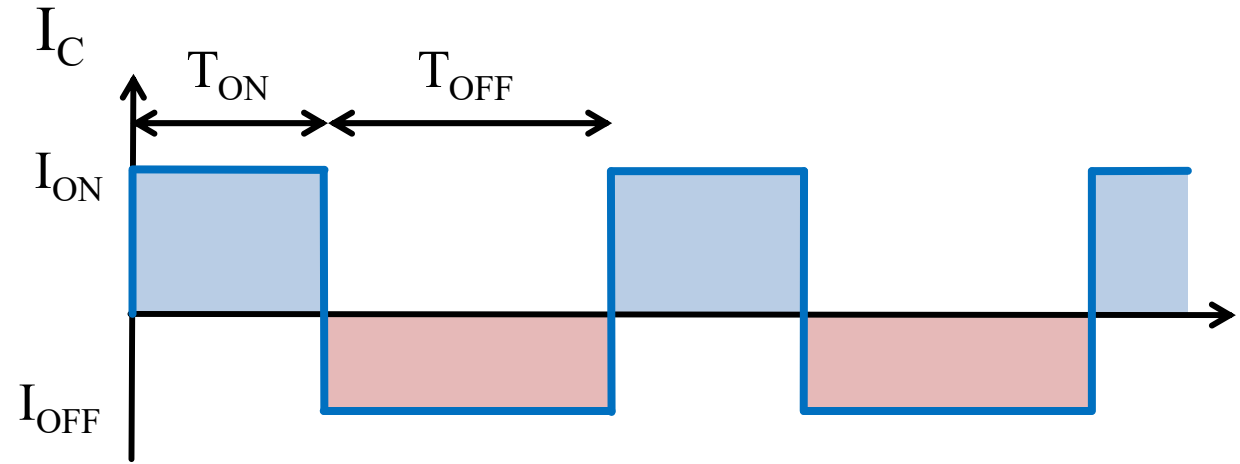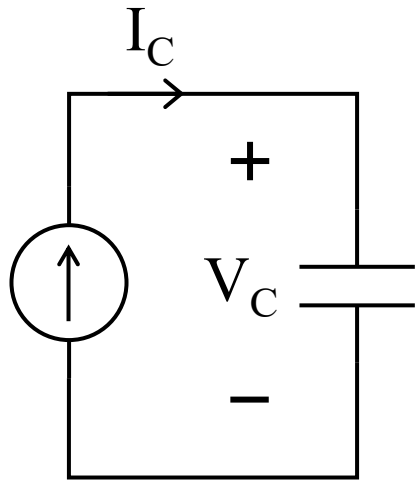

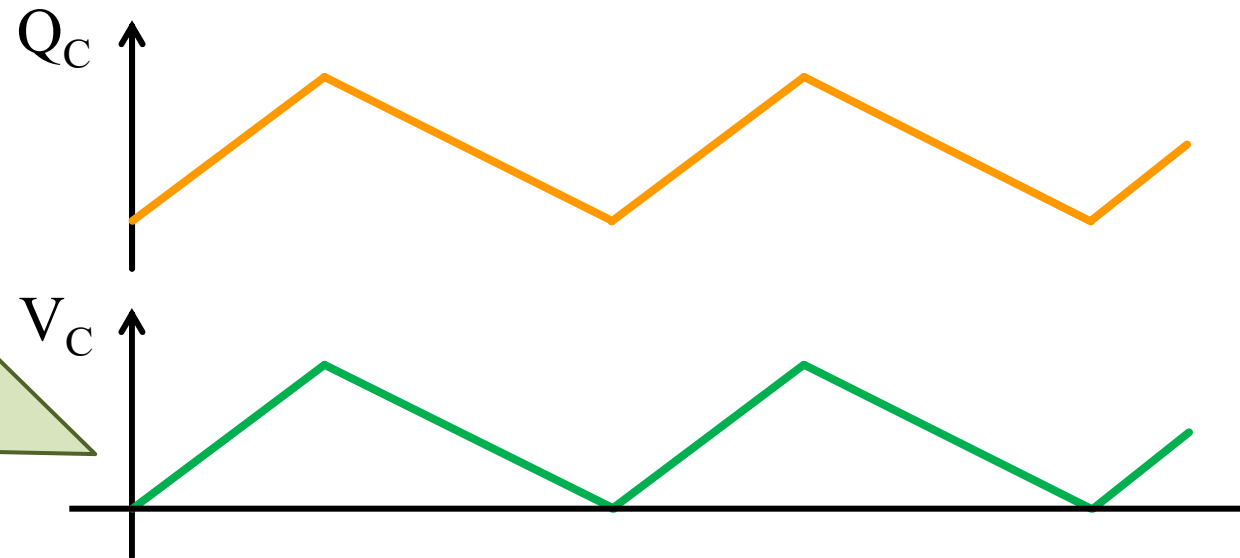In Steady State: Starting Value = Final Value




Capacitor Ripple Voltage

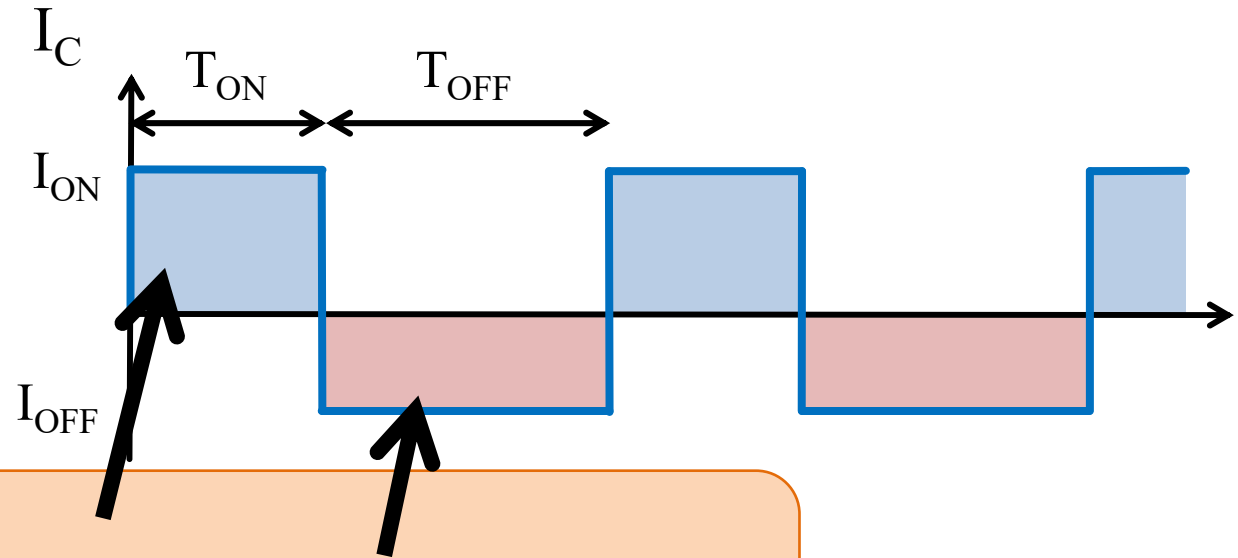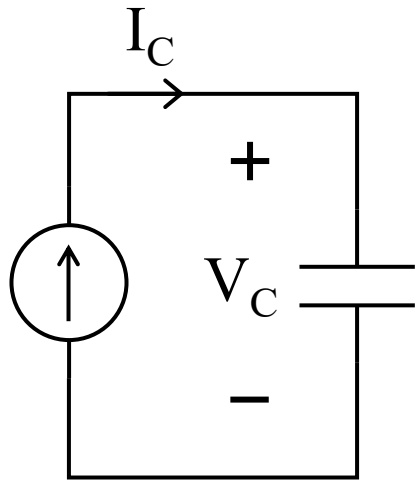


$$I_{ON} \cdot T_{ON} + I_{OFF} \cdot T_{OFF} = 0$$

Capacitor Charge Balance

Transformer


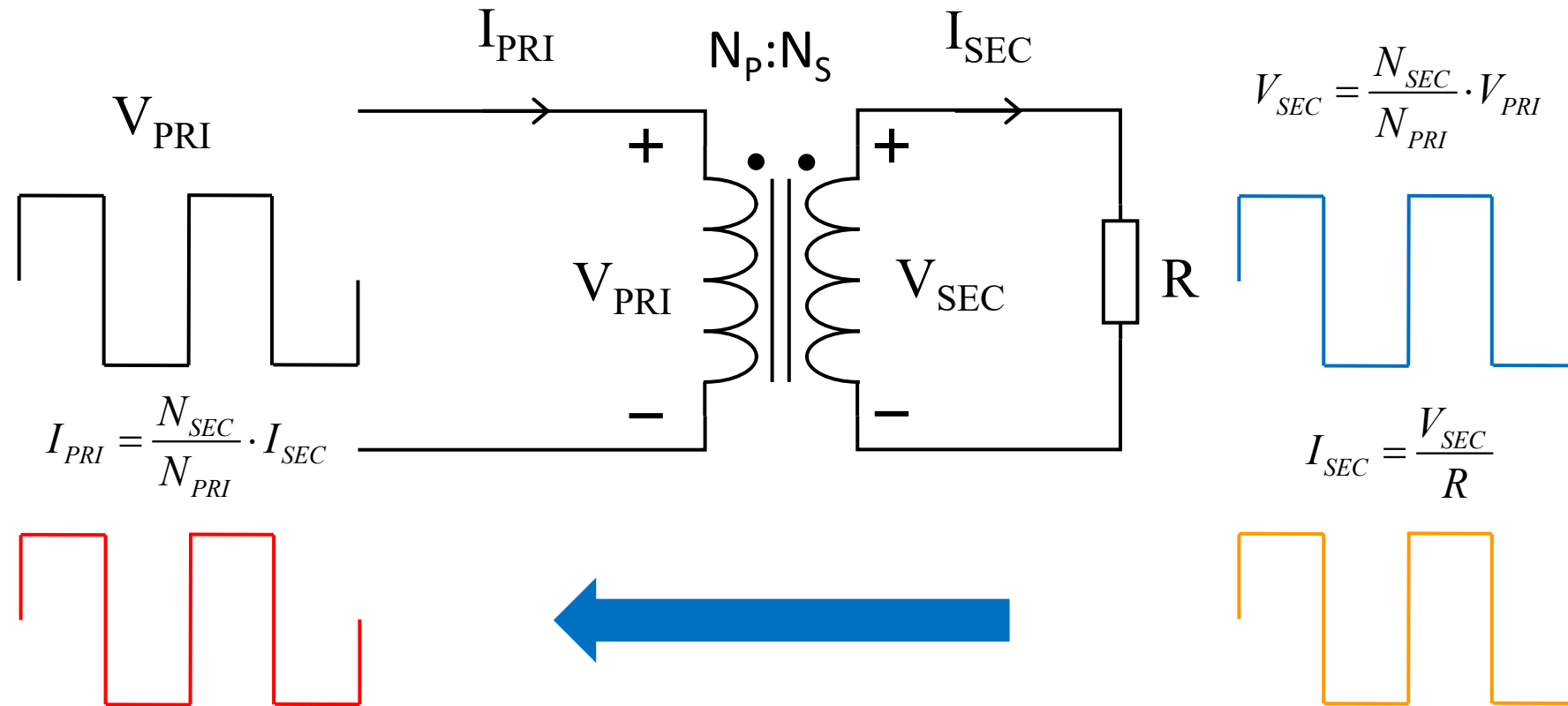


Transformer Magnetizing Current

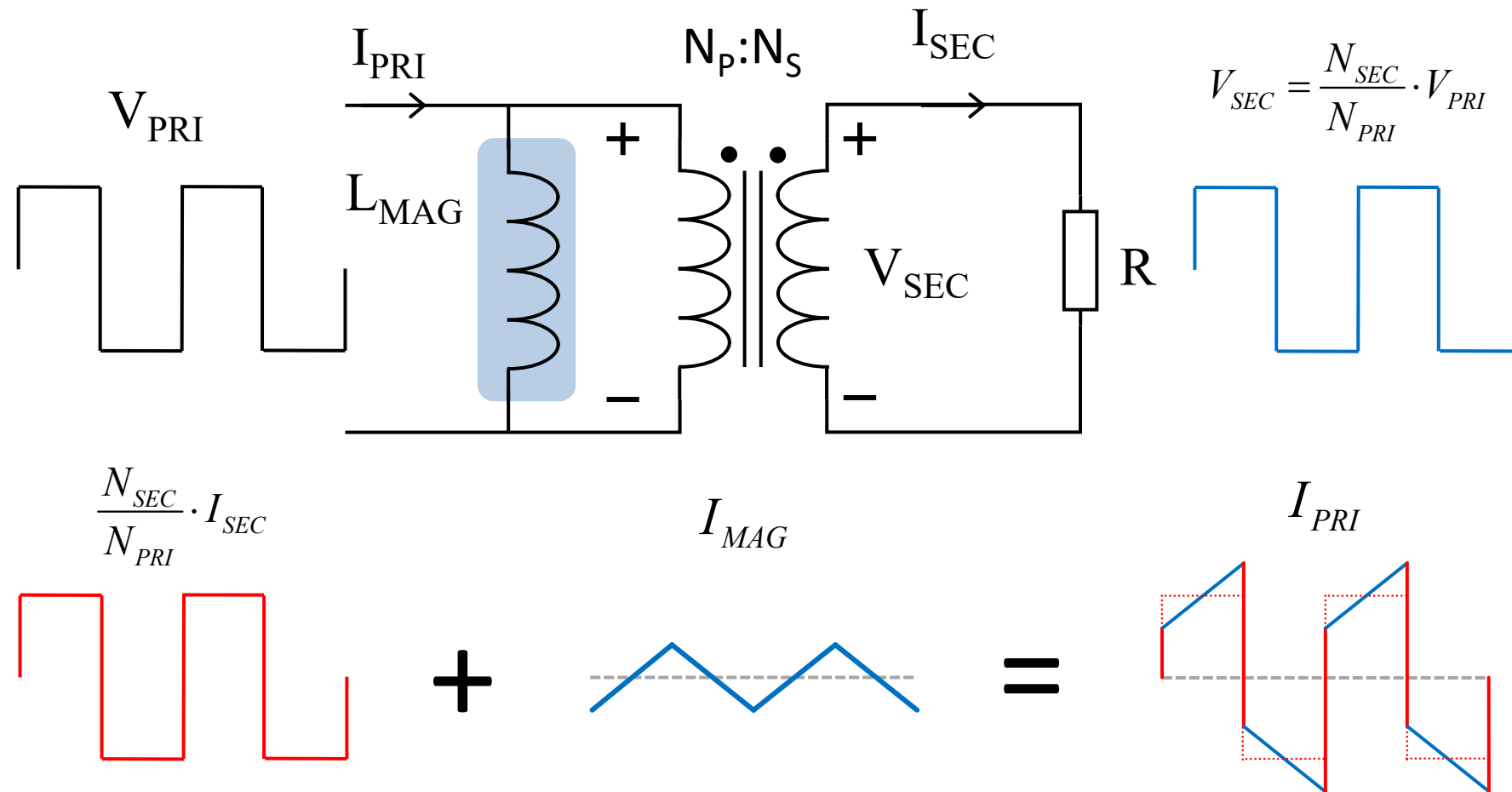


Buck Converter


Switch Mode Concept

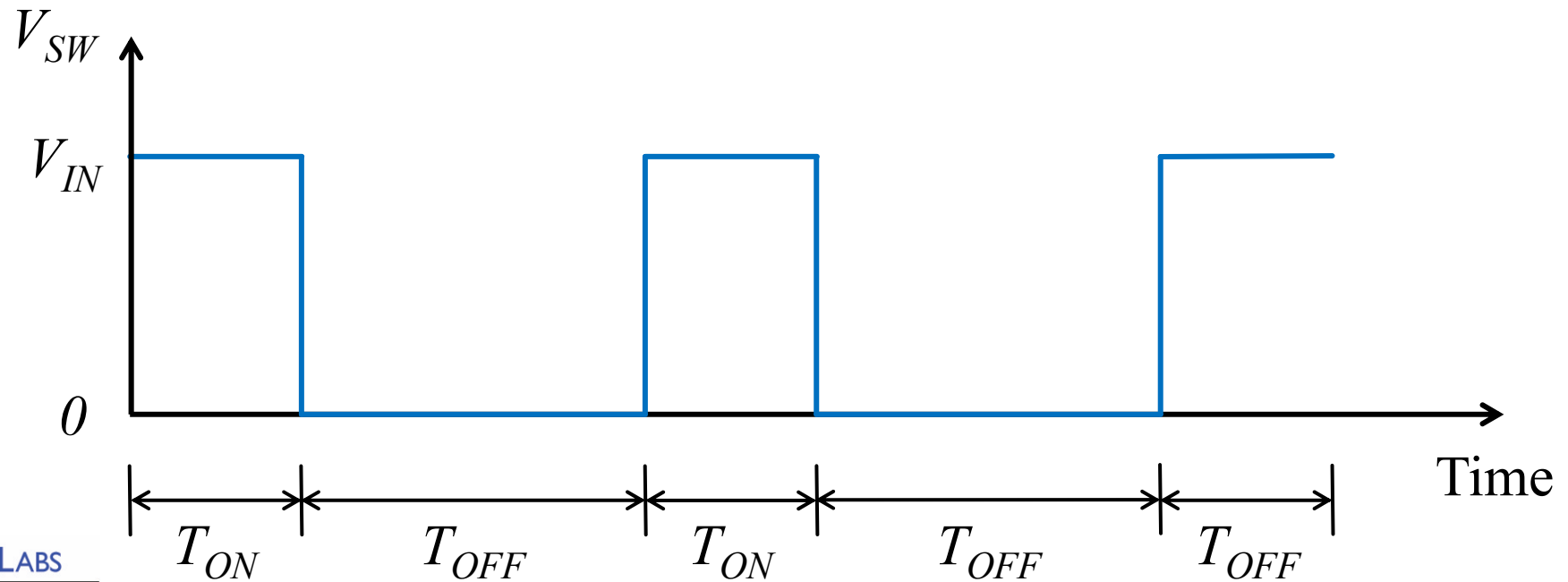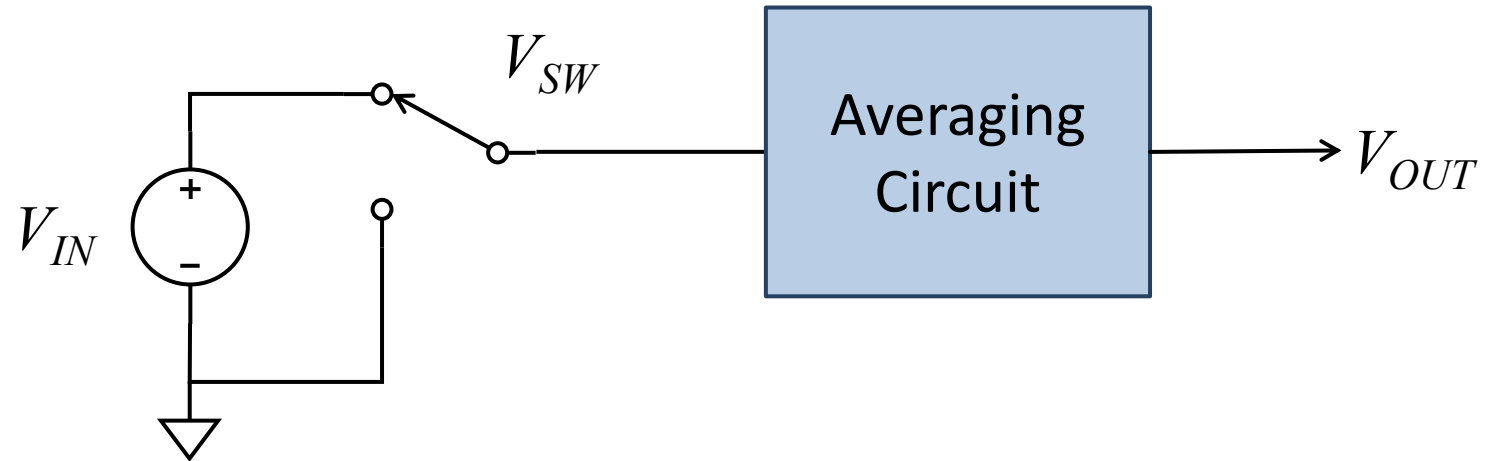


Buck Converter

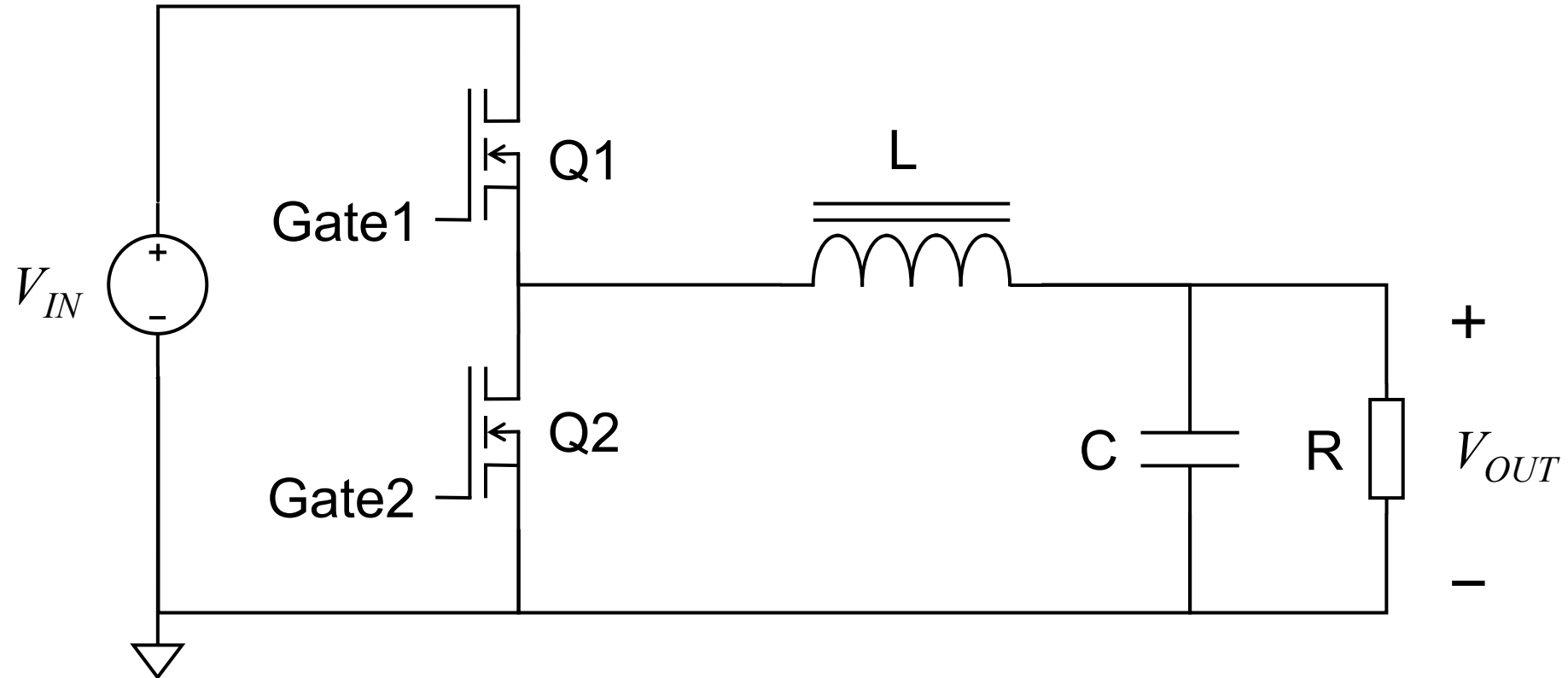

Buck Converter

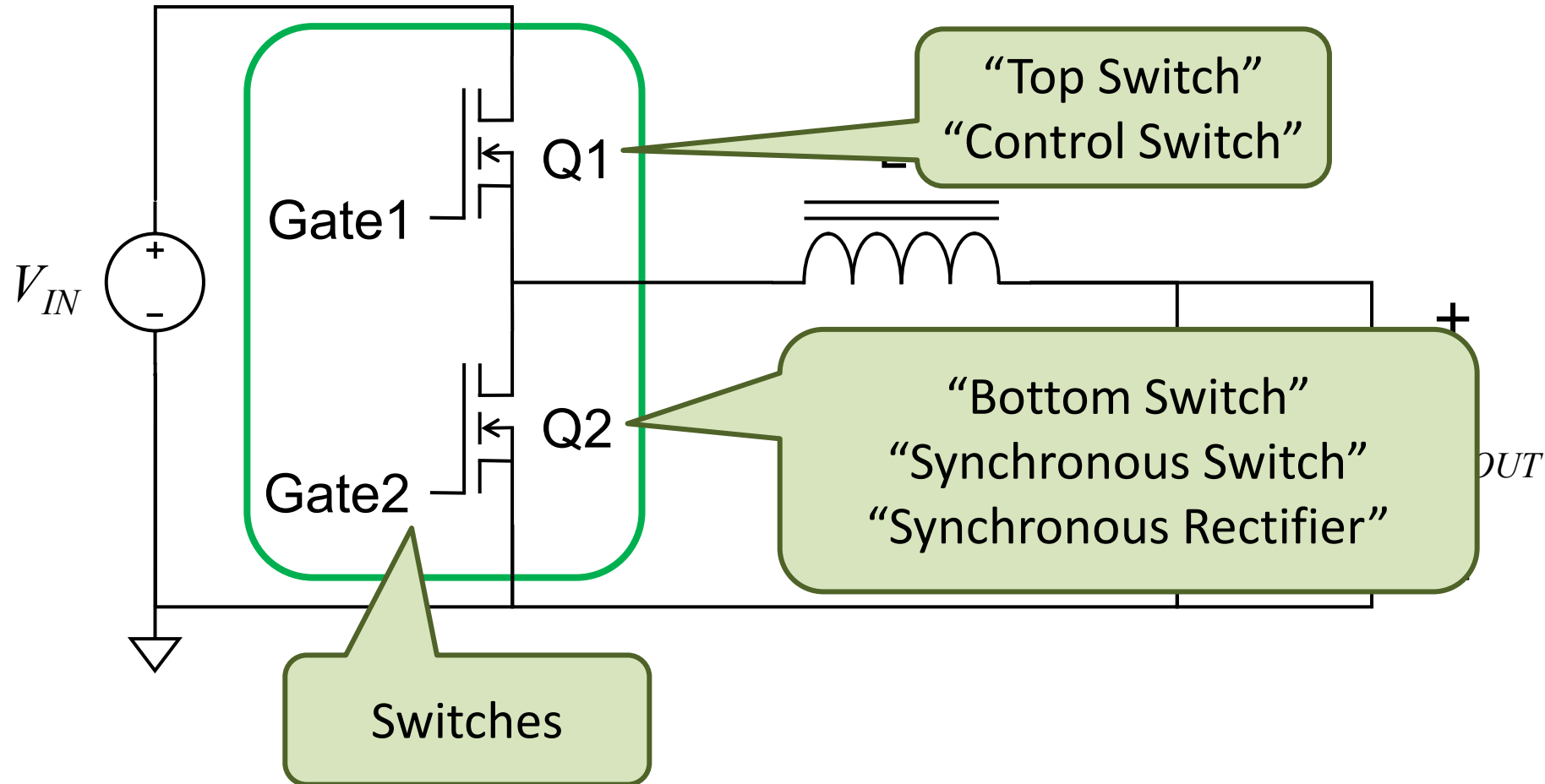


Buck Converter

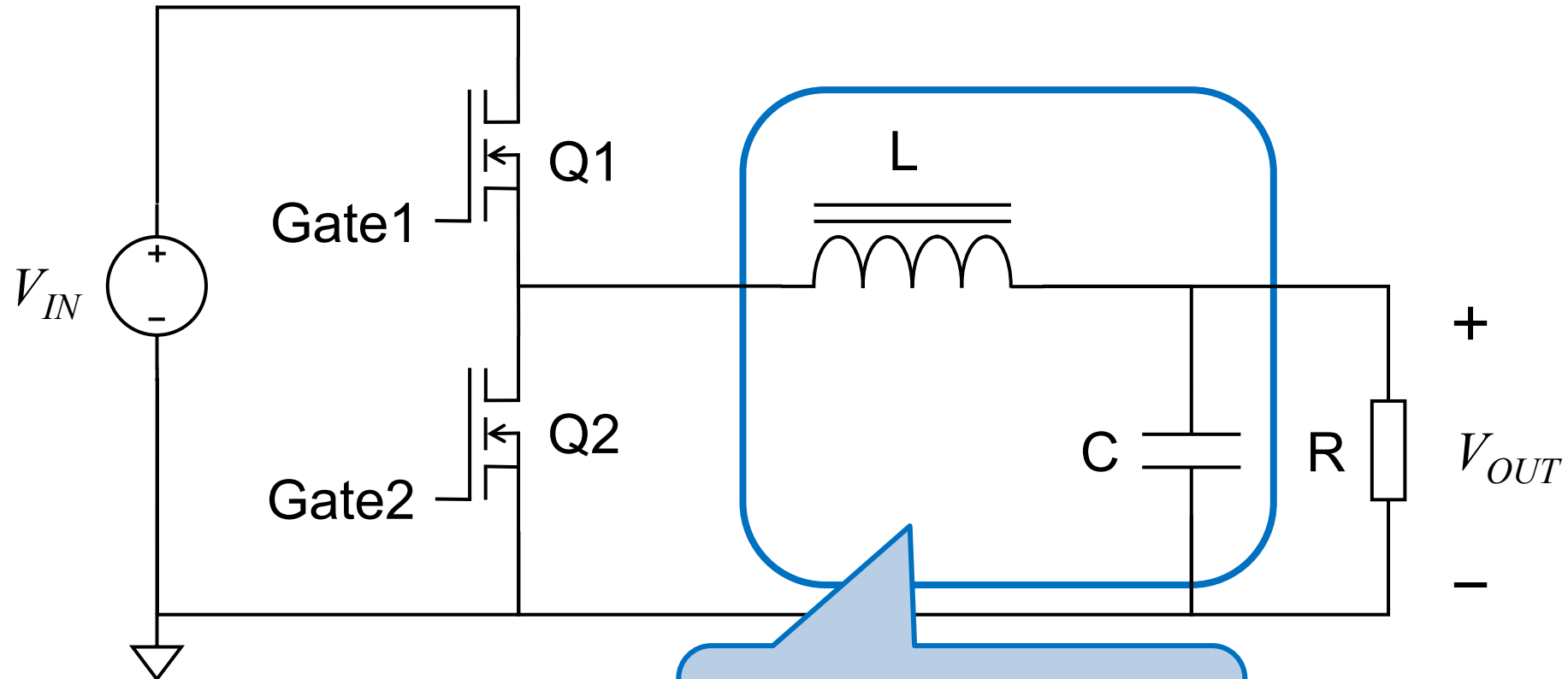


Low Pass Filter \Rightarrow
Averaging Circuit


Buck Converter

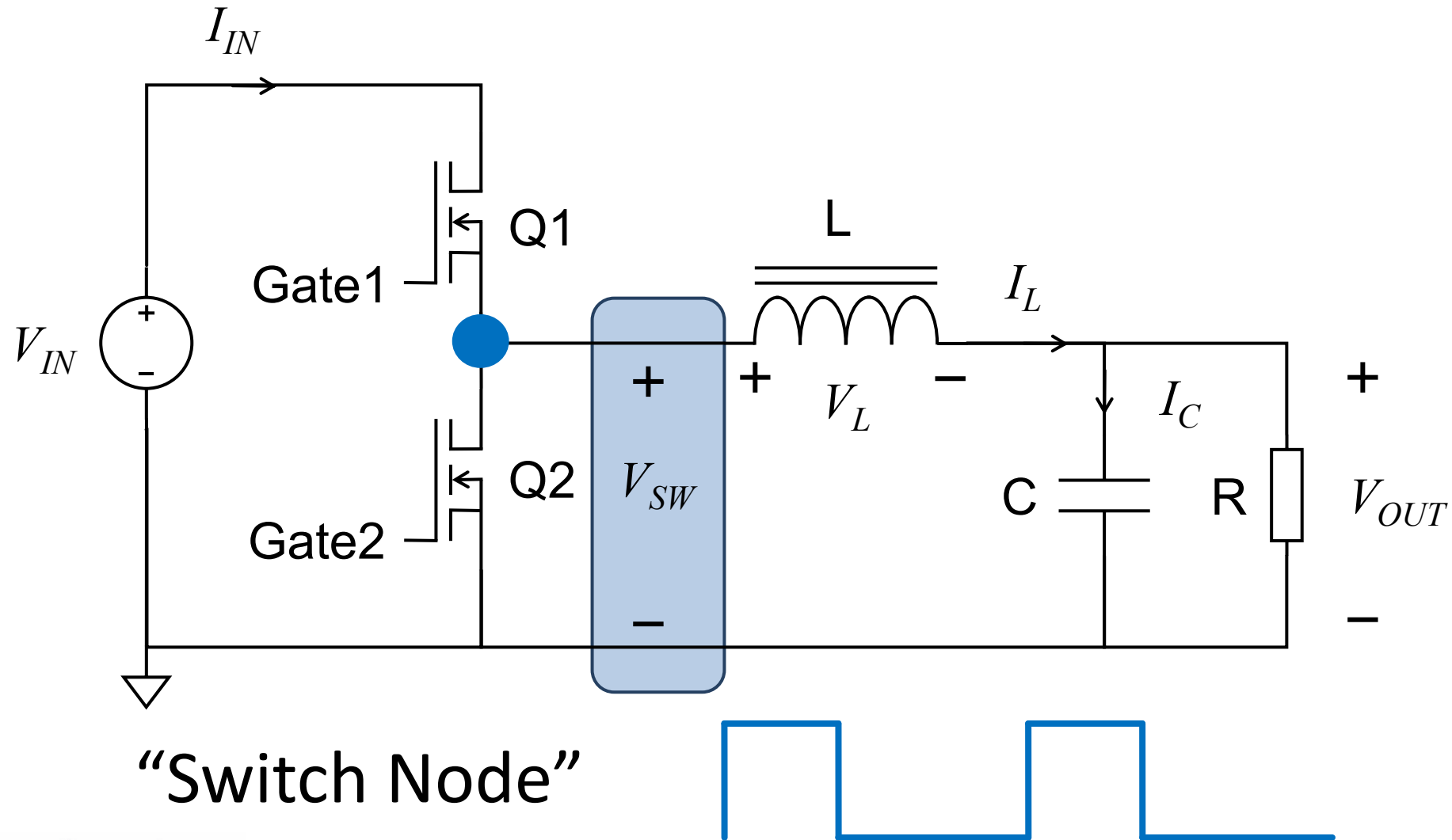


Buck Converter On Time

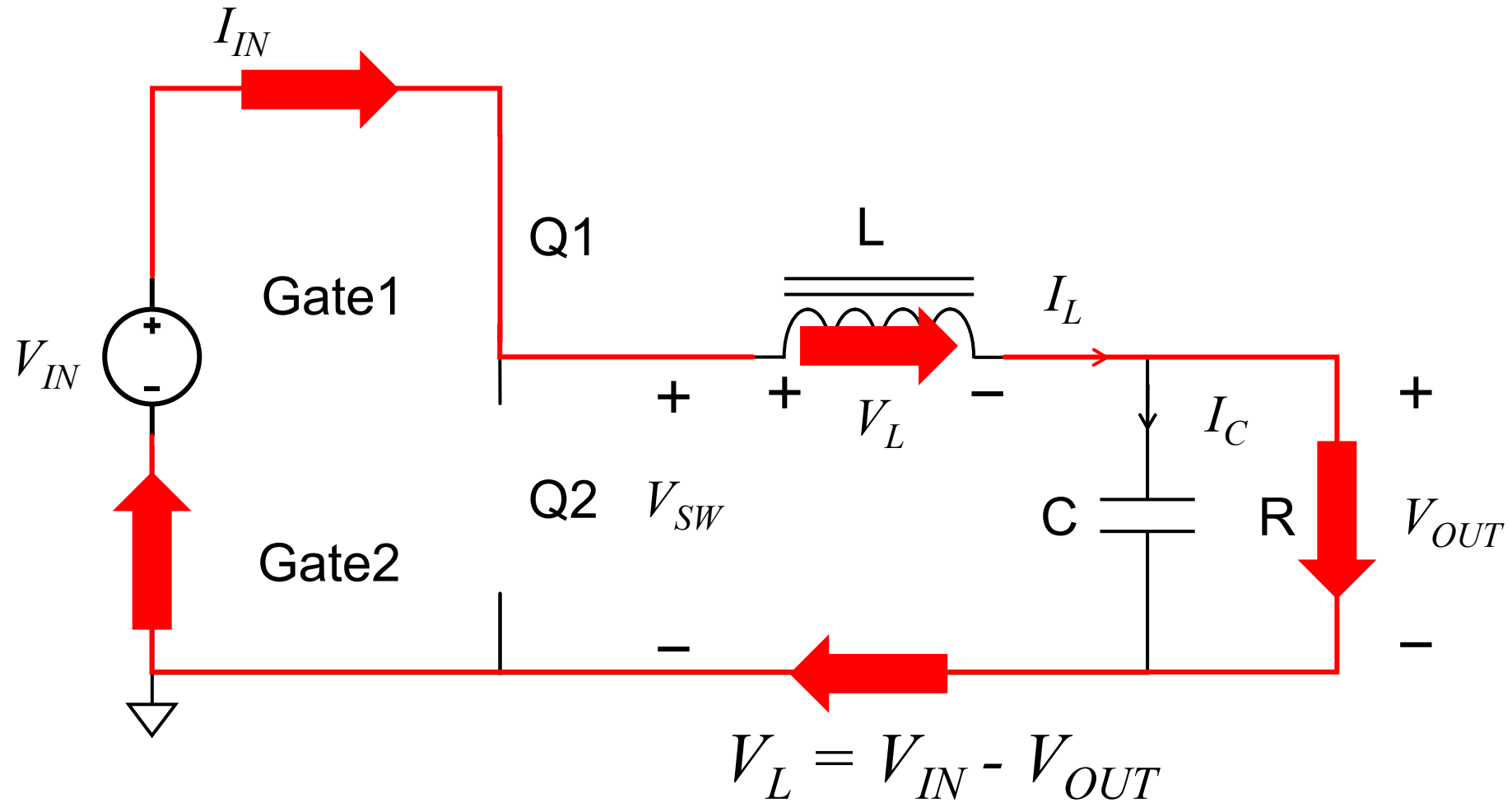


Buck Converter On Time

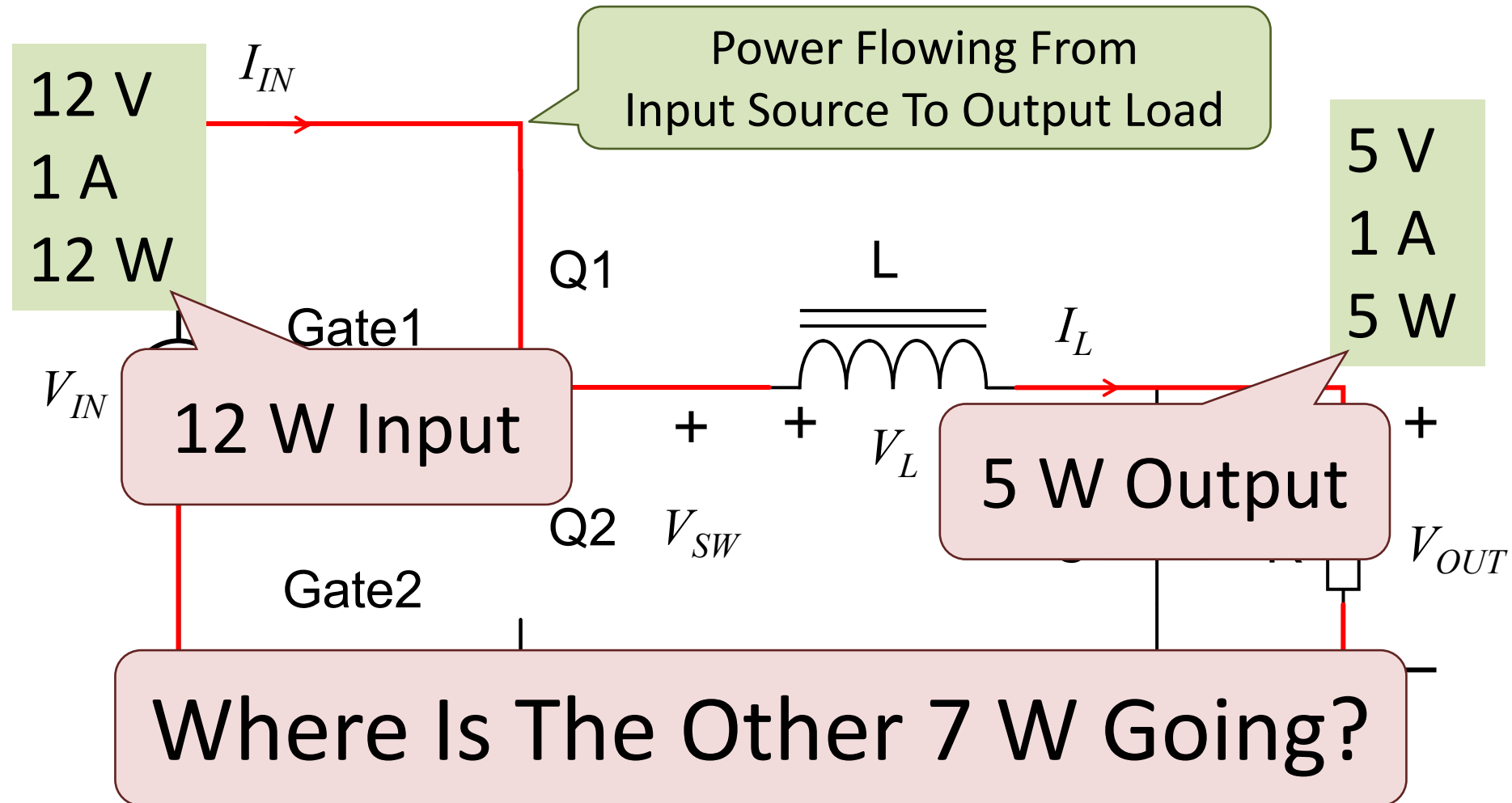


Buck Converter On Time

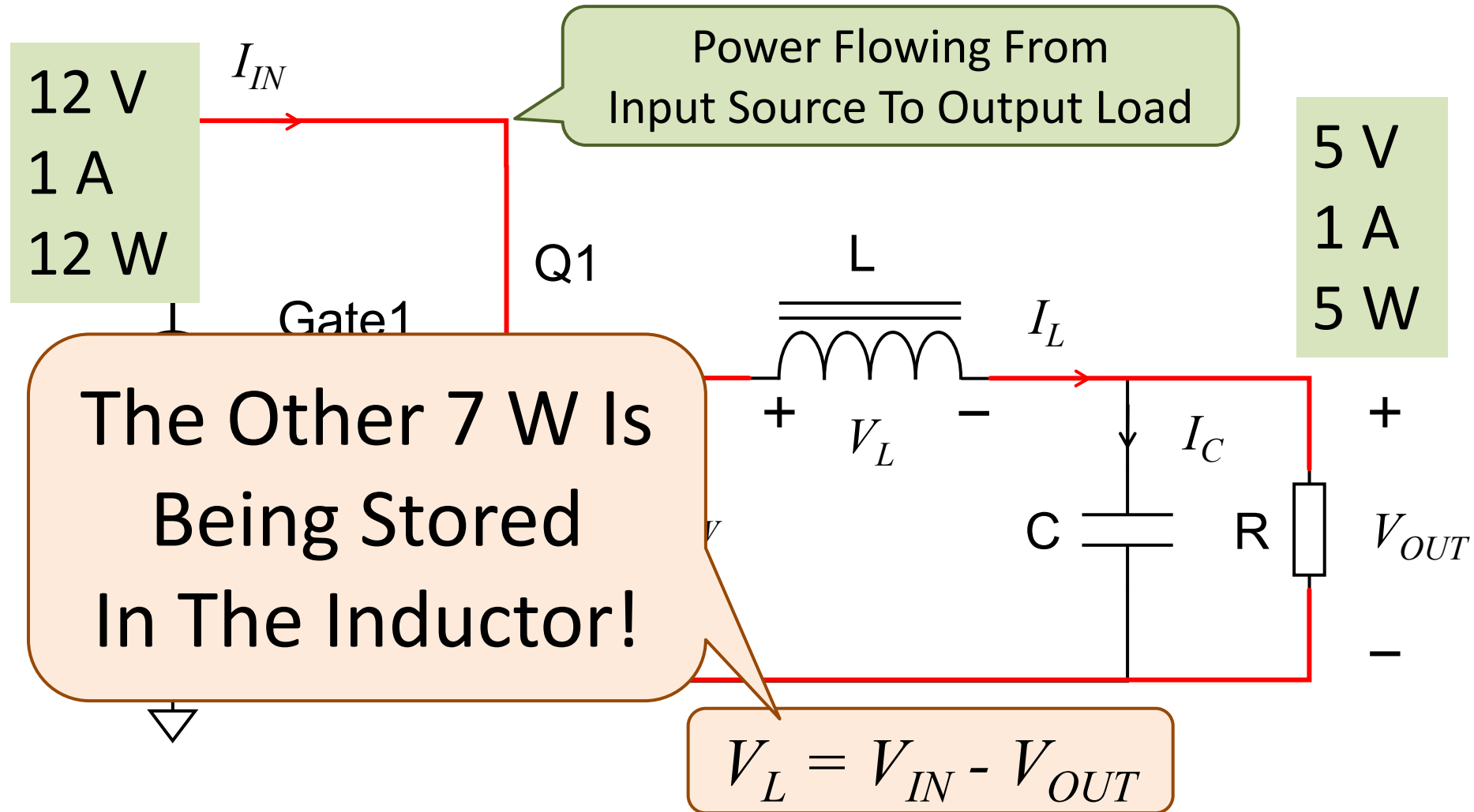

Buck Converter Off Time

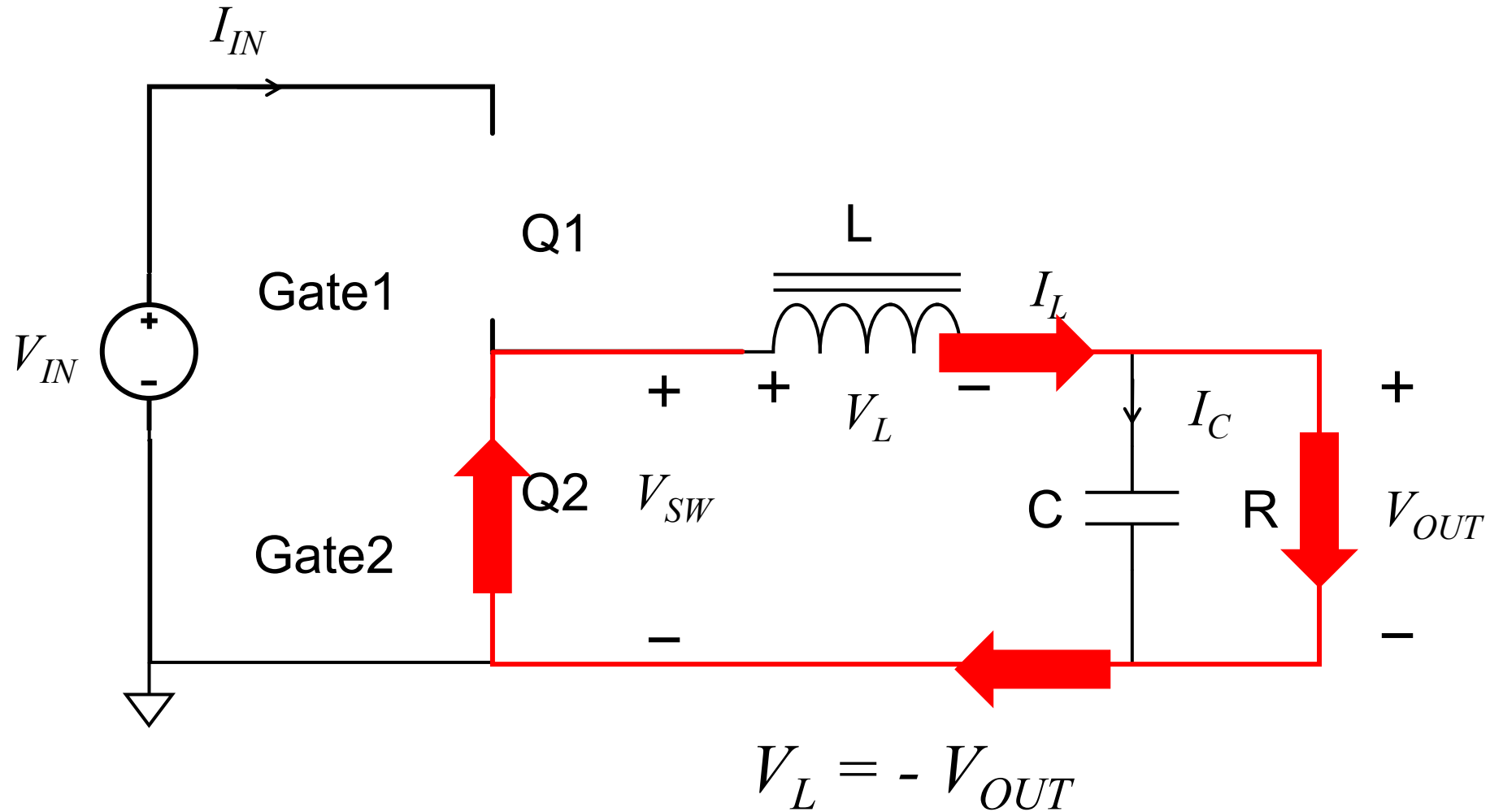


Buck Converter Off Time

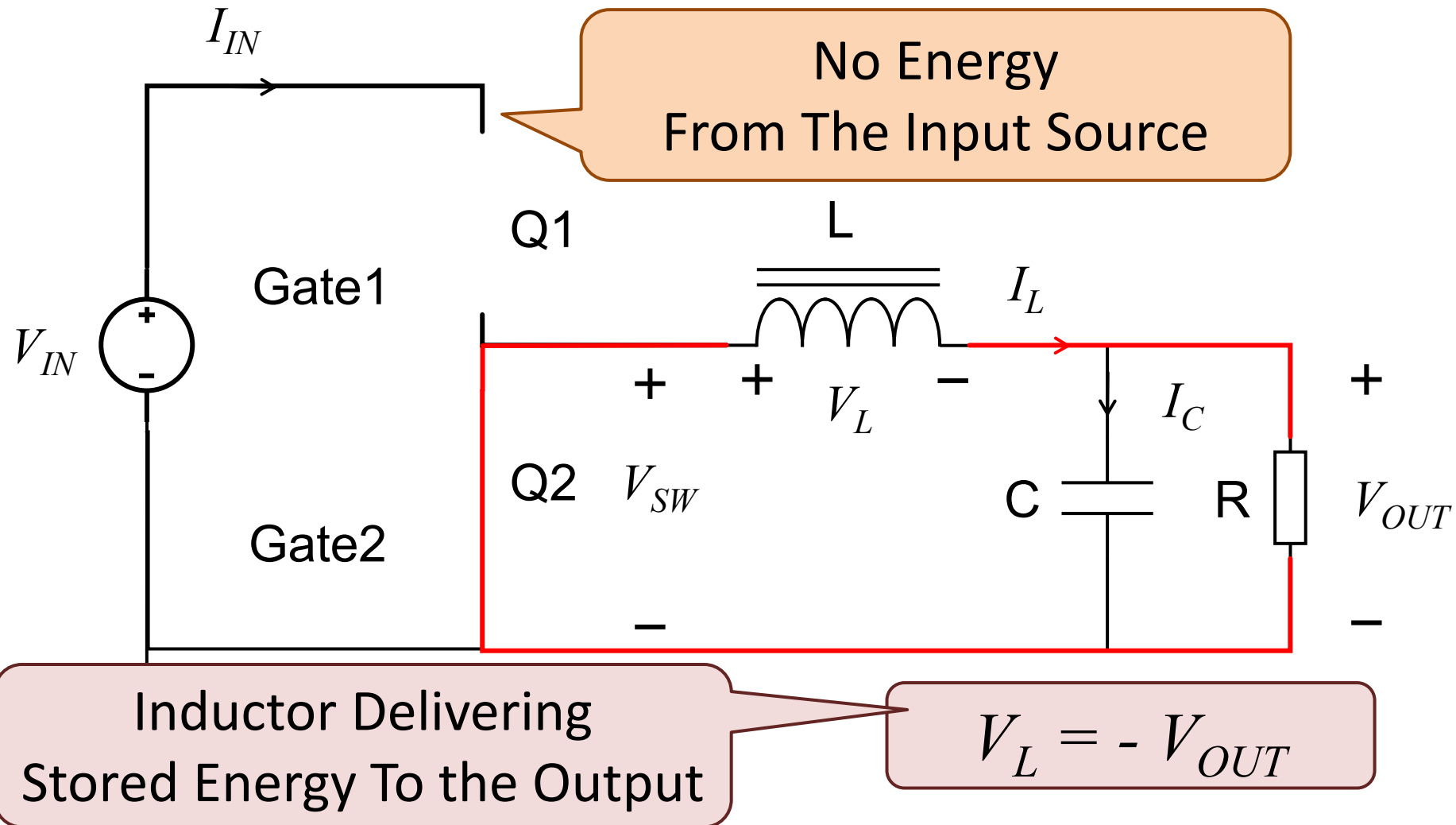


Buck Converter Energy Flow

On Time

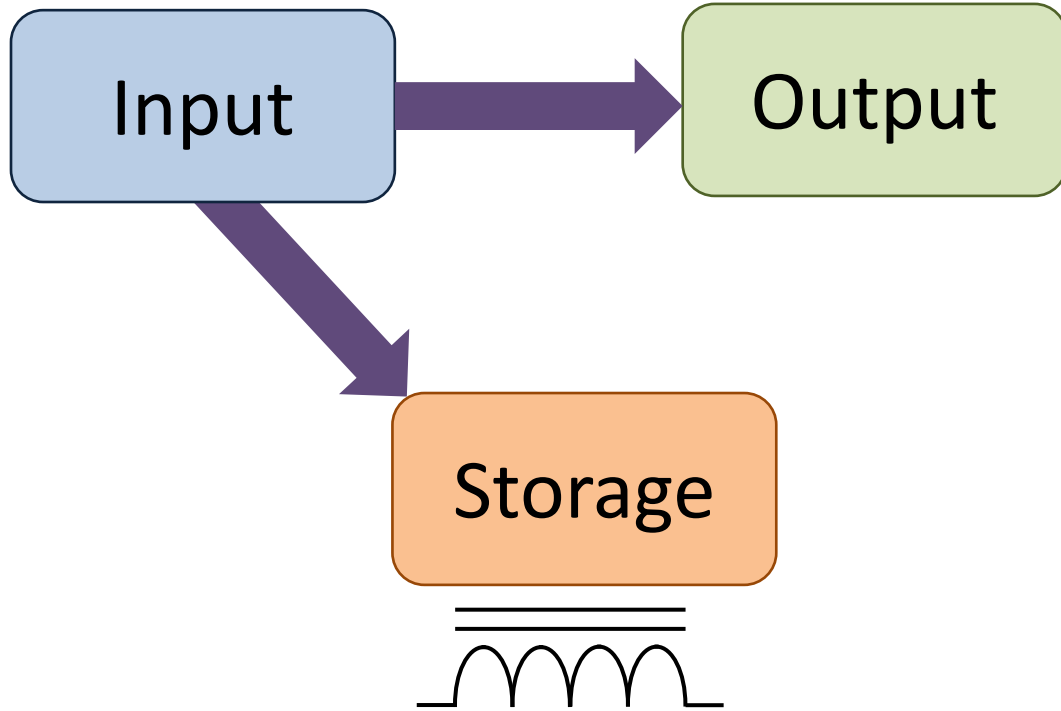


Off Time

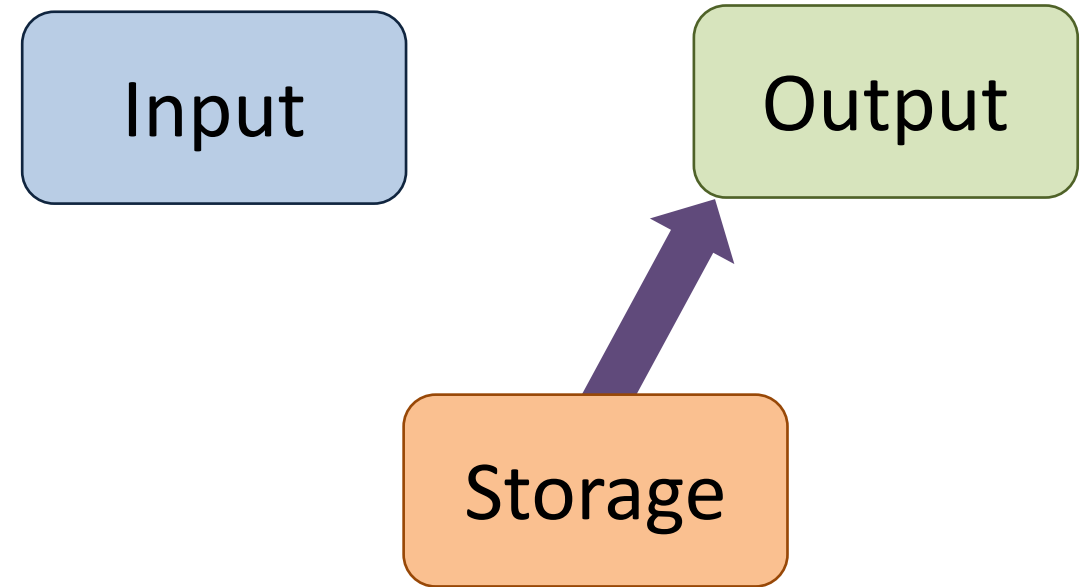

Buck Converter

Inductor Voltage And Current

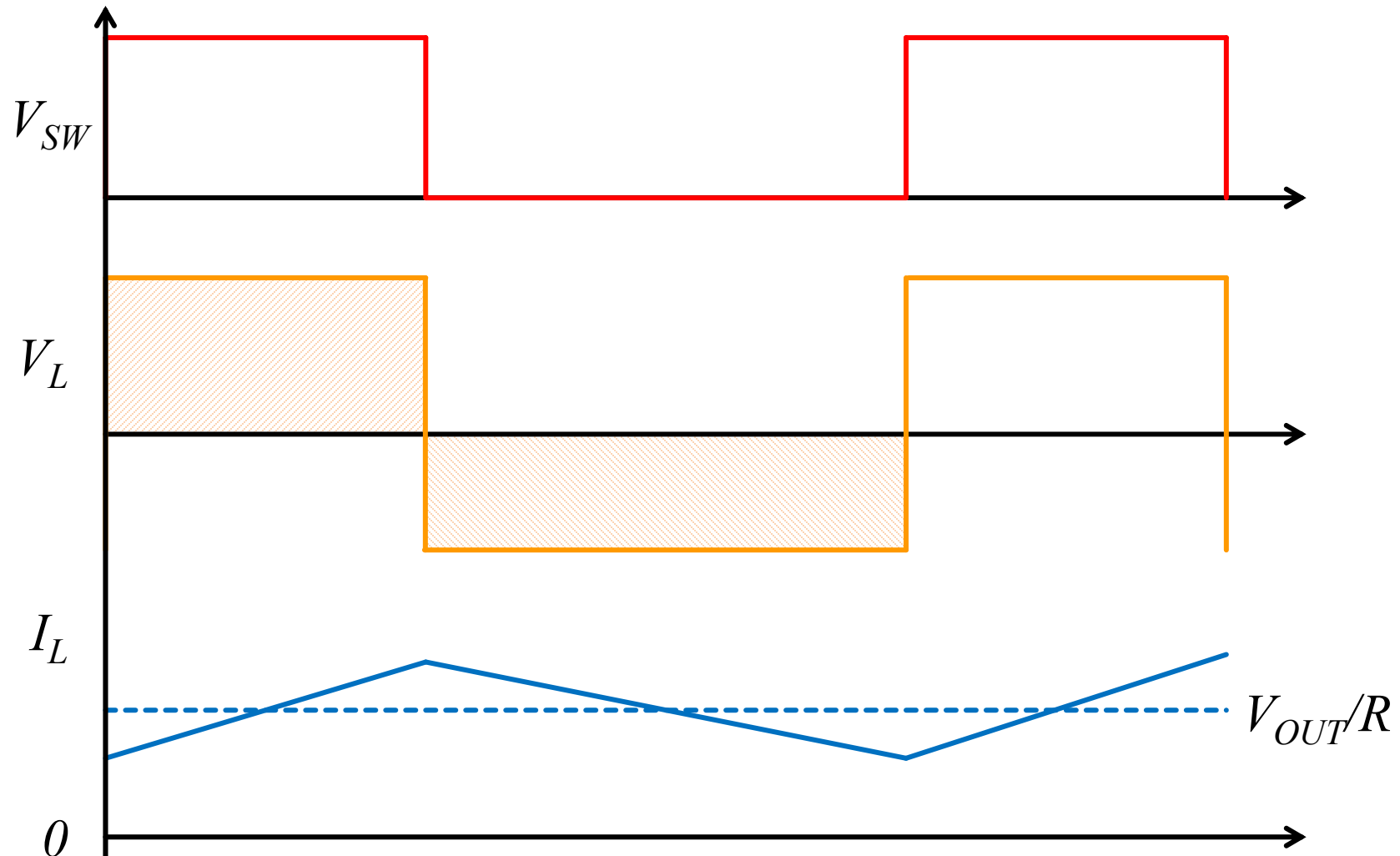

Inductor Volt-Second Balance

$$V_L(T_{ON}) \cdot T_{ON} + V_L(T_{OFF}) \cdot T_{OFF} = 0$$

$$(V_{IN} - V_{OUT}) \cdot T_{ON} + (-V_{OUT}) \cdot T_{OFF} = 0$$

$$(V_{IN} - V_{OUT}) \cdot D \cdot T_{SW} + (-V_{OUT}) \cdot (1 - D) \cdot T_{SW} = 0$$

$$(V_{IN} - V_{OUT}) \cdot D + (-V_{OUT}) \cdot (1 - D) = 0$$

$$D \cdot V_{IN} - D \cdot V_{OUT} - V_{OUT} + D \cdot V_{OUT} = 0$$

$$D \cdot V_{IN} - V_{OUT} = 0$$

$$V_{OUT} = D \cdot V_{IN}$$



Open Loop Buck Converter Waveforms


$F_{SW} = 100 \text{ kHz}$ $D = 25\%$ $V_{IN} = 12 \text{ V}$ $V_{OUT} = 3.0 \text{ V}$ $I_{LOAD} = 1 \text{ A}$ (Constant)

-  V_{SW}
-  I_L
-  V_{OUT}
-  PWM




Video Lab 2

Buck Converter Waveforms

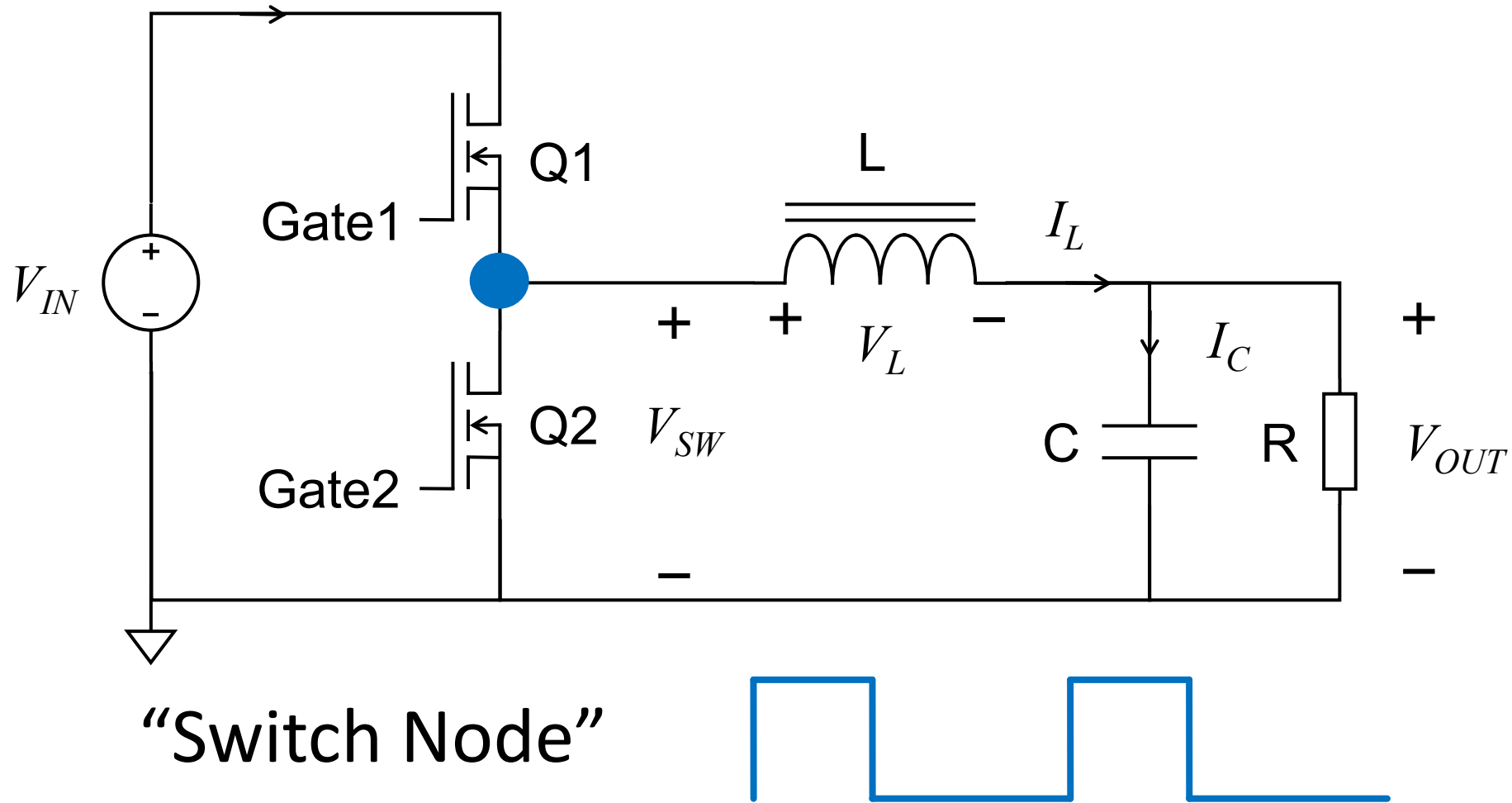


Buck Converter

Capacitor Current And Voltage

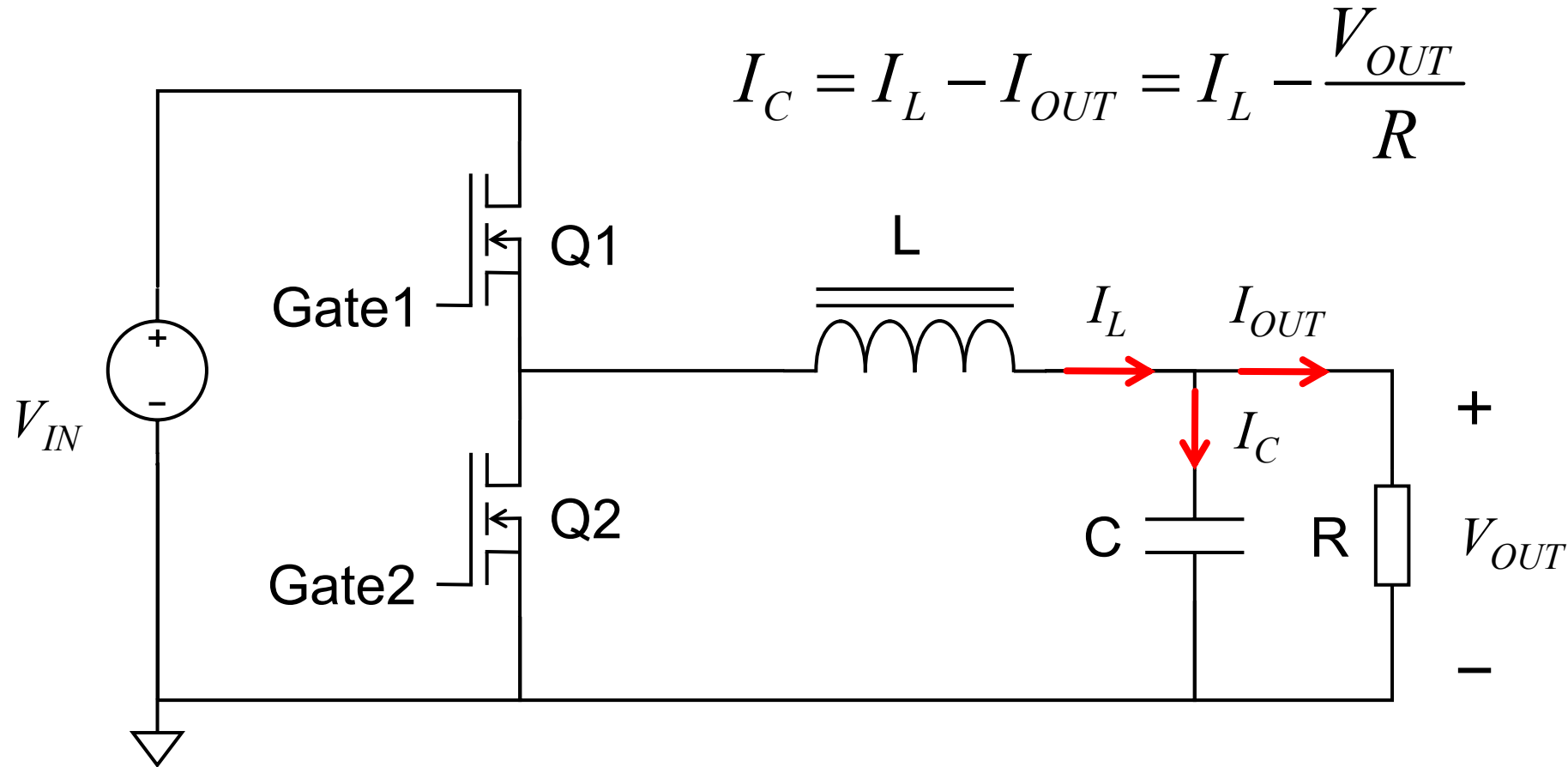


Buck Converter


Capacitor Current And Voltage

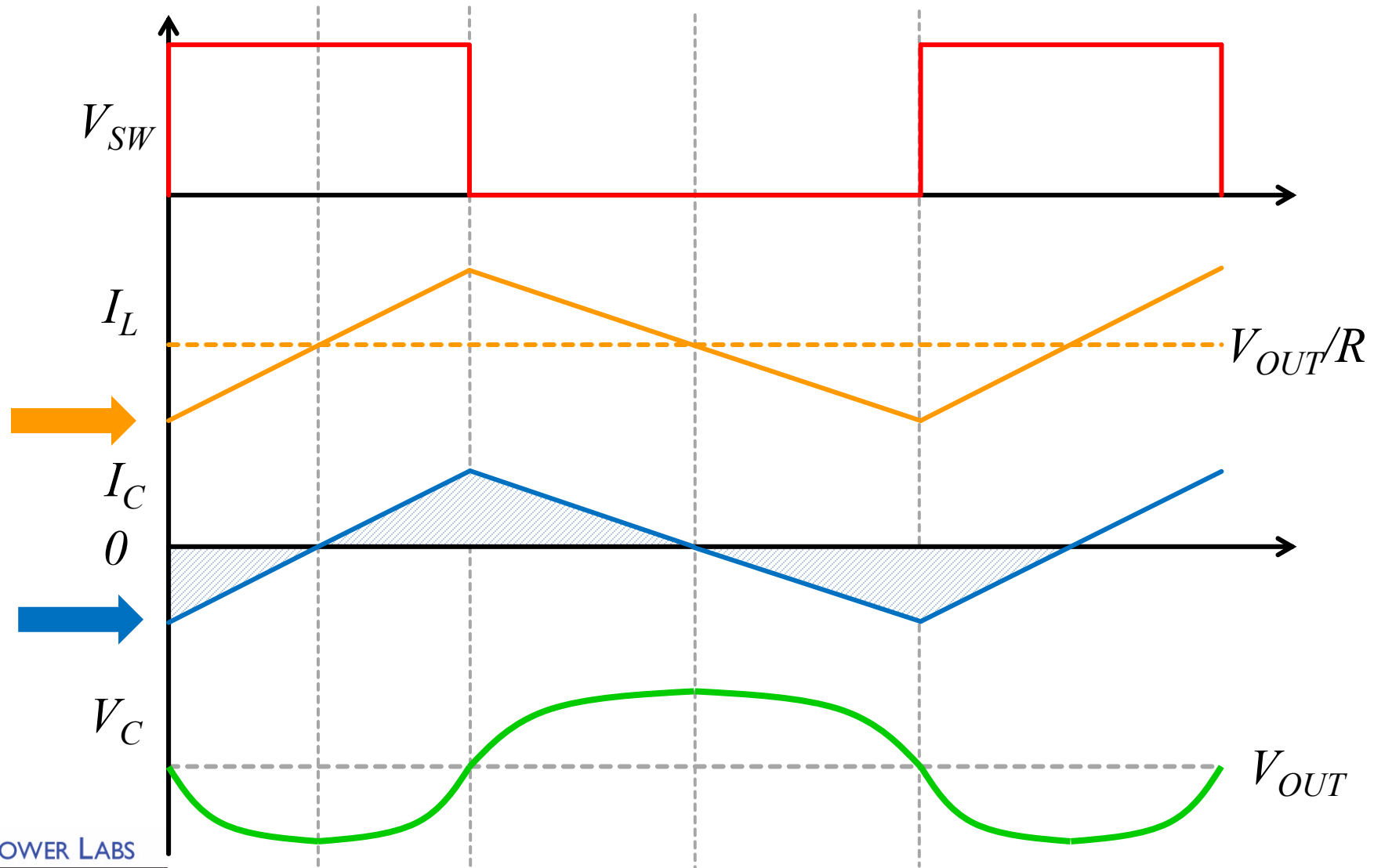

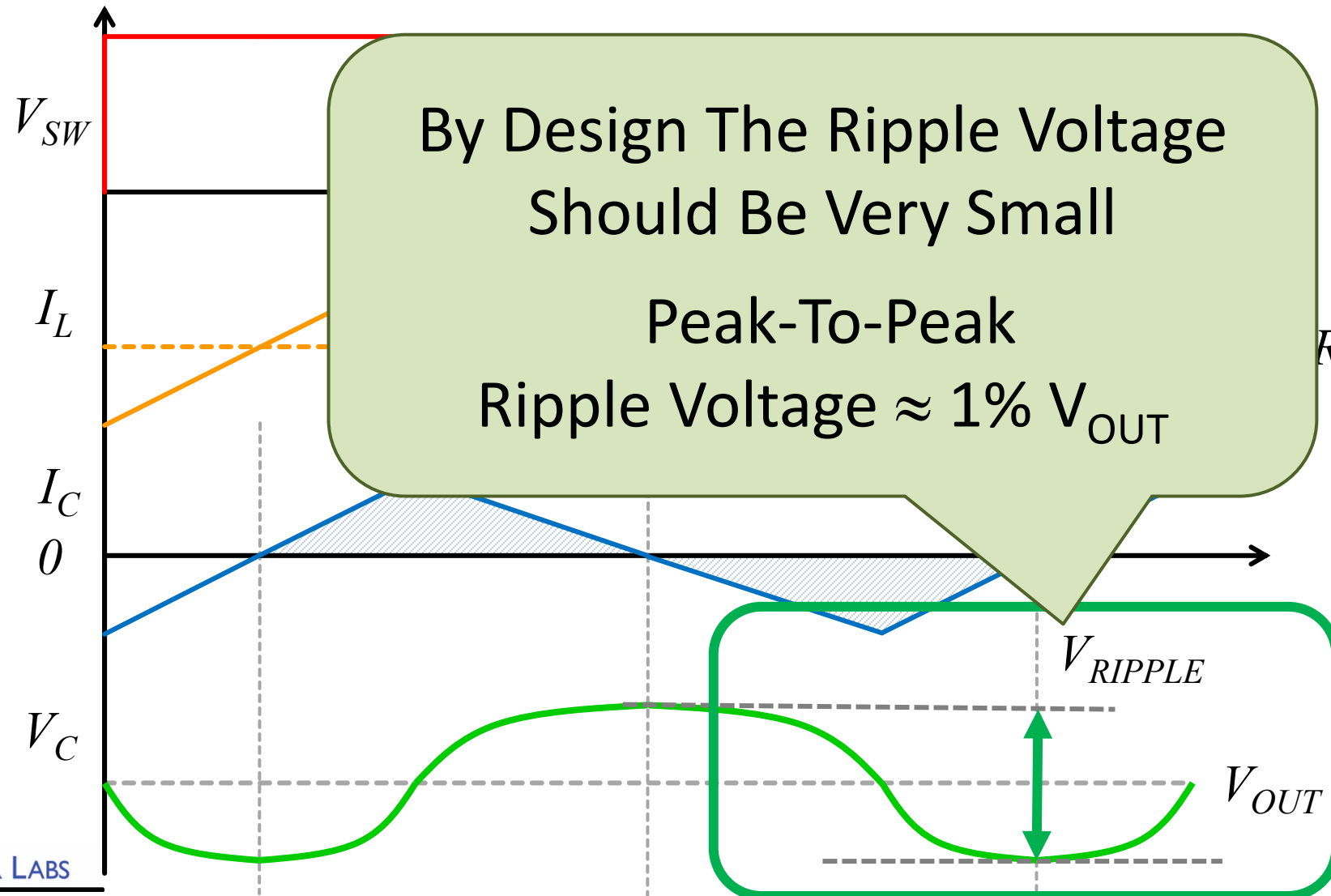Buck Converter Capacitor Current And Voltage



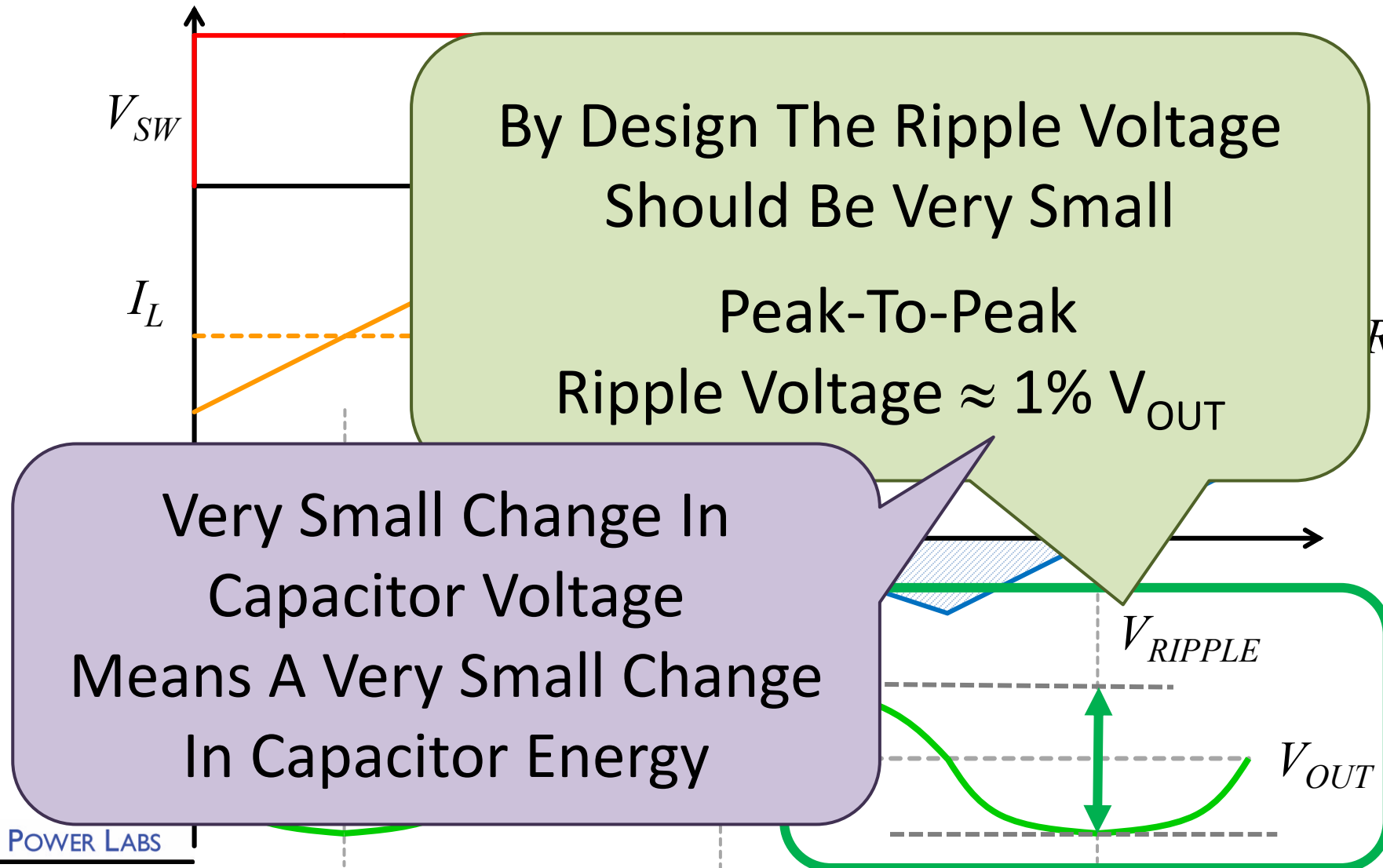Buck Converter Capacitor Current And Voltage



Capacitor Charge Balance

$$I_C(T_{ON}) \cdot T_{ON} + I_C(T_{OFF}) \cdot T_{OFF} = 0$$

$$I_C(T_{ON}) = I_L - \frac{V_{OUT}}{R}$$

$$I_C(T_{OFF}) = I_L - \frac{V_{OUT}}{R}$$


$$\left(I_L - \frac{V_{OUT}}{R} \right) \cdot T_{ON} + \left(I_L - \frac{V_{OUT}}{R} \right) \cdot T_{OFF} = 0$$

$$\left(I_L - \frac{V_{OUT}}{R} \right) \cdot T_{SW} = 0$$


$$I_L - \frac{V_{OUT}}{R} = 0$$

$$I_L = \frac{V_{OUT}}{R}$$

This Sets The Inductor Current Rating

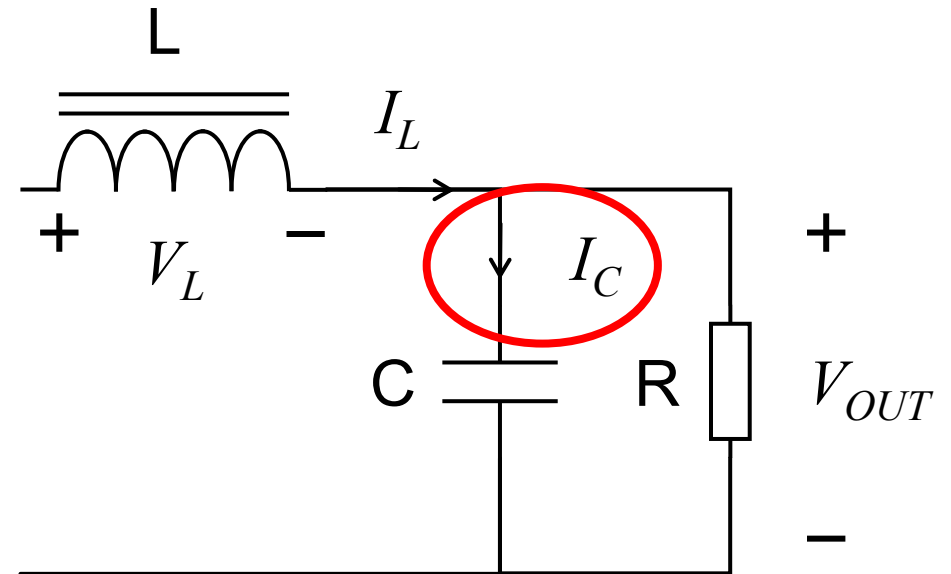

Buck Converter With Feedback

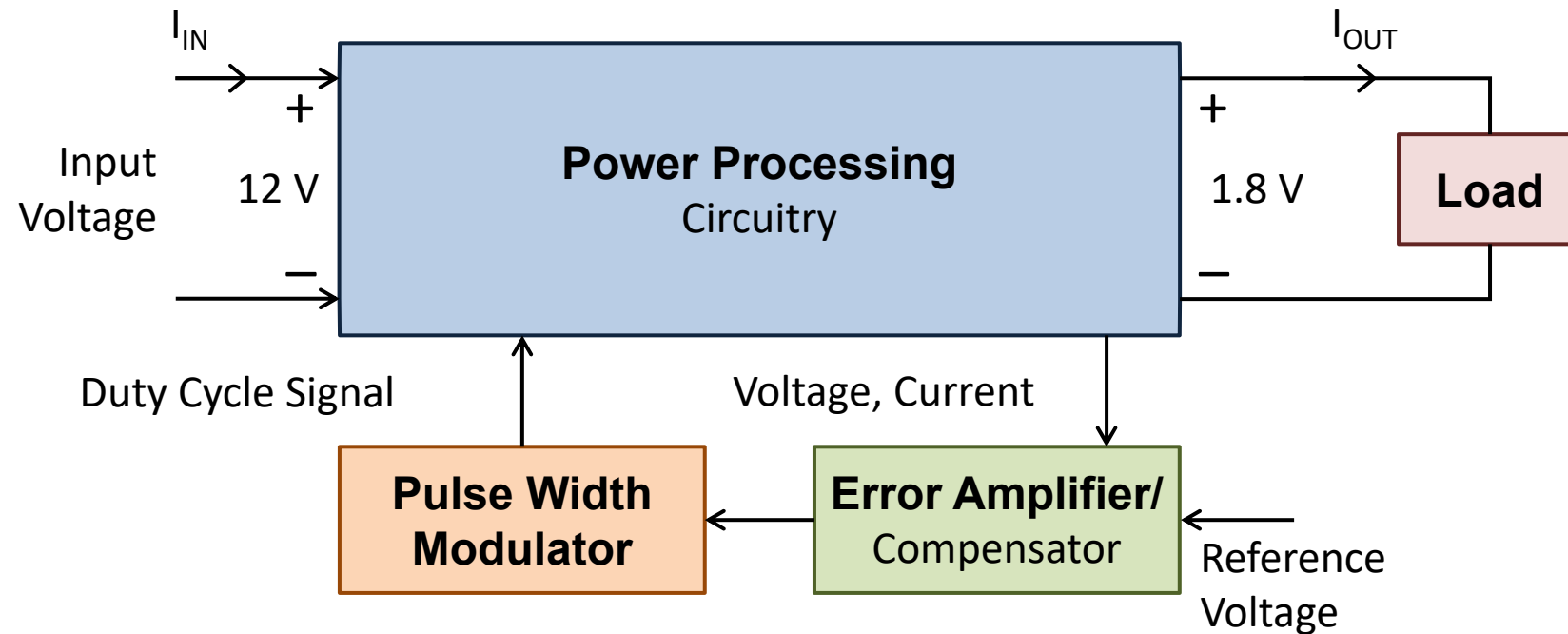


$$V_{OUT} = 1.8 \text{ V}$$

$$V_{IN} = 12 \text{ V}$$

$$I_{OUT} = 5 \text{ A}$$

Closed Loop Control:
Output Voltage Held Constant

Buck Converter With Feedback

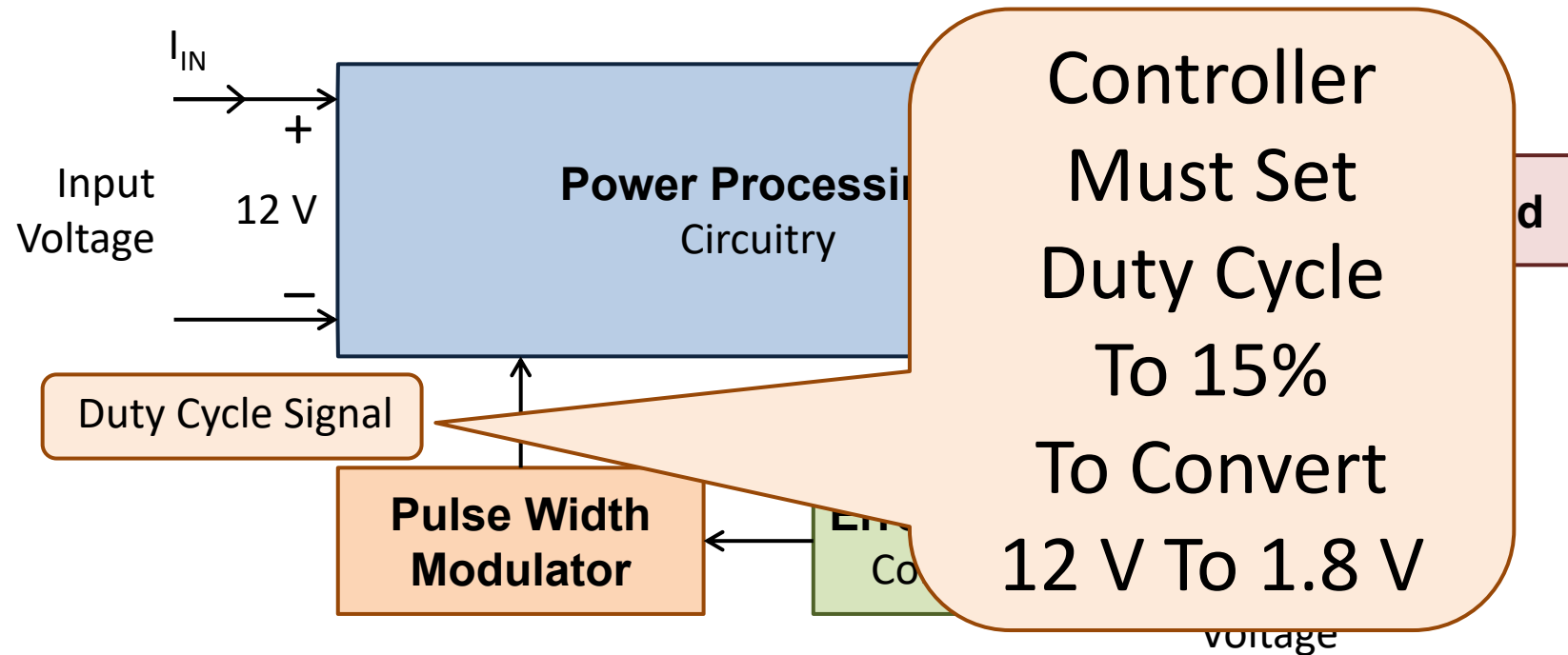

$$V_{OUT} = 1.8 \text{ V}$$


$$V_{IN} = 12 \text{ V}$$

$$I_{OUT} = 5 \text{ A}$$


$$V_{OUT} = D \cdot V_{IN}$$

$$D = \frac{V_{OUT}}{V_{IN}} = \frac{1.8 \text{ V}}{12 \text{ V}} = 0.15 = 15\%$$

Buck Converter With Feedback

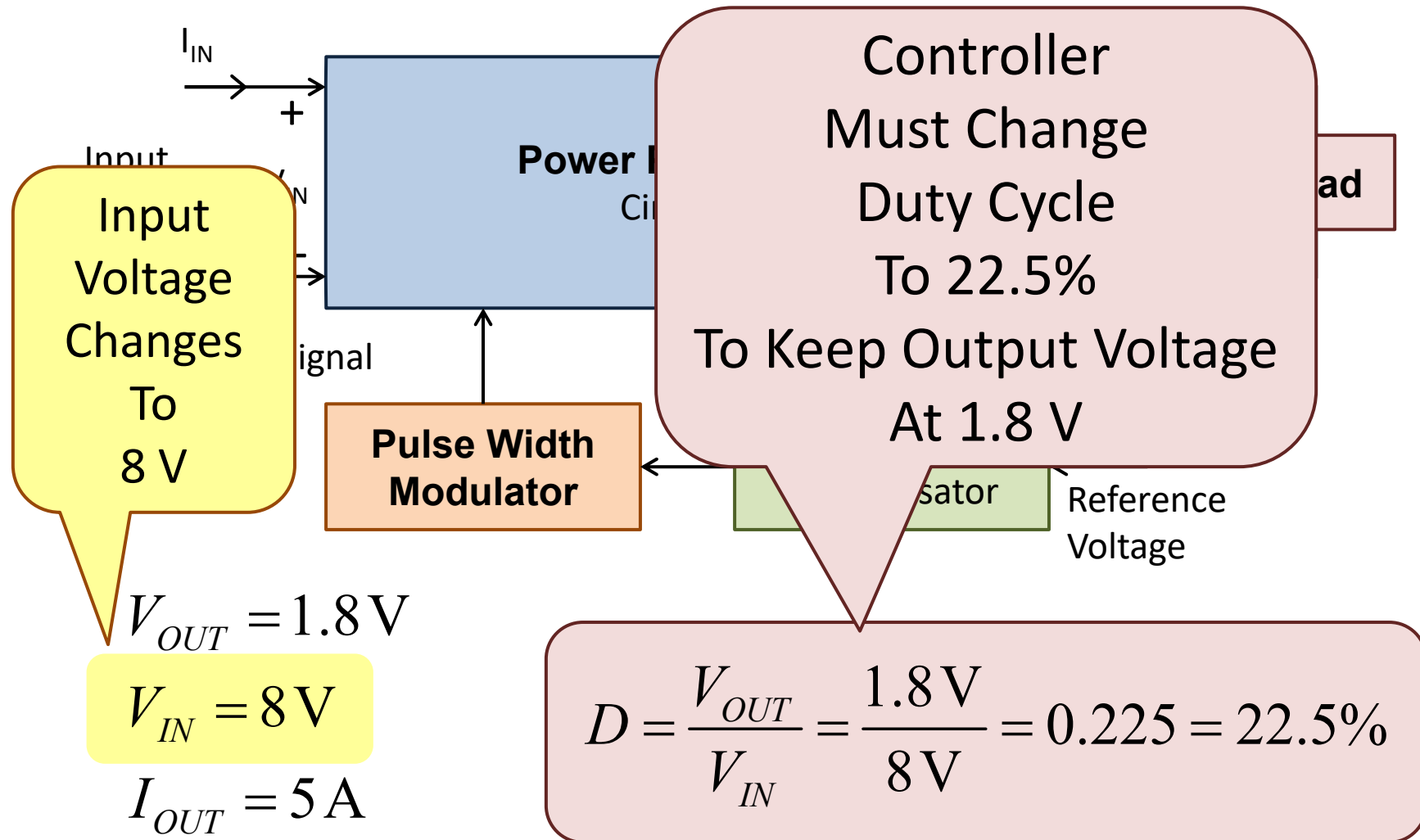

Buck Converter With Feedback

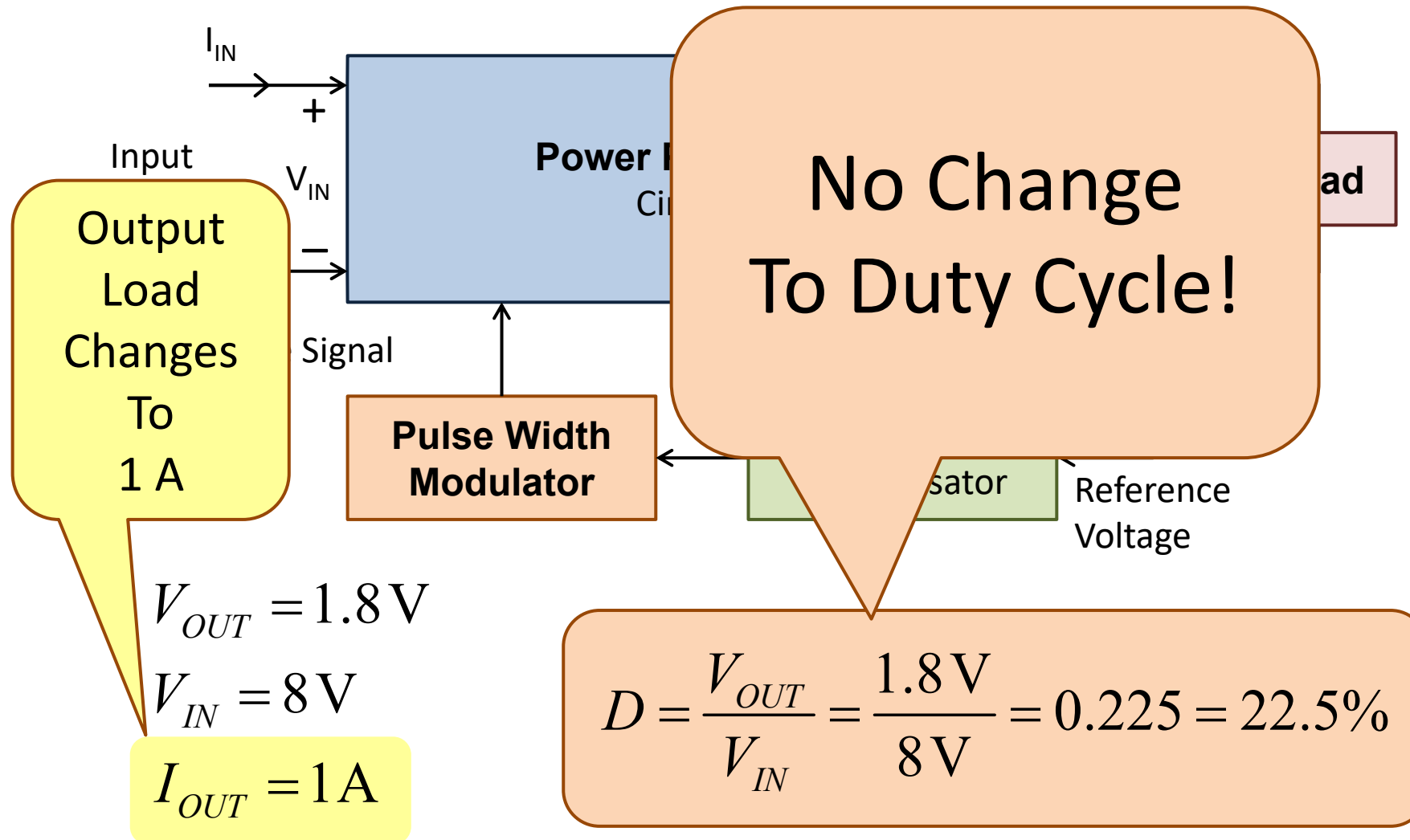

Buck Converter With Feedback

Not Exactly True
Duty Cycle Changes
To Compensate
For Changes In Losses

See Example
In Appendix I

e
le!

ad

erence
age


$$25 = 22.5\%$$

In
ou
L
Cha


$$I_{OUT} = I_{IN}$$

Video Lab 3


Buck Converter With Feedback

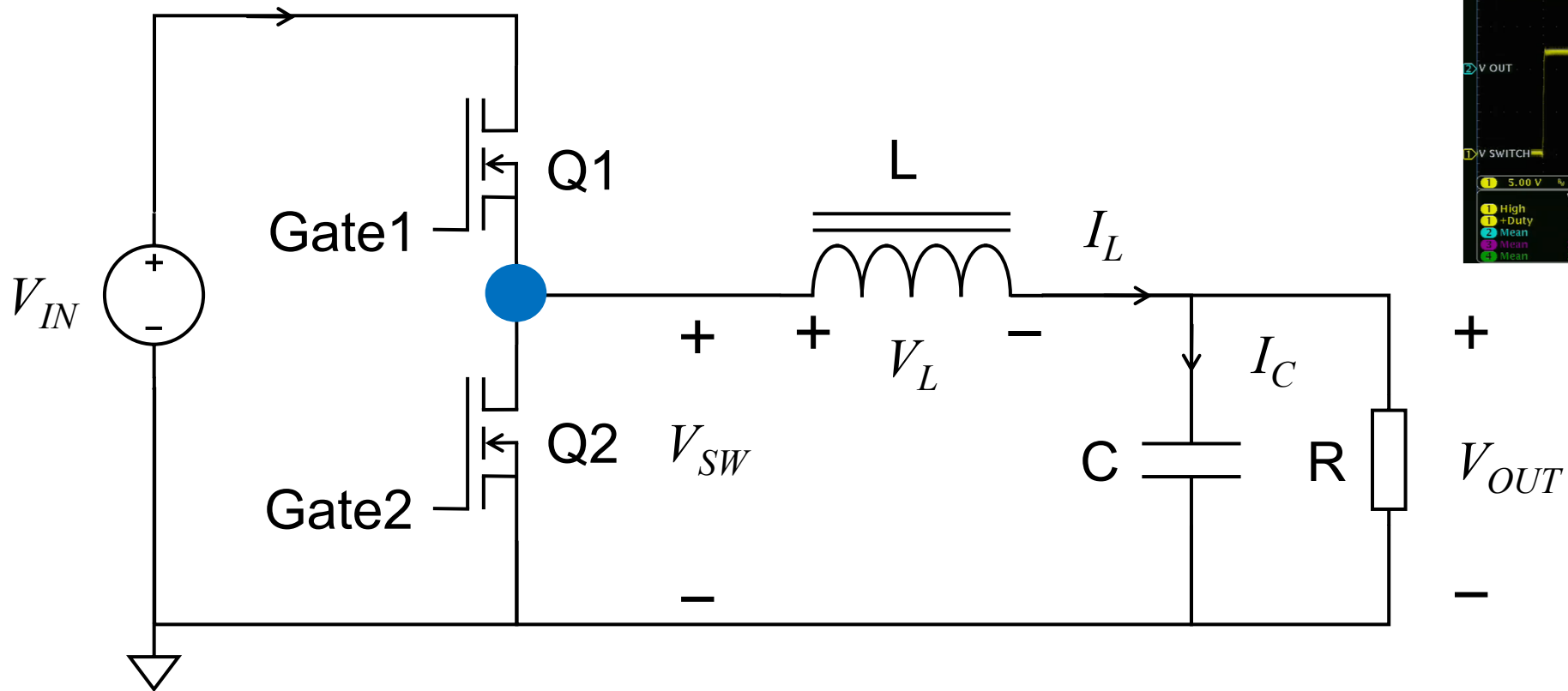


“Switch Node”

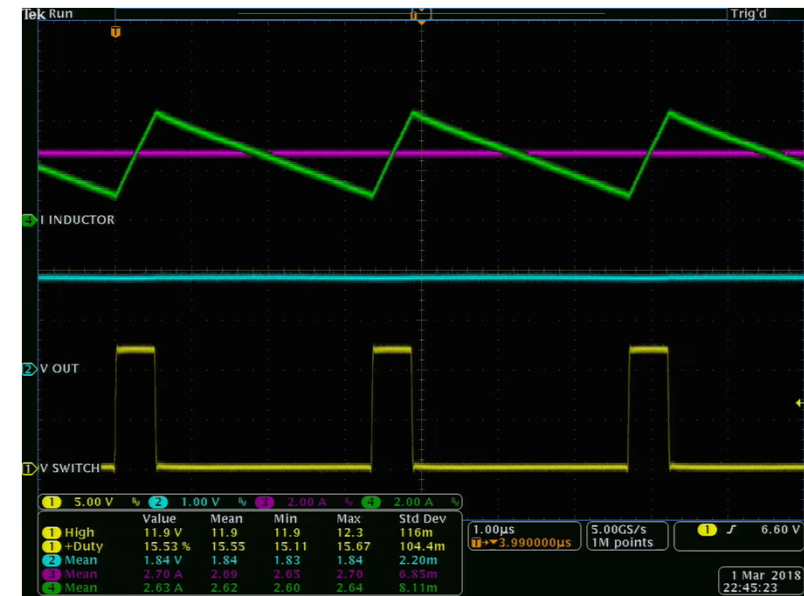

Discontinuous Conduction Mode (DCM)

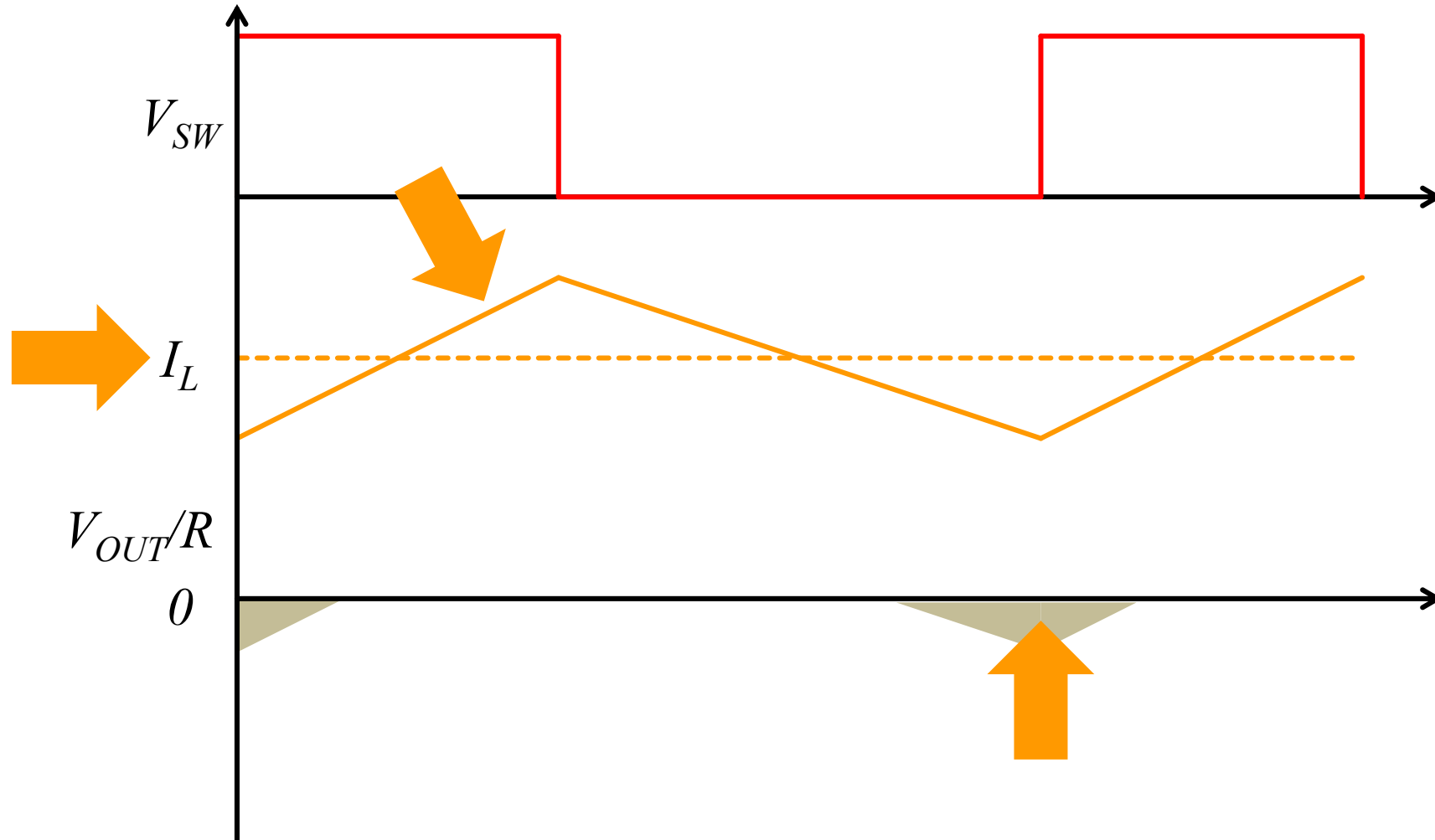


Discontinuous Conduction Mode (DCM)

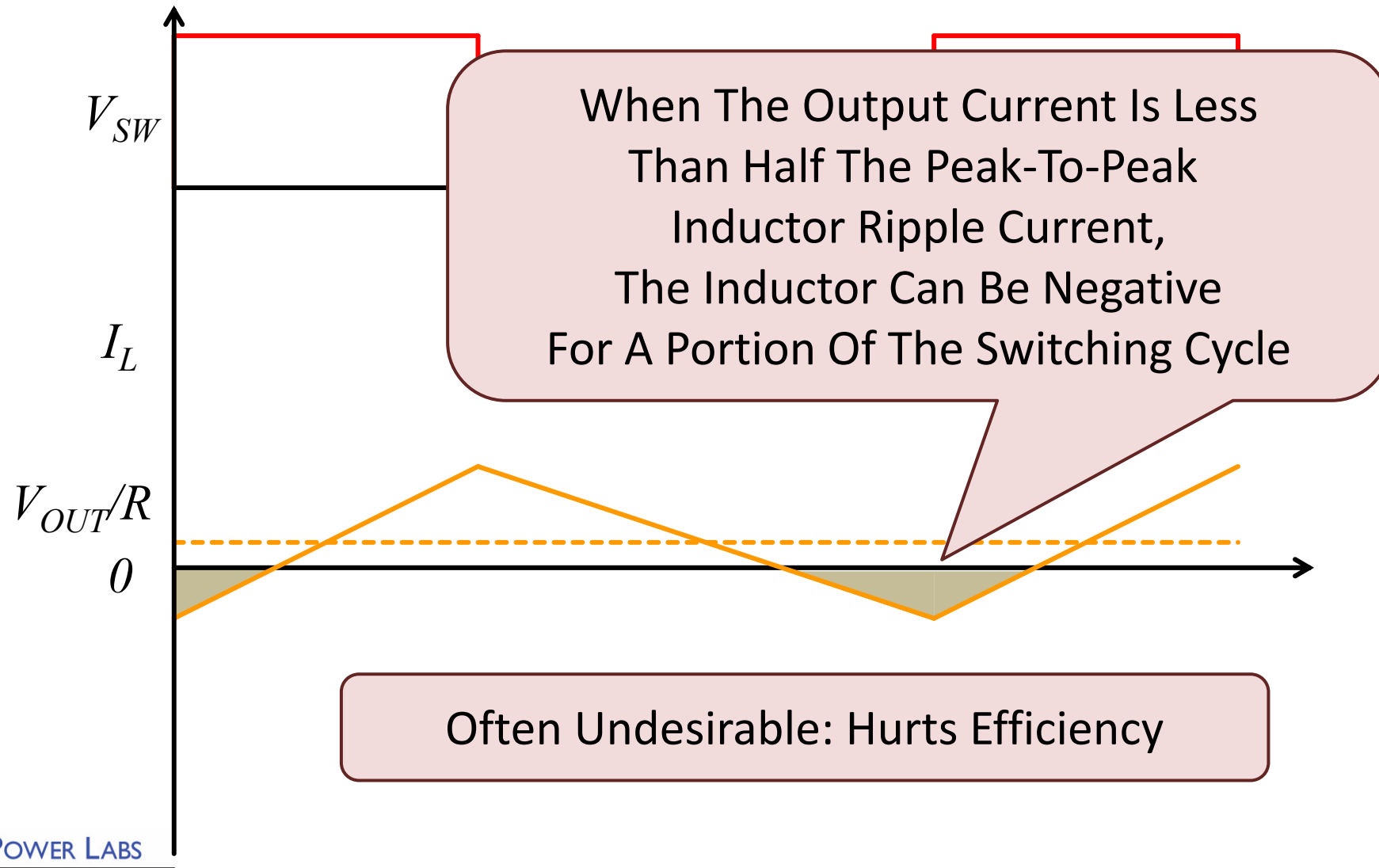

Video Lab 4

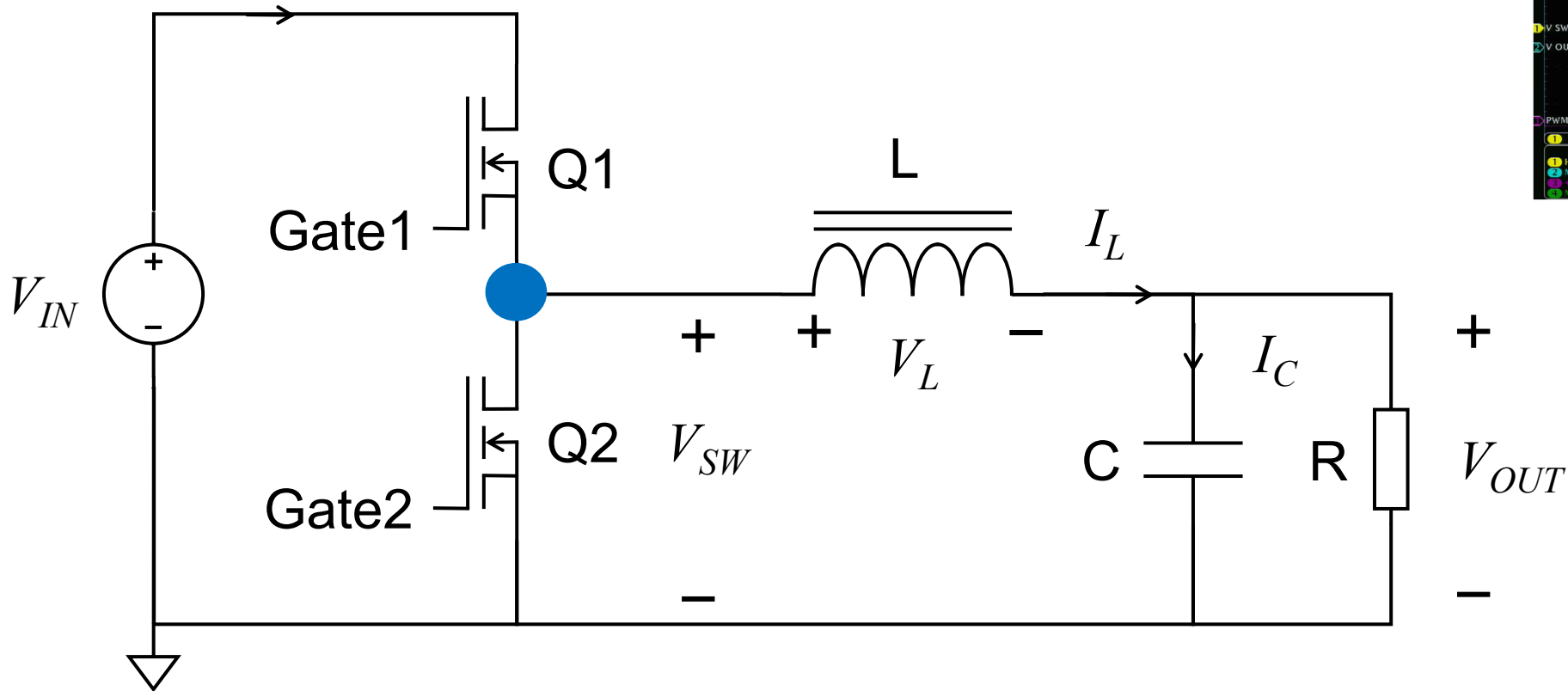
Buck Converter: Negative Inductor Current




“Switch Node”




Discontinuous Conduction Mode (DCM)

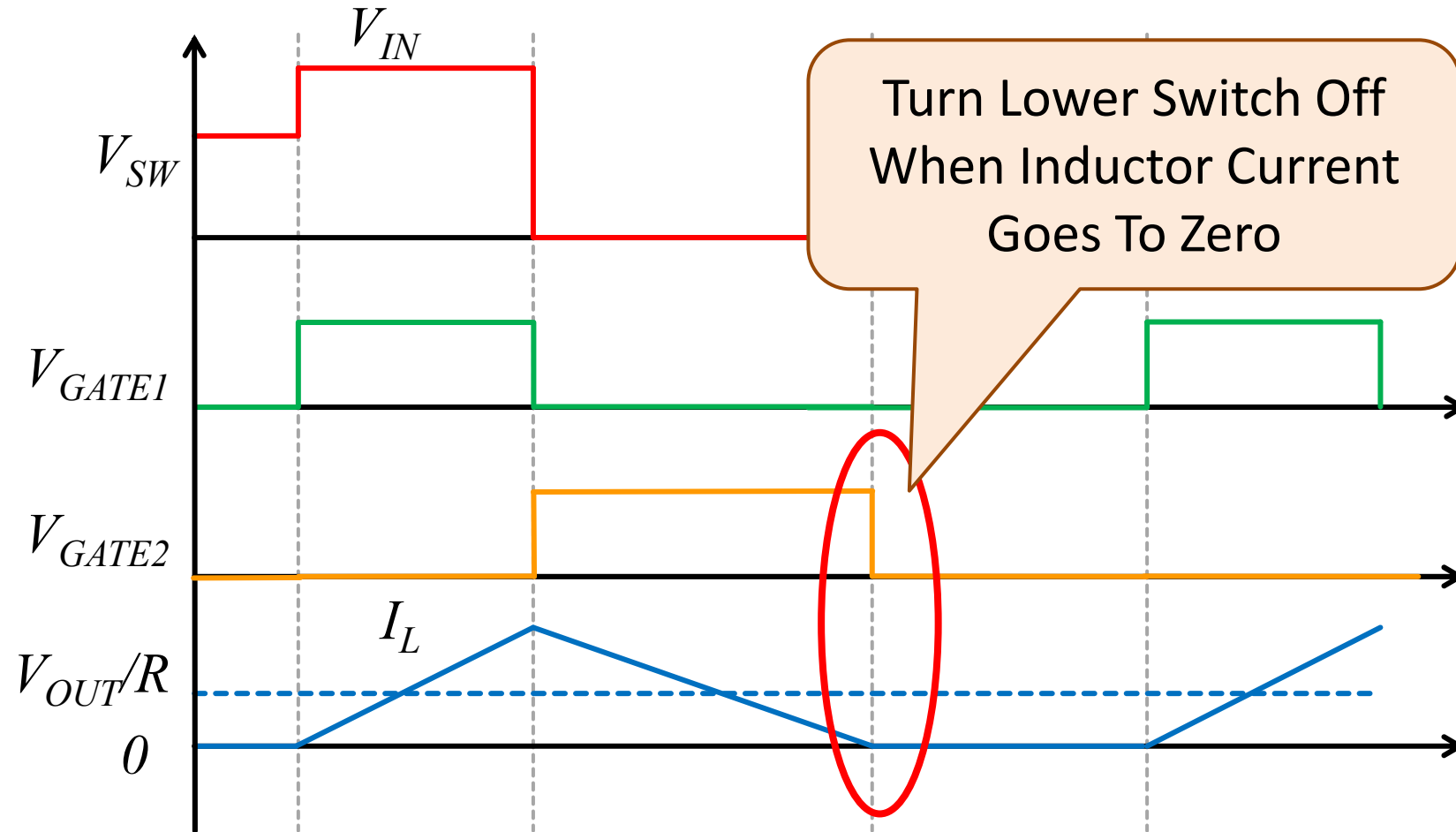


DCM Buck Converter On Time

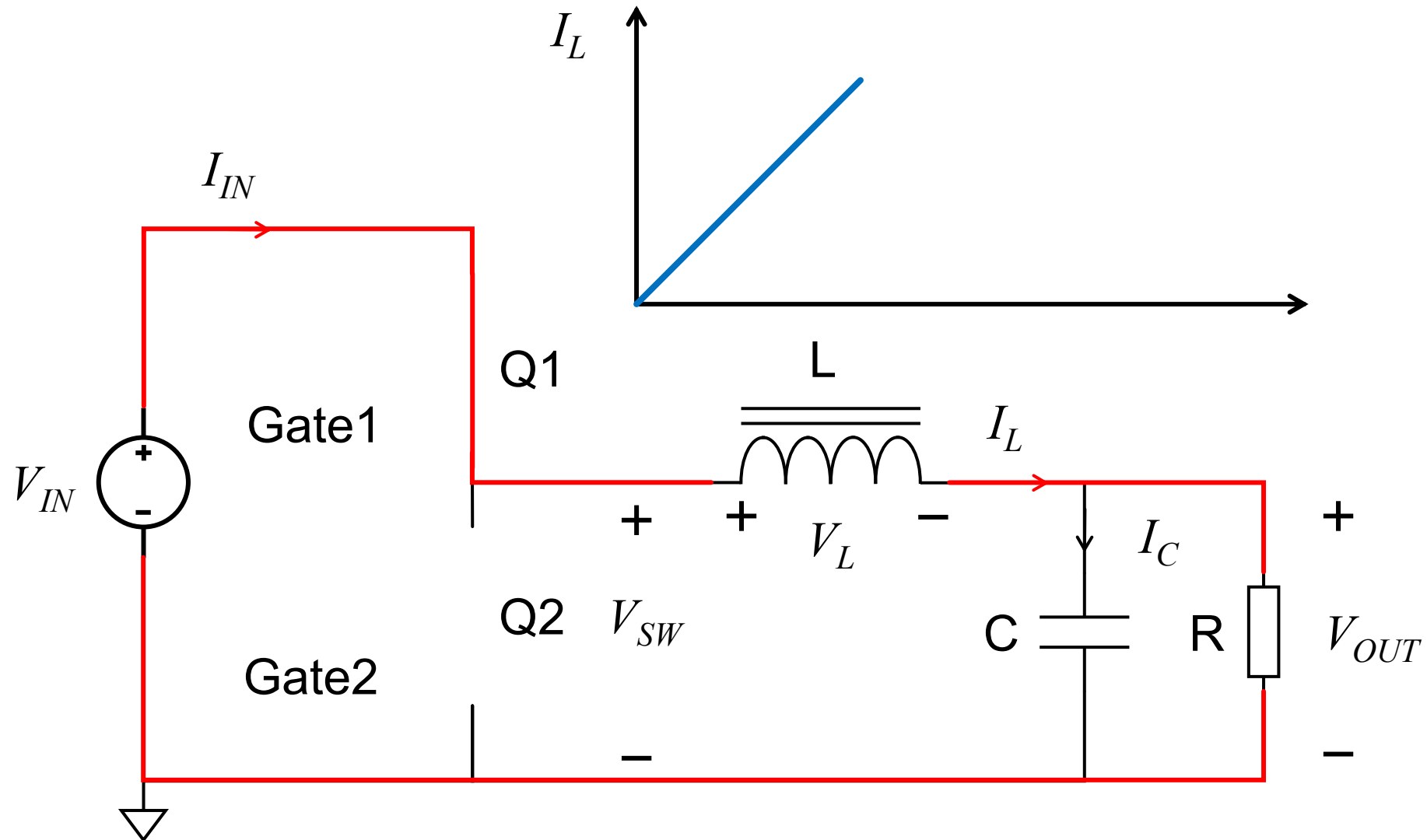


DCM Buck Converter Off Time

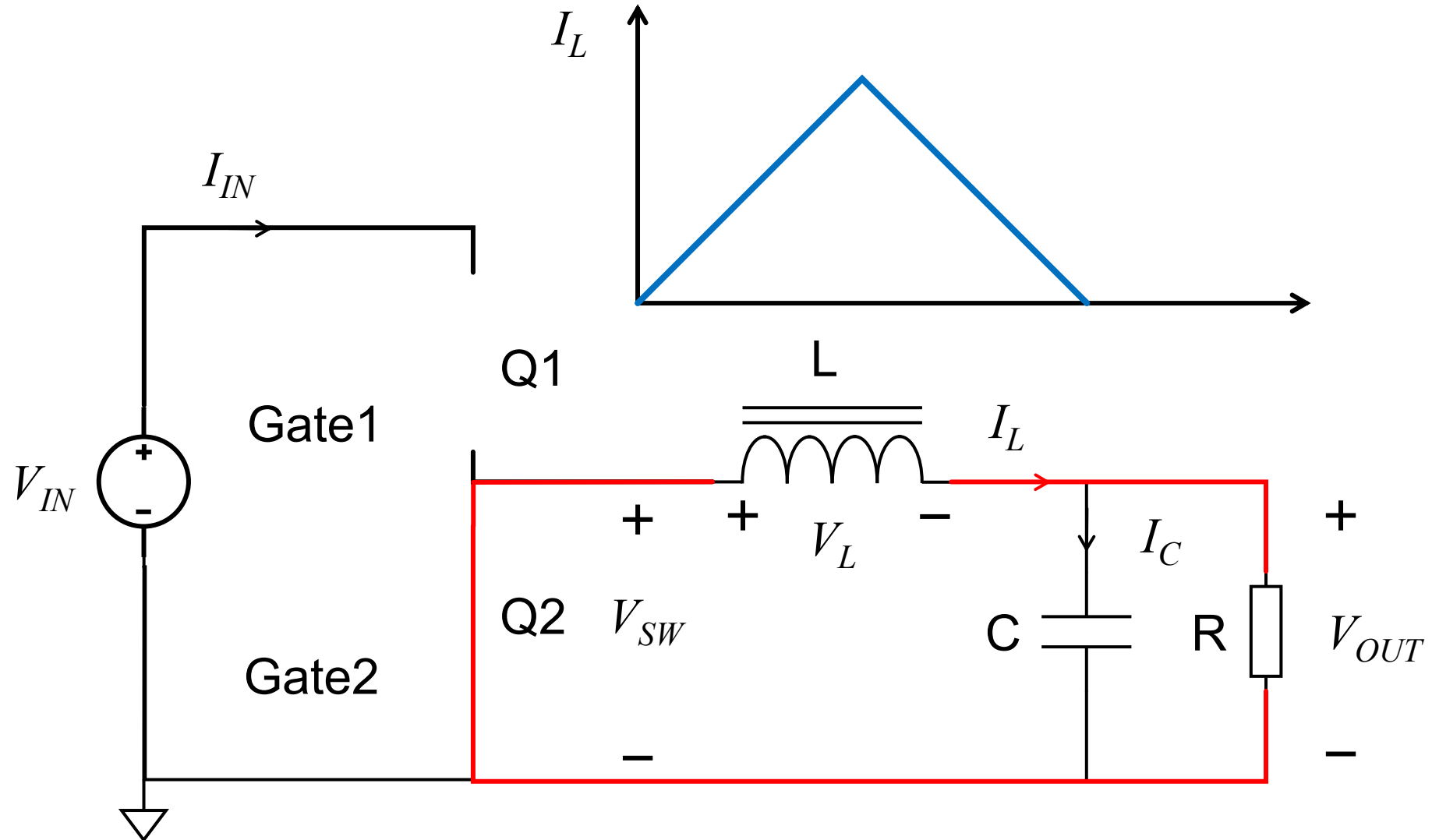

Buck Converter Idle Time

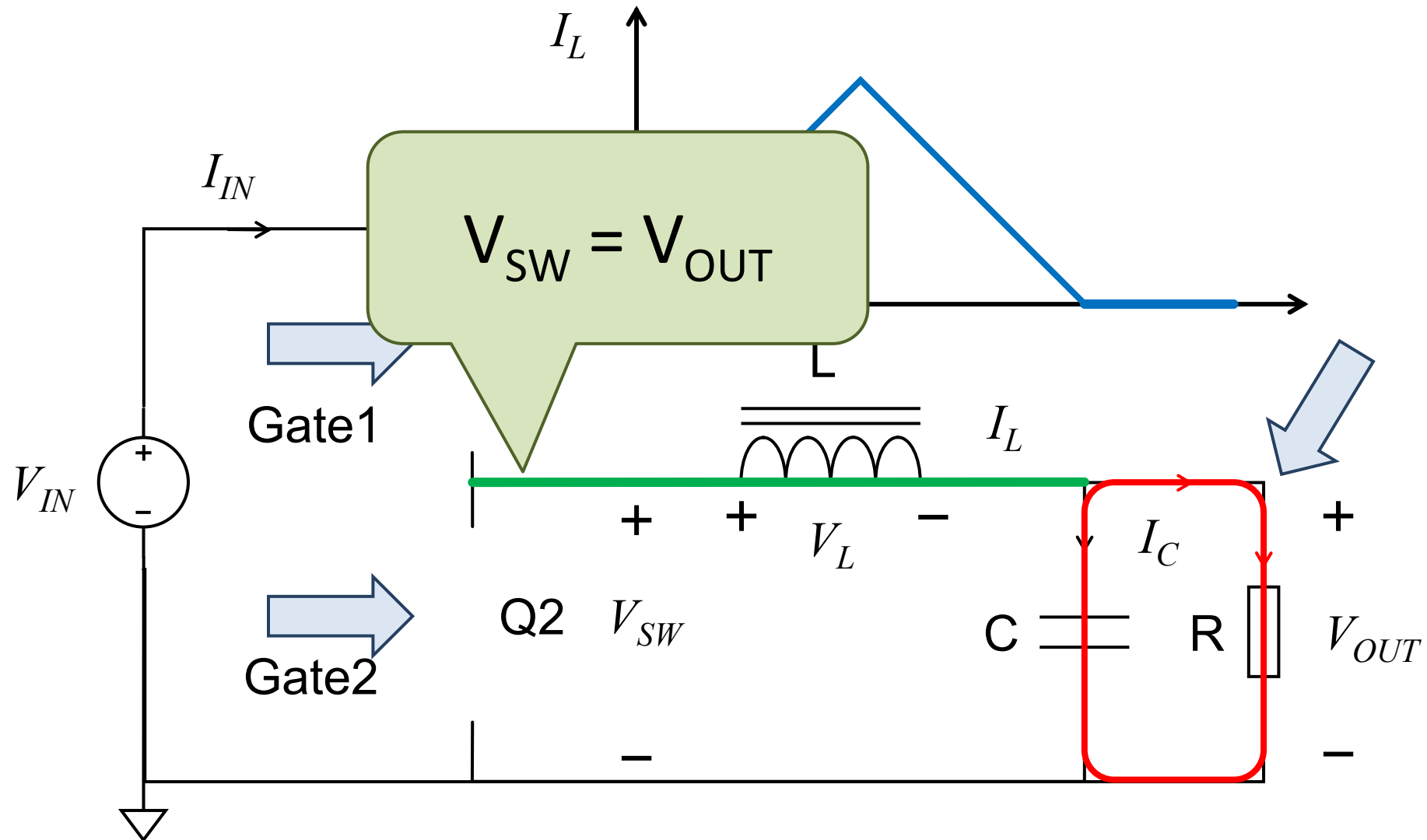


Discontinuous Conduction Mode (DCM)

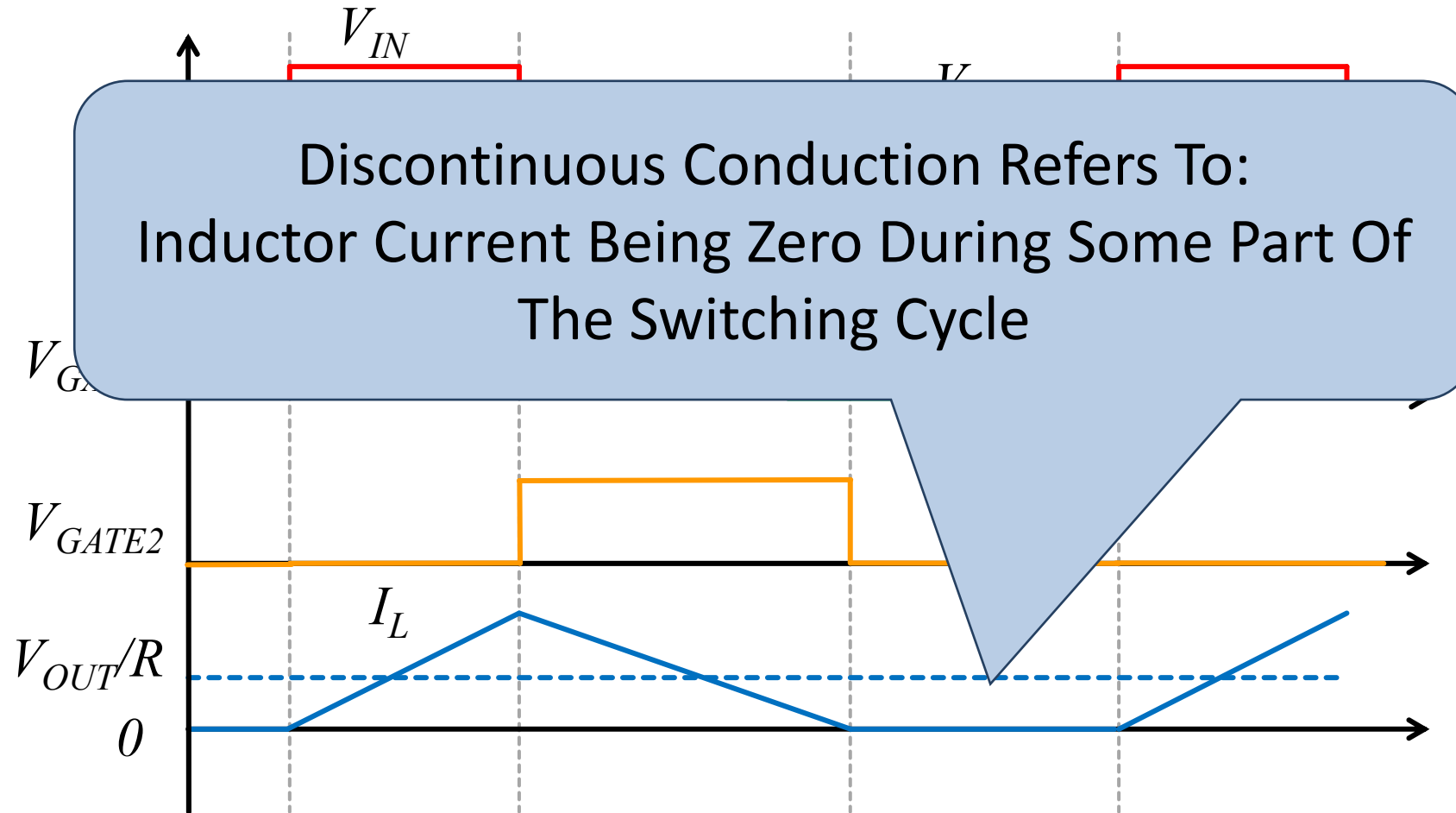

Buck DCM Waveforms




Buck DCM Waveforms

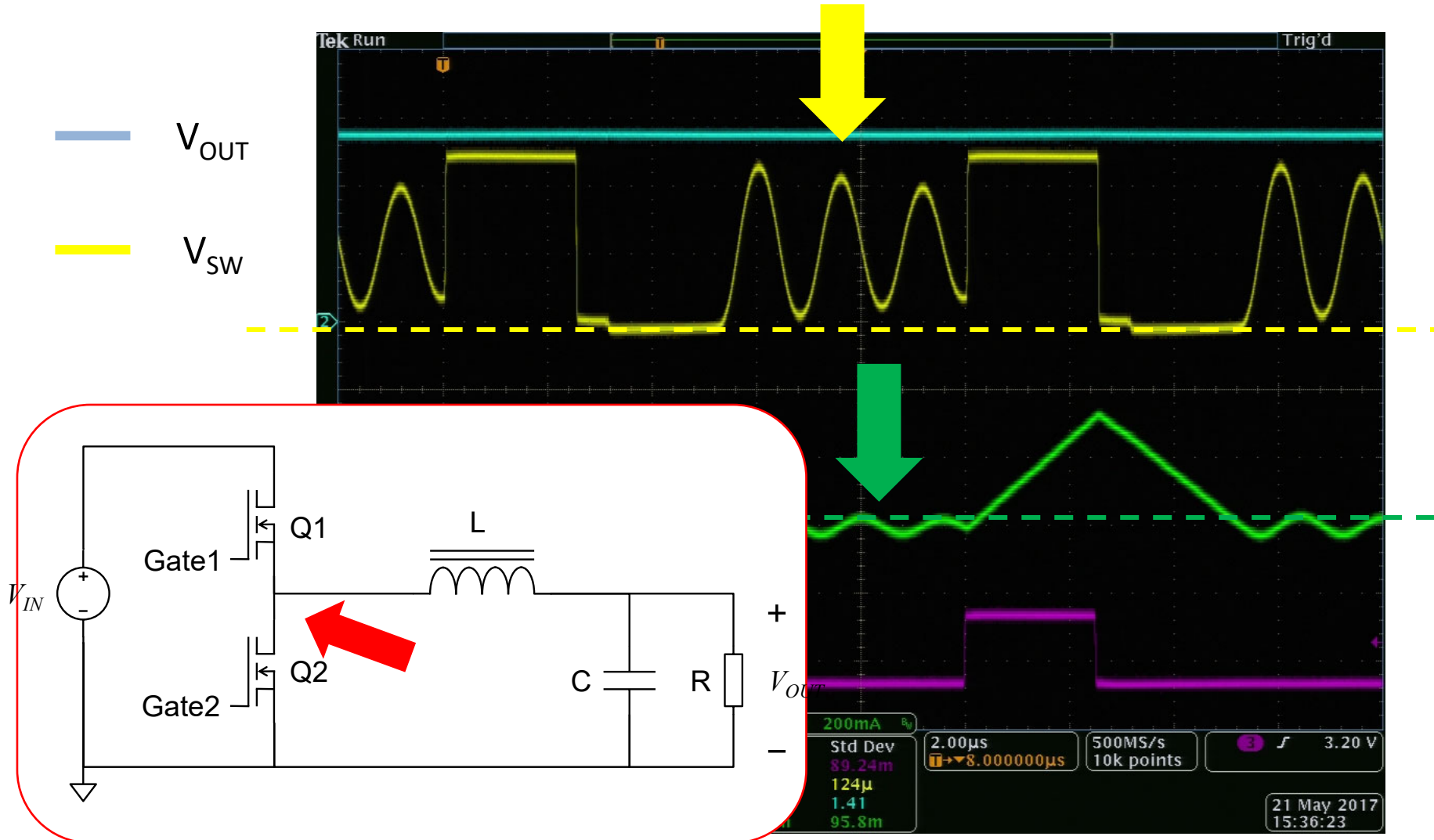

Video Lab 5

Buck Converter Waveforms: DCM

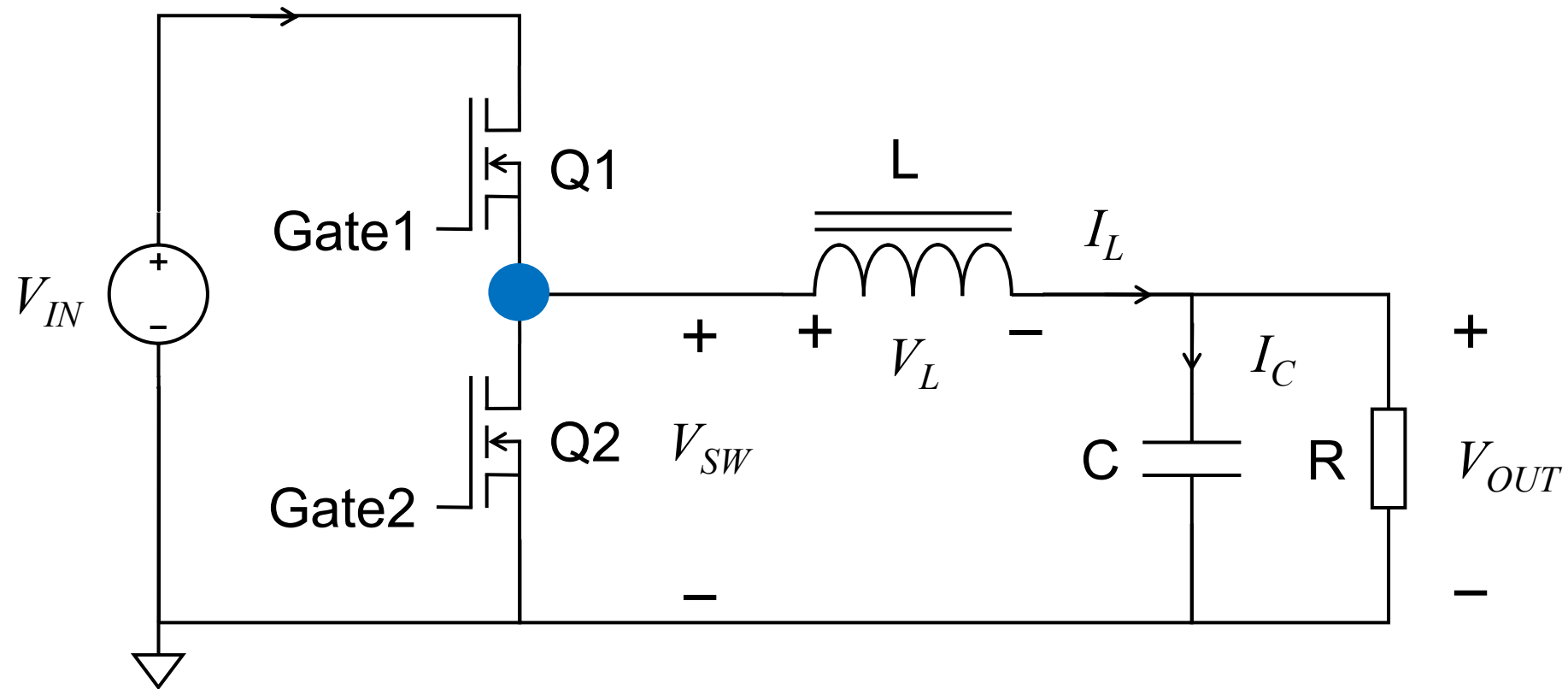

“Switch Node”



Buck DCM Waveforms



Gate Drive IC
Detects
Negative
Sync Switch
Current And
Turns Off The
Sync Switch

Conversion Characteristic

- For Buck Converter Operating In Discontinuous Conduction Mode (DCM):


$$V_{OUT} = \frac{2}{1 + \sqrt{1 + \frac{4}{D^2} \cdot \frac{2 \cdot L}{R \cdot T_{SW}}}} \cdot V_{IN}$$

Derivation
In Appendix


Nonlinear
With Duty Cycle

Dependent On
Load Resistance


Buck Converter w/Diode

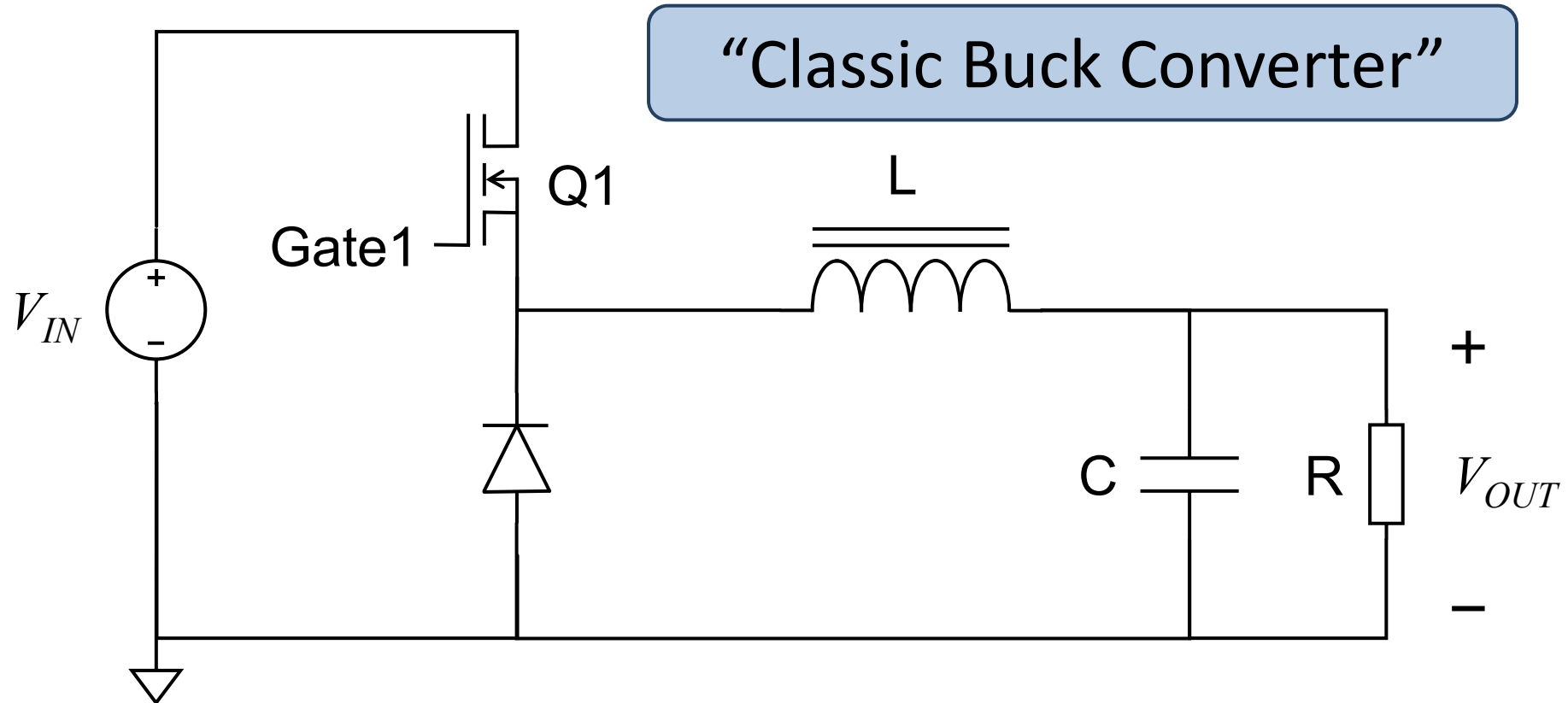

Buck Converter w/Diode: On Time

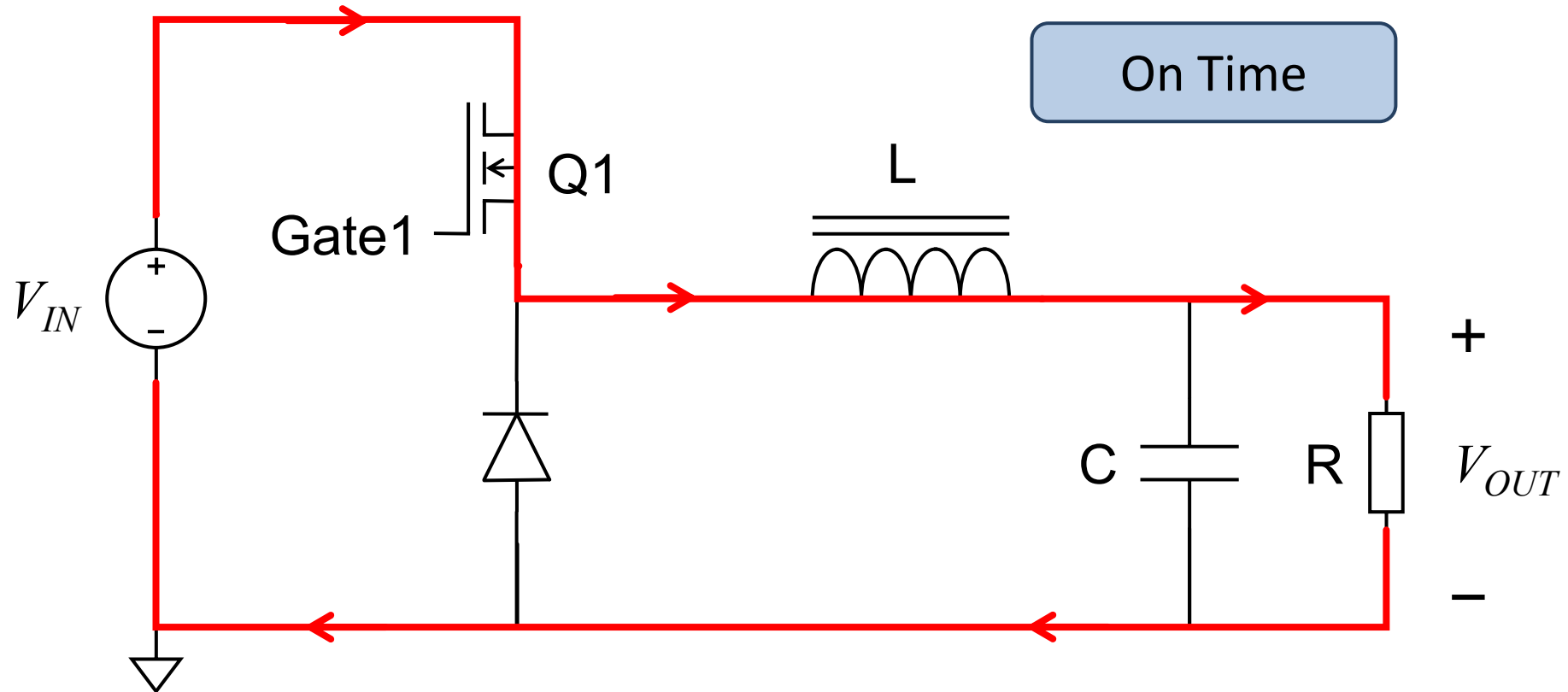


Buck Converter w/Diode: Off Time

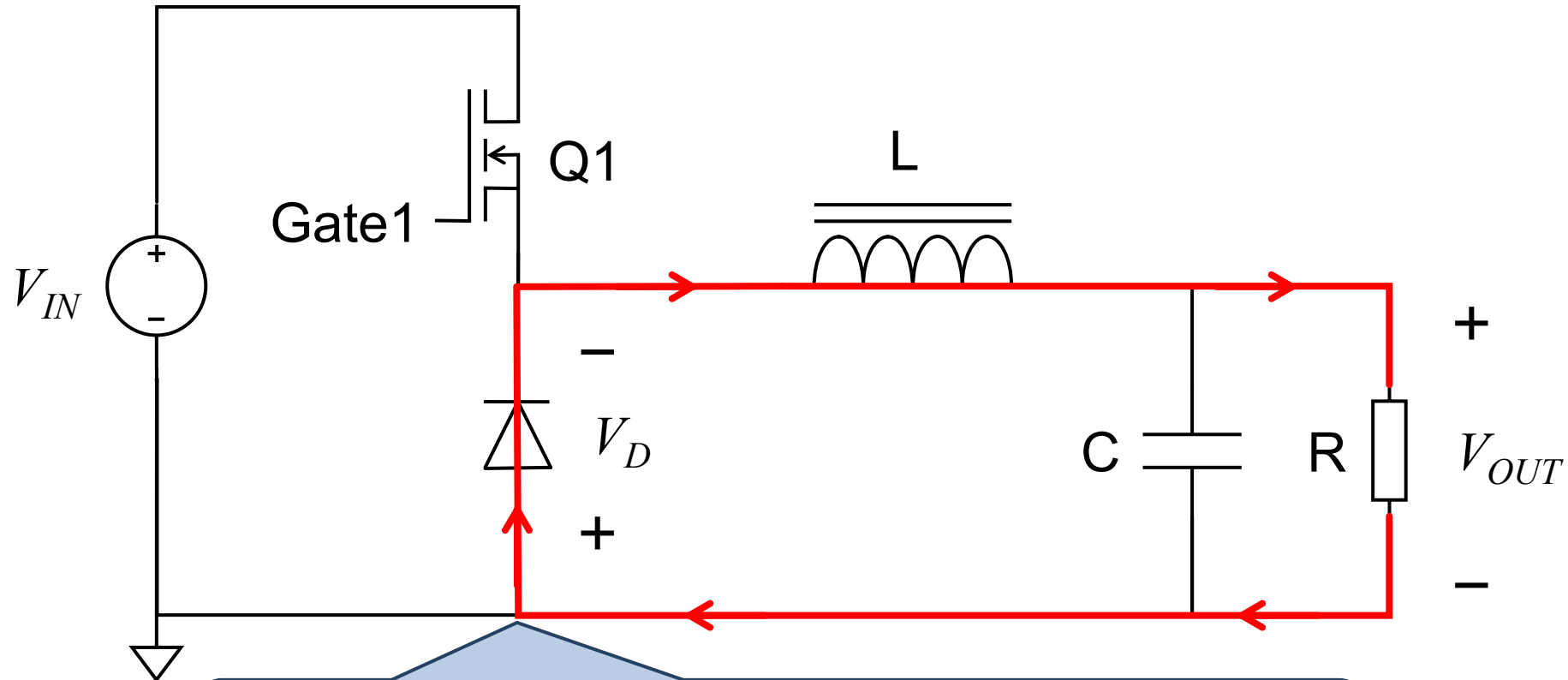


For Good Efficiency, Diode Forward Voltage Must Be Much Less Than Output Voltage

Buck Converter w/Diode

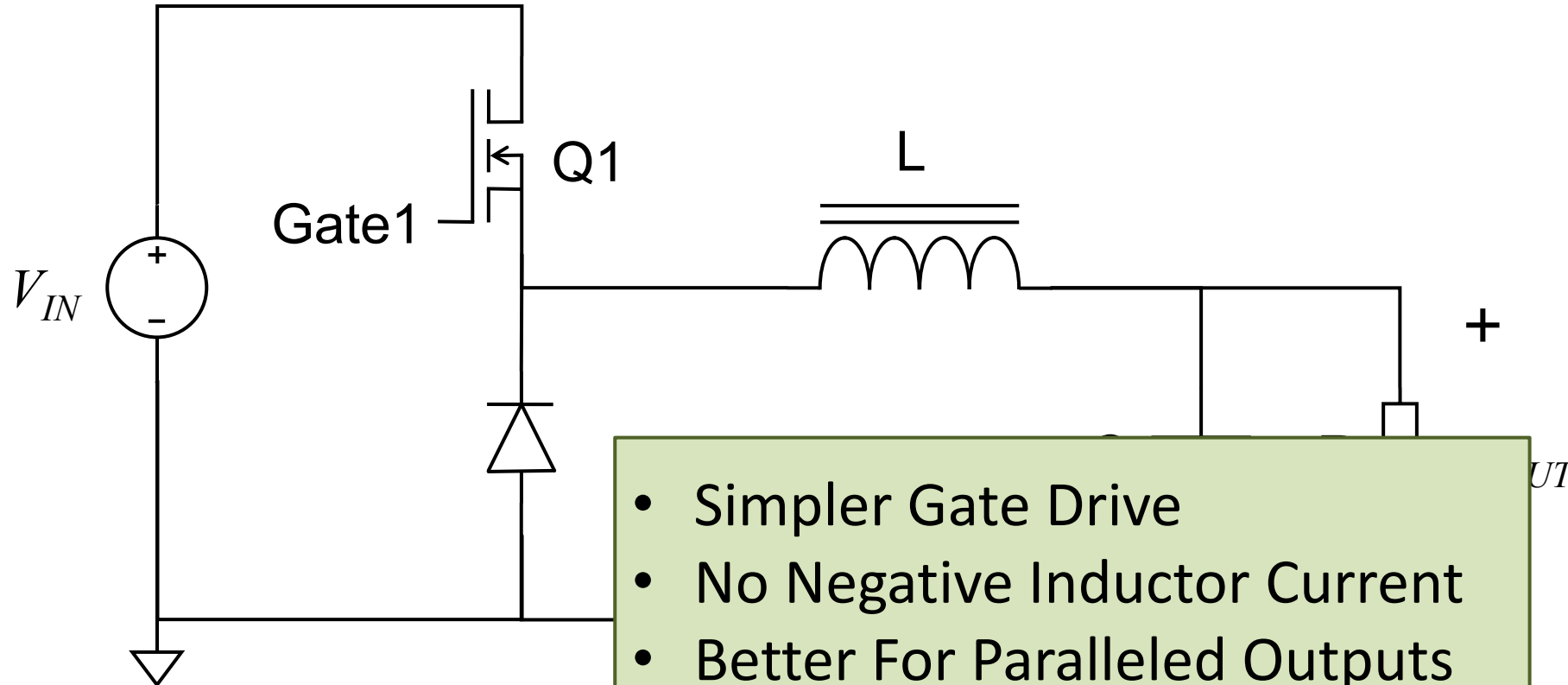


- Simpler Gate Drive
- No Negative Inductor Current
- Better For Paralleled Outputs
- Less Expensive


Buck Converter Input Current

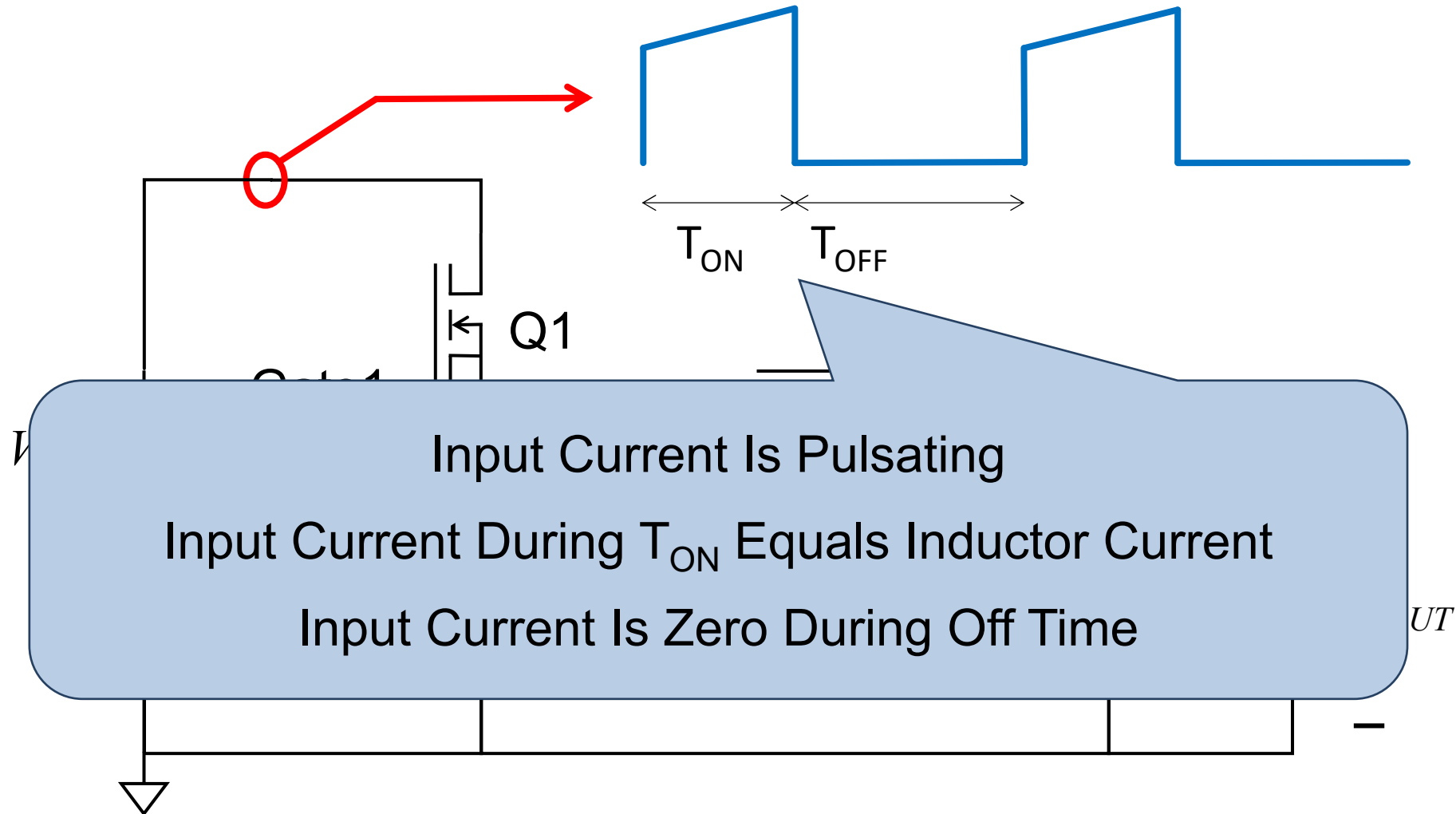


Buck Converter Input Current

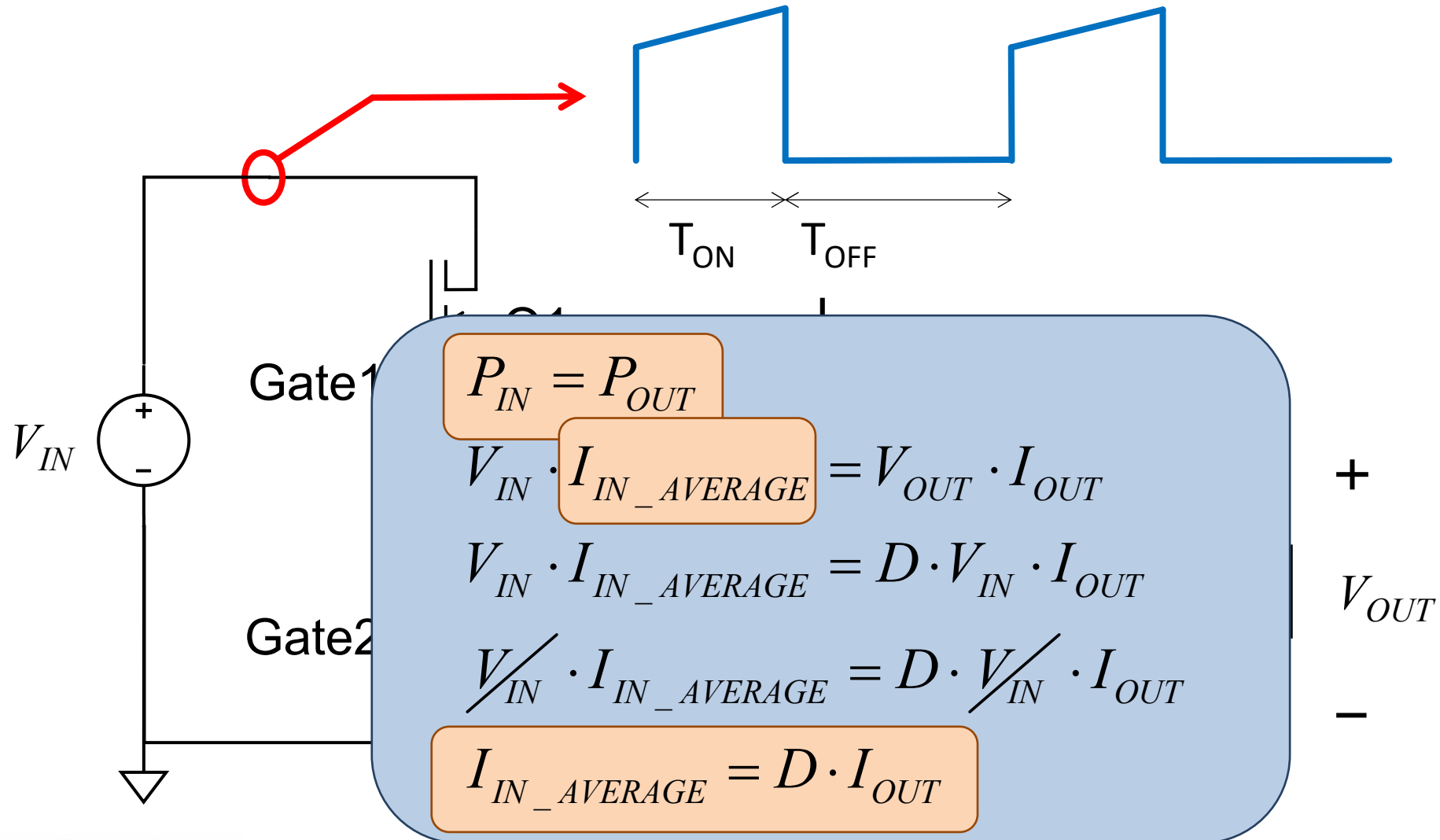

Buck Converter Input Current

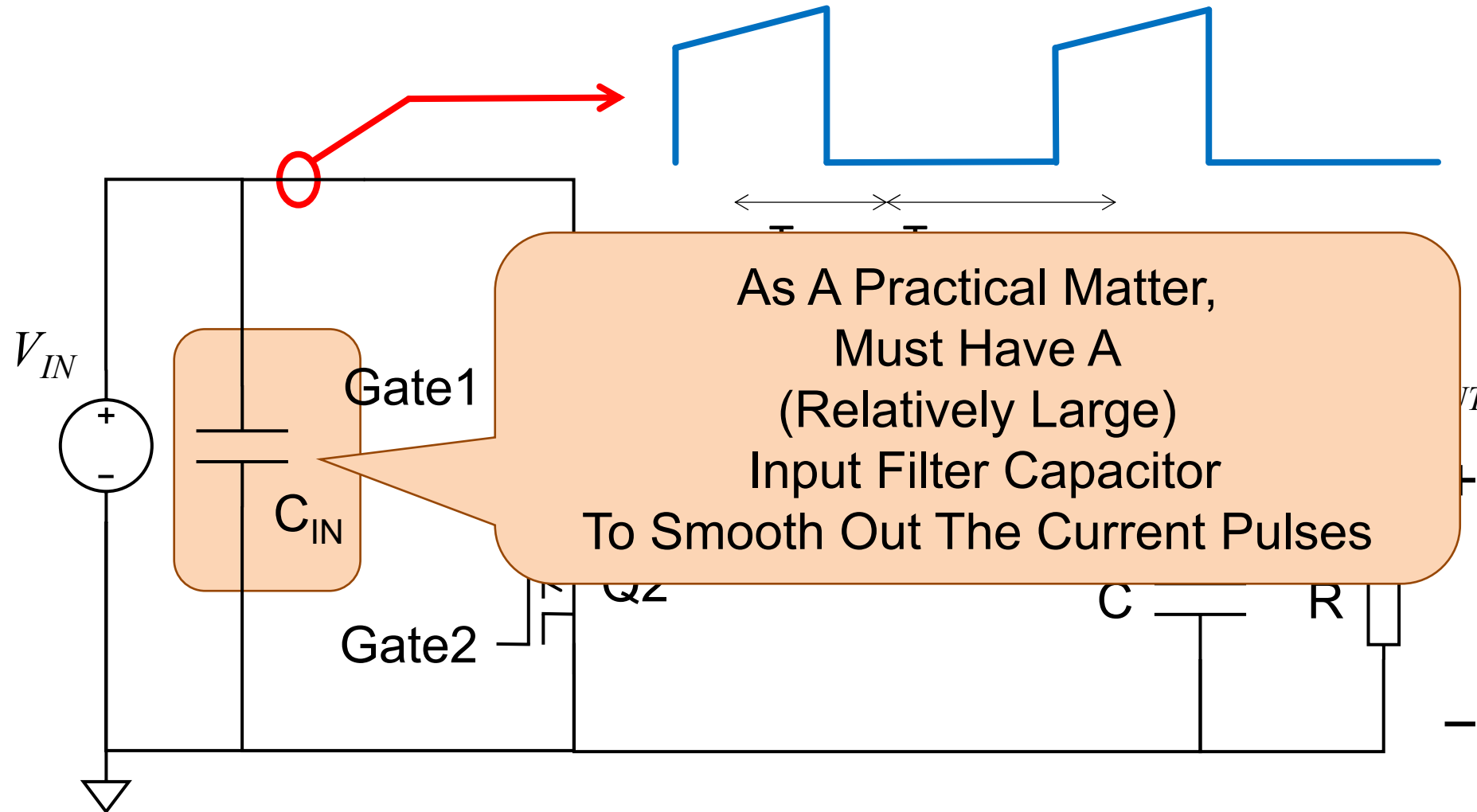

Buck Converter Output Current

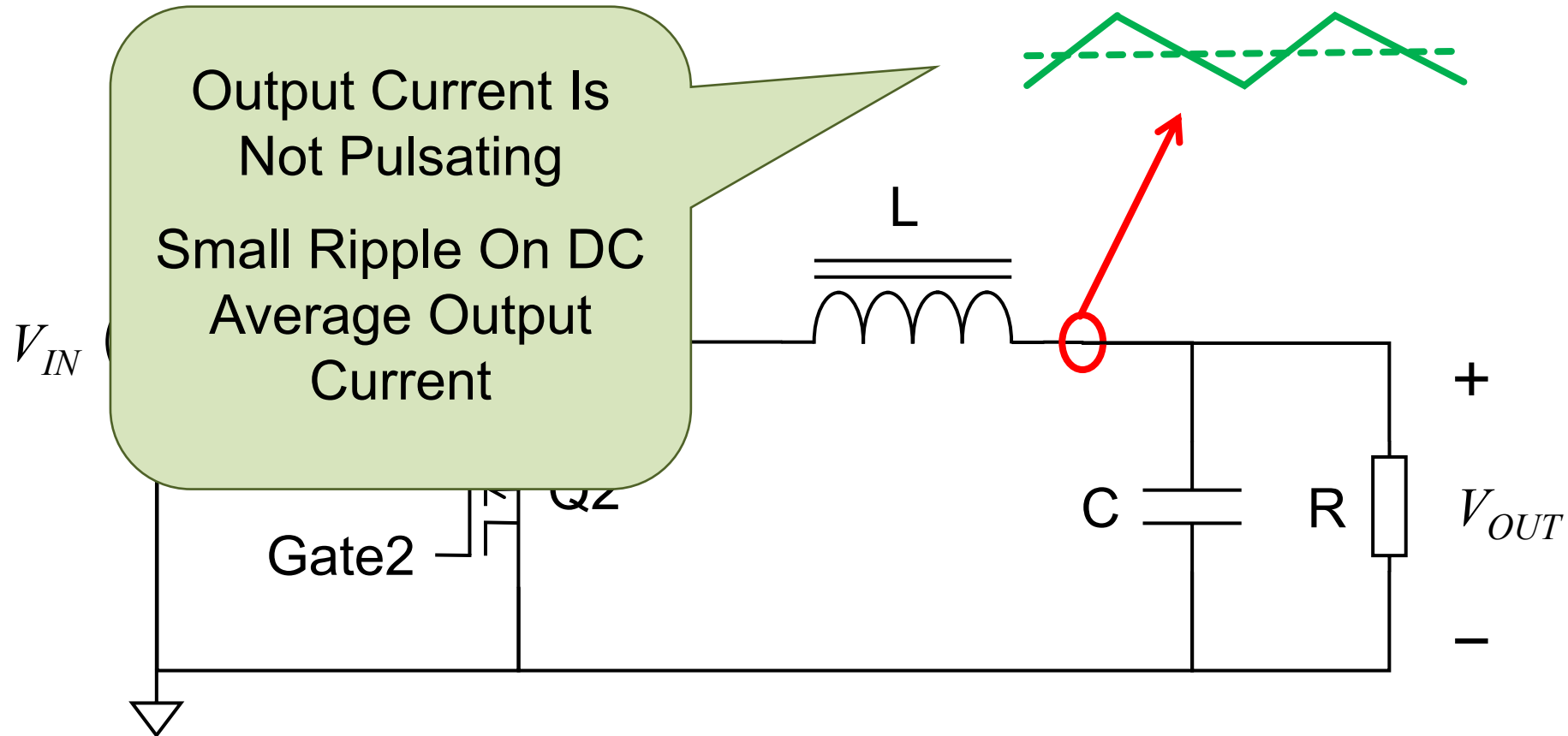

Buck Converter

Advantages

- Low Cost
- Low Parts Count
- Good Efficiency
- Simple To Control
- Many Controller ICs Available
- Available As Fully Integrated Converters

Disadvantages


- Non-Isolated
- Only Voltage Step Down
- Floating Gate Drive For Control MOSFET
- Protecting Against Control Switch Short Failure

Transformer Isolated Buck Converters


Transformer Isolated Buck Converters

Forward Converters

Single Transistor Forward Converter

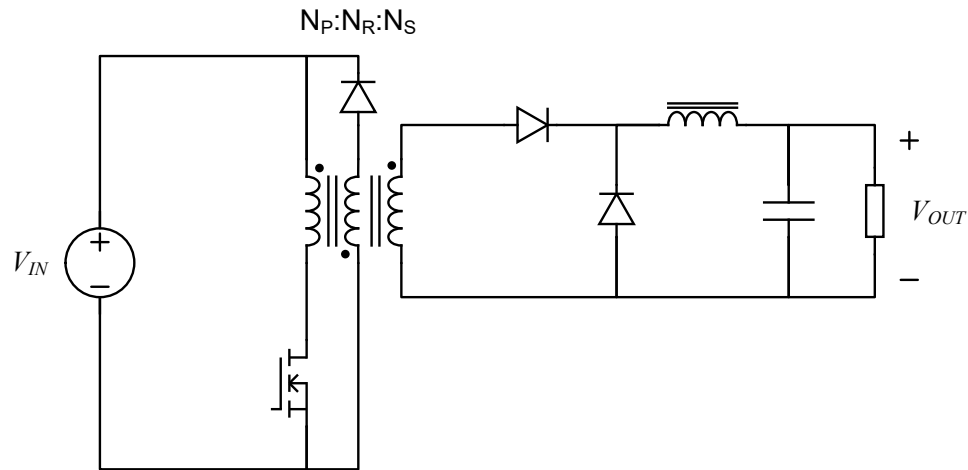

Two Transistor Forward Converter

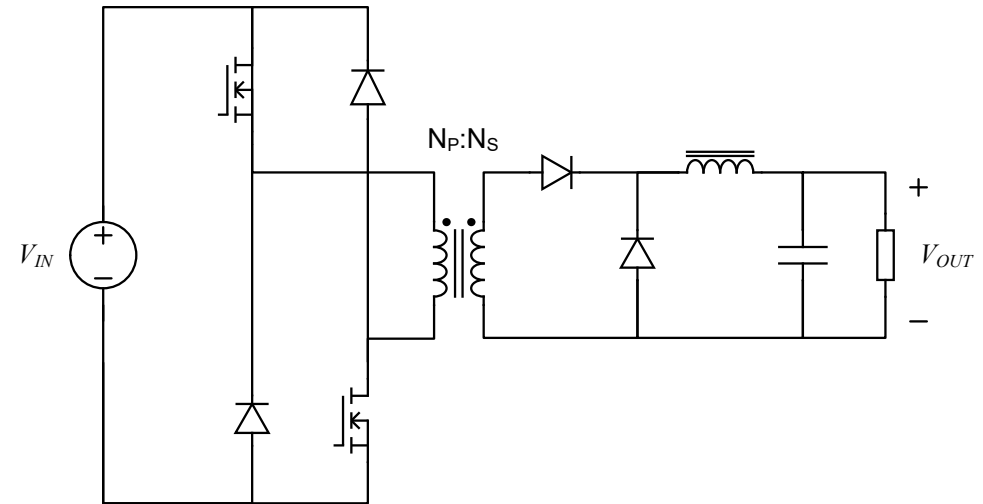


Described In The Appendices


Transformer Isolated Buck Converters

Half And Full Bridge Converters

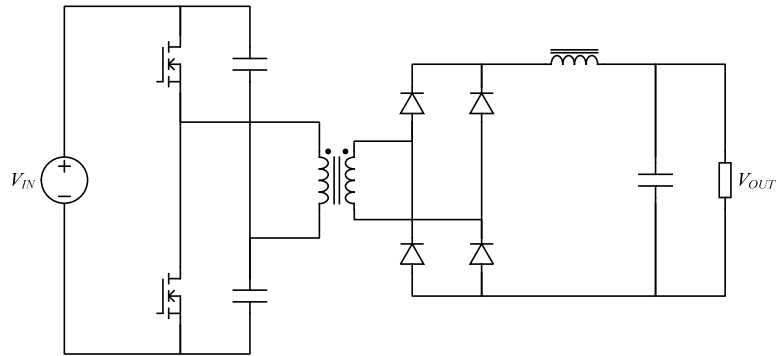
Half Bridge Converter
With Full Wave Rectifier Output



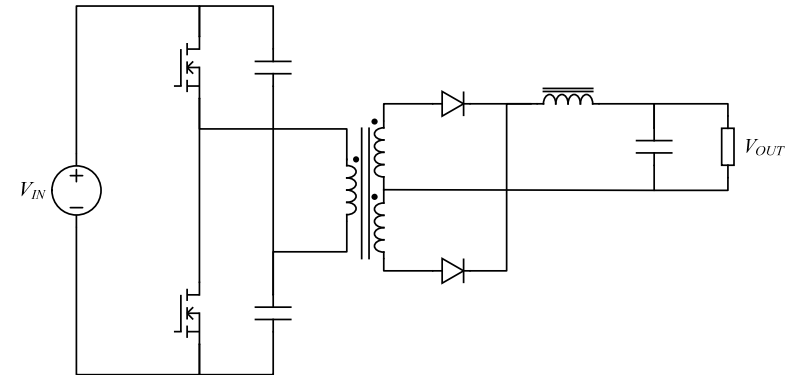
Half Bridge Converter
With Center Tapped Rectifier Output



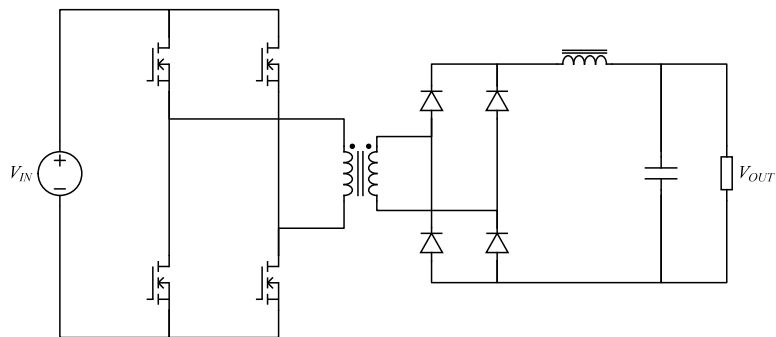Full Bridge Converter
With Full Wave Rectifier Output




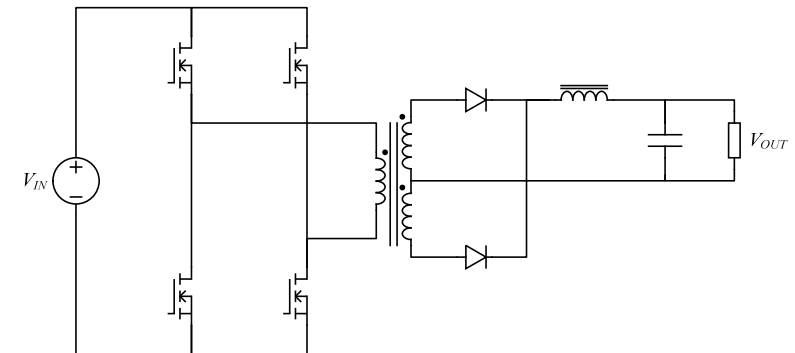Full Bridge Converter
With Center Tapped Rectifier Output




Boost Converter


Boost Converter

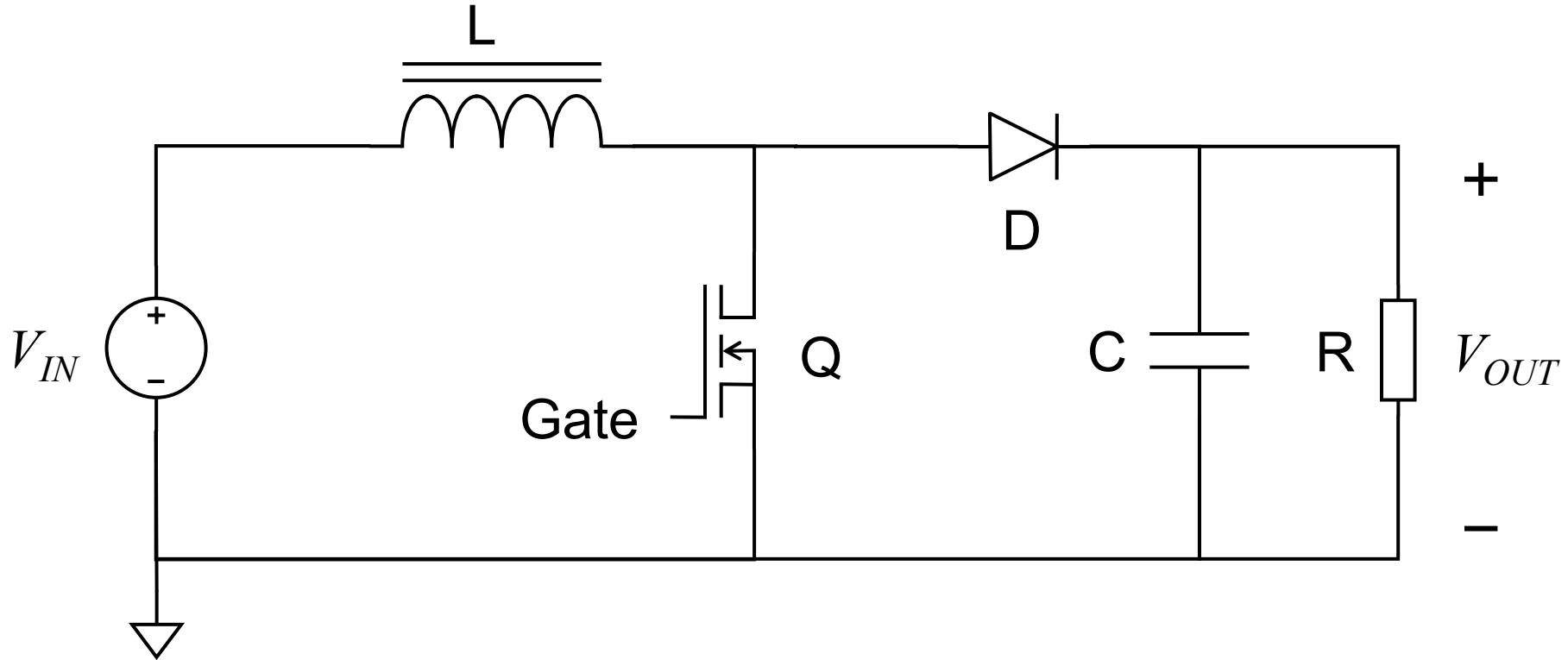


Boost Converter

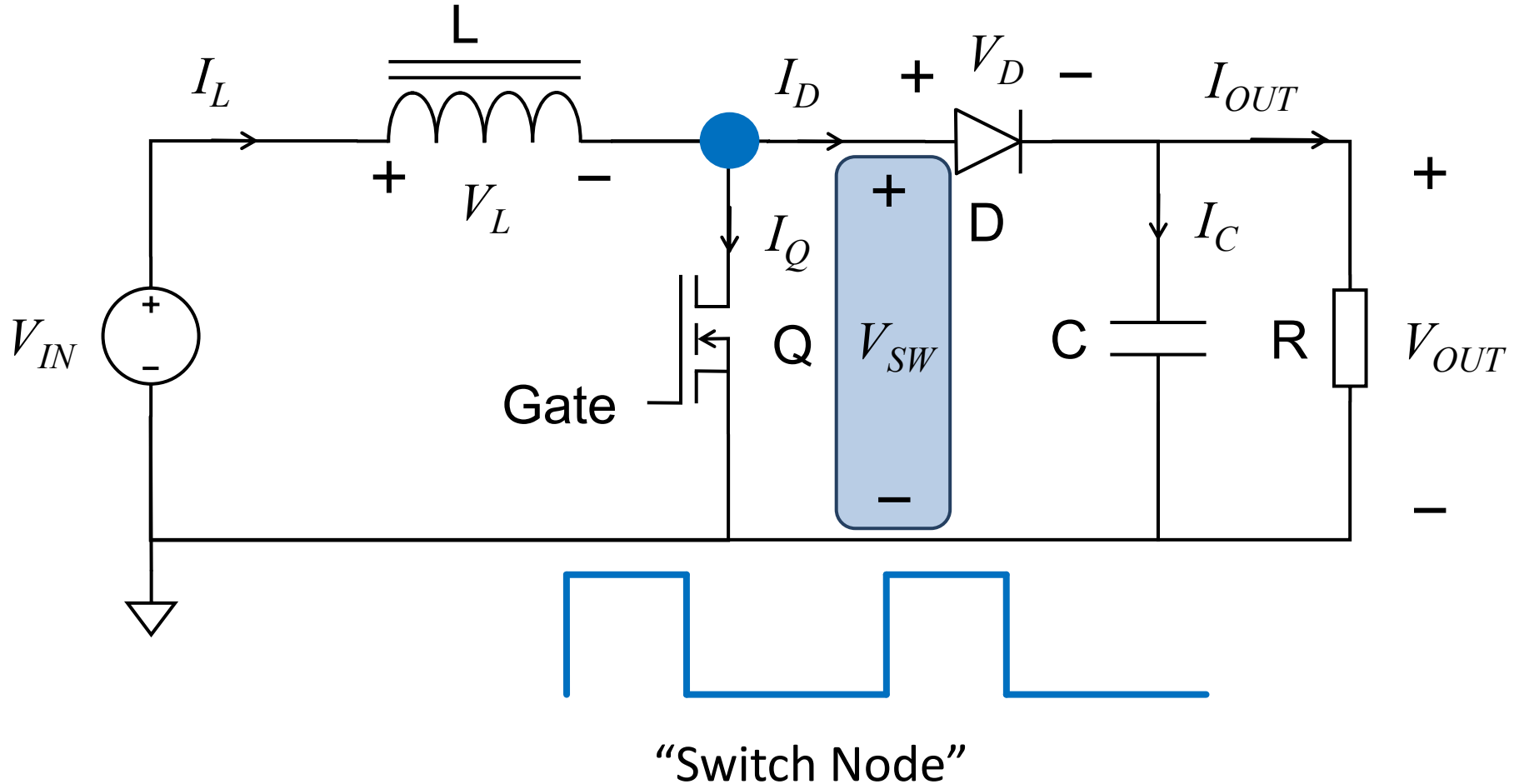


Boost Converter: On Time

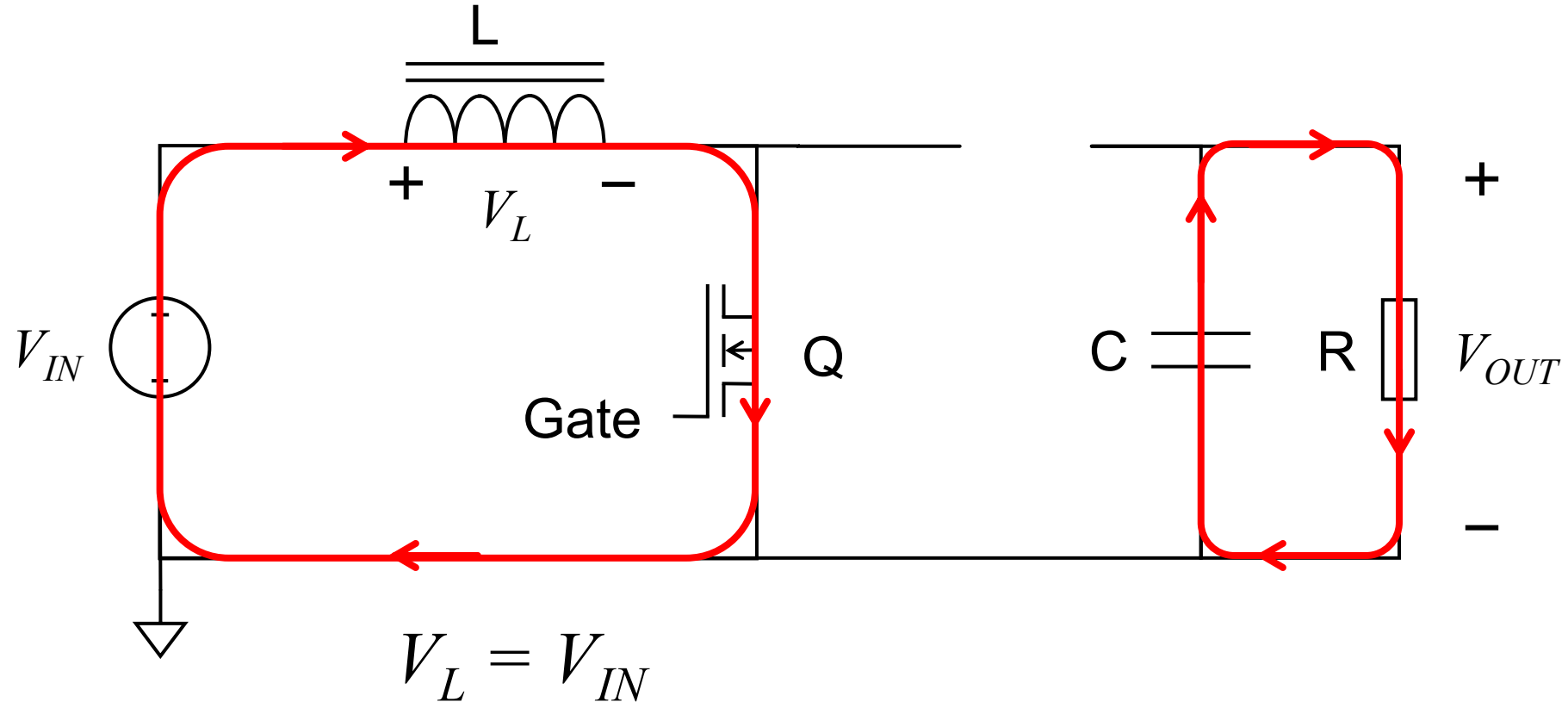


Boost Converter: On Time

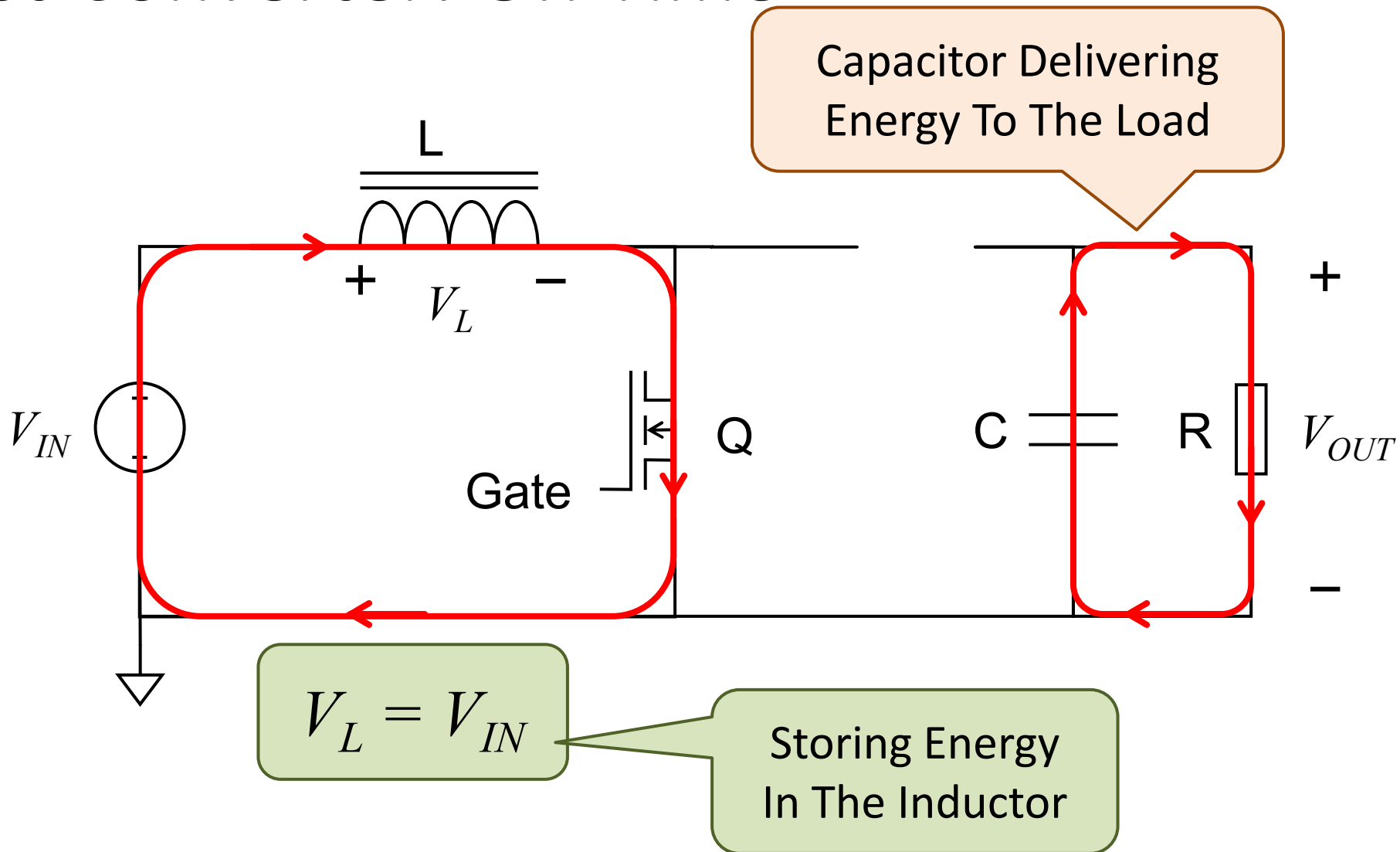

Boost Converter: Off Time

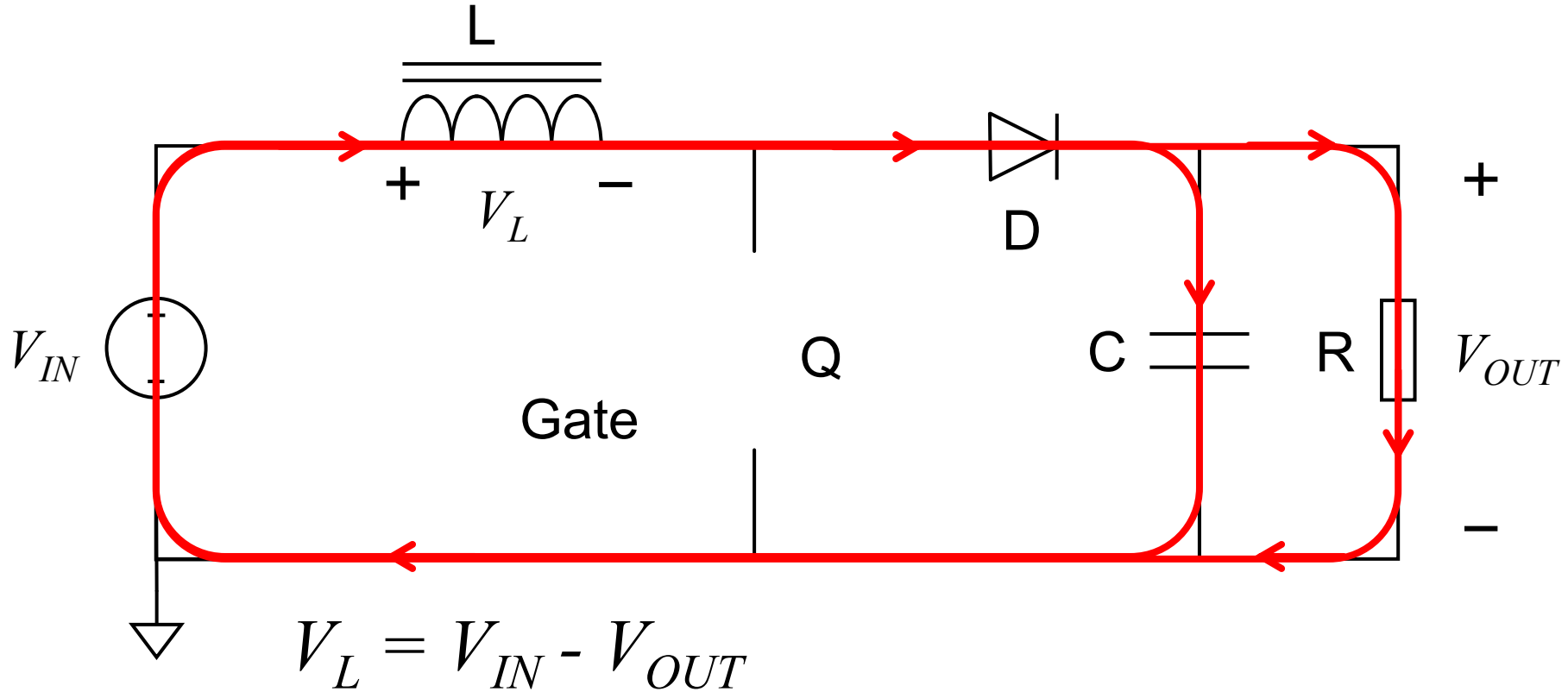

Boost Converter: Off Time

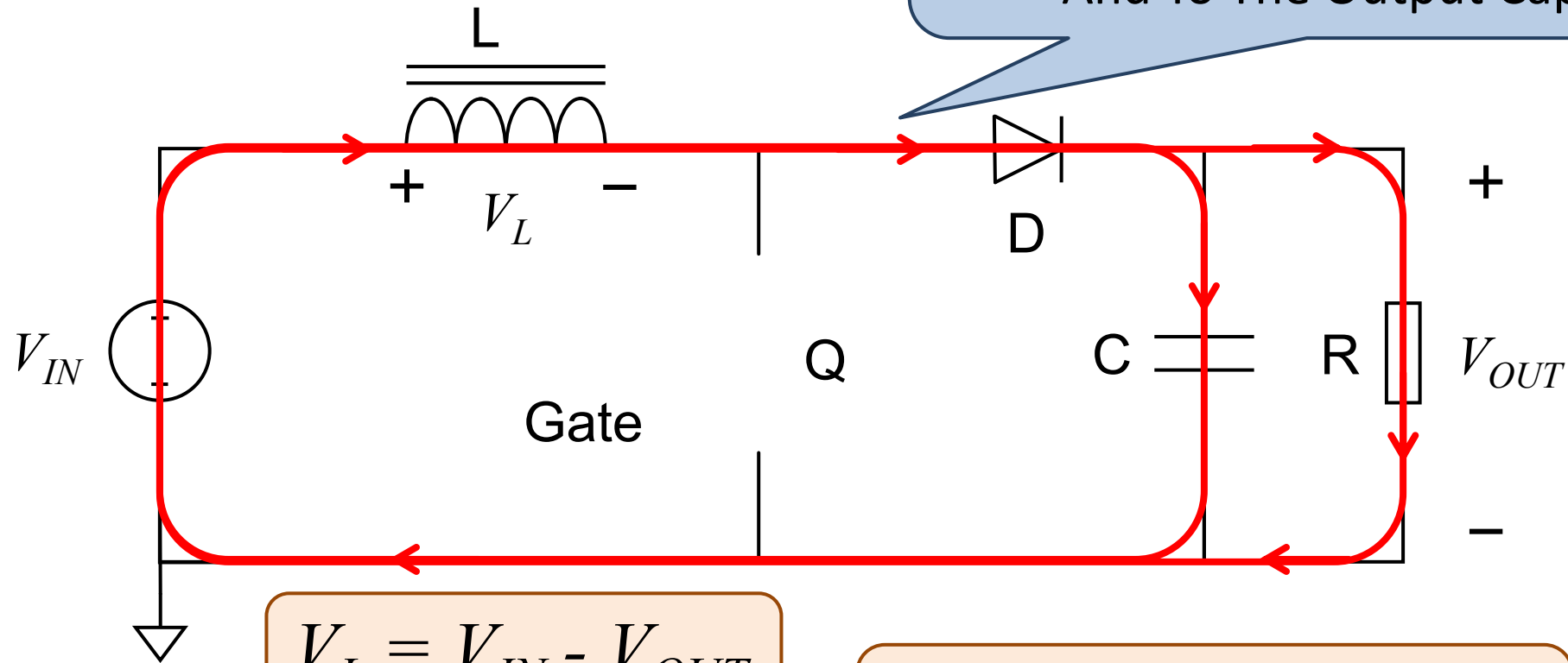


Power Flowing
From Input To The Output Load
And To The Output Capacitor

$$V_L = V_{IN} - V_{OUT}$$


Also Releasing Stored Energy
In The Inductor

Boost Converter Energy Flow


On Time

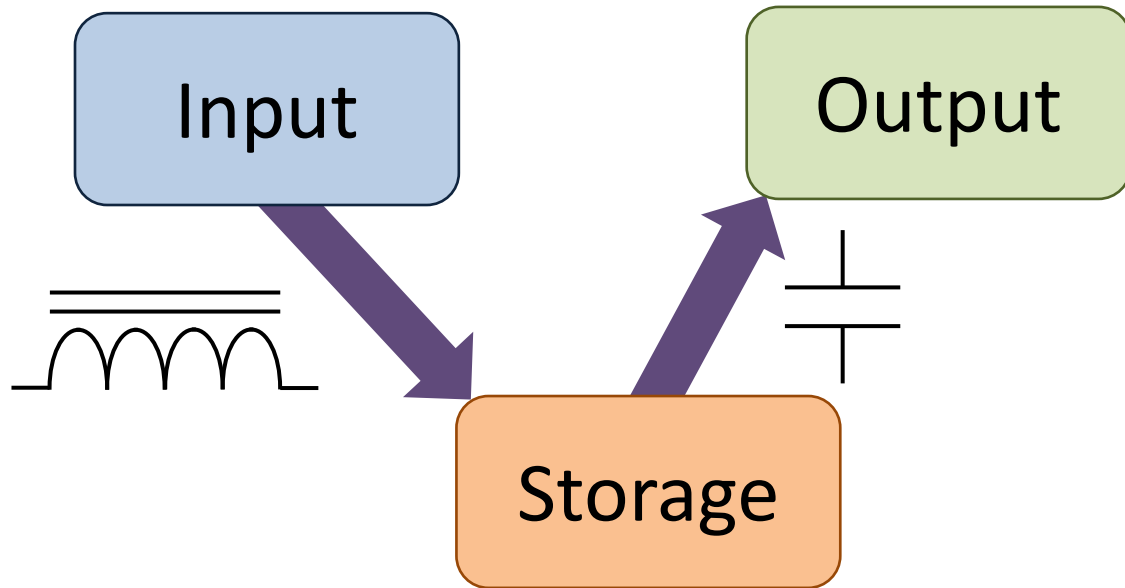

Off Time

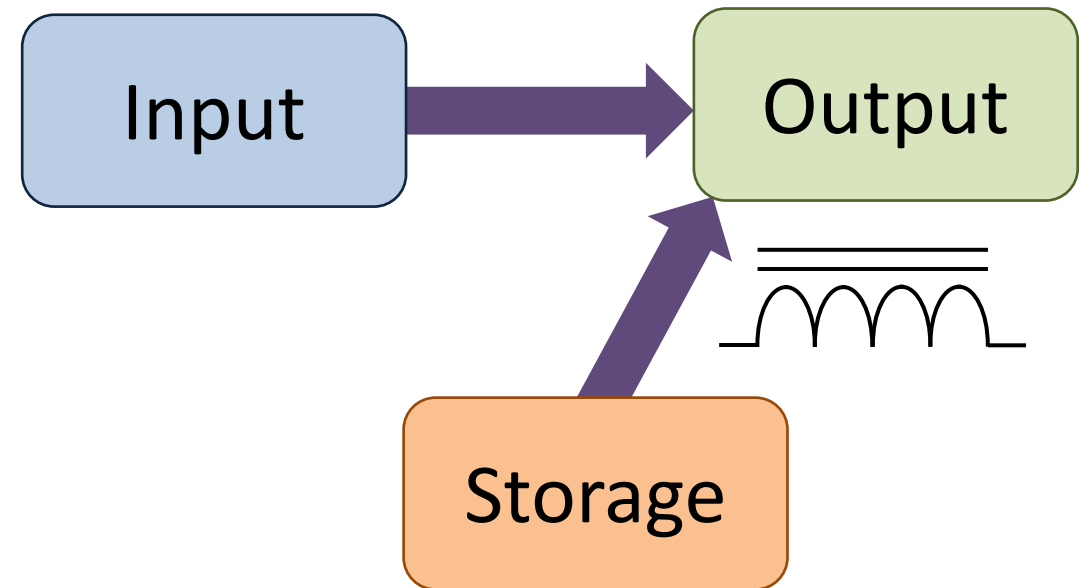


Boost Converter Waveforms

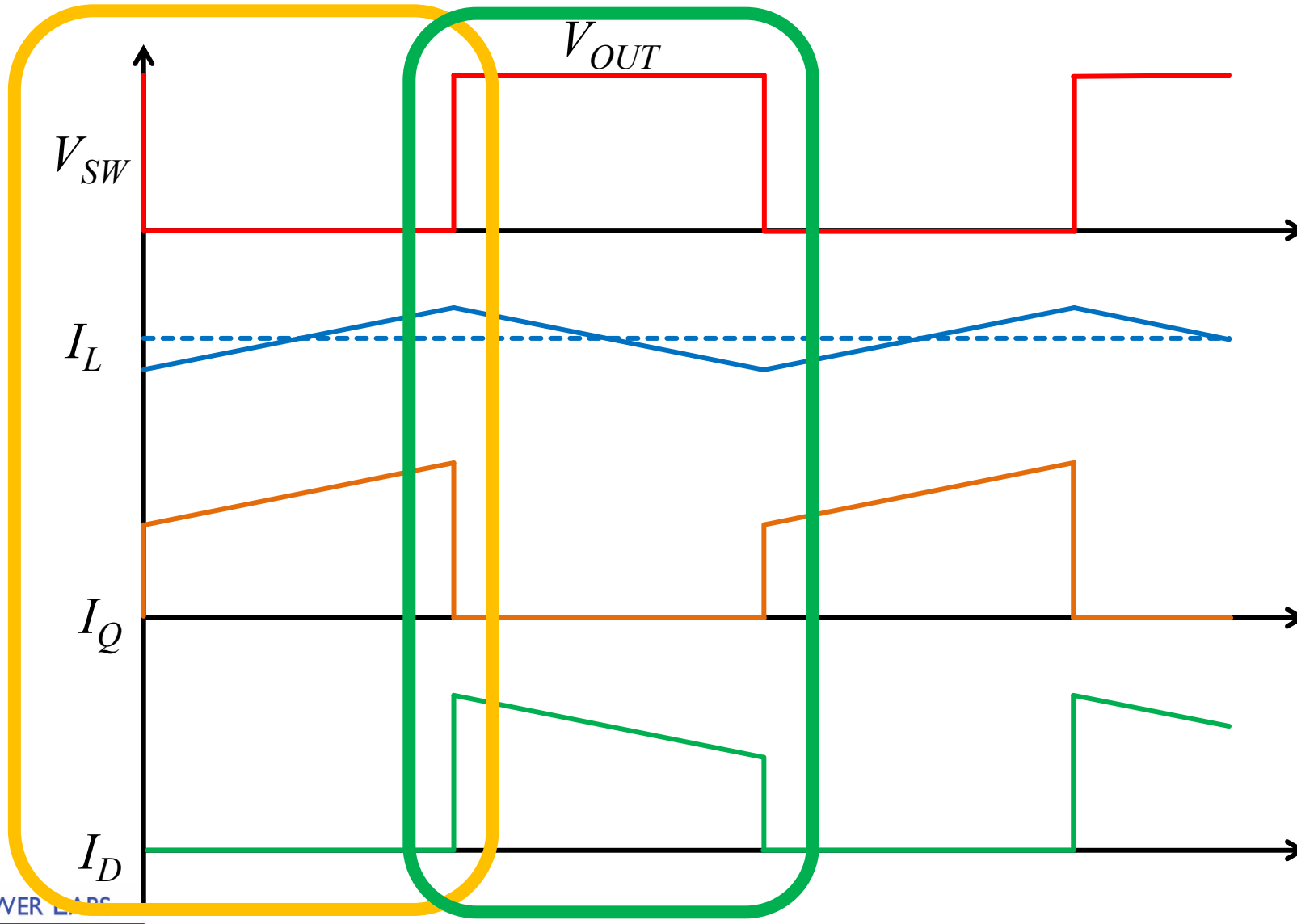


Video Lab 6

Open Loop Boost Converter Waveforms

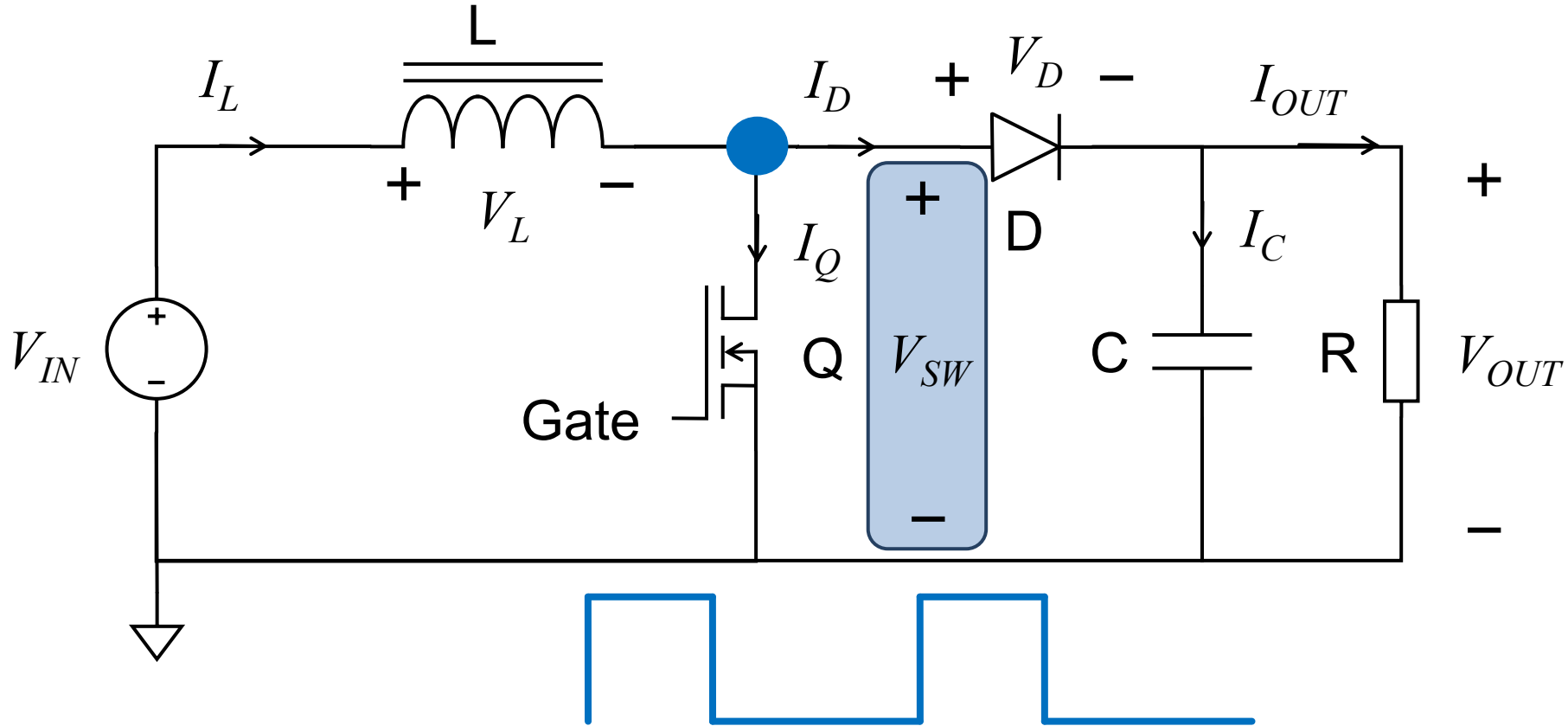

"Switch Node"

Open Loop Boost Converter Waveforms

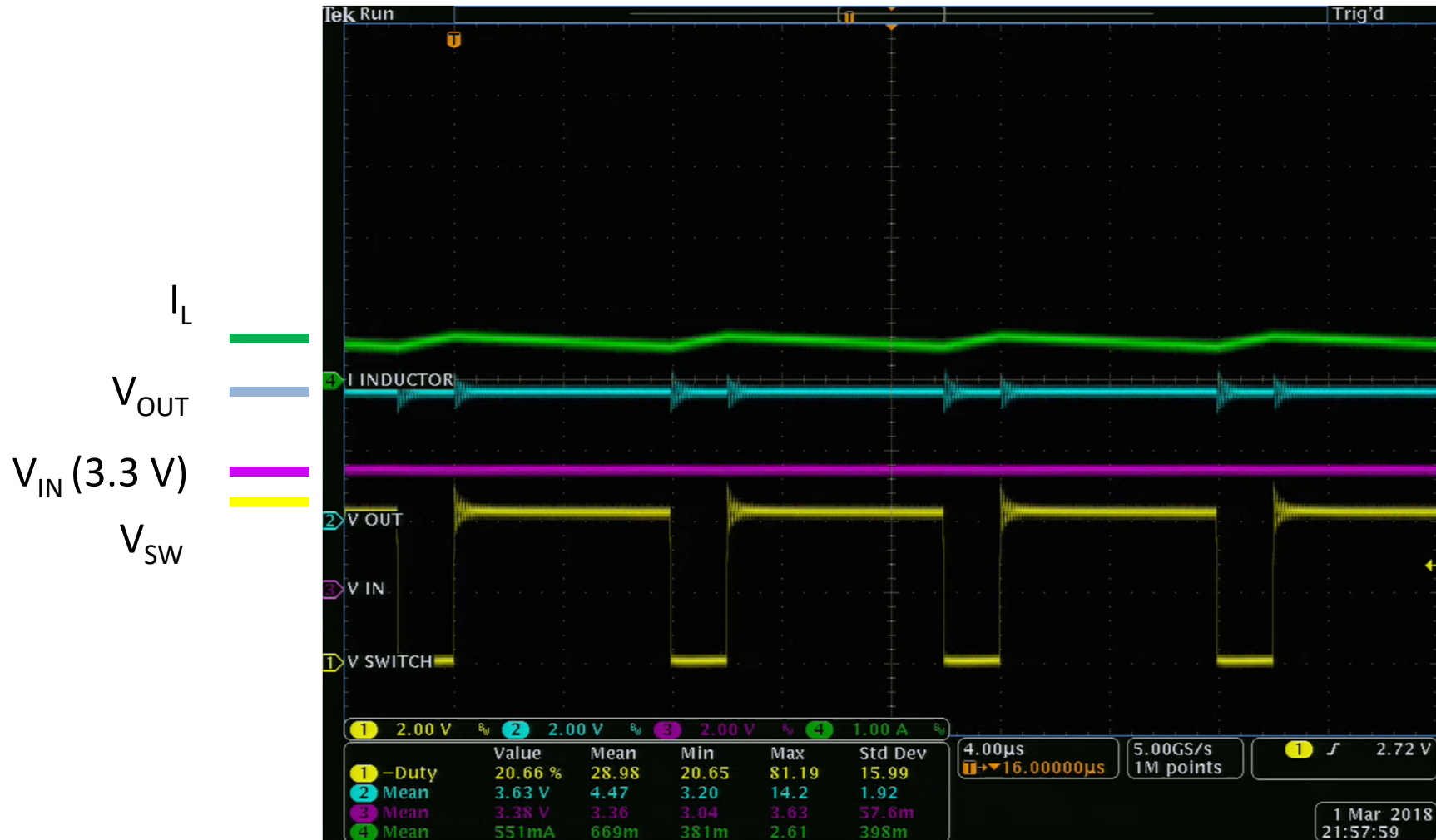

Conversion Ratio

$$V_L(T_{ON}) \cdot T_{ON} + V_L(T_{OFF}) \cdot T_{OFF} = 0$$

$$V_{IN} \cdot T_{ON} + (V_{IN} - V_{OUT}) \cdot T_{OFF} = 0$$

$$V_{IN} \cdot D \cdot T_{SW} + (V_{IN} - V_{OUT}) \cdot (1 - D) \cdot T_{SW} = 0$$

$$V_{IN} \cdot D + (V_{IN} - V_{OUT}) \cdot (1 - D) = 0$$

$$D \cdot V_{IN} + V_{IN} - D \cdot V_{IN} - V_{OUT} + D \cdot V_{OUT} = 0$$

$$V_{IN} - V_{OUT} + D \cdot V_{OUT} = 0$$

$$V_{OUT} - D \cdot V_{OUT} = V_{IN}$$


$$(1 - D) \cdot V_{OUT} = V_{IN}$$

$$V_{OUT} = \frac{1}{1 - D} \cdot V_{IN} = \frac{V_{IN}}{D'}$$




$$D \rightarrow 1 \Rightarrow V_{OUT} \rightarrow \infty$$

Conversion Ratio Plot

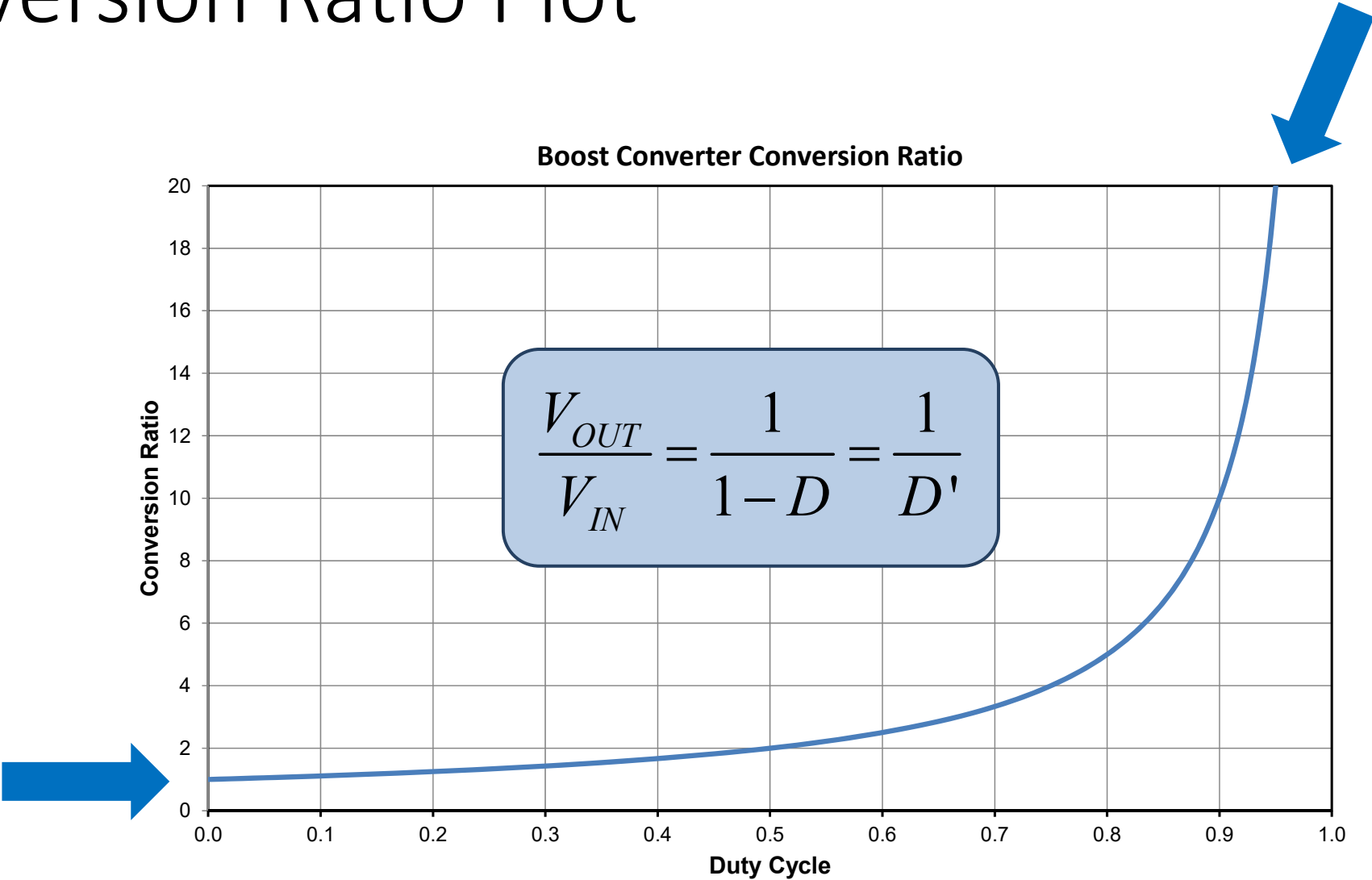

Example

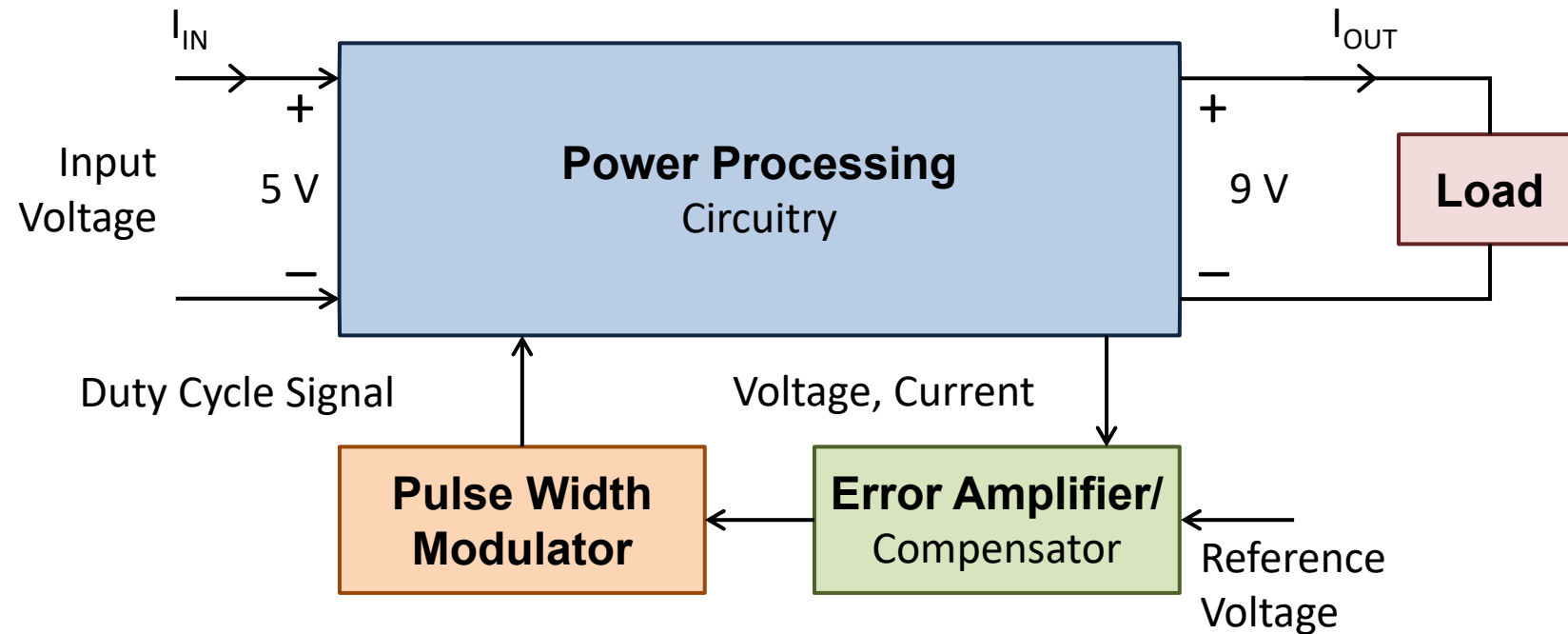


$$V_{OUT} = \frac{1}{D'} V_{IN} = \frac{1}{1-D} \cdot V_{IN}$$

$$1-D = \frac{V_{IN}}{V_{OUT}}$$

$$D = 1 - \frac{V_{IN}}{V_{OUT}}$$

Example

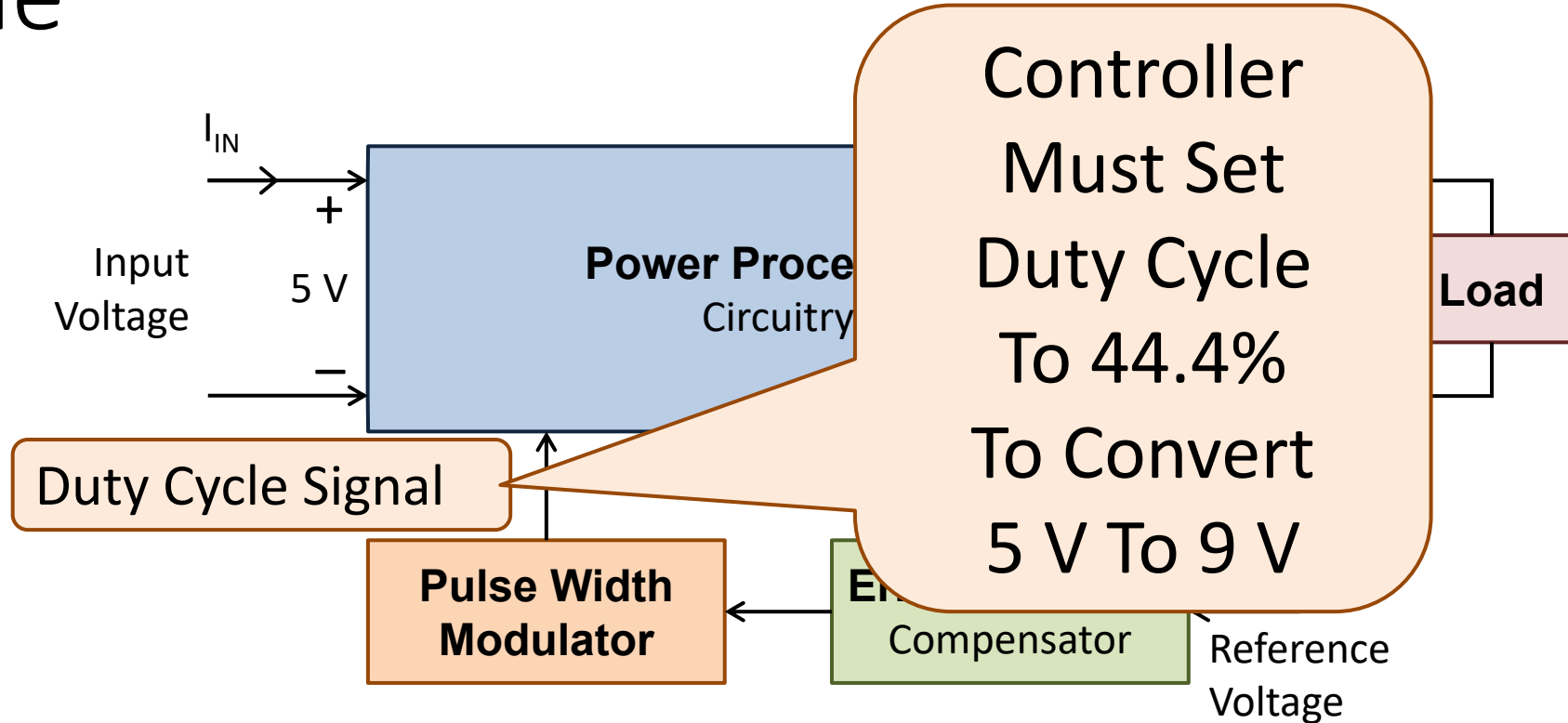


Controller
Must Set
Duty Cycle
To 44.4%
To Convert
5 V To 9 V

$$V_{IN} = 5\text{ V}$$
$$V_{OUT} = 9\text{ V}$$
$$I_{OUT} = 5\text{ A}$$



$$D = 1 - \frac{V_{IN}}{V_{OUT}} = 1 - \frac{5\text{ V}}{9\text{ V}}$$
$$= 0.444 = 44.4\%$$

Example

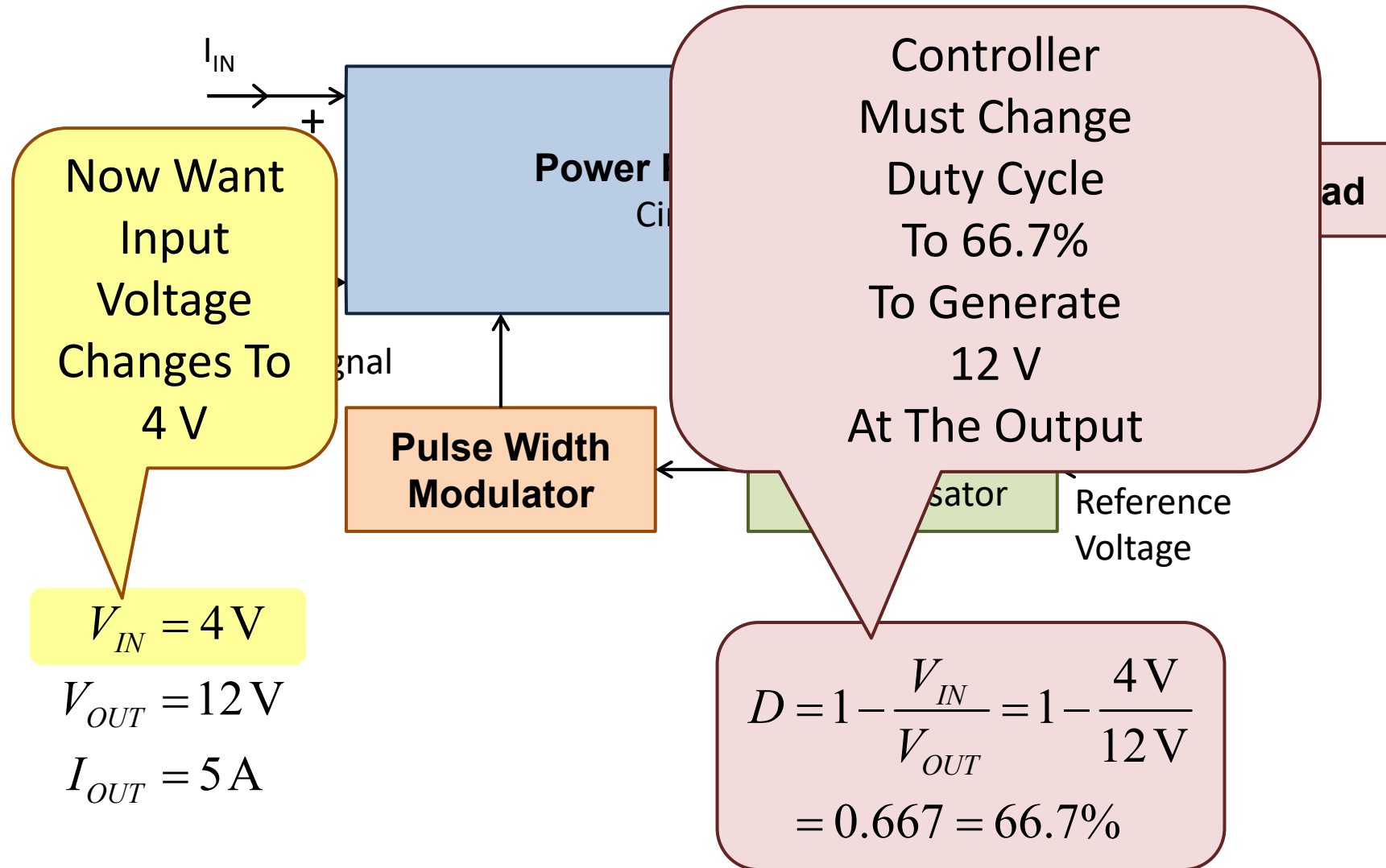

Video Lab 7

Boost Converter With Feedback

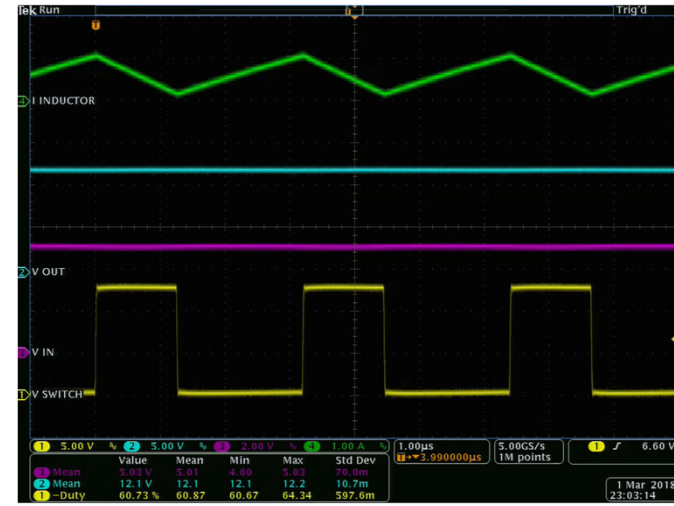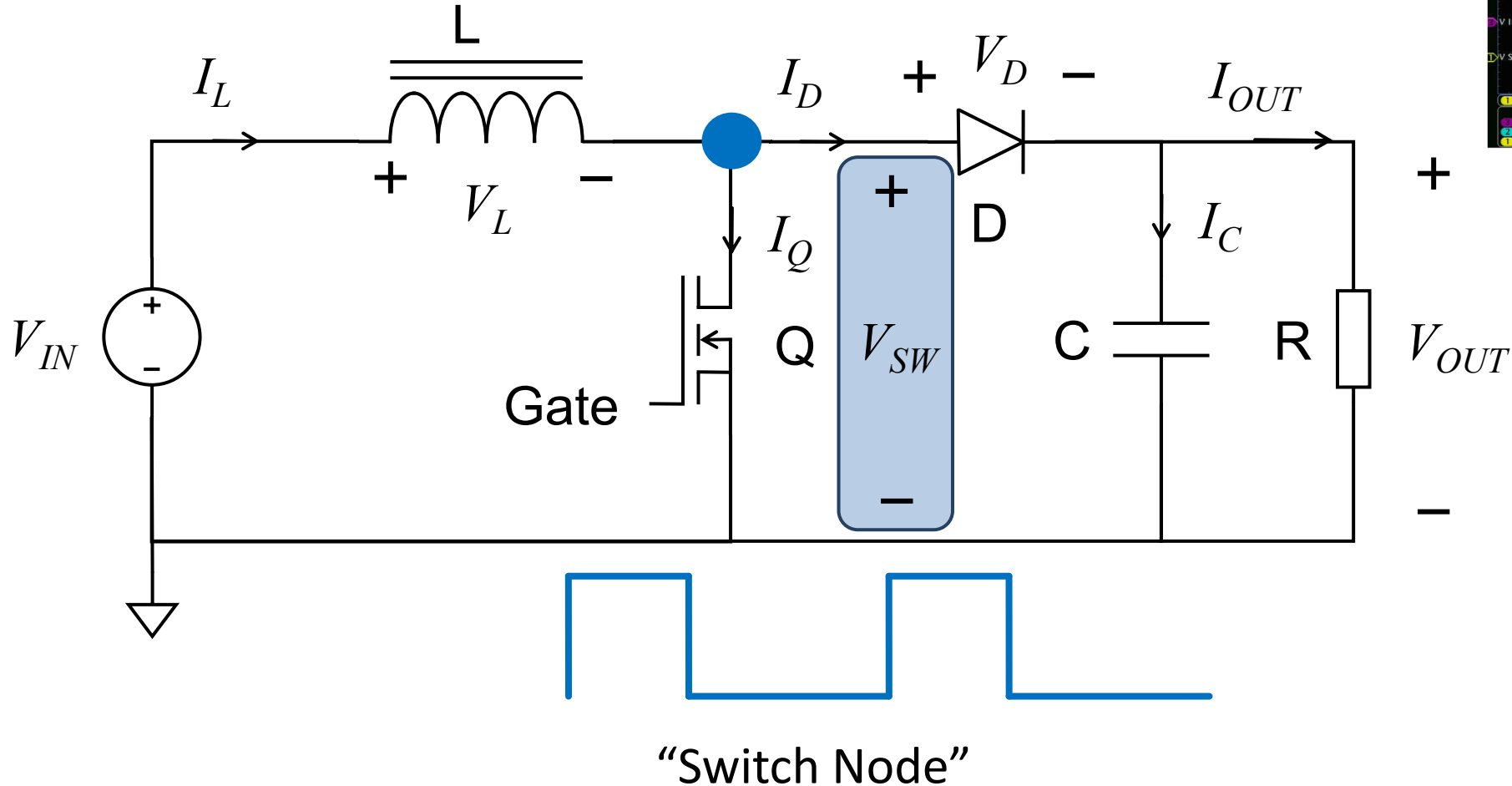

Inductor Current

$$I_C(T_{ON}) \cdot T_{ON} + I_C(T_{OFF}) \cdot T_{OFF} = 0$$

Capacitor Charge Balance

$$I_{OUT} \cdot T_{ON} + (I_L - I_{OUT}) \cdot T_{OFF} = 0$$

$$I_{OUT} = \frac{1}{R_{OUT}} \cdot V_{OUT}$$

$$I_{OUT} \cdot D \cdot T_{SW} + (I_L - I_{OUT}) \cdot (1 - D) \cdot T_{SW} = 0$$

$$I_{OUT} \cdot D + (I_L - I_{OUT}) \cdot (1 - D) = 0$$

$$D \cdot I_{OUT} + I_{OUT} - D \cdot I_{OUT} - I_L + D \cdot I_L = 0$$

$$I_{OUT} - I_L + D \cdot I_L = 0$$

$$I_L - D \cdot I_L = I_{OUT}$$


$$(1 - D) \cdot I_L = I_{OUT}$$

$$I_L = \frac{1}{1 - D} \cdot I_{OUT} = \frac{1}{D'} \cdot I_{OUT}$$




$$D \rightarrow 1 \Rightarrow I_L \rightarrow \infty$$


Boost Converter Current

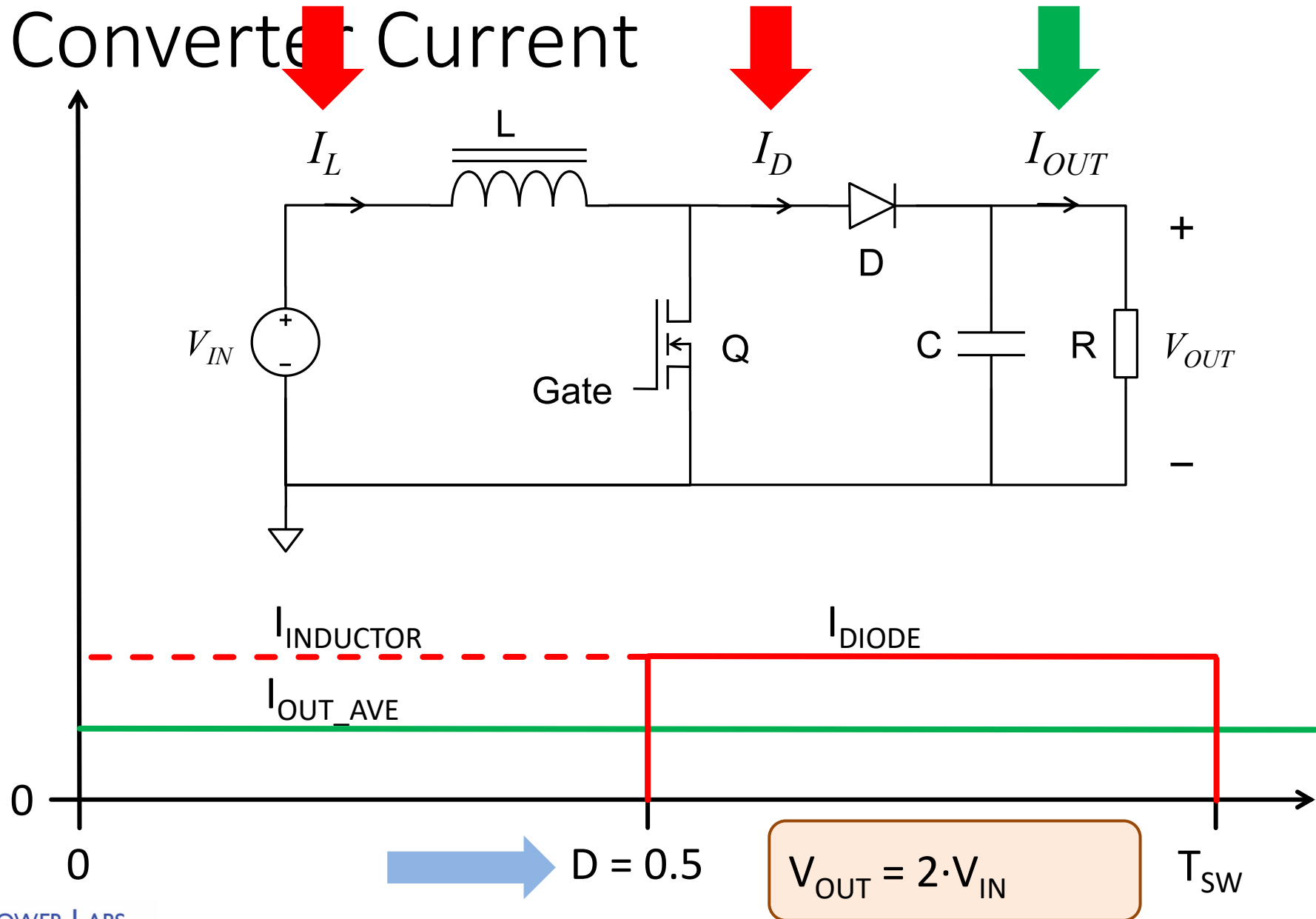


Boost Converter Current

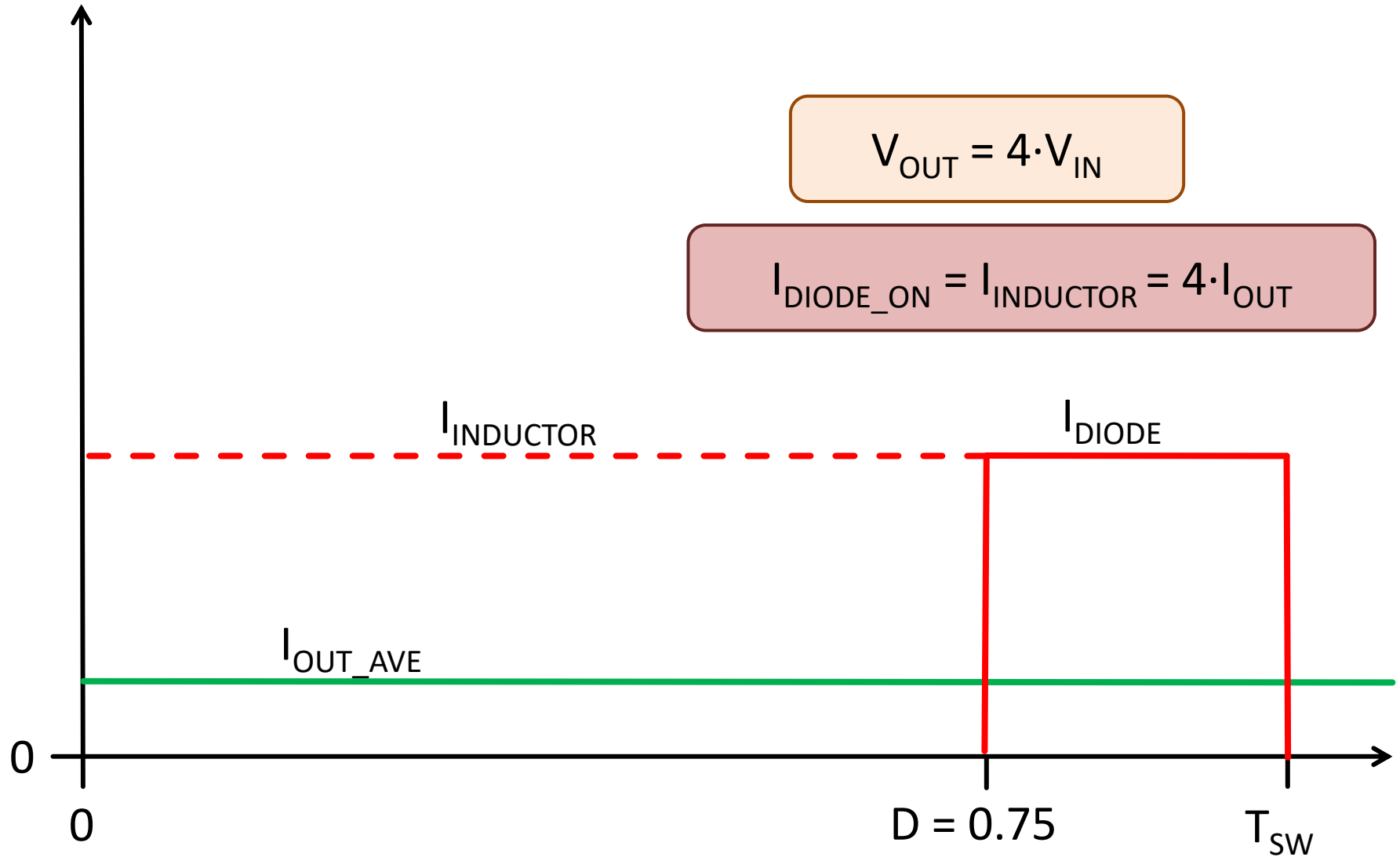

Boost Converter Current

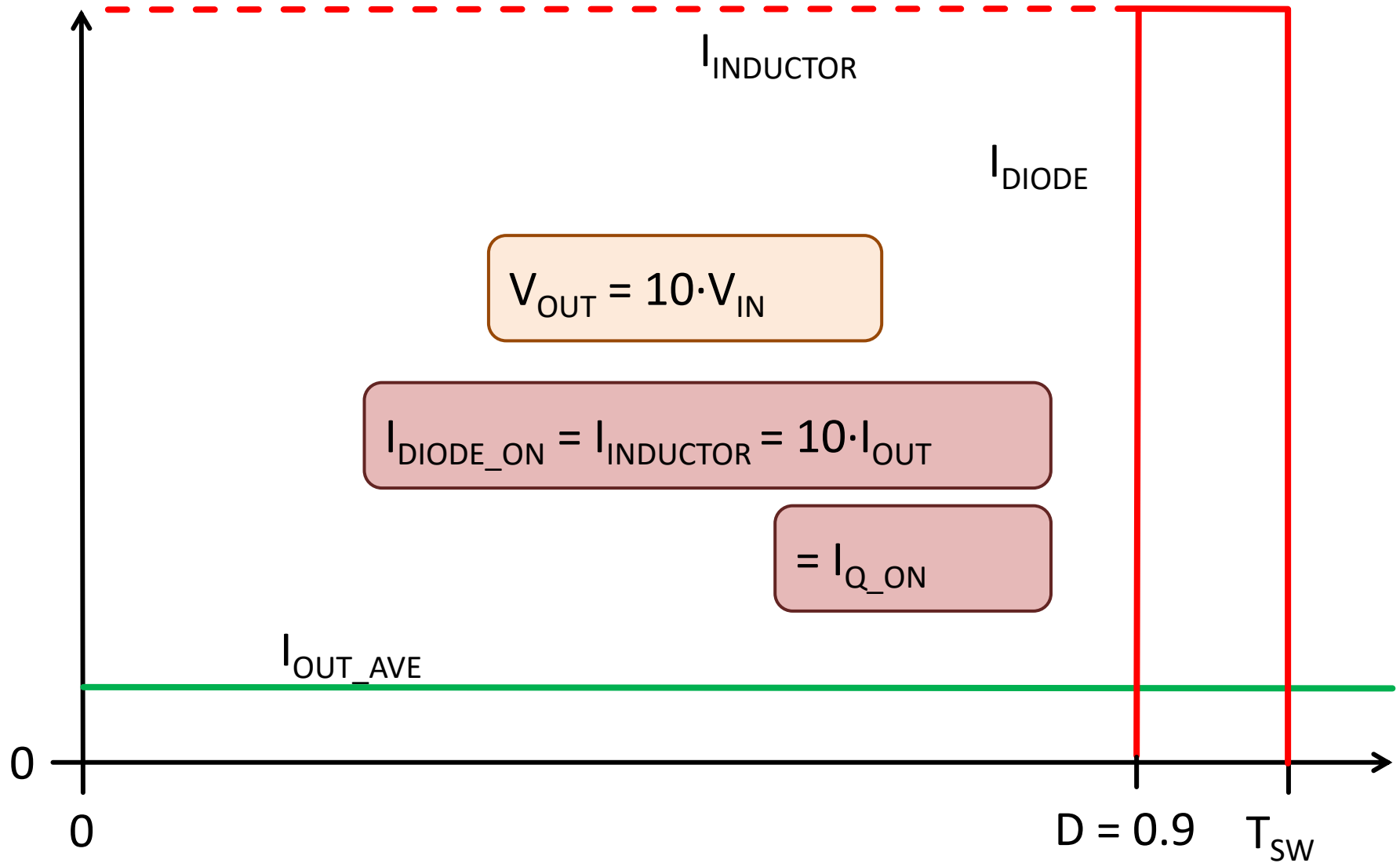


Conversion Ratio Plot

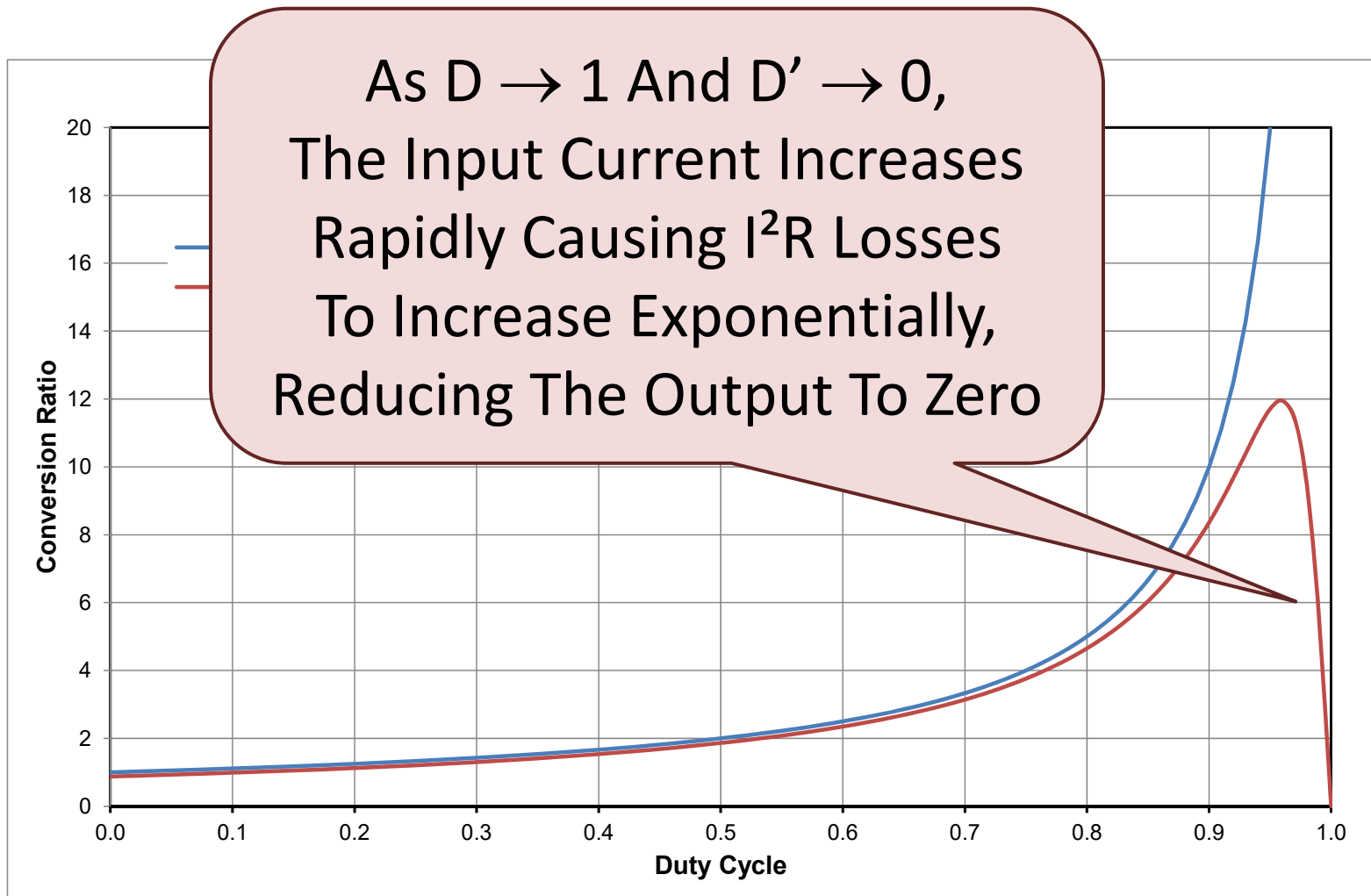


Video Lab 8


Boost Converter At High Duty Cycle

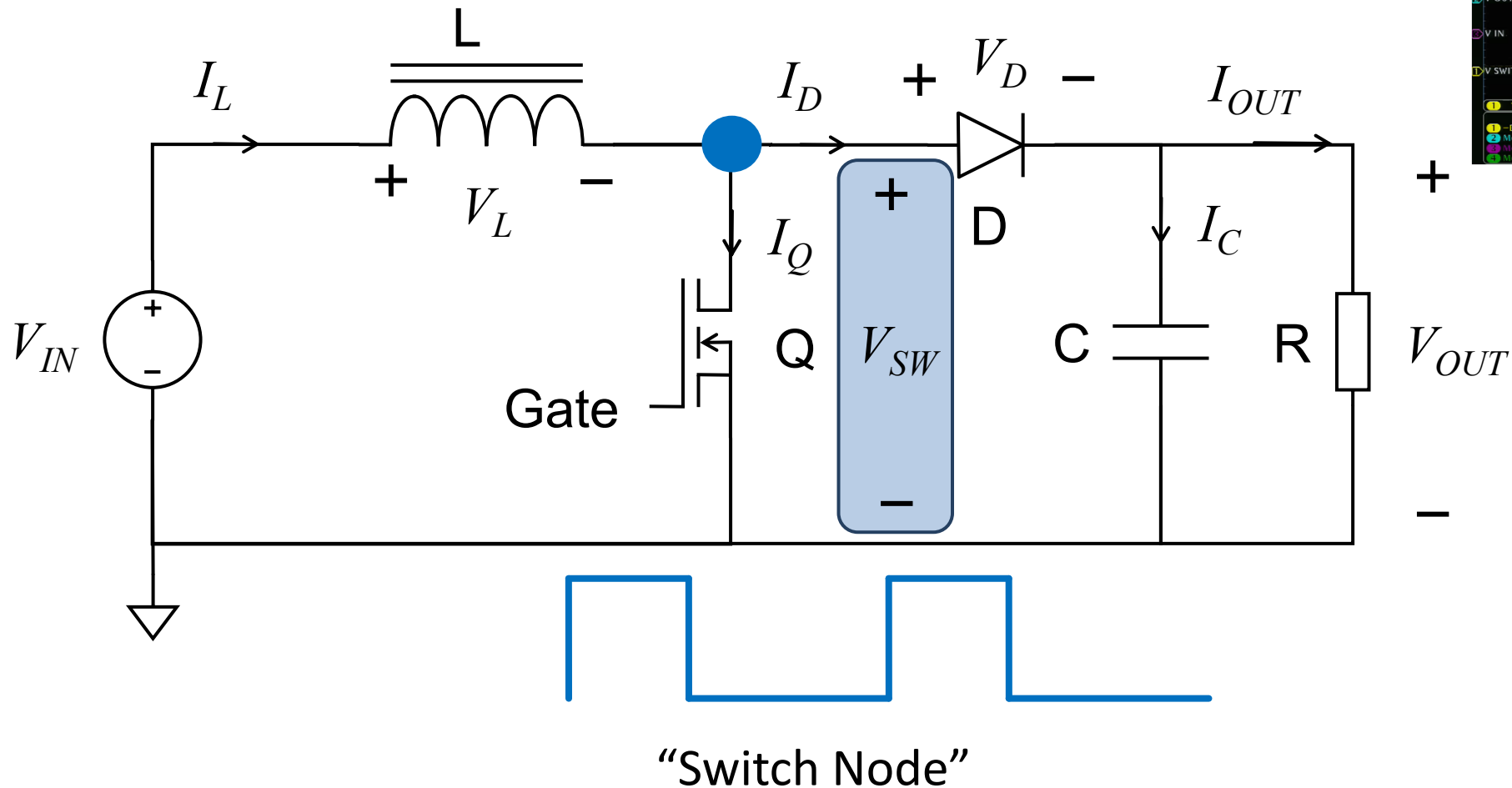

Boost Converter Output Current

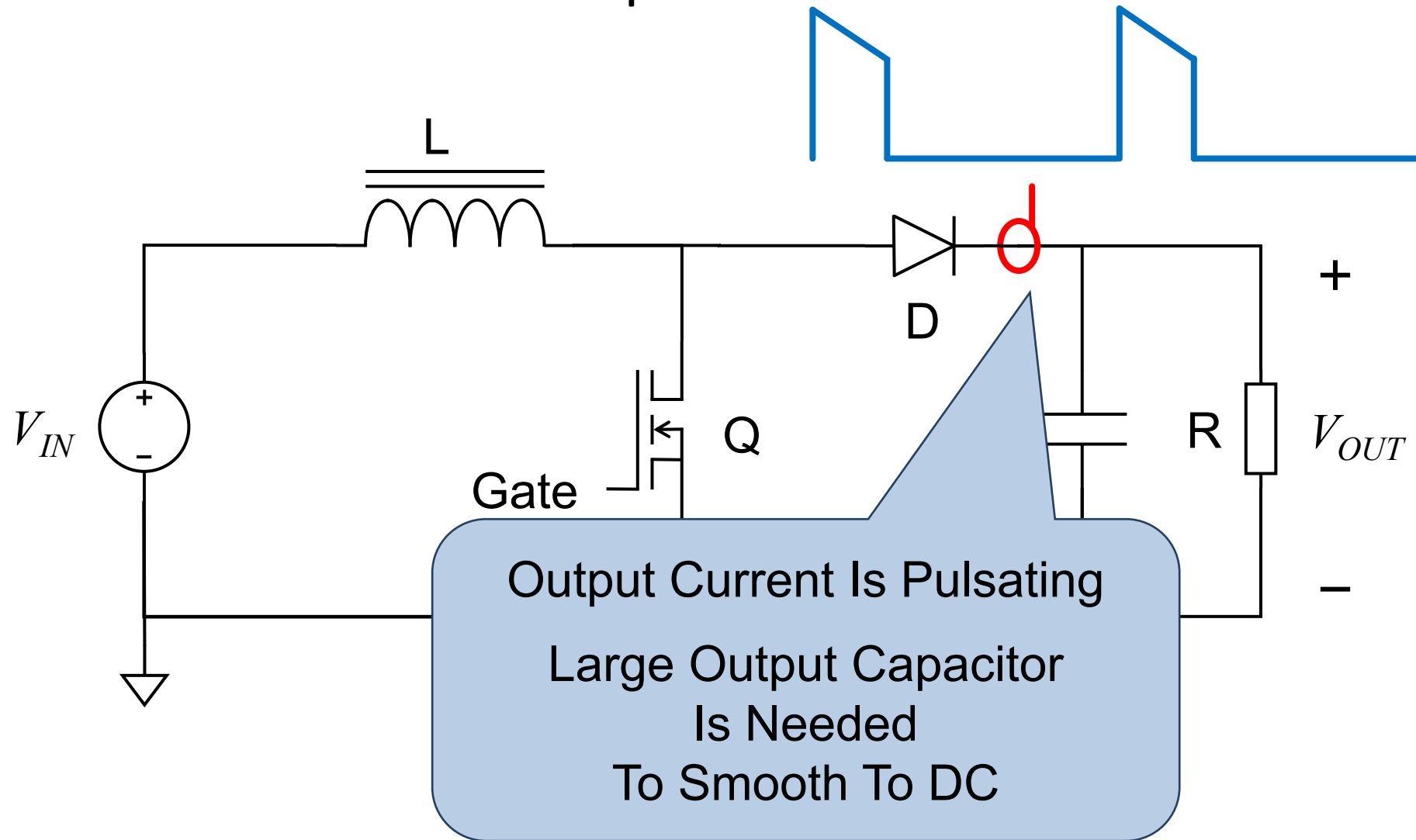

Boost Converter Input Current

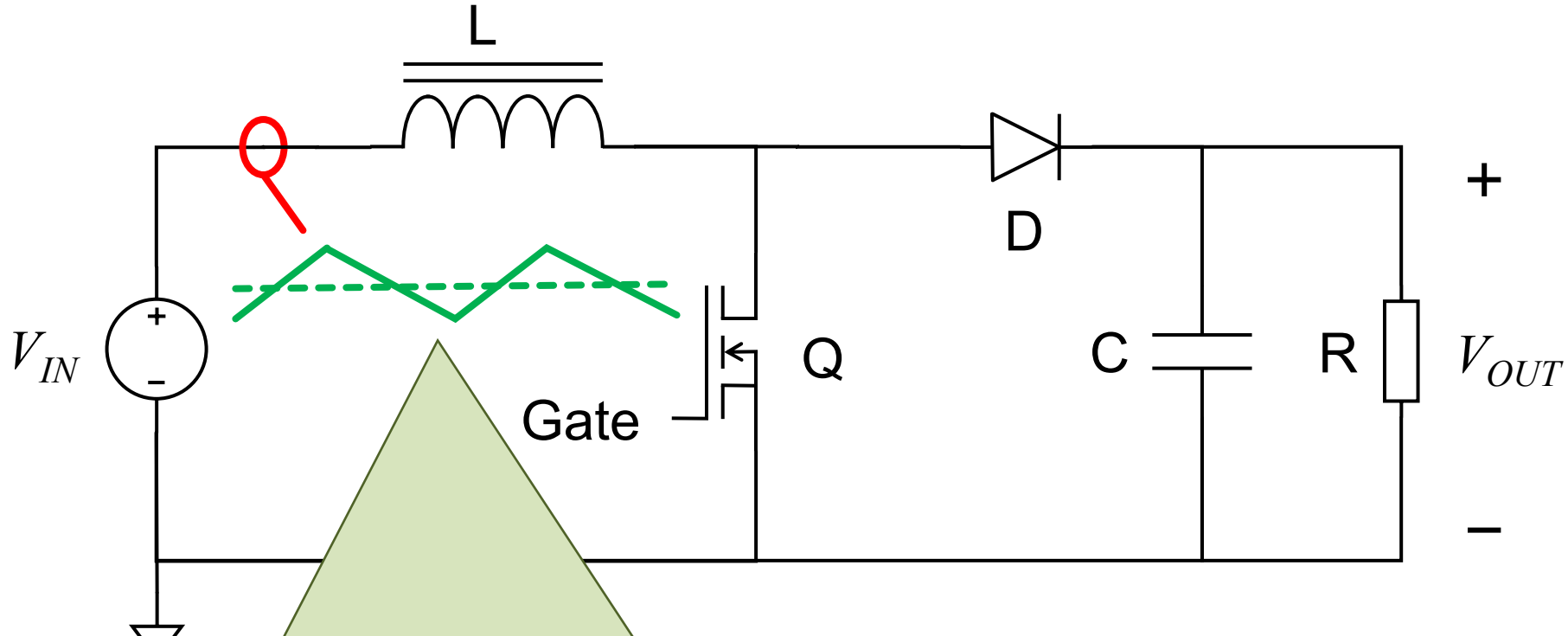

Input Current Is Not Pulsating
Small Ripple On DC Average Output Current

Boost Converter

Advantages


- Low Cost
- Low Parts Count

Disadvantages


- Non-Isolated
- Only Voltage Step Up
- High Efficiency Is Difficult
- Continuous Conduction Mode Harder To Control

Buck-Boost Converter


Buck-Boost Converter

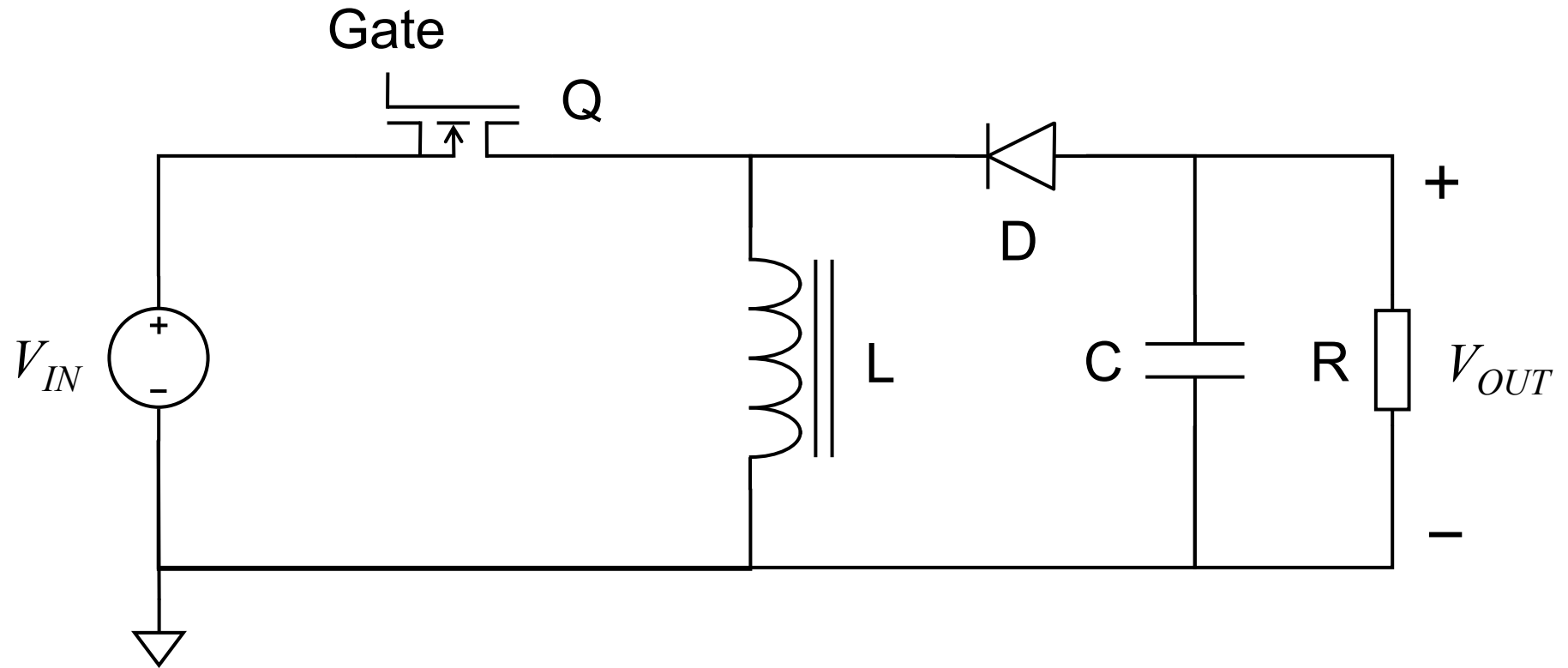


Buck-Boost Converter

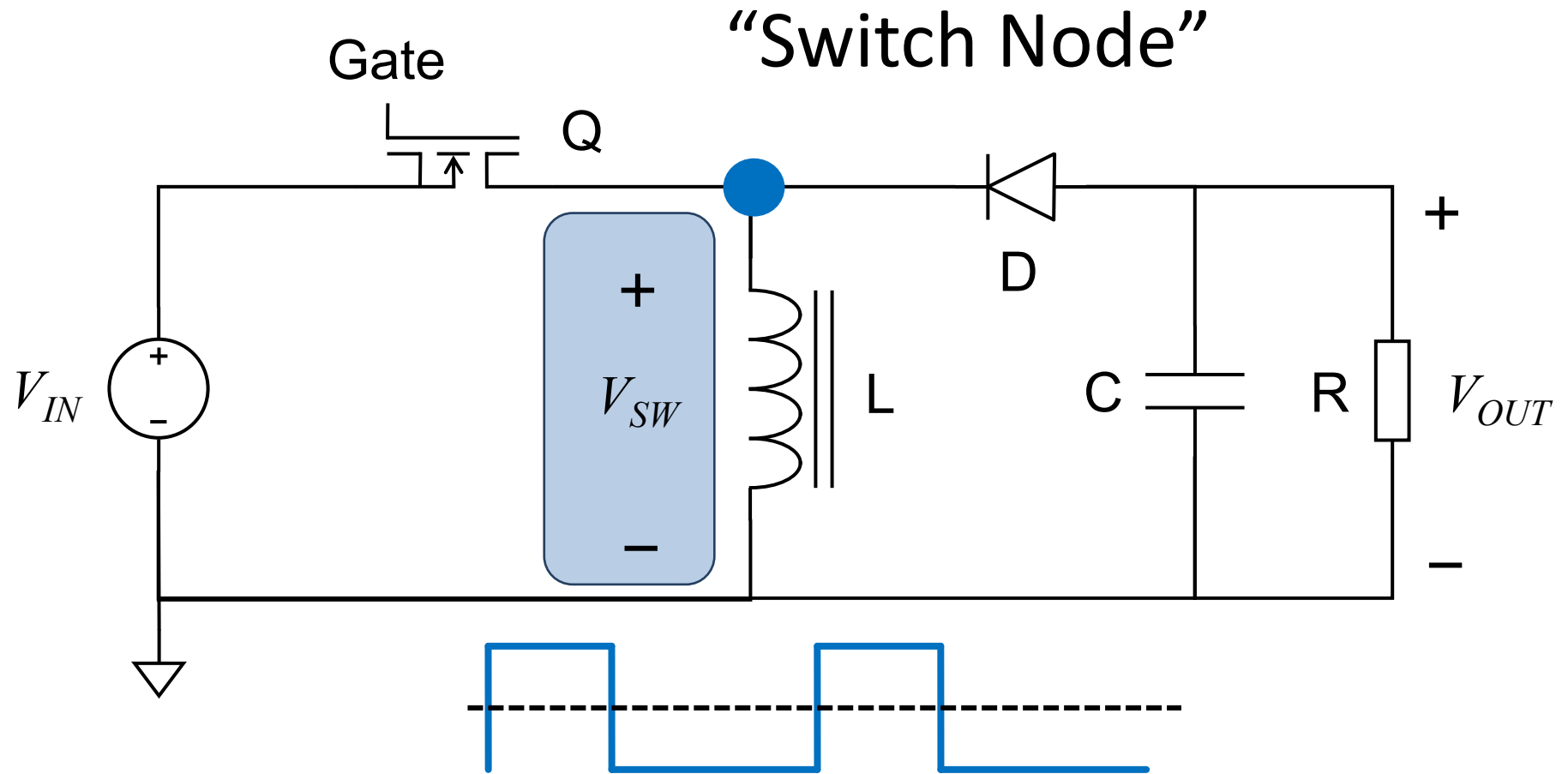

Buck-Boost Converter On Time

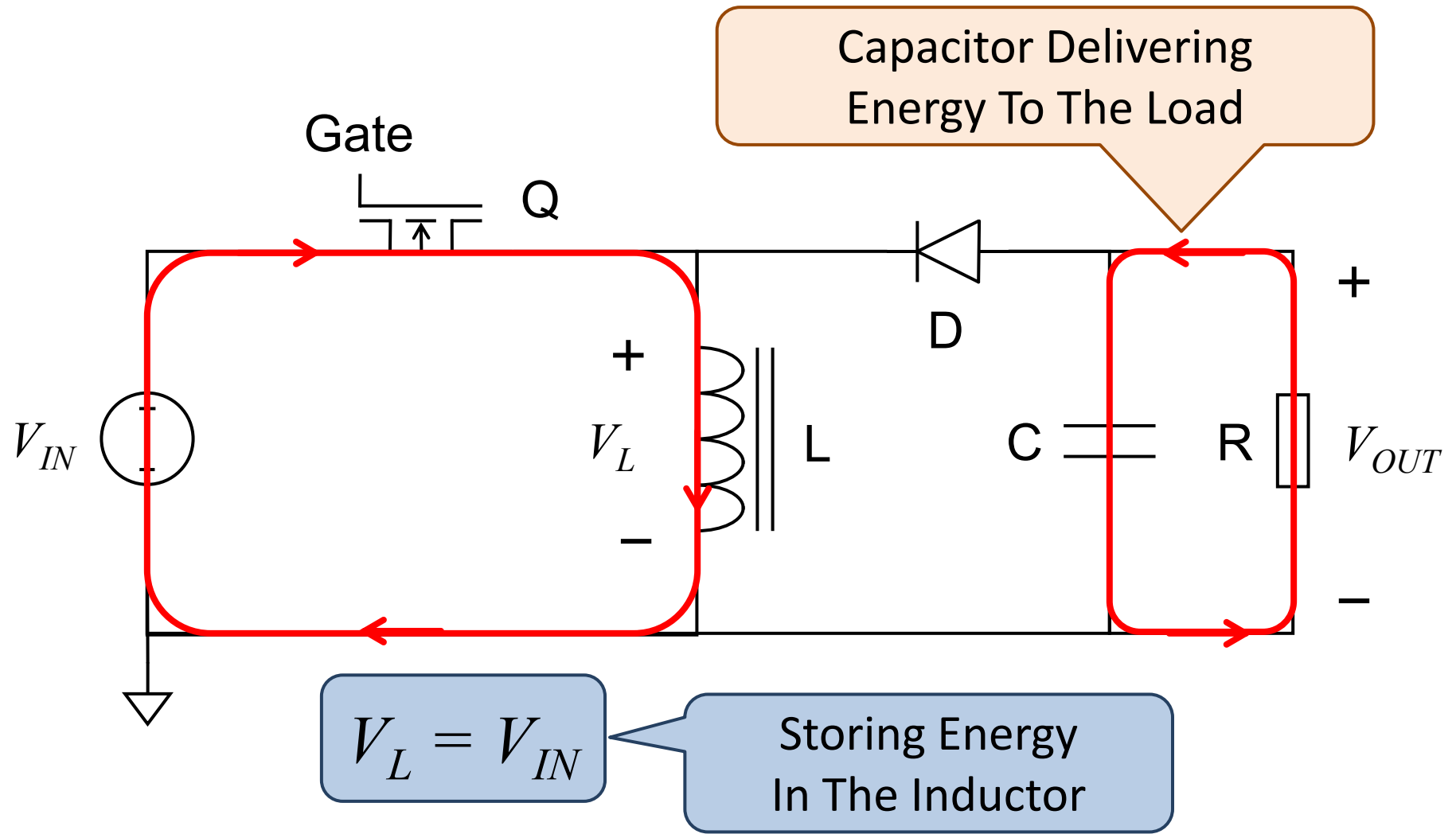

Buck-Boost Converter Off Time

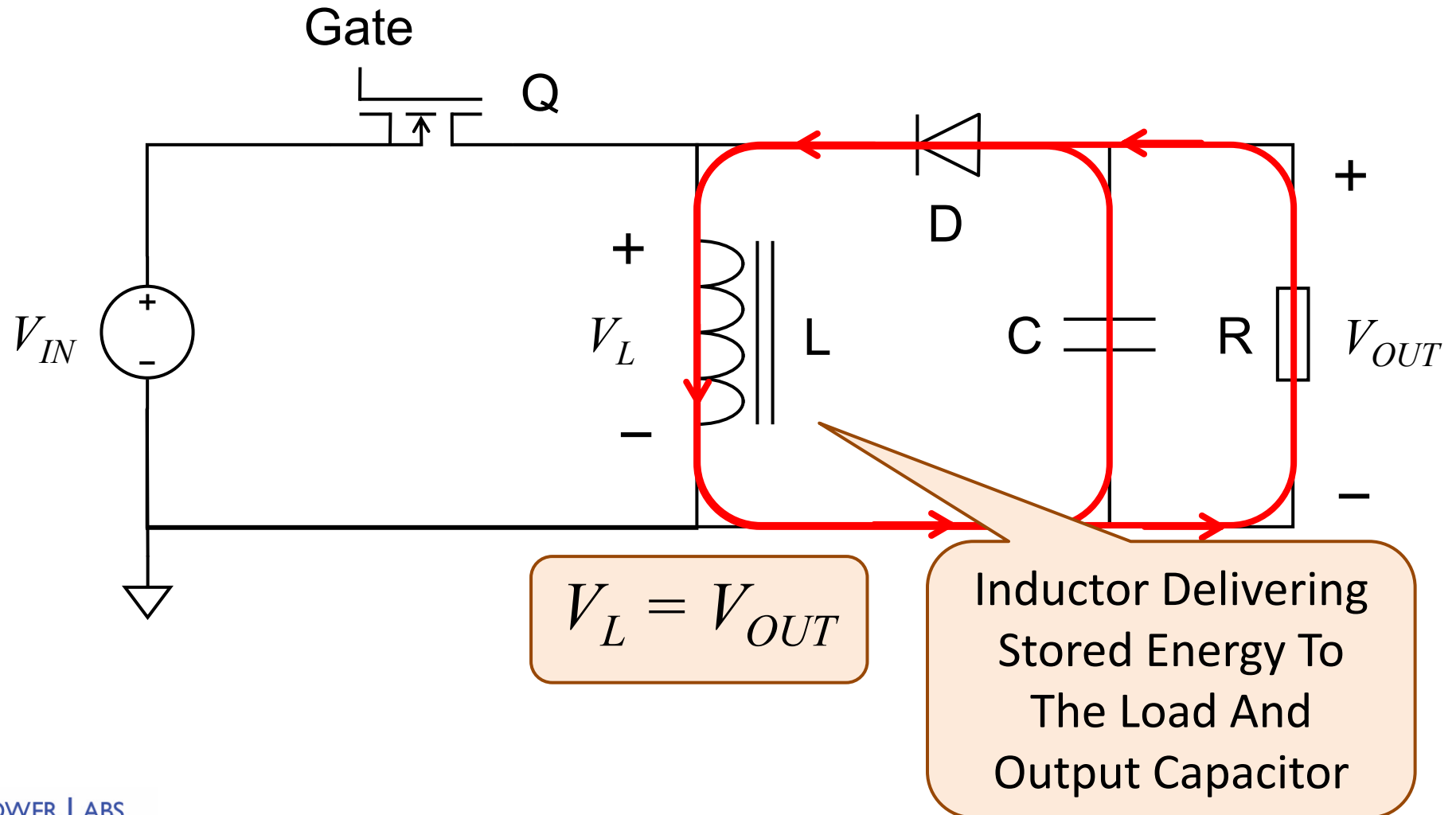

Inductor Volt-Second Balance


If V_{IN} Is Positive

$$V_{IN} \cdot T_{ON} + V_{OUT} \cdot T_{OFF} = 0$$


If V_{OUT} Must Be Negative

Buck-Boost Converter Energy Flow


On Time

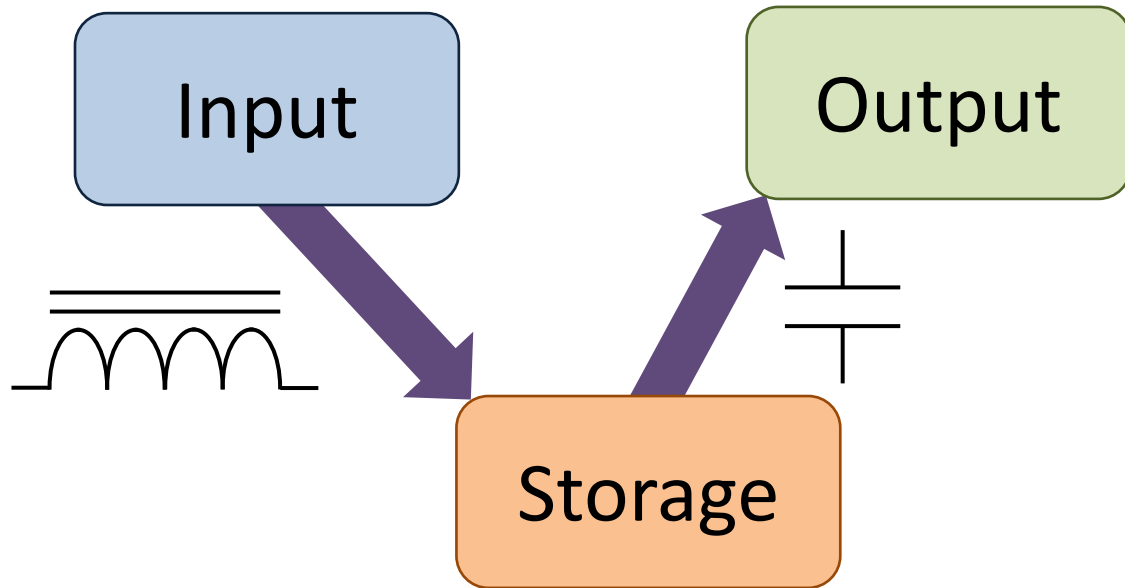

Off Time

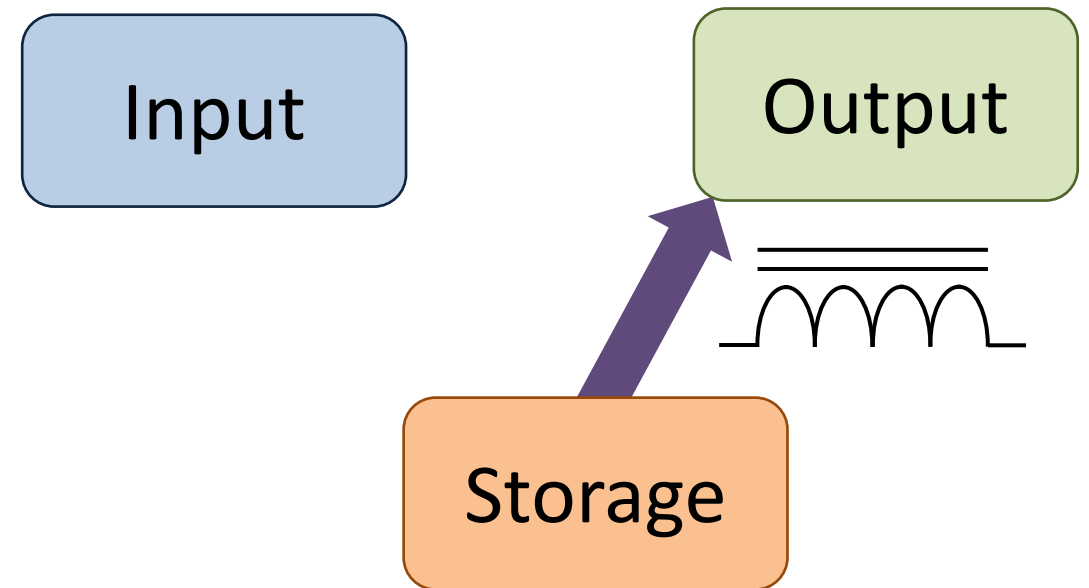


Buck-Boost Converter Waveforms

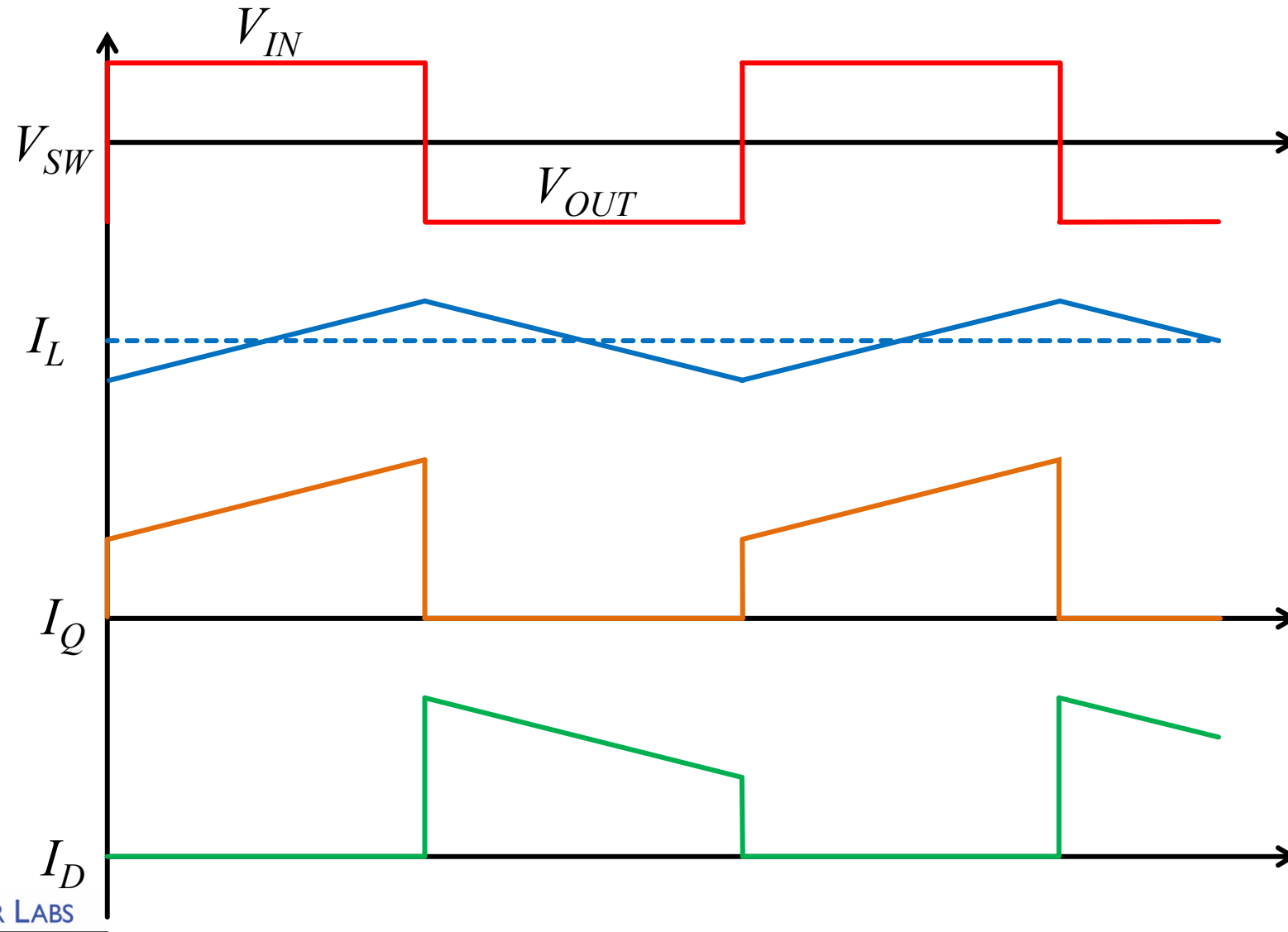

Buck-Boost Conversion Ratio
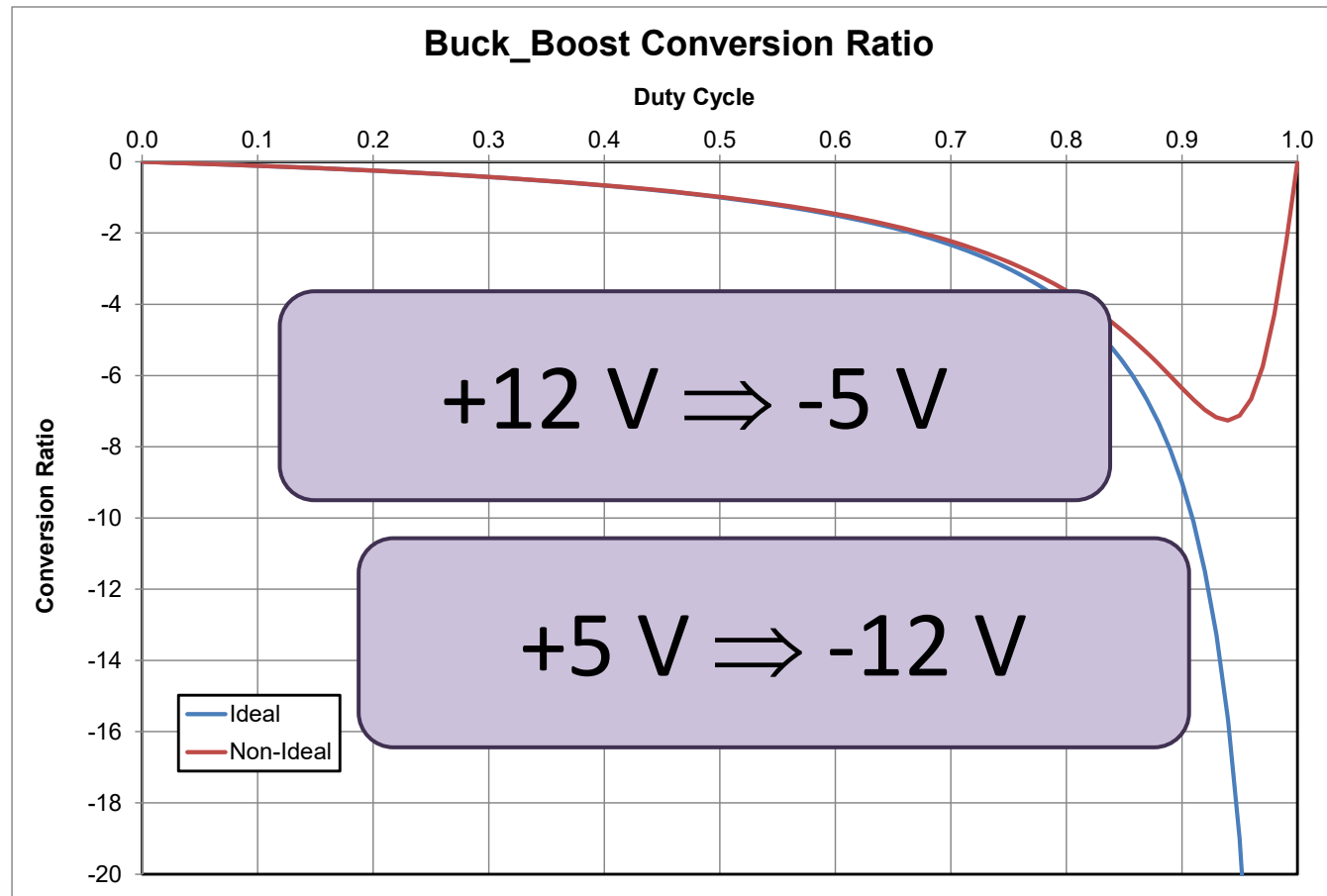
$$V_{OUT} = -\frac{D}{1-D} \cdot V_{IN} = -\frac{D}{D'} \cdot V_{IN}$$




Buck-Boost Converter

Advantages

- Negative Voltage From Positive Voltage
- Low Cost
- Low Parts Count

No Direct Flow
Of Energy From
Input To Output




Disadvantages


- Non-Isolated
- High Voltage Stress On Transistor And Diode
- Continuous Conduction Mode Harder To Control
- High Efficiency Is Difficult

Flyback Converter (Transformer Isolated Buck-Boost Converter)


Flyback Converter

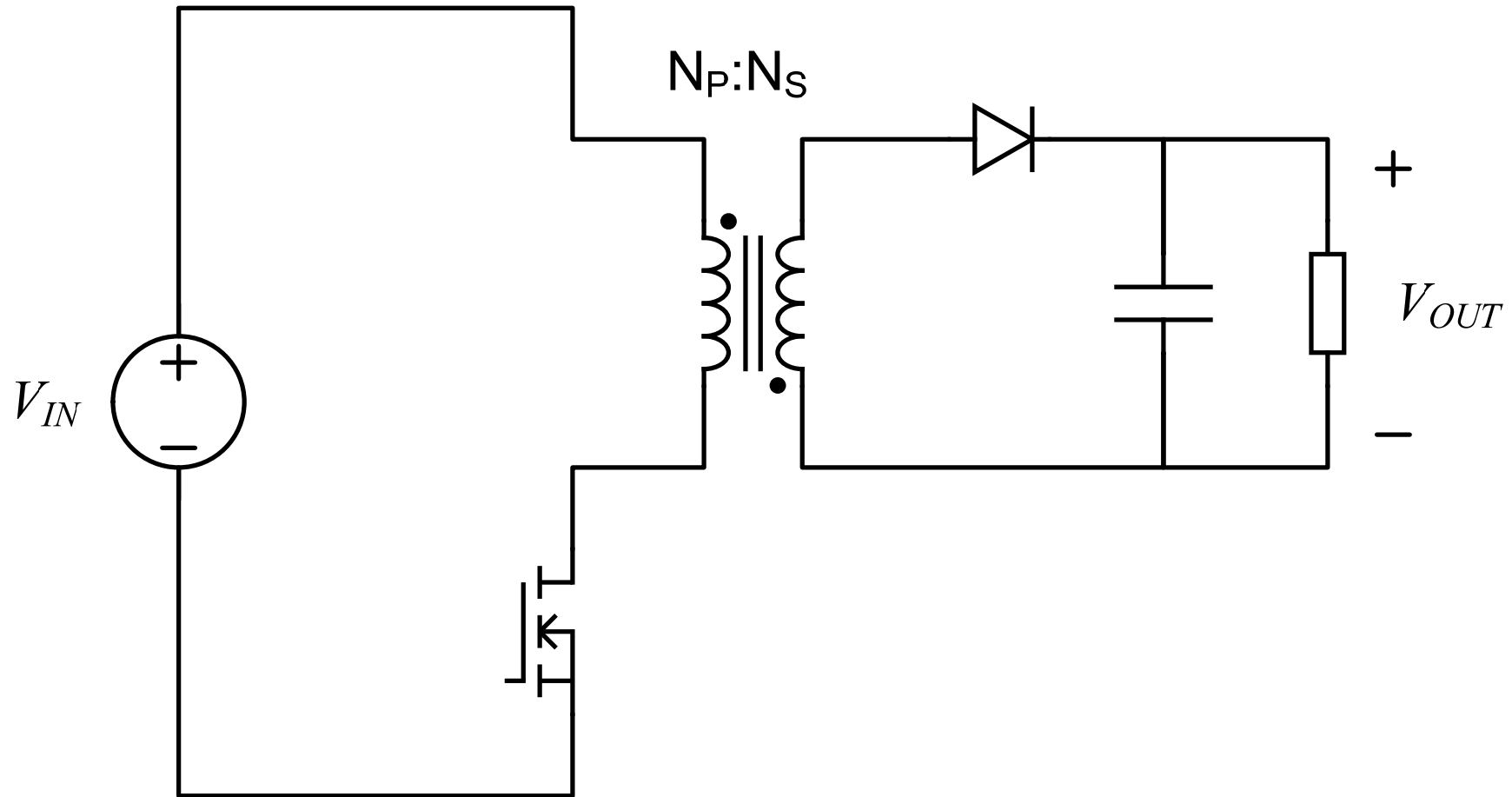


Flyback Converter

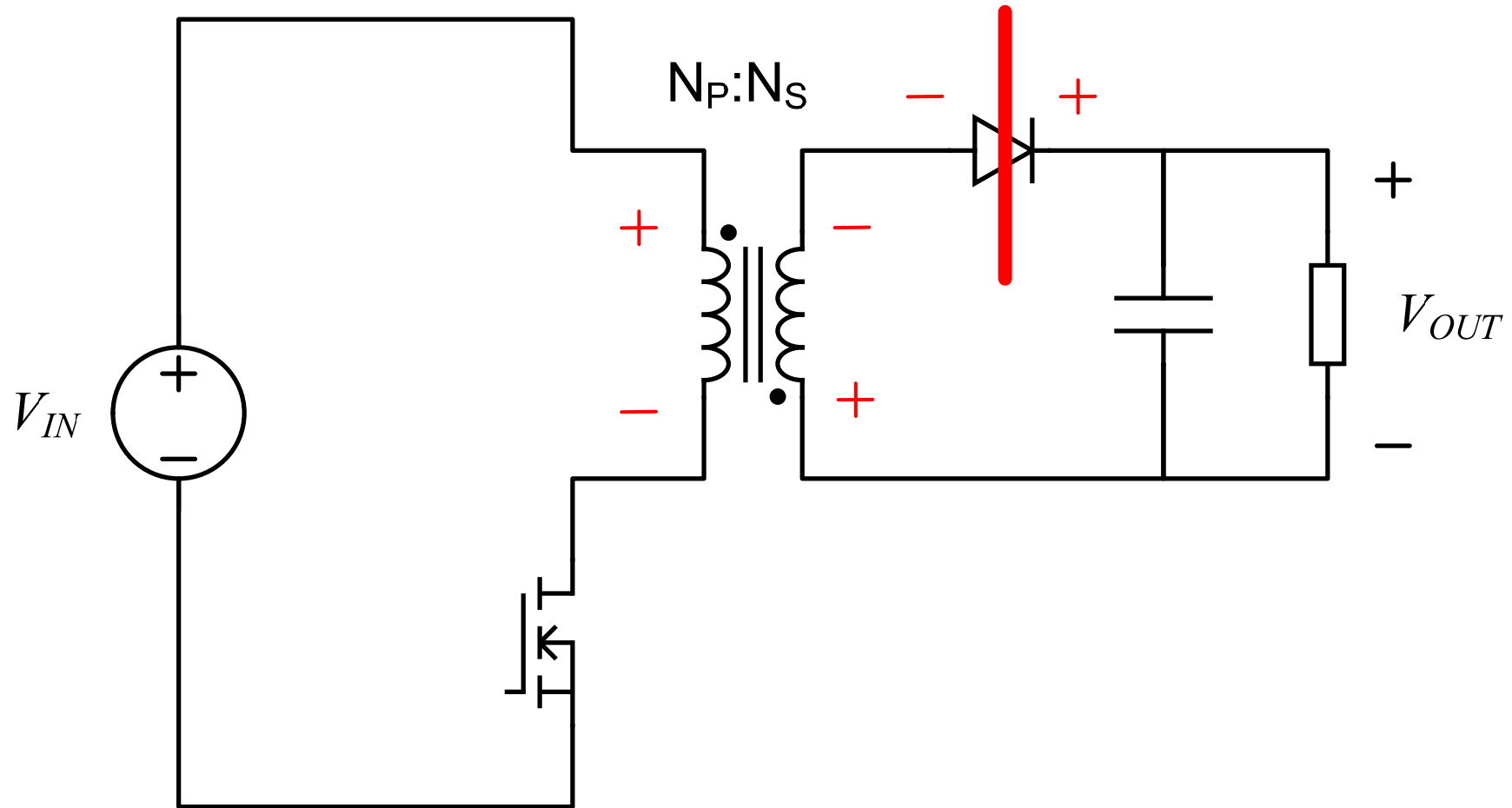


Flyback Converter

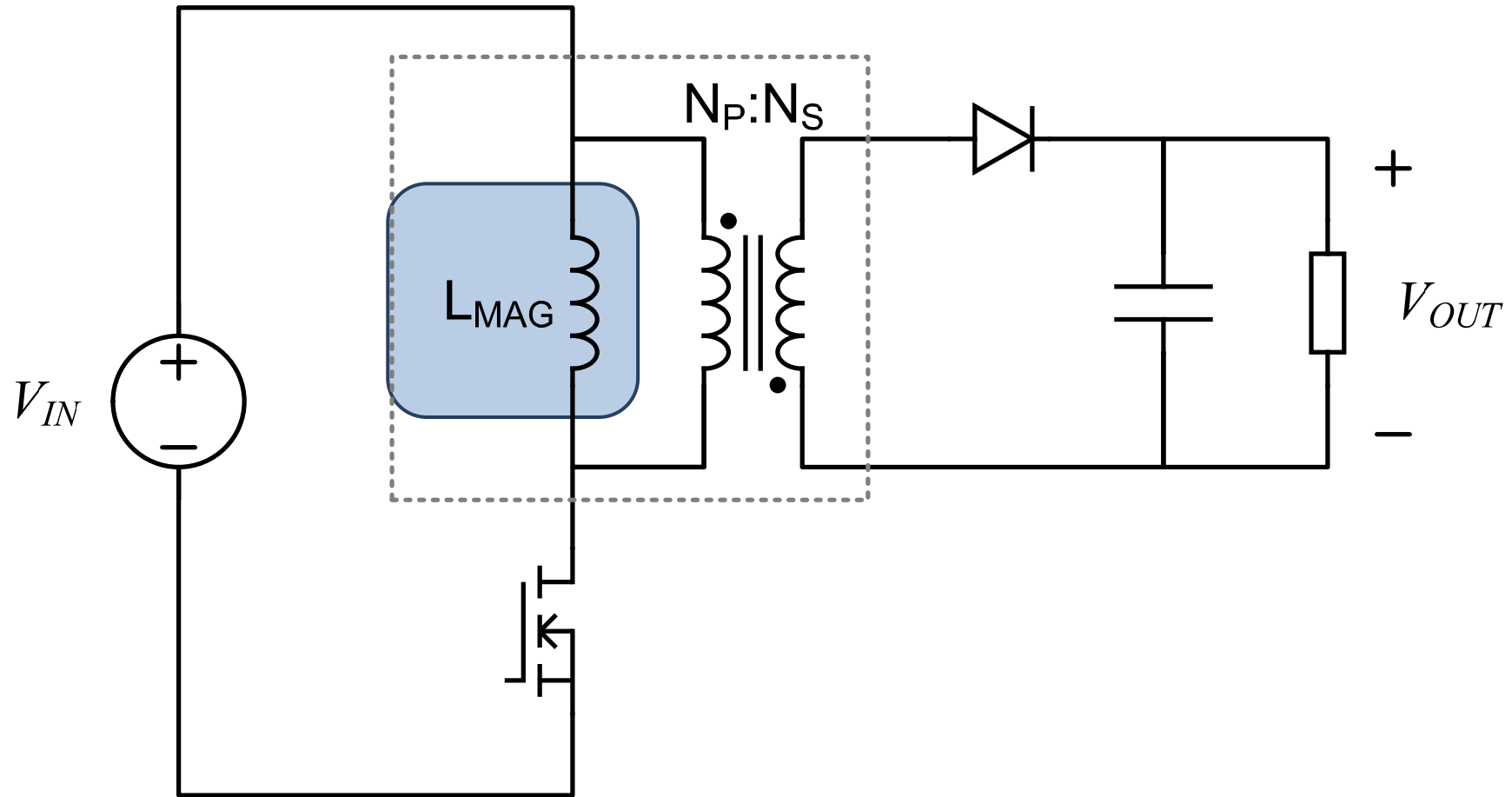


Flyback Converter On Time

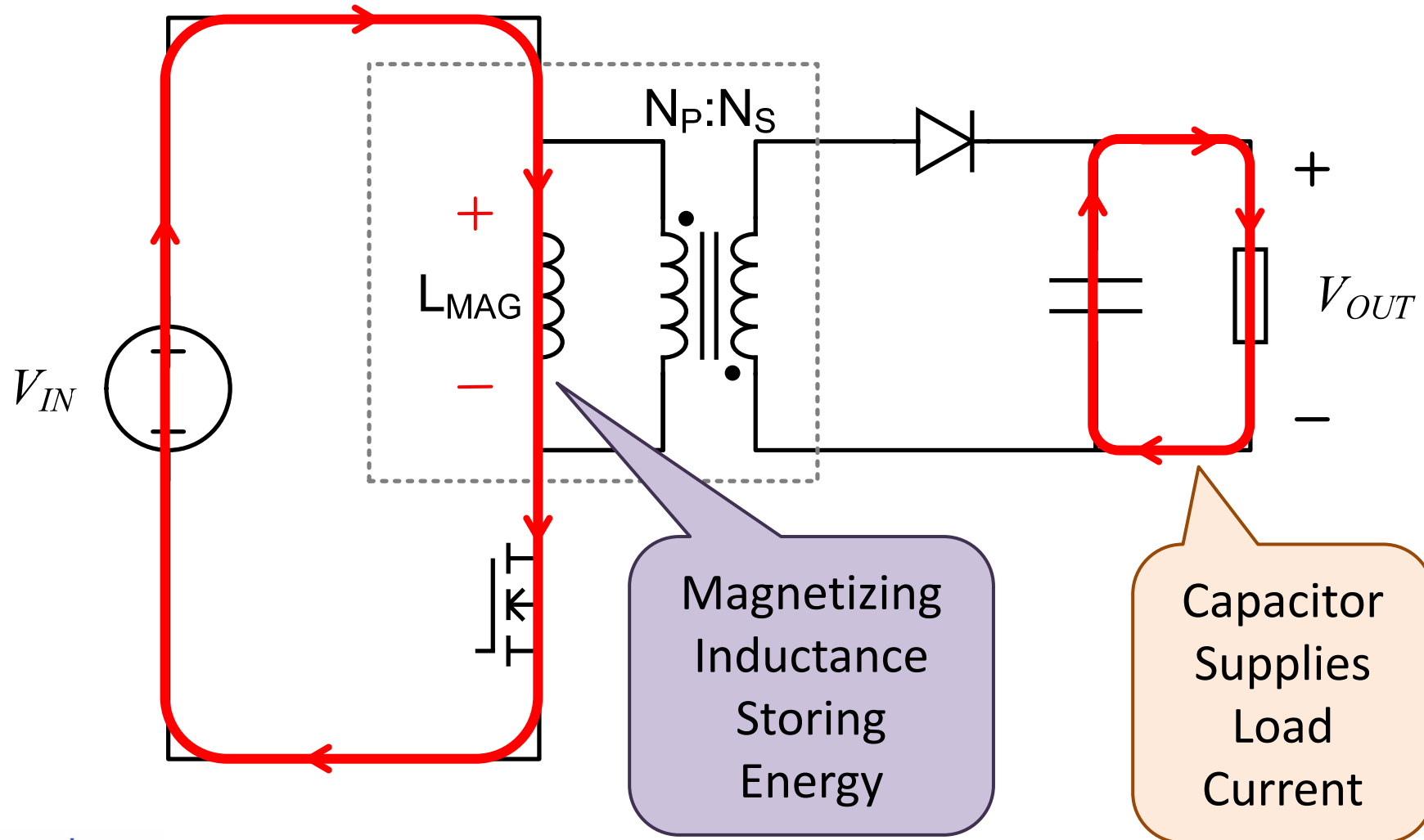


Flyback Converter Reset Time

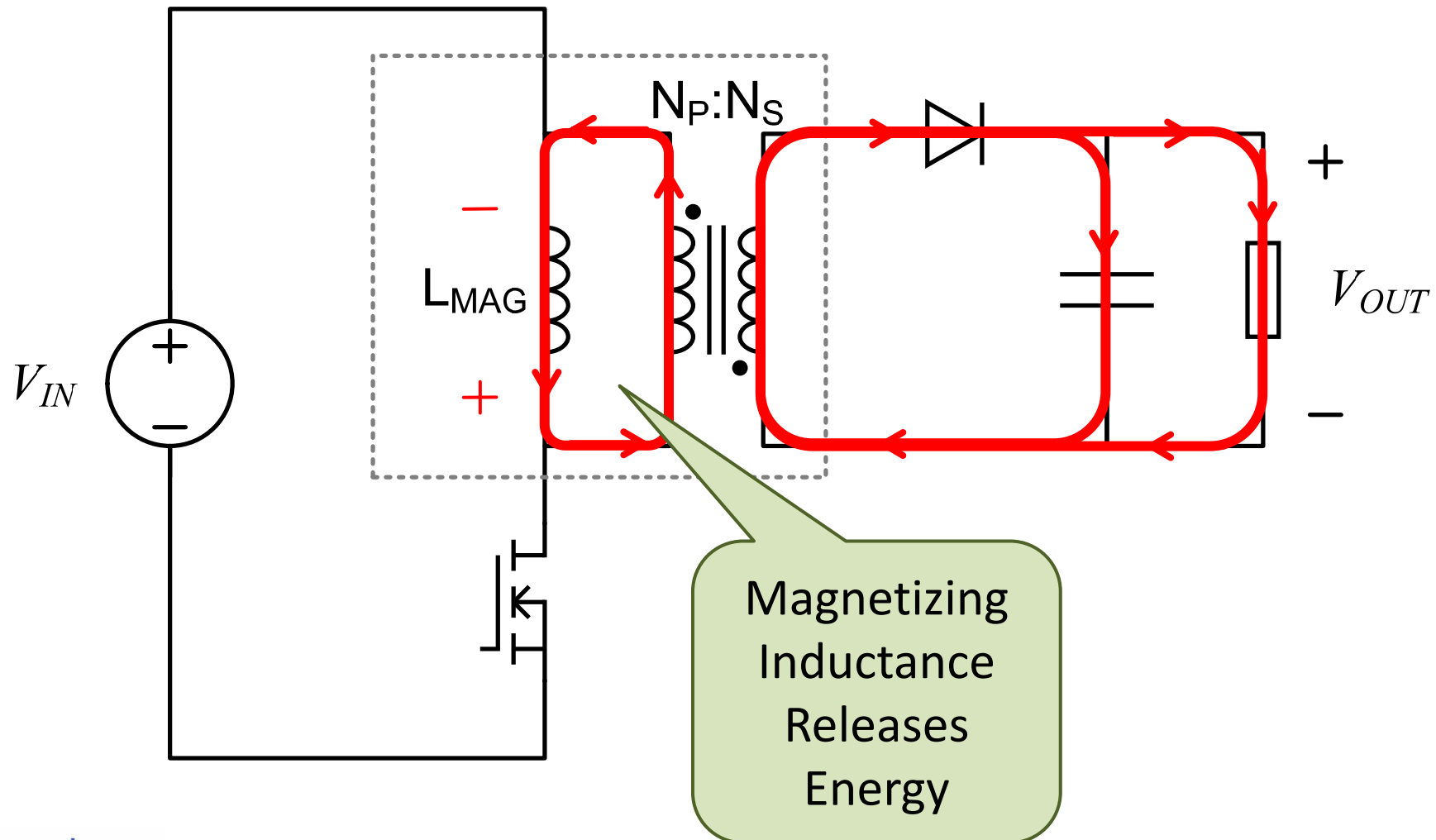

Flyback Converter Reset Time

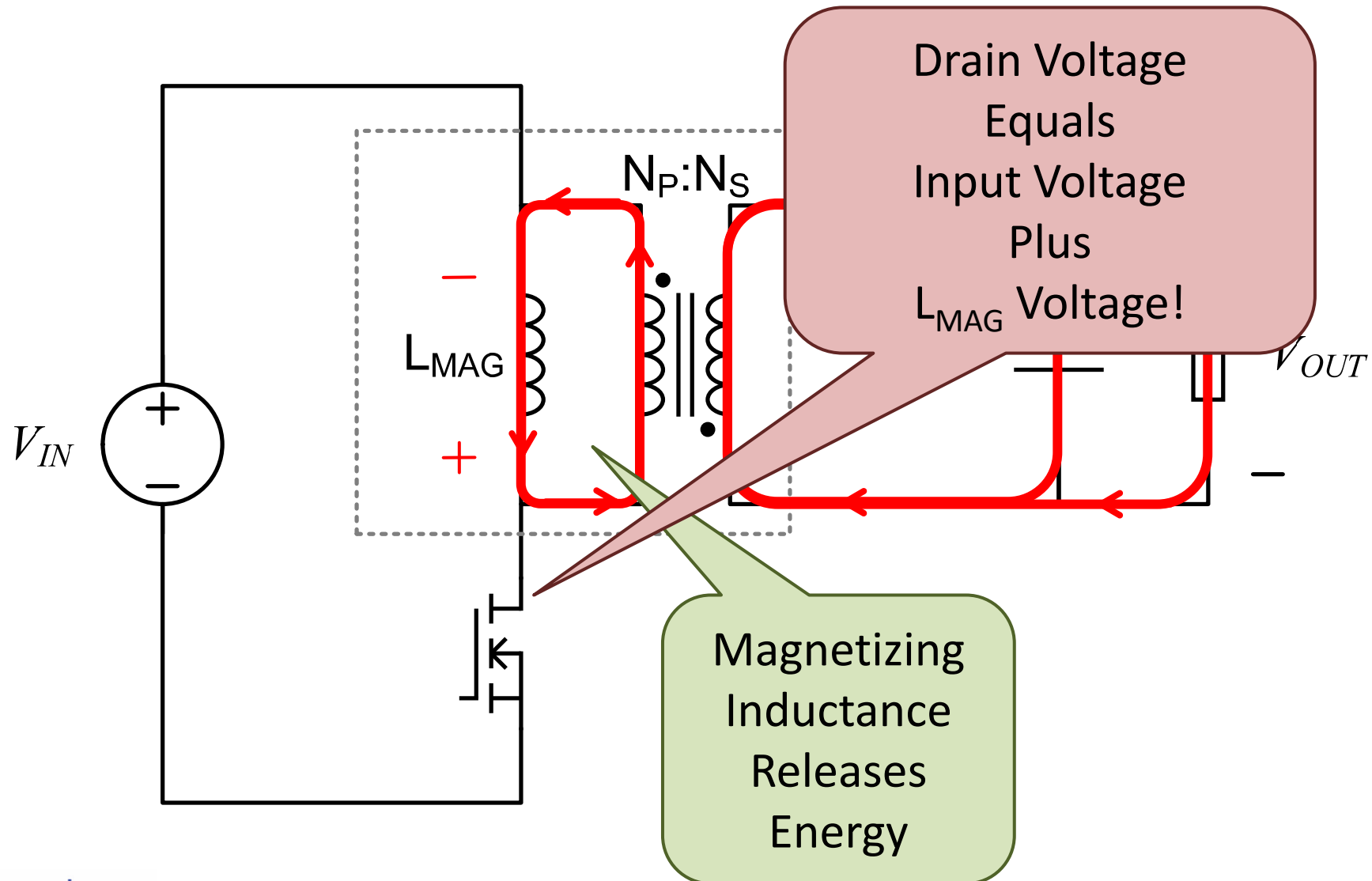


Flyback Converter Idle Time

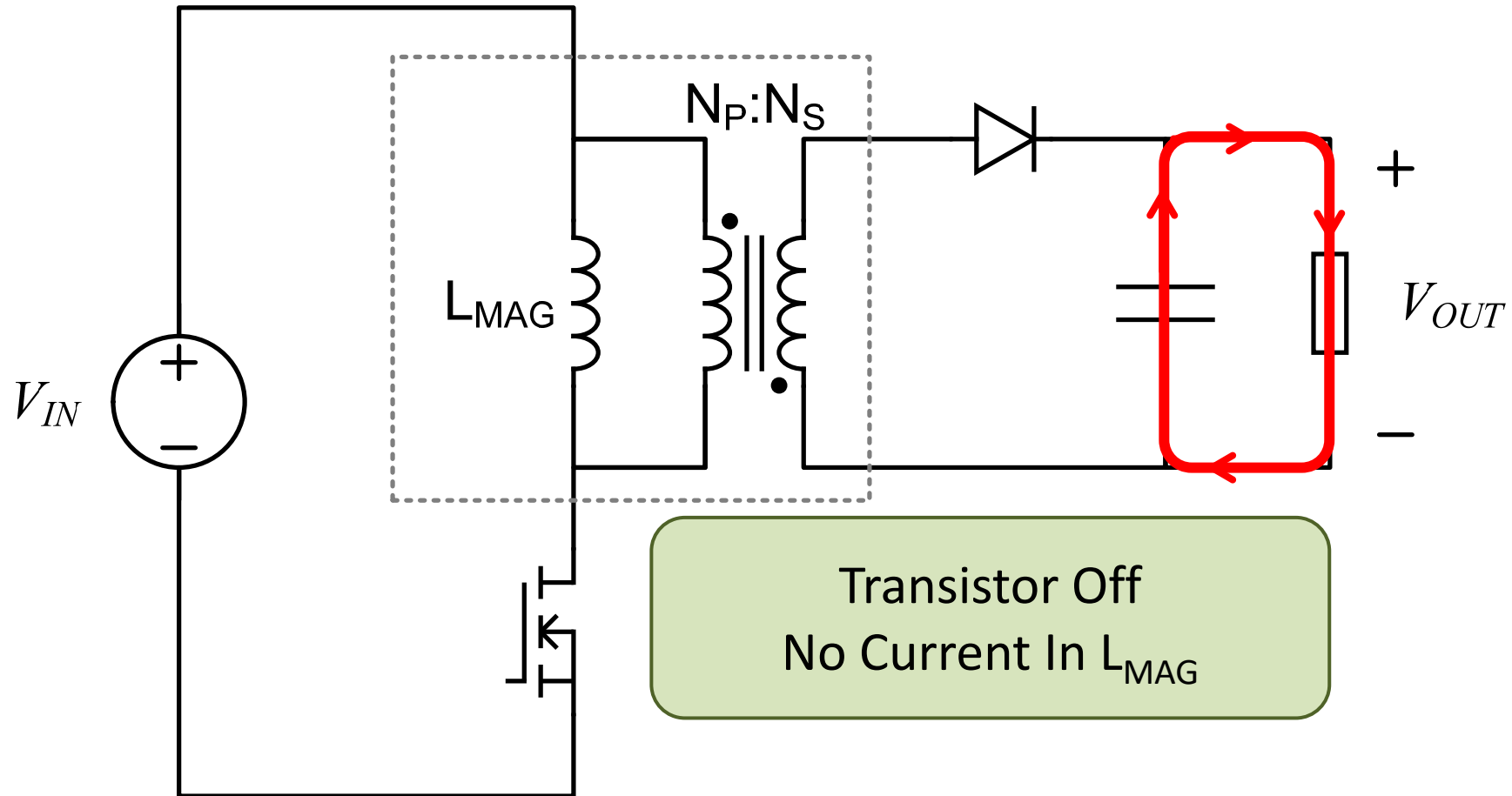


Flyback Converter Energy Flow

On Time

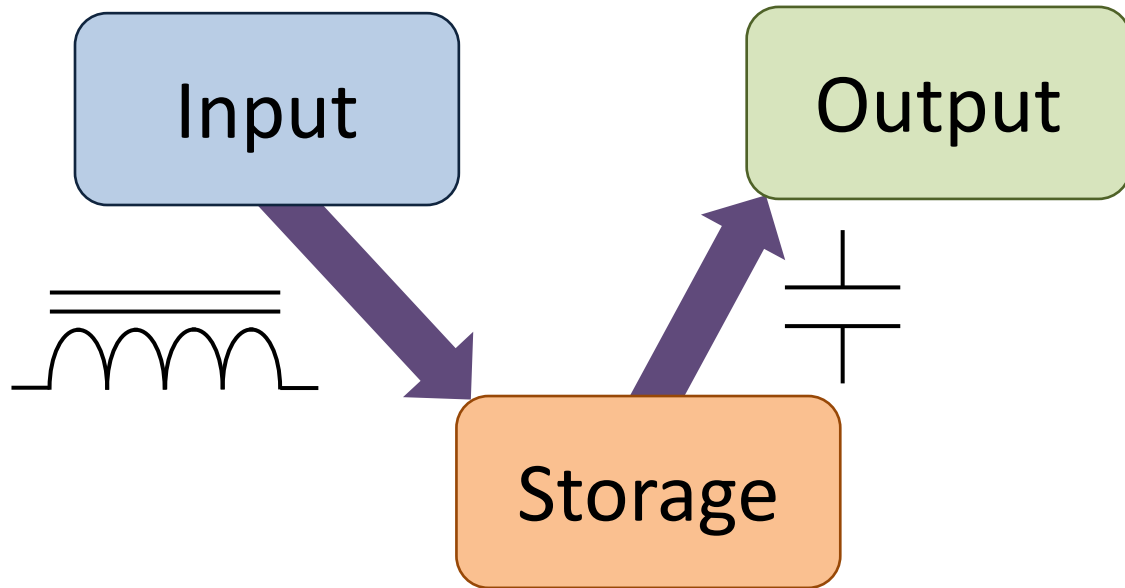

Off Time

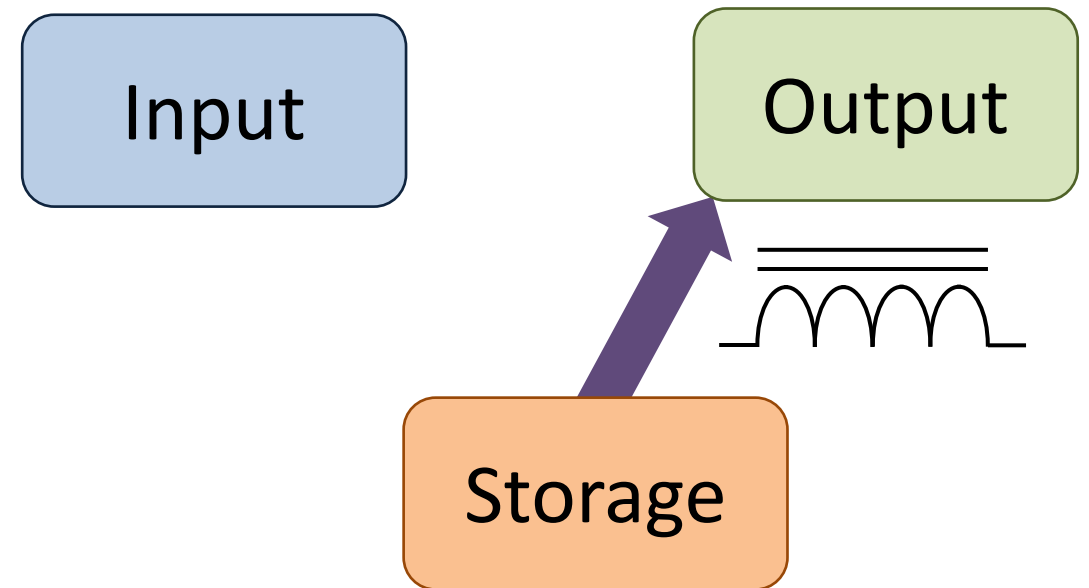


Flyback Energy Flow

On Time:
Store Energy In Flyback
Inductor Core
“Fill The Bucket”


Reset Time:
Deliver Stored Energy
To The Output
“Empty The Bucket”

Idle Time:
“Take A Break”

Discontinuous Conduction Mode

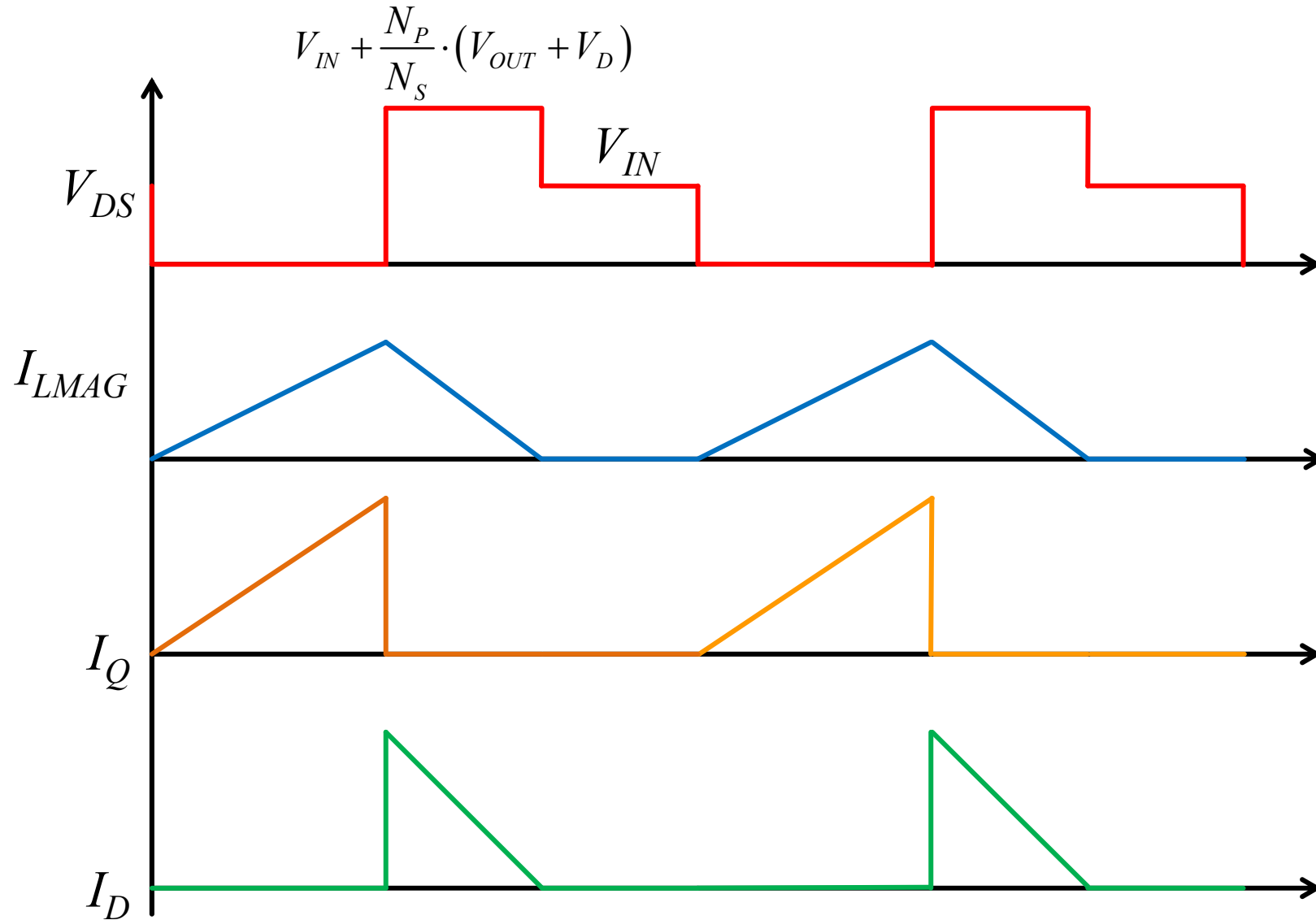

Discontinuous Conduction Mode

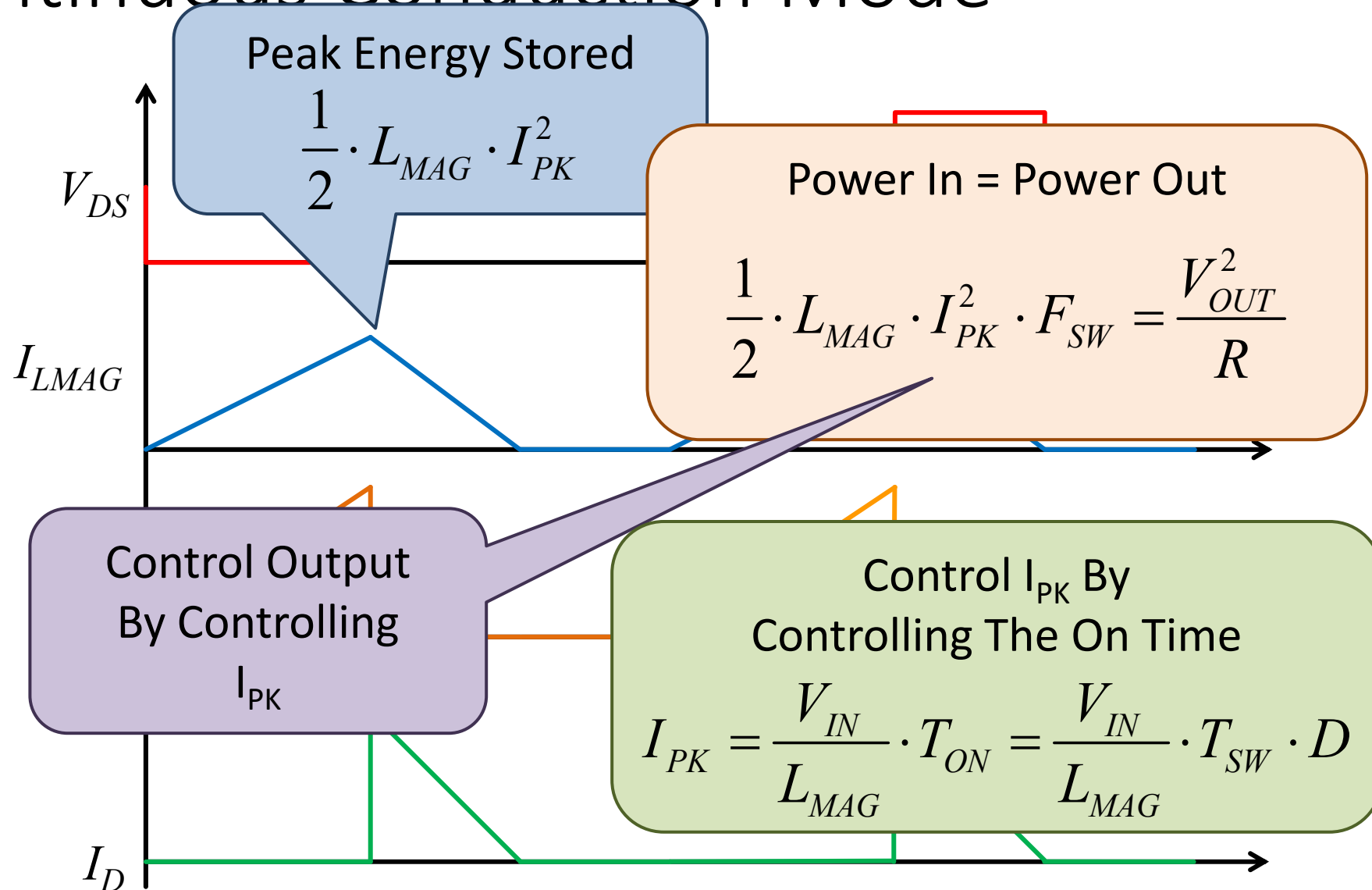

Discontinuous Conduction Mode

$$\frac{V_{OUT}^2}{R} = \frac{1}{2} \cdot L_{MAG} \cdot I_{PK}^2 \cdot F_{SW}$$

Start With
Power In = Power Out

$$= \frac{1}{2} \cdot L_{MAG} \cdot \left(\frac{V_{IN} \cdot T_{ON}}{L_{MAG}} \right)^2 \cdot F_{SW}$$

$$V_{OUT}^2 = \frac{R \cdot L_{MAG}}{2} \cdot \frac{V_{IN}^2 \cdot T_{ON}^2}{L_{MAG}^2} \cdot \frac{1}{T_{SW}} \cdot \frac{T_{SW}}{T_{SW}}$$

$$= \frac{R \cdot T_{SW}}{2 \cdot L_{MAG}} \cdot \frac{V_{IN}^2 \cdot T_{ON}^2}{T_{SW}^2} = \frac{R \cdot T_{SW}}{2 \cdot L_{MAG}} \cdot V_{IN}^2 \cdot D^2$$


$$V_{OUT} = \sqrt{\frac{R \cdot T_{SW}}{2 \cdot L_{MAG}} \cdot V_{IN}^2 \cdot D^2}$$

Get A
"Buck Like"
Conversion
Ratio


$$V_{OUT} = D \cdot V_{IN} \cdot \sqrt{\frac{R \cdot T_{SW}}{2 \cdot L_{MAG}}}$$

Discontinuous Conduction Mode
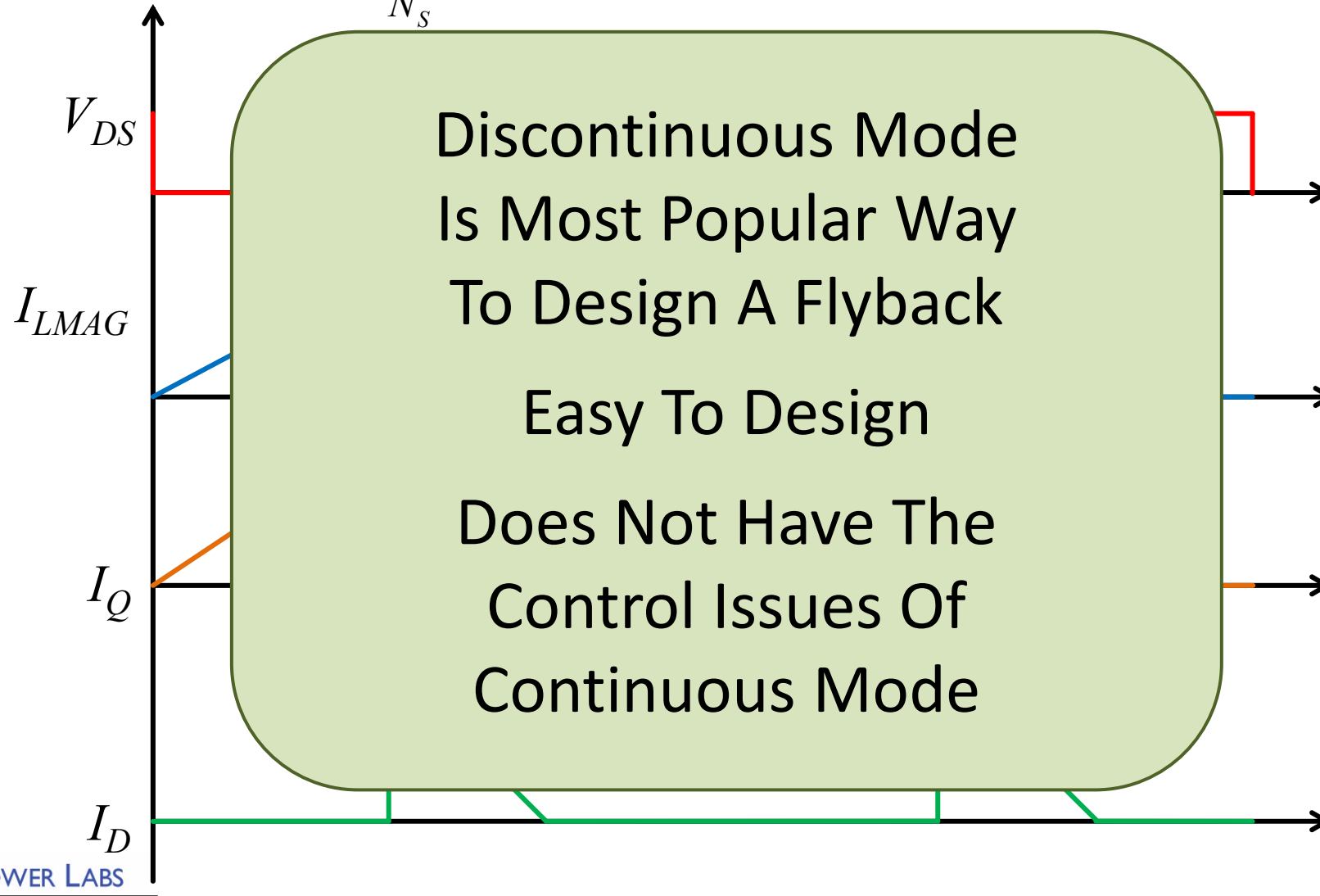
$$V_{IN} + \frac{N_P}{N_S} \cdot (V_{OUT} + V_D)$$




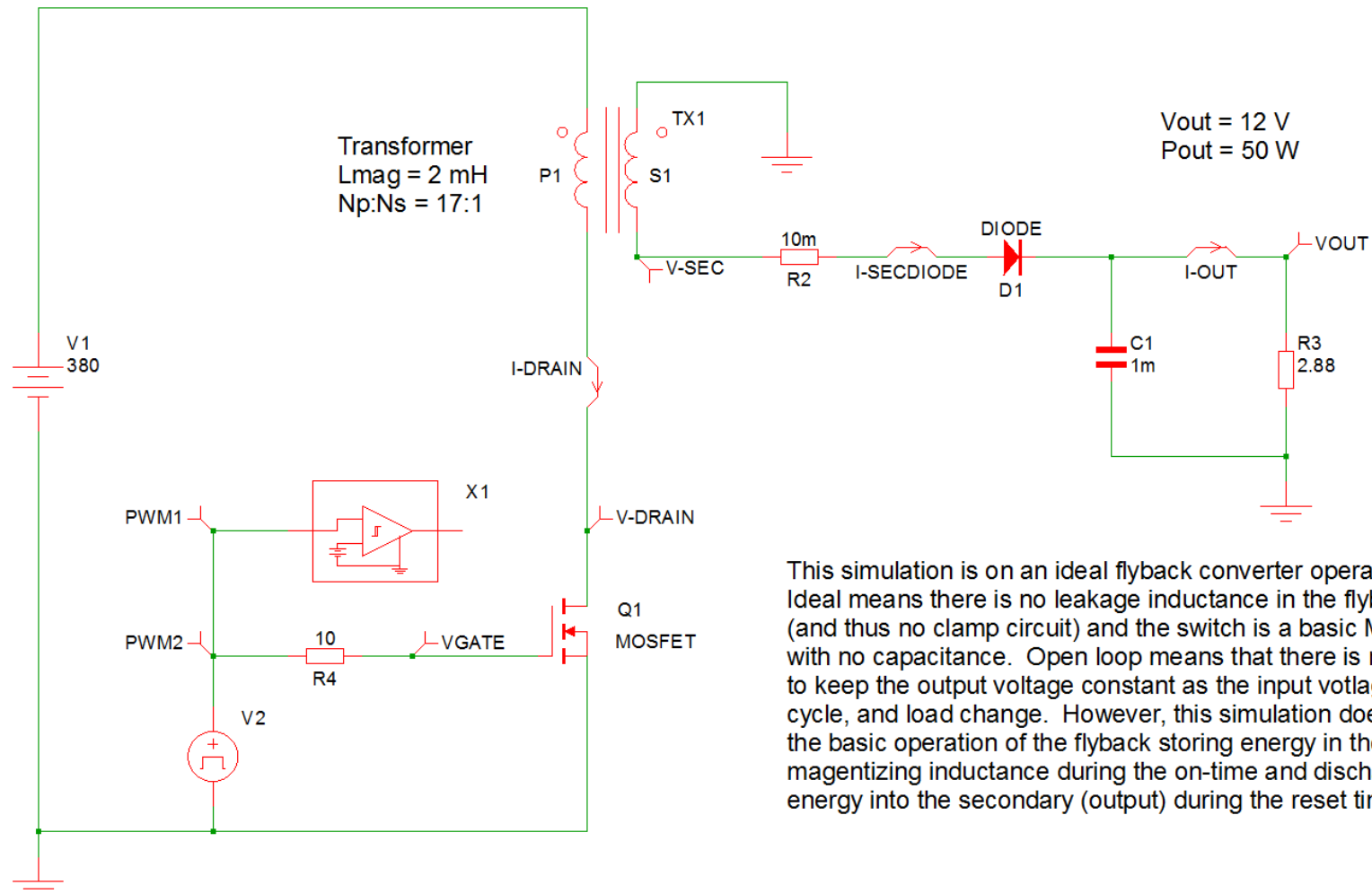Discontinuous Conduction Mode Ideal Flyback Simulation




This simulation is on an ideal flyback converter operating open loop. Ideal means there is no leakage inductance in the flyback inductor (and thus no clamp circuit) and the switch is a basic MOSFET with no capacitance. Open loop means that there is no feedback to keep the output voltage constant as the input voltage, duty cycle, and load change. However, this simulation does illustrate the basic operation of the flyback storing energy in the magnetizing inductance during the on-time and discharging that energy into the secondary (output) during the reset time.


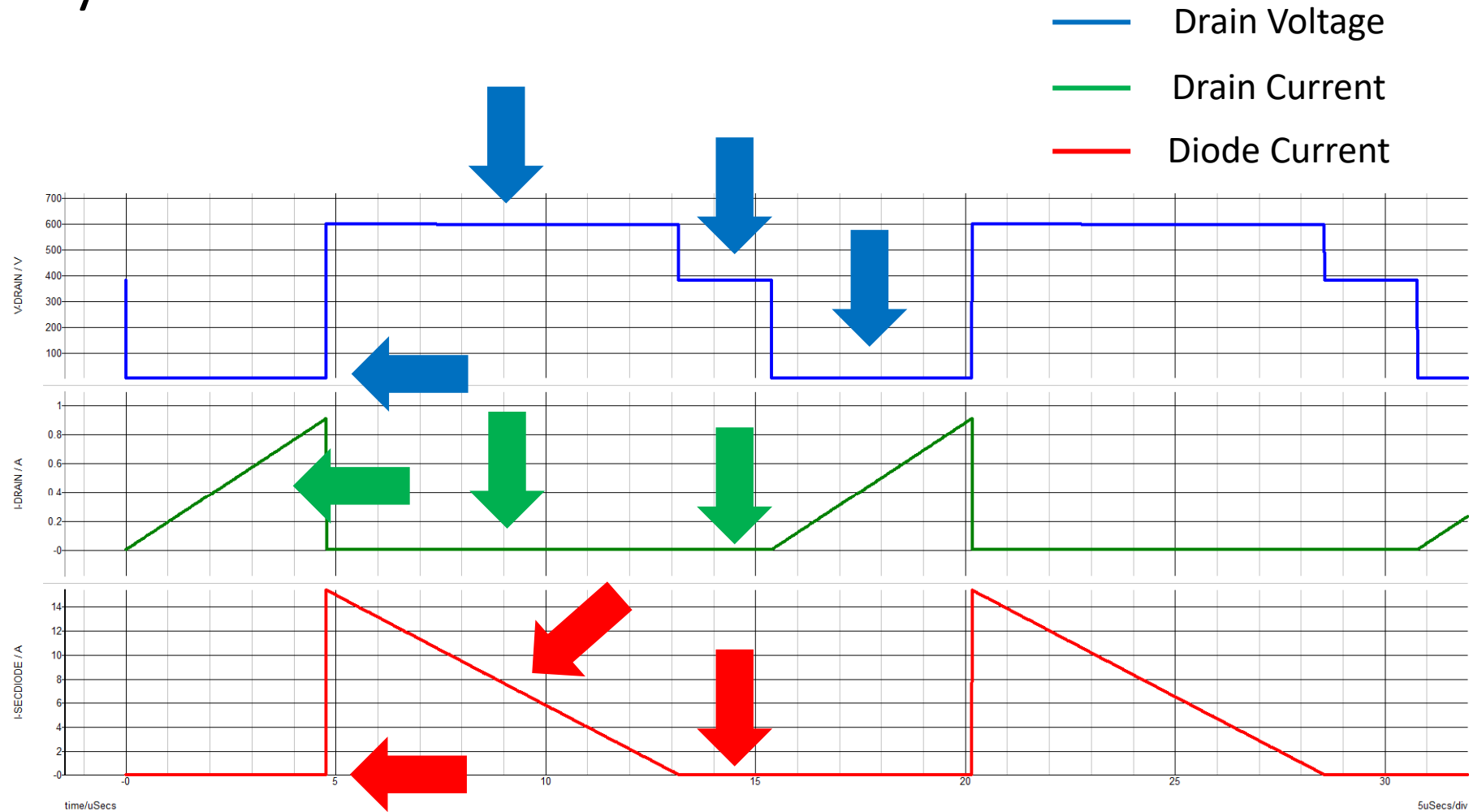
Discontinuous Conduction Mode Ideal Flyback Simulation




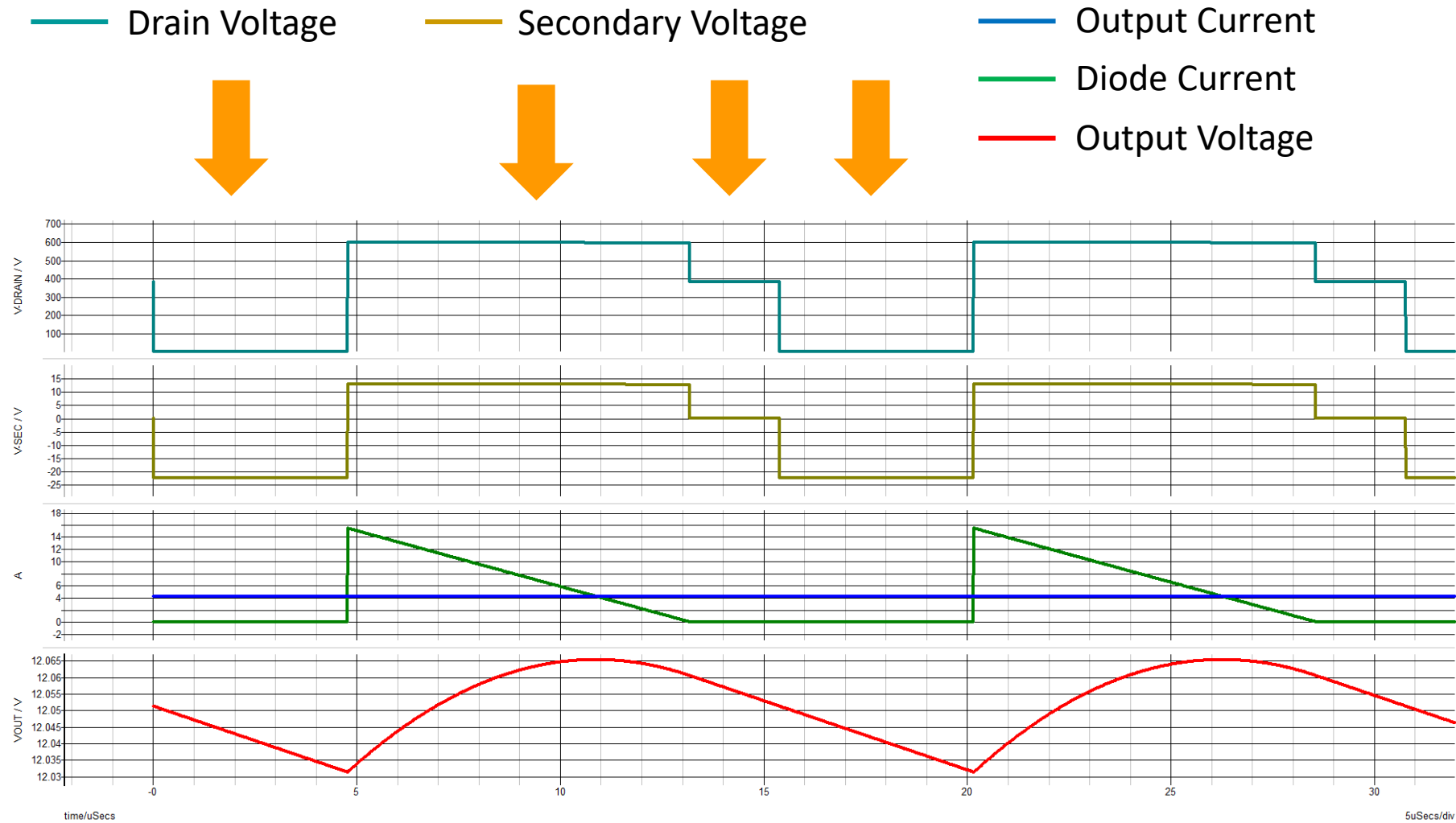
Discontinuous Conduction Mode Ideal Flyback Simulation



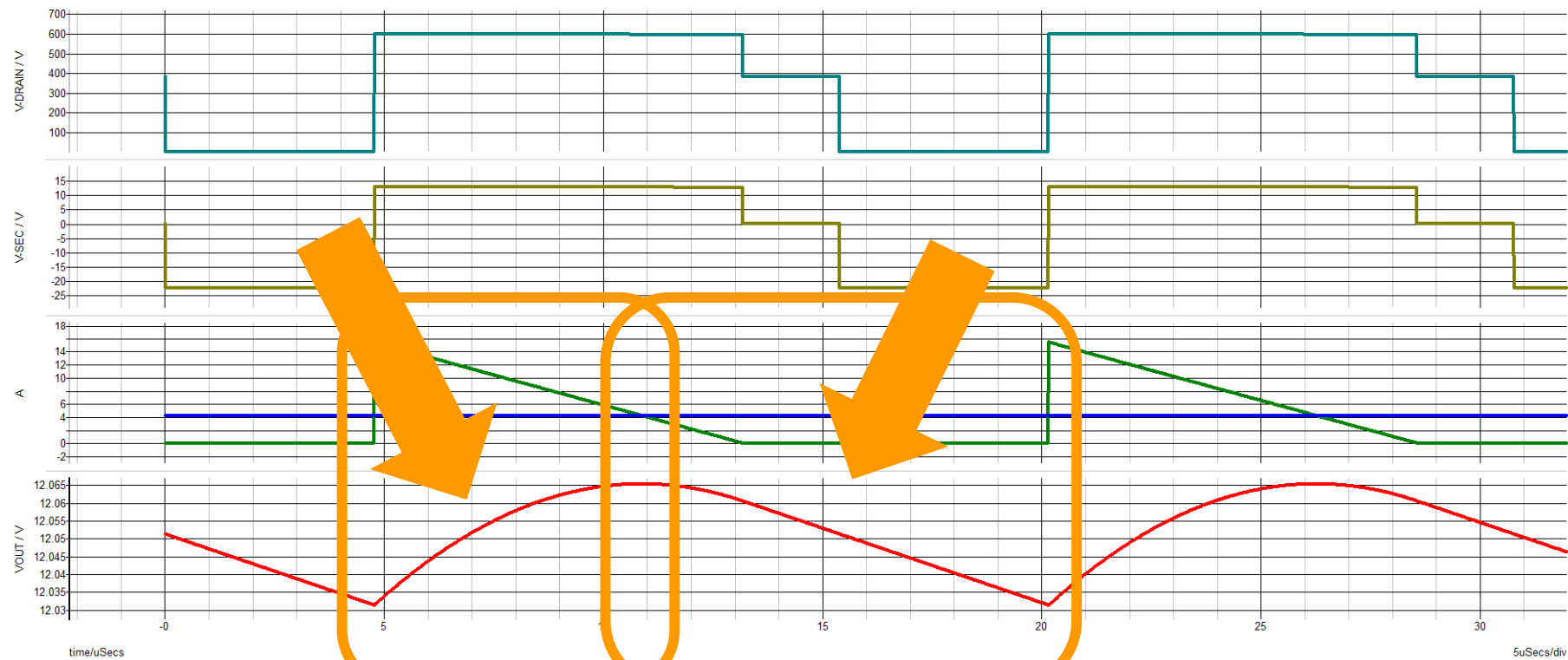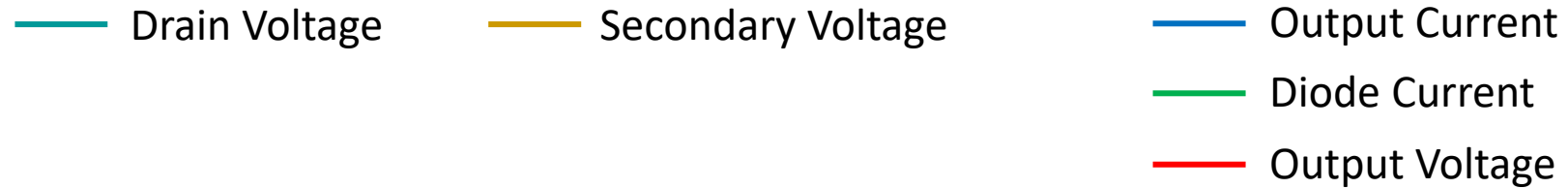
Discontinuous Conduction Mode Ideal Flyback Simulation



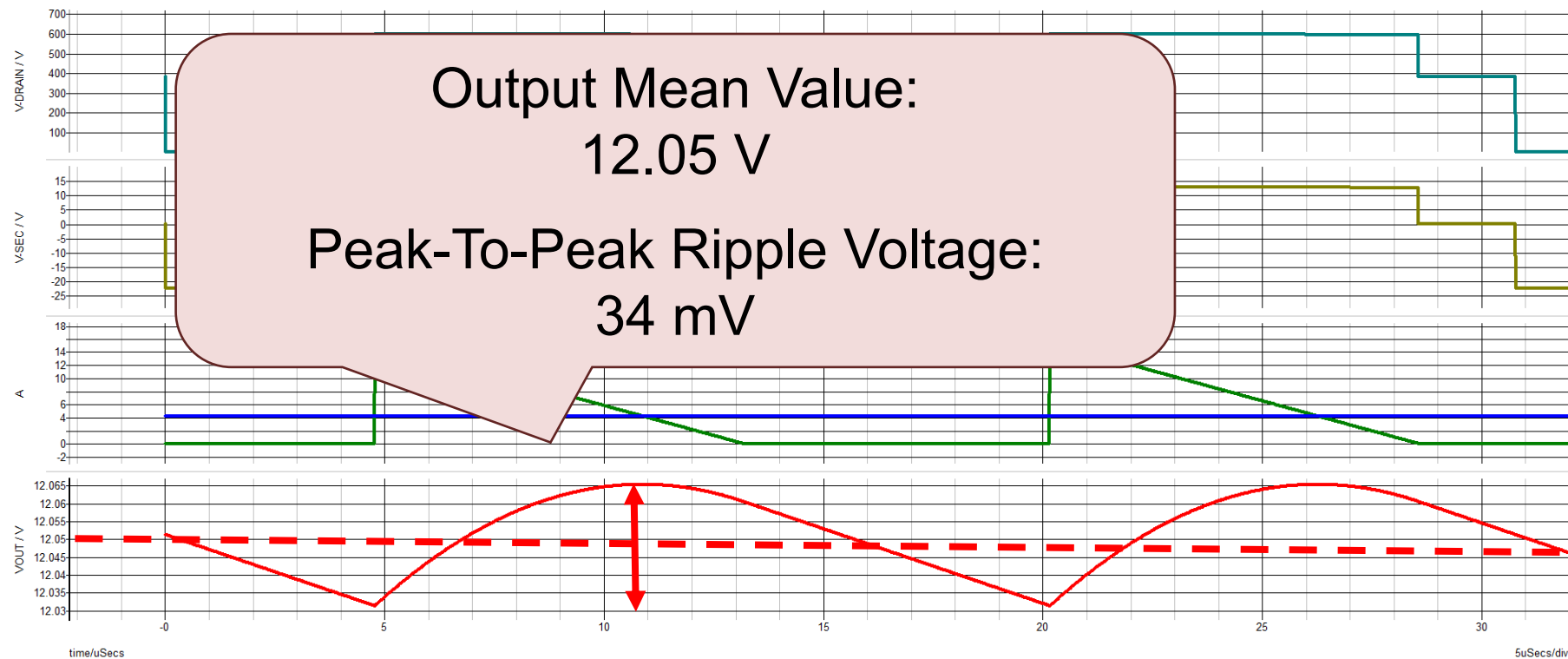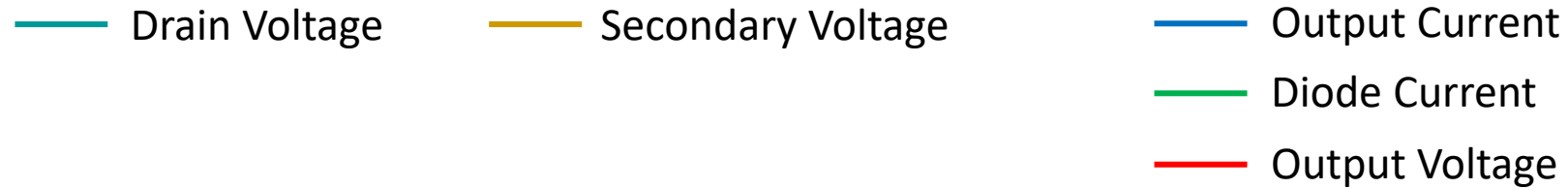
Discontinuous Conduction Mode Ideal Flyback Simulation



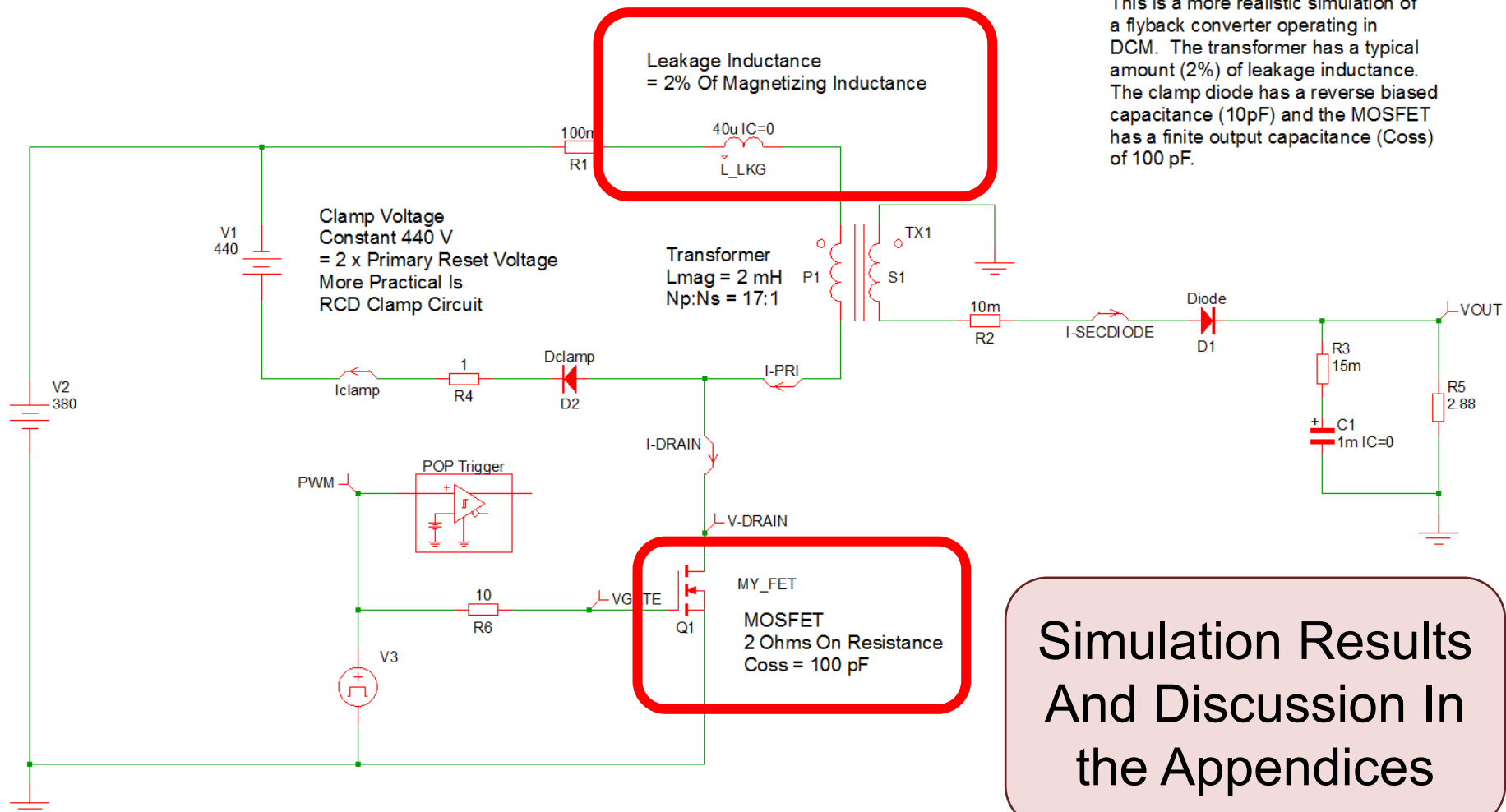Discontinuous Conduction Mode More Realistic Flyback Simulation



Multiple Output Flyback

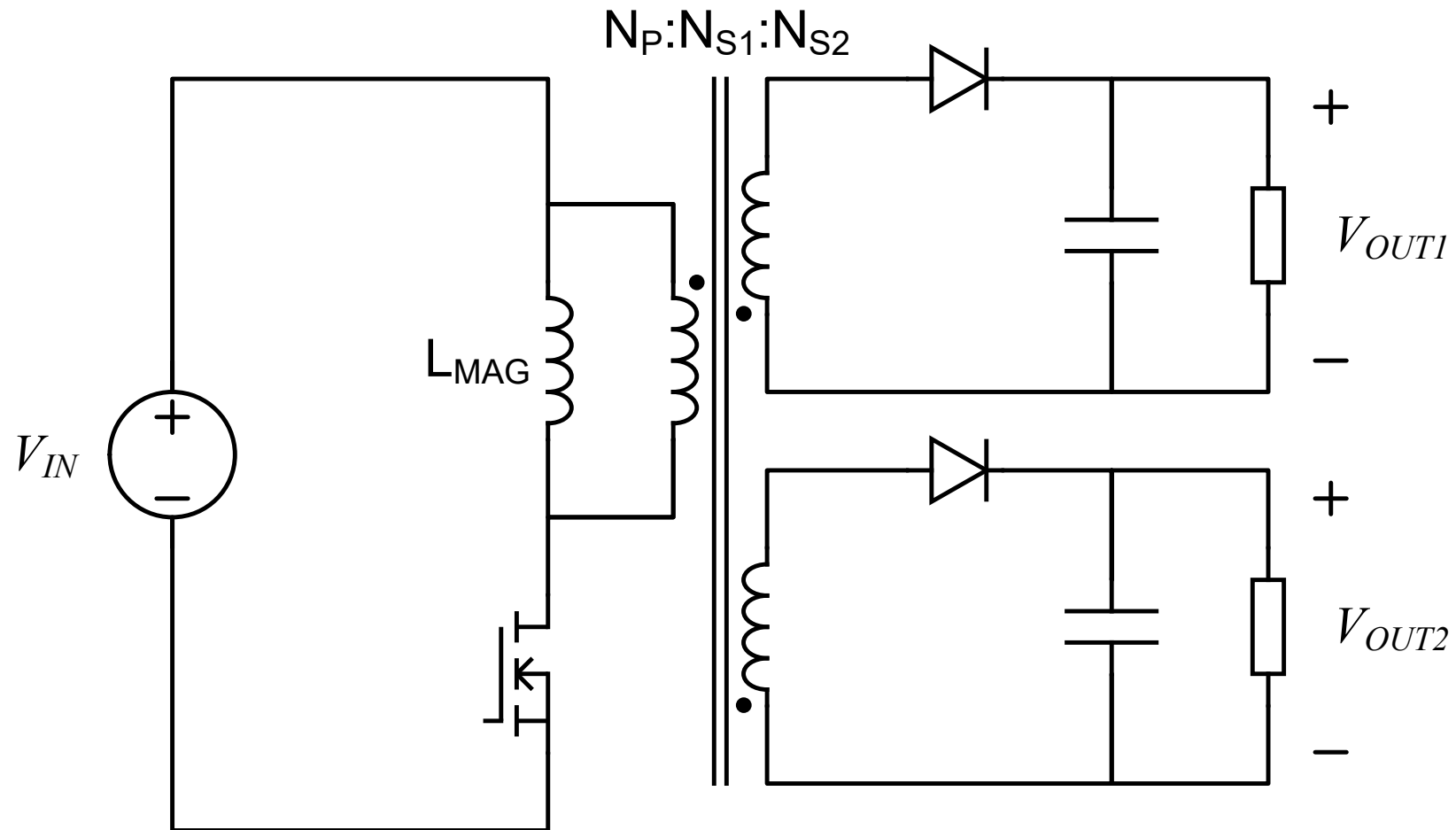

Flyback Converter

Advantages

- Isolated
- Good Up To 150 W
- Multiple Isolated Outputs Possible
- Easy To Control (Discontinuous Mode)


Disadvantages

- Transformer Needed
- Single Transistor: High Voltage Stress On Transistor And Diode
- Large Output Capacitor

SEPIC Topology


SEPIC

Single-Ended, Primary Inductor Converter

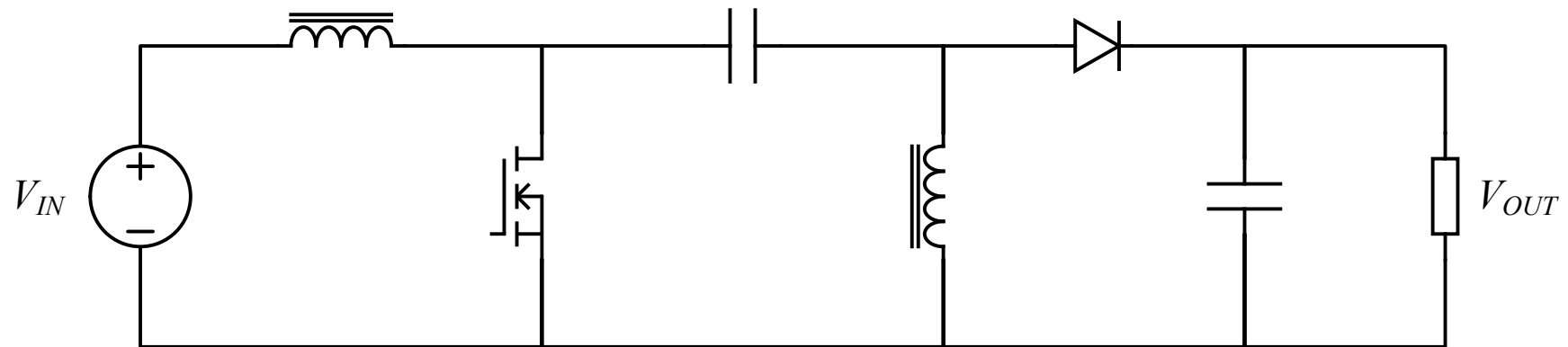

SEPIC


Single-Ended, Primary Inductor Converter

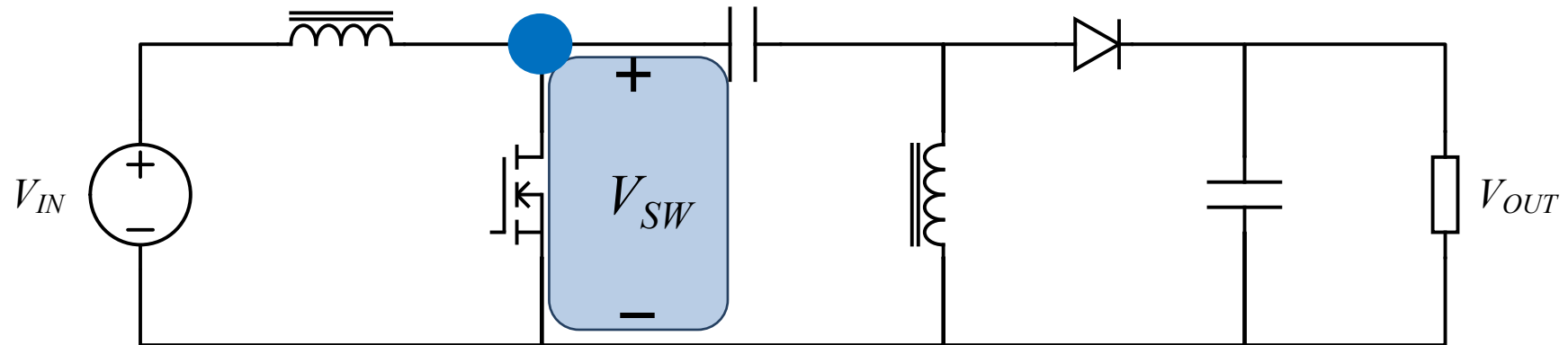

“Switch Node”

SEPIC On Time

Single-Ended, Primary Inductor Converter

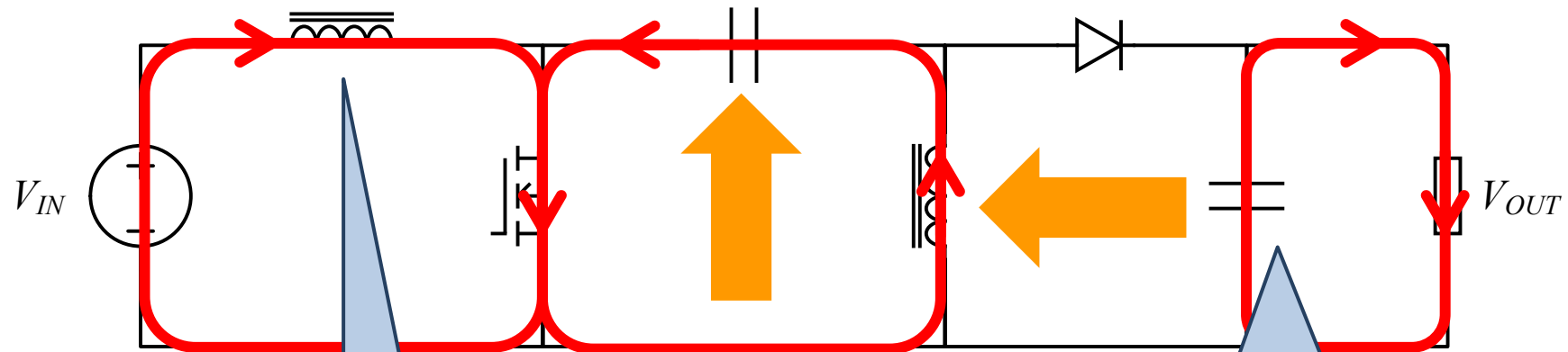


Input Inductor Stores Energy

Output Capacitor Delivers Energy To The Output

SEPIC Off Time

Single-Ended, Primary Inductor Converter

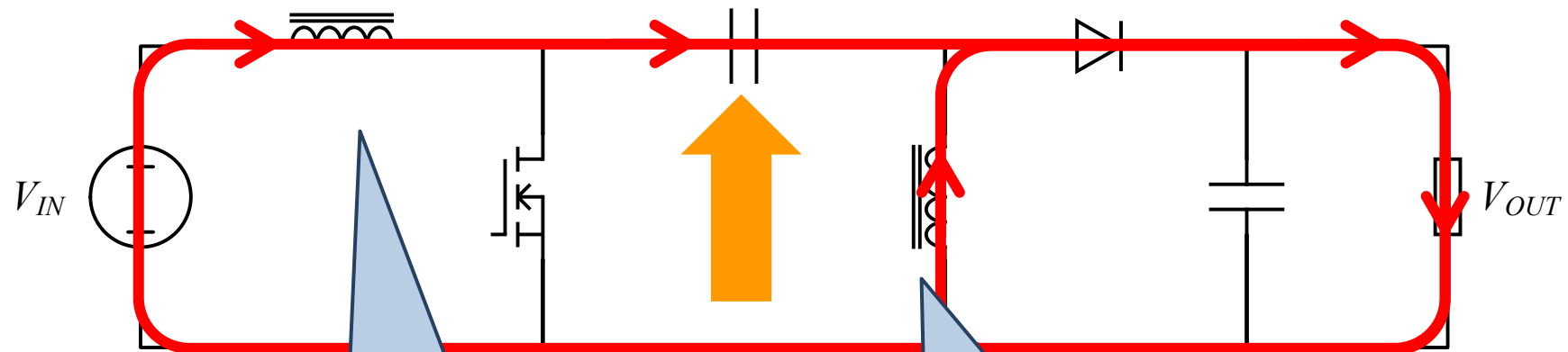


Input Inductor
Deliver Energy
To The Output



Second Inductor
Also Delivers Energy To The
Output

SEPIC Conversion Ratio
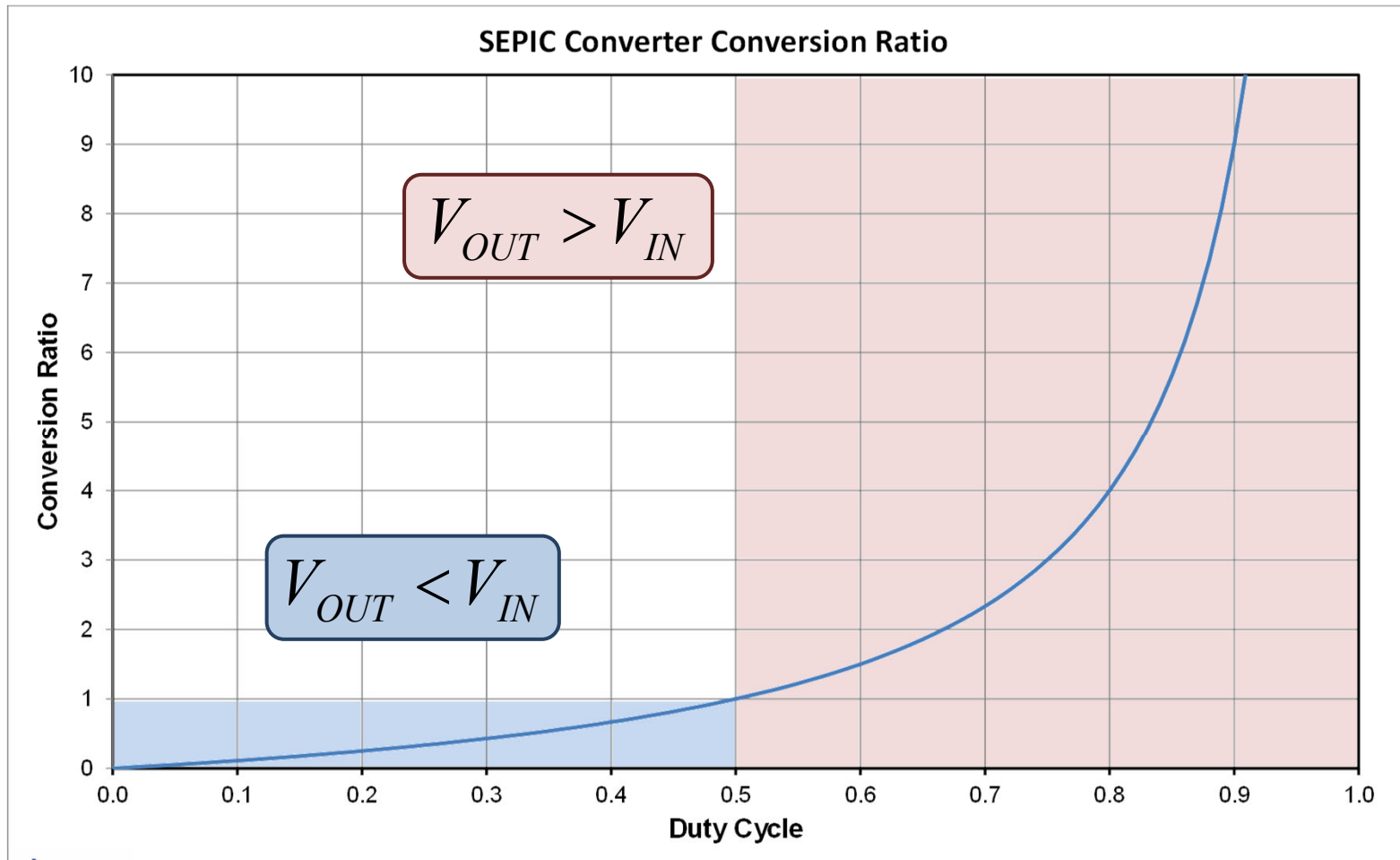
$$V_{OUT} = \frac{D}{1-D} \cdot V_{IN} = \frac{D}{D'} \cdot V_{IN}$$




SEPIC With Coupled Inductor

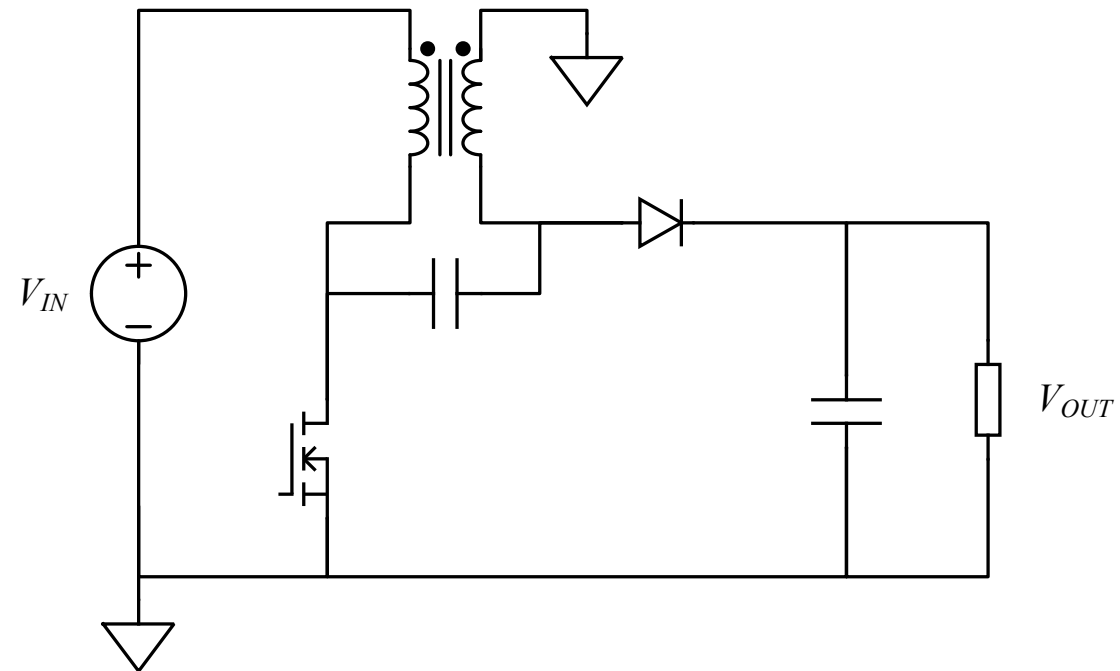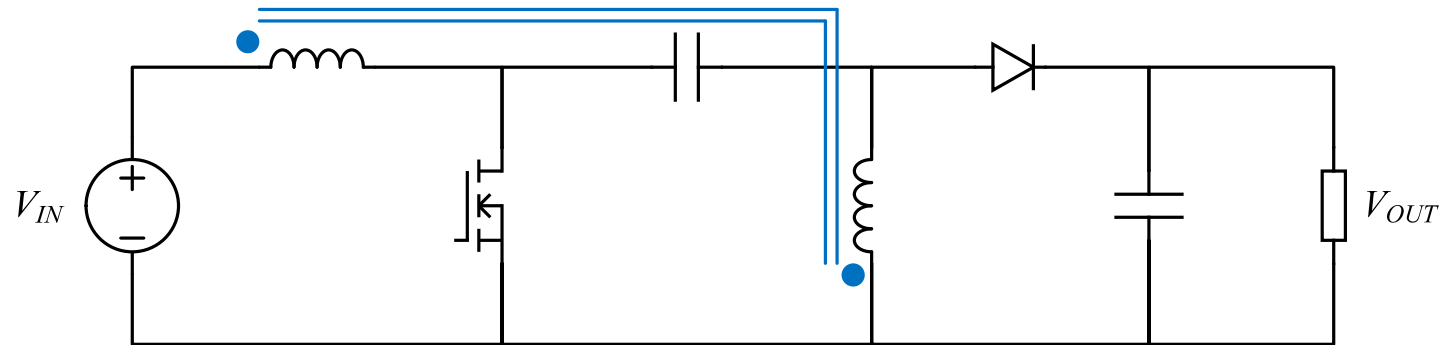

SEPIC

Single-Ended, Primary Inductor Converter

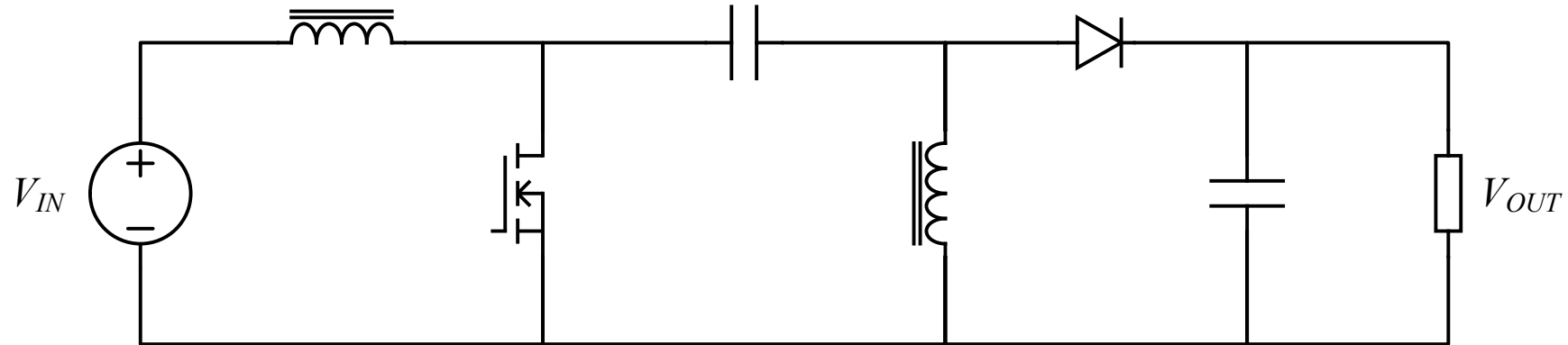

Advantages

- Output Voltage Higher Or Lower Than Input Voltage
- Single Grounded Switch
- Capacitor Blocks Output Short From Input Source

Disadvantages

- All Power Passes Through The “Flying” Capacitor
- Very Difficult Controller Design

Resonant Converters

- More Complex, Typically Specialized Application
 - Very Common: CFL Ballast
- LLC Resonant Converter Is An Important Topology Today
 - Complex Operation
 - Complex To Design
 - Offers High Efficiency

Summary


In Part 1 We Covered

- Switch Mode Conversion Principle
 - Lossless Switches Plus Energy Storage
- Inductors And Capacitors As Energy Storage Devices
- Common Switching Converter Topologies
 - Buck Converter
 - Boost Converter
 - Buck-Boost Converter
 - Flyback Converter
 - SEPIC Converter

Questions?


Fundamentals of Switch-Mode Power Conversion Part 2: Control

Switch Mode Converter

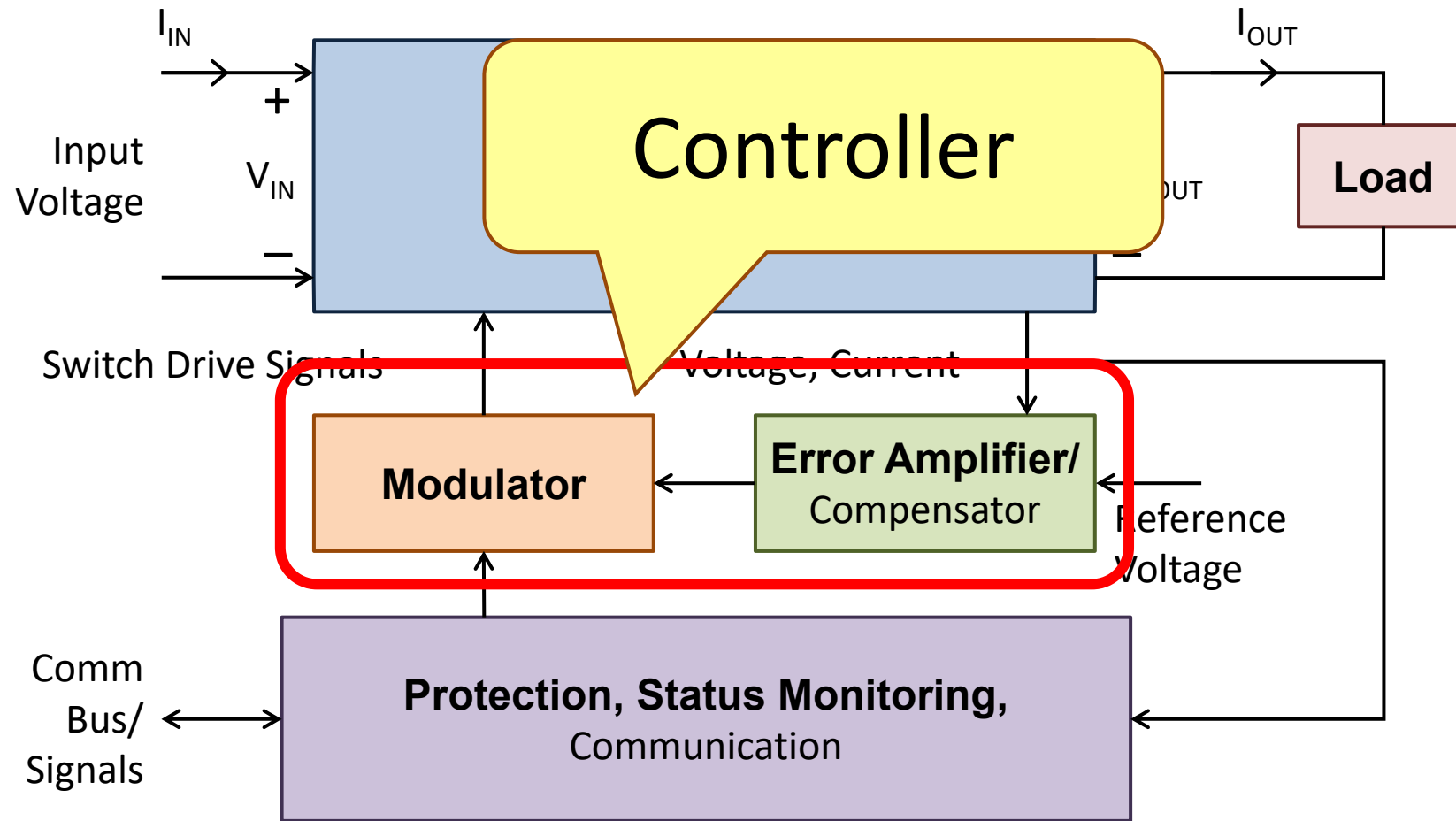


Switch Mode Converter

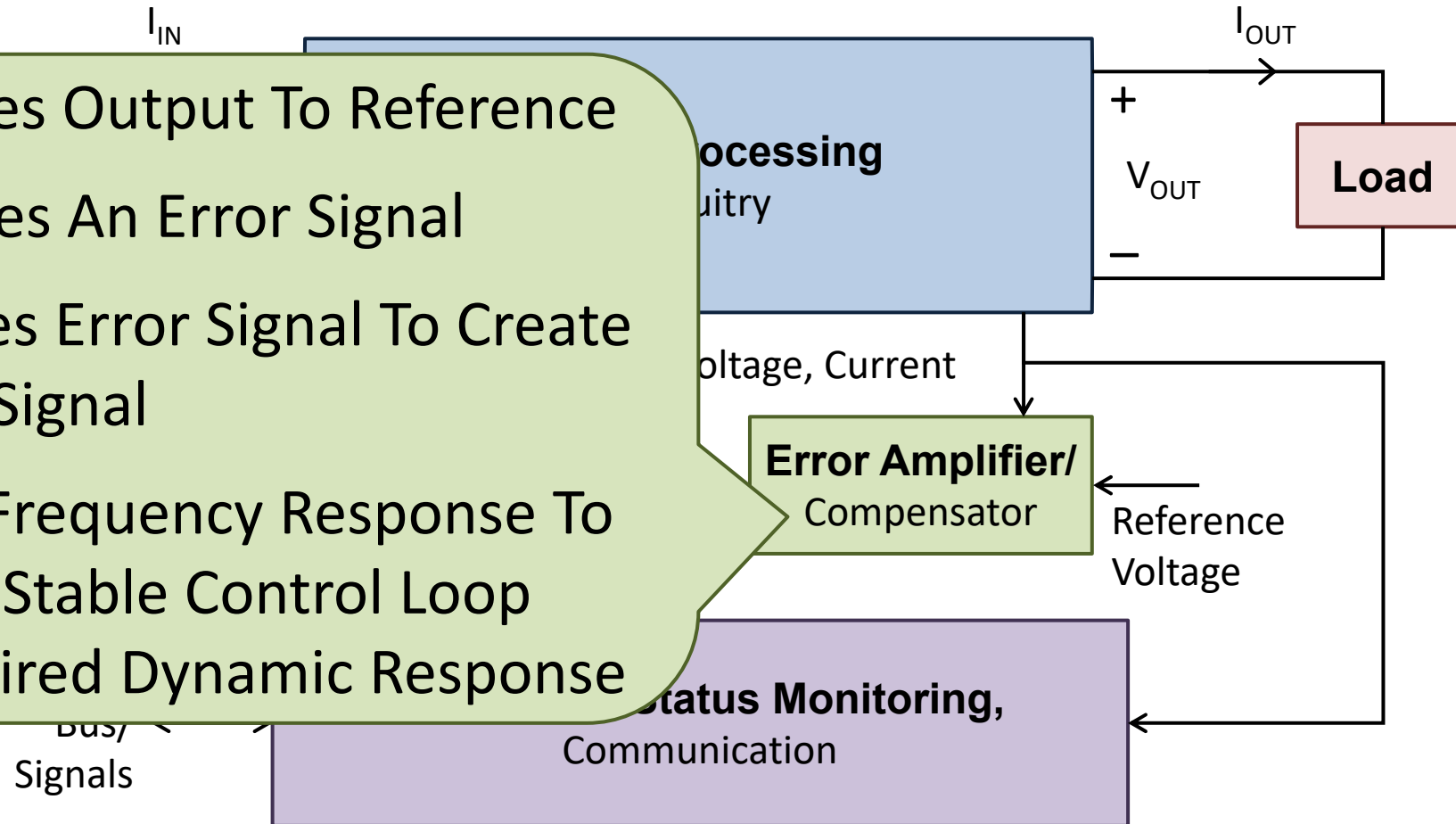
- Compares Output To Reference
- Generates An Error Signal
- Processes Error Signal To Create Control Signal
- Shapes Frequency Response To Achieve Stable Control Loop And Desired Dynamic Response



Switch Mode Converter

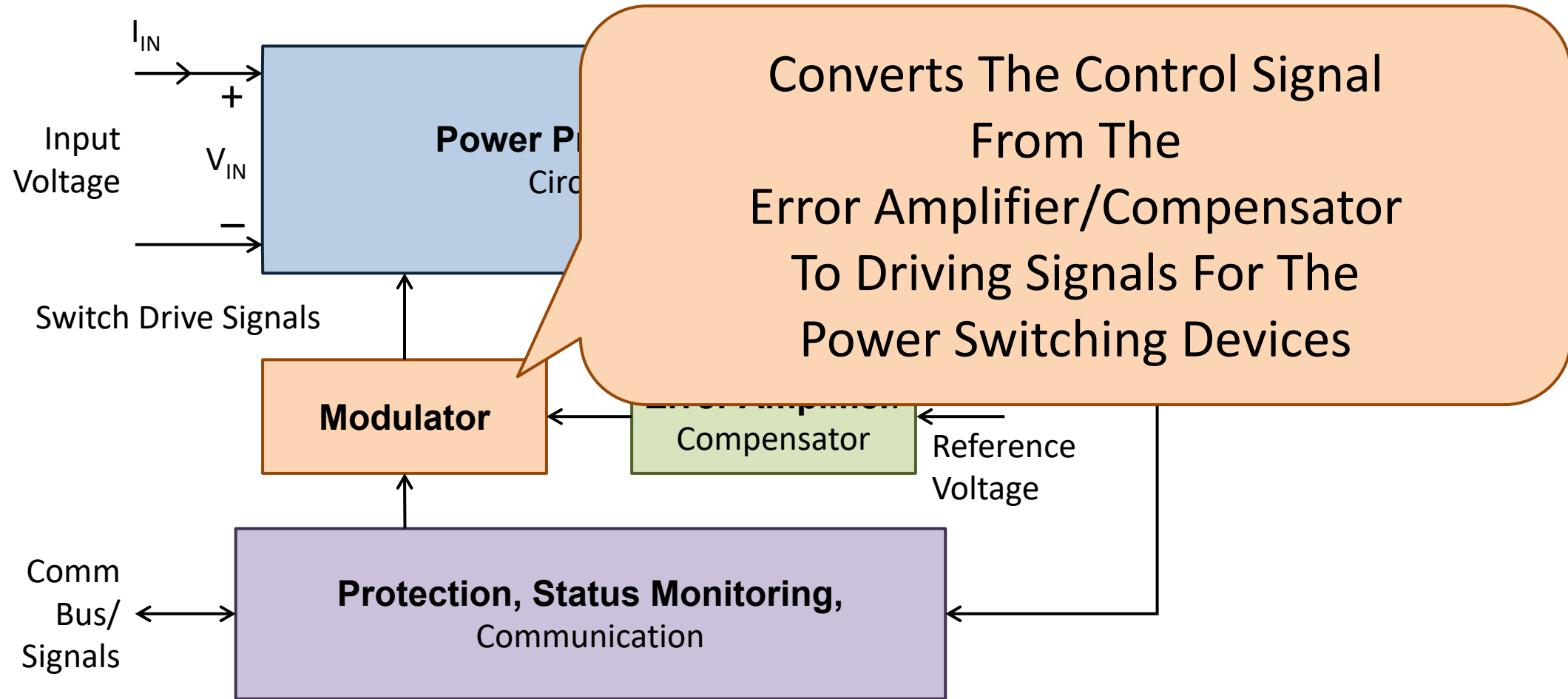


Control Loop

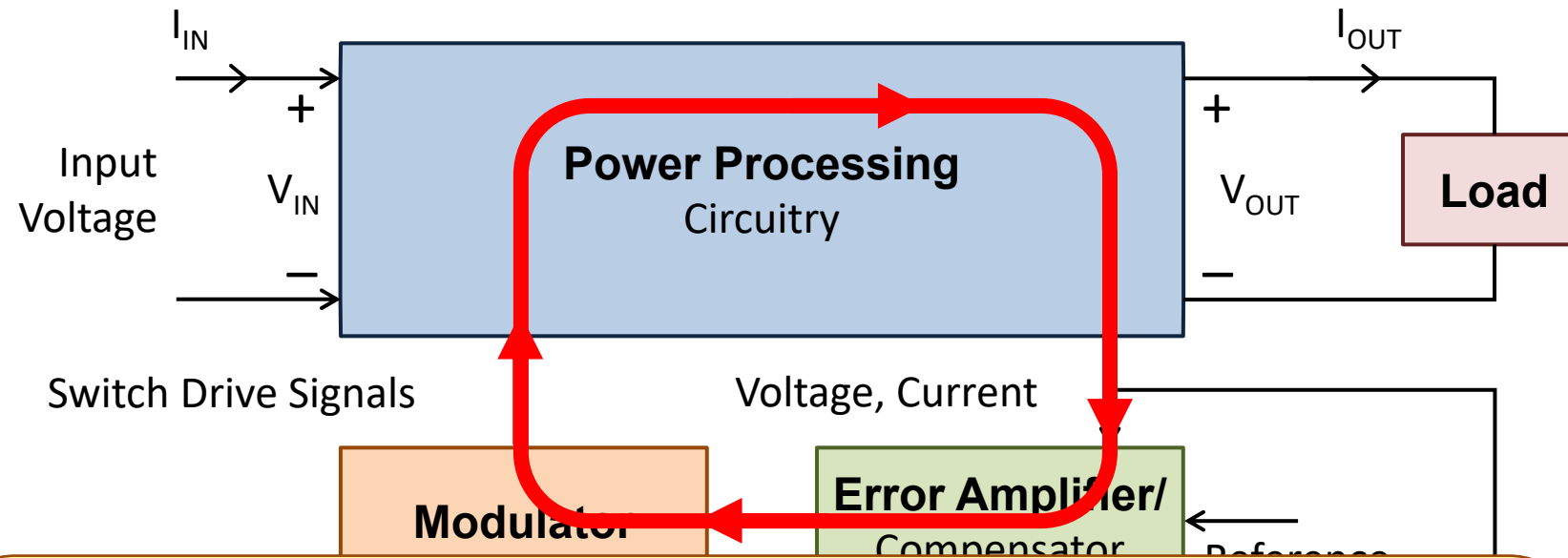

Important:
We Will Be VERY Concerned
With The Frequency Response
Of Signals Flowing Through This Loop

Transfer Functions And Bode Plots


Transfer Function

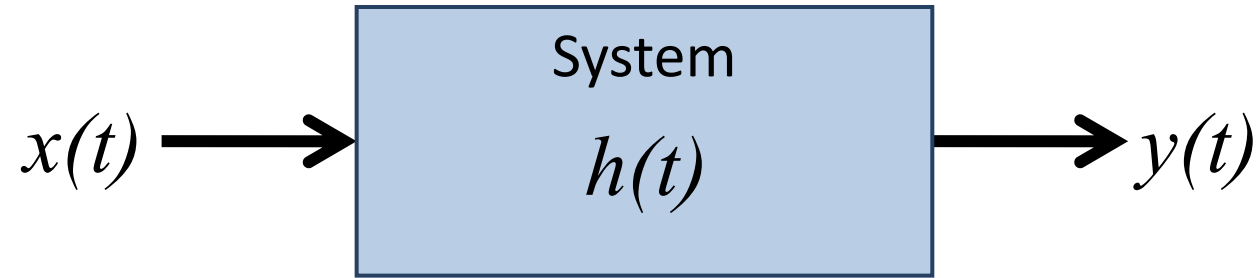

Find output $y(t)$ by convolution

$$y(t) = h(t) * x(t) = \int_{-\infty}^{\infty} h(\tau) \cdot x(t - \tau) d\tau$$

Transfer Function

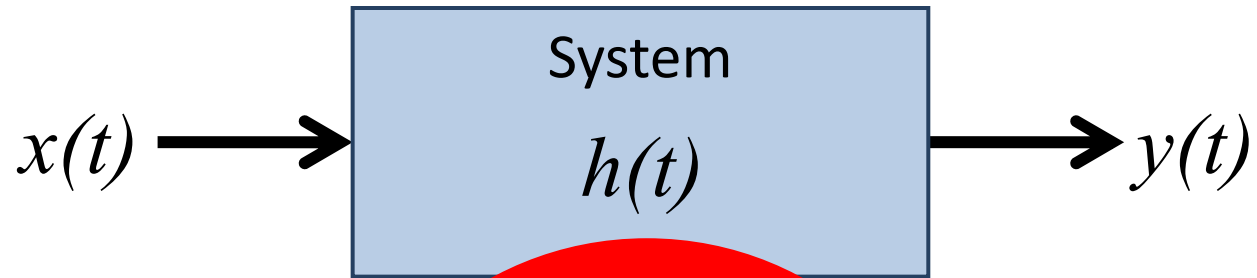


Find out how to convert

$$y(t) = h(t) * x(t) = \int_{-\infty}^{\infty} x(\tau) h(t - \tau) d\tau$$

Transfer Function

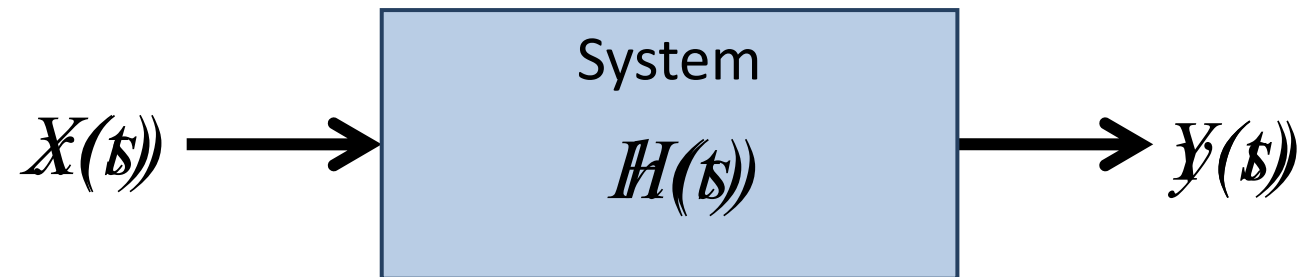Use LaPlace transform to convert to frequency domain




$$Y(s) = H(s) \cdot X(s)$$

$H(s)$
Is The
"Transfer
Function"

$$H(s) = \frac{Y(s)}{X(s)}$$


Describes The
Frequency Response
Of The System:
Gain
Phase

Transfer Function

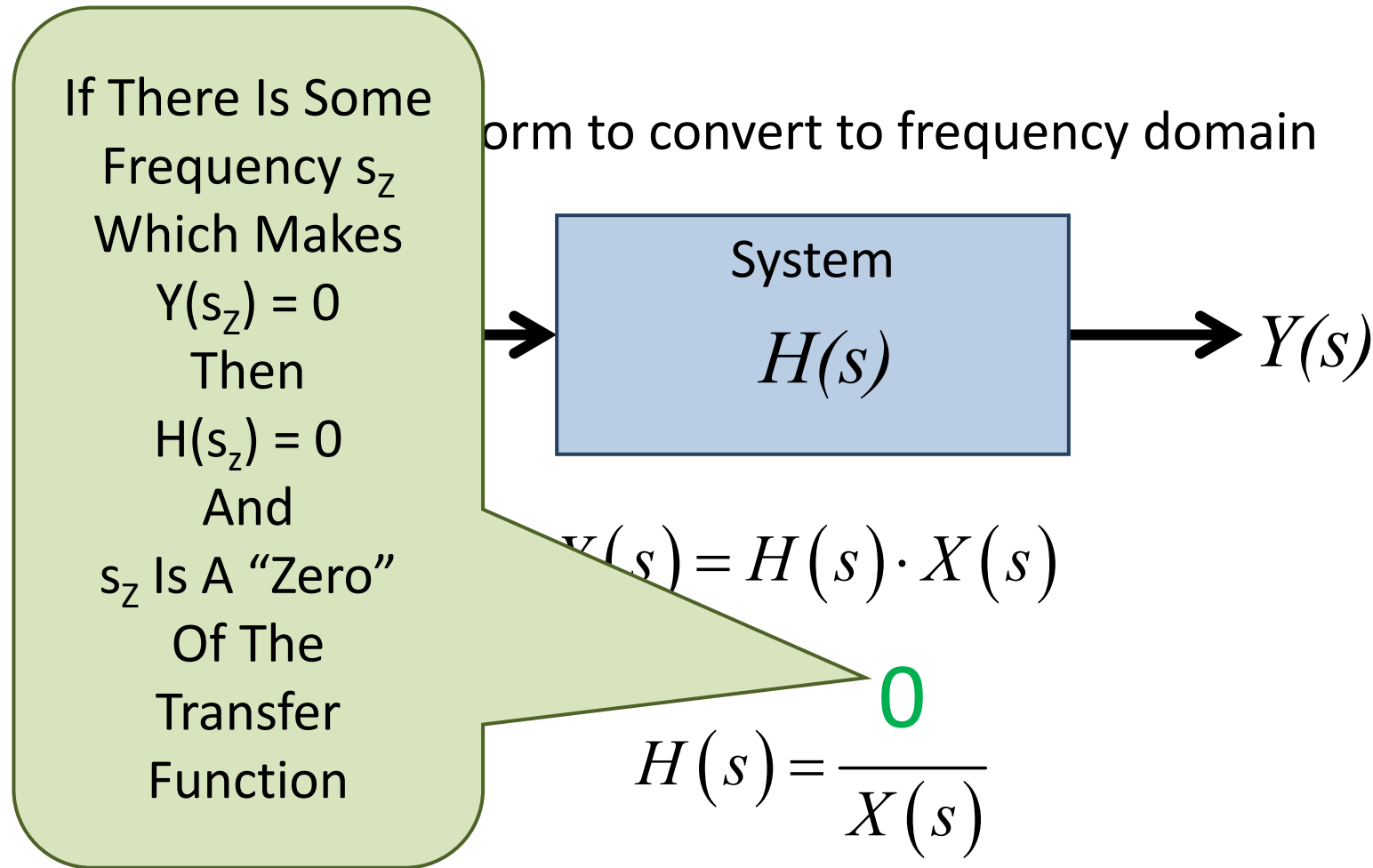

Transfer Function

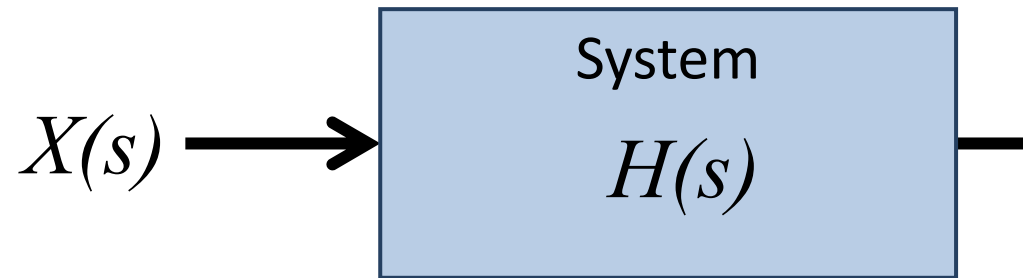Use LaPlace transform to convert to frequency




$$Y(s) = H(s) \cdot X(s)$$

$$H(s) = \frac{Y(s)}{0}$$

If There Is Some Frequency s_p Which Makes $X(s_p) = 0$ Then $H(s_p) \rightarrow \infty$ And s_p Is A "Pole" Of The Transfer Function


Simple Op-Amp Pole

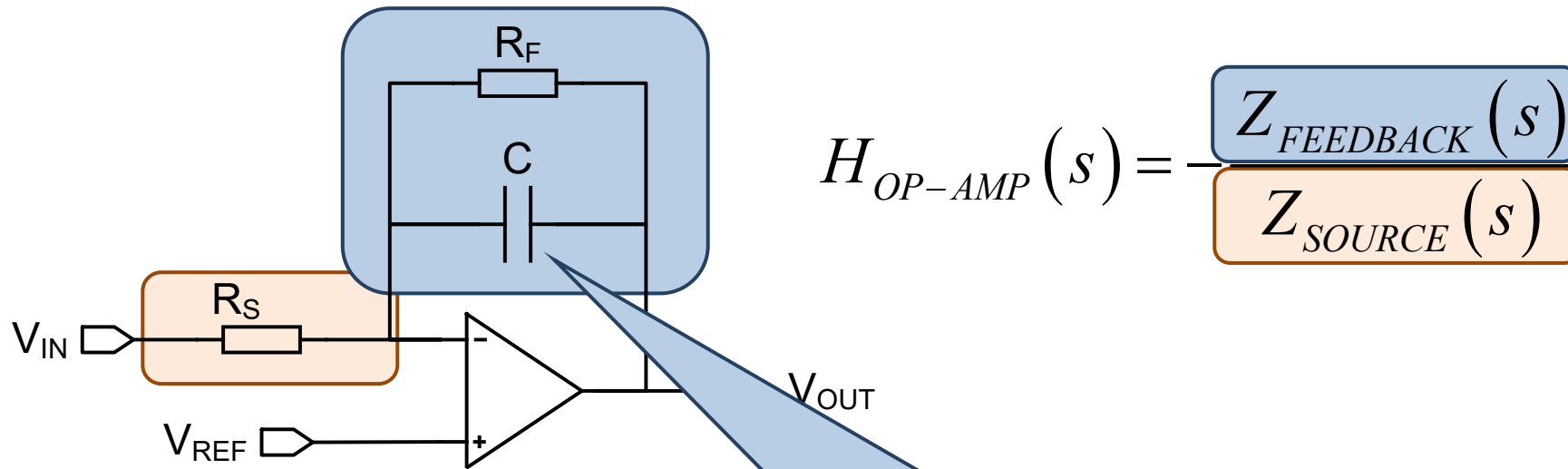

$$H_{OP-AMP}(s) = -\frac{Z_{FEEDBACK}(s)}{Z_{SOURCE}(s)}$$

As Frequency \uparrow
Capacitor Impedance \downarrow
 $Z_{FEEDBACK} \downarrow \Rightarrow$ Gain \downarrow

Simple Op-Amp Pole

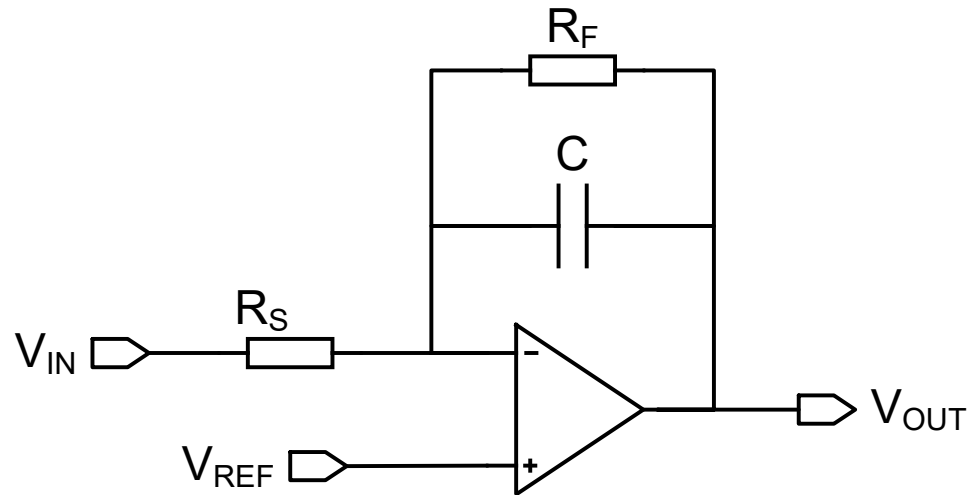

$$H_P(s) = \frac{R_F}{R_S} \cdot \frac{1}{1 + s \cdot R_F \cdot C}$$

$$H_P(s) = G_0 \cdot \frac{1}{1 + \frac{s}{\omega_P}}$$

A blue arrow points to the pole term $\frac{s}{\omega_P}$ in the denominator of the transfer function.


$$G_0 = -\frac{R_F}{R_S}$$

$$\omega_P = 2 \cdot \pi \cdot f_P = \frac{1}{R_F \cdot C}$$

$$f_P = \frac{1}{2 \cdot \pi \cdot R_F \cdot C}$$

Simple Op-Amp Pole

Negative Frequency
Valid In s-Domain

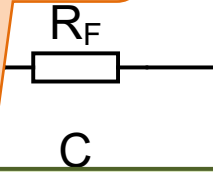

$$\begin{aligned} H_P\left(-\frac{1}{R_F \cdot C}\right) &= H_P(-\omega_P) \\ &= G_0 \cdot \frac{1}{1 + \frac{-\omega_P}{\omega_P}} = G_0 \cdot \frac{1}{1 + (-1)} \\ &= G_0 \cdot \left(\frac{1}{0}\right) \end{aligned}$$

$$H_P(s) = -\frac{R_F}{R_S} \cdot \frac{1}{1 + s \cdot R_F \cdot C}$$


$$H_P(s) = G_0 \cdot \frac{1}{1 + \frac{s}{\omega_P}}$$

$$G_0 = -\frac{R_F}{R_S}$$


Denominator Is Zero
So $-\omega_P$ Is A
Pole Of This
Transfer Function

$$\frac{1}{R_F \cdot C}$$

Simple Pole Bode Plot

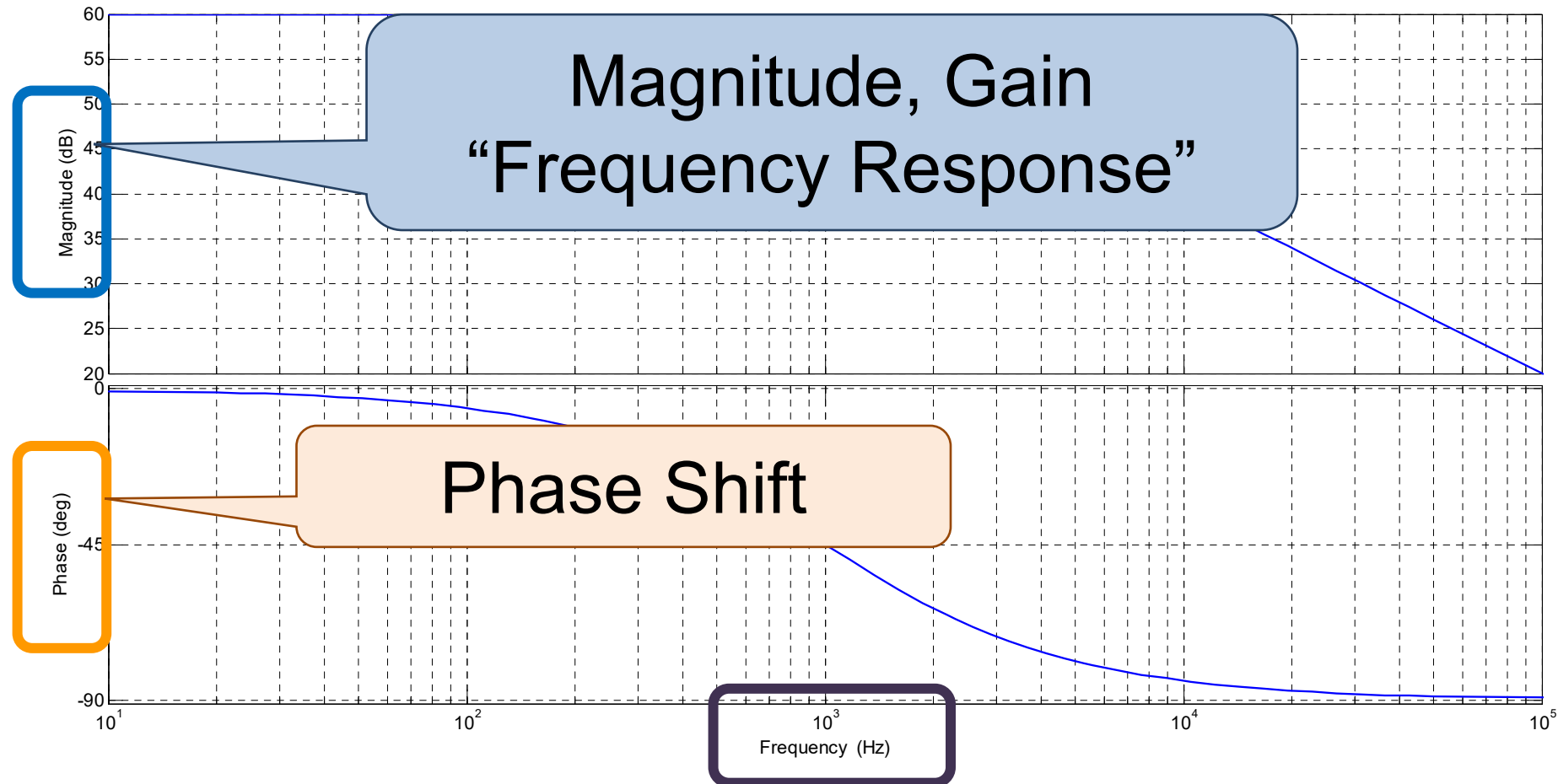


Simple Pole Bode Plot

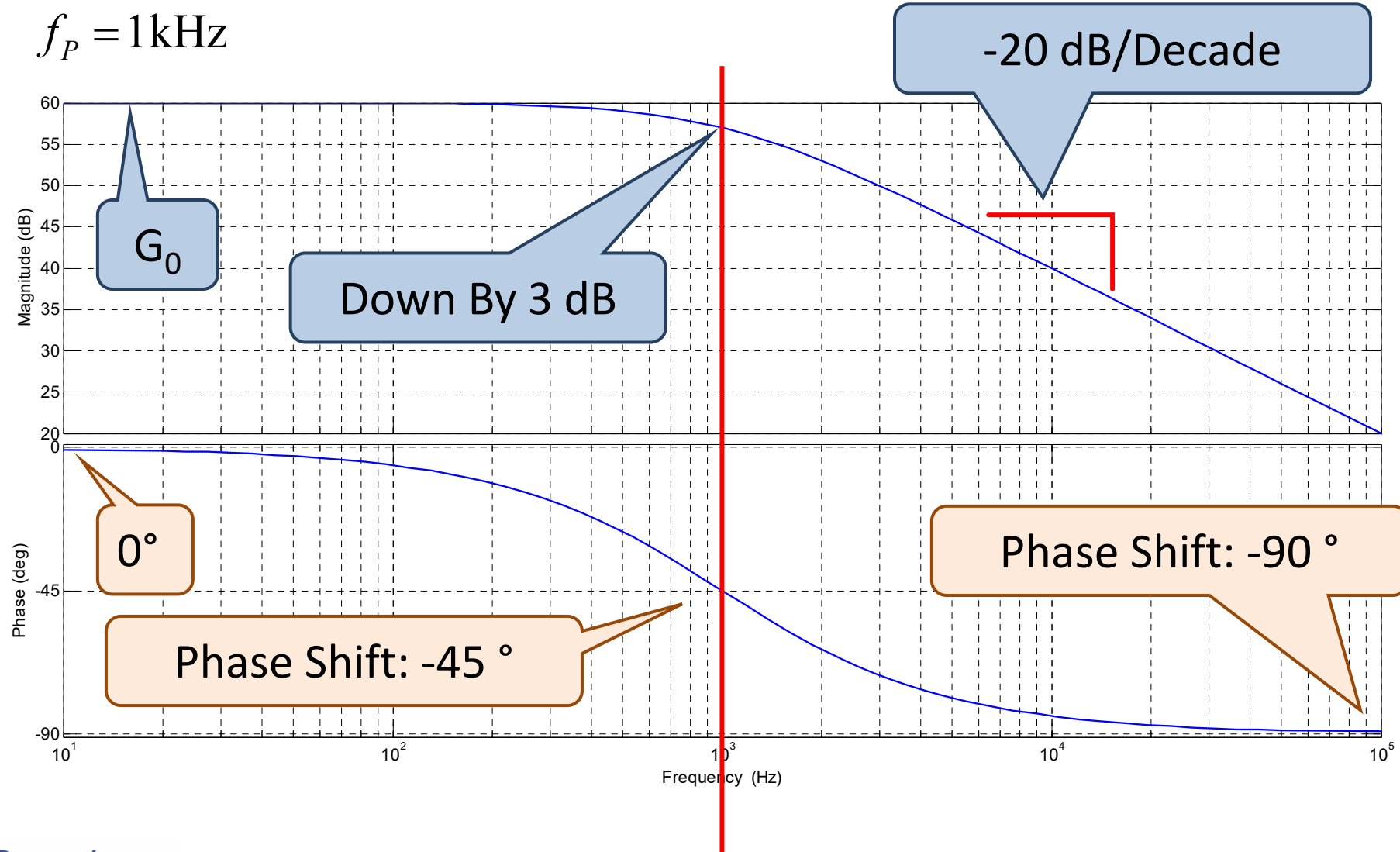


Simple Pole Bode Plot

$$f_P = 1\text{kHz}$$

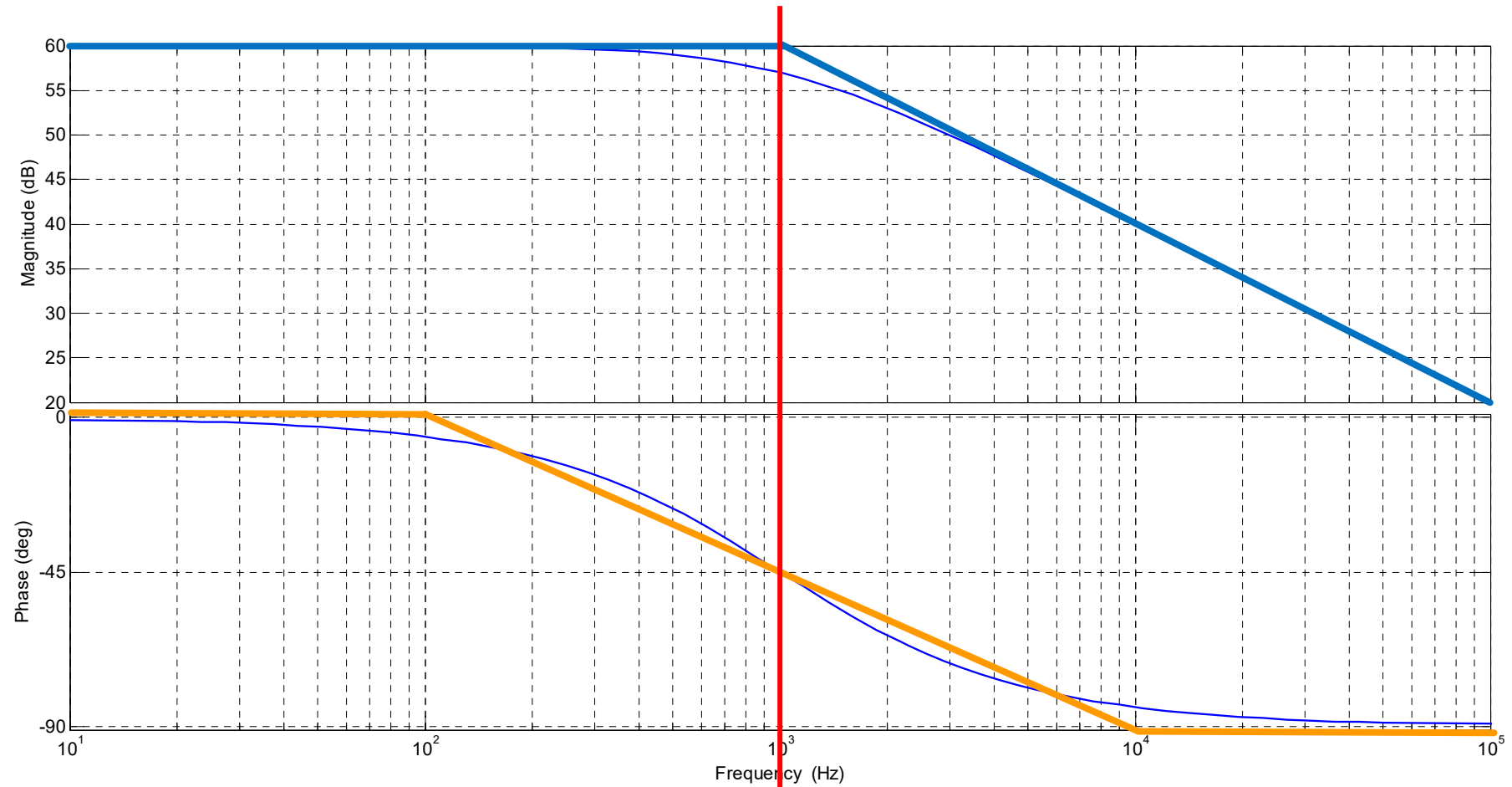


Simple Zero

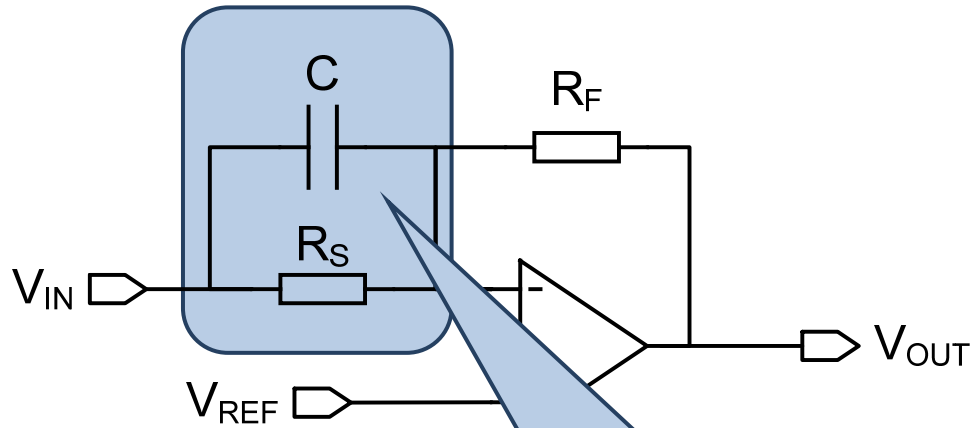

As Frequency \uparrow
Capacitor Impedance \downarrow
 $Z_{SOURCE} \downarrow \Rightarrow$ Gain \uparrow

Simple Zero

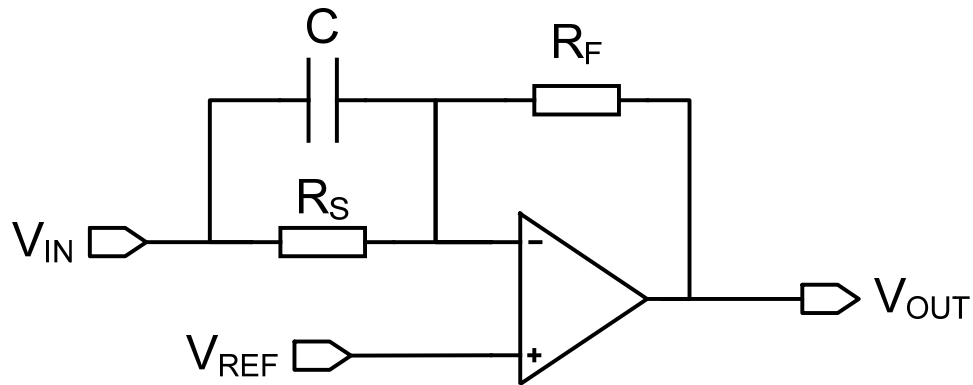

$$H_Z(s) = -\frac{R_F}{R_S} \cdot (1 + s \cdot R_S \cdot C)$$

$$H_Z(s) = G_0 \cdot \left(1 + \frac{s}{\omega_Z}\right)$$


$$G_0 = -\frac{R_F}{R_S}$$

$$\omega_Z = 2 \cdot \pi \cdot f_Z = \frac{1}{R_S \cdot C}$$


$$f_Z = \frac{1}{2 \cdot \pi \cdot R_S \cdot C}$$

Simple Zero Bode Plot

$$f_z = 1\text{kHz}$$

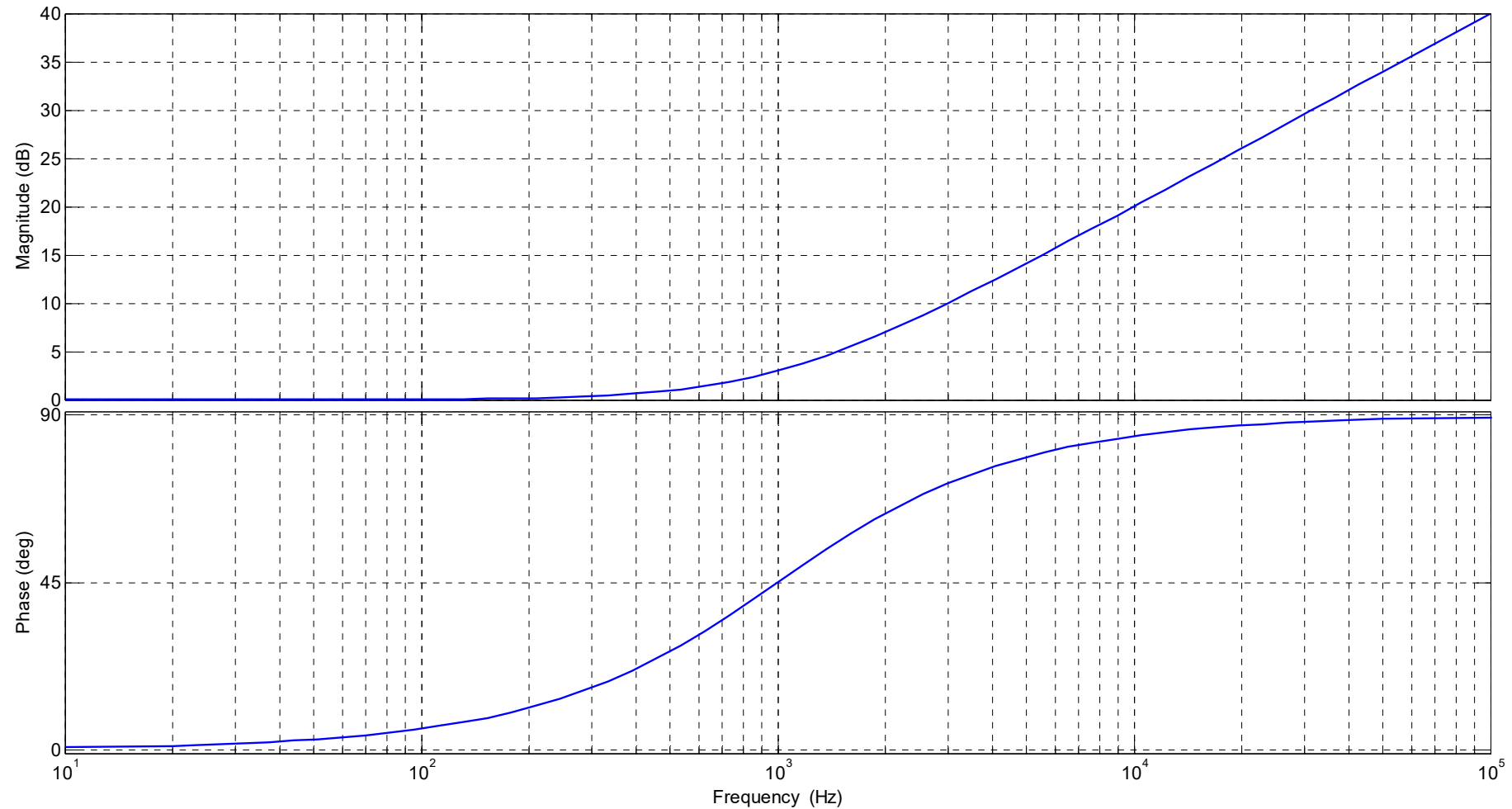

Simple Zero Bode Plot

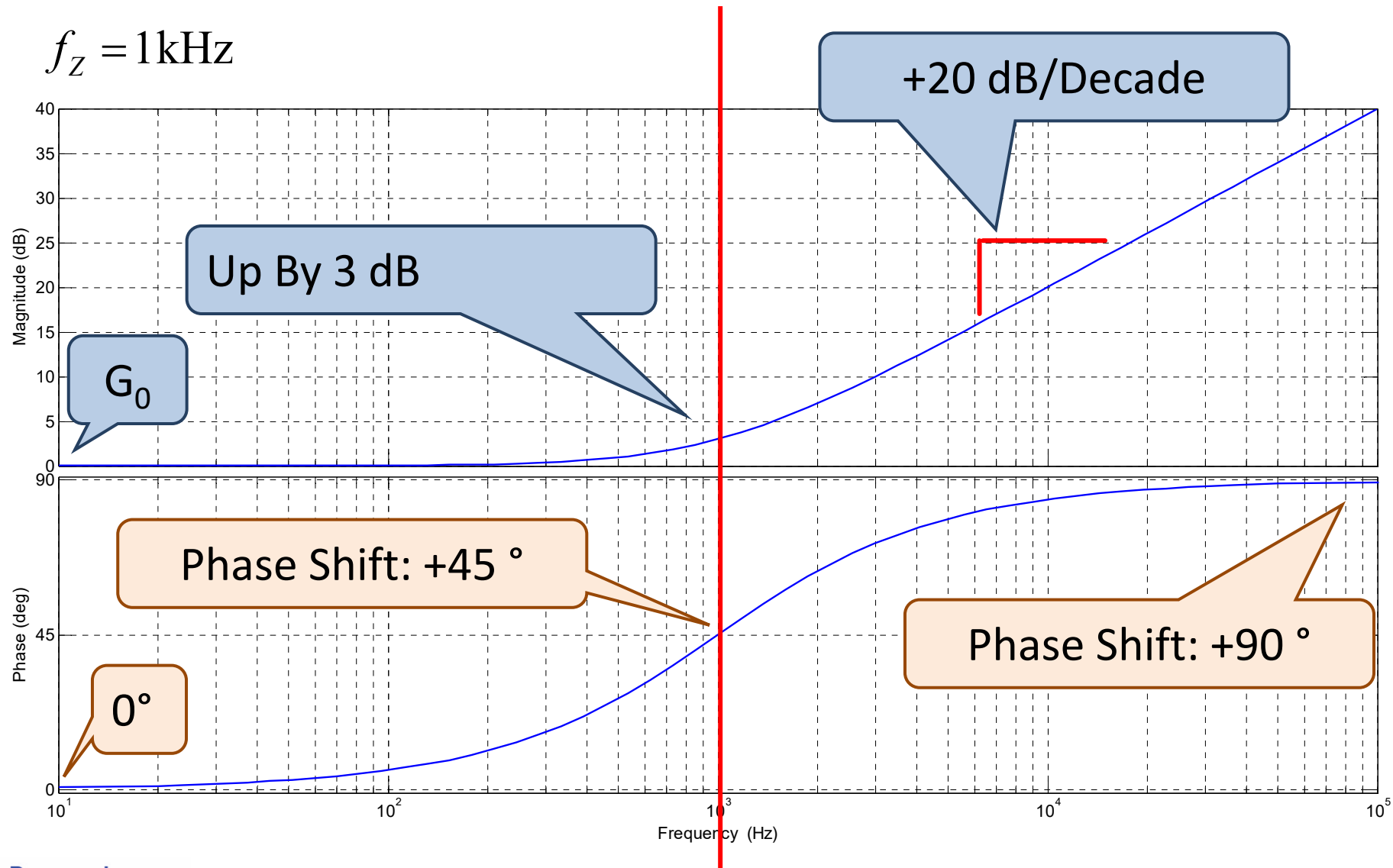


Example: Simple Transfer Function

$$H(s) = \frac{v_{out}(s)}{v_{in}(s)}$$

$$v_{OUT}(s) = \frac{\left(R2 + \frac{1}{s \cdot C}\right)}{R1 + \left(R2 + \frac{1}{s \cdot C}\right)} \cdot v_{IN}(s)$$
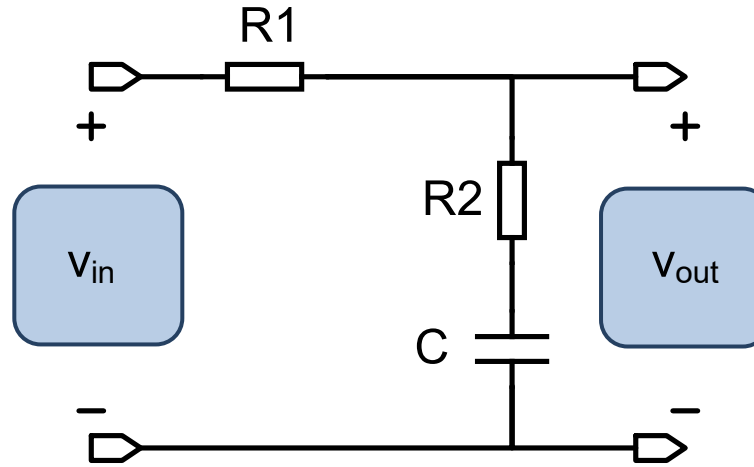
$$H(s) = \frac{v_{out}(s)}{v_{in}(s)} = \frac{1 + s \cdot R2 \cdot C}{1 + s \cdot (R1 + R2) \cdot C}$$




$$H(s) = \frac{1 + \frac{s}{\omega_Z}}{1 + \frac{s}{\omega_P}}$$


A blue arrow points from ω_Z in the numerator to $\omega_Z = \frac{1}{R2 \cdot C}$.

A yellow arrow points from ω_P in the denominator to $\omega_P = \frac{1}{(R1 + R2) \cdot C}$.

Simple Transfer Function Bode Plot

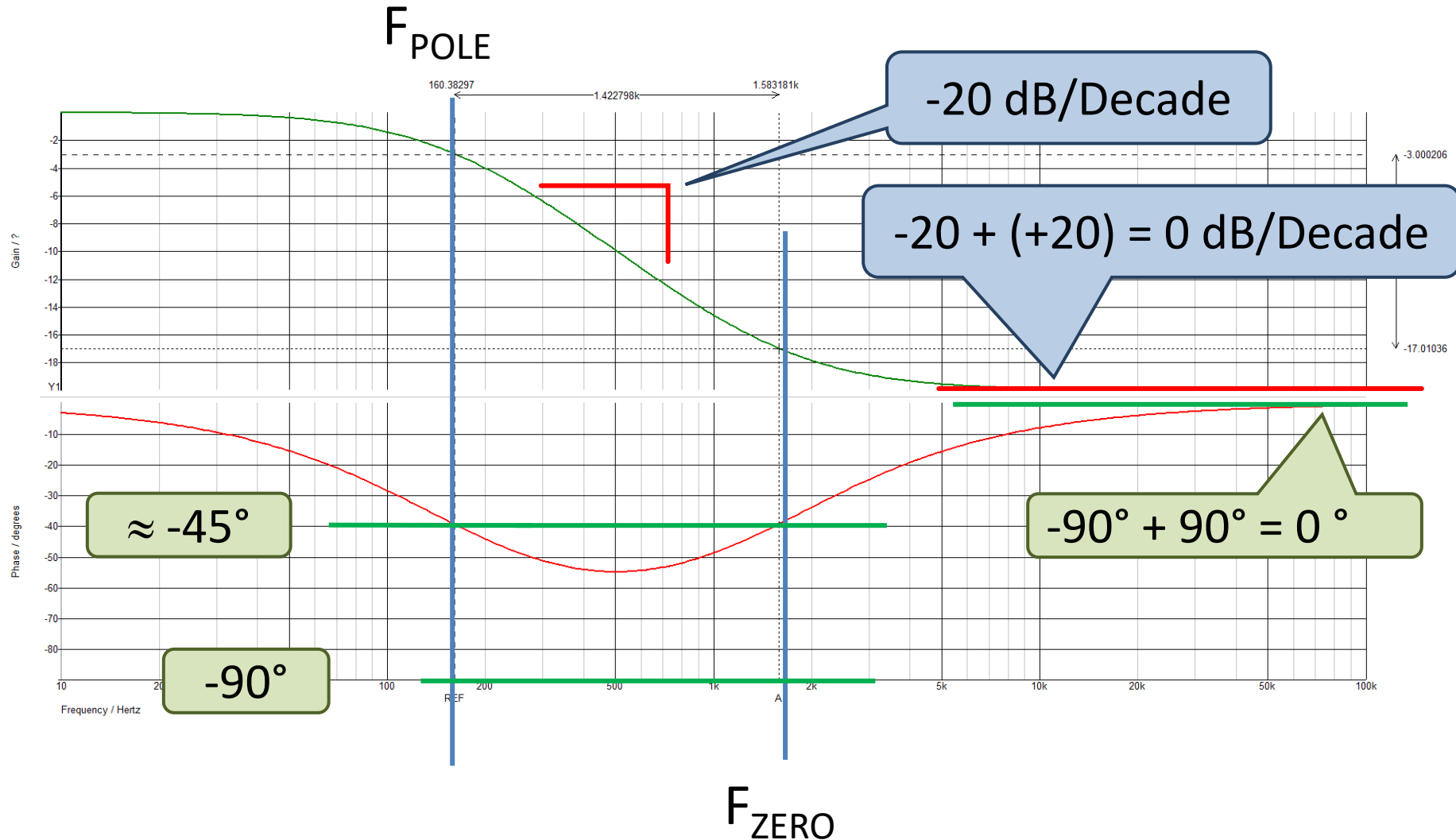

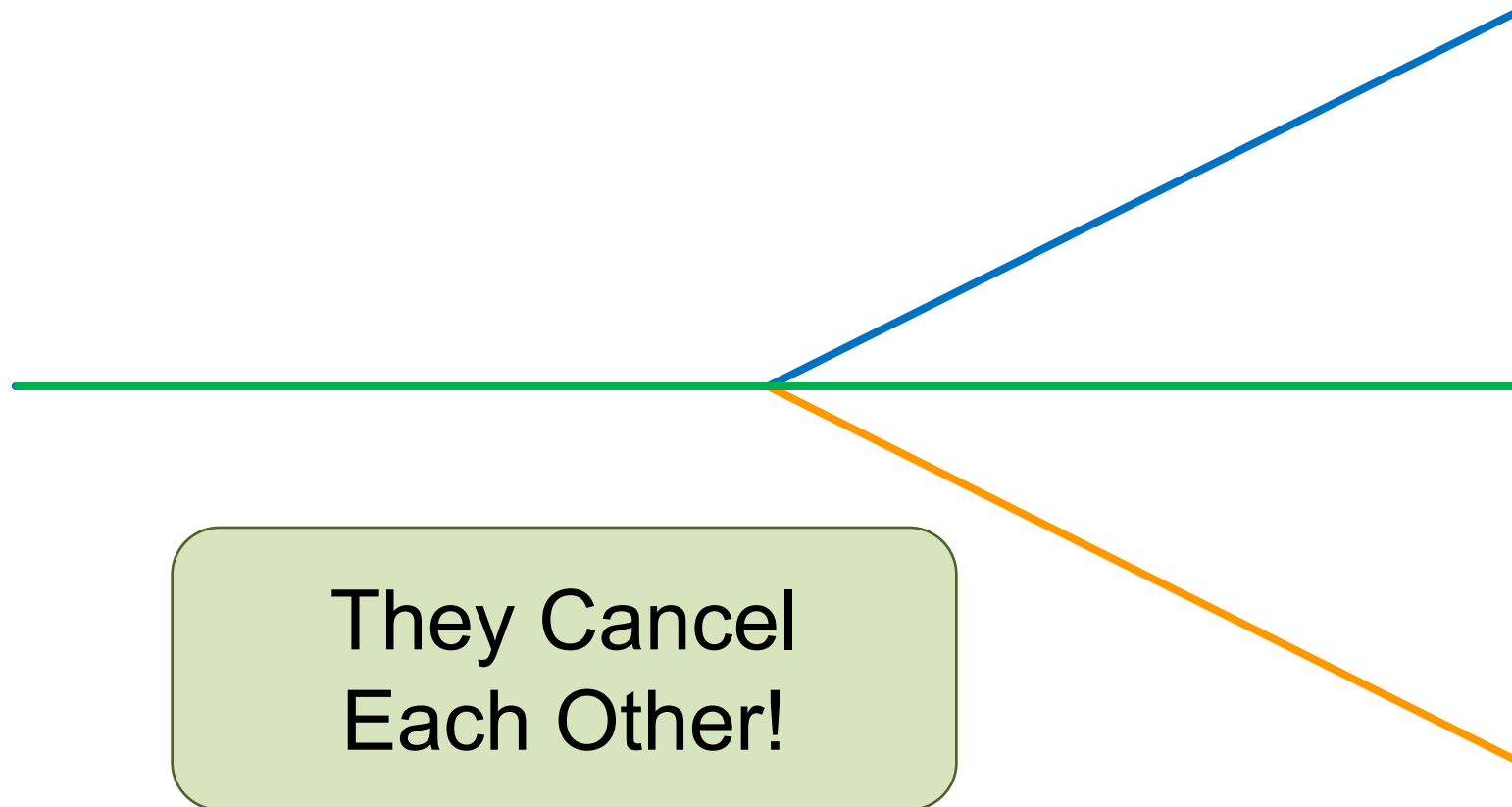What If System Has Pole And Zero At Same Frequency?




Basic Feedback Loop Review

Basic Feedback Review

Note


Next 16 Slides Not In Your USB PDF
Or Printed Workbook
They Are In The Version You Can
Download From
Embedded Power Labs Website

Basic Feedback Review

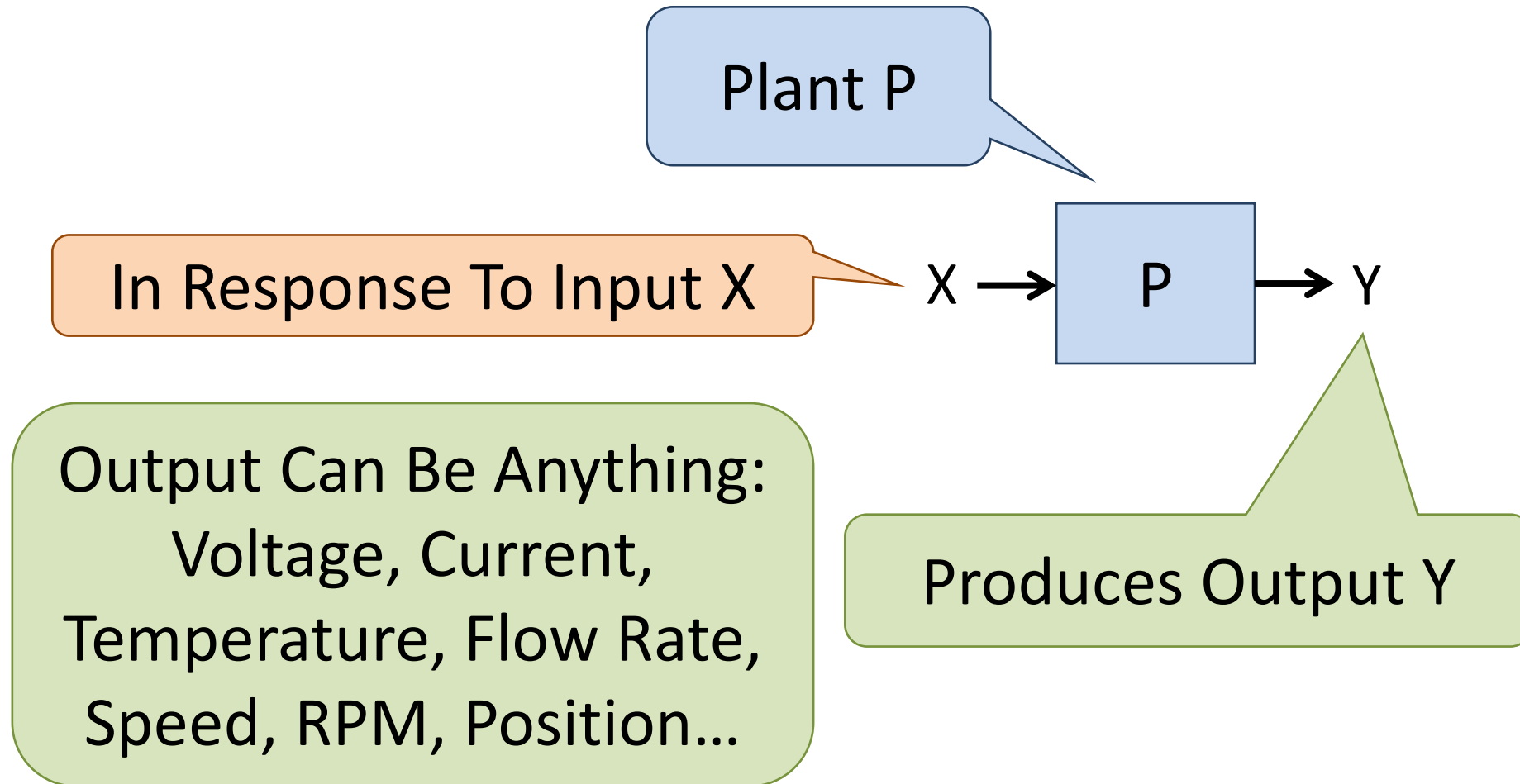

Basic Feedback Review

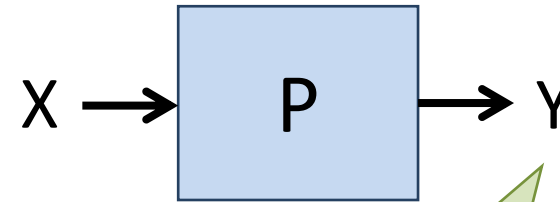
So How Do We Set
Input X To Get The
Desired Output Y?



What We Want Is To Have Y
Be Some Desired Value


Basic Feedback Review

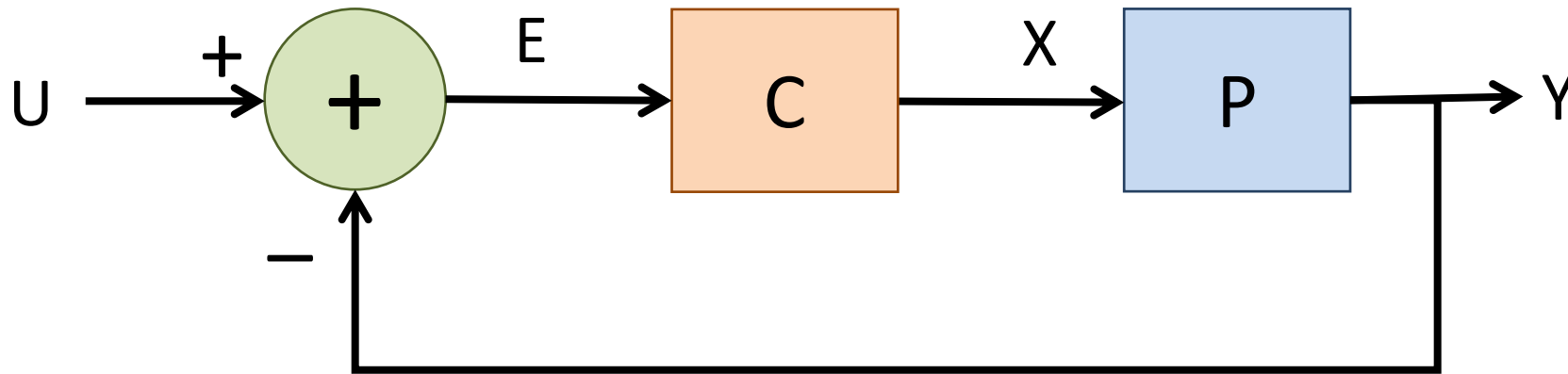Use Feedback To Get Desired Output Y
In Response To Command U




Basic Feedback Review

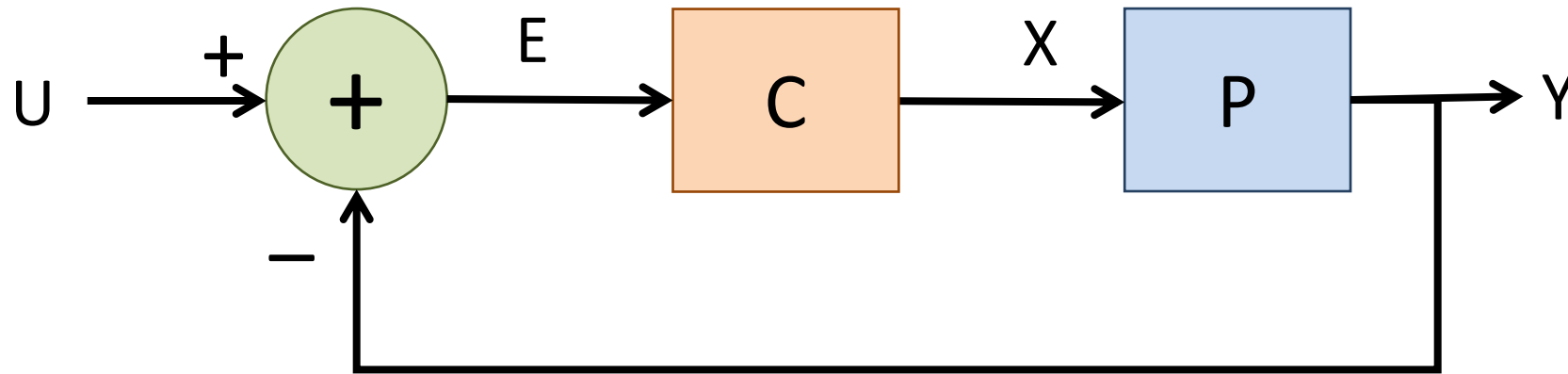Subtract Actual Output Y From Command U
To Generate Difference (Error) Signal E
 $E = U - Y$




Basic Feedback Review

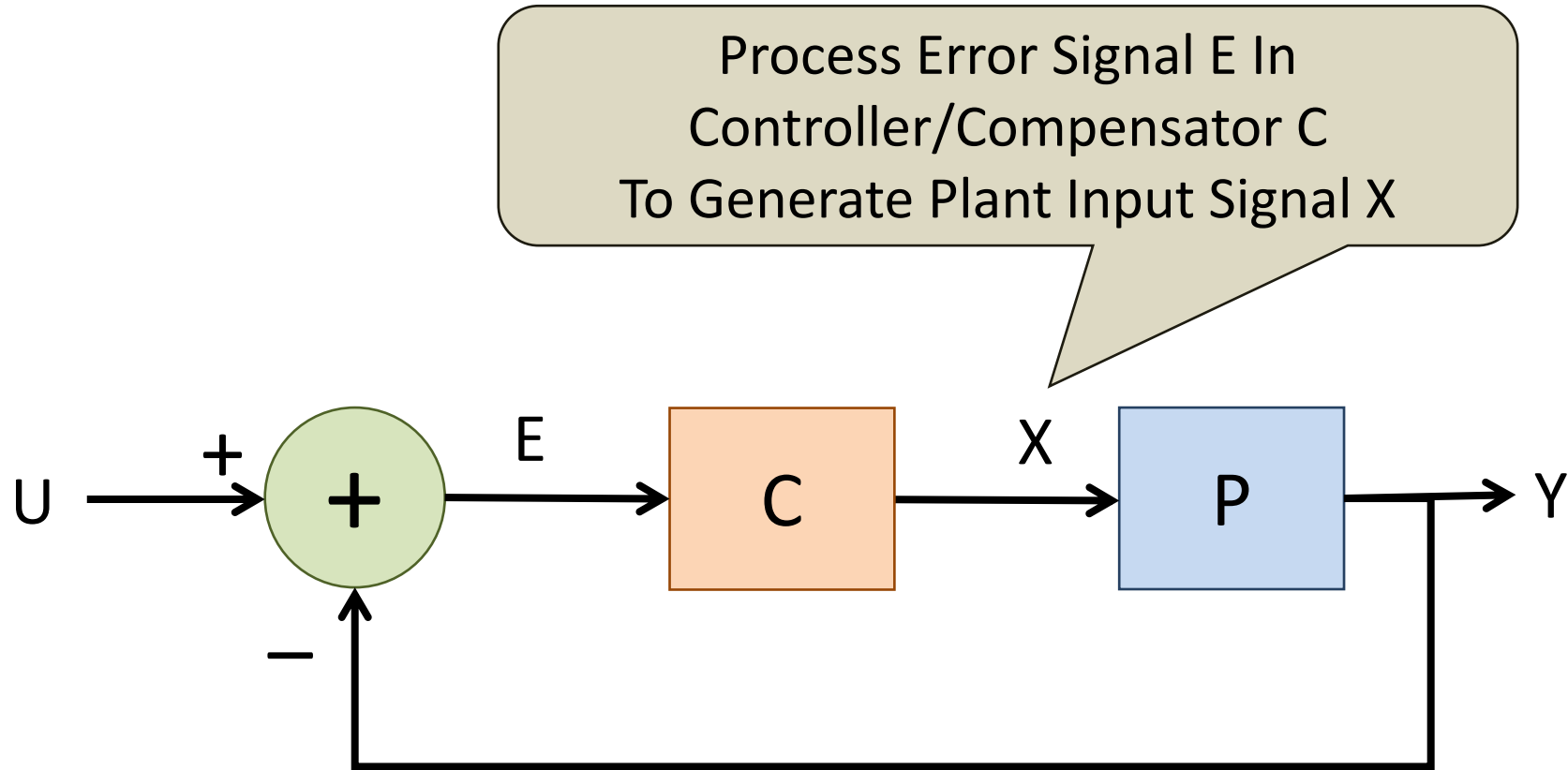


Basic Feedback Review

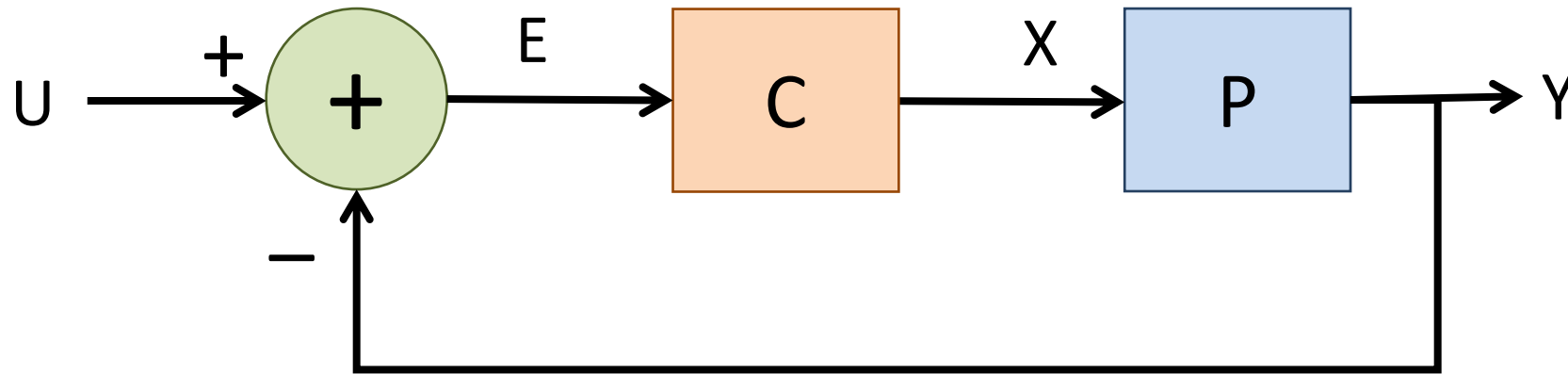For This Discussion Let An Increase In X Cause An Increase In Y (And Vice Versa)




Basic Feedback Review

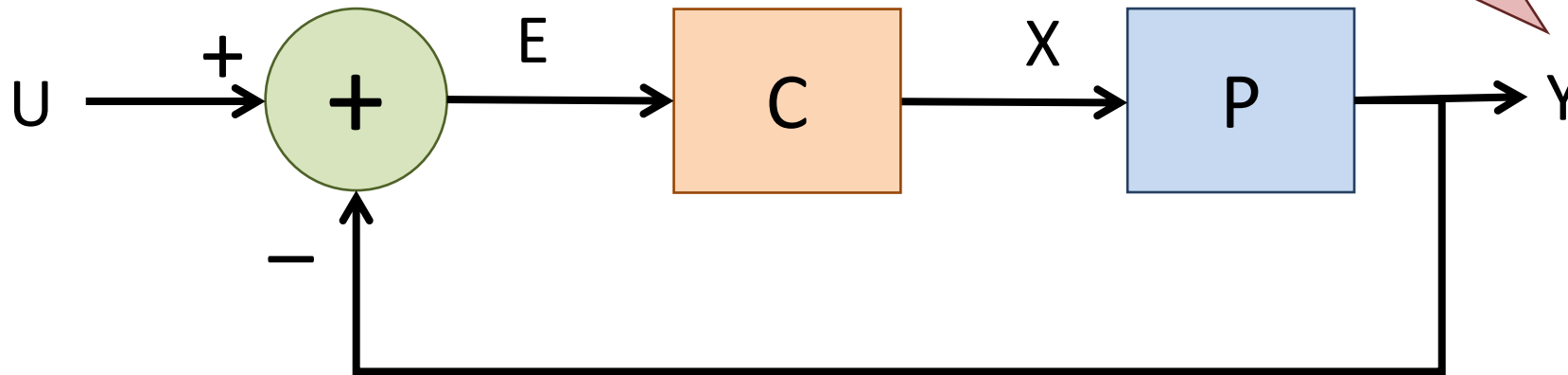To Start The Description Of How The Feedback Works
Suppose Y Is Greater Than The Desired Value




Basic Feedback Review

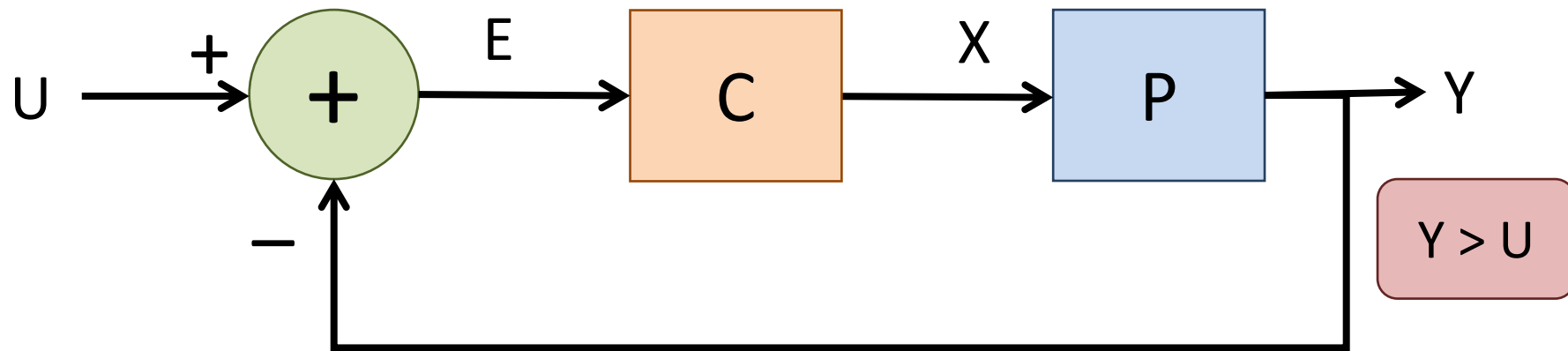
Then The Error, E, Is
Negative
 $E = U - Y$



Basic Feedback Review

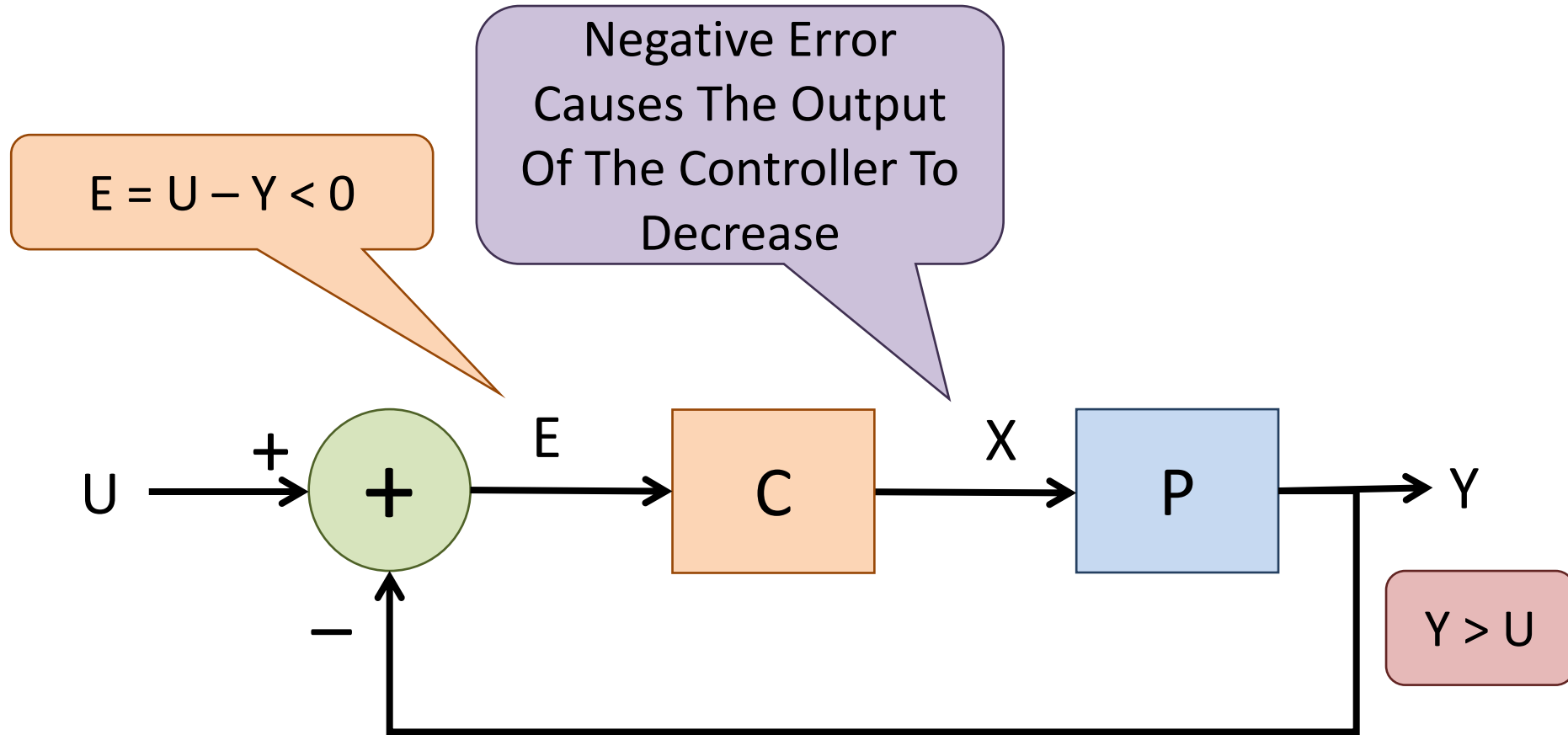


Basic Feedback Review

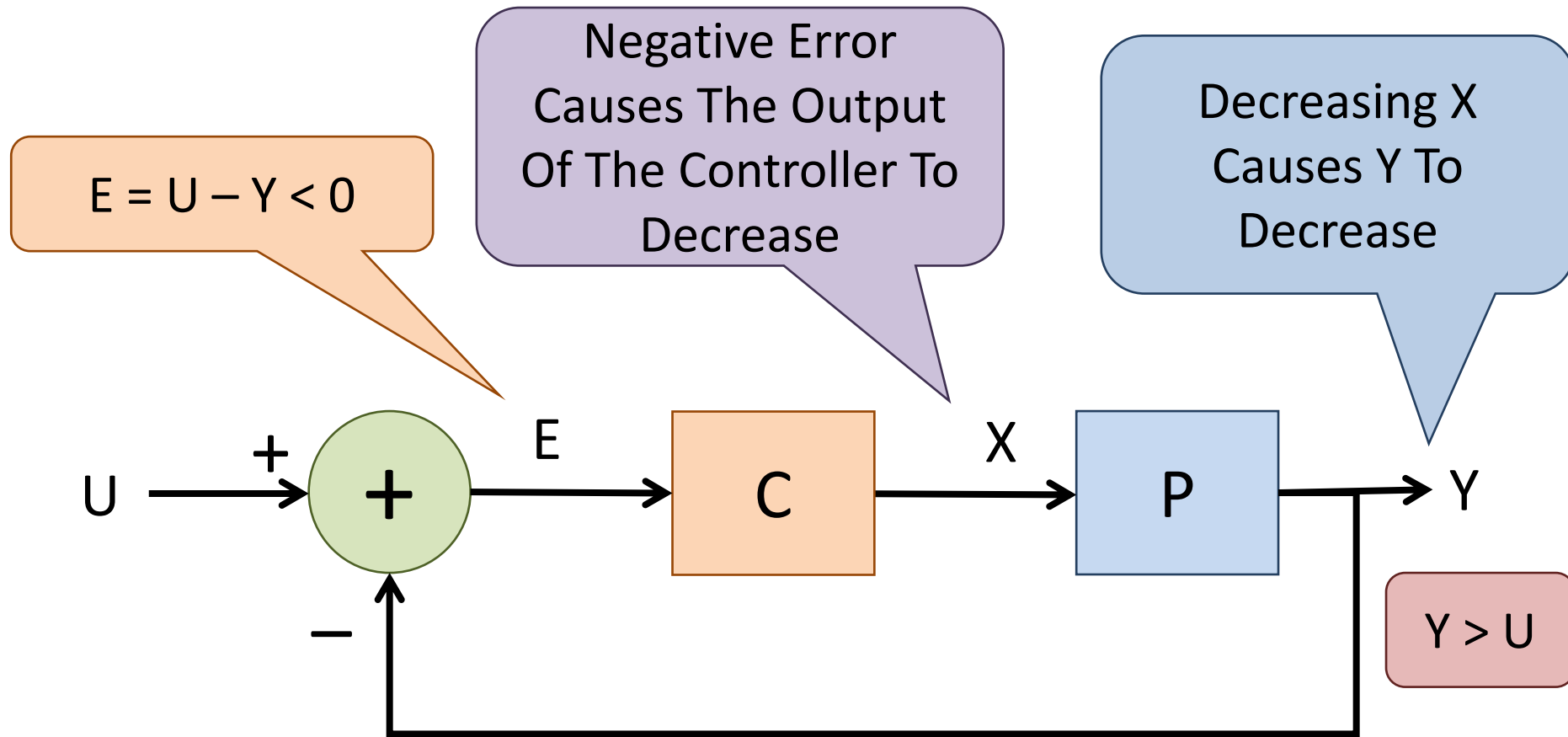


Basic Feedback Review

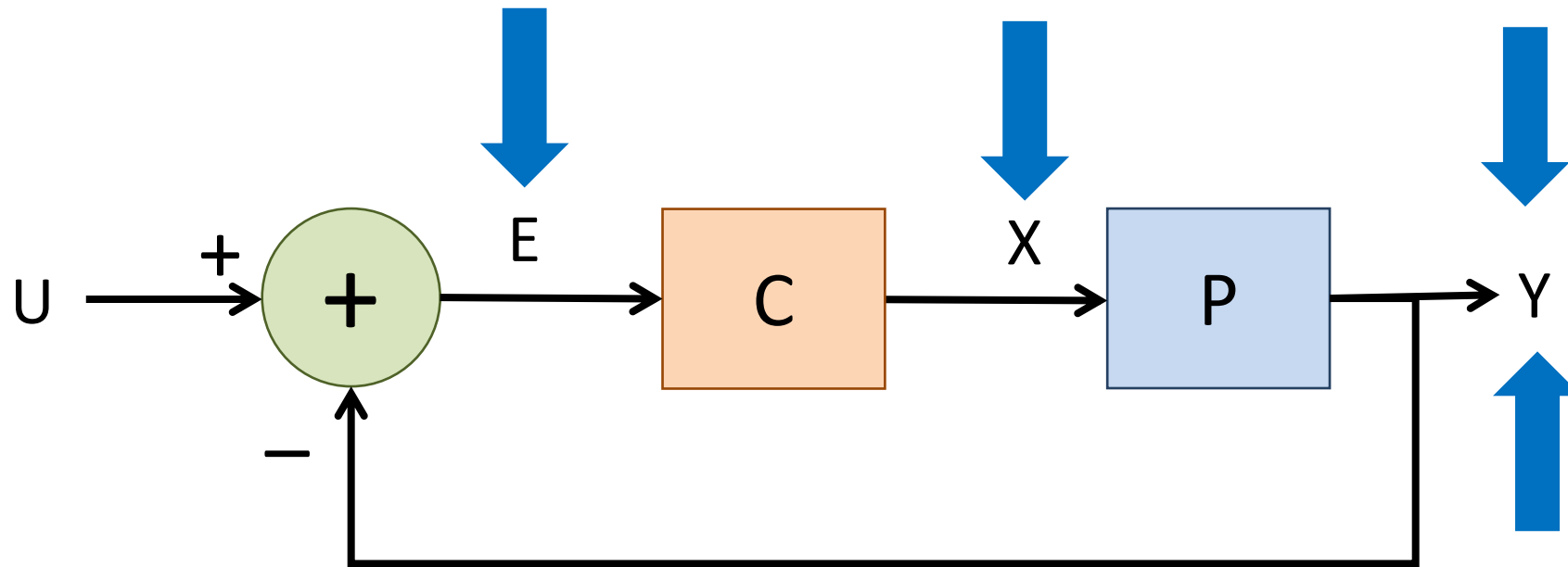Step By Step Starting With Output Too High



Basic Feedback Review

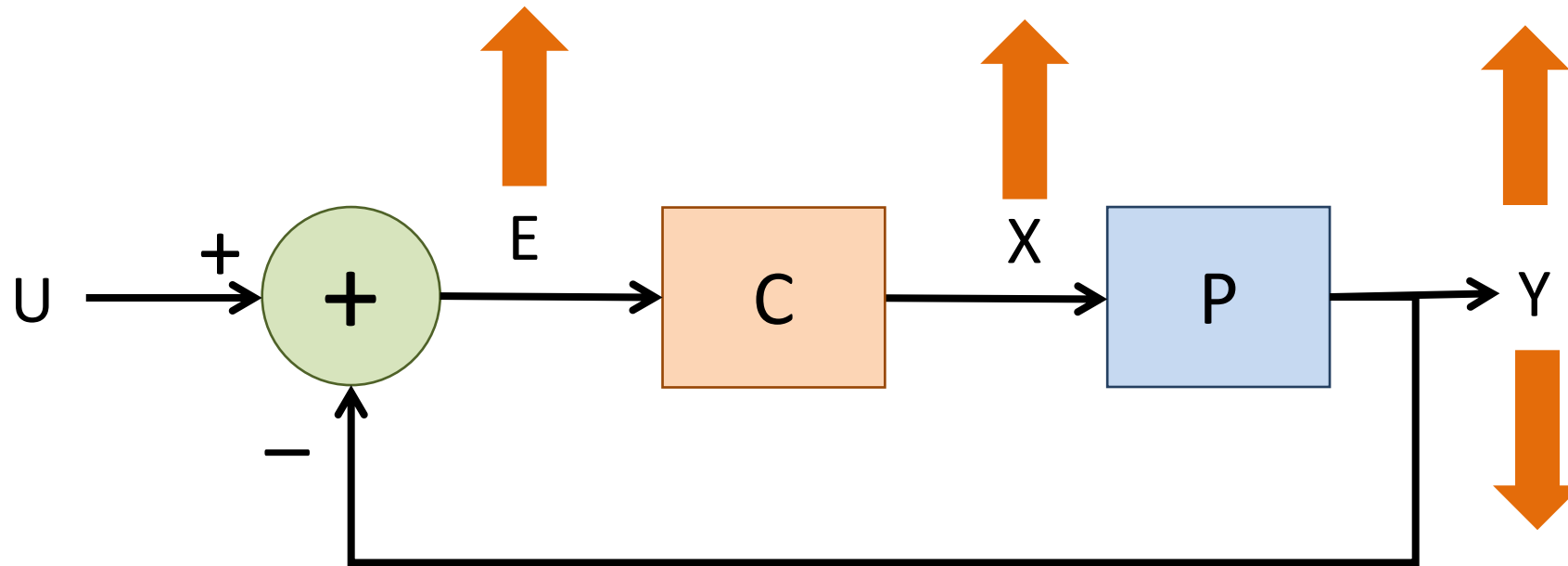Step By Step Starting With Output Too Low



Basic Feedback: The Math

$$Y = P \cdot X$$

$$X = C \cdot E$$

$$E = U - Y$$


$$Y = P \cdot C \cdot E$$

$$= P \cdot C \cdot (U - Y)$$

$$= P \cdot C \cdot U - P \cdot C \cdot Y$$

$$Y + P \cdot C \cdot Y = P \cdot C \cdot U$$
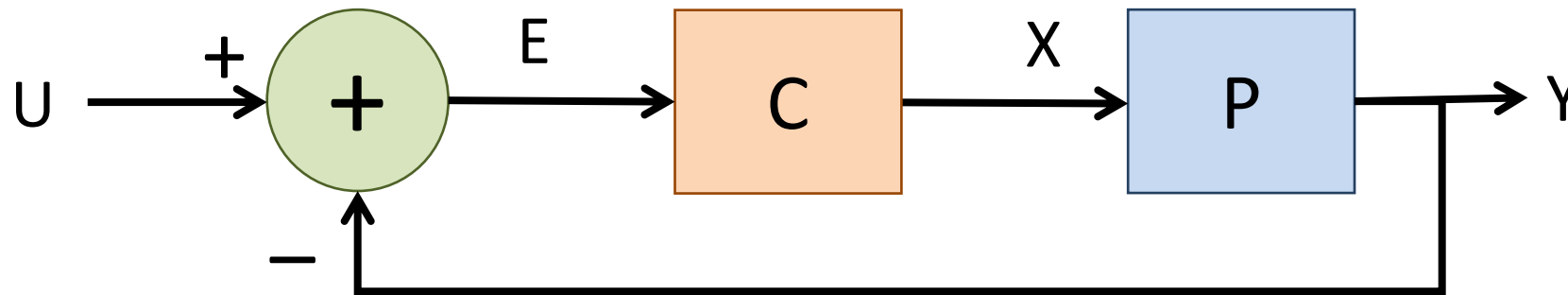
$$Y = \frac{P \cdot C}{1 + P \cdot C} \cdot U$$



Basic Feedback: The Math

$$Y = P \cdot X$$

$$Y = P \cdot C \cdot E$$

Small Signal

$$Y(s) = \frac{P(s) \cdot C(s)}{1 + P(s) \cdot C(s)} \cdot U(s)$$


$$H_{\text{CLOSED_LOOP}}(s) = \frac{Y(s)}{U(s)} = \frac{P(s) \cdot C(s)}{1 + P(s) \cdot C(s)}$$

$$(U - Y)$$

$$U - P \cdot C \cdot Y$$

$$U$$

$$\frac{Y}{1 + P \cdot C} \cdot U$$

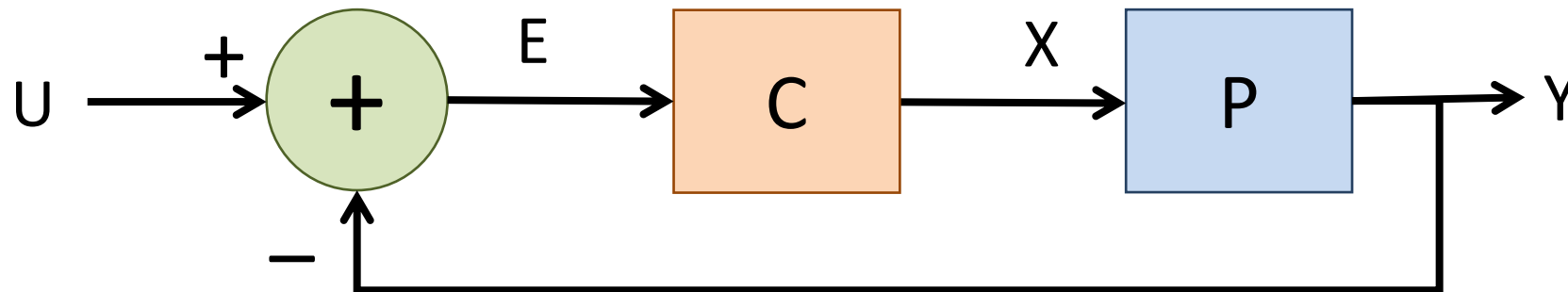

Basic Feedback: The Math

$$Y = P \cdot X$$

$$Y = P \cdot C \cdot E$$

Small Signal

$$Y(s) = \frac{P(s) \cdot C(s)}{1 + P(s) \cdot C(s)} \cdot U(s)$$

$$H_{\text{CLOSED_LOOP}}(s) = \frac{Y(s)}{U(s)} = \frac{P(s) \cdot C(s)}{1 + P(s) \cdot C(s)}$$

$$(U - Y)$$

$$U - P \cdot C \cdot Y$$

$$U$$

$$\cdot U$$

$$P \cdot C$$

This Is The “Closed Loop Gain”

Basic Feedback: Open Loop Gain


$$H_{CLOSED_LOOP}(s) = \frac{Y(s)}{U(s)} = \frac{P(s) \cdot C(s)}{1 + P(s) \cdot C(s)}$$

If Denominator Is Zero
Then The Loop Is Unstable
 $P(s) \cdot C(s) = -1$


$$H_{OPEN_LOOP}(s) = T(s) = C(s) \cdot P(s)$$

When Designing The Feedback
Loop We Will Focus On The
Open Loop Gain
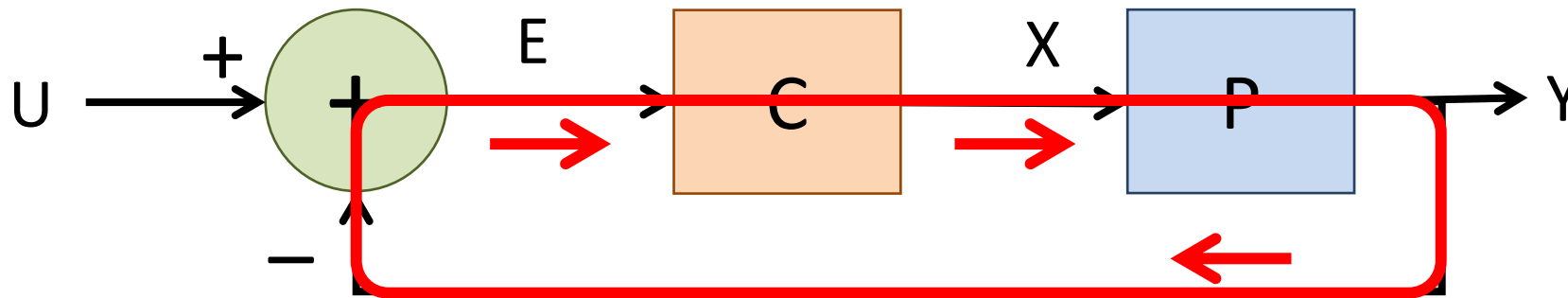
$$H_{CLOSED_LOOP}(s) = \frac{Y(s)}{U(s)} = \frac{T(s)}{1 + T(s)}$$



Buck Converter

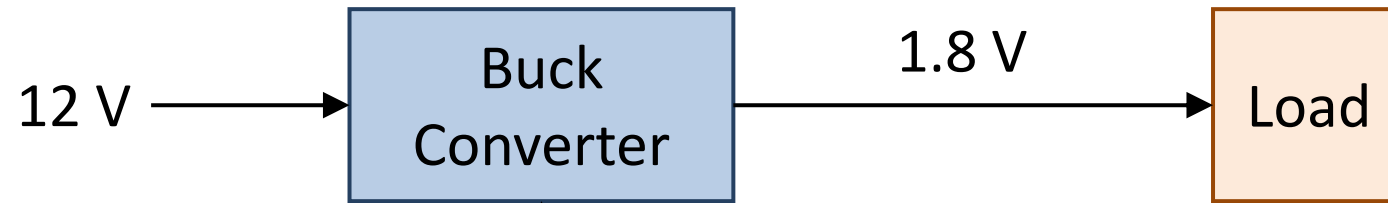


$$\begin{aligned} V_{OUT} &= D \cdot V_{IN} \\ &= 0.15 \cdot 12 \text{ V} \\ &= 1.8 \text{ V} \end{aligned}$$


What Happens If:
Input Voltage Changes?
Load Changes?

Output
Voltage
Changes

Buck Converter With Feedback

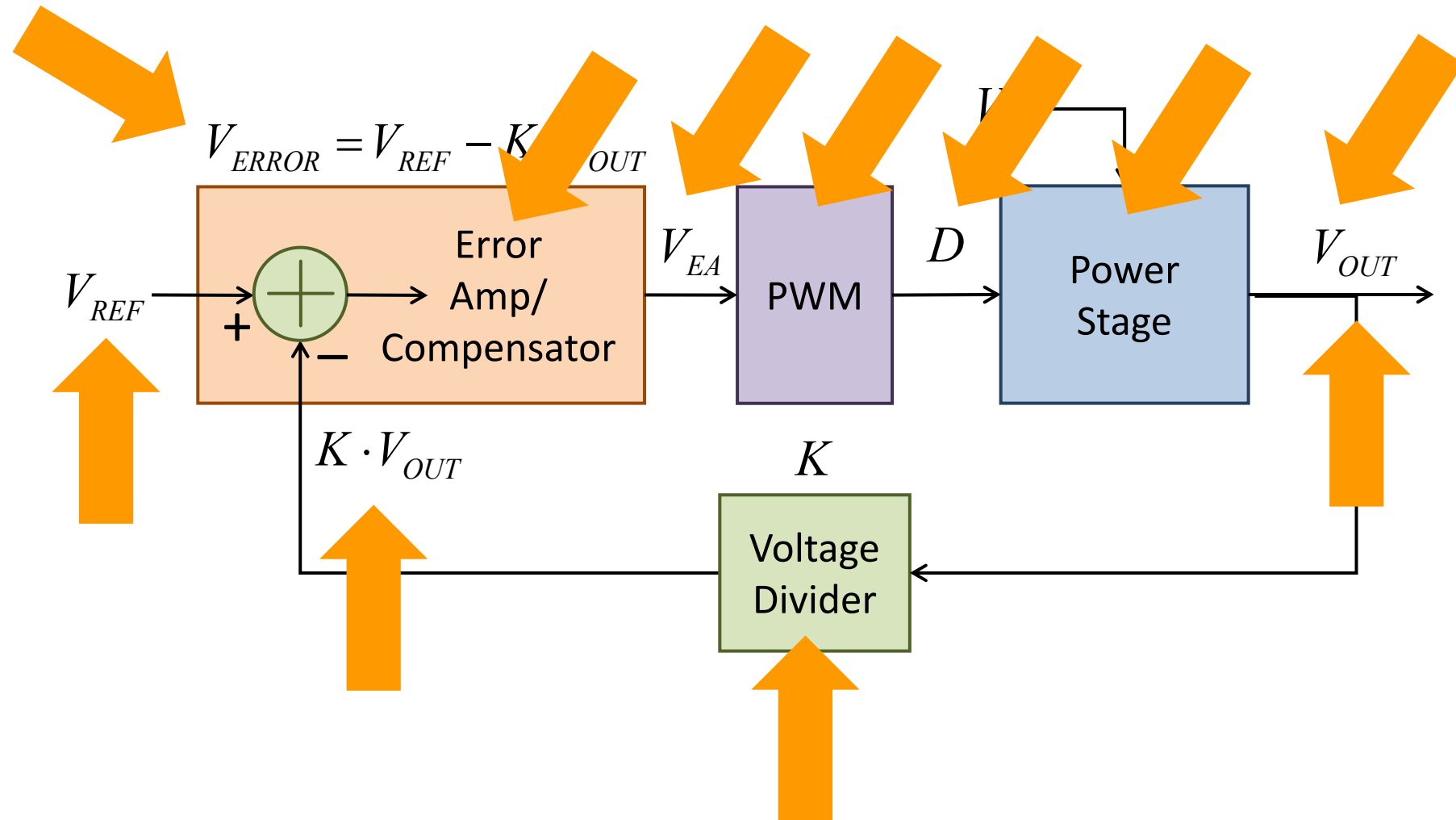


Buck Converter With Feedback

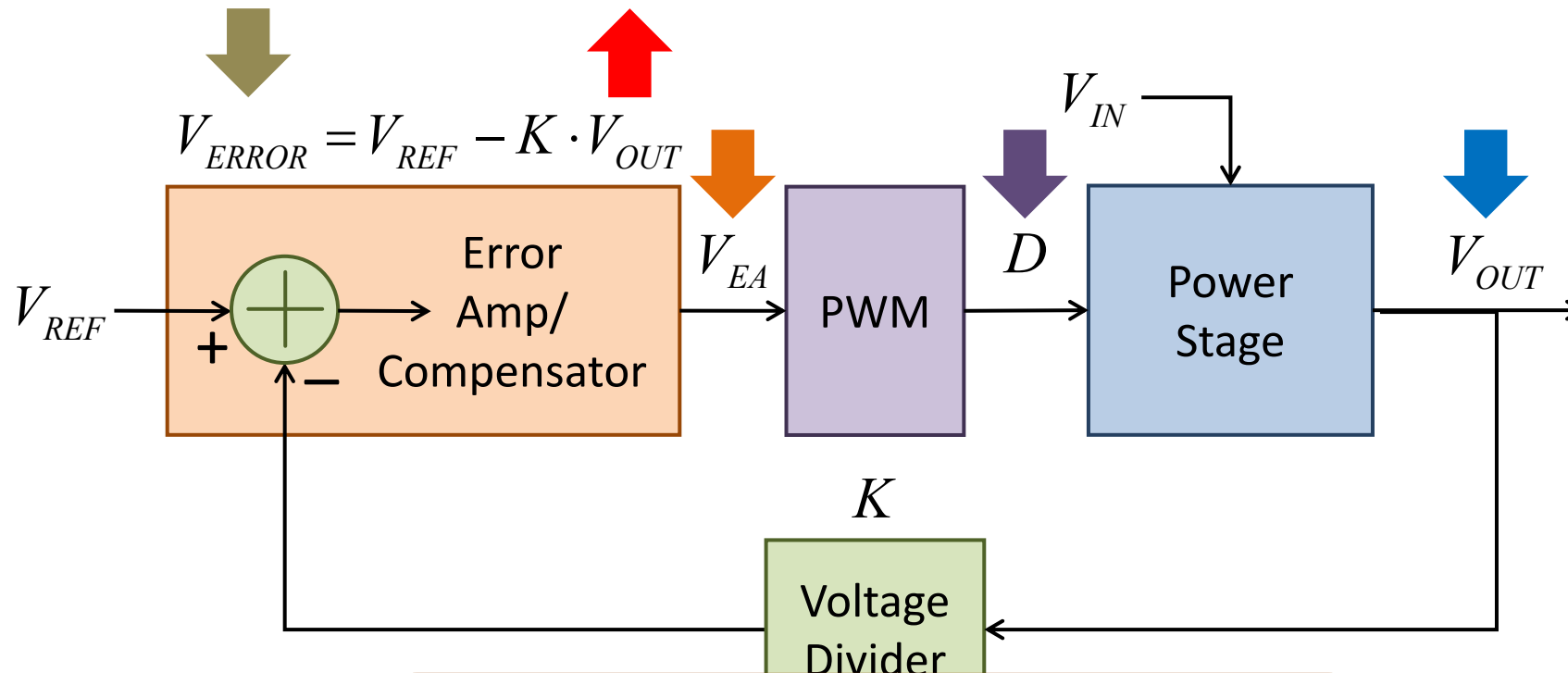

Output Voltage Too High \Rightarrow
Error Voltage Is Negative \Rightarrow
Duty Cycle Is Decreased \Rightarrow
Output Voltage Is Reduced

Buck Converter With Feedback

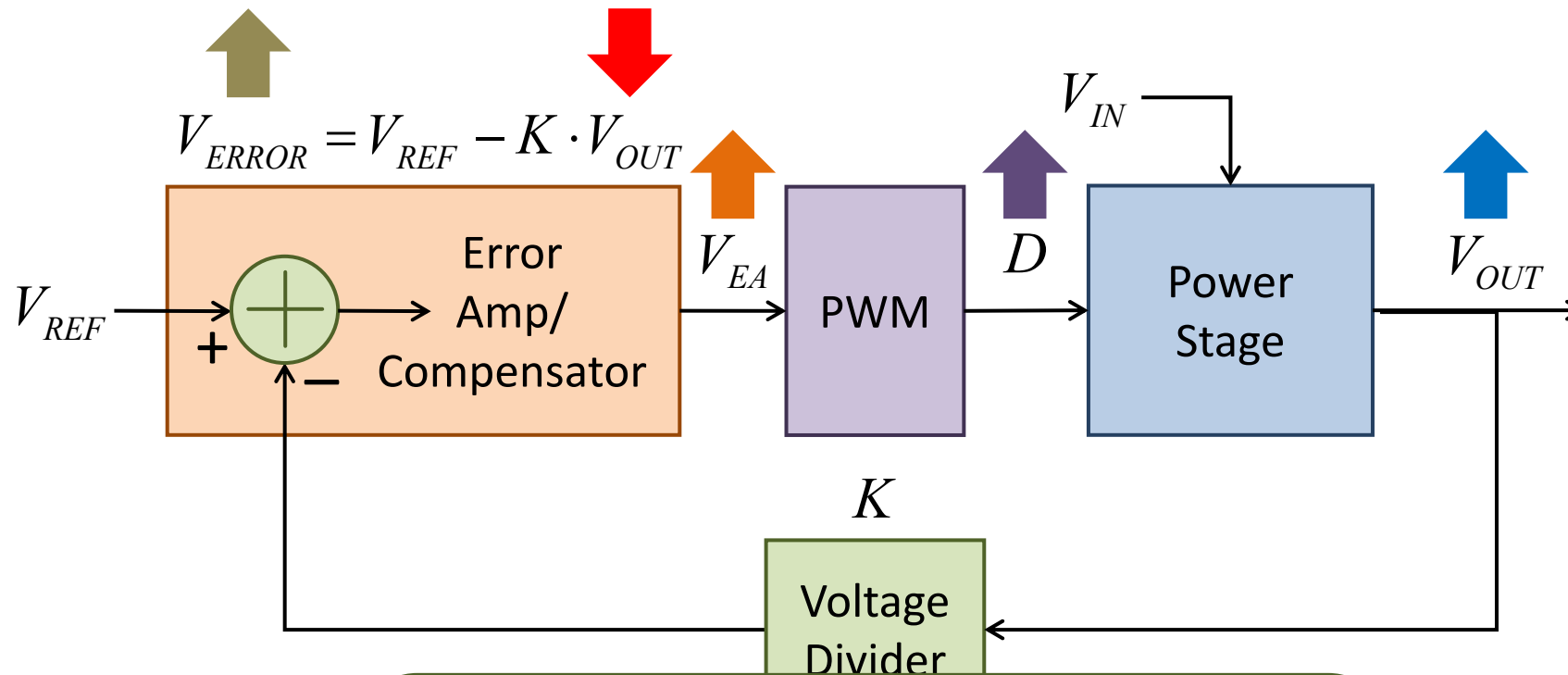

Output Voltage Too Low \Rightarrow
Error Voltage Is Positive \Rightarrow
Duty Cycle Is Increased \Rightarrow
Output Voltage Is Increased


Feedback Concerns

Tracking

Disturbance
Rejection

Stability

Feedback Concerns

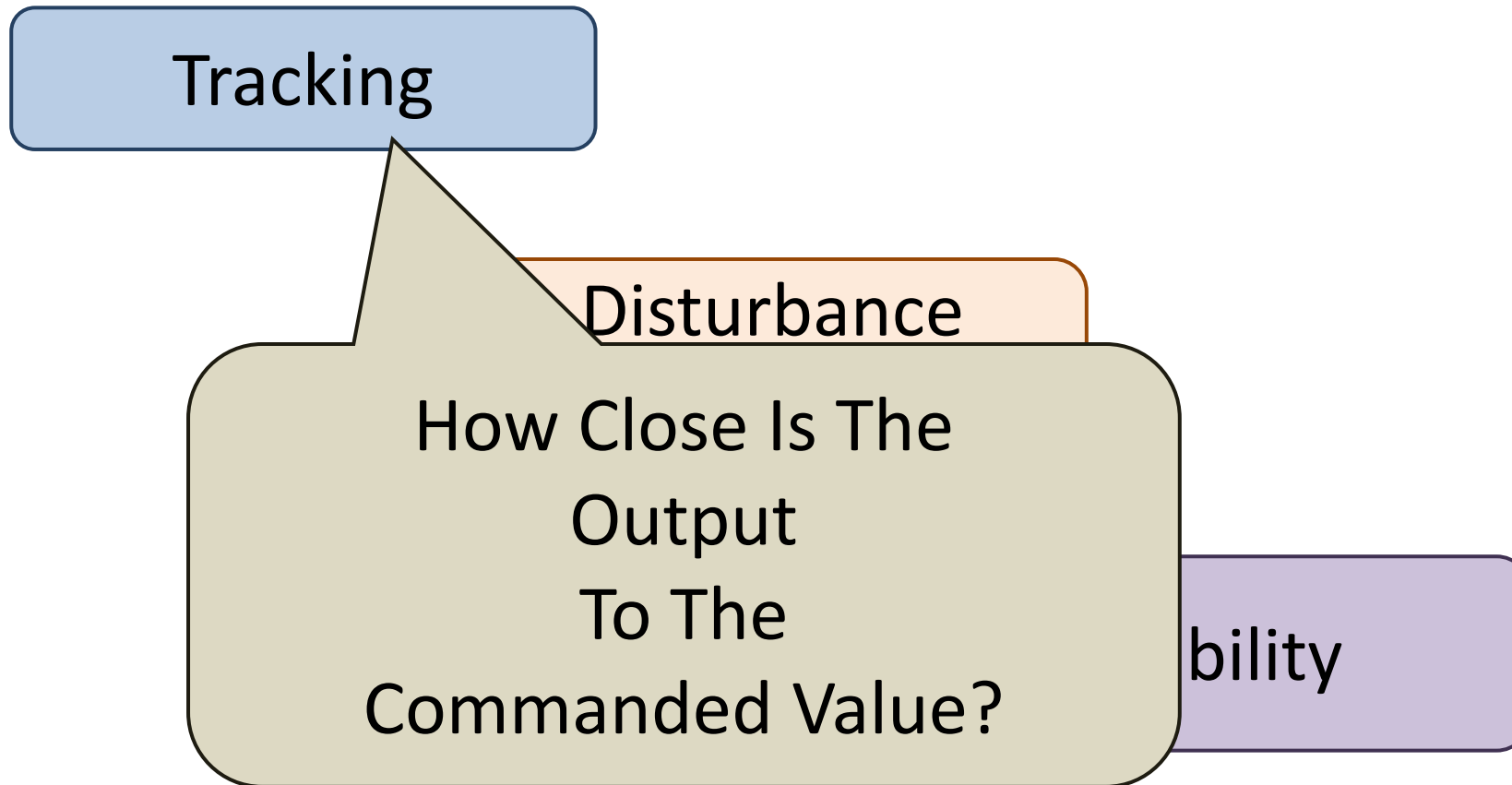

Feedback Concerns

Tracking

Disturbance
Rejection

If The Input Voltage Changes,
Or The Load Changes,
Or There Is Noise, How Well Does
The Output Return To The Proper Value?

Feedback Concerns


Output Does Not “Run Away”

“Bounded Input, Bounded Output”

“Lyapunov”


Stability

Loop Gain

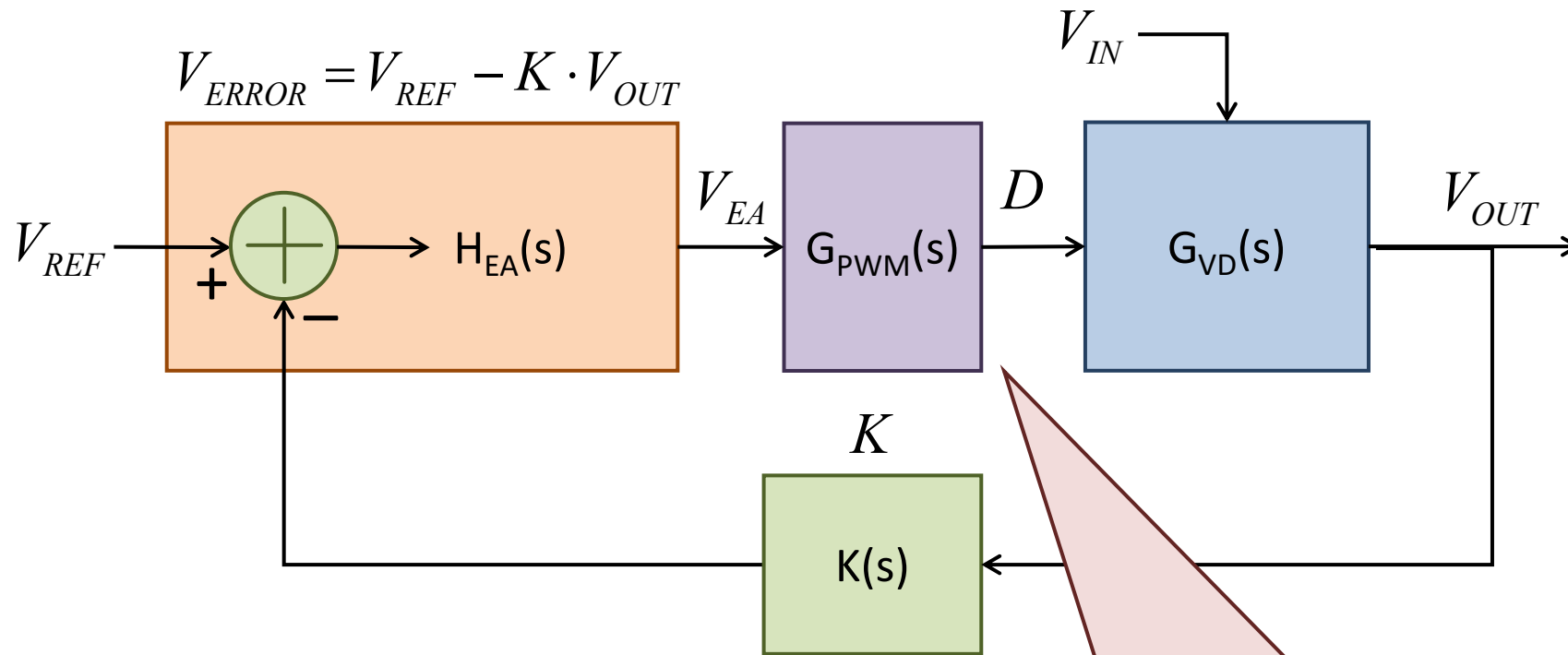


Each Block Of The Control Loop
Has Its Own Transfer Function

Loop Gain

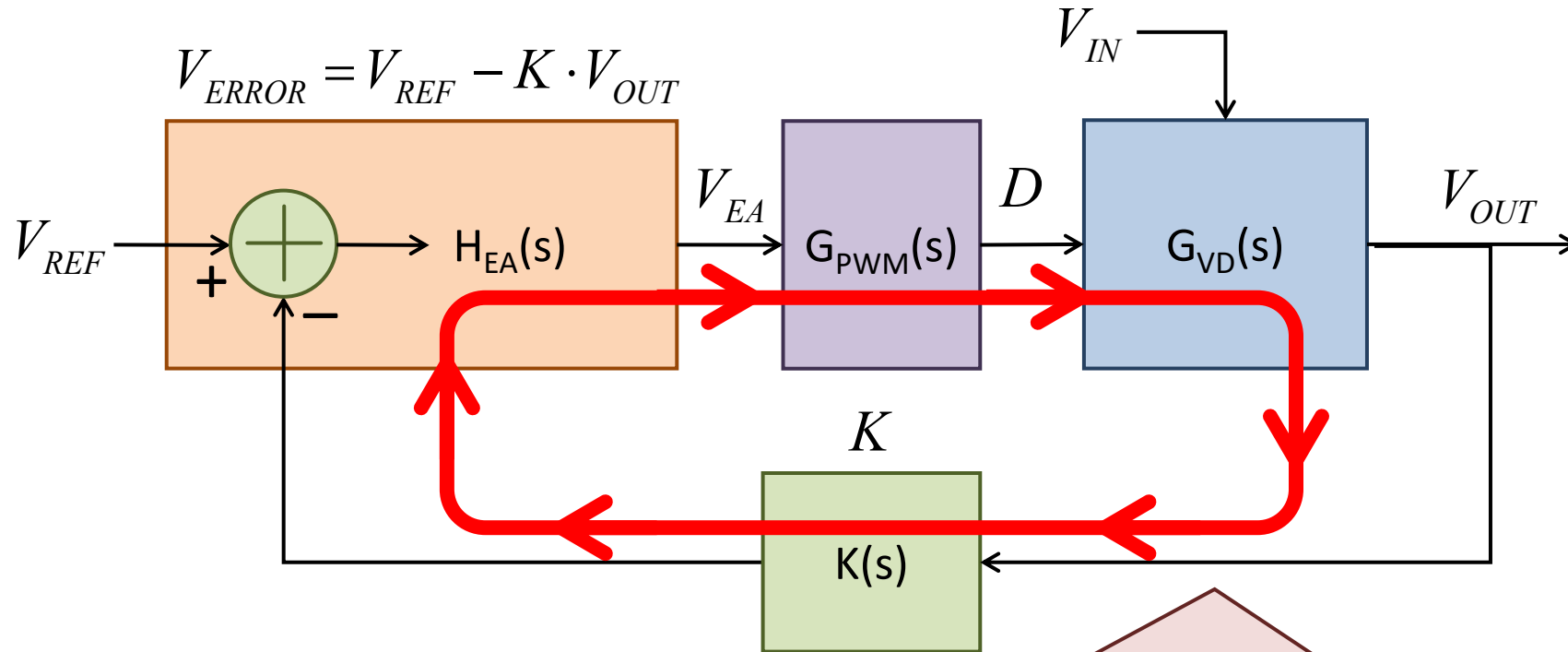

What Happens To A Signal As It Goes Around The Control Loop?


Loop Gain $T(s)$

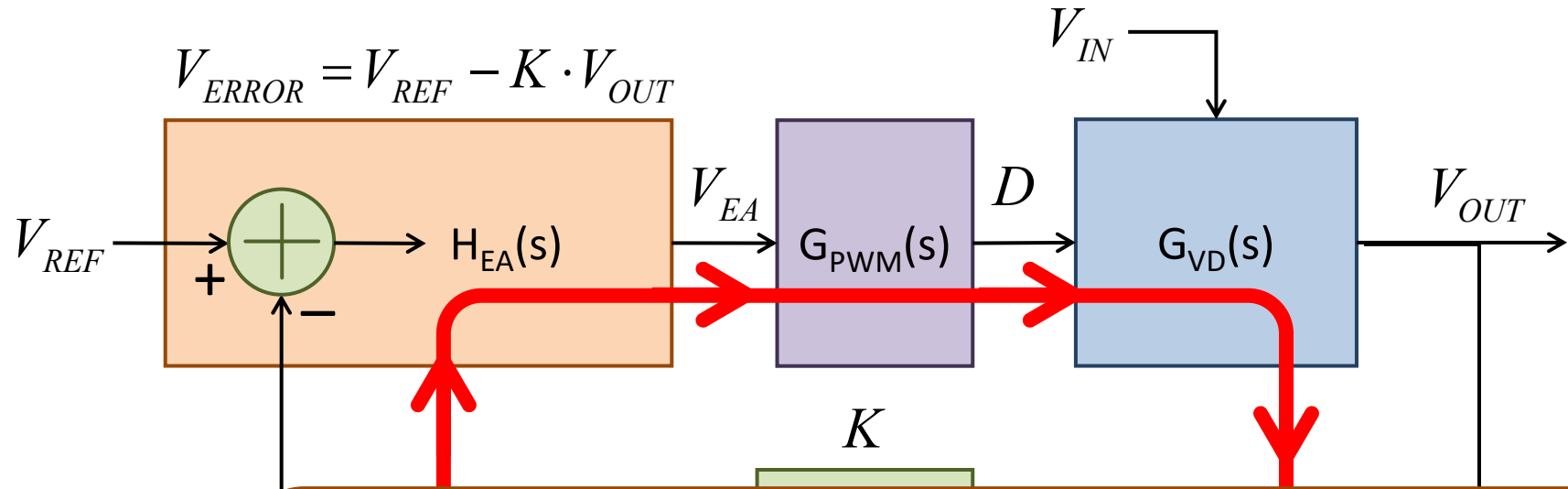

Open Loop Gain

$$T(s) = K(s) \cdot H_{EA}(s) \cdot G_{PWM}(s) \cdot G_{VD}(s)$$

How To Get Good Tracking?

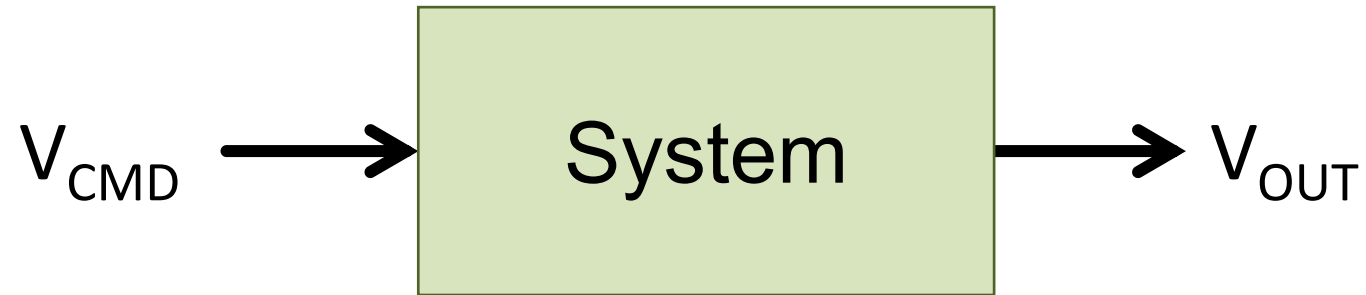


Good Tracking Means


$$V_{\text{OUT}} = V_{\text{CMD}}$$

That Is, We Get The Output We Want
Based On The Input Command


Op-Amp Buffer/Follower

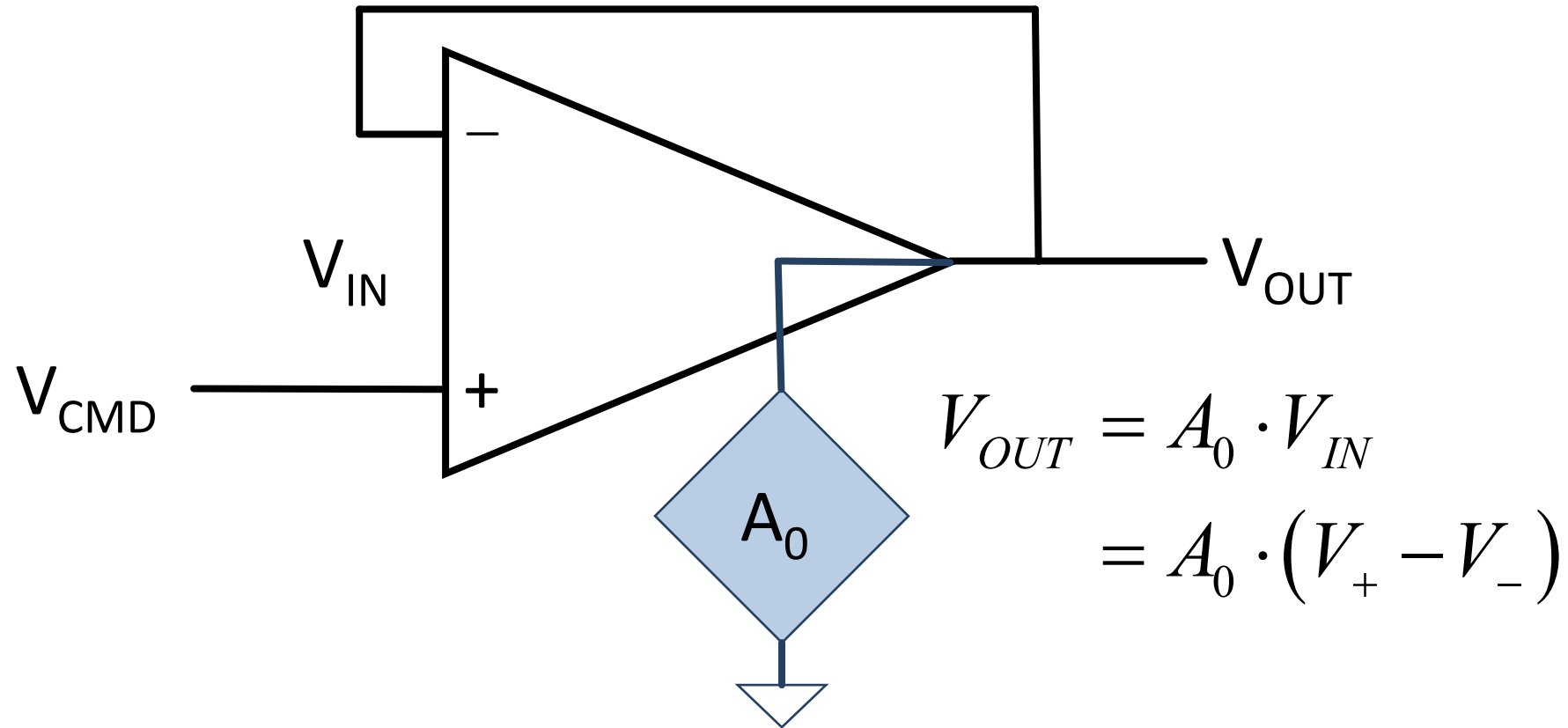


Op-Amp Buffer/Follower Example

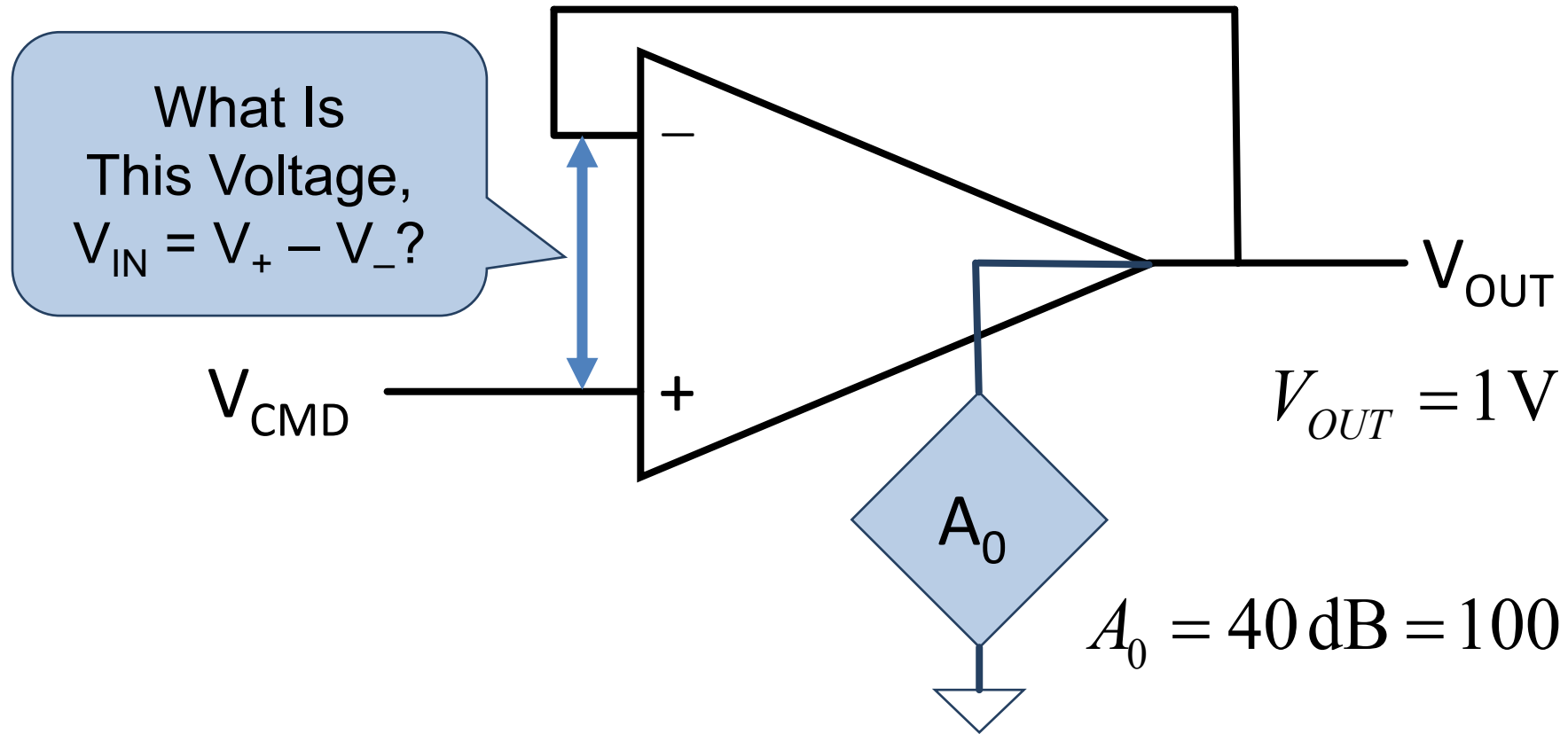

Op-Amp Buffer/Follower Example

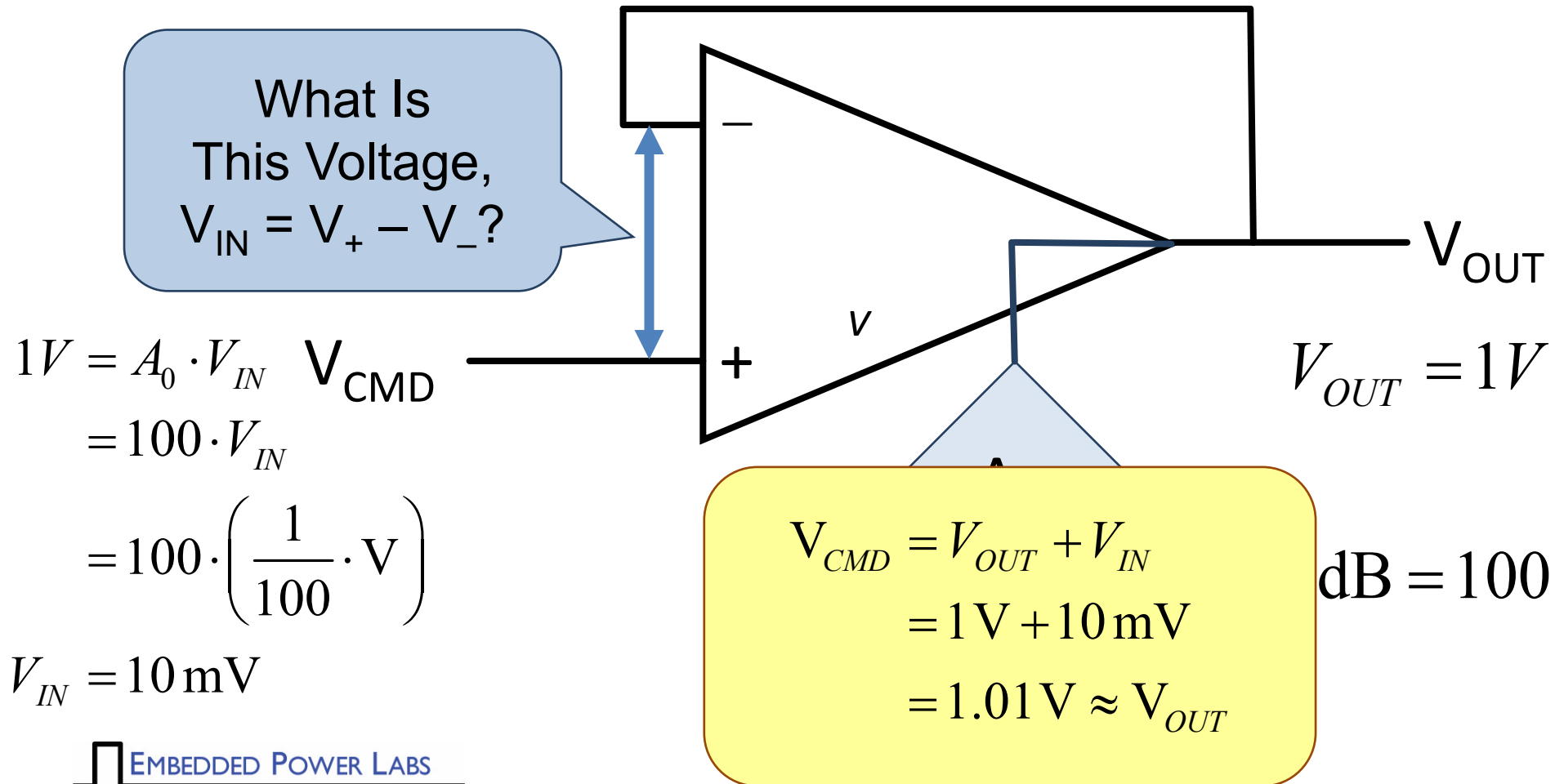

Op-Amp Buffer/Follower Example

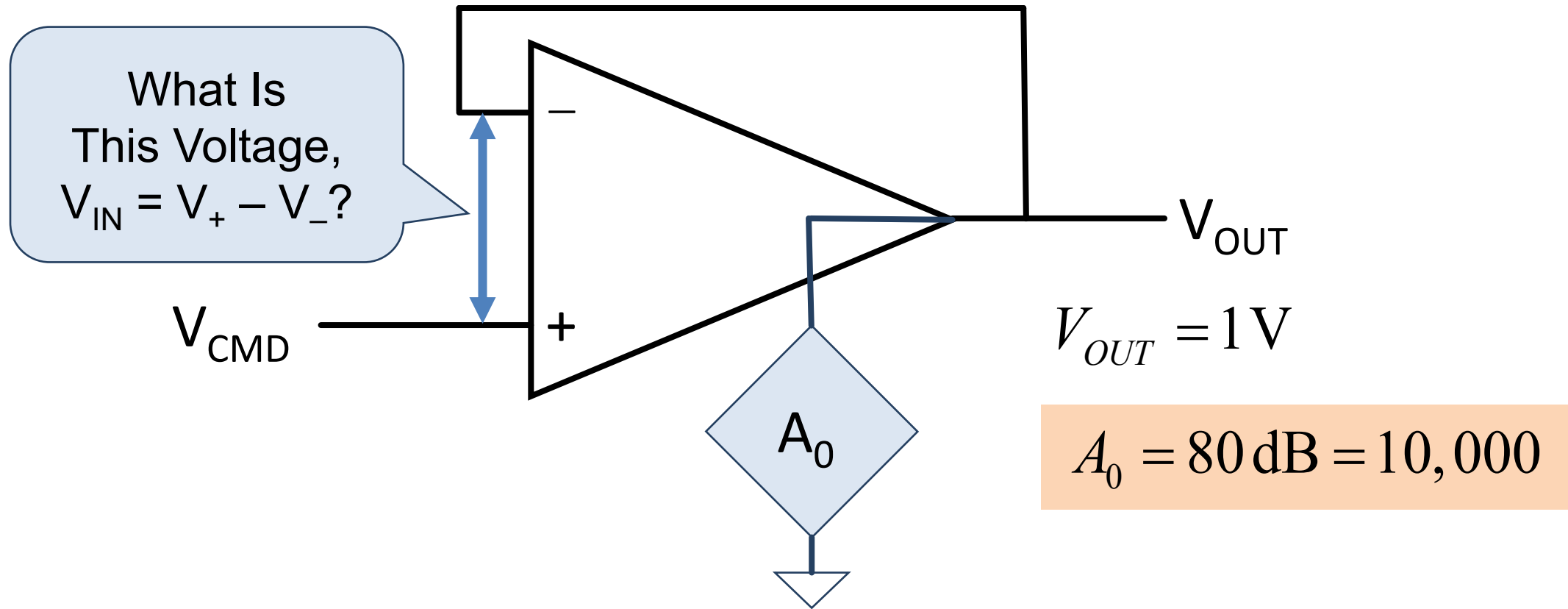


Op-Amp Buffer/Follower Example

What Is This Voltage, $V_{IN} = V_+ - V_-$?


$$\begin{aligned} 1V &= A_0 \cdot V_{IN} \quad V_{CMD} \\ &= 10,000 \cdot V_{IN} \\ &= 10,000 \cdot \left(\frac{1}{10,000} \cdot V \right) \end{aligned}$$

$$V_{IN} = 100 \mu V$$

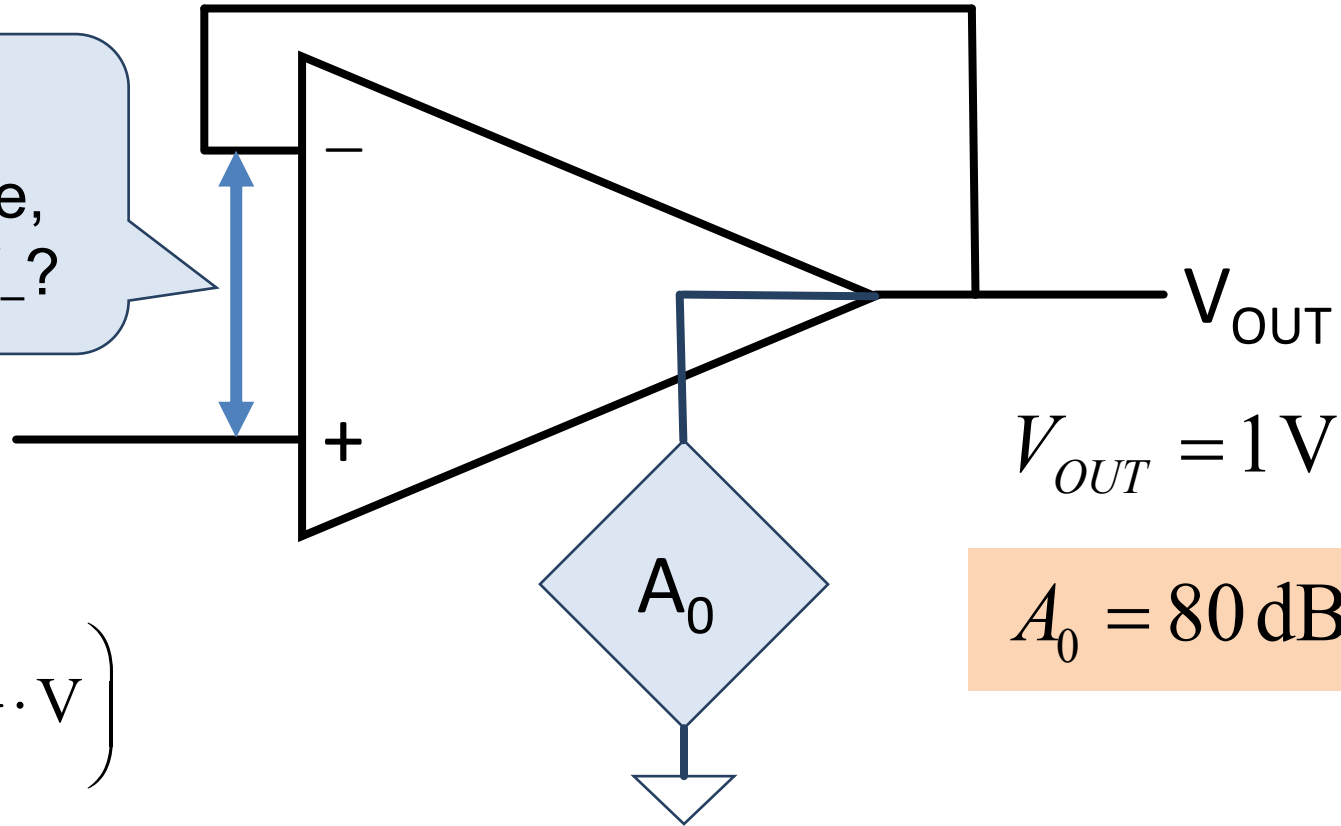


$$A_0 = 80 \text{ dB} = 10,000$$


Op-Amp Buffer/Follower Example

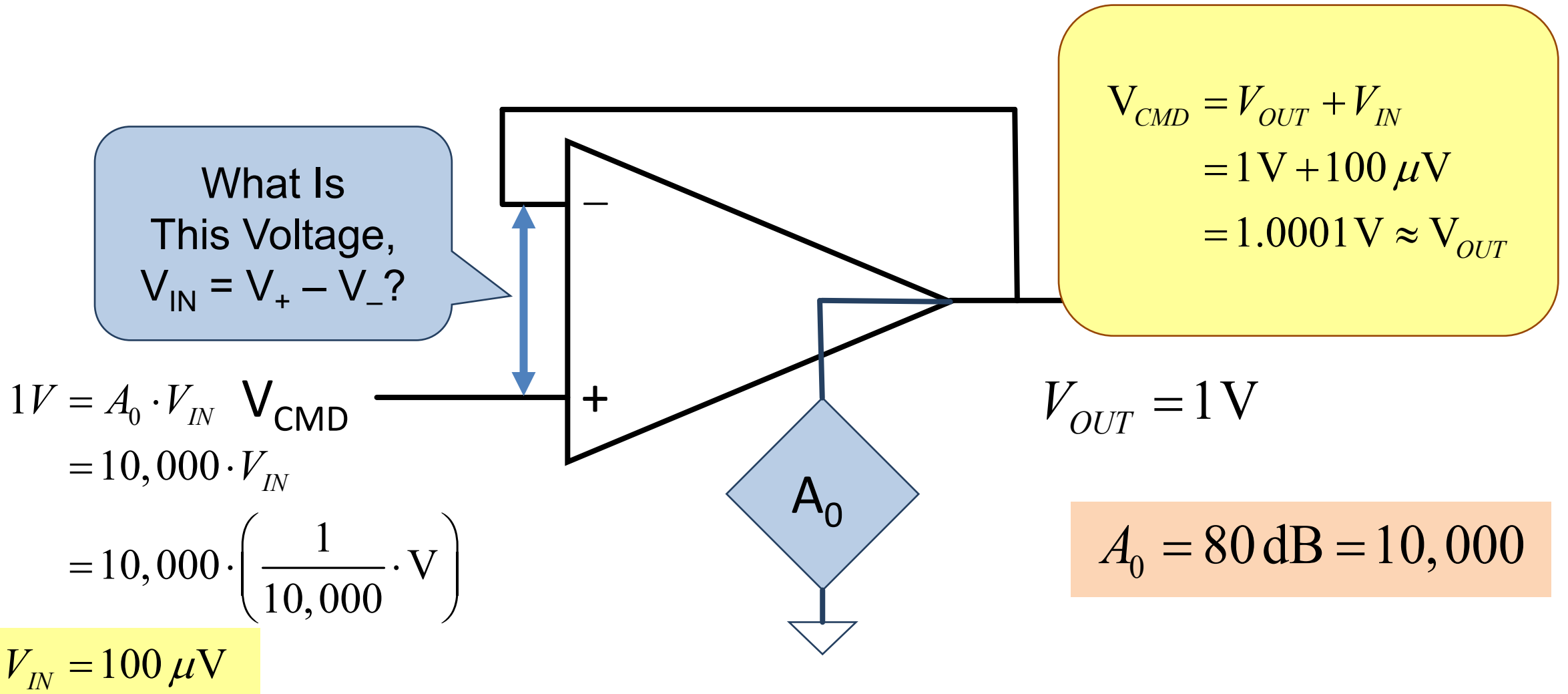


Op-Amp Buffer/Follower

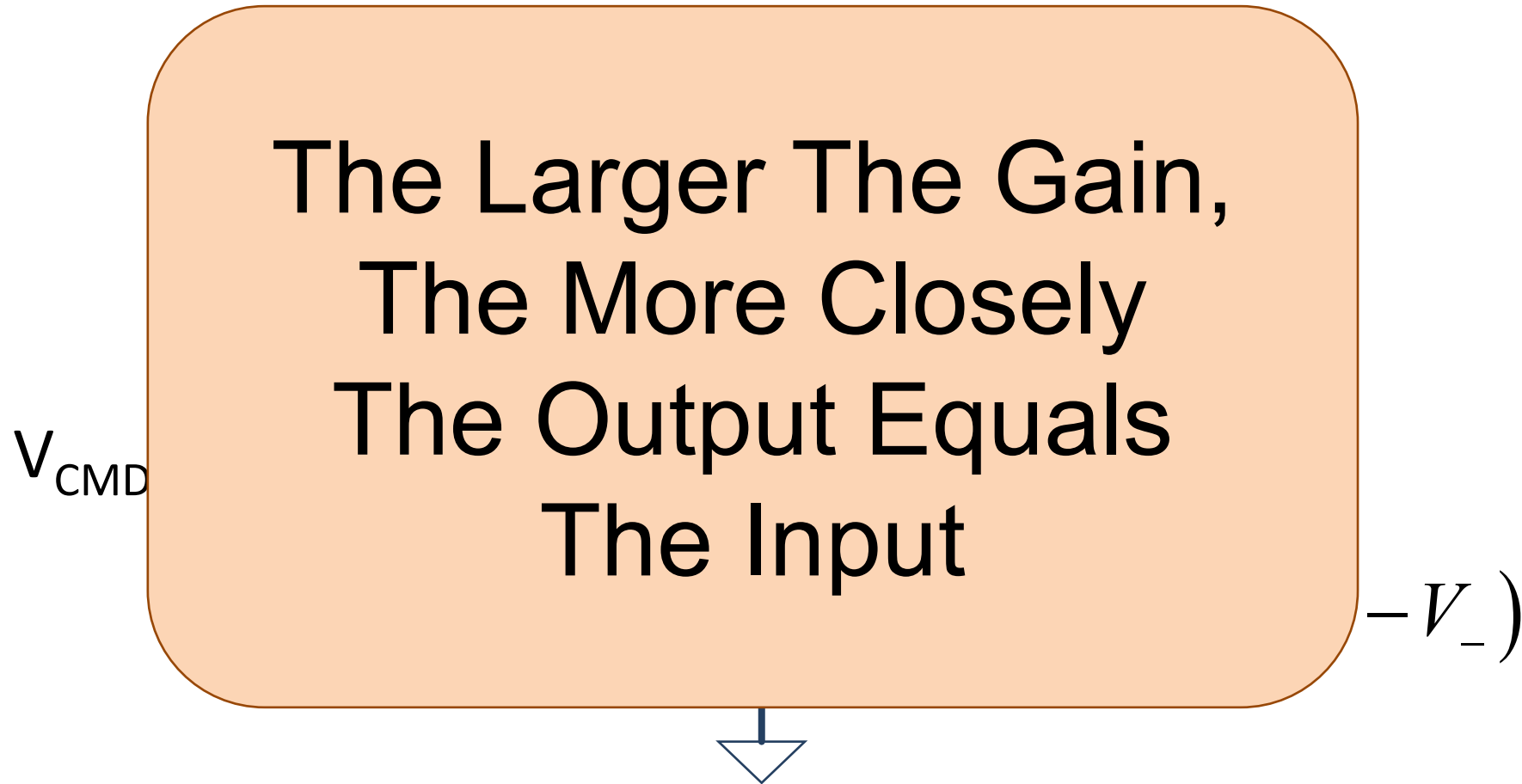

How To Get Good Tracking?

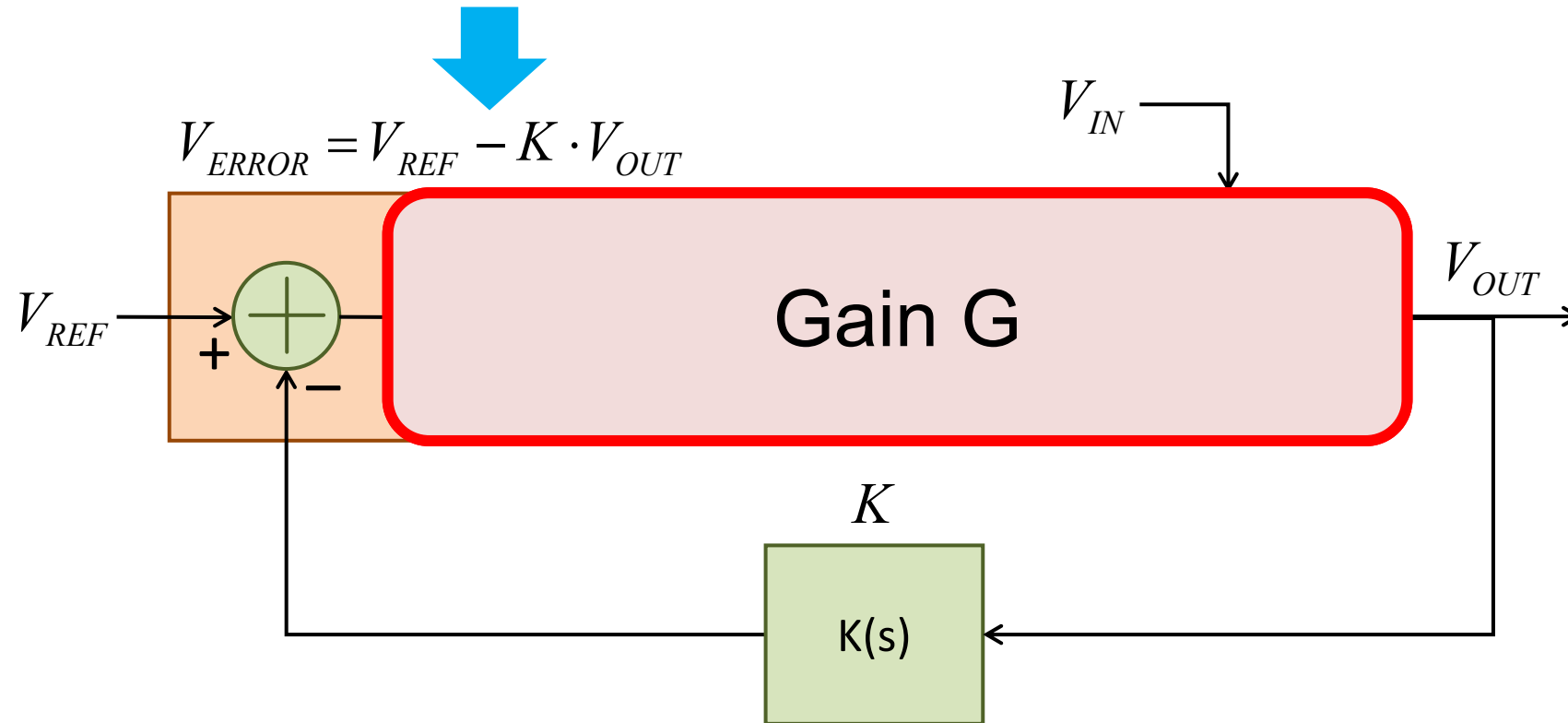


How To Get Good Tracking?

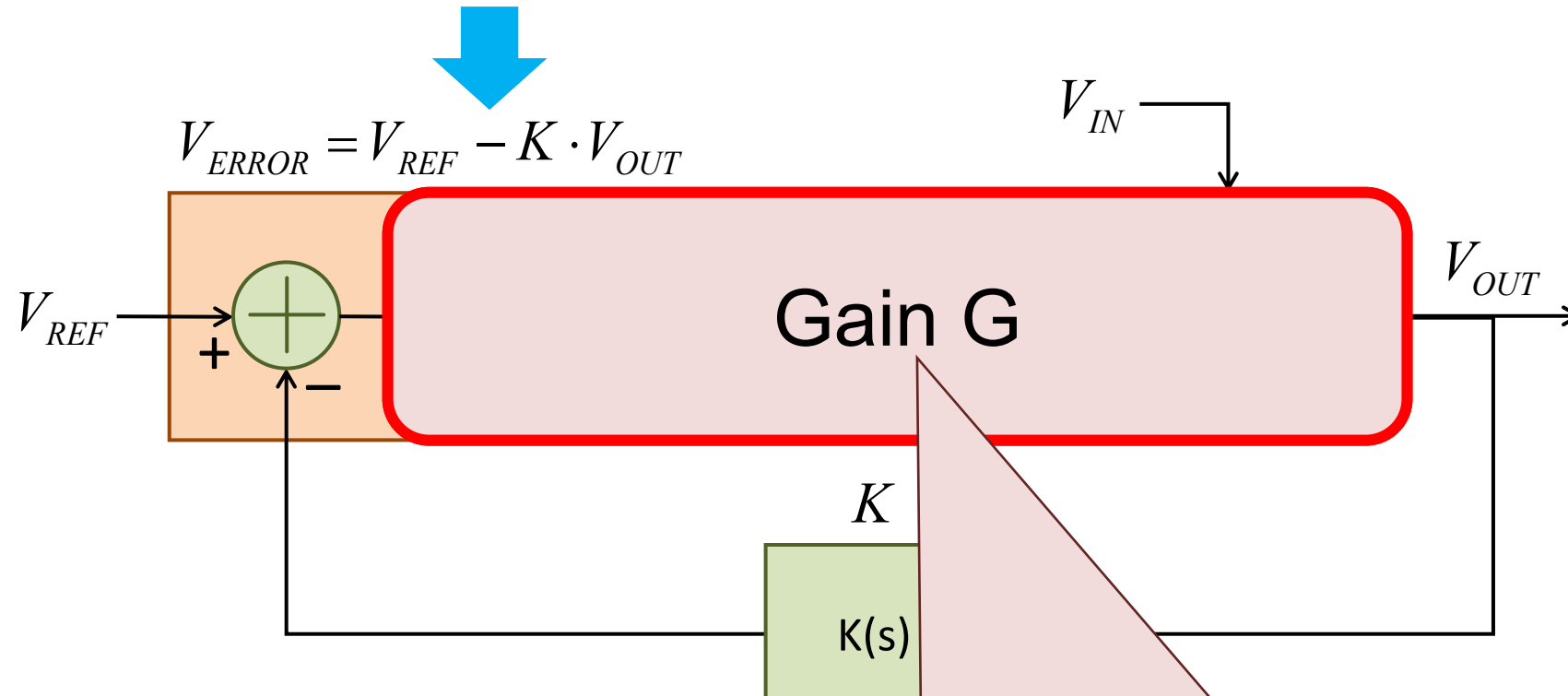


The Larger Gain G ,
The More Closely The Output
Follows The Reference Input


How To Get Good Tracking?

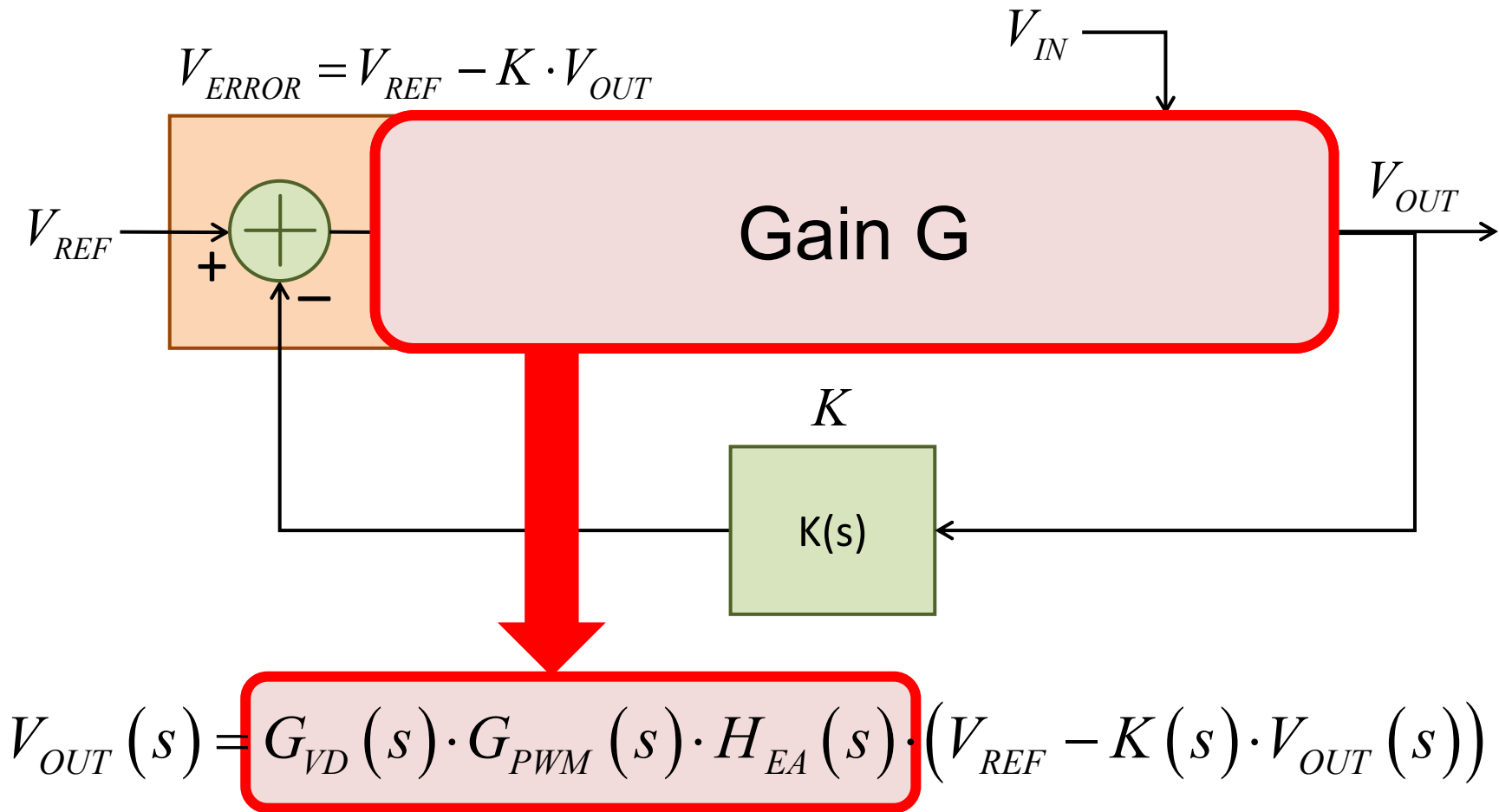

Loop Gain $T(s)$

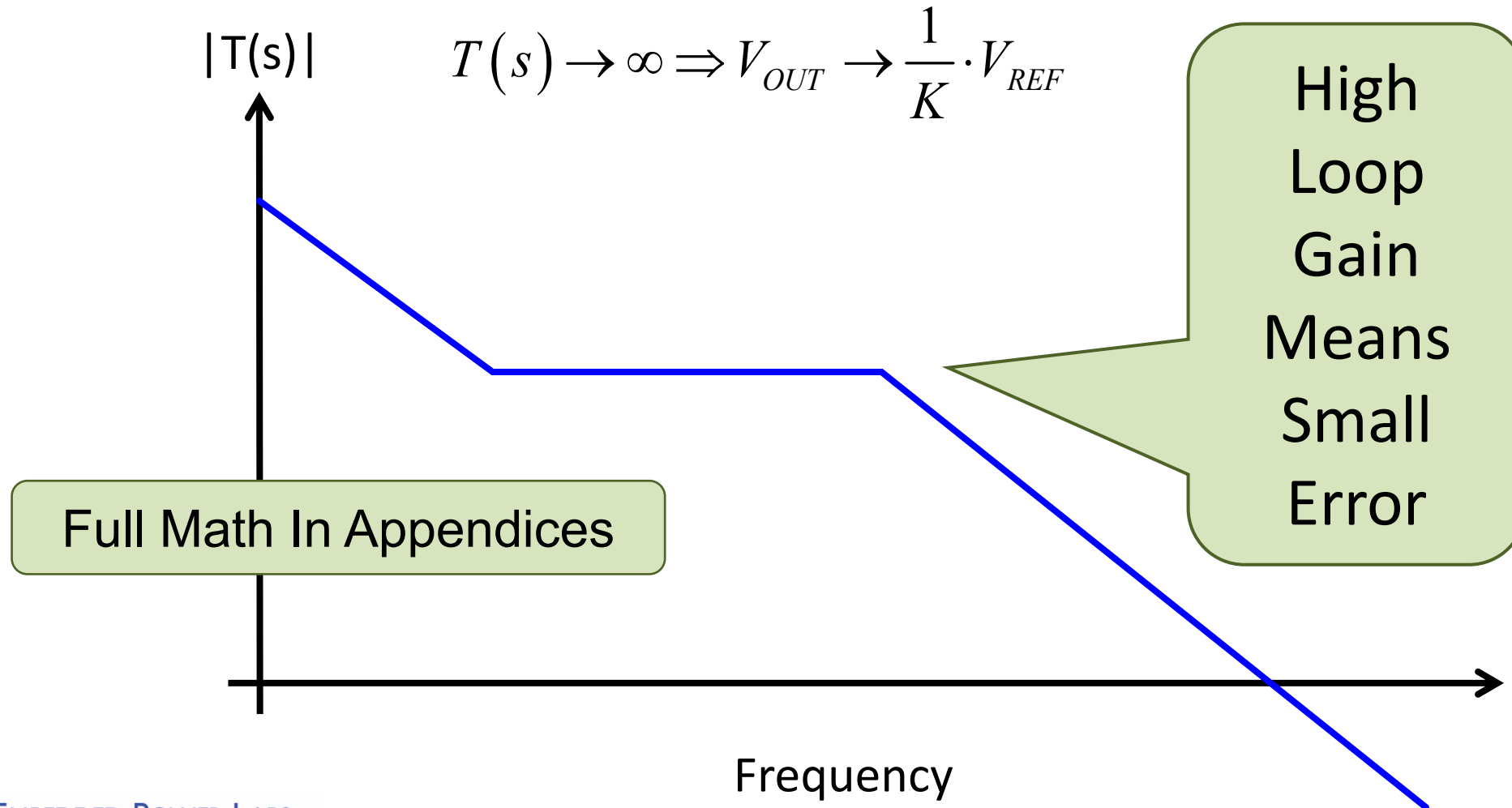


Assuring Steady State Tracking

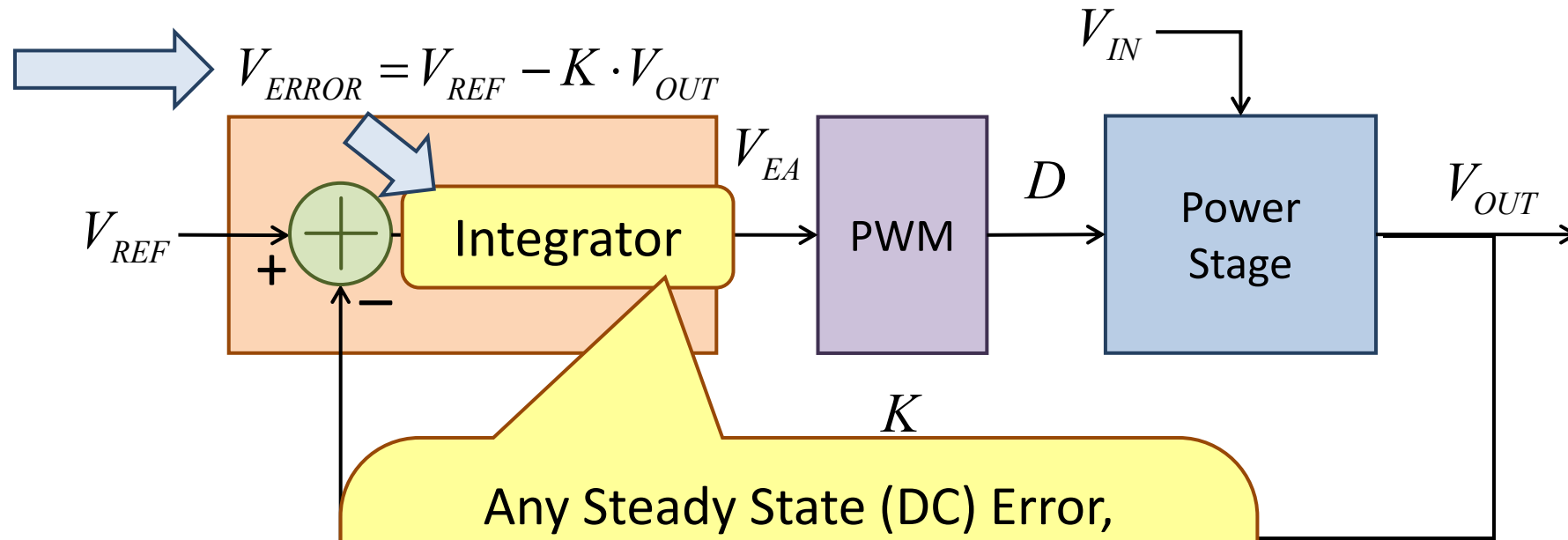

Any Steady State (DC) Error,
No Matter How Small,
Is Integrated Over Time
To Make An Error Amp Output
That Corrects The Duty Cycle
To Drive The Error To Zero


Analog Integrator

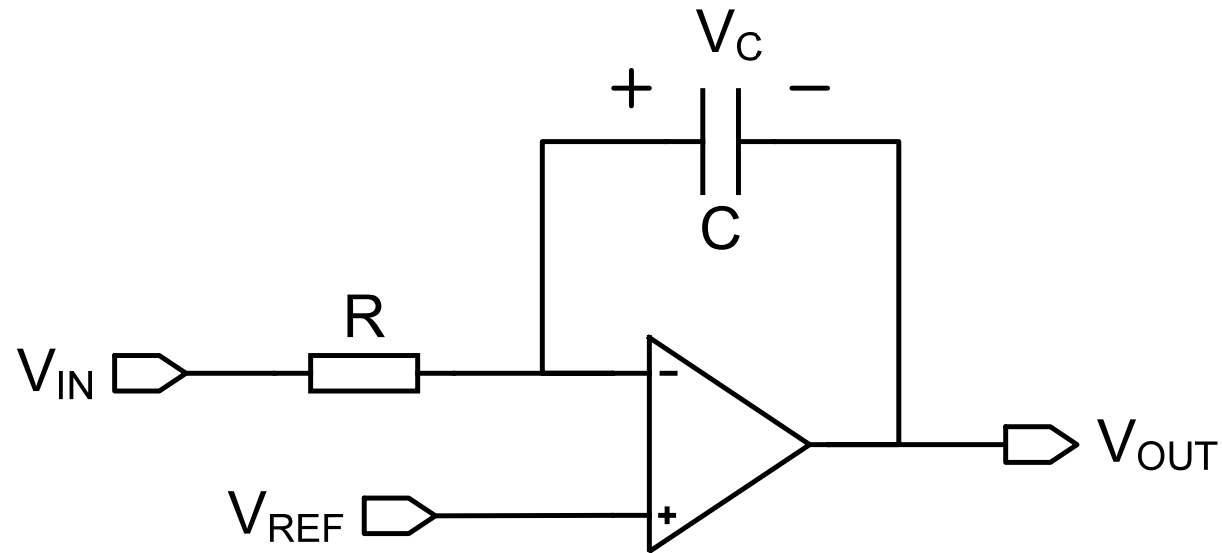

$$\begin{aligned}v_{OUT}(t) &= V_{REF} - v_C(t) \\ &= V_{REF} - \frac{1}{C} \cdot \int_0^t i_C(\tau) d\tau\end{aligned}$$


$$\begin{aligned}v_{OUT}(t) &= V_{REF} - \frac{1}{C} \cdot \int_0^t \frac{v_{in}(\tau) - V_{REF}}{R} d\tau \\ &= V_{REF} - \frac{1}{R \cdot C} \cdot \int_0^t v_{ERROR}(\tau) d\tau\end{aligned}$$

Analog Integrator

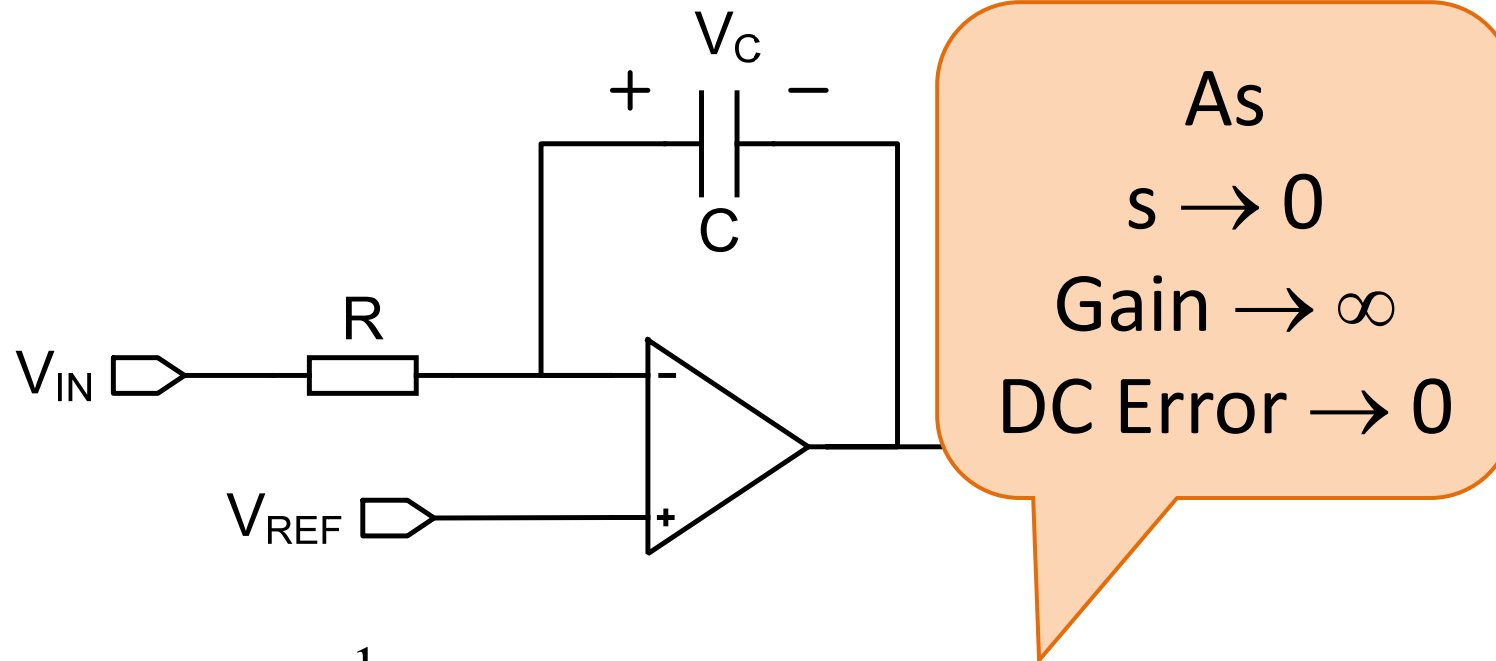


$$\frac{v_{OUT}(s)}{v_{IN}(s)} = -\frac{Z_F(s)}{Z_S(s)} = -\frac{1}{s \cdot C} = -\frac{1}{s \cdot R \cdot C} = -\frac{1}{s} = -\frac{\omega_P}{s} \quad \omega_P = \frac{1}{R \cdot C}$$


Crossover Frequency, F_C

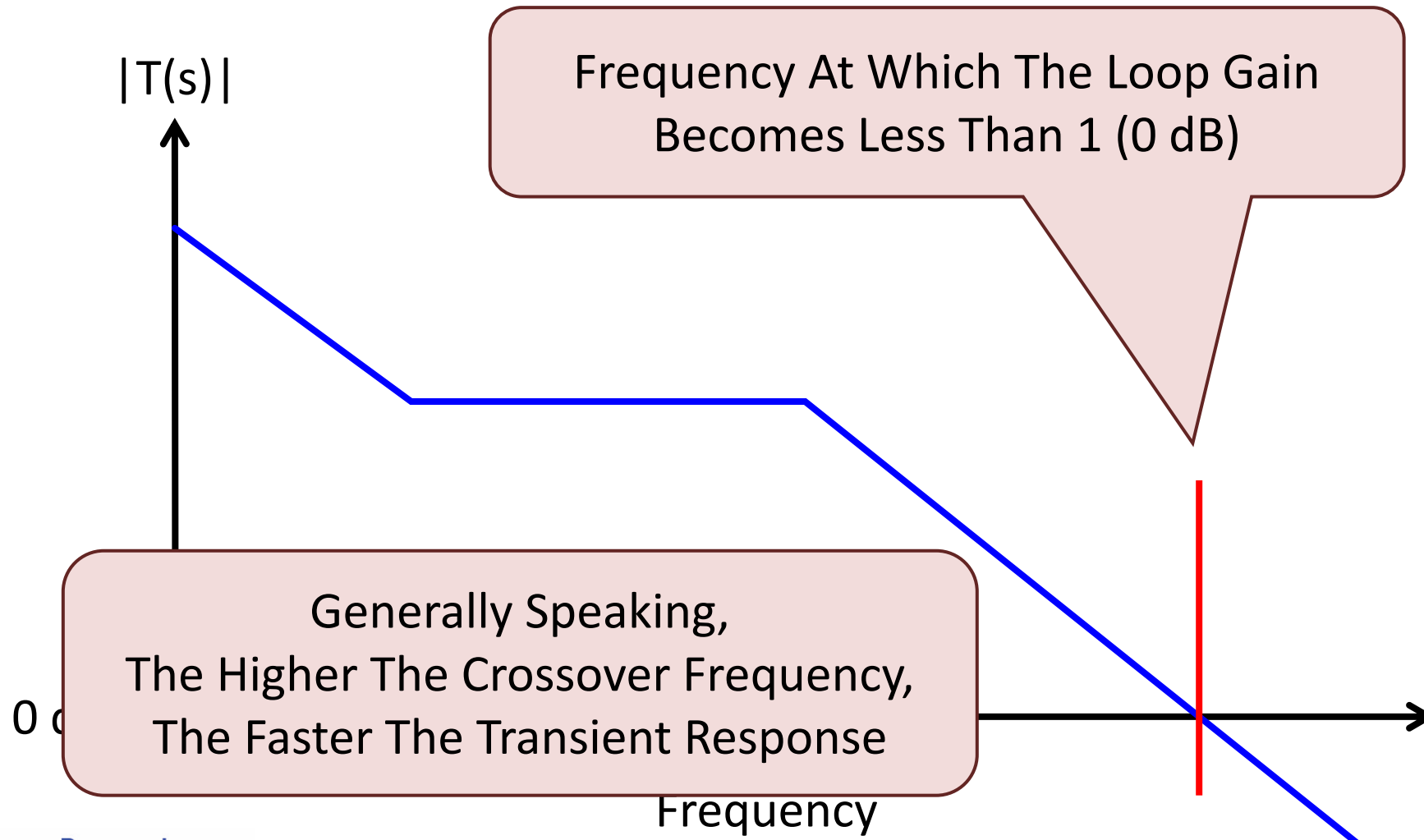


Response Time Vs. Bandwidth

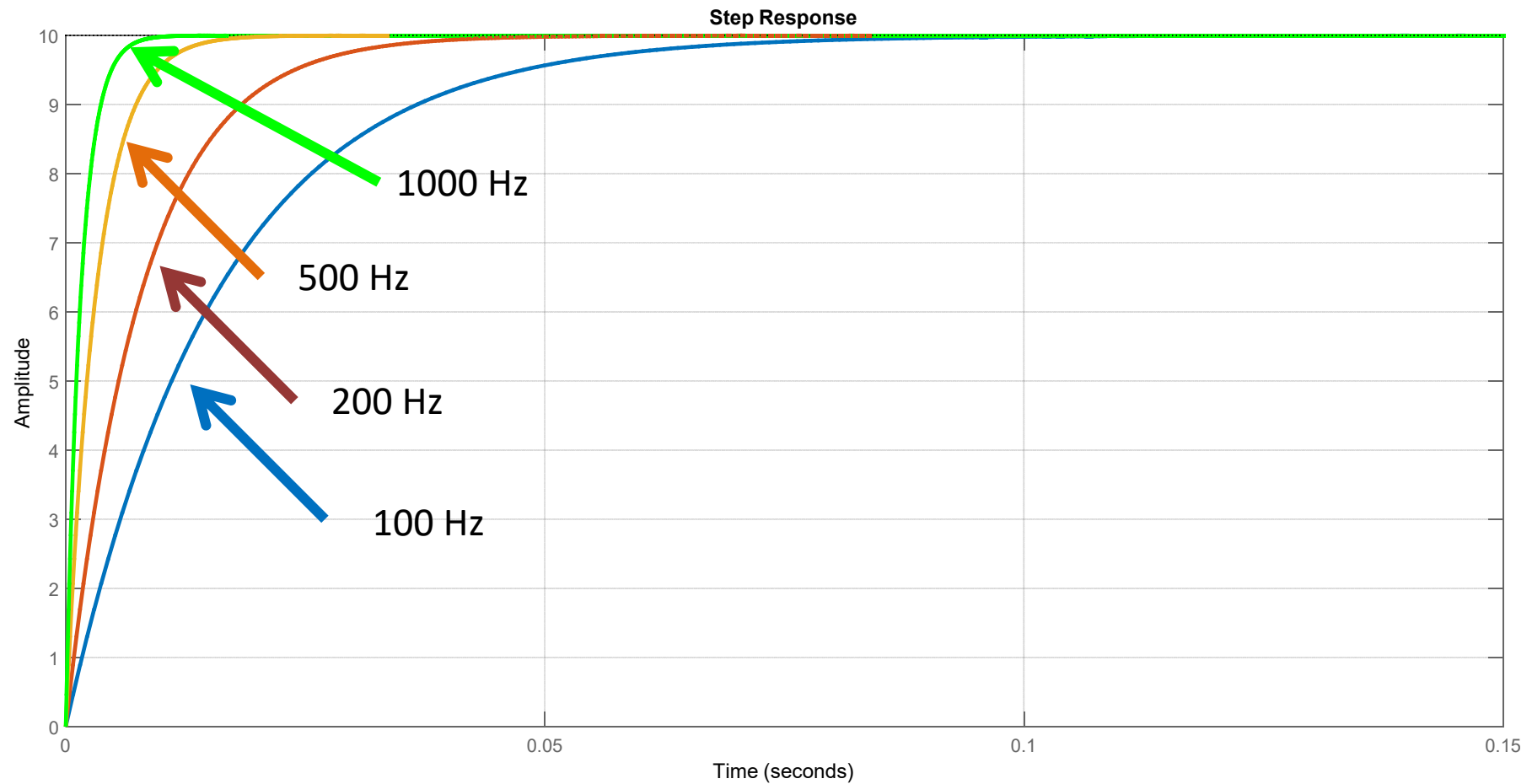


Loop Phase

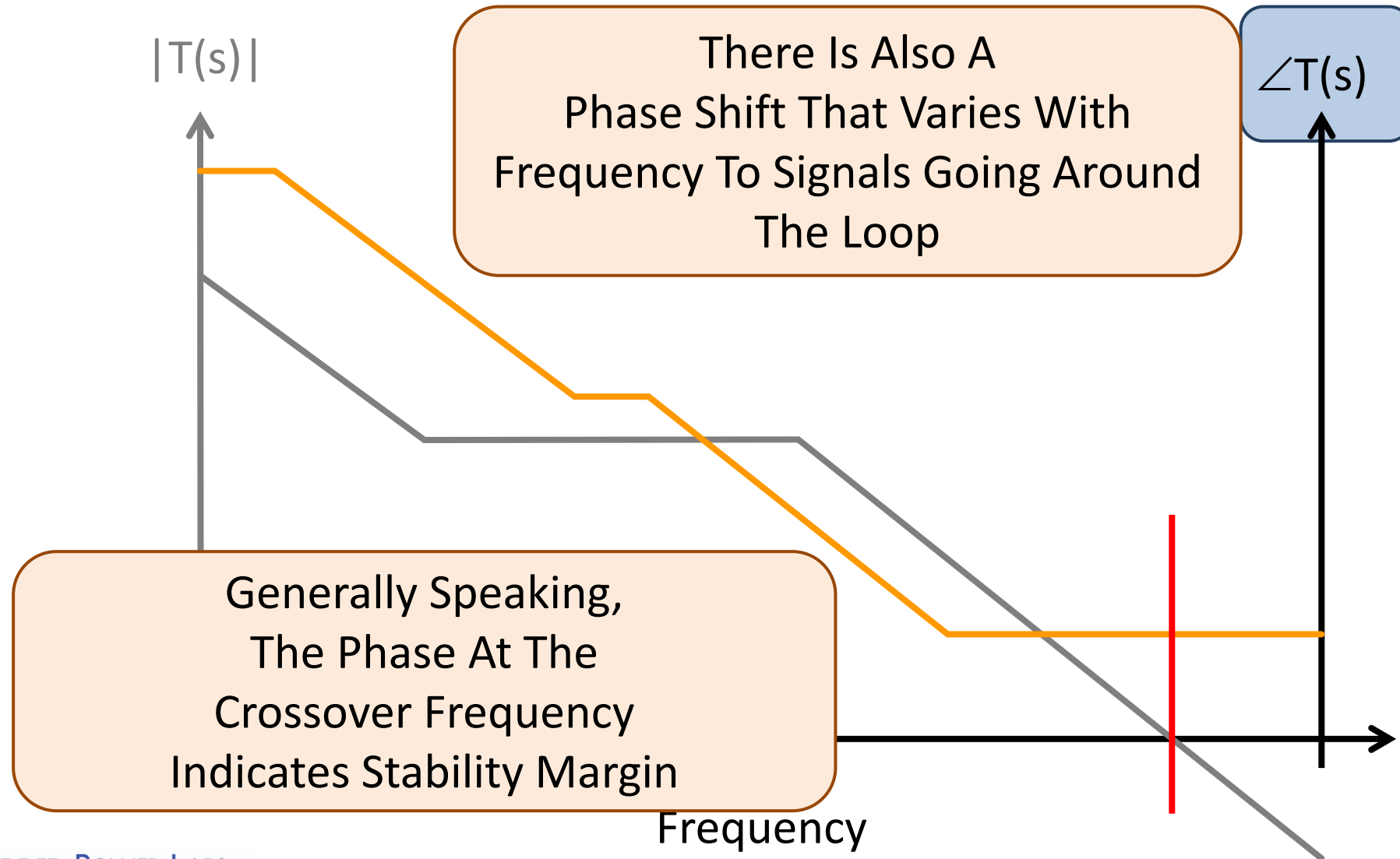

Stability

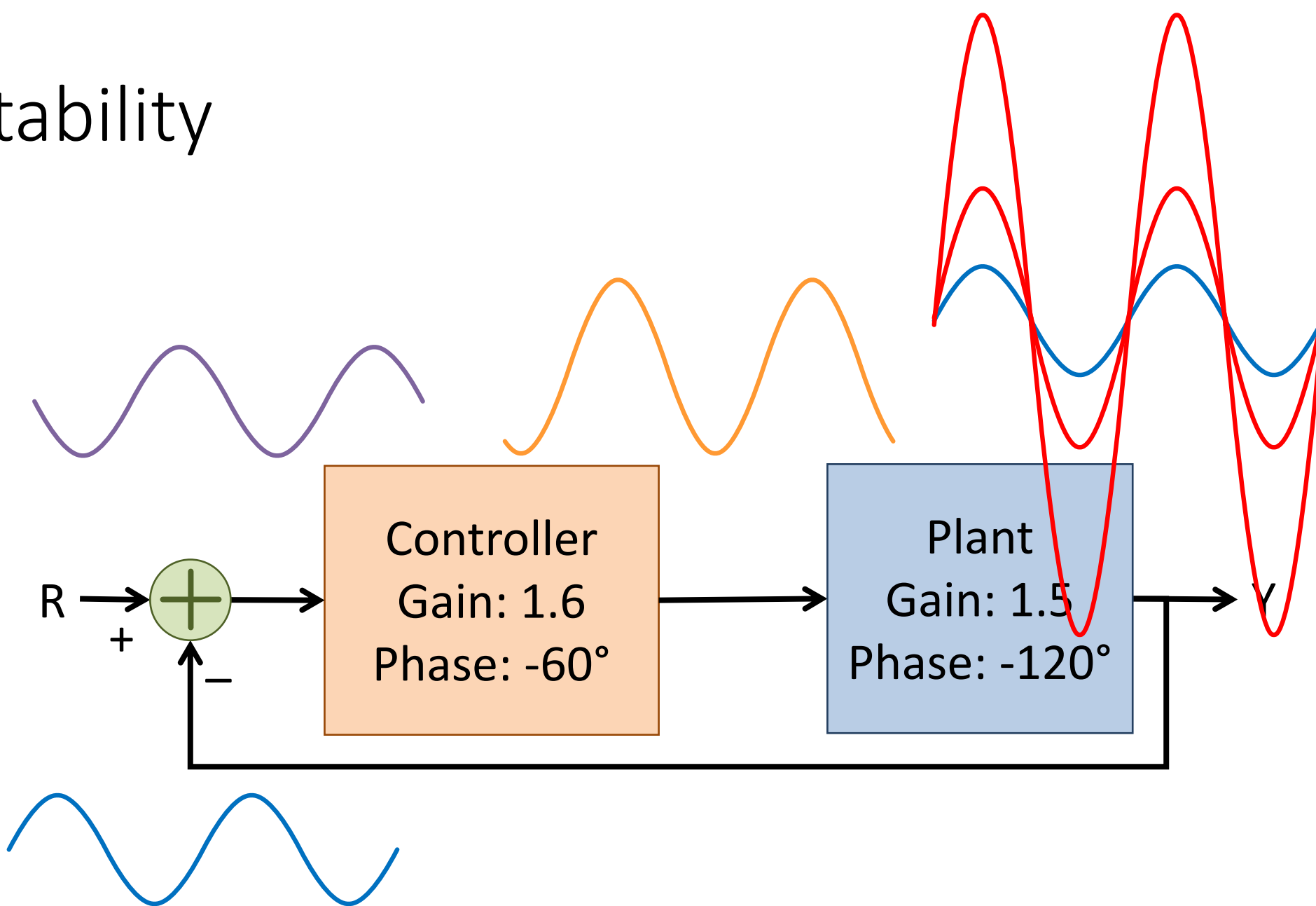


Stability

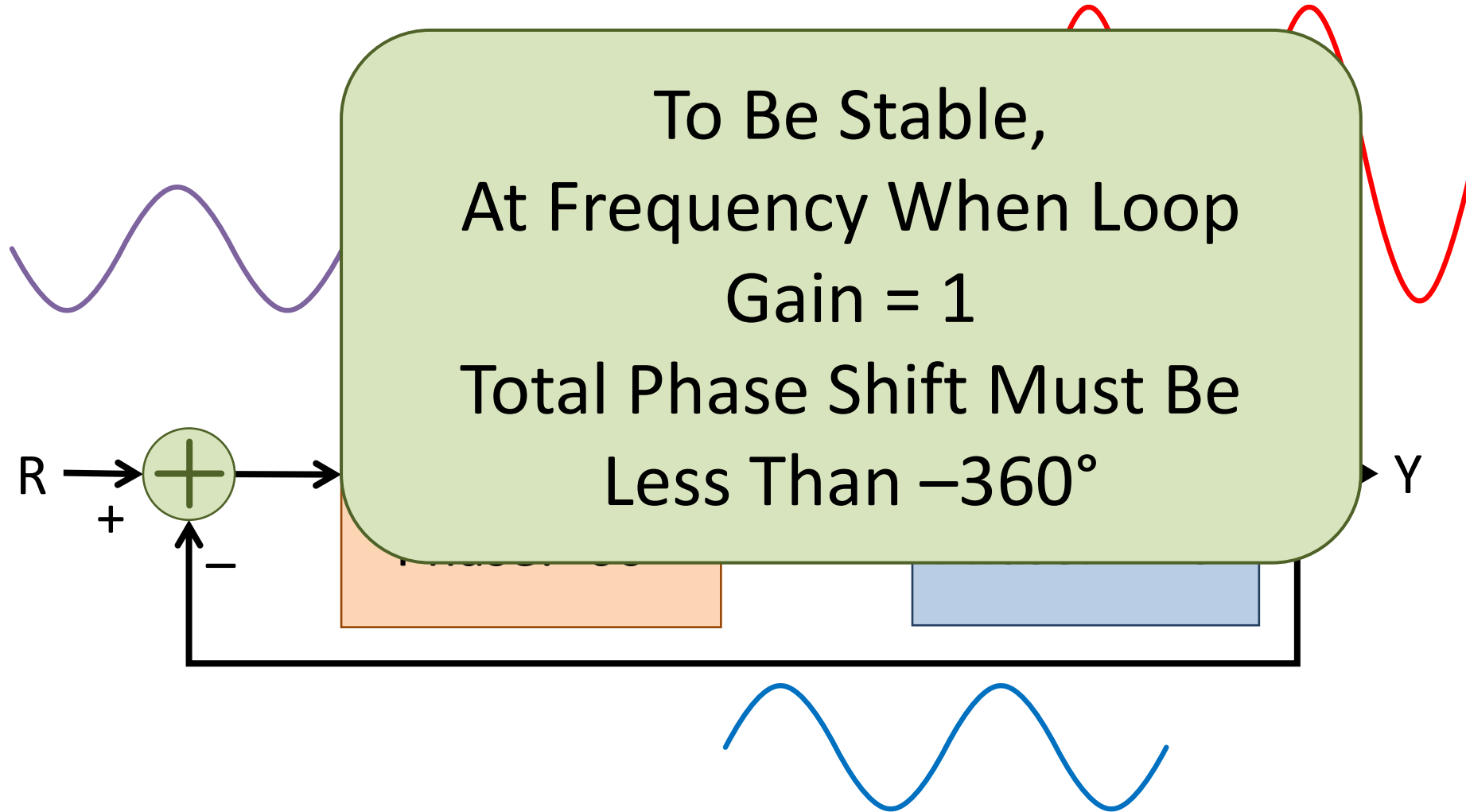


Stability

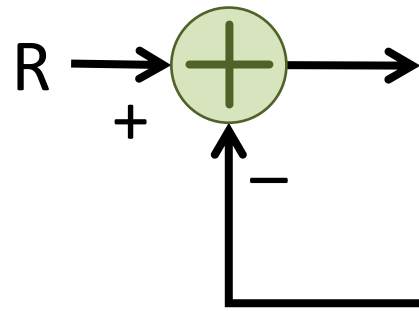Note: Inverting Error Amplifier
Phase Shift Equals -180°




So Phase Shift
In The Rest Of The Loop
Must Be Less Than -180°

Step Response vs. Phase Margin

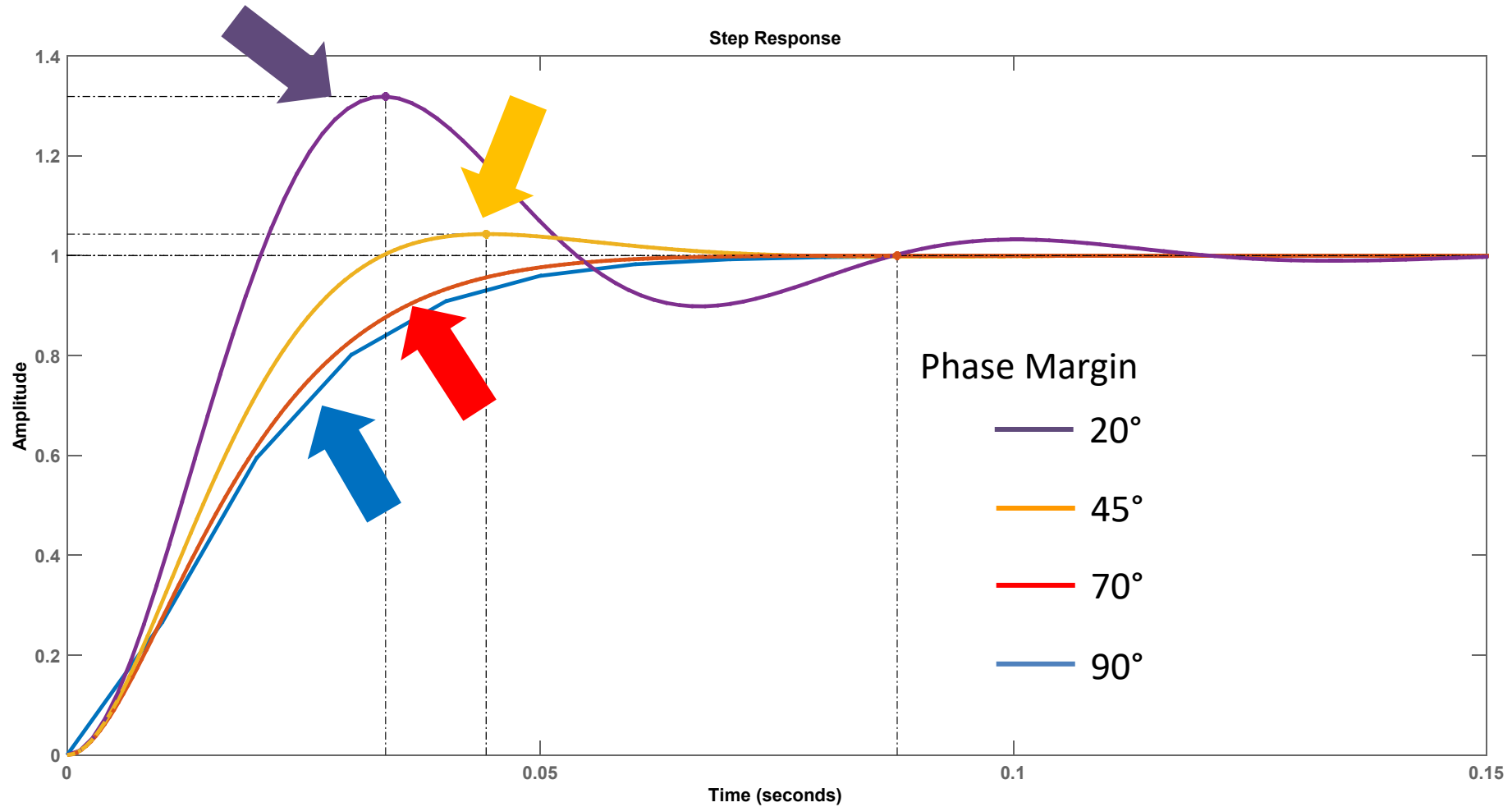


Stability vs. Phase Margin

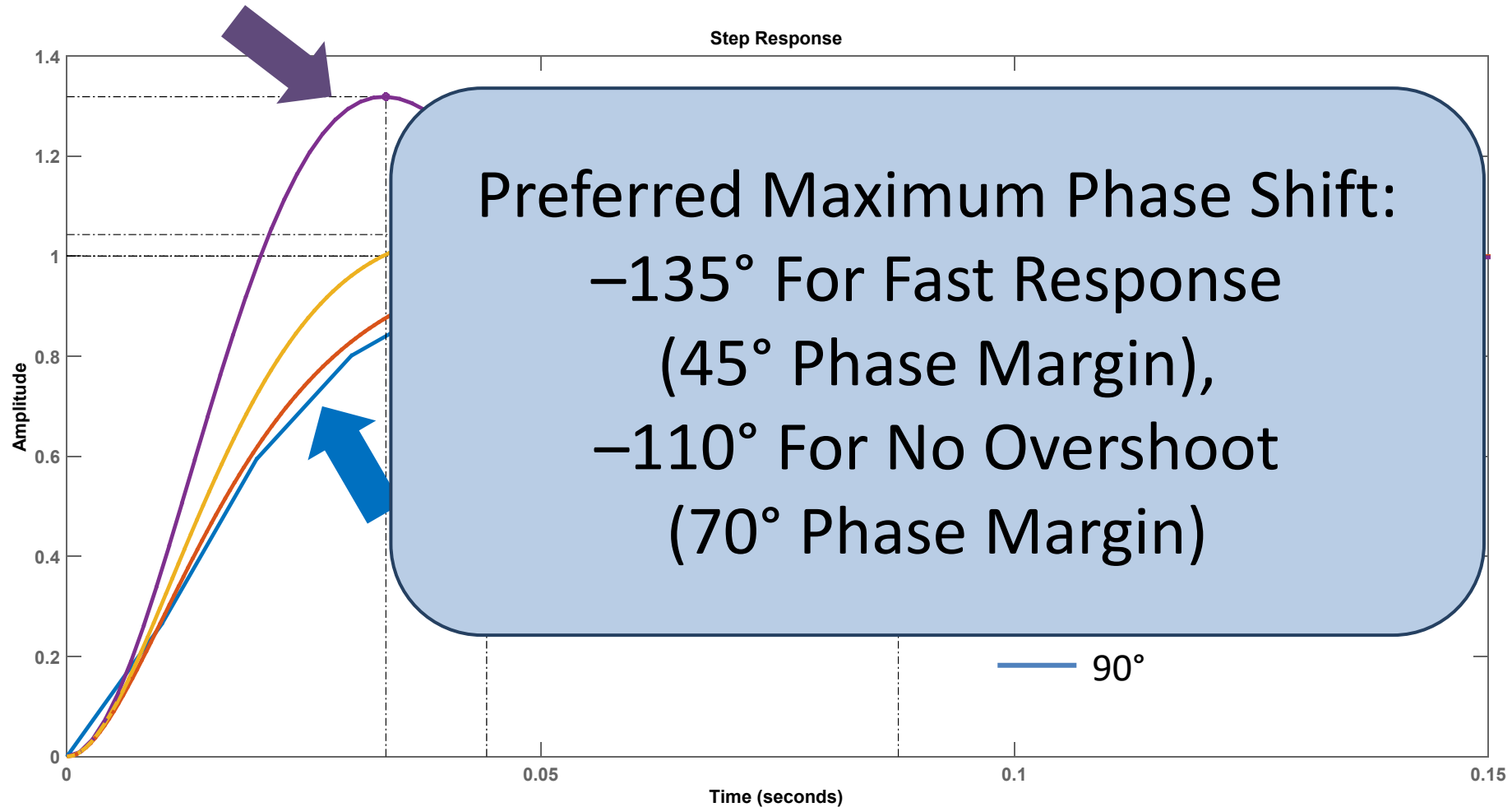


Buck Converter With Feedback Control

Buck Converter With Feedback

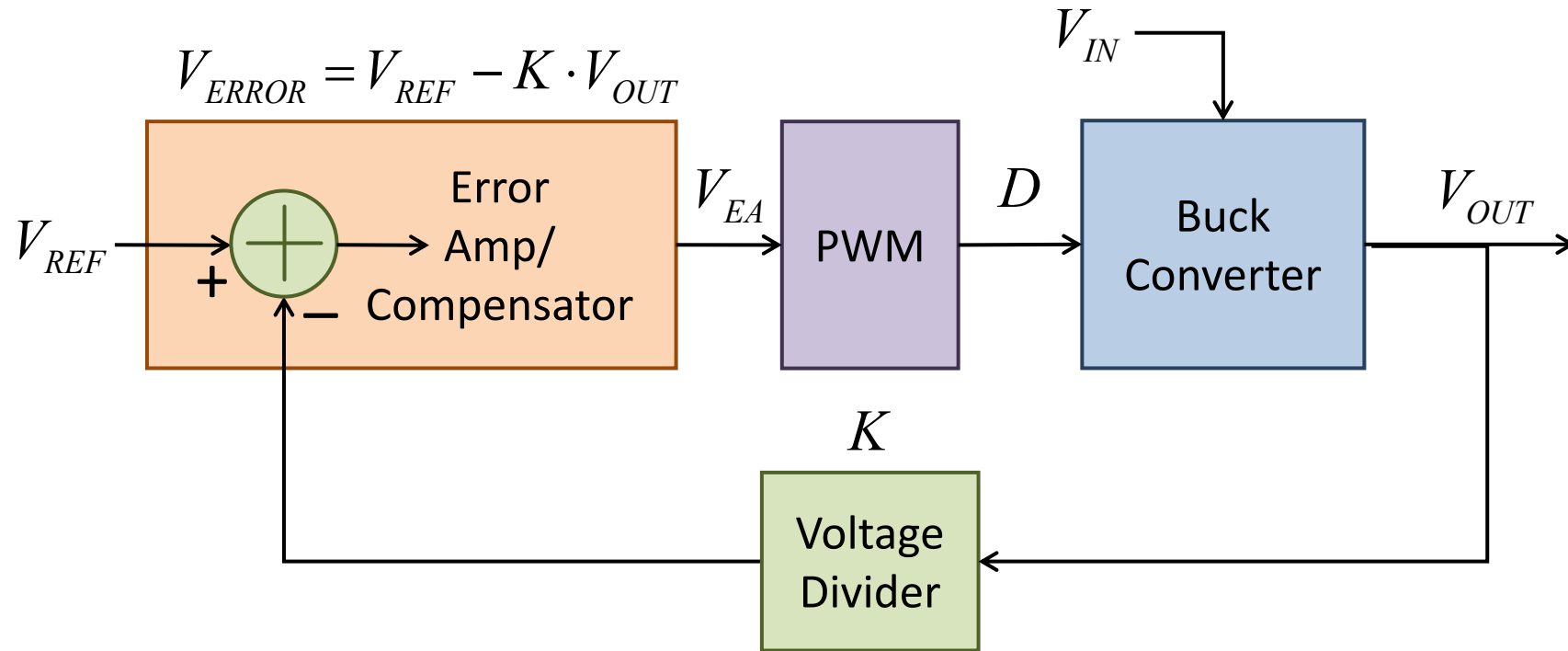

Loop Gain $T(s)$

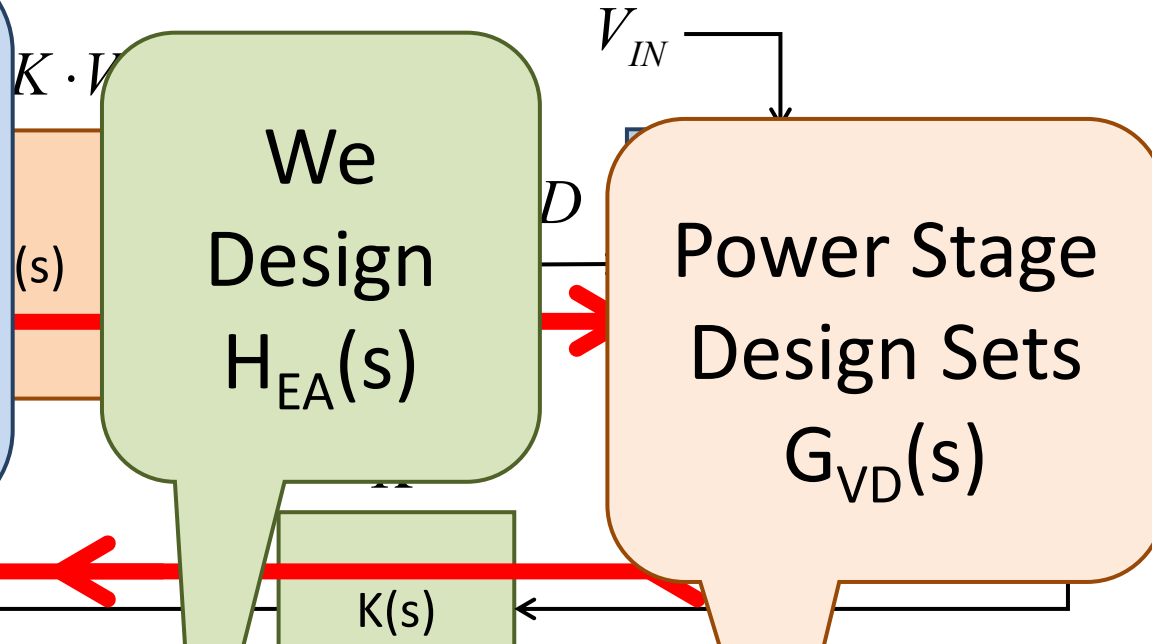So That $T(s)$
Gives Desired
Performance
And Stability



Loop Gain

$$T(s) = K \cdot H_{EA}(s) \cdot G_{PWM} \cdot G_{VD}(s)$$


Compensator Design: Plan Of Attack

- Solve For $H_{EA}(s)$

$$T(s) = K \cdot H_{EA}(s) \cdot G_{PWM} \cdot G_{VD}(s)$$



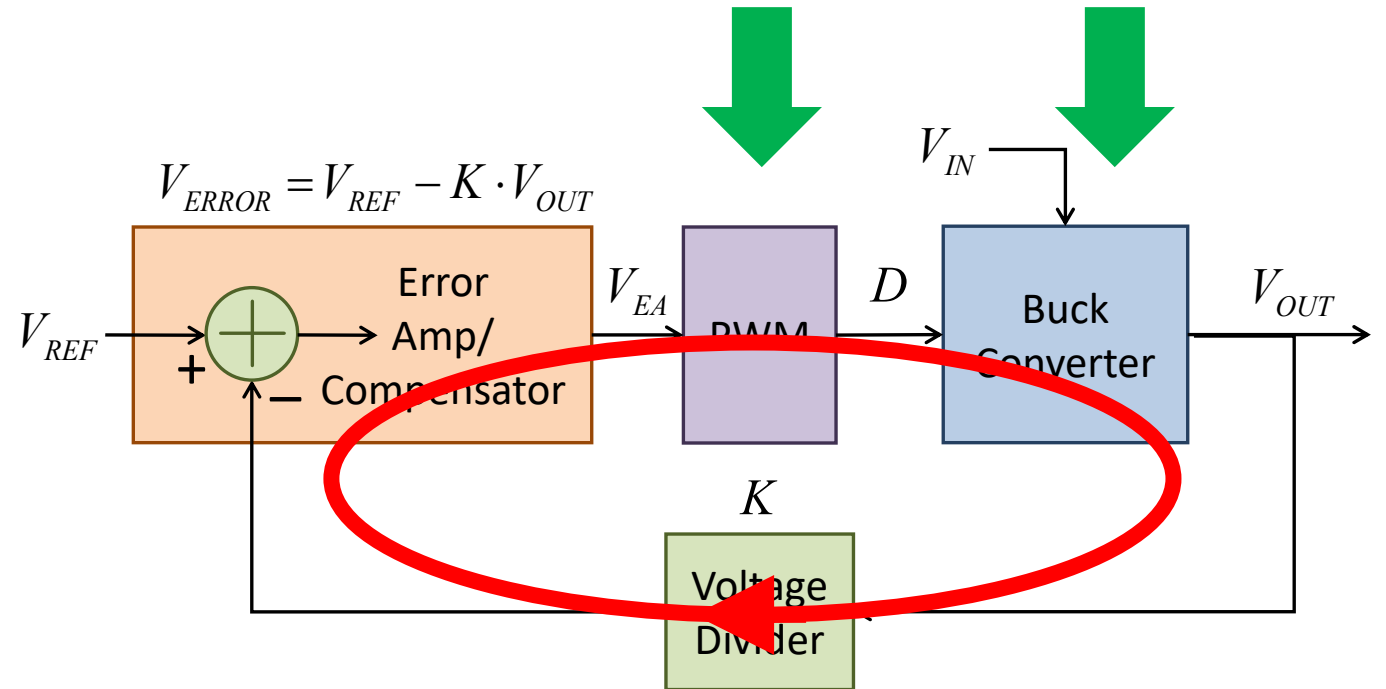
$$H_{EA}(s) = \frac{T(s)}{K \cdot G_{PWM} \cdot G_{VD}(s)}$$




Choose $T(s)$


Loop Gain $T(s)$

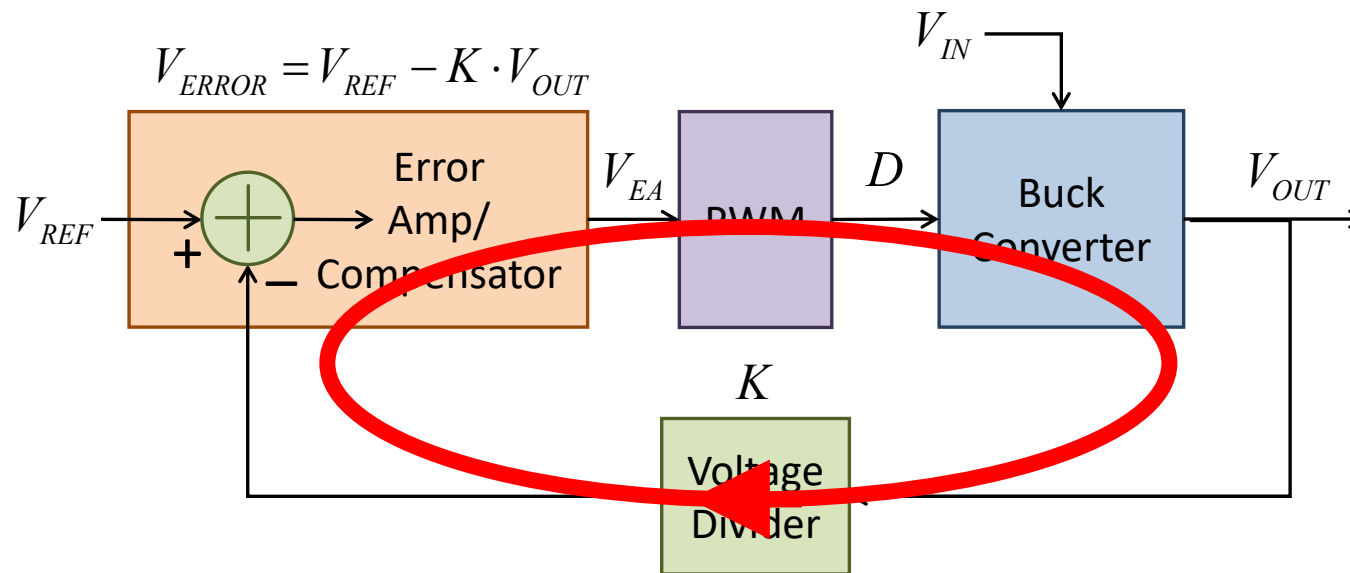

Ideal $T(s)$: Simple Integrator?

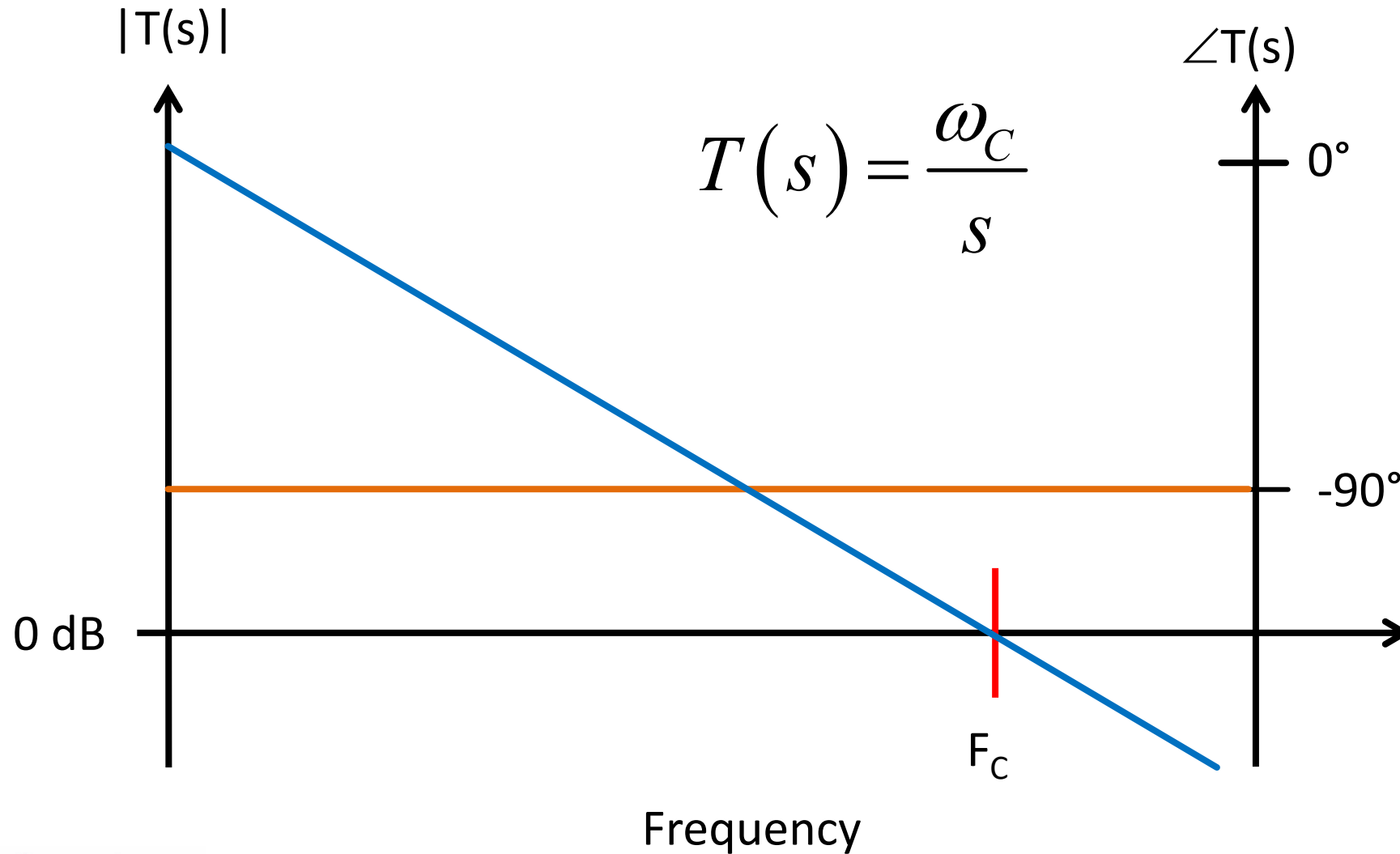

Ideal T(s): Simple Integrator?

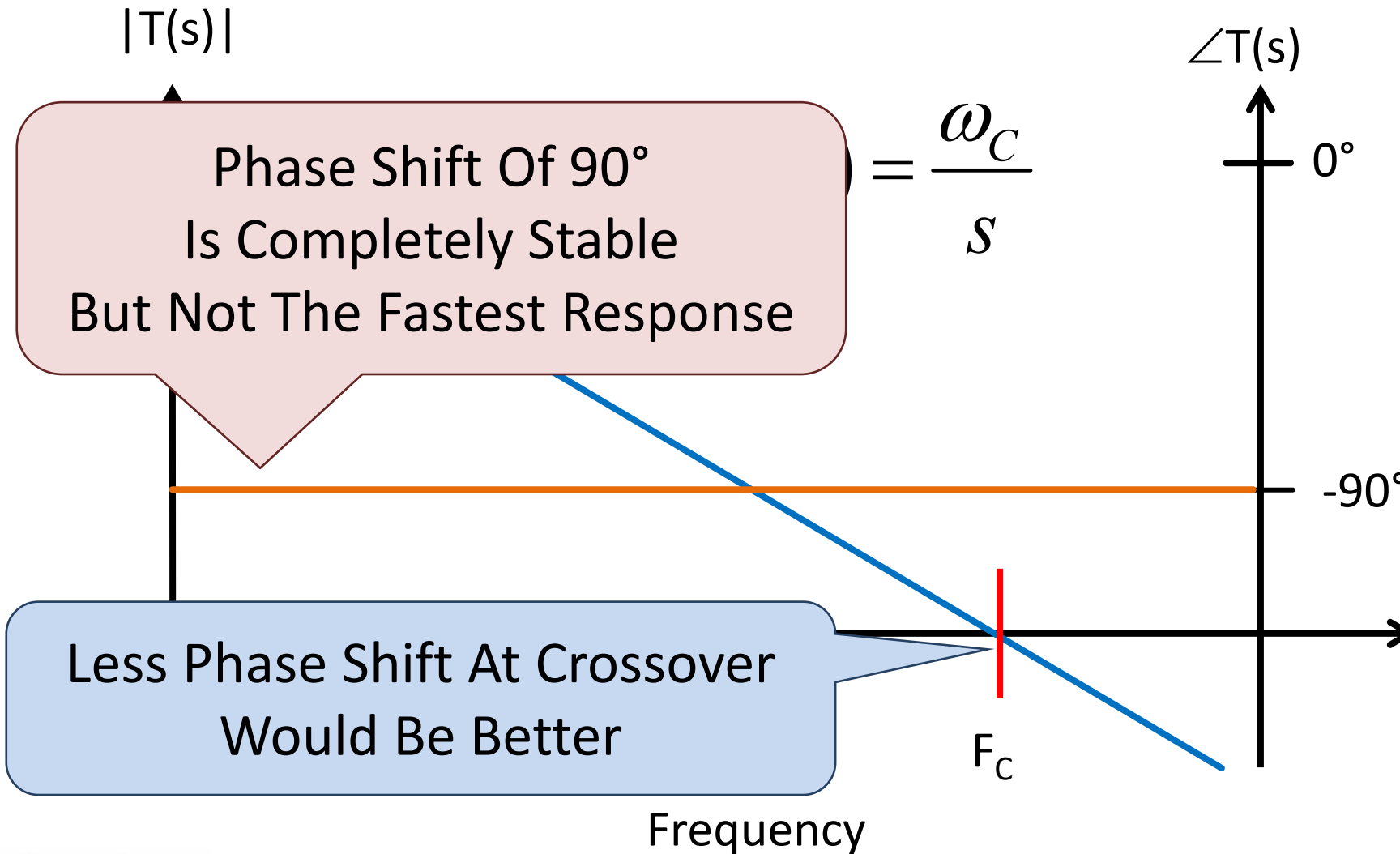

Better $T(s)$

$|T(s)|$

$\angle T(s)$

0 dB

0°

-45°

-90°

-110°

-135°

-180°


Phase Margin
= 70°

F_C

F_{HFP}

Frequency
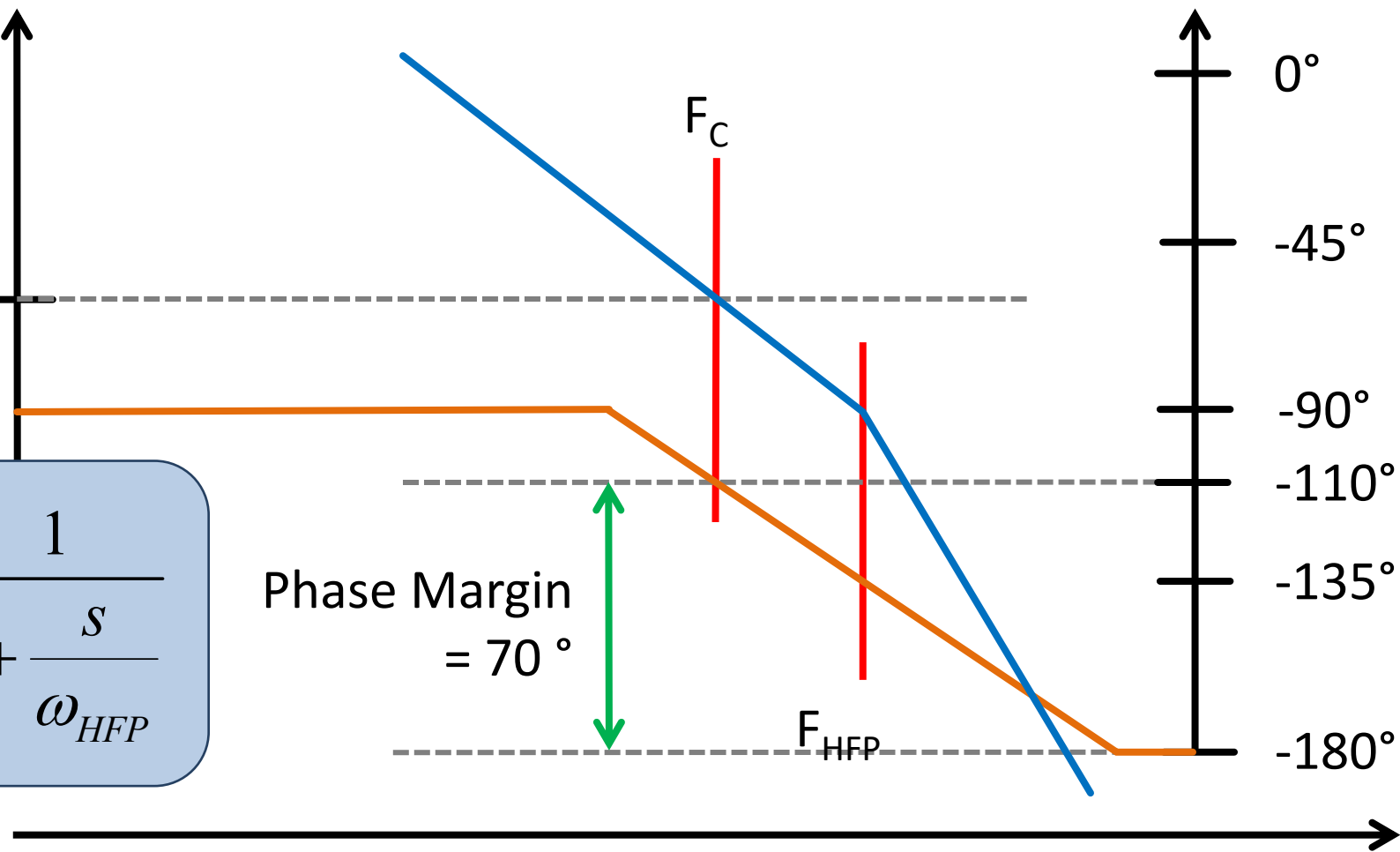
$$T(s) = \frac{\omega_0}{s} \cdot \frac{1}{1 + \frac{s}{\omega_{HFP}}}$$



Better T(s)

$|T(s)|$

Adjust ω_0 Such That
Loop Gain = 1
At Crossover Frequency
 $|T(j \cdot \omega_C)| = 1$

$$T(s) = \frac{\omega_0}{s} \cdot \frac{1}{1 + \frac{s}{\omega_{HFP}}}$$

Phase Margin
= 70°

$$\omega_0 = \omega_C \cdot \sqrt{1 + \left(\frac{\omega_C}{\omega_{HFP}}\right)^2}$$

$\angle T(s)$

0°

-45°


-90°

-135°

-180°


Frequency

Better T(s)

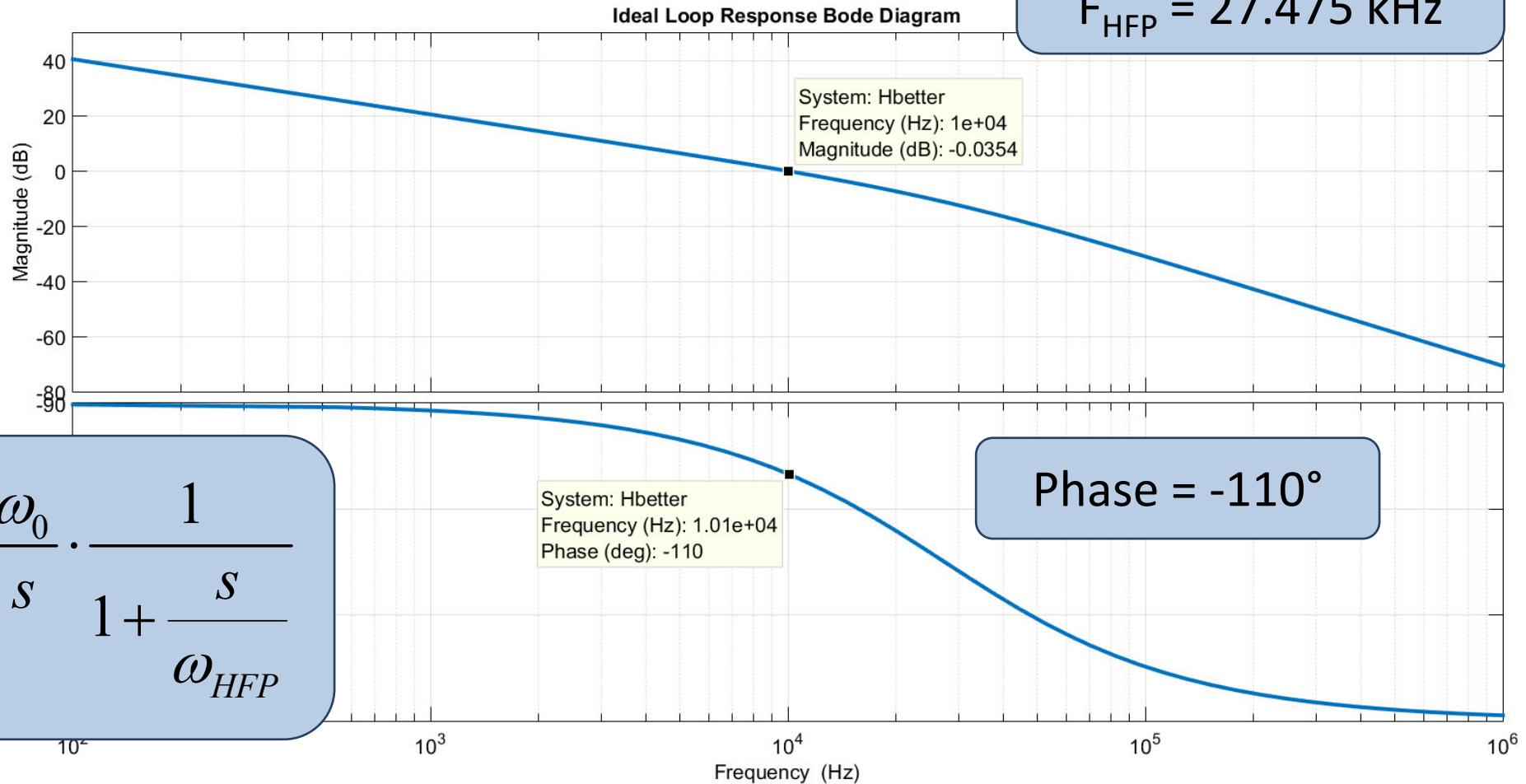

$$T(s) = \frac{\omega_0}{s} \cdot \frac{1}{1 + \frac{s}{\omega_{HFP}}}$$

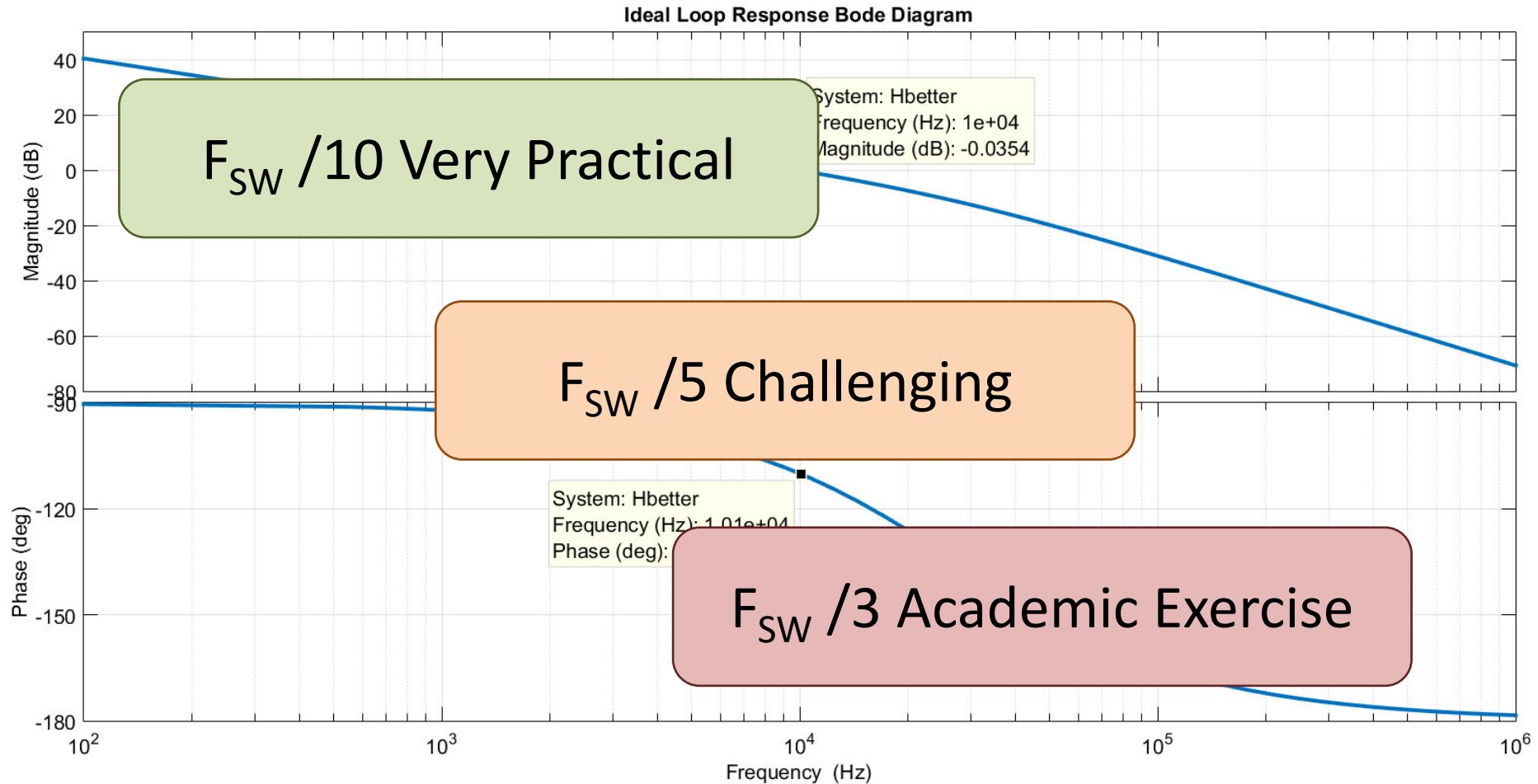
Better T(s): Practical Crossover Frequency



Small Signal Model Of The Pulse Width Modulator


$$G_{\text{PWM}}$$

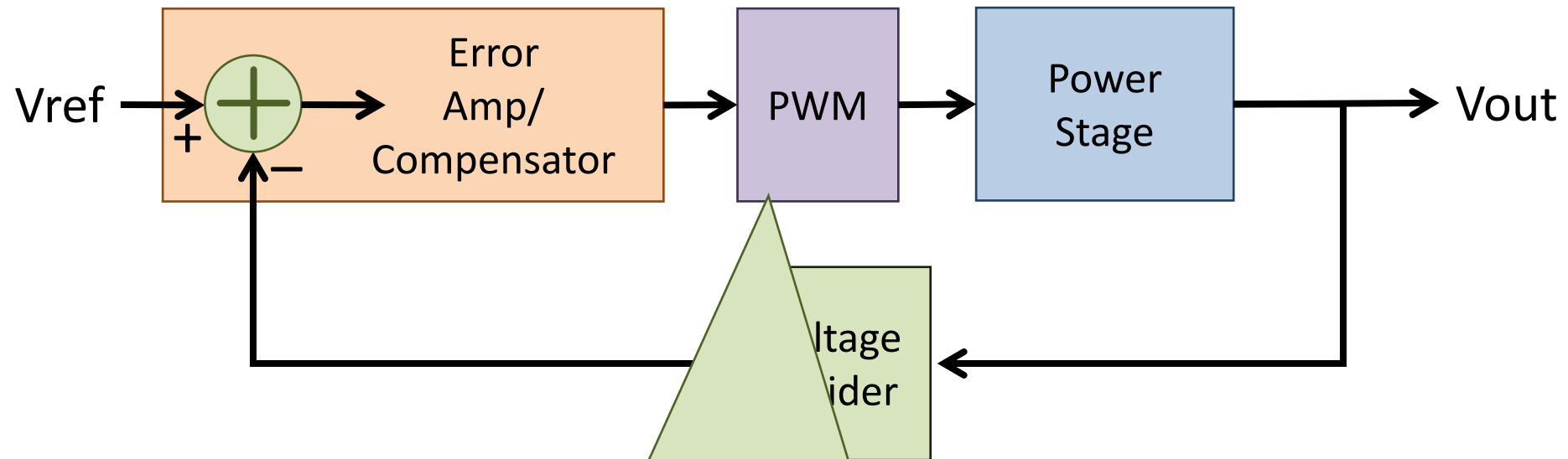Small Signal Model Of Pulse-Width Modulator




We Need To Calculate The Gain Of the Modulator: $G_{PWM}(s)$



Pulse Width Modulator

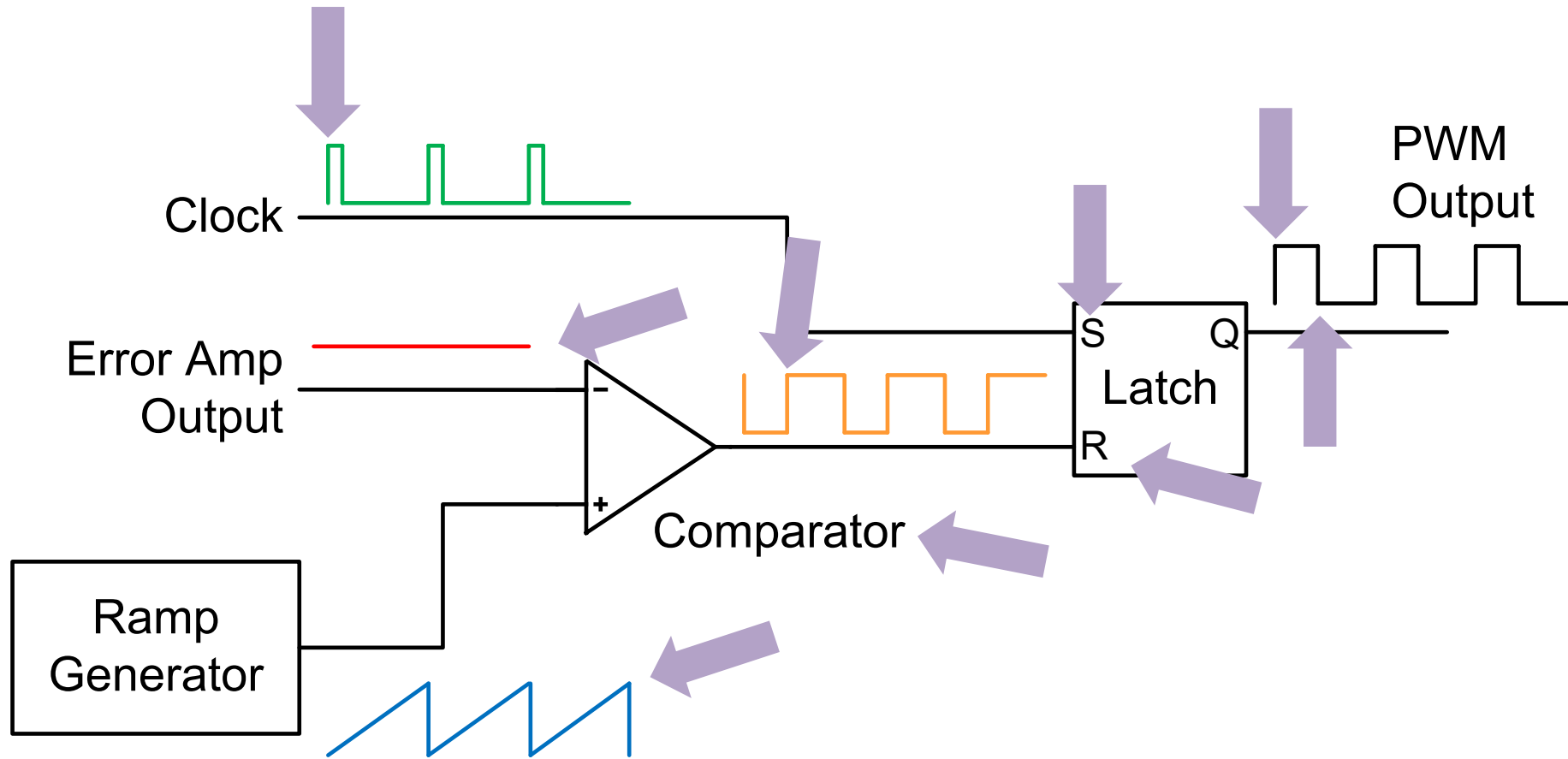


Analog Pulse Width Modulator

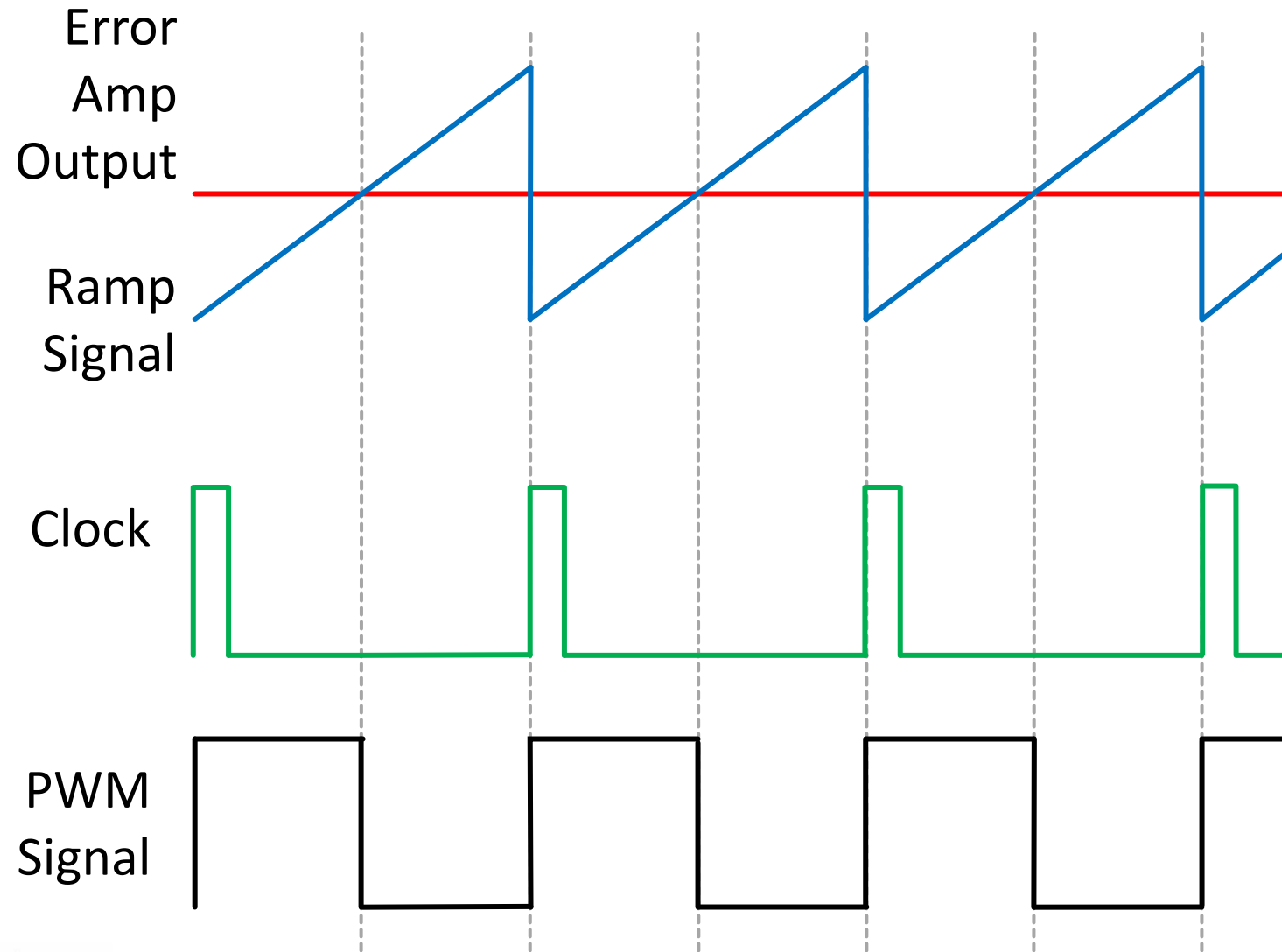


Video Lab 9: Trailing Edge PWM

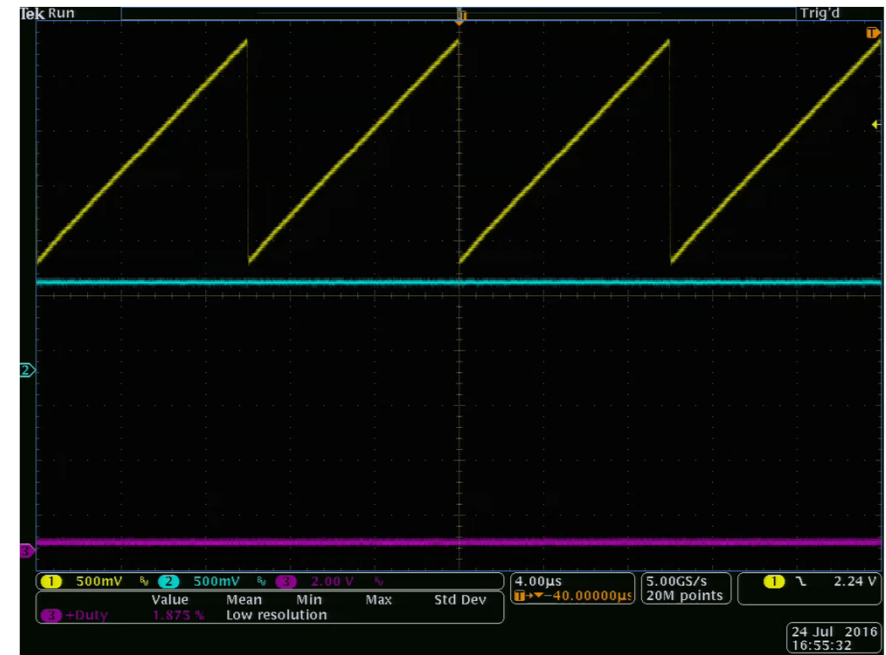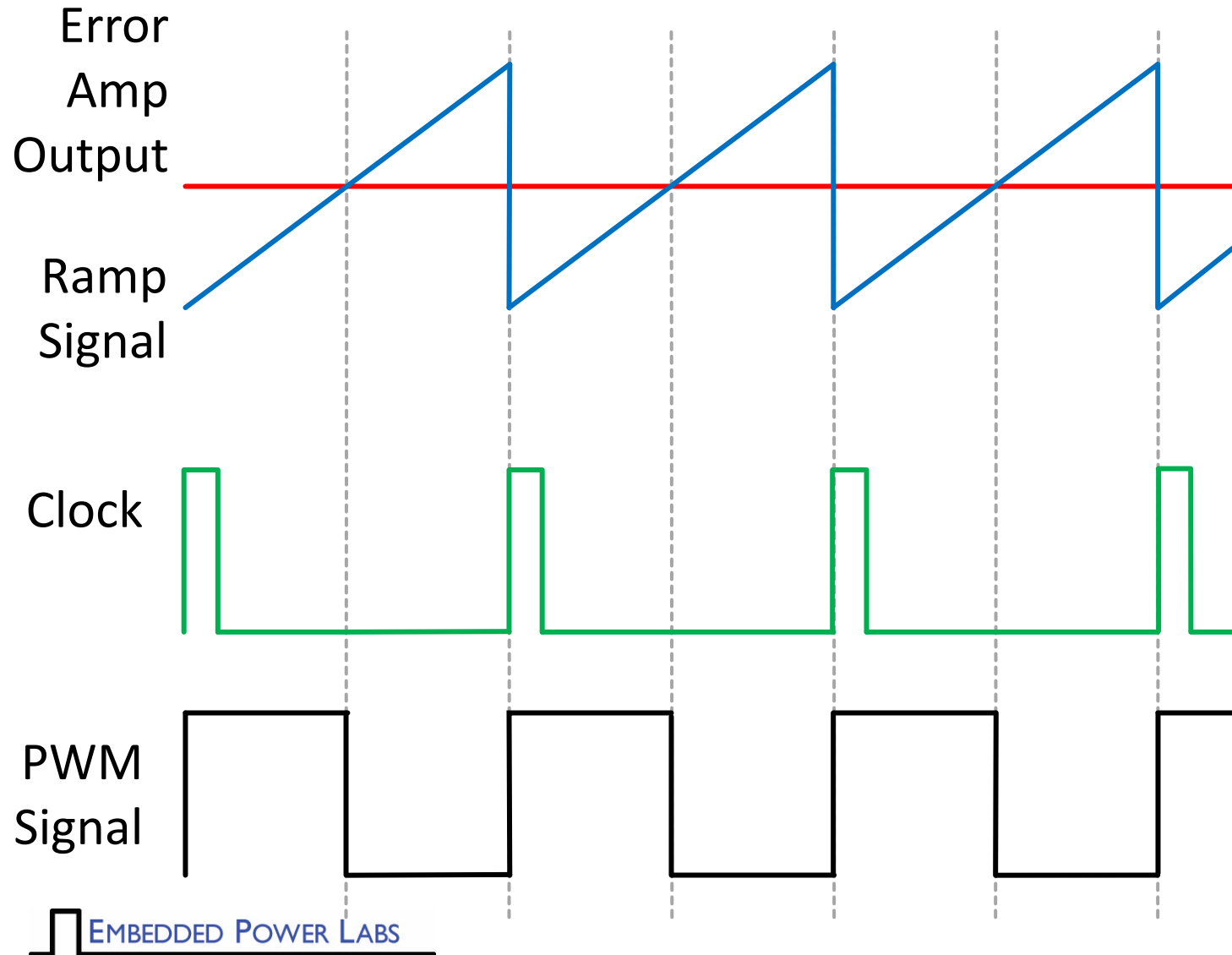

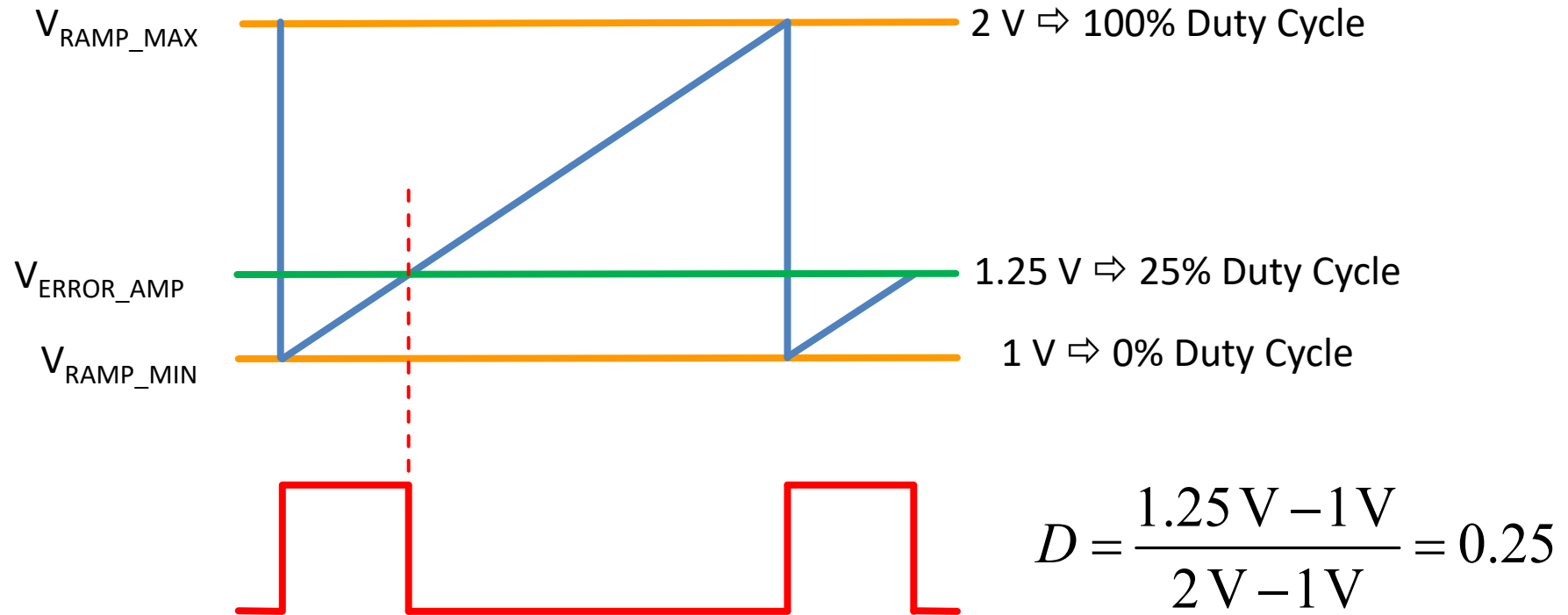Small Signal Model Of Pulse-Width Modulator



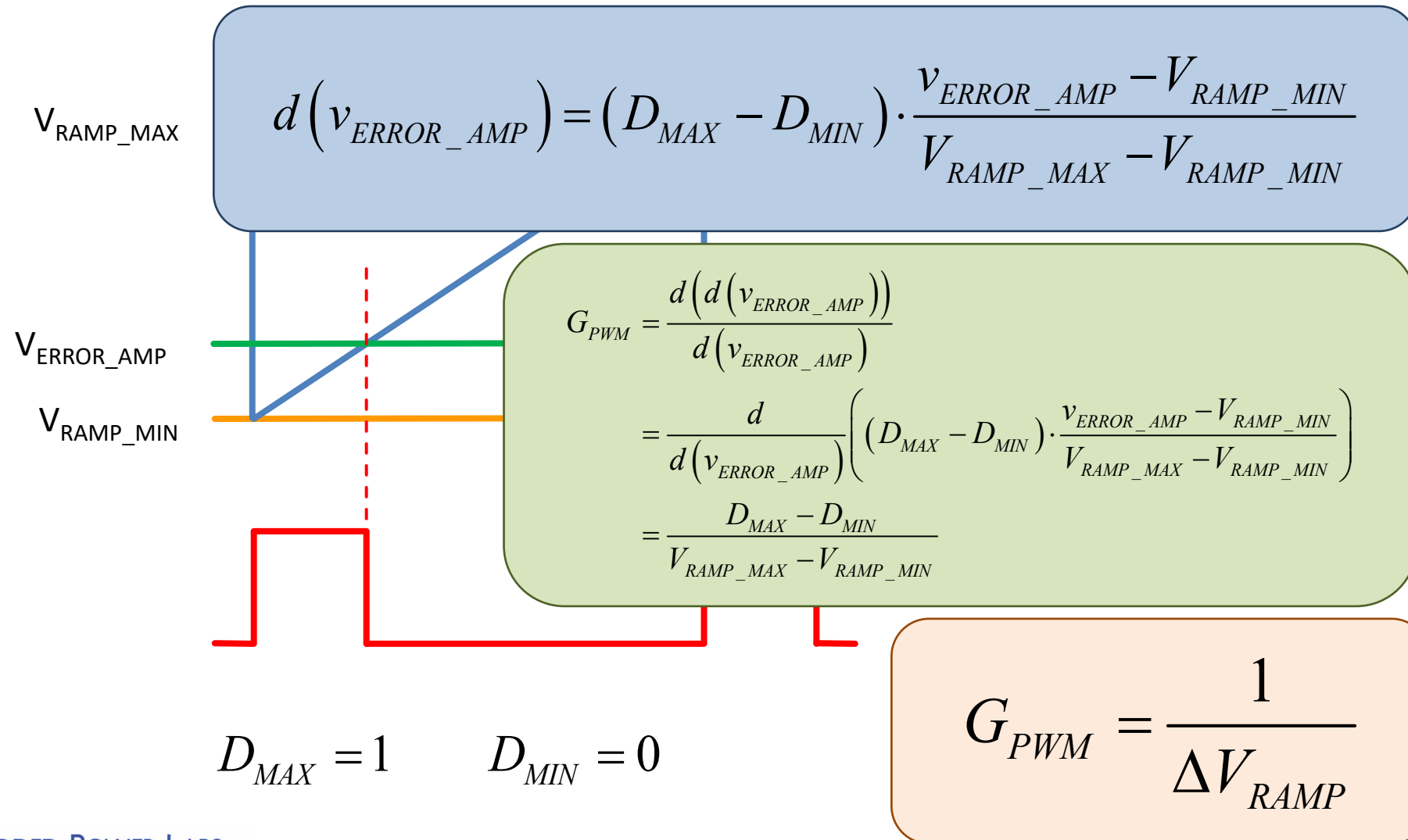
Small Signal Model Of Pulse-Width Modulator



Control-To-Output Transfer Function


$$G_{VD}$$

Buck Converter G_{VD}

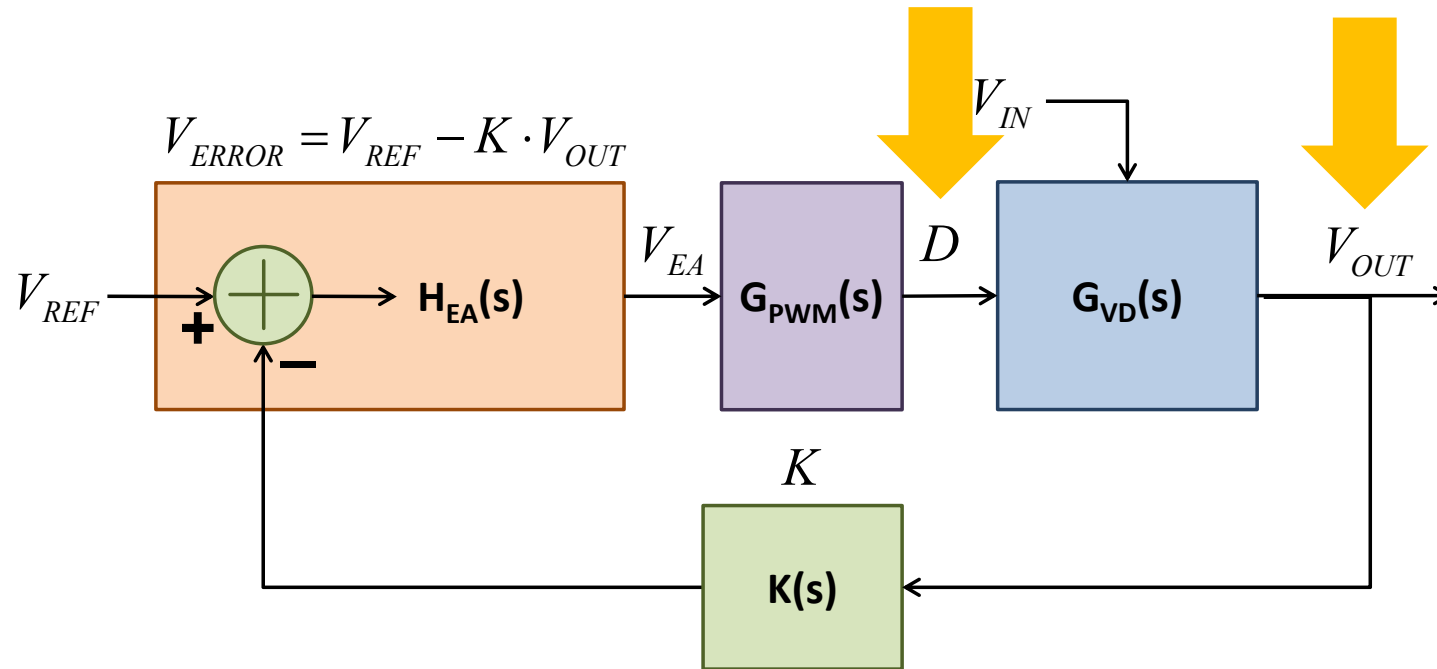

- Derivation Of Control-To-Output Transfer Functions Generally Not Trivial
 - See Additional Resources To Learn More

Buck Converter

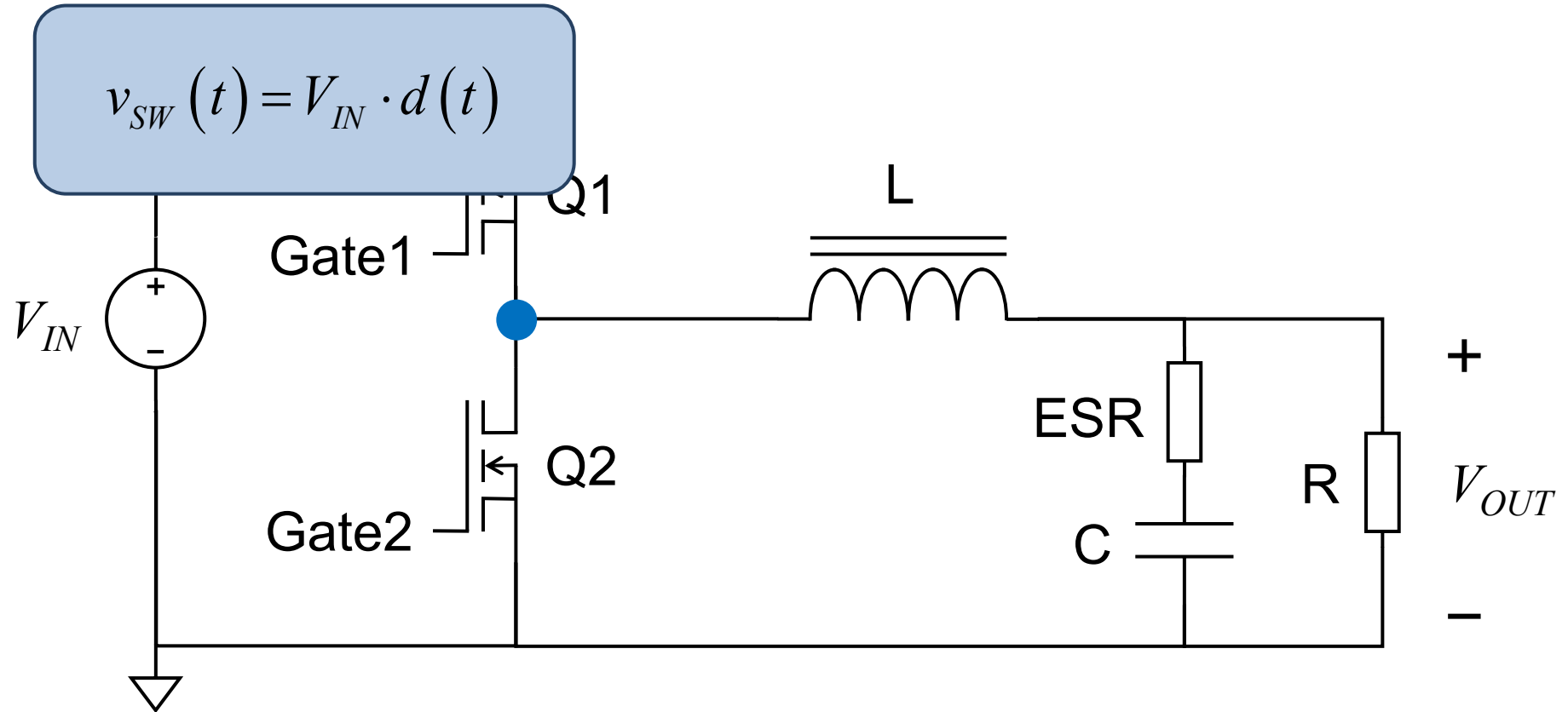


$$d(t) = D + \hat{d}(t)$$


$$\hat{d} \ll D$$

$$\omega \ll \omega_{SW}$$


Buck Converter

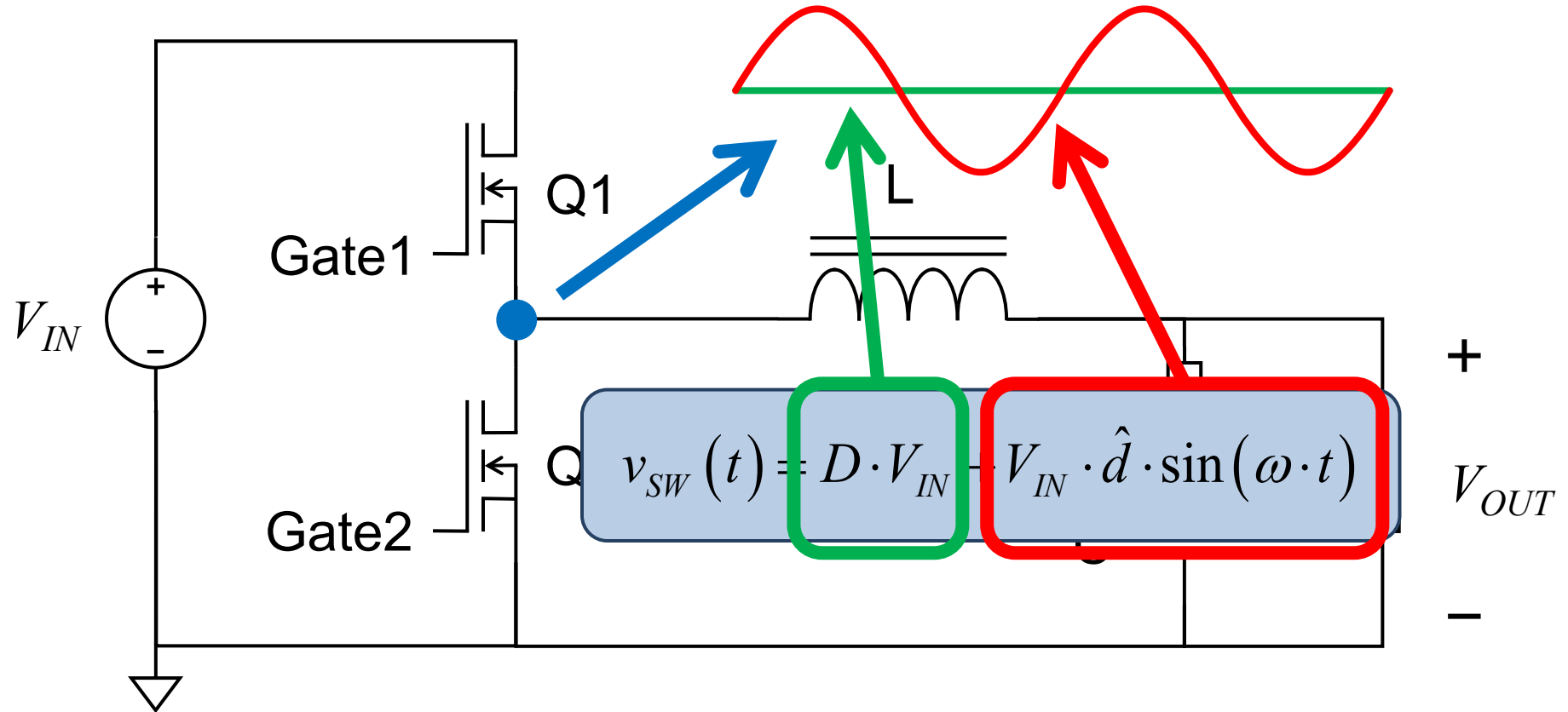


Buck Converter

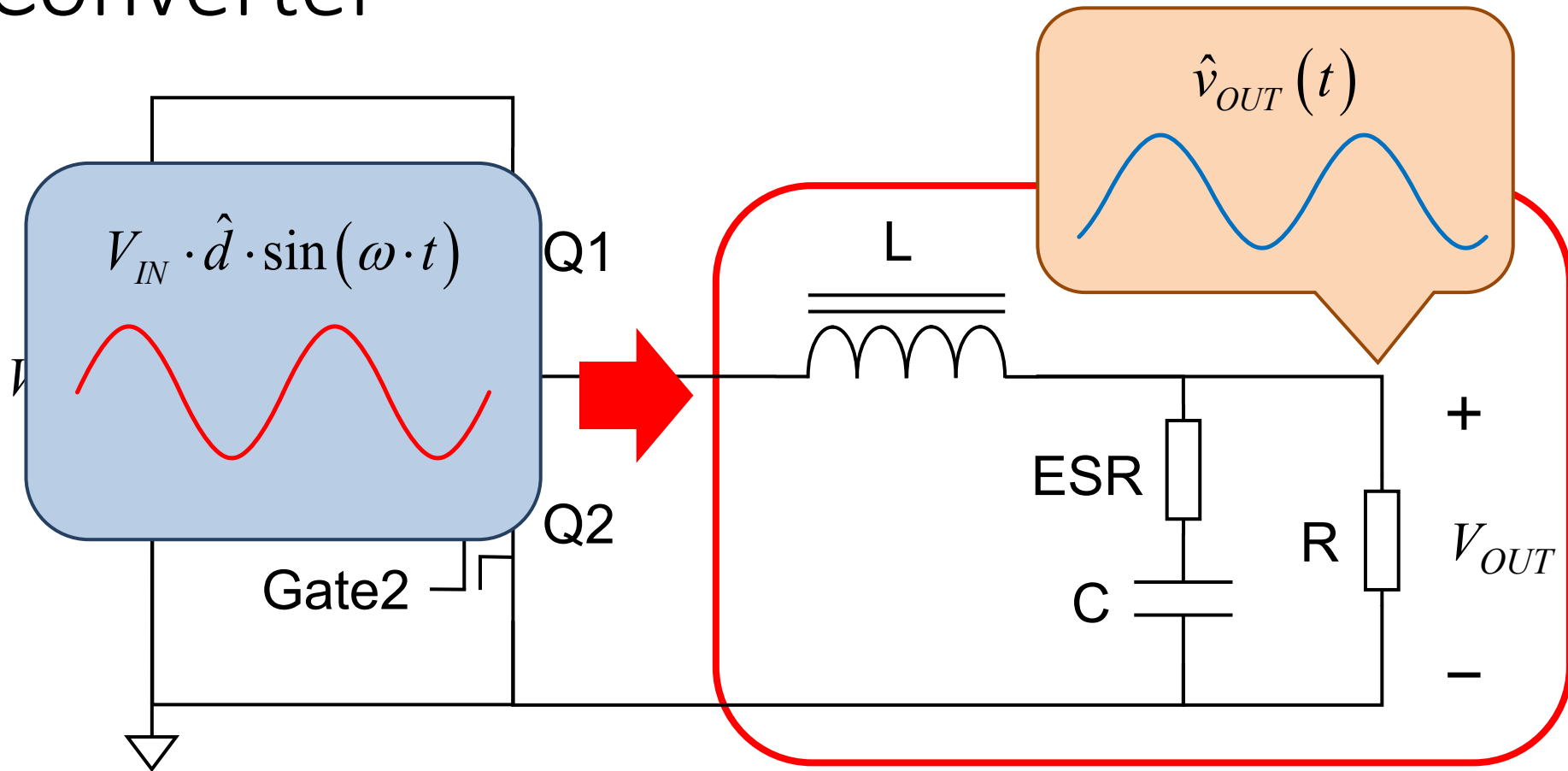

Buck Converter

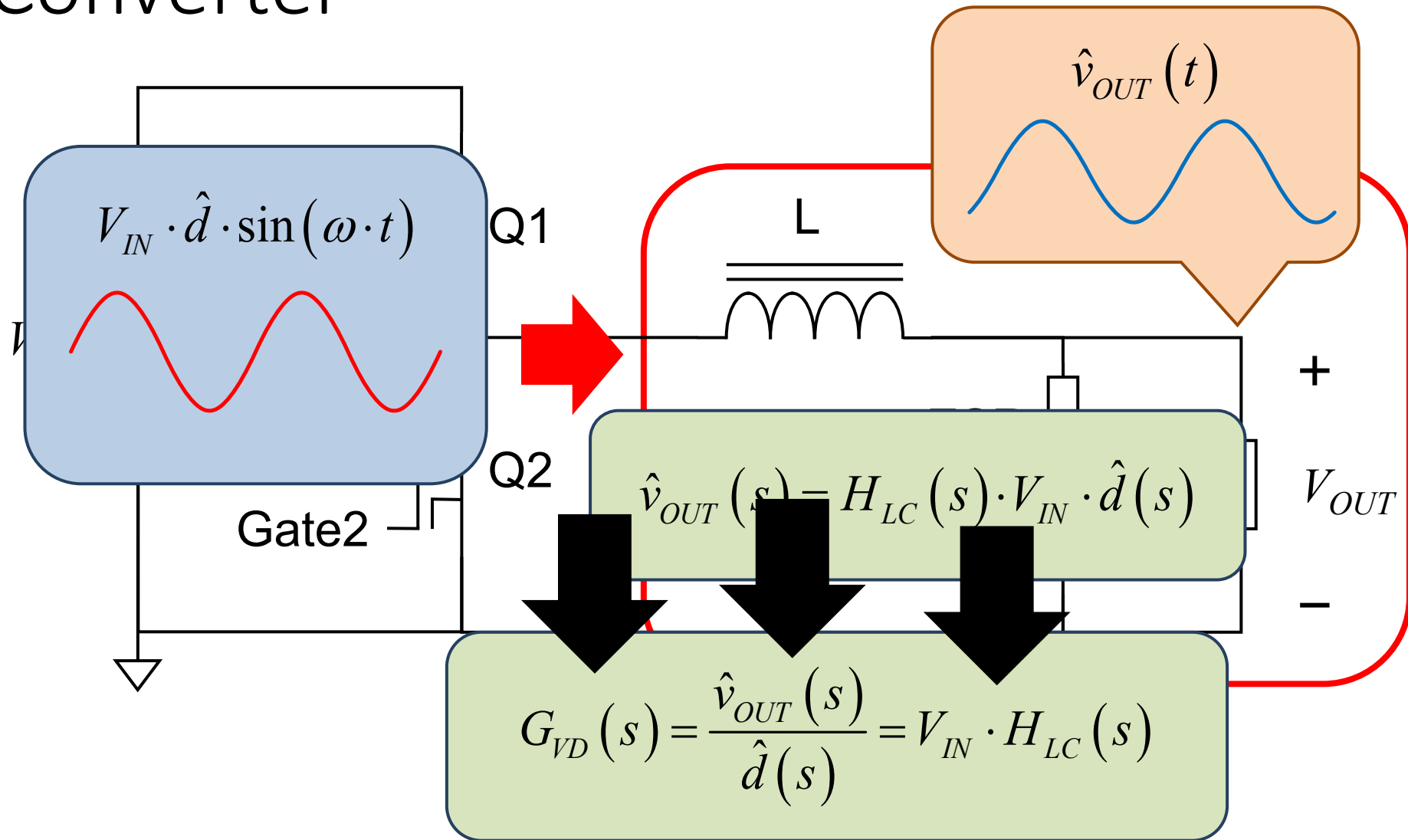

L-C Filter Transfer Function

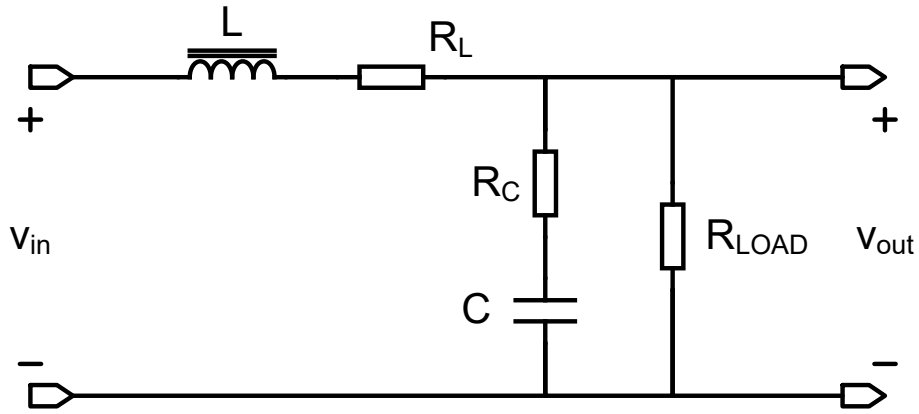

$$v_{out}(s) = \frac{R_{LOAD} \parallel \left(R_C + \frac{1}{s \cdot C} \right)}{s \cdot L + R_L + R_{LOAD} \parallel \left(R_C + \frac{1}{s \cdot C} \right)} \cdot v_{in}(s)$$


$$R_C \ll R_{LOAD} \quad R_L \ll R_{LOAD}$$

ESR Zero

$$H_{LC}(s) \approx \frac{1 + s \cdot R_C \cdot C}{1 + \frac{L}{R_{LOAD}} \cdot s + L \cdot C \cdot s^2}$$

LC Double Pole

L-C Filter Transfer Function

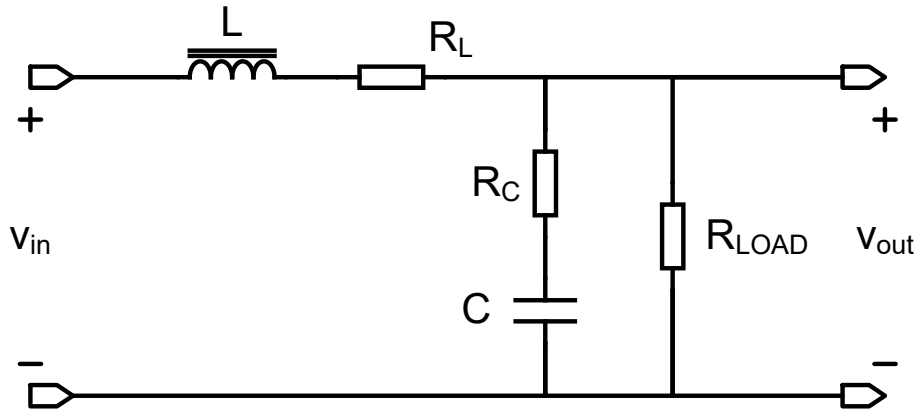

$$v_{out}(s) = \frac{R_{LOAD} \parallel \left(R_C + \frac{1}{s \cdot C} \right)}{s \cdot L + R_L + R_{LOAD} \parallel \left(R_C + \frac{1}{s \cdot C} \right)} \cdot v_{in}(s)$$

$$R_C \ll R_{LOAD} \quad R_L \ll R_{LOAD}$$

$$H_{LC}(s) \approx \frac{1 + \frac{s}{\omega_Z}}{1 + \frac{\omega_P \cdot L}{R_{LOAD}} \cdot \left(\frac{s}{\omega_P} \right) + \left(\frac{s}{\omega_P} \right)^2}$$



$$H_{LC}(s) \approx \frac{1 + s \cdot R_C \cdot C}{1 + \frac{L}{R_{LOAD}} \cdot s + L \cdot C \cdot s^2}$$


$$Q = \frac{R_{LOAD}}{\omega_P \cdot L}$$

$$= \frac{1 + \frac{s}{\omega_Z}}{1 + \frac{1}{Q} \cdot \left(\frac{s}{\omega_P} \right) + \left(\frac{s}{\omega_P} \right)^2}$$

$$\omega_Z = \frac{1}{R_C \cdot C}$$

$$\omega_P^2 = \frac{1}{L \cdot C}$$

Buck Converter $G_{VD}(s)$


$$G_{VD}(s) = V_{IN} \cdot H_{LC}(s) \approx V_{IN} \cdot \frac{1 + s \cdot R_C \cdot C}{1 + \frac{L}{R_{LOAD}} \cdot s + L \cdot C \cdot s^2}$$


$$= V_{IN} \cdot \frac{1 + \frac{s}{\omega_{Z_ESR}}}{1 + \frac{1}{Q} \cdot \left(\frac{s}{\omega_{LC}} \right) + \left(\frac{s}{\omega_{LC}} \right)^2}$$

$$\omega_{Z_ESR} = \frac{1}{R_C \cdot C}$$


$$\omega_{LC}^2 = \frac{1}{L \cdot C}$$

$$Q = \frac{R_{LOAD}}{\omega_{LC} \cdot L}$$


Buck Converter $G_{VD}(s)$

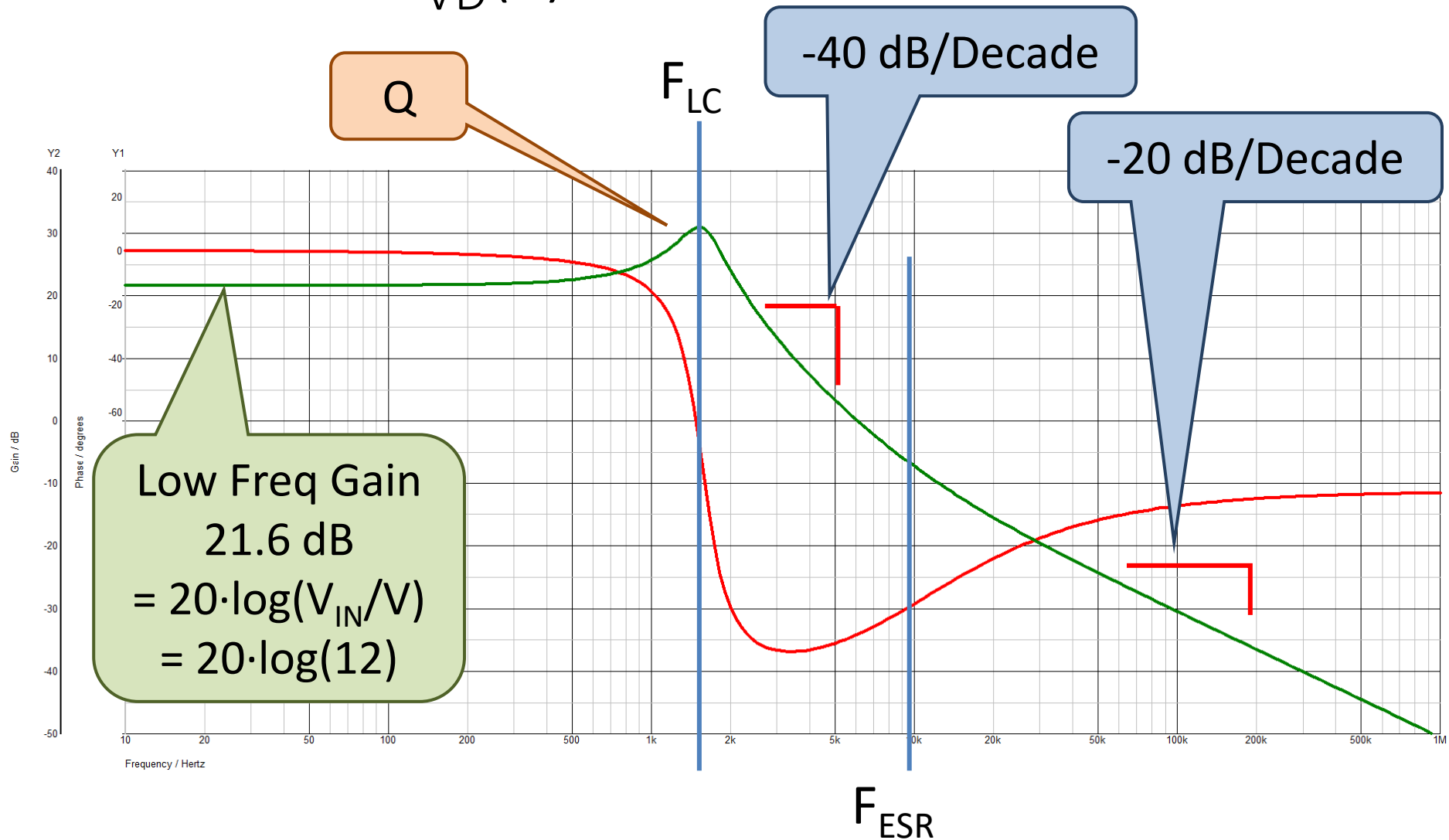


Buck Converter $G_{VD}(s)$

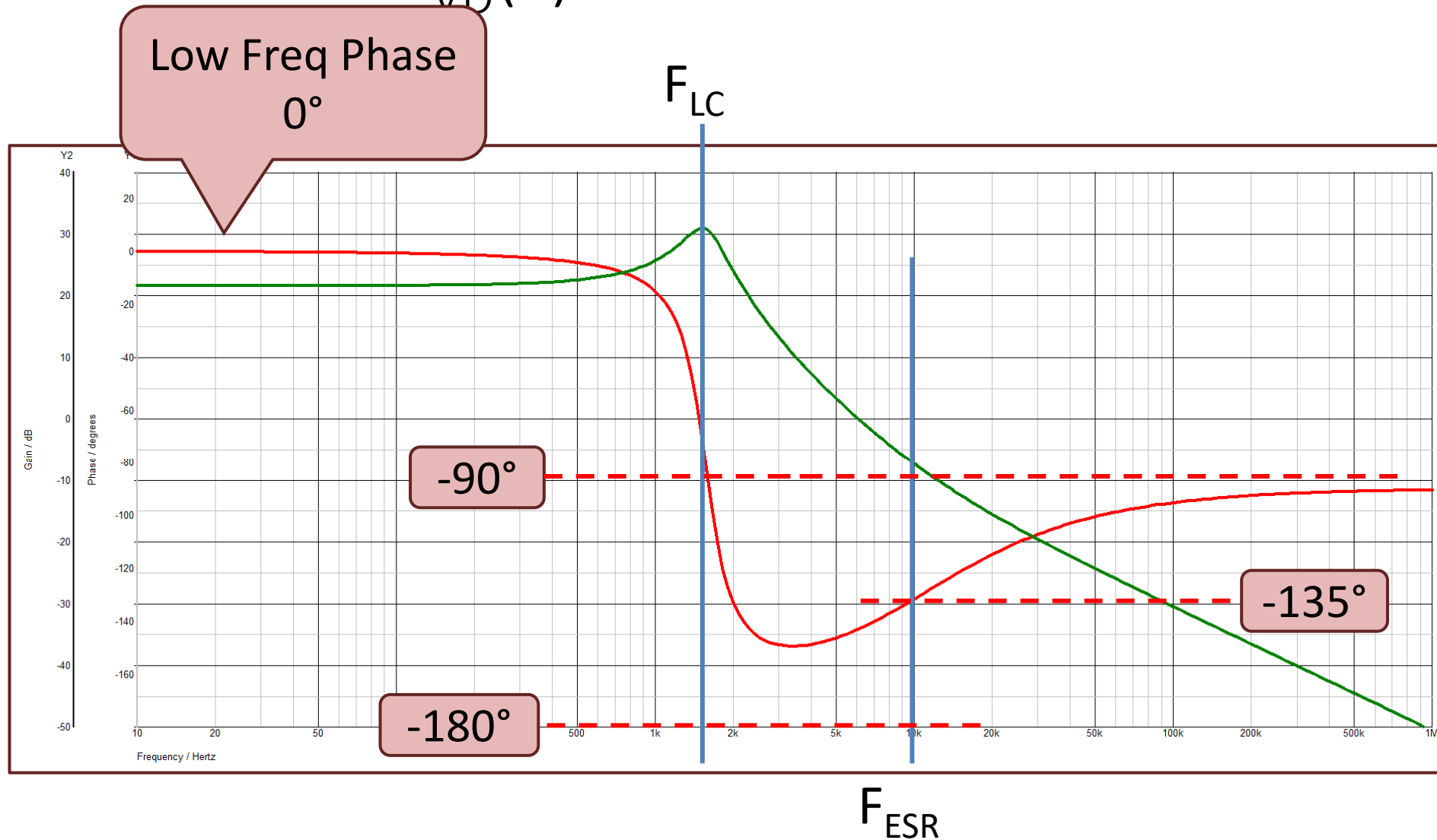

Buck Converter $G_{VD}(s)$

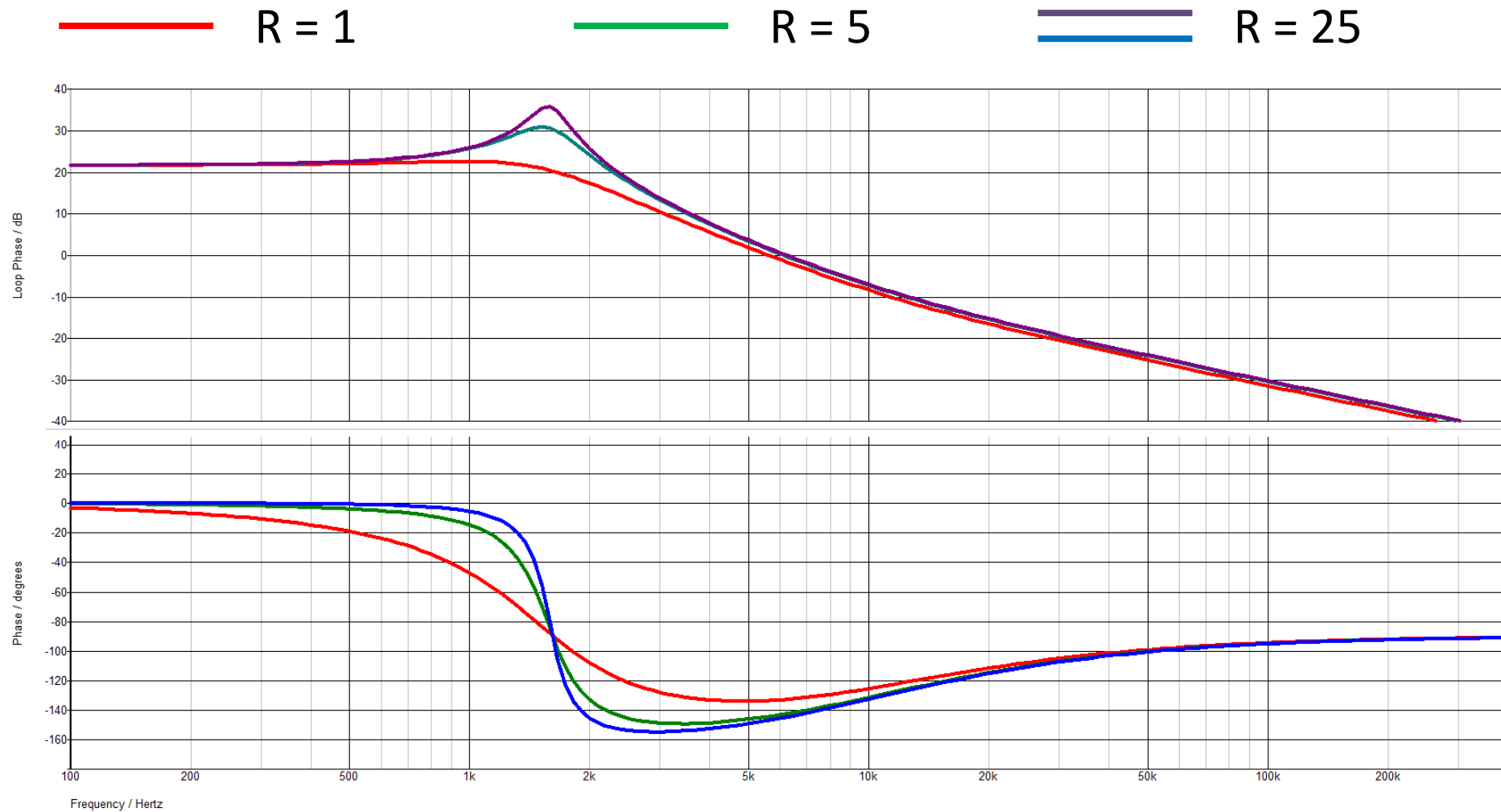


Buck Converter $G_{VD}(s)$

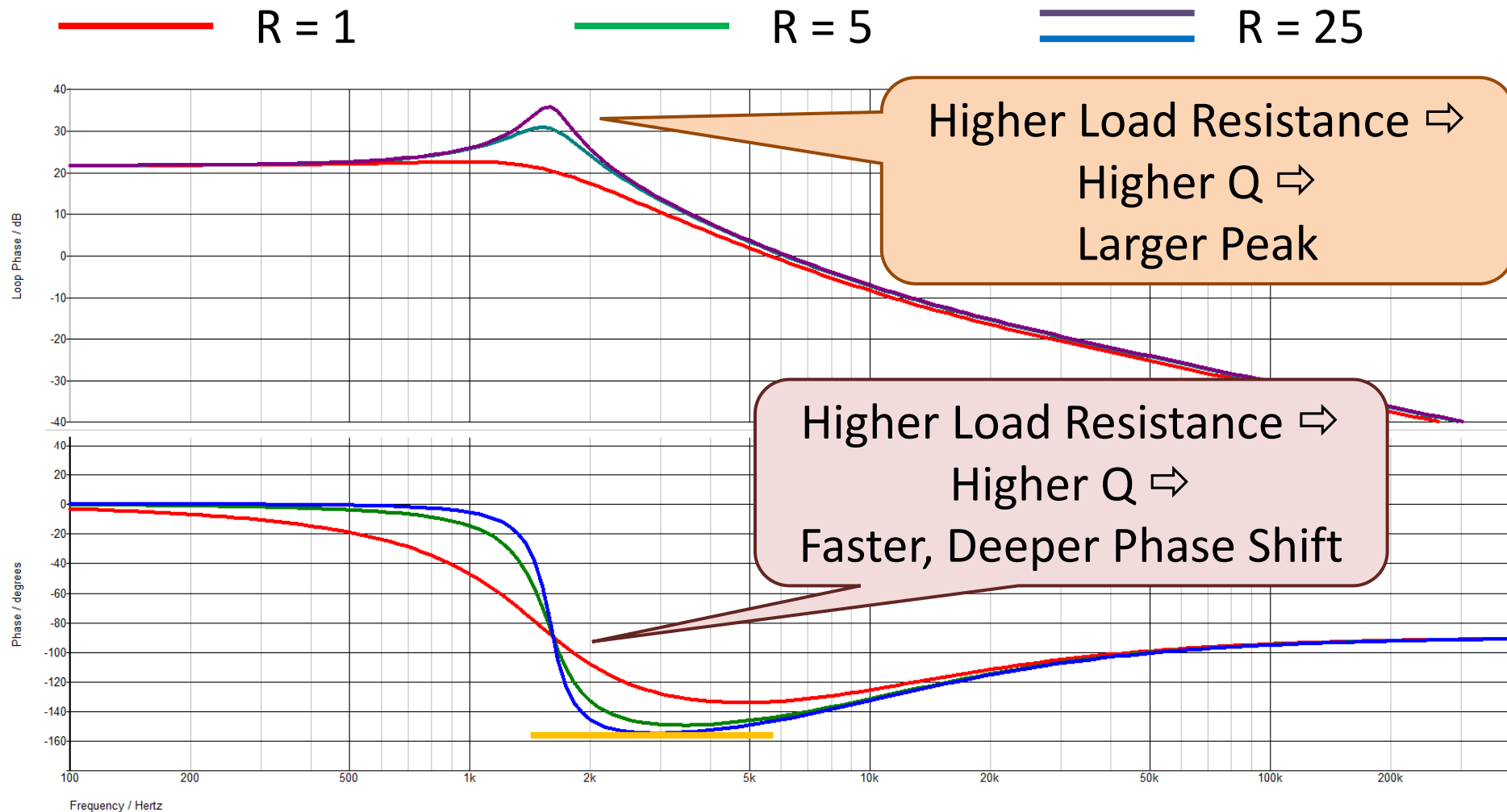


Solving For The Compensator

Compensator Poles And Zeros

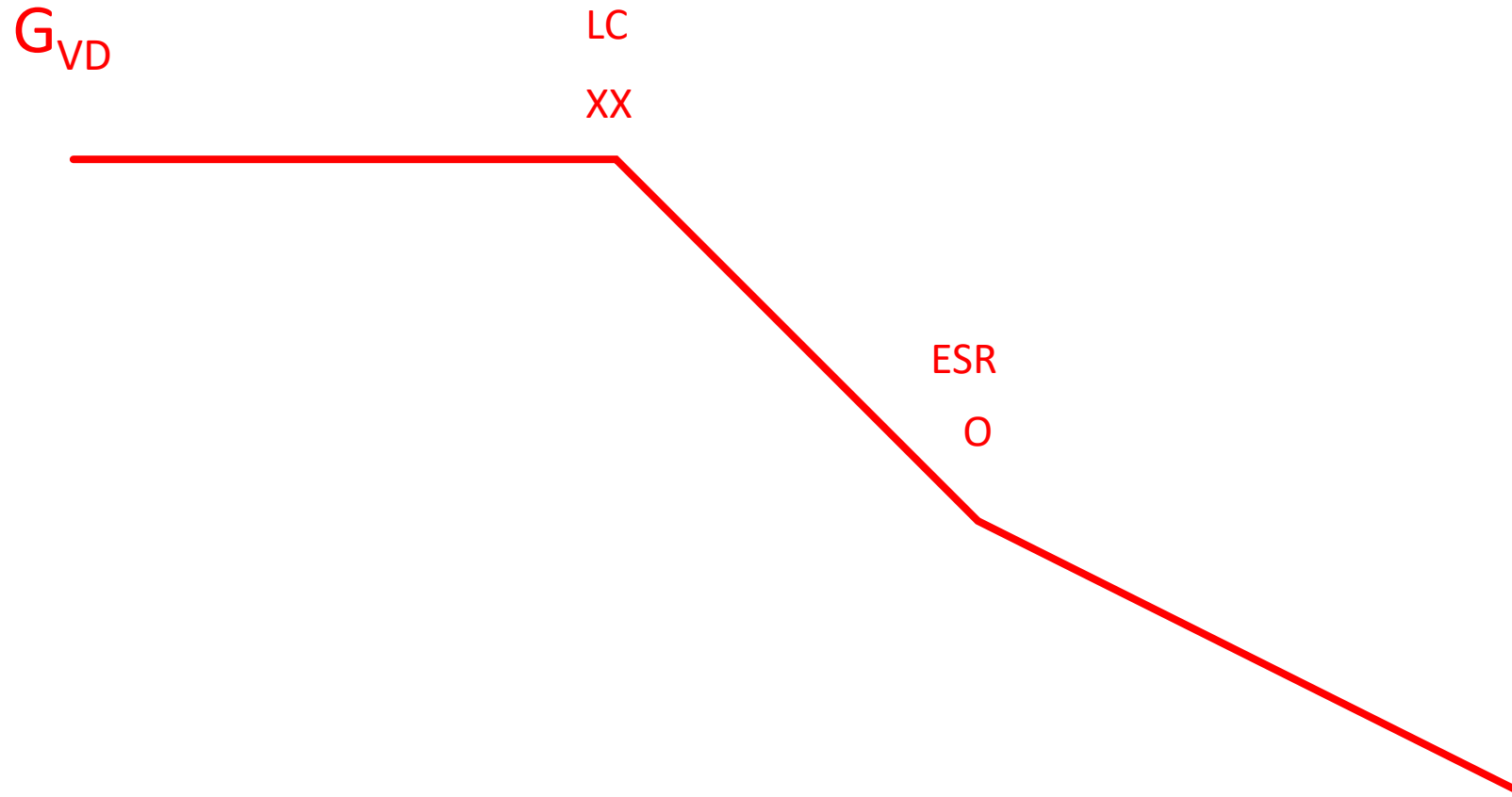


Compensator Poles And Zeros

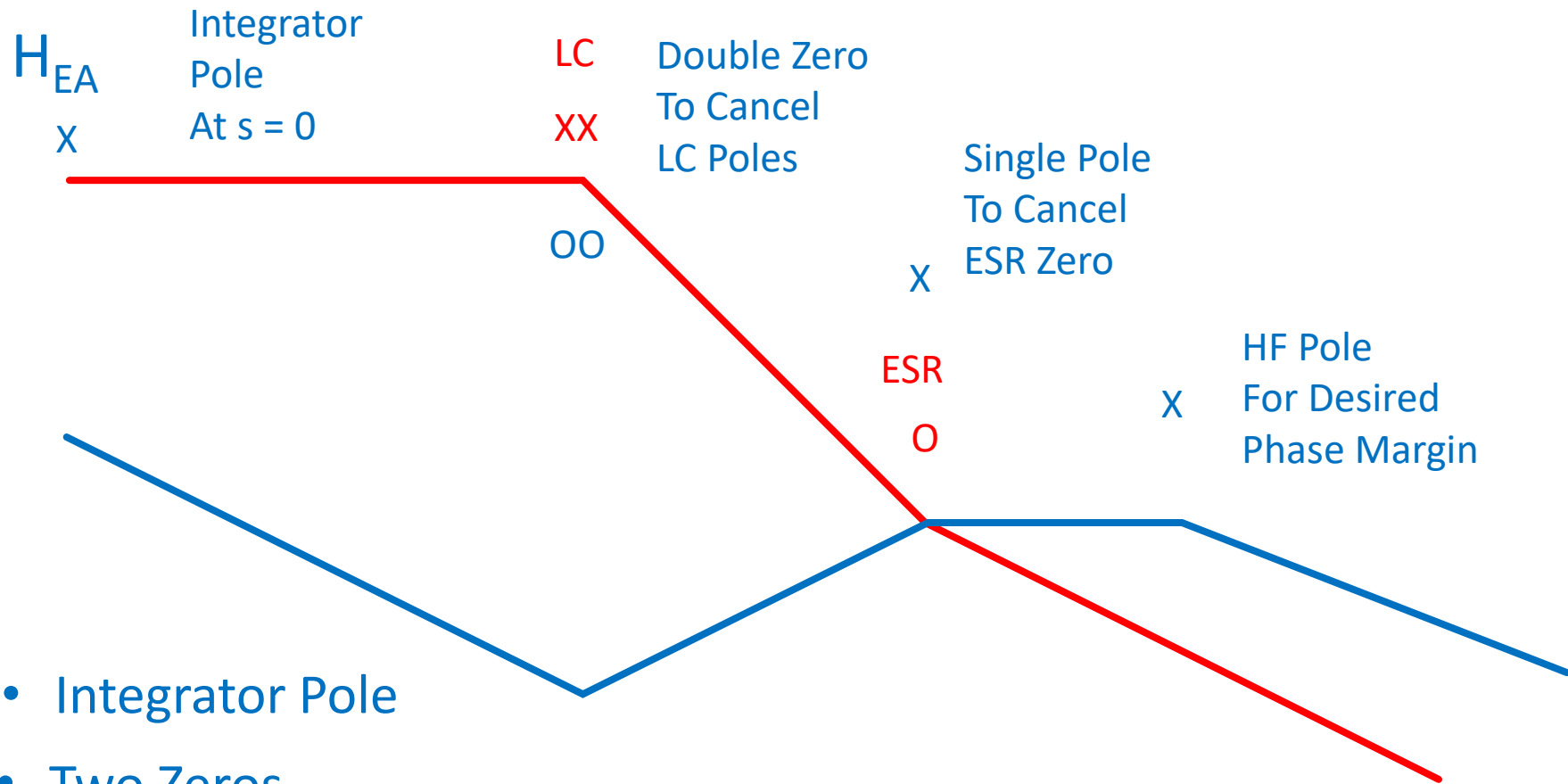

- Integrator Pole
- Two Zeros
- Two Poles

Compensator Poles And Zeros

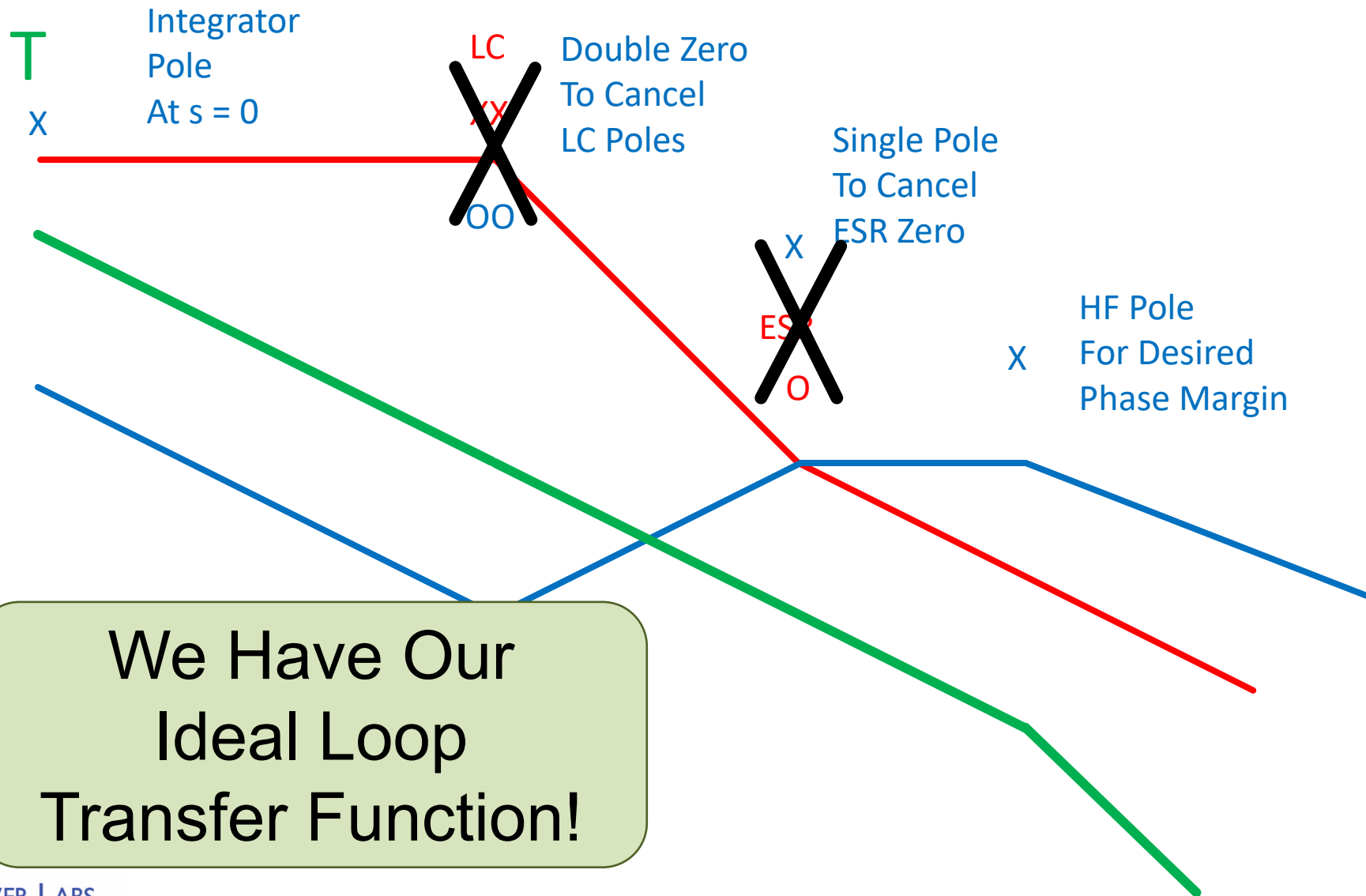

Solving For The Compensator

$$T(s) = K(s) \cdot H_{EA}(s) \cdot G_{PWM}(s) \cdot G_{VD}(s)$$

$$T(s) = \frac{\omega_0}{s} \cdot \frac{1}{1 + \frac{s}{\omega_{HFP}}}$$

$$H_{EA}(s) = \frac{T(s)}{K \cdot G_{PWM} \cdot G_{VD}(s)}$$

$$\omega_0 = \omega_C \cdot \sqrt{1 + \left(\frac{\omega_C}{\omega_{HFP}}\right)^2}$$

$$\omega_{HFP} = \frac{\omega_C}{\tan(90 - PM)}$$

$$K = 1$$

$$G_{PWM} = \frac{1}{V_{RAMP}}$$

$$G_{VD}(s) = V_{IN} \cdot \frac{1 + \frac{s}{\omega_{Z_ESR}}}{1 + \frac{1}{Q} \cdot \left(\frac{s}{\omega_{LC}}\right) + \left(\frac{s}{\omega_{LC}}\right)^2}$$

Solving For The Compensator

Ideal
Compensator
Transfer

Full

$$H_{EA}(s) = \frac{\frac{\omega_0}{s} \cdot \frac{1}{1 + \frac{s}{\omega_{HFP}}}}{\frac{1}{V_{RAMP}} \cdot \left[V_{IN} \cdot \frac{1 + \frac{s}{\omega_{Z_ESR}}}{1 + \frac{1}{Q} \cdot \left(\frac{s}{\omega_{LC}} \right) + \left(\frac{s}{\omega_{LC}} \right)^2} \right]}$$

Two Zeros

Integrator Pole

$$= \frac{\omega_{P0}}{s} \frac{1 + \frac{1}{Q} \cdot \left(\frac{s}{\omega_{LC}} \right) + \left(\frac{s}{\omega_{LC}} \right)^2}{\left(1 + \frac{s}{\omega_{Z_ESR}} \right) \cdot \left(1 + \frac{s}{\omega_{HFP}} \right)}$$

Two Poles

$$\omega_{P0} = \frac{V_{RAMP} \cdot \omega_0}{V_{IN}} = \frac{V_{RAMP}}{V_{IN}} \cdot \omega_C \cdot \sqrt{1 + \left(\frac{\omega_C}{\omega_{HFP}} \right)^2}$$


Practical Compensator Transfer Function

$$H_{EA}(s) = \frac{\omega_{PC}}{s} \cdot \frac{\left(1 + \frac{s}{\omega_{Z1}}\right) \cdot \left(1 + \frac{s}{\omega_{Z2}}\right)}{\left(1 + \frac{s}{\omega_{P1}}\right) \cdot \left(1 + \frac{s}{\omega_{P2}}\right)}$$


How Do We
Implement
This In A Circuit?

How Do We
Choose The
Pole And Zero
Frequencies?

Type III Compensator

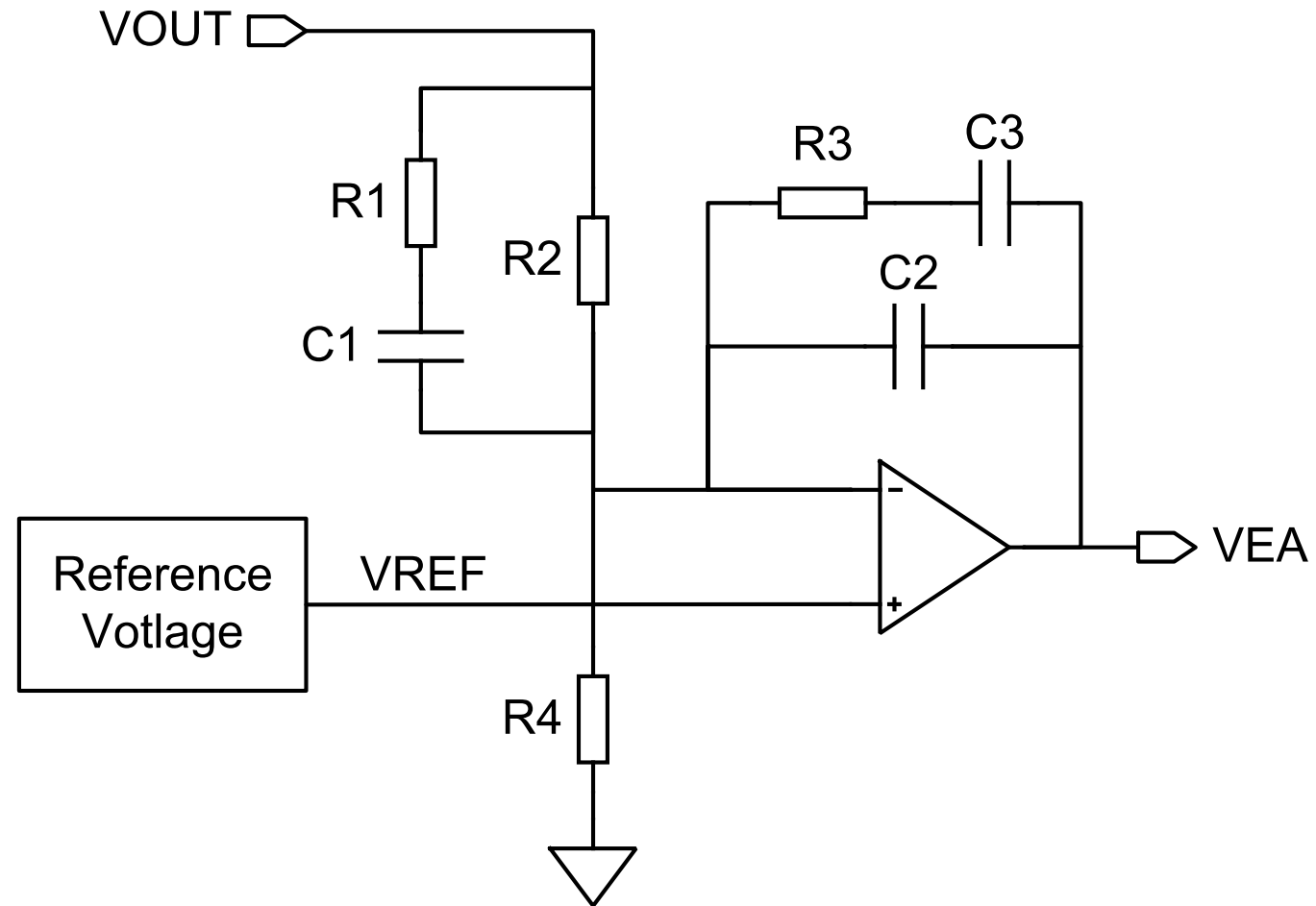

Type III Compensator

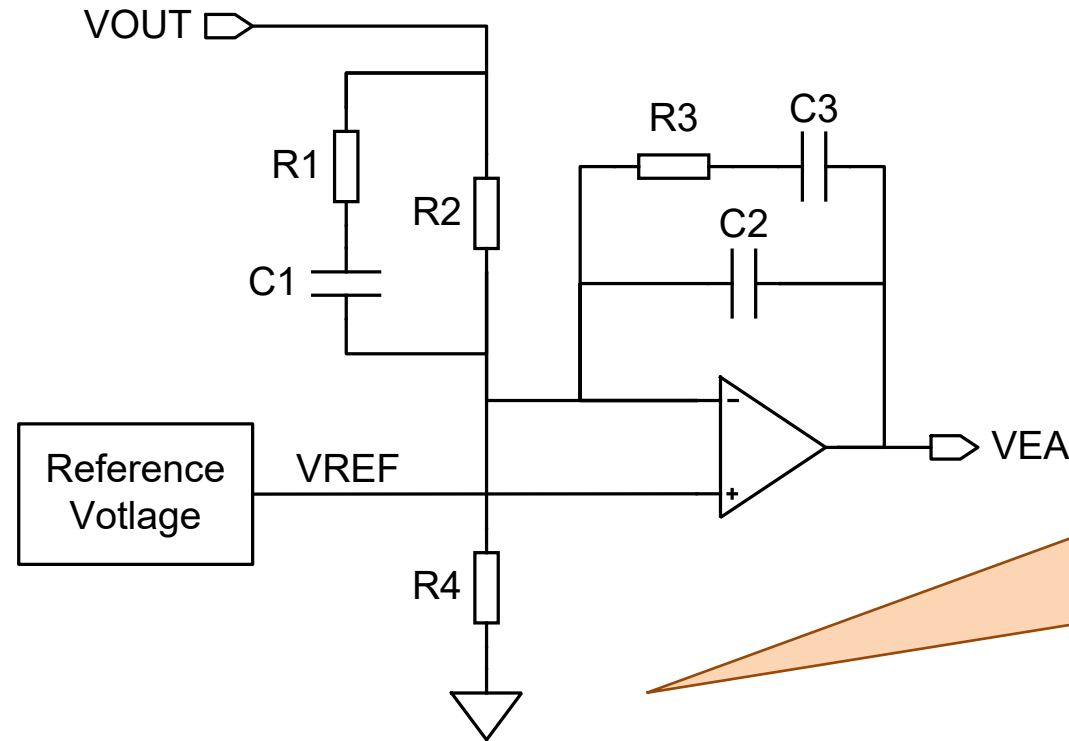

$$H_{EA}(s) = \frac{v_{EA}(s)}{v_{OUT}(s)}$$

$$= \frac{1}{s \cdot R_2 \cdot (C_2 + C_3)} \cdot \frac{1 + s \cdot R_3 \cdot C_3}{1 + s \cdot R_1 \cdot C_1} \cdot \frac{1 + s \cdot (R_1 + R_2) \cdot C_1}{1 + s \cdot R_3 \cdot \frac{C_2 \cdot C_3}{C_2 + C_3}}$$


Note
No Voltage
Divider
Term!

Note
R4 Does NOT
Appear!

Type III Compensator

Integrator
Pole
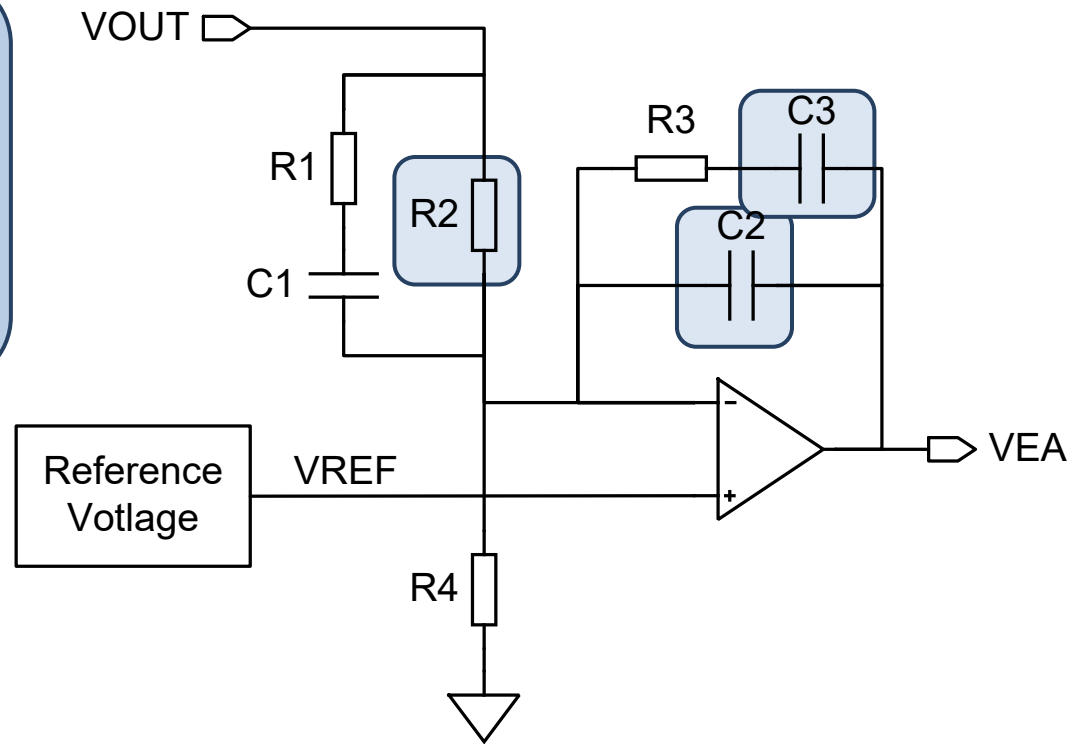
$$\omega_{P0} = \frac{1}{R_2 \cdot (C_2 + C_3)}$$




$$H_{EA}(s) = \frac{v_{EA}(s)}{v_{OUT}(s)}$$

$$= \frac{1}{s \cdot R_2 \cdot (C_2 + C_3)} \cdot \frac{1 + s \cdot R_3 \cdot C_3}{1 + s \cdot R_1 \cdot C_1} \cdot \frac{1 + s \cdot (R_1 + R_2) \cdot C_1}{1 + s \cdot R_3 \cdot \frac{C_2 \cdot C_3}{C_2 + C_3}}$$

Type III Compensator

First Zero
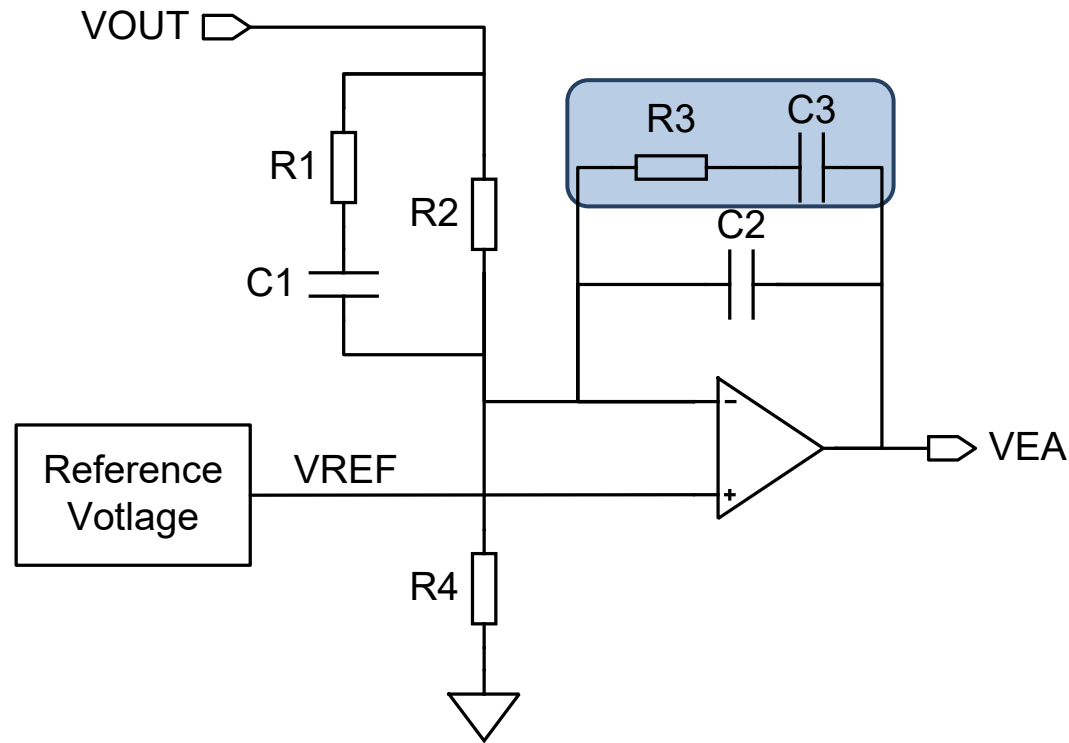
$$\omega_{Z1} = \frac{1}{R_3 \cdot C_3}$$




$$H_{EA}(s) = \frac{v_{EA}(s)}{v_{OUT}(s)}$$

$$= \frac{1}{s \cdot R_2 \cdot (C_2 + C_3)} \cdot \frac{1 + s \cdot R_3 \cdot C_3}{1 + s \cdot R_1 \cdot C_1} \cdot \frac{1 + s \cdot (R_1 + R_2) \cdot C_1}{1 + s \cdot R_3 \cdot \frac{C_2 \cdot C_3}{C_2 + C_3}}$$

Type III Compensator

Second Zero
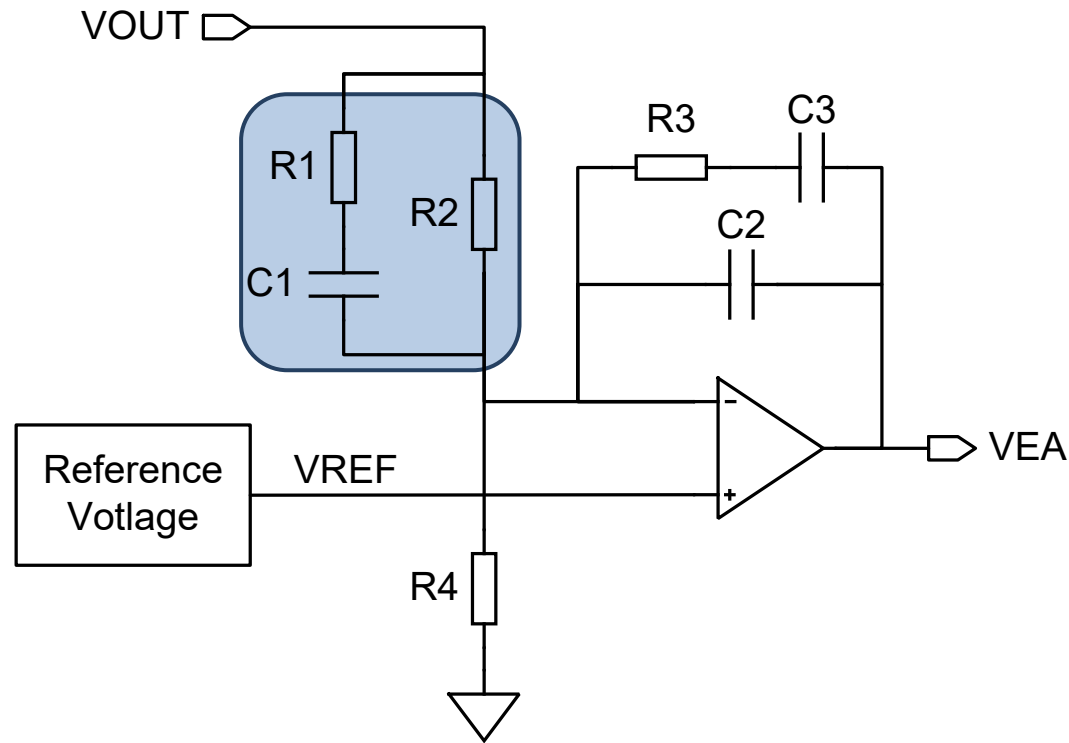
$$\omega_{z2} = \frac{1}{(R_1 + R_2) \cdot C_1}$$




$$H_{EA}(s) = \frac{v_{EA}(s)}{v_{OUT}(s)}$$

$$= \frac{1}{s \cdot R_2 \cdot (C_2 + C_3)} \cdot \frac{1 + s \cdot R_3 \cdot C_3}{1 + s \cdot R_1 \cdot C_1} \cdot \frac{1 + s \cdot (R_1 + R_2) \cdot C_1}{1 + s \cdot R_3 \cdot \frac{C_2 \cdot C_3}{C_2 + C_3}}$$

Type III Compensator

Second Pole
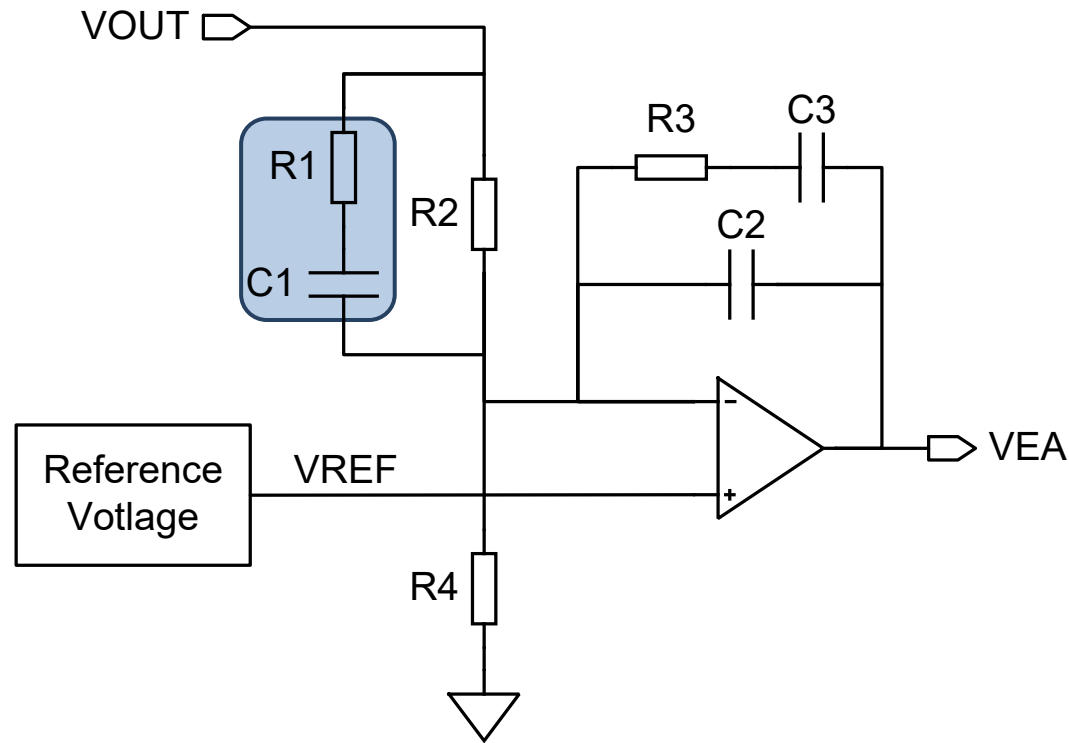
$$\omega_{P1} = \frac{1}{R_1 \cdot C_1}$$




$$H_{EA}(s) = \frac{v_{EA}(s)}{v_{OUT}(s)}$$

$$= \frac{1}{s \cdot R_2 \cdot (C_2 + C_3)} \cdot \frac{1 + s \cdot R_3 \cdot C_3}{1 + s \cdot R_1 \cdot C_1} \cdot \frac{1 + s \cdot (R_1 + R_2) \cdot C_1}{1 + s \cdot R_3 \cdot \frac{C_2 \cdot C_3}{C_2 + C_3}}$$

Type III Compensator

Third Pole
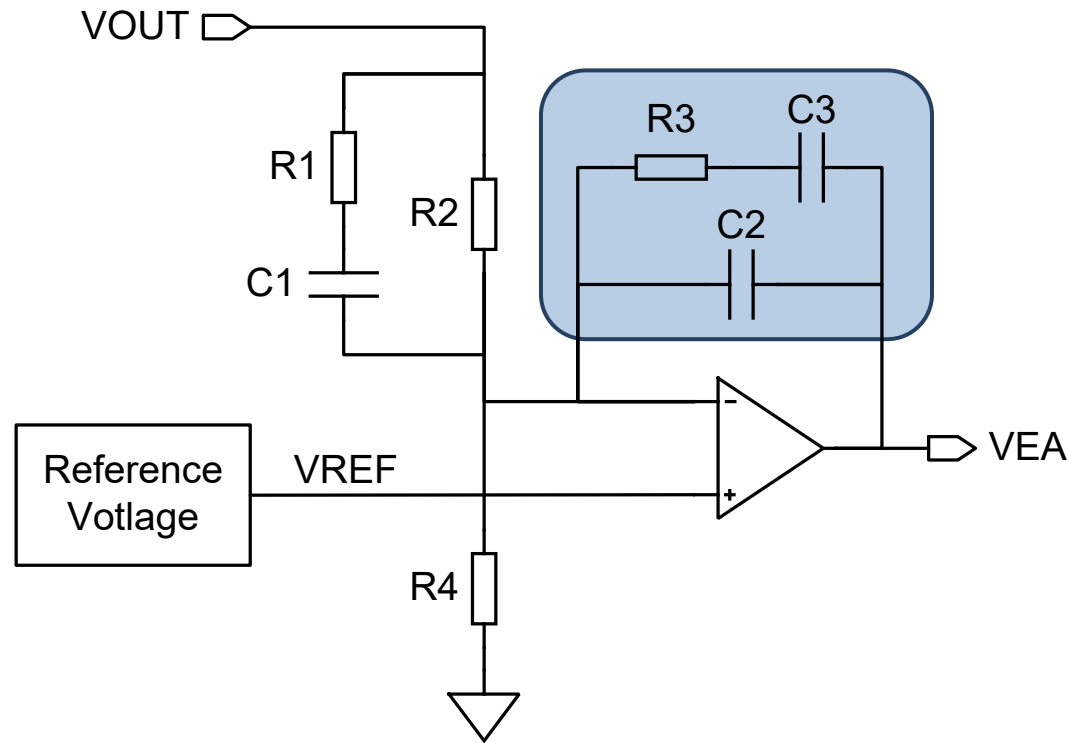
$$\omega_{P2} = \frac{1}{R_3 \cdot \frac{C_2 \cdot C_3}{C_2 + C_3}}$$




$$H_{EA}(s) = \frac{v_{EA}(s)}{v_{OUT}(s)}$$

$$= \frac{1}{s \cdot R_2 \cdot (C_2 + C_3)} \cdot \frac{1 + s \cdot R_3 \cdot C_3}{1 + s \cdot R_1 \cdot C_1} \cdot \frac{1 + s \cdot (R_1 + R_2) \cdot C_1}{1 + s \cdot R_3 \cdot \frac{C_2 \cdot C_3}{C_2 + C_3}}$$


Type III Bode Plot
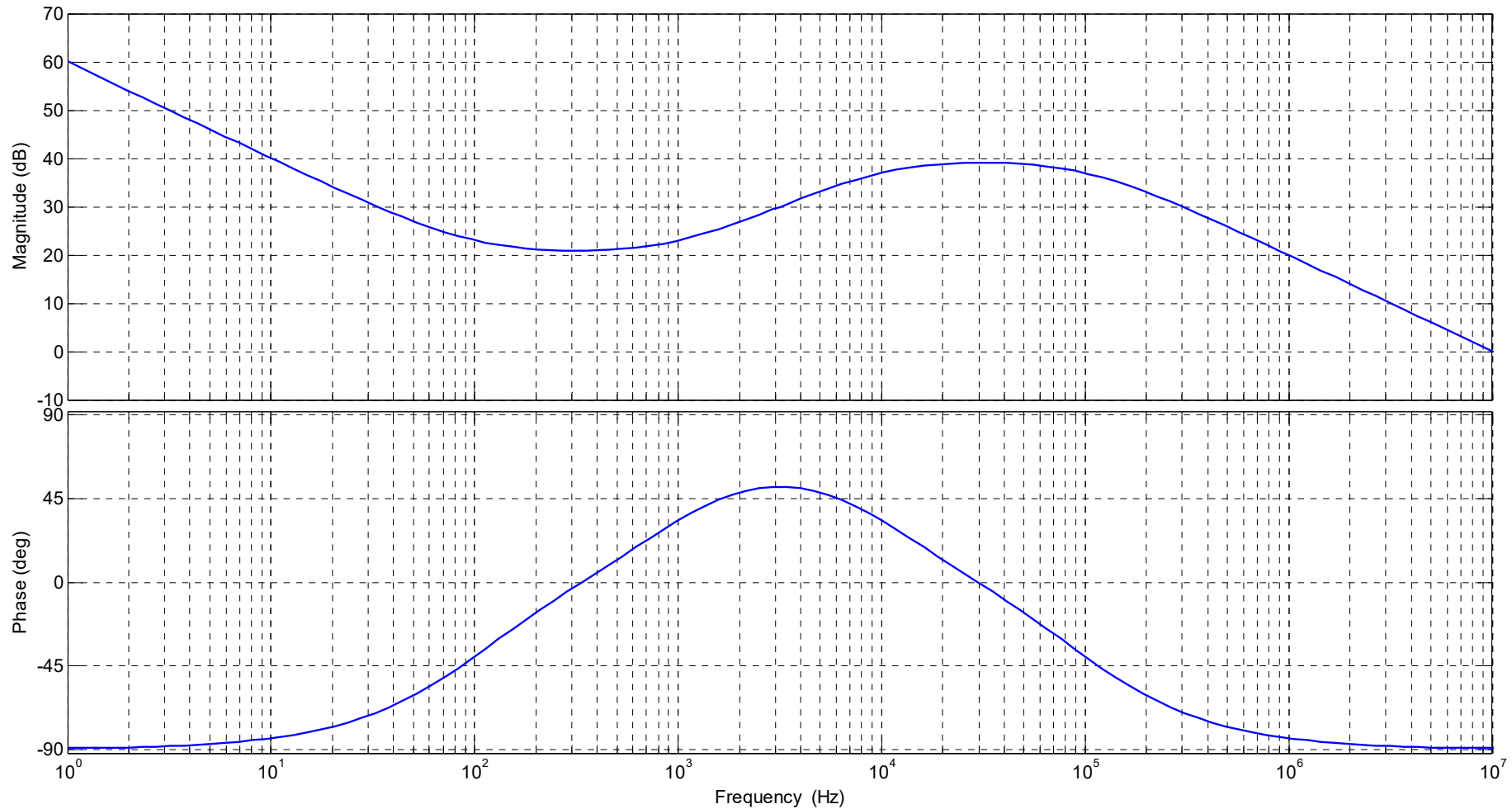
$$f_{P0} = 1000\text{Hz} \quad f_{Z1} = 100\text{Hz} \quad f_{Z2} = 1000\text{Hz} \quad f_{P1} = 10\text{kHz} \quad f_{P2} = 100\text{kHz}$$



Type III Bode Plot
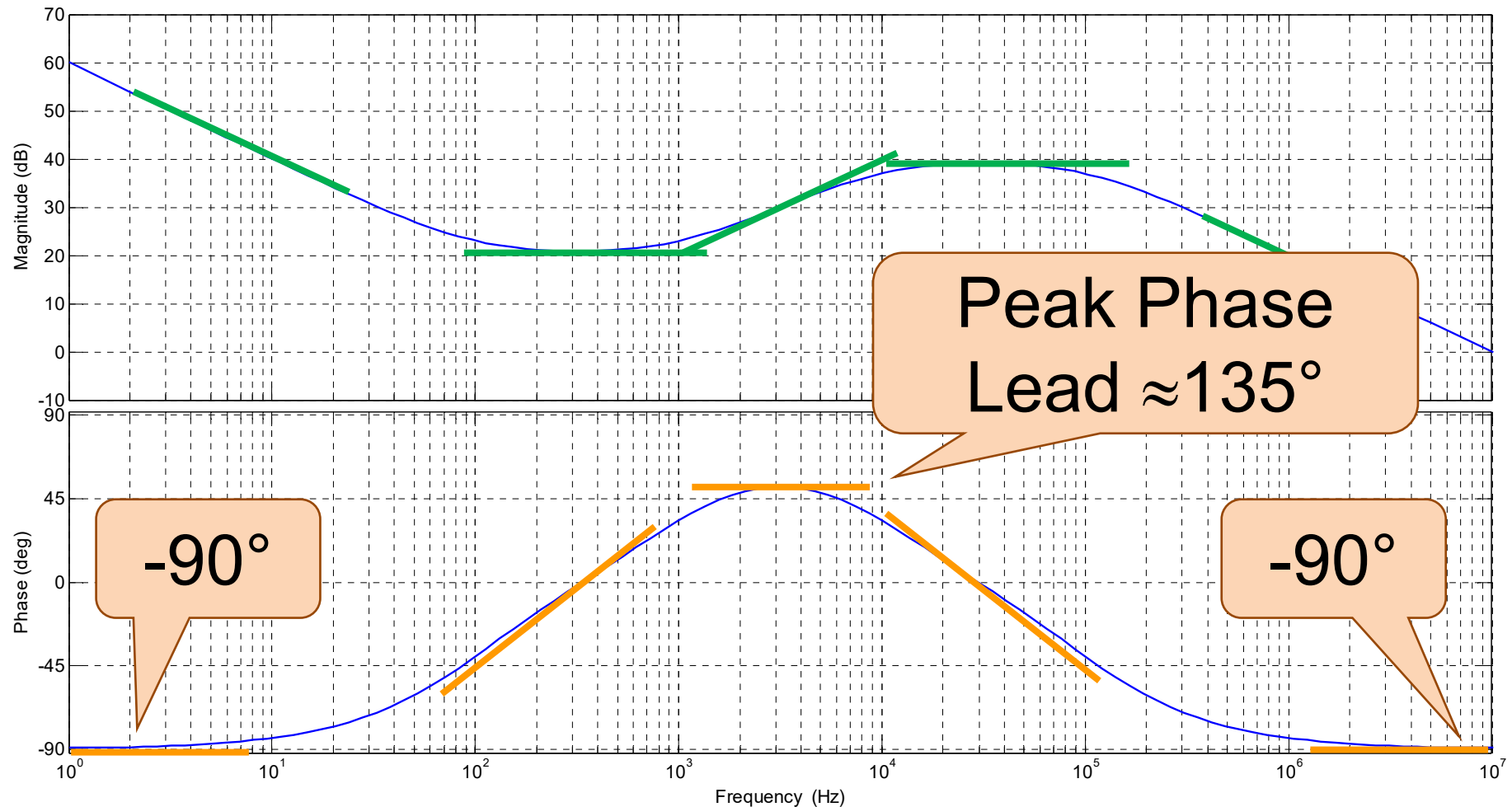
$$f_{P0} = 1000\text{Hz} \quad f_{Z1} = 100\text{Hz} \quad f_{Z2} = 1000\text{Hz} \quad f_{P1} = 10\text{kHz} \quad f_{P2} = 100\text{kHz}$$



Choosing Compensator Poles And Zeroes

$$T(s) = K(s) \cdot H_{EA}(s) \cdot G_{PWM}(s) \cdot G_{VD}(s)$$

$$T(s) = \frac{\omega_0}{s} \cdot \frac{1}{1 + \frac{s}{\omega_{HFP}}} = \left[\frac{\omega_{P0}}{s} \cdot \frac{\left(1 + \frac{s}{\omega_{Z1}}\right) \cdot \left(1 + \frac{s}{\omega_{Z2}}\right)}{\left(1 + \frac{s}{\omega_{P1}}\right) \cdot \left(1 + \frac{s}{\omega_{P2}}\right)} \right] \cdot \frac{1}{V_{RAMP}} \cdot \left[V_{IN} \cdot \frac{1 + \frac{s}{\omega_{Z_ESR}}}{1 + \frac{1}{Q} \cdot \left(\frac{s}{\omega_{LC}}\right) + \left(\frac{s}{\omega_{LC}}\right)^2} \right]$$

To Design The Compensator We Need These Five Frequencies

Choosing Compensator Poles And Zeroes

$$T(s) = K(s) \cdot H_{EA}(s) \cdot G_{PWM}(s) \cdot G_{VD}(s)$$

$$T(s) = \frac{\omega_0}{s} \cdot \frac{1}{1 + \frac{s}{\omega_{HFP}}} \cdot \left[\frac{\omega_{P0}}{s} \cdot \frac{\left(1 + \frac{s}{\omega_{Z1}}\right) \cdot \left(1 + \frac{s}{\omega_{Z2}}\right)}{\left(1 + \frac{s}{\omega_{P1}}\right) \cdot \left(1 + \frac{s}{\omega_{P2}}\right)} \right] \cdot \frac{1}{V_{RAMP}} \cdot \left[V_{IN} \cdot \frac{1 + \frac{s}{\omega_{Z_ESR}}}{1 + \frac{1}{Q} \cdot \left(\frac{s}{\omega_{LC}}\right) + \left(\frac{s}{\omega_{LC}}\right)^2} \right]$$

$$\omega_{Z1} = \omega_{Z2} = \omega_{LC}$$

$$\omega_{P1} = \omega_{Z_ESR}$$

$$\omega_{P2} = \omega_{HFP}$$

Choosing Compensator Poles And Zeroes

$$T(s) = K(s) \cdot H_{EA}(s) \cdot G_{PWM}(s) \cdot G_{VD}(s)$$

$$T(s) = \frac{\omega_0}{s} \cdot \frac{1}{1 + \frac{s}{\omega_{HFP}}} = \left[\frac{\omega_{P0}}{s} \cdot \frac{\left(1 + \frac{s}{\omega_{Z1}}\right) \cdot \left(1 + \frac{s}{\omega_{Z2}}\right)}{\left(1 + \frac{s}{\omega_{P1}}\right) \cdot \left(1 + \frac{s}{\omega_{P2}}\right)} \right] \cdot \left[\frac{1}{V_{RAMP}} \right] \cdot \left[\frac{V_{IN} \cdot \frac{1 + \frac{s}{\omega_{Z_ESR}}}{1 + \frac{1}{Q} \cdot \left(\frac{s}{\omega_{LC}}\right) + \left(\frac{s}{\omega_{LC}}\right)^2}} \right]$$


DC Gain Term/Integrator Pole Frequency: $\omega_{P0} = \frac{V_{RAMP} \cdot \omega_0}{V_{IN}} = \frac{V_{RAMP}}{V_{IN}} \cdot \omega_C \cdot \sqrt{1 + \left(\frac{\omega_C}{\omega_{HFP}}\right)^2}$

Calculating Component Values

- If $V_{OUT} > V_{REF}$ Choose Current (I_{BIAS}) Through R2 And R4
 - 100 μ A – 1 mA Typical

$$R_4 = \frac{V_{REF}}{I_{BIAS}}$$
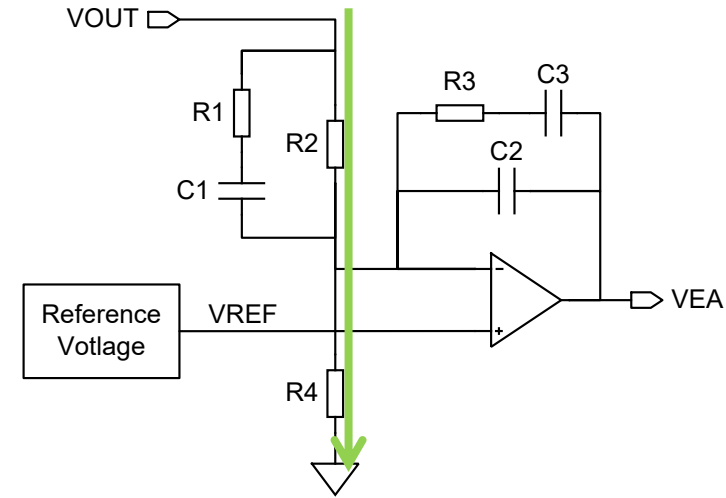
$$R_2 = \frac{V_{OUT} - V_{REF}}{V_{REF}} \cdot R_4$$



- If $V_{OUT} = V_{REF}$:
 - R4 Not Used
 - Choose Convenient Value For R2 (10 k Ω)


Calculating Component Values

$$R_1 = \frac{f_{Z2}}{f_{P1} - f_{Z2}} \cdot R_2$$

$$C_1 = \frac{1}{2 \cdot \pi \cdot f_{P1} \cdot R_1}$$

$$C_2 = \frac{f_{Z1}}{2 \cdot \pi \cdot f_{P2} \cdot f_{P0} \cdot R_2}$$
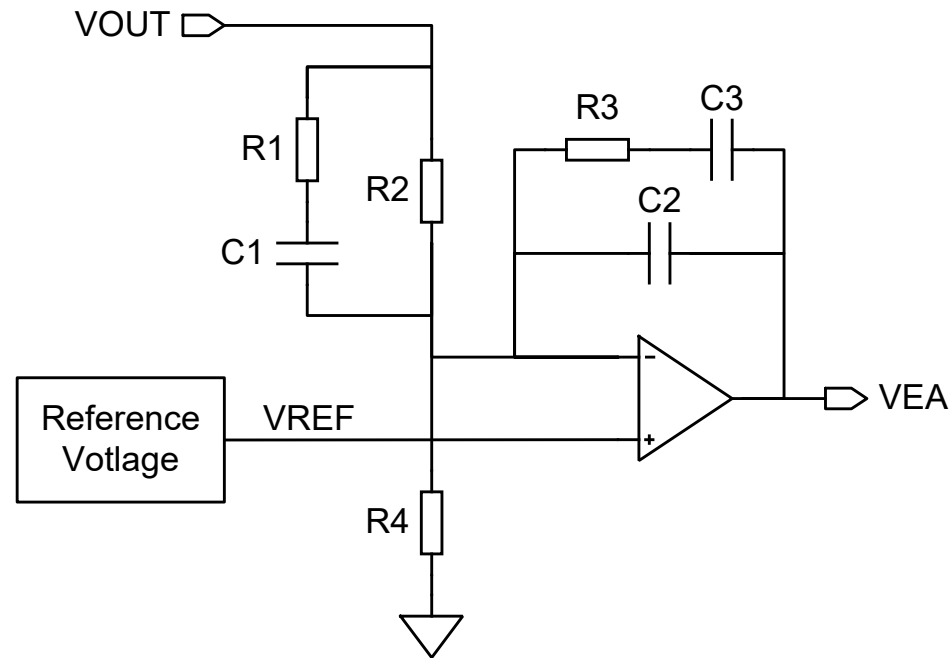
$$C_3 = \frac{1}{2 \cdot \pi \cdot f_{P0} \cdot R_2} - C_2 \quad R_3 = \frac{1}{2 \cdot \pi \cdot f_{Z1} \cdot C_3}$$



Buck Converter Example

$$V_{IN} = 12Vdc$$

$$V_{OUT} = 3.3Vdc$$

$$I_{OUT} = 1A dc$$

$$V_{REF} = 2.5Vdc$$

$$F_{SW} = 300\text{ kHz}$$

$$L_{OUT} = 18\mu\text{H}$$

$$C_{OUT} = 47\mu\text{F}$$

$$R_{COUT} = 20\text{ m}\Omega$$

$$F_C = \frac{1}{10} F_{SW} = 30\text{ kHz}$$

$$PM = 70^\circ$$

$$F_{LC} = \frac{1}{2 \cdot \pi \cdot \sqrt{L_{OUT} \cdot C_{OUT}}} = 5.472\text{ kHz}$$

$$F_{ESR} = \frac{1}{2 \cdot \pi \cdot R_{COUT} \cdot C_{OUT}} = 169.3\text{ kHz}$$

Buck Converter Example

Choose Compensator Zero Frequencies
And One Pole Frequency

$$F_{Z1} = F_{Z2} = F_{LC} = 5.472 \text{ kHz}$$

$$F_{P1} = F_{ESR} = 169.3 \text{ kHz}$$

Calculate Other Pole Frequency To Give
Desired Phase Margin At Crossover

$$PM = 70^\circ$$

$$Phase_Lag(F_C) = PM - 90^\circ = -20^\circ$$

$$F_{P2} = \frac{F_C}{-\tan(Phase_Lag)} = 82.4 \text{ kHz}$$

Calculate F_{P0}

$$\begin{aligned} F_{P0} &= \frac{V_{RAMP}}{V_{IN}} \cdot F_C \cdot \sqrt{1 + \left(\frac{\omega_C}{\omega_{HFP}}\right)^2} \\ &= \frac{1 \text{ V}}{12 \text{ V}} \cdot 30 \text{ kHz} \cdot \sqrt{1 + \left(\frac{2 \cdot \pi \cdot 30 \text{ kHz}}{2 \cdot \pi \cdot 82.4 \text{ kHz}}\right)^2} \\ &= 2661 \text{ kHz} \end{aligned}$$


Calculating Component Values

- $V_{OUT} > V_{REF}$ Choose Current (I_{BIAS}) Through R_2 And R_4
- $I_{BIAS} = 100 \mu A$

$$R_4 = \frac{V_{REF}}{I_{BIAS}} = \frac{2.5V}{100 \mu A} = 25 k\Omega \Rightarrow 24.9 k\Omega$$

$$R_2 = \frac{V_{OUT} - V_{REF}}{V_{REF}} \cdot R_4 = \frac{3.3V - 2.5V}{2.5V} \cdot 24.9 k\Omega = 7.968 k\Omega \Rightarrow 8.06 k\Omega$$
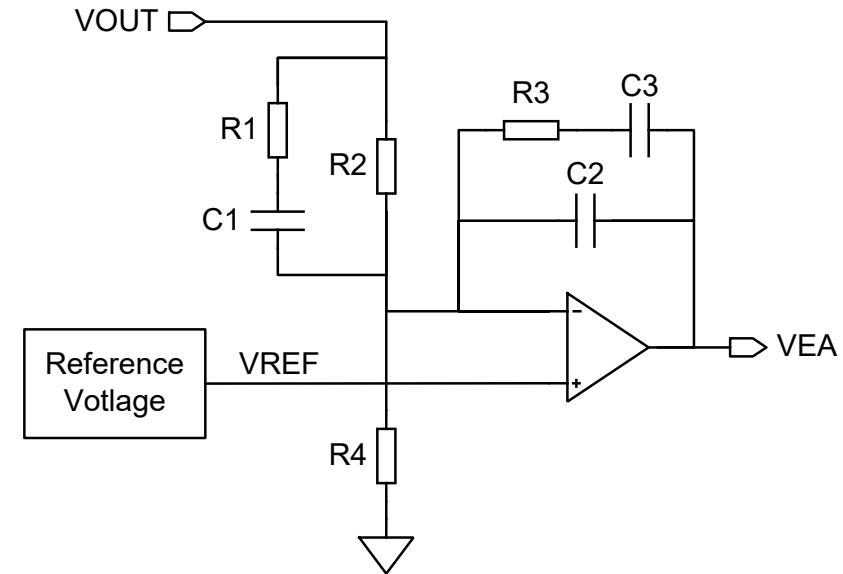
$$V_{OUT} = \frac{R_2 + R_4}{R_4} \cdot V_{REF} = 3.309V$$



Calculate Component Values

$$R_1 = \frac{F_{Z2}}{F_{P1} - F_{Z2}} \cdot R_2 = 269.18 \Omega \Rightarrow 267 \Omega$$

$$C_2 = \frac{F_{Z1}}{2 \cdot \pi \cdot F_{P2} \cdot F_{P0} \cdot R_2} = 492.7 \text{ pF} \Rightarrow 510 \text{ pF}$$

$$C_1 = \frac{1}{2 \cdot \pi \cdot F_{P1} \cdot R_1} = 3.521 \text{ nF} \Rightarrow 3.6 \text{ nF}$$

$$C_3 = \frac{1}{2 \cdot \pi \cdot F_{P0} \cdot R_2} = 6.912 \text{ nF} \Rightarrow 6.8 \text{ nF}$$

$$R_3 = \frac{1}{2 \cdot \pi \cdot F_{Z1} \cdot C_3} = 4.277 \text{ k}\Omega \Rightarrow 4.22 \text{ k}\Omega$$

Check Actual Compensator Pole And Zero Frequencies

Desired

As Designed

$$F_{P0} = 2.661 \text{ kHz}$$

$$F_{P0} = 2.701 \text{ kHz}$$

$$F_{Z1} = 5.472 \text{ kHz}$$

$$F_{Z1} = 5.546 \text{ kHz}$$

$$F_{Z2} = 5.472 \text{ kHz}$$

$$F_{Z2} = 5.309 \text{ kHz}$$

$$F_{P1} = 169.314 \text{ kHz}$$

$$F_{P1} = 165.6 \text{ kHz}$$


$$F_{P2} = 82.424 \text{ kHz}$$

$$F_{P2} = 79.50 \text{ kHz}$$


Simulation Schematic

Basic Synchronous Buck Regulator With Type III Compensator

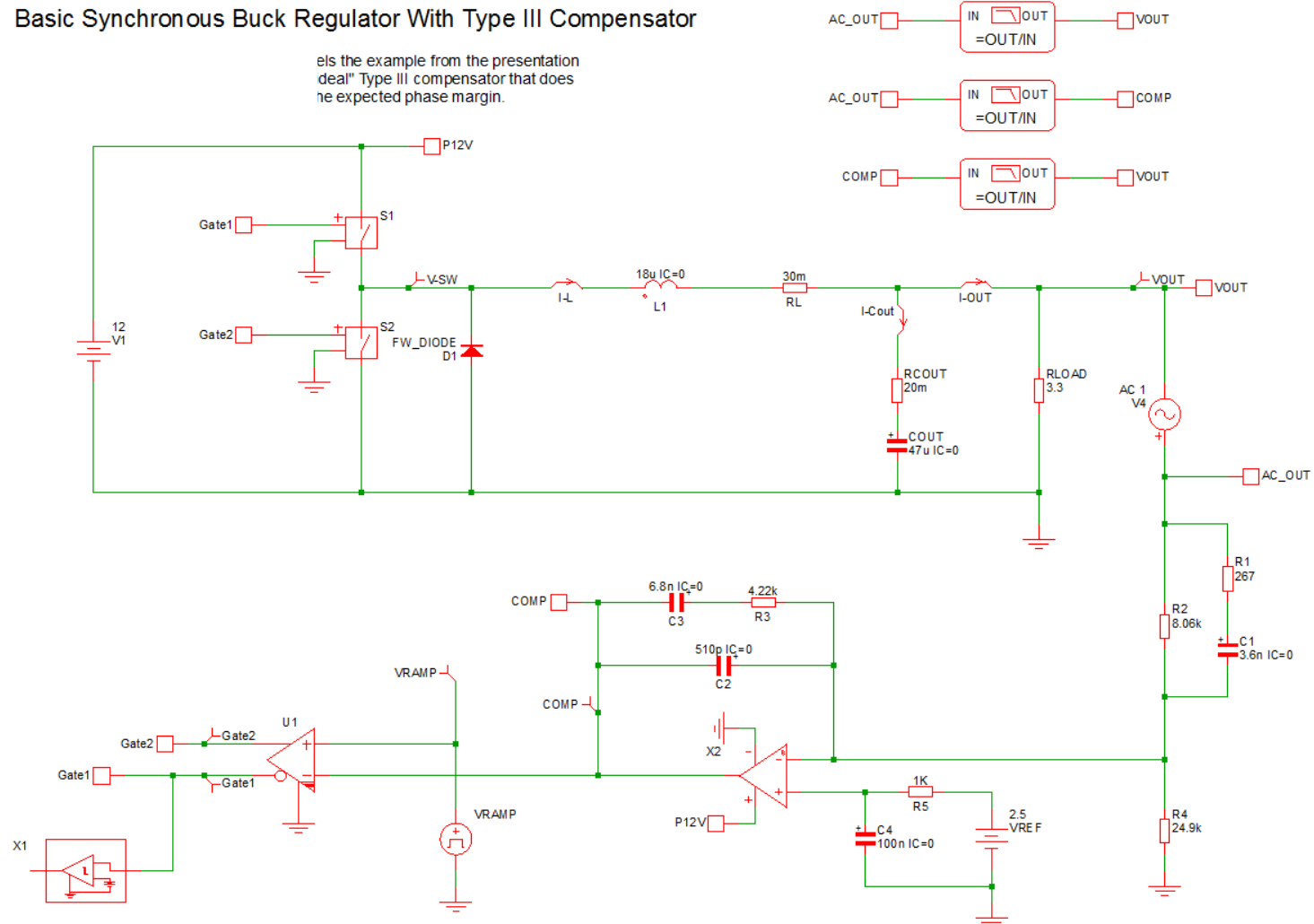
is the example from the presentation deal" Type III compensator that does ne expected phase margin.




Simulation Schematic

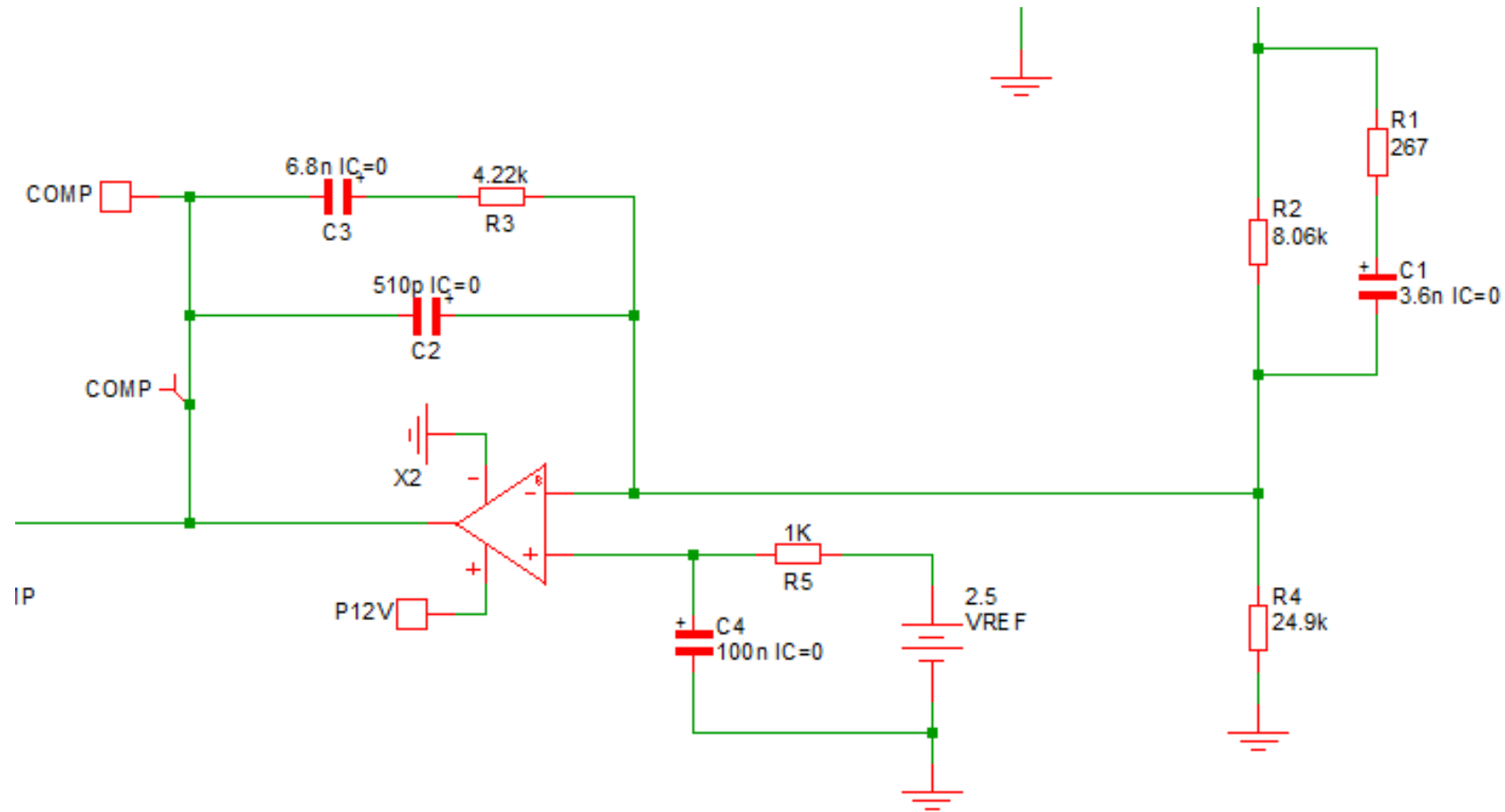


Example Bode Plot

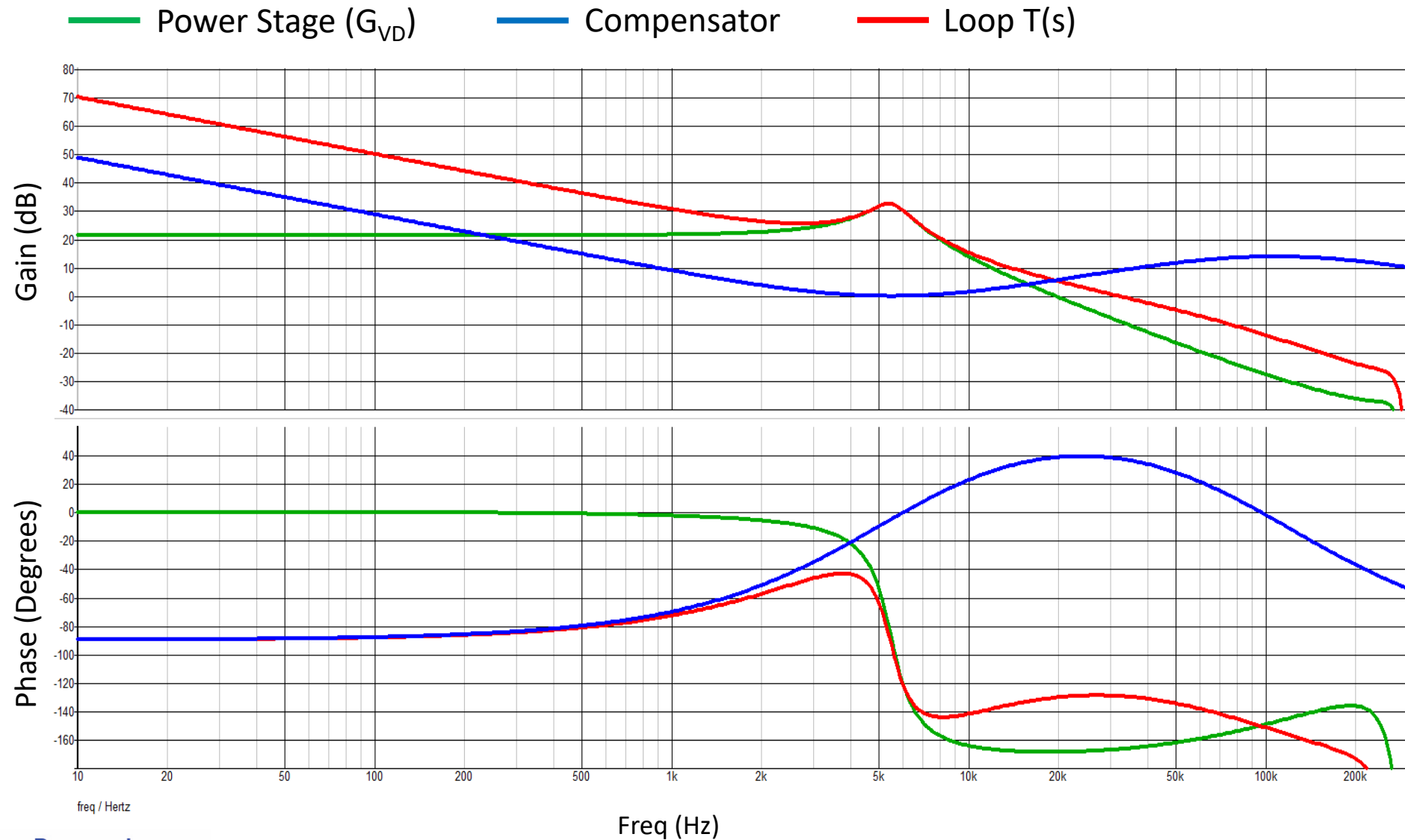


Example: Bode Plot $G_{VD}(s)$

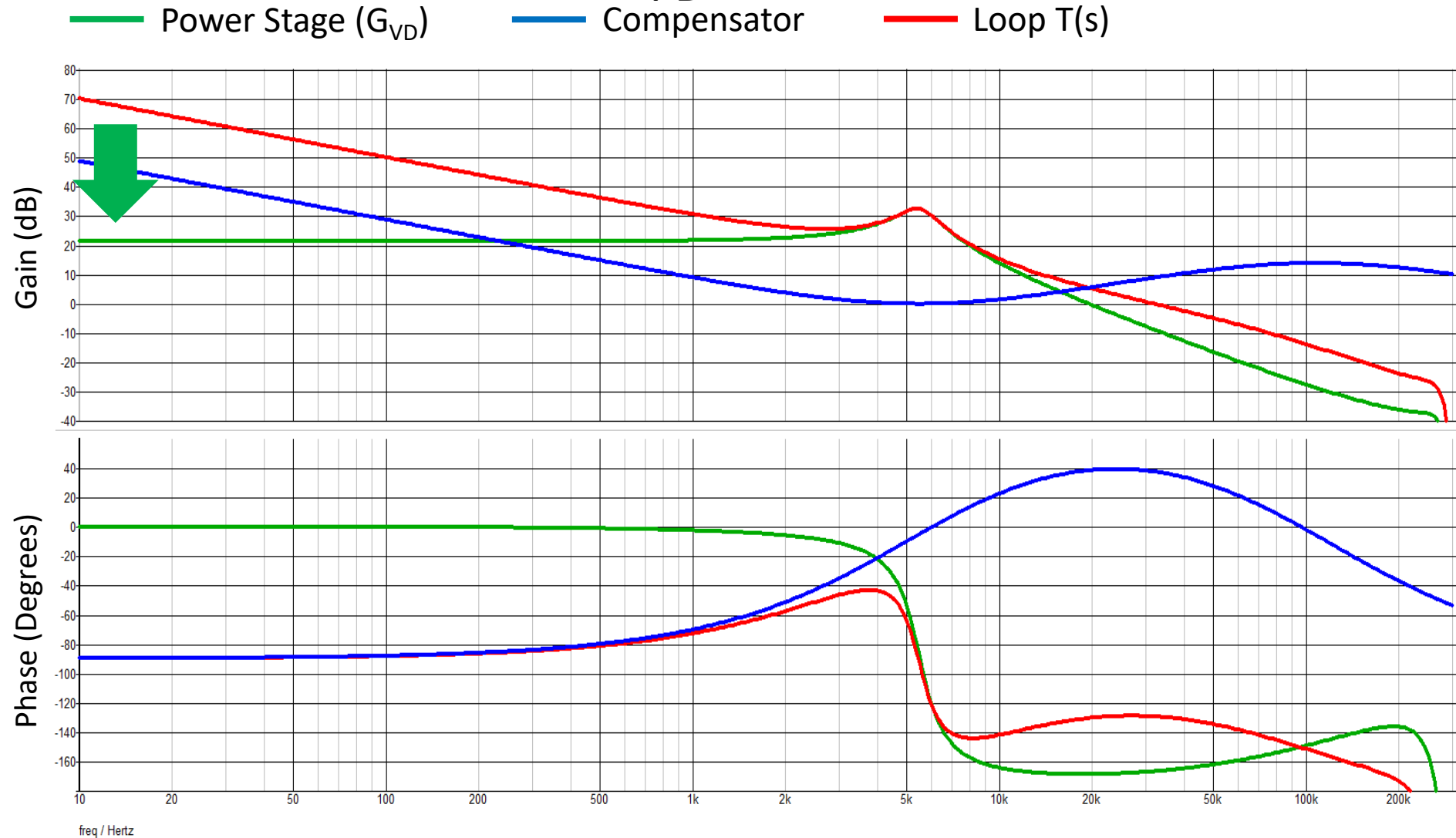


Example: Compensator Bode Plot

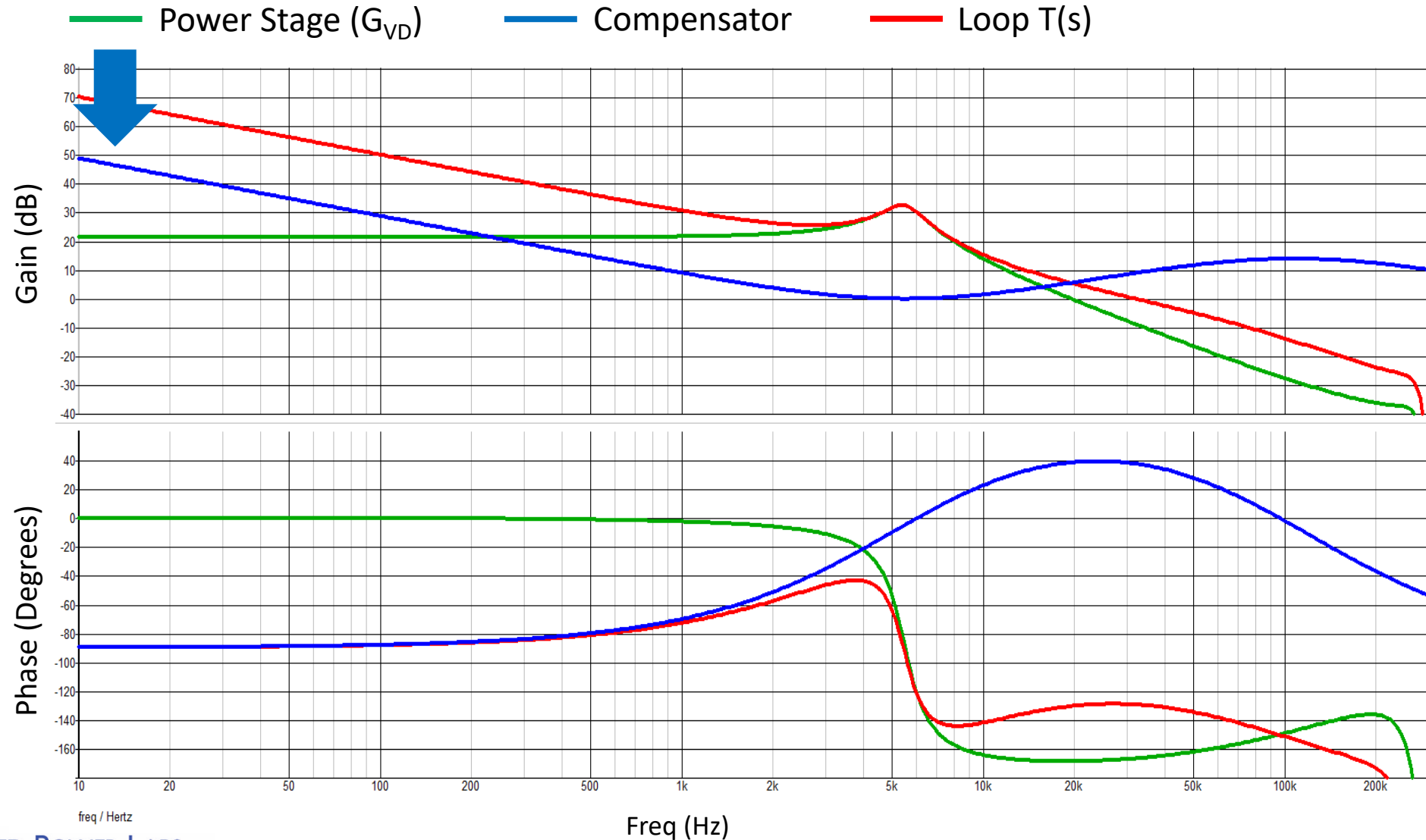

Example: Closed Loop Bode Plot

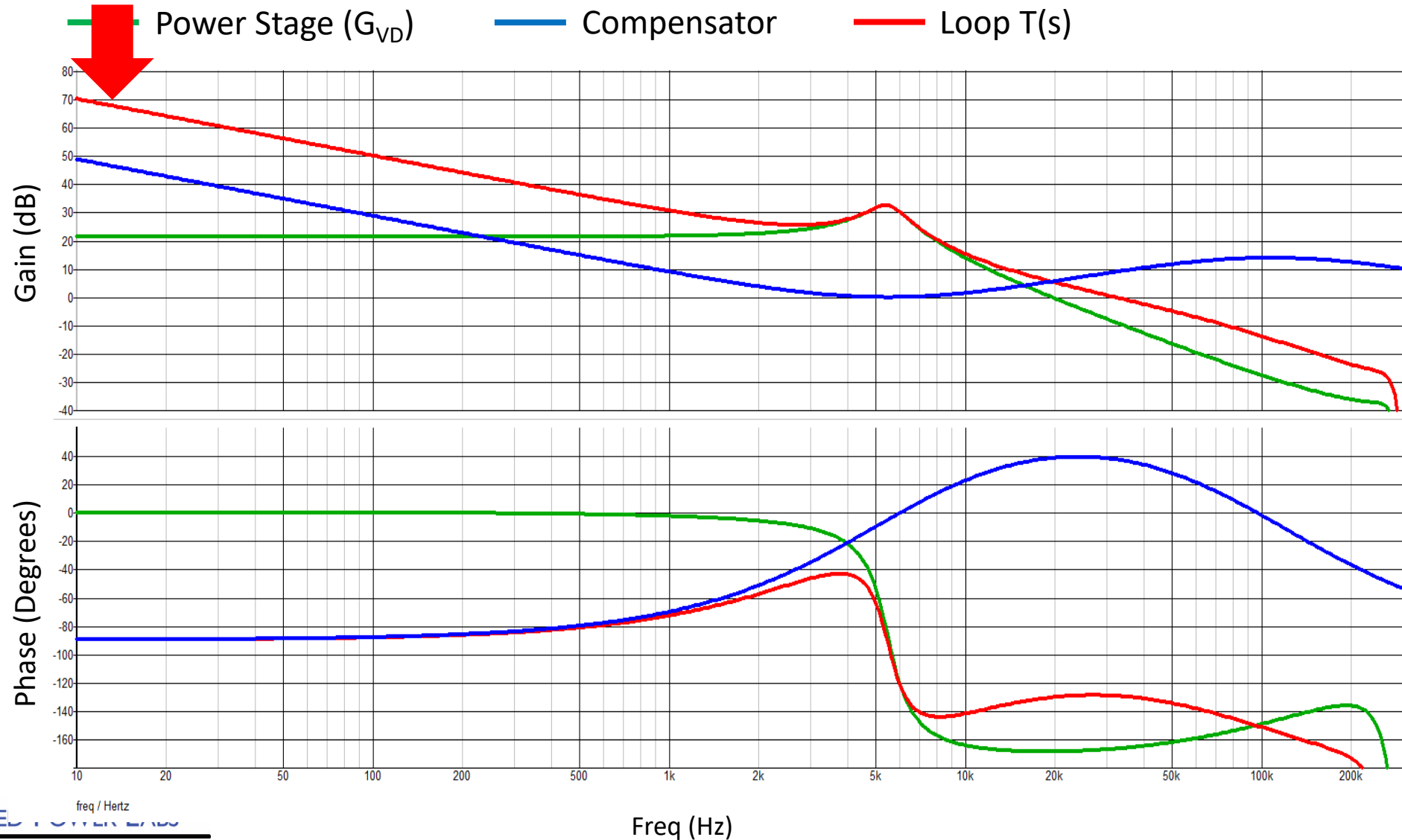

Example: Closed Loop Bode Plot

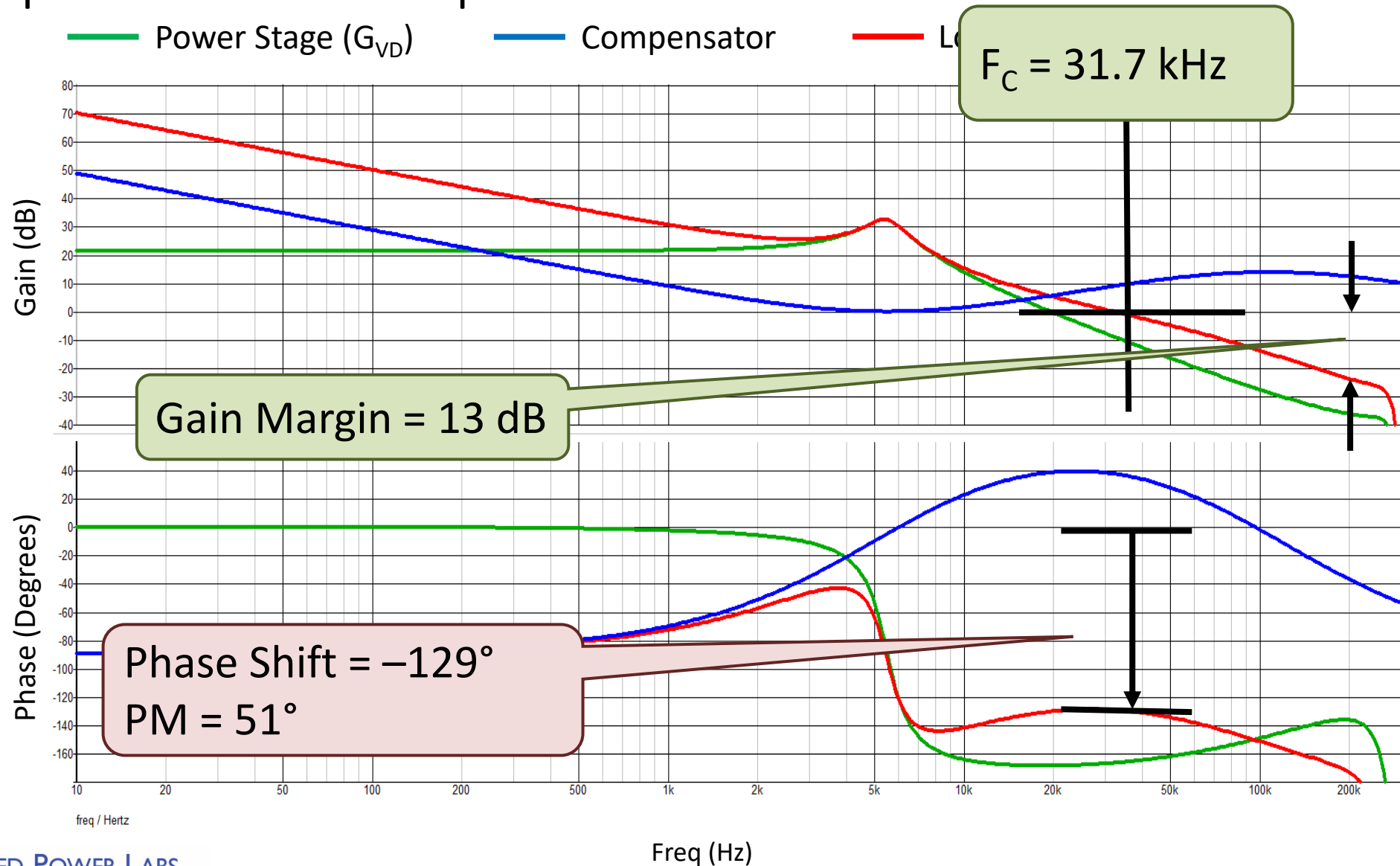

Where This Went Wrong

$$T(s) = K(s)$$


We Tried To Cancel Two Complex Poles..

$$T(s) = \frac{\omega_0}{s} \cdot \frac{1}{1 + \frac{s}{\omega_{HFP}}} = \left[\frac{\omega_{P0}}{s} \cdot \frac{\left(1 + \frac{s}{\omega_{Z1}}\right) \cdot \left(1 + \frac{s}{\omega_{Z2}}\right)}{\left(1 + \frac{s}{\omega_{P1}}\right) \cdot \left(1 + \frac{s}{\omega_{P2}}\right)} \right] \cdot \frac{1}{V_{RAMP}} \cdot \left[V_{IN} \cdot \frac{s + \frac{s}{\omega_{Z_ESR}}}{1 + \frac{1}{Q} \cdot \left(\frac{s}{\omega_{LC}}\right)^2} \right]$$

With Two Real Zeros

$$\left(\frac{V_{RAMP} \cdot \omega_0}{V_{IN}} \right) \cdot \frac{V_{IN}}{V_{RAMP}}$$


Example Bode Plot

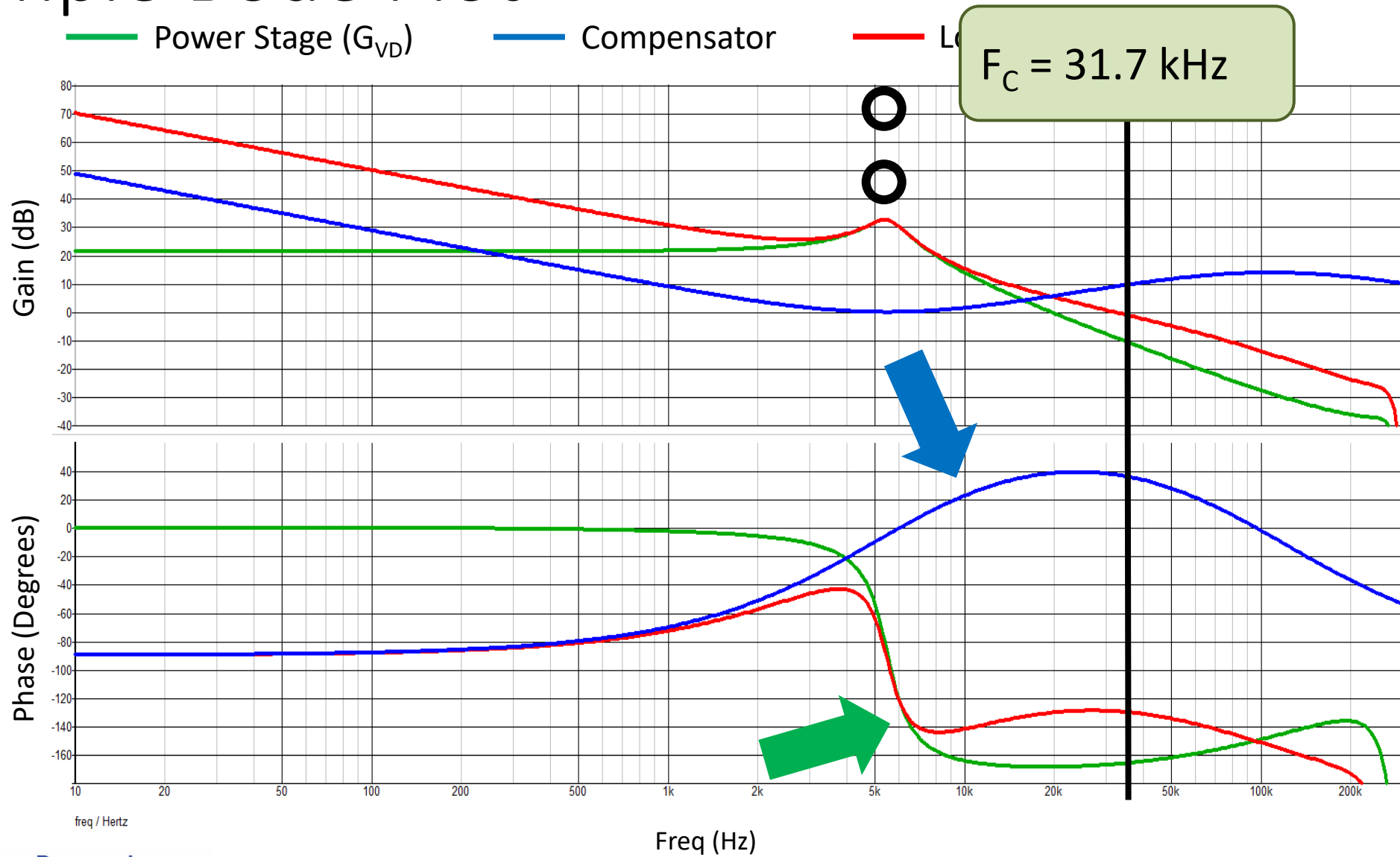

K-Factor Method

- A Popular Cookbook Method For Choosing Compensator Pole And Zero Locations
- Published By Dean Venable In 1983
 - "The K Factor: A New Mathematical Tool for Stability Analysis and Synthesis"; Proceedings of Powercon 10, March 1983
 - Reprints And App Notes Widely Available Through A Web Search

K-Factor Method

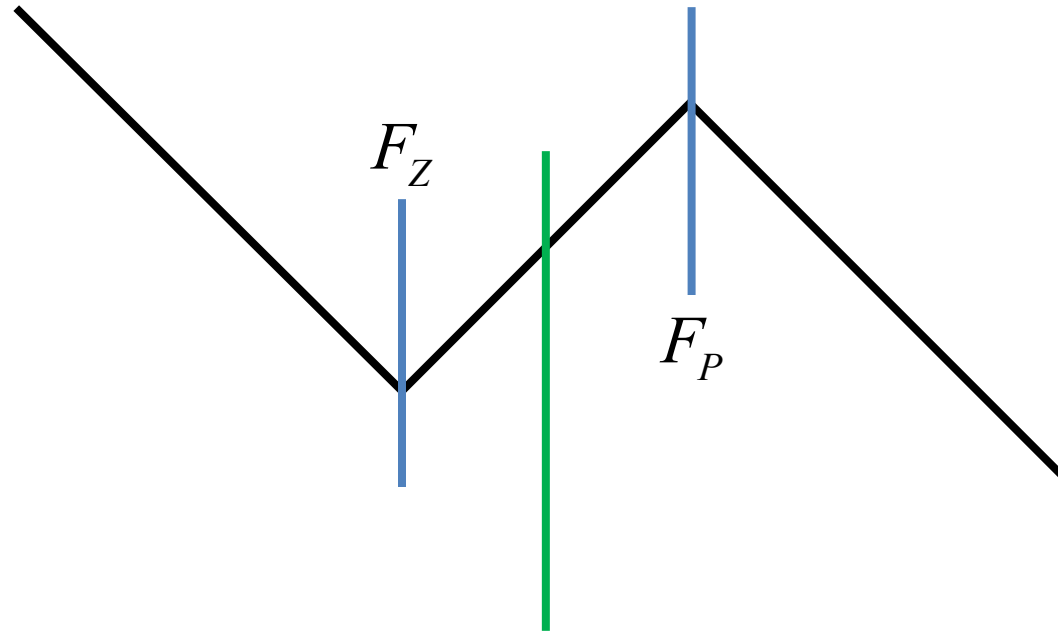

$$F_{MAX_BOOST} = \sqrt{F_Z \cdot F_P} = F_C$$

$$F_Z = \frac{F_C}{\sqrt{K}}$$

$$F_P = F_C \cdot \sqrt{K}$$

$$K = \left[\tan \left(\frac{Phase_Boost}{4} + 45^\circ \right) \right]^2$$

K-Factor Method Summary

- Choose Desired F_C And Phase Margin (PM)
- Examine $G_{VD}(s)$
 - Determine Phase Lag At F_C
 - Determine Gain At F_C
- Calculate Required Phase Boost At F_C
 - Phase Boost = $PM - \text{Phase}(G_{VD}(F_C)) - 90^\circ$
- Calculate K-Factor
- Calculate F_Z And F_P
- Calculate Component Values As Function Of F_Z , F_P , And Required Gain

K-Factor Example

- $F_C = 30 \text{ kHz}$, $PM = 70^\circ$
- $G_{VD}(F_C)$: Phase = -167° ,
Gain = -7.7 dB (0.412)
- Phase Boost = $70^\circ - (-167^\circ) - 90^\circ = 147^\circ$
- Calculate K-Factor

$$K = \left[\tan\left(\frac{147^\circ}{4} + 45^\circ\right) \right]^2 = 47.6$$

- Calculate F_Z And F_P

$$F_Z = \frac{F_C}{\sqrt{K}} = \frac{30 \text{ kHz}}{\sqrt{47.6}} = 4.350 \text{ kHz}$$

$$F_P = F_C \cdot \sqrt{K} = 30 \text{ kHz} \cdot \sqrt{47.6} = 206.9 \text{ kHz}$$

K-Factor Example

- Component Values Are:

$$R2 = 8.04 \text{ k}\Omega$$

$$R4 = 24.9 \text{ k}\Omega$$

$$R1 = 174 \Omega$$

$$C1 = 4.3 \text{ nF}$$

$$C2 = 270 \text{ pF}$$

$$R3 = 3.09 \text{ k}\Omega$$

$$C3 = 12 \text{ nF}$$

- Desired And Actual Frequencies

$$F_{P0} = 1.527 \text{ kHz}$$

$$F_Z = 4.35 \text{ kHz}$$

$$F_P = 206.9 \text{ kHz}$$

$$F_{P0} = 1.609 \text{ kHz}$$


$$F_{Z1} = 4.292 \text{ kHz}$$

$$F_{Z2} = 4.495 \text{ kHz}$$


$$F_{P1} = 212.7 \text{ kHz}$$

$$F_{P2} = 195.1 \text{ kHz}$$


K-Factor Example: Simulated Compensator

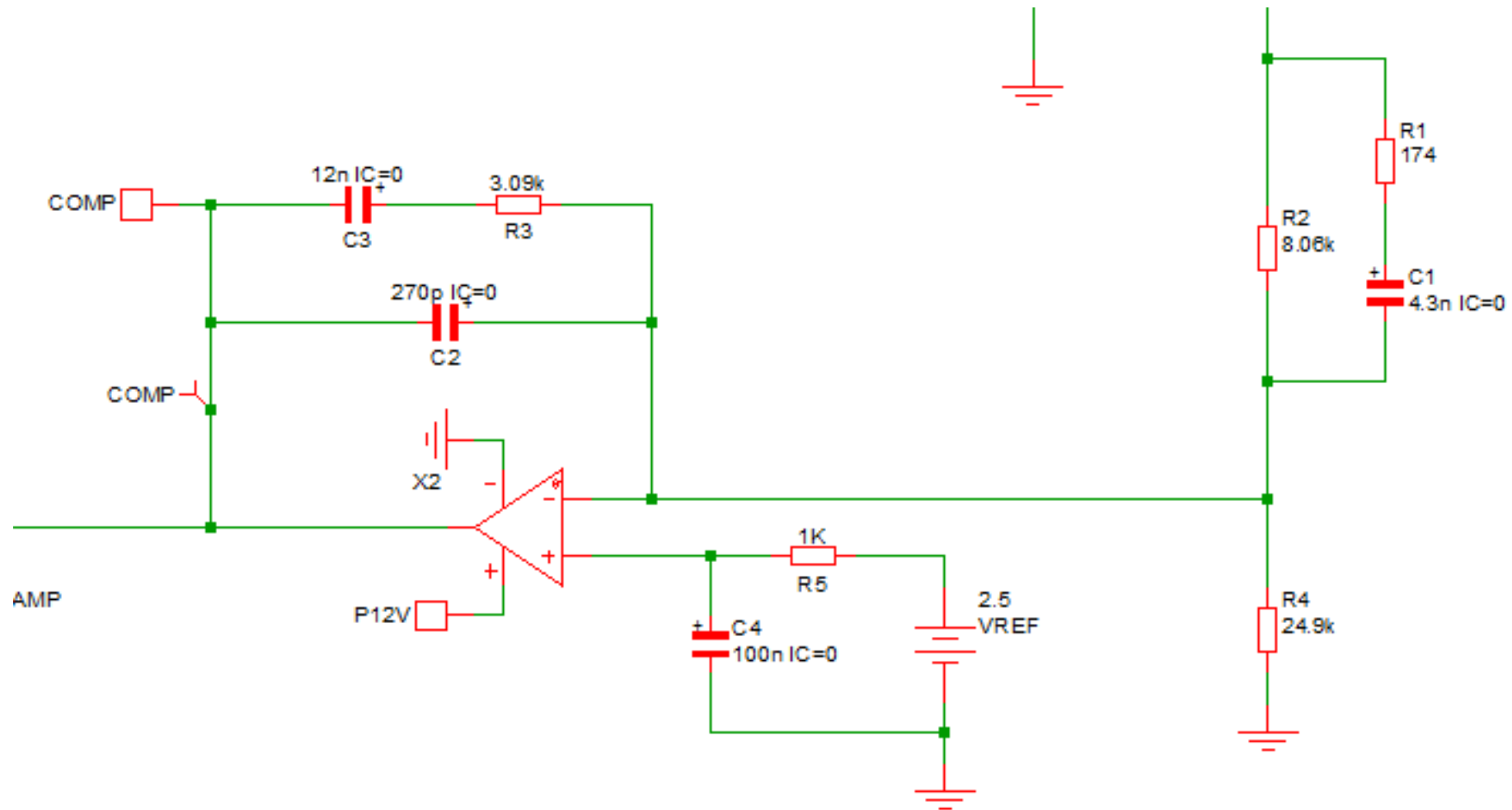


K-Factor Example: Simulation Bode Plot

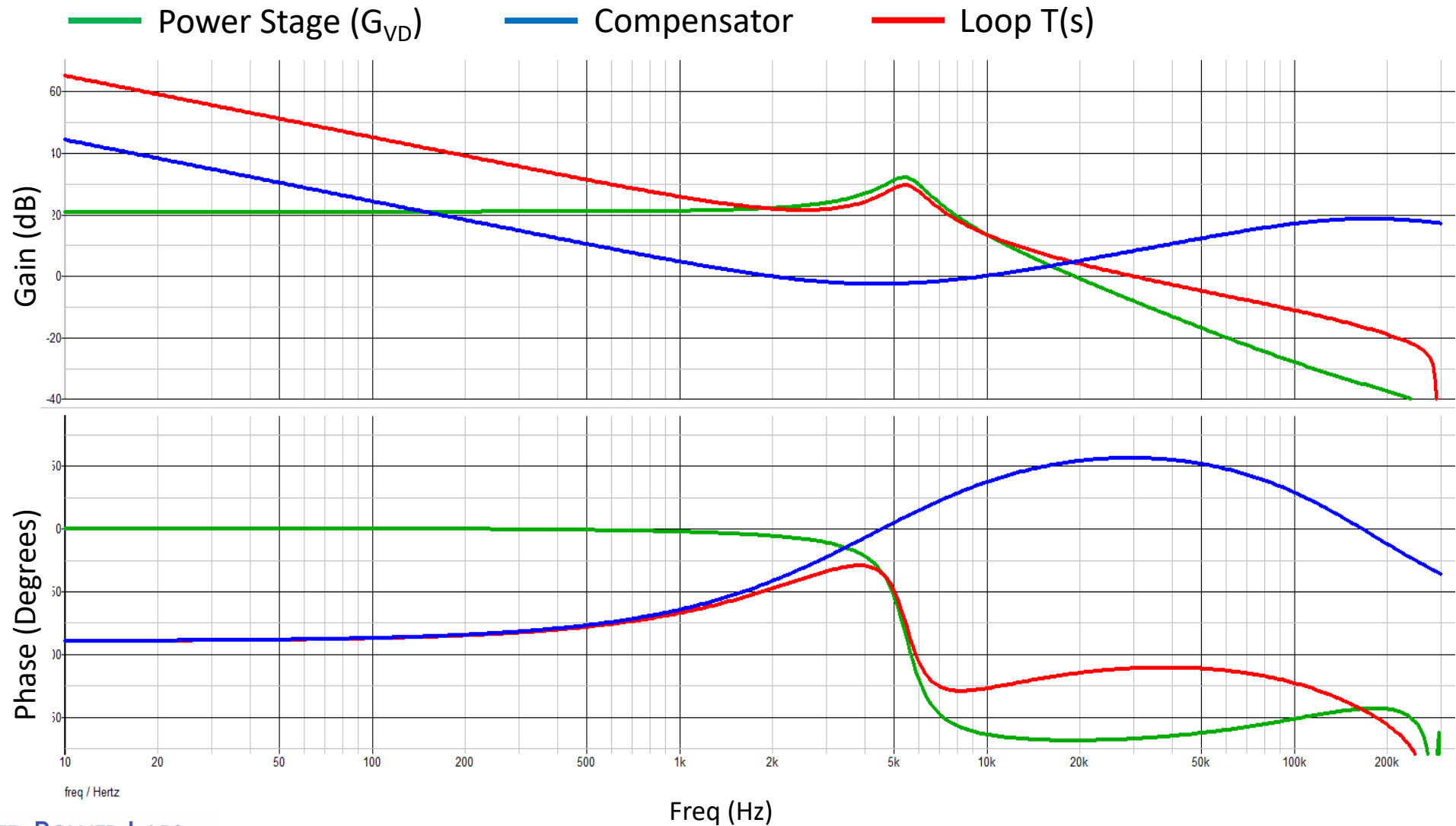

K-Factor Example: Simulation Bode Plot

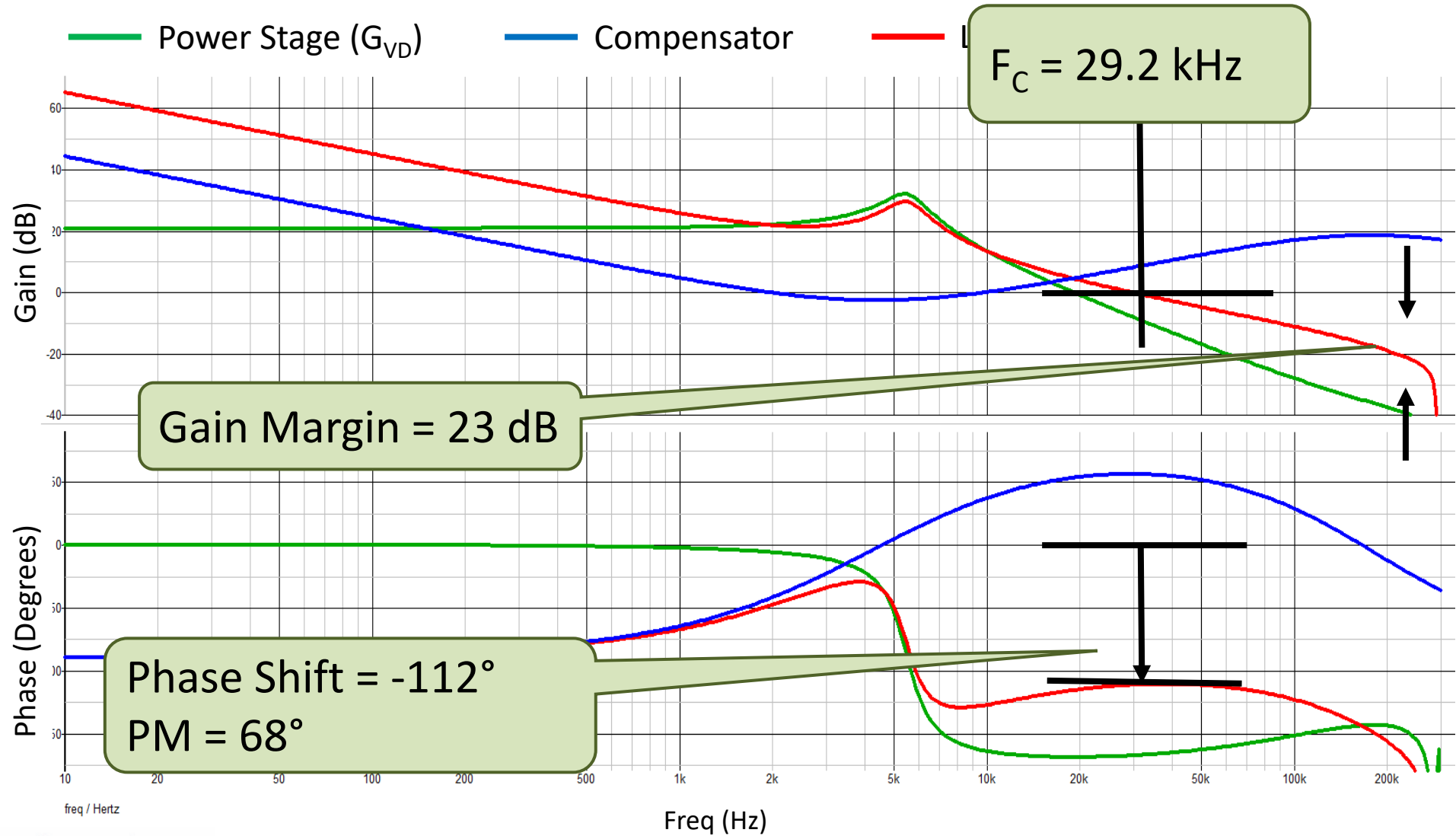

K-Factor Example: Caveats

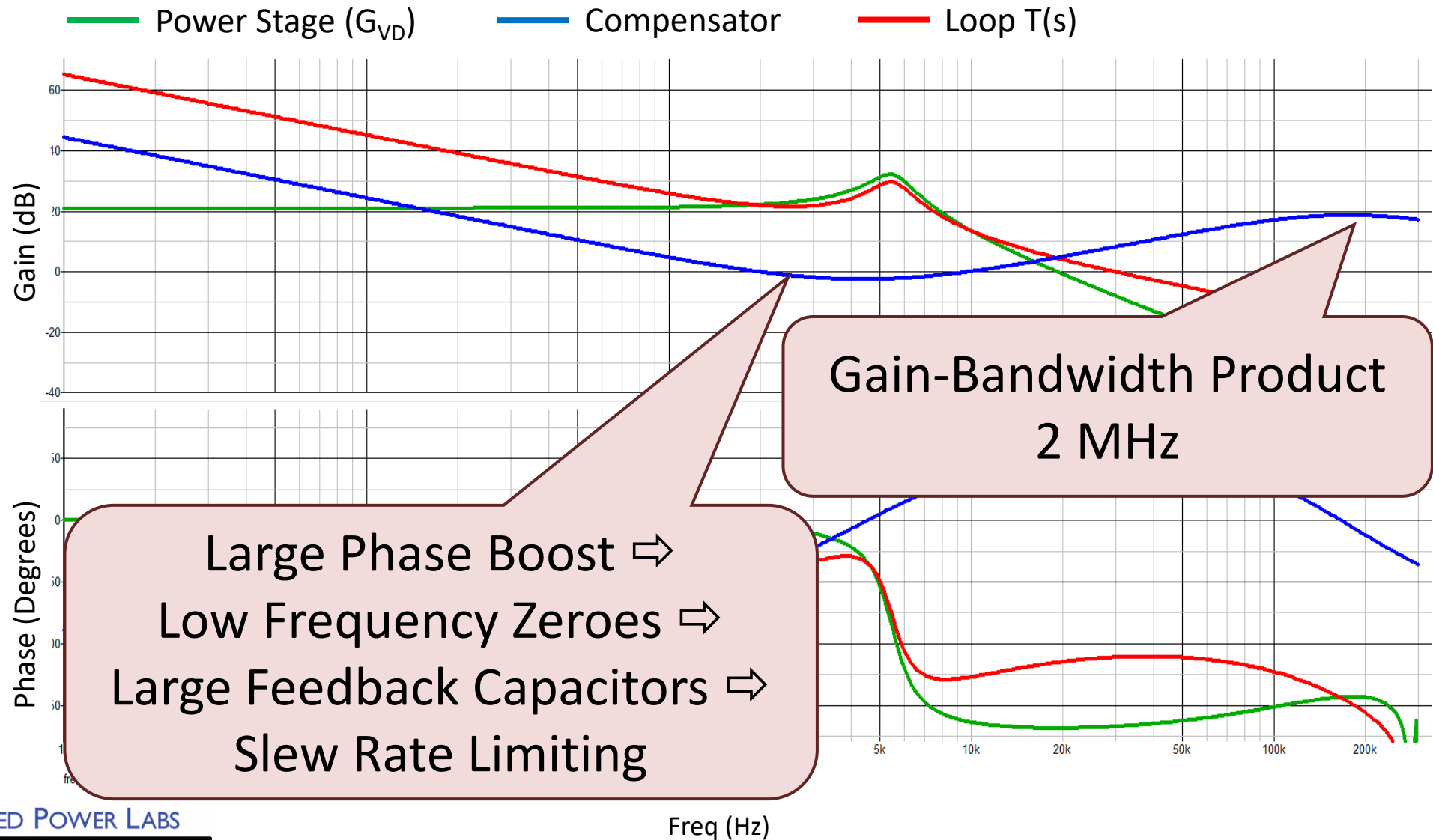

Loop Design Considerations

- Loop Characteristics Typically Vary A Lot!
 - Variations In G_{VD} With Input Voltage And Load
 - Tolerance Of Components In Output Filter And Compensator
 - Variation In Crossover Frequency Of One Octave Common

Loop Design Considerations

- Loop Characteristics Typically Vary A Lot!
 - Variations In G_{VD} With Input Voltage And Load
 - Tolerance Of Components In Output Filter And Compensator
 - Variation In F_c Of One Octave Common



You MUST Do
Some Kind Of
Worst Case
Analysis

You MUST
Measure
The Loop

Other Compensators And Modulators


Other Standard Compensators

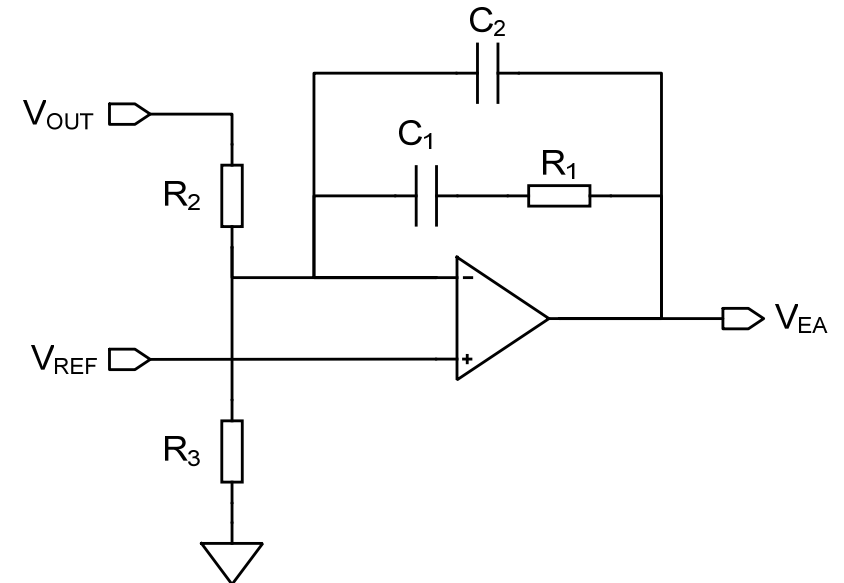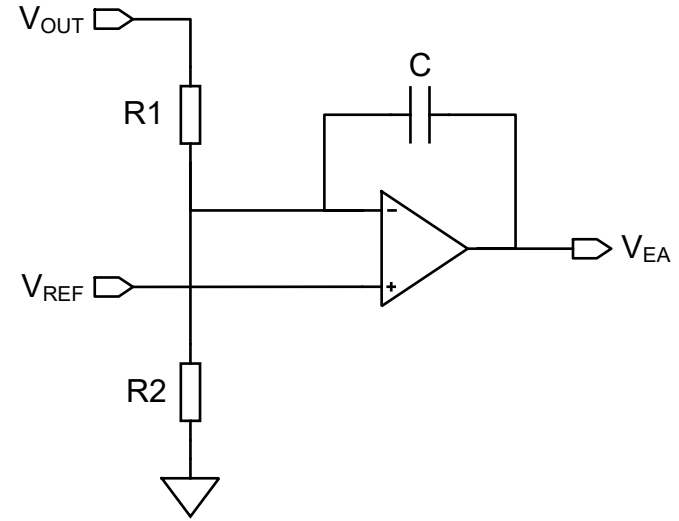- How Much Phase Boost Needed?
 - Type I: No Phase Boost
 - Integrator Pole Only
 - Type II: Up To 90° Phase Boost
 - Integrator Pole
 - One Zero And One Pole
 - Type III: Up To 180° Phase Boost
 - Integrator Pole
 - Two Zeros And Two Poles
- See Appendices For Details



PID Compensator

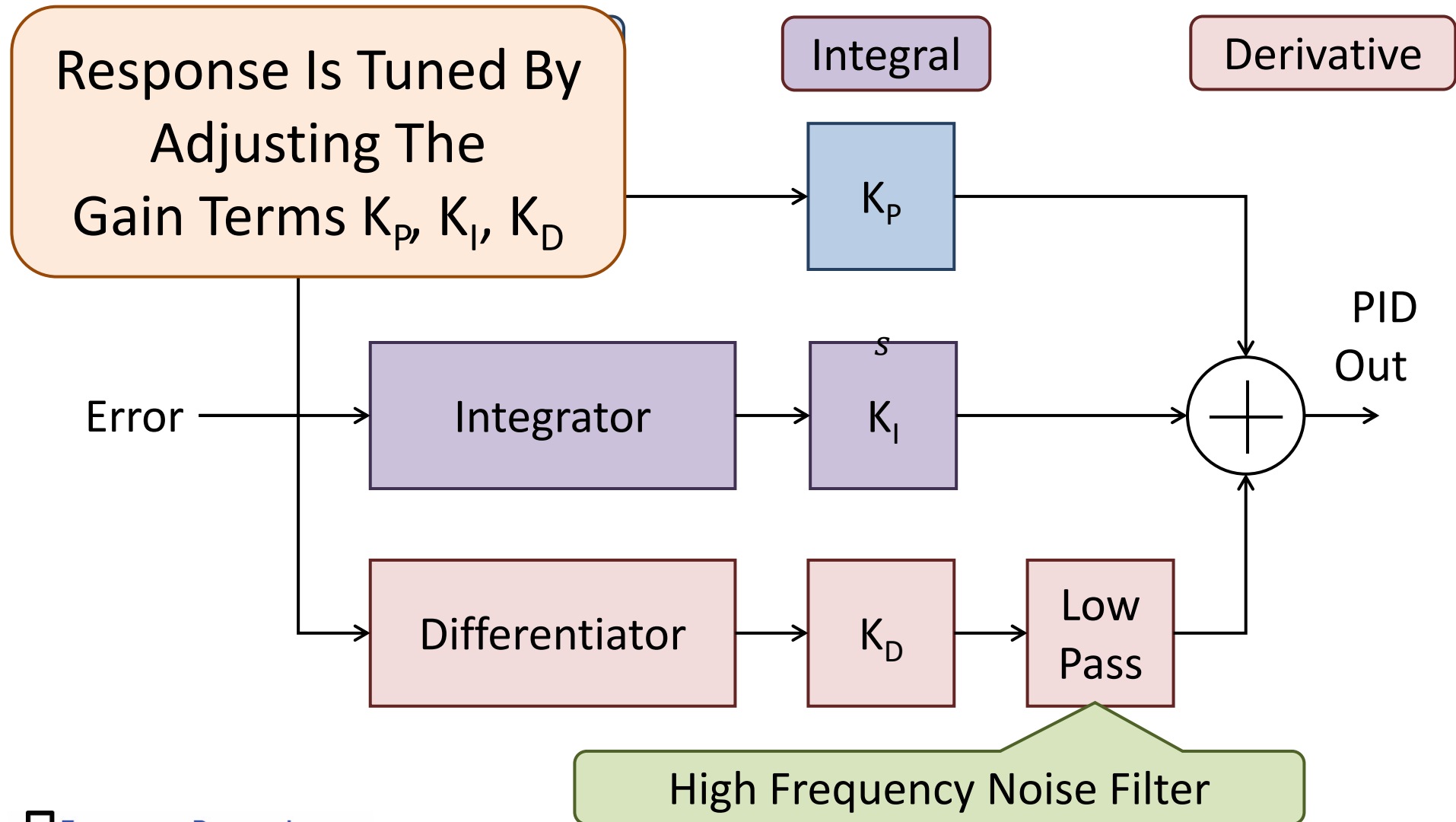
$$H_{PID}(s) = K_P + K_I \cdot \frac{1}{s} + K_D \cdot s$$



PID Compensator


- PID Loved By Academics
 - Good Commercial Applications Are Limited
- Good For “One Of” Designs Where Plant Characteristics Are Not Well Known
 - Examples: Motor Drive, Industrial Processes
- Various Tuning Algorithms
 - e.g. Ziegler-Nichols

Analog Pulse Width Modulator


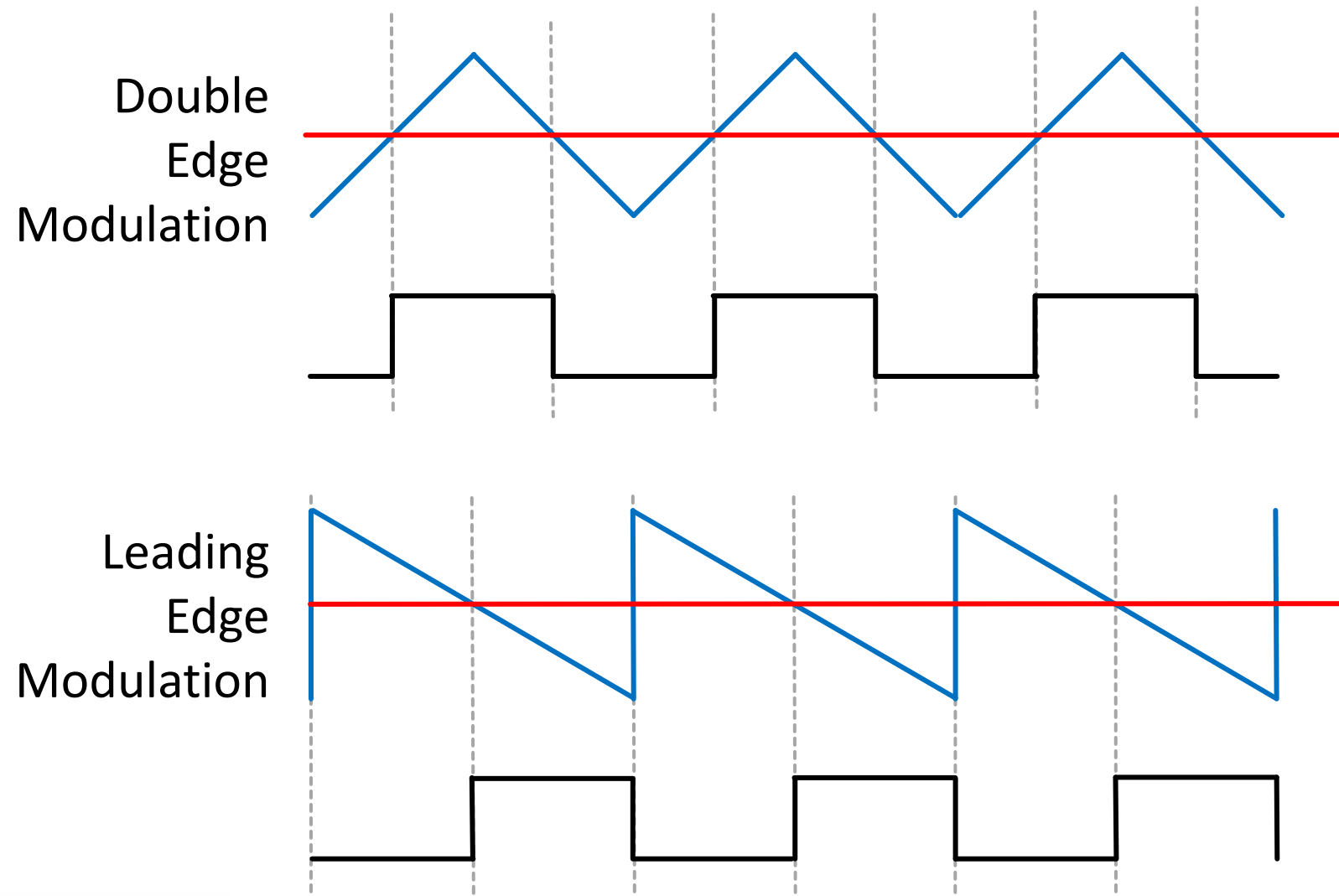


Video Lab 10: Leading Edge And Double Edge PWM

Double Edge Modulation

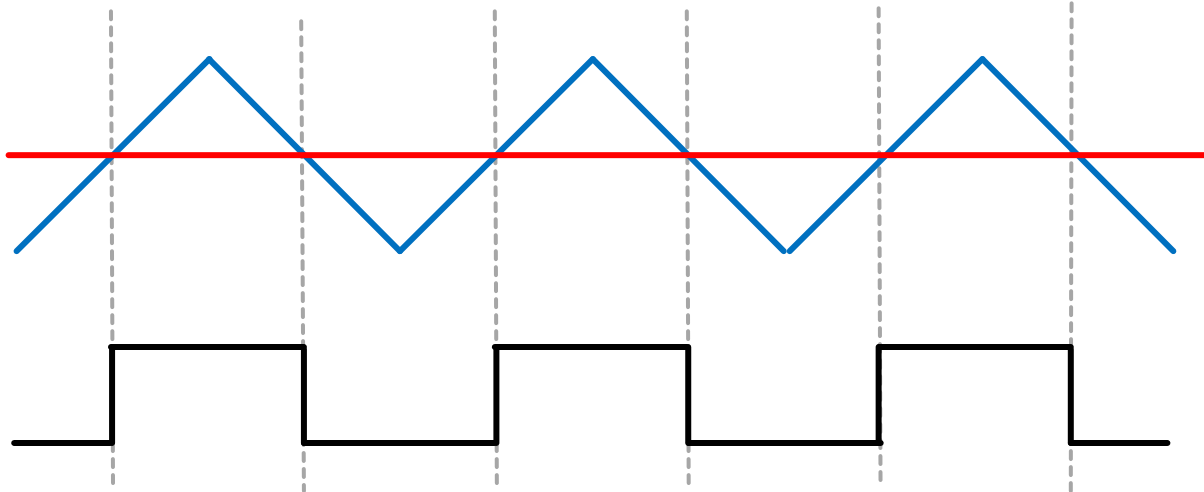


Leading Edge Modulation

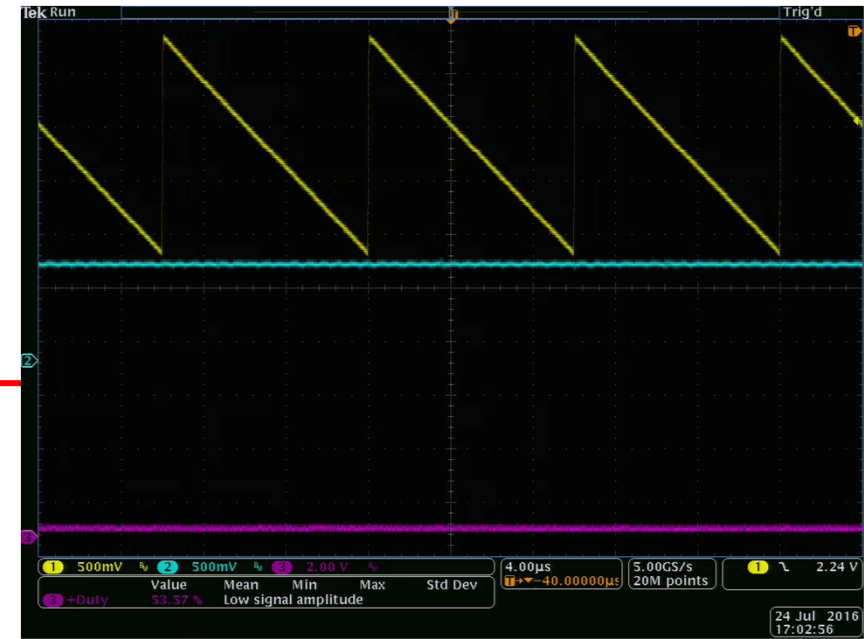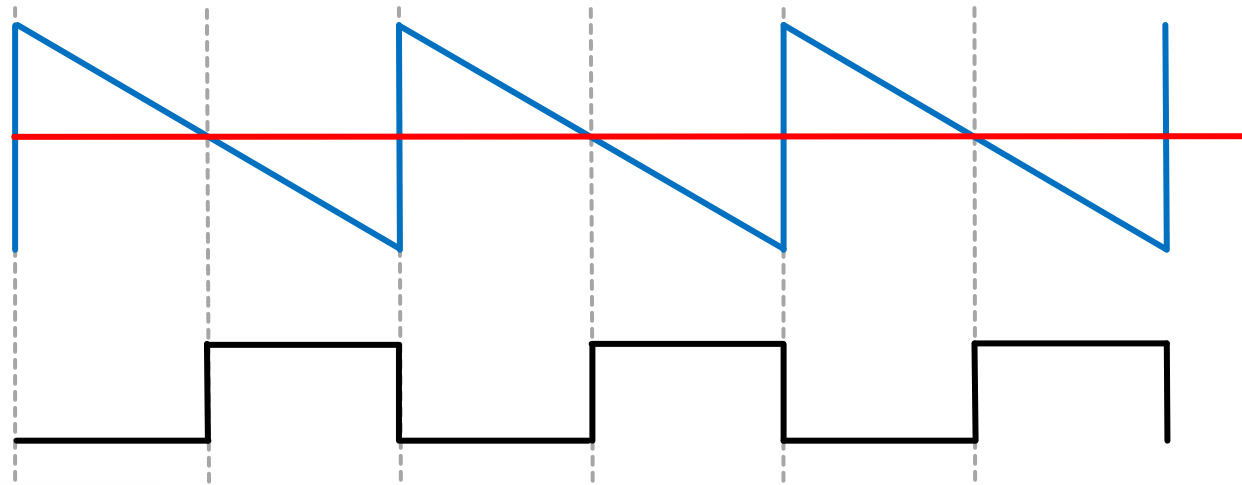


Variable Frequency Modulators


Constant Duty Cycle, Variable Frequency

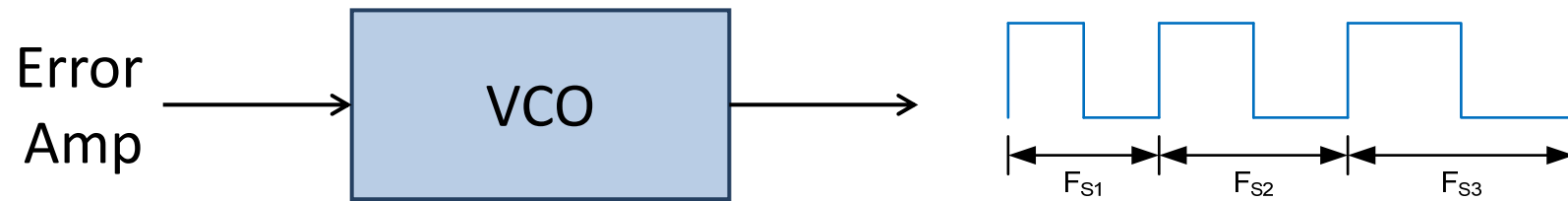

Constant On Time

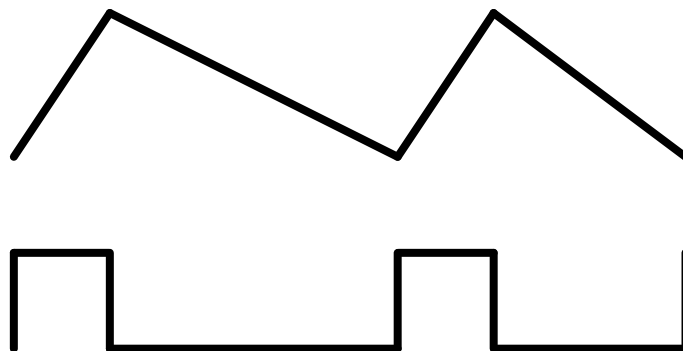


Constant Off Time

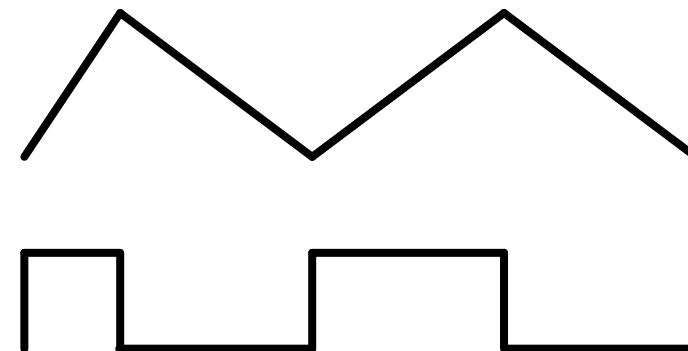


Current Mode Control Overview


Analog PWM Reminder

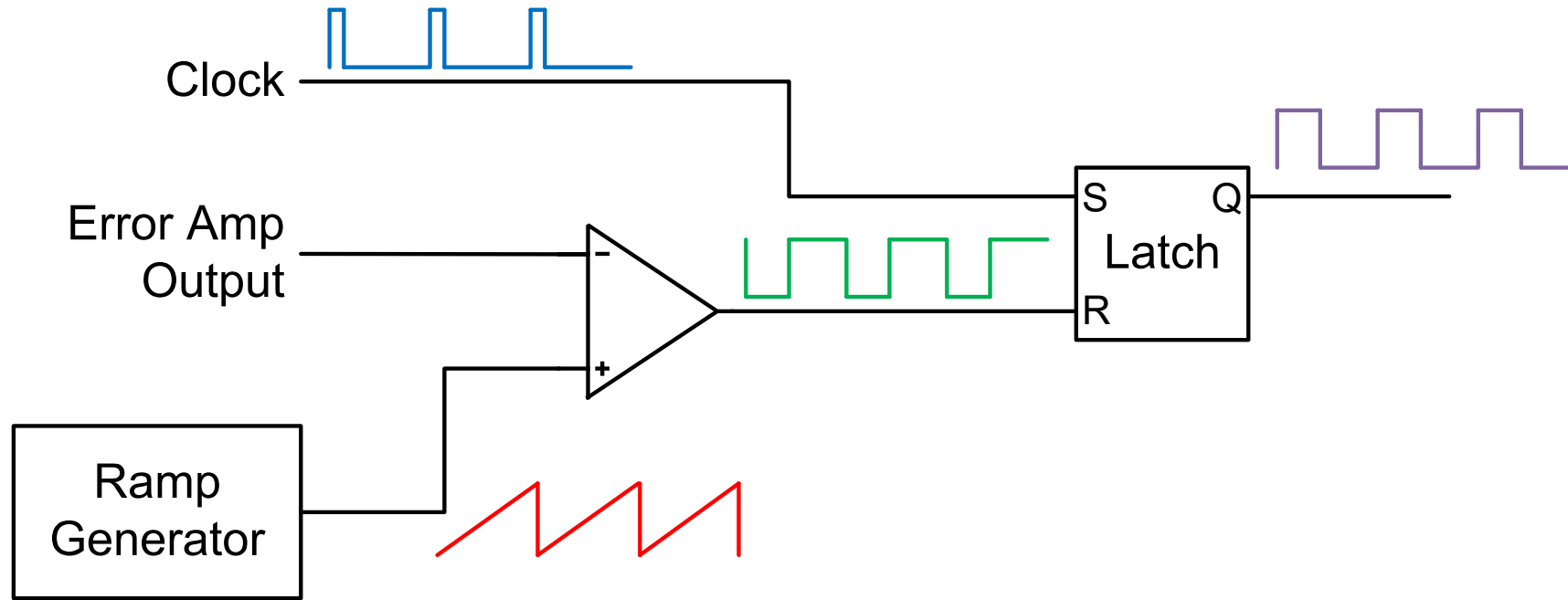


Peak Current Mode Control

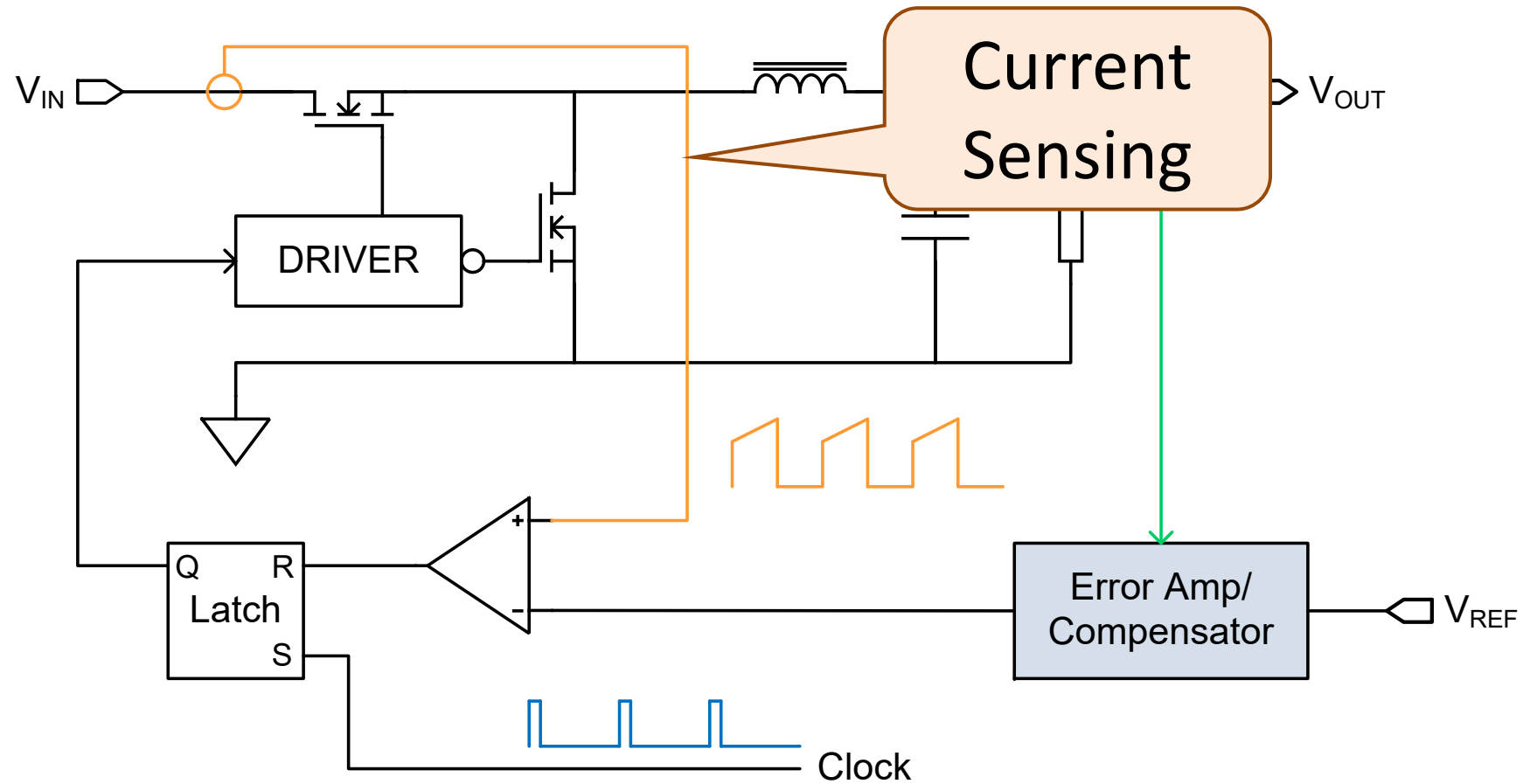


Peak Current Mode Control

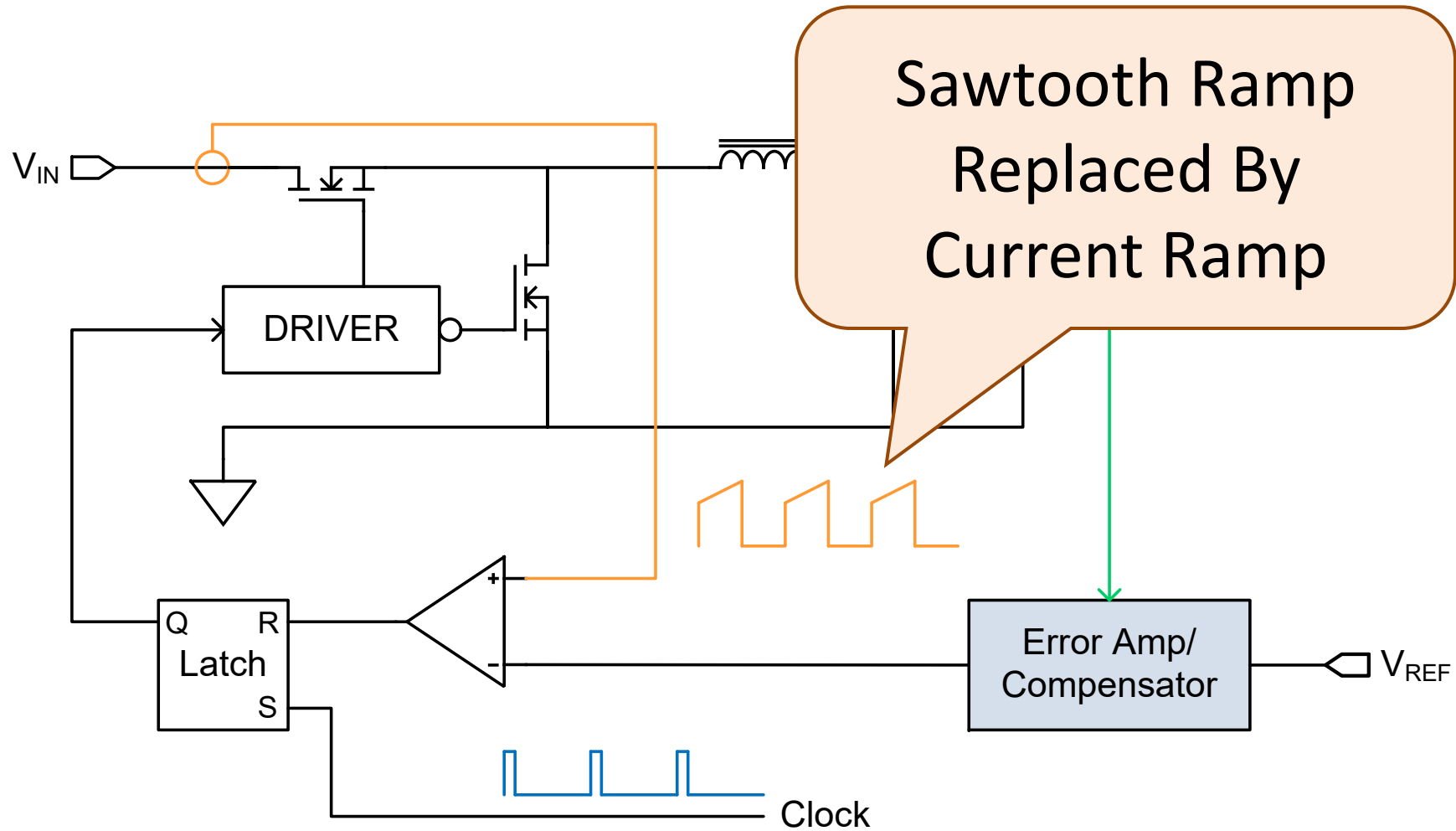


Peak Current Mode Control

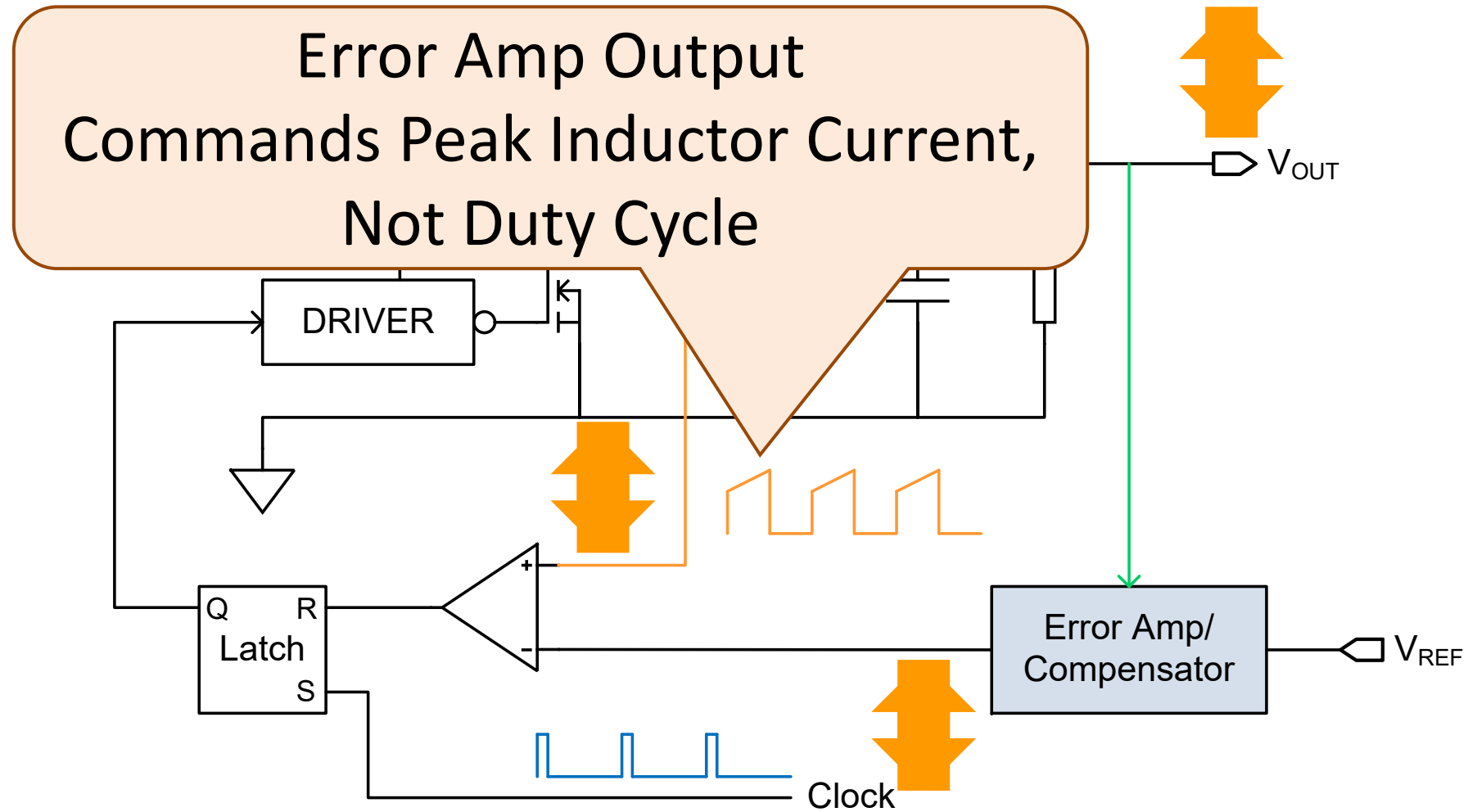


Peak Current Mode Control

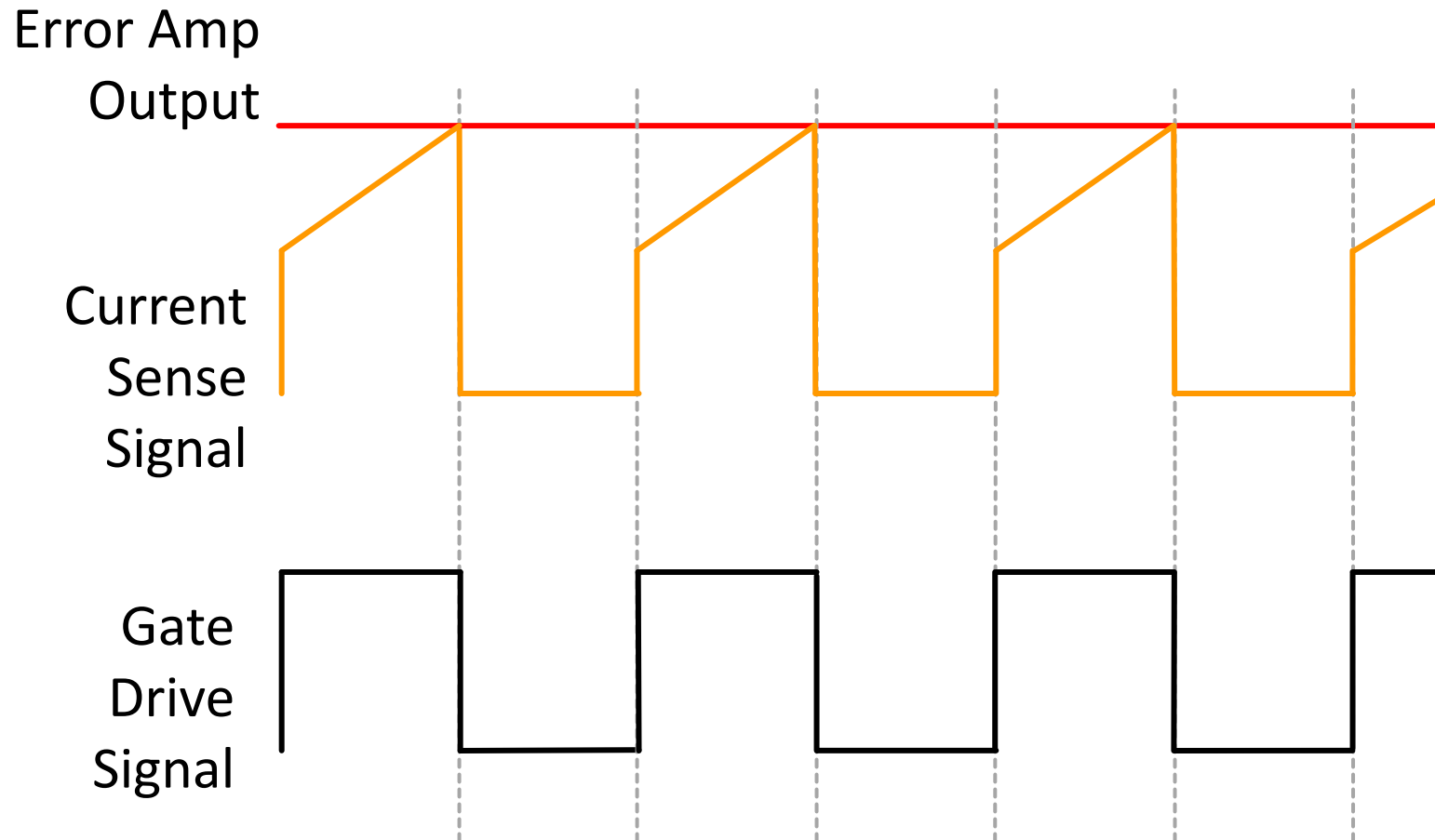

Feed Forward

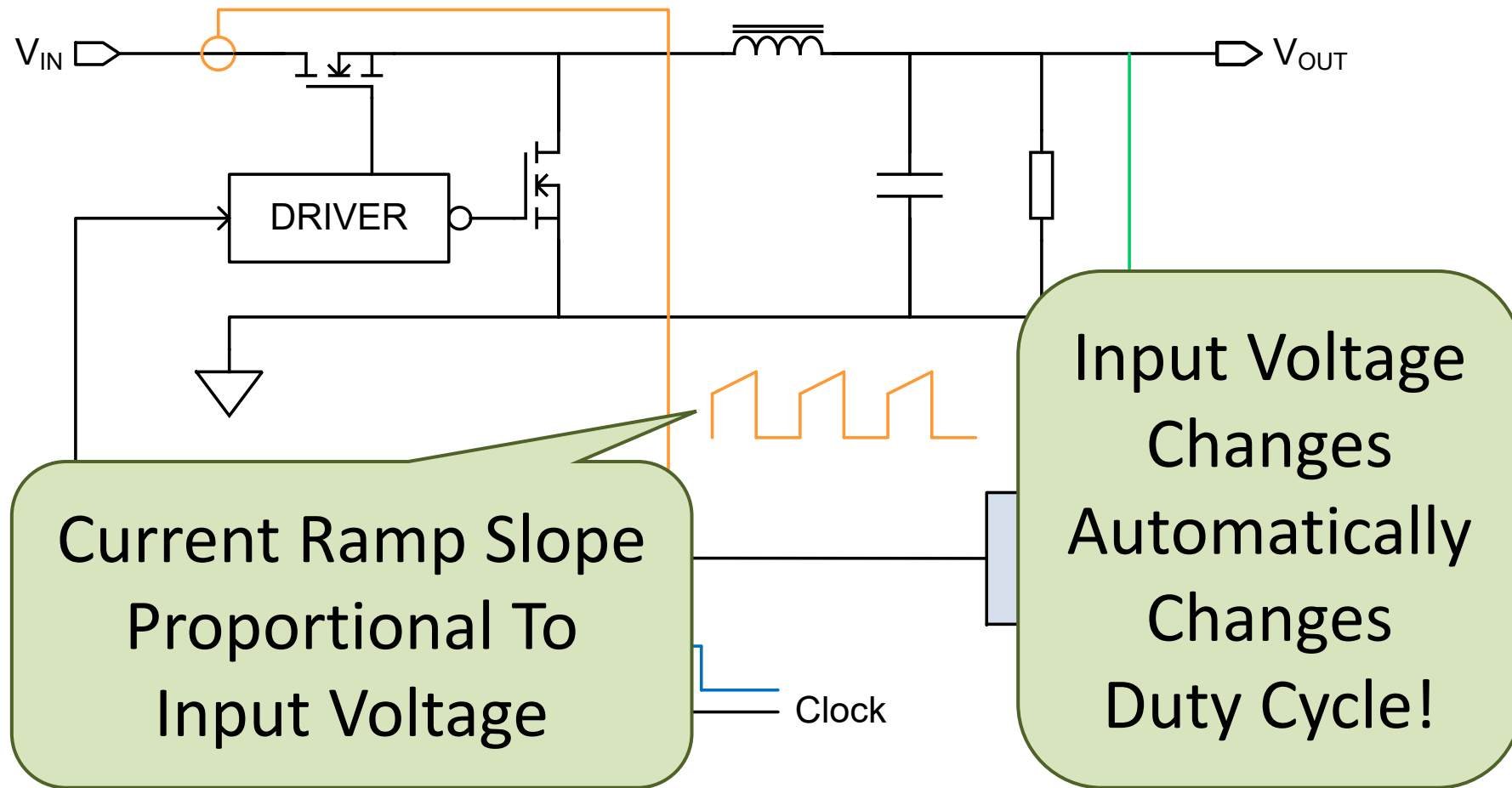

Control Characteristic G_{vC}

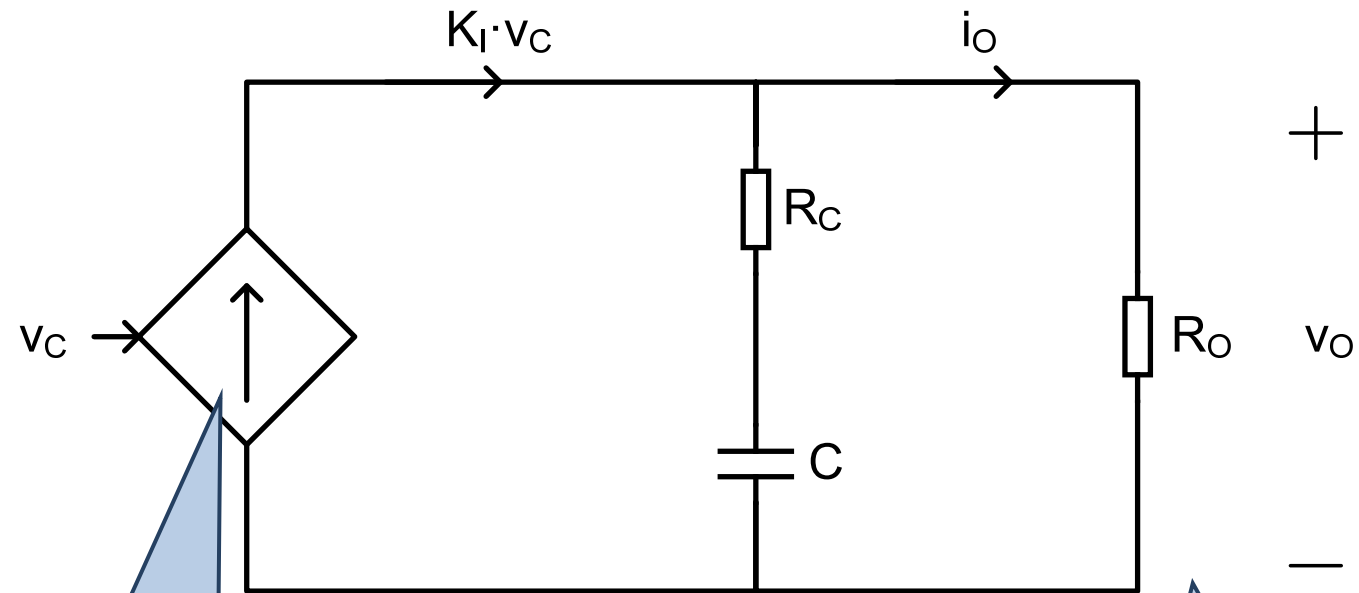

Programmable
Current Source
 $I = K_I \cdot v_C$

Filter Capacitor
And ESR

Load
Resistance

Control Characteristic G_{VC}


$$v_o(s) = K_I \cdot v_c(s) \cdot Z_o(s)$$

$$G_{VC}(s) = \frac{v_o(s)}{v_c(s)} = K_I \cdot Z_o(s)$$

$$G_{VC}(s) = K_I \cdot R_o \cdot \frac{1 + s \cdot R_c \cdot C}{1 + s \cdot (R_c + R_o) \cdot C}$$


$$G_{VC}(s) = G_o \cdot \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}}$$

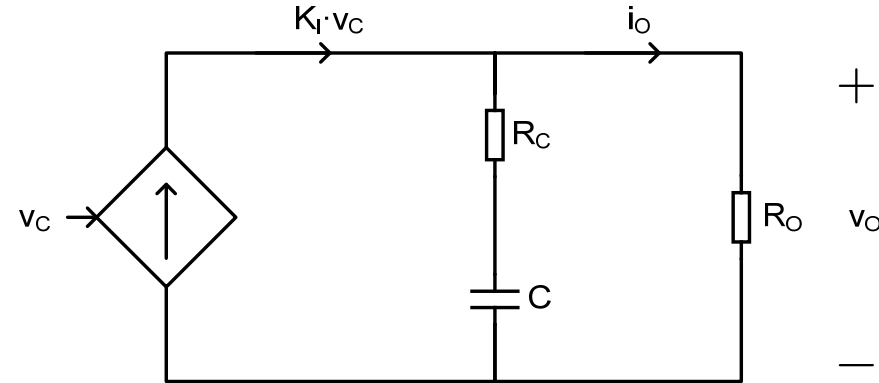$\omega_z = \frac{1}{R_c \cdot C}$
 $\omega_p = \frac{1}{(R_c + R_o) \cdot C} \approx \frac{1}{R_o \cdot C}$




Control Characteristic G_{VC}

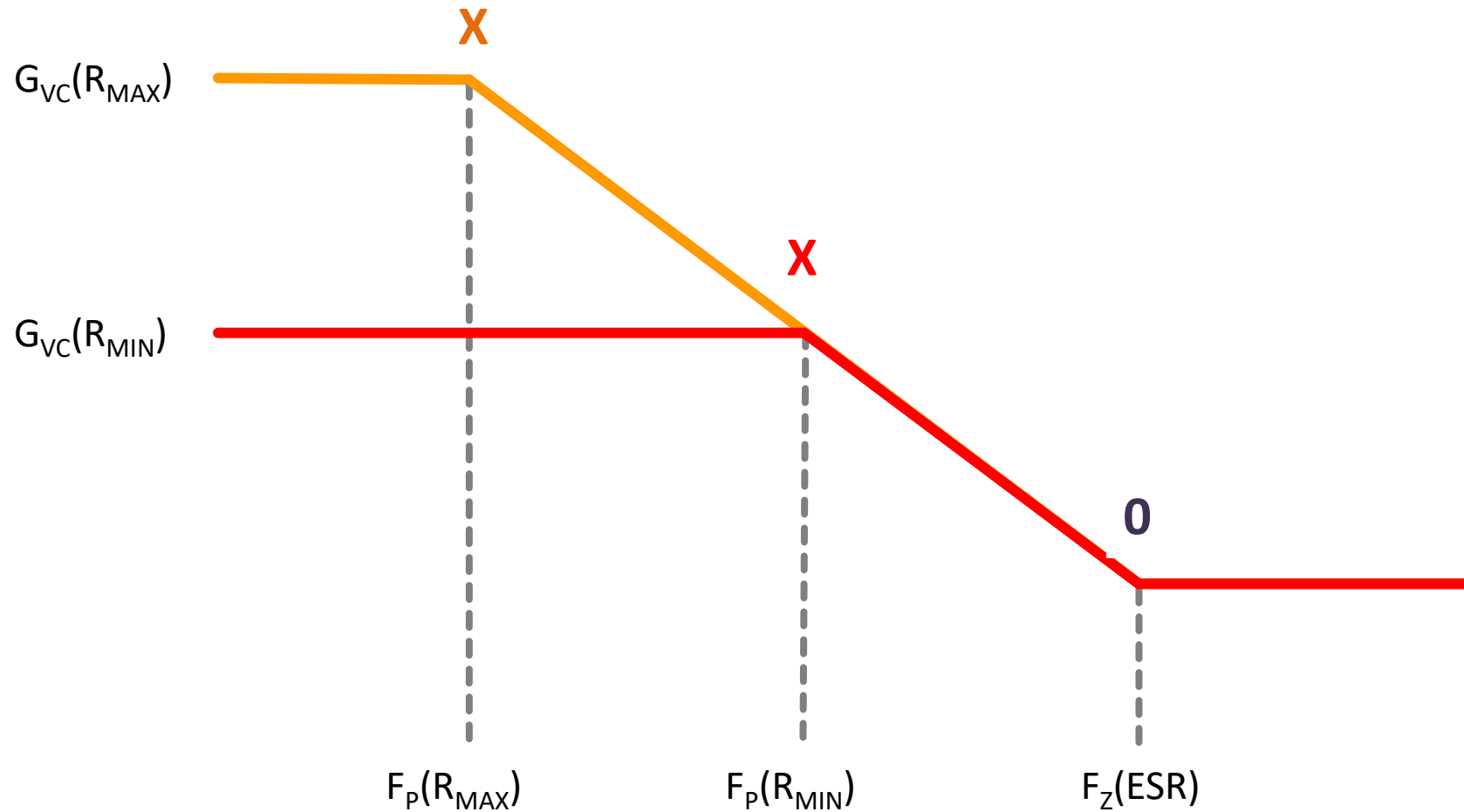
$$G_{VC}(s) = G_O \cdot \frac{1 + \frac{s}{\omega_Z}}{1 + \frac{s}{\omega_P}} = K_I \cdot R_O \cdot \frac{1 + \frac{s}{\omega_Z}}{1 + \frac{s}{\omega_P}}$$




Compensator H_{EA}

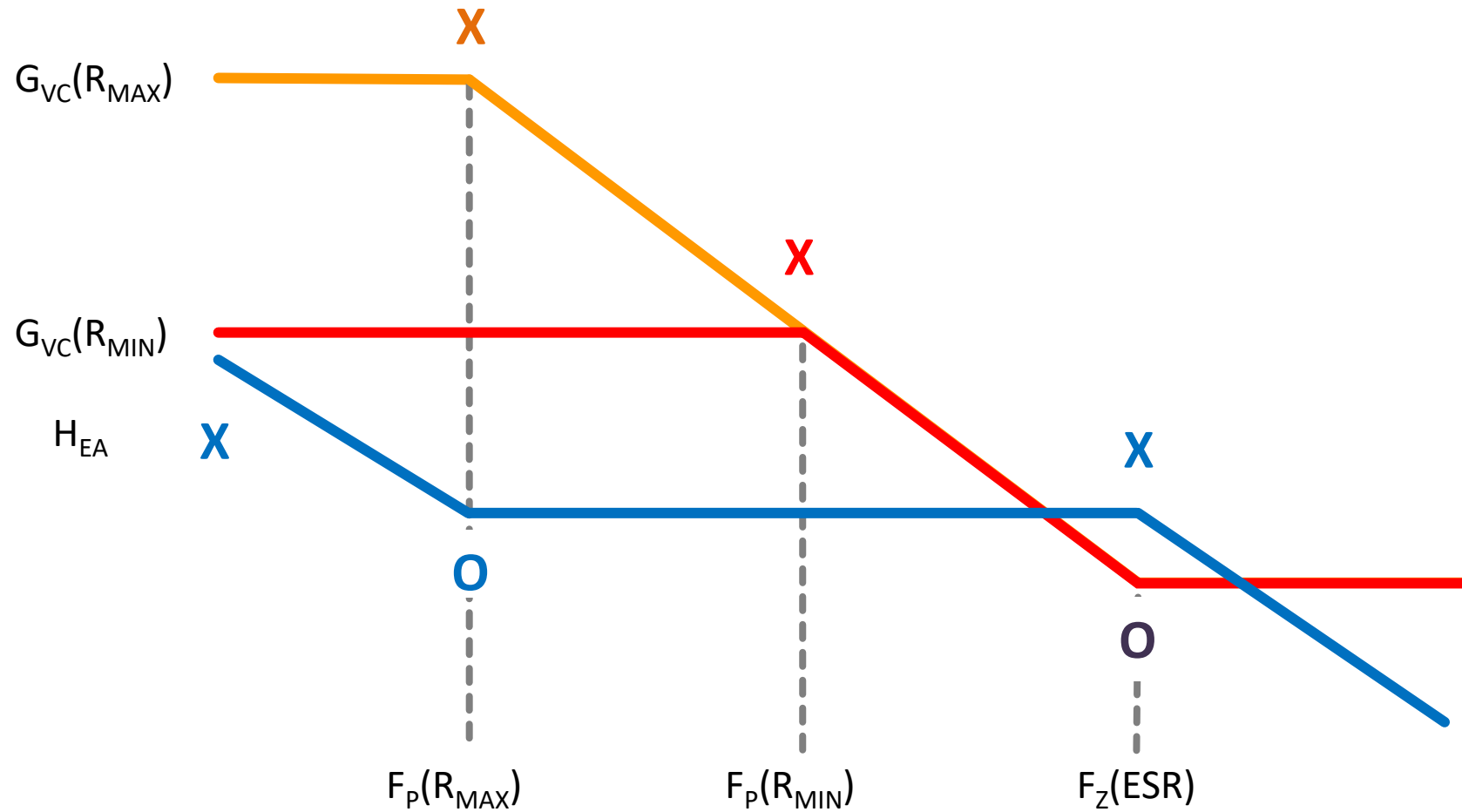


Loop Gain T(s)

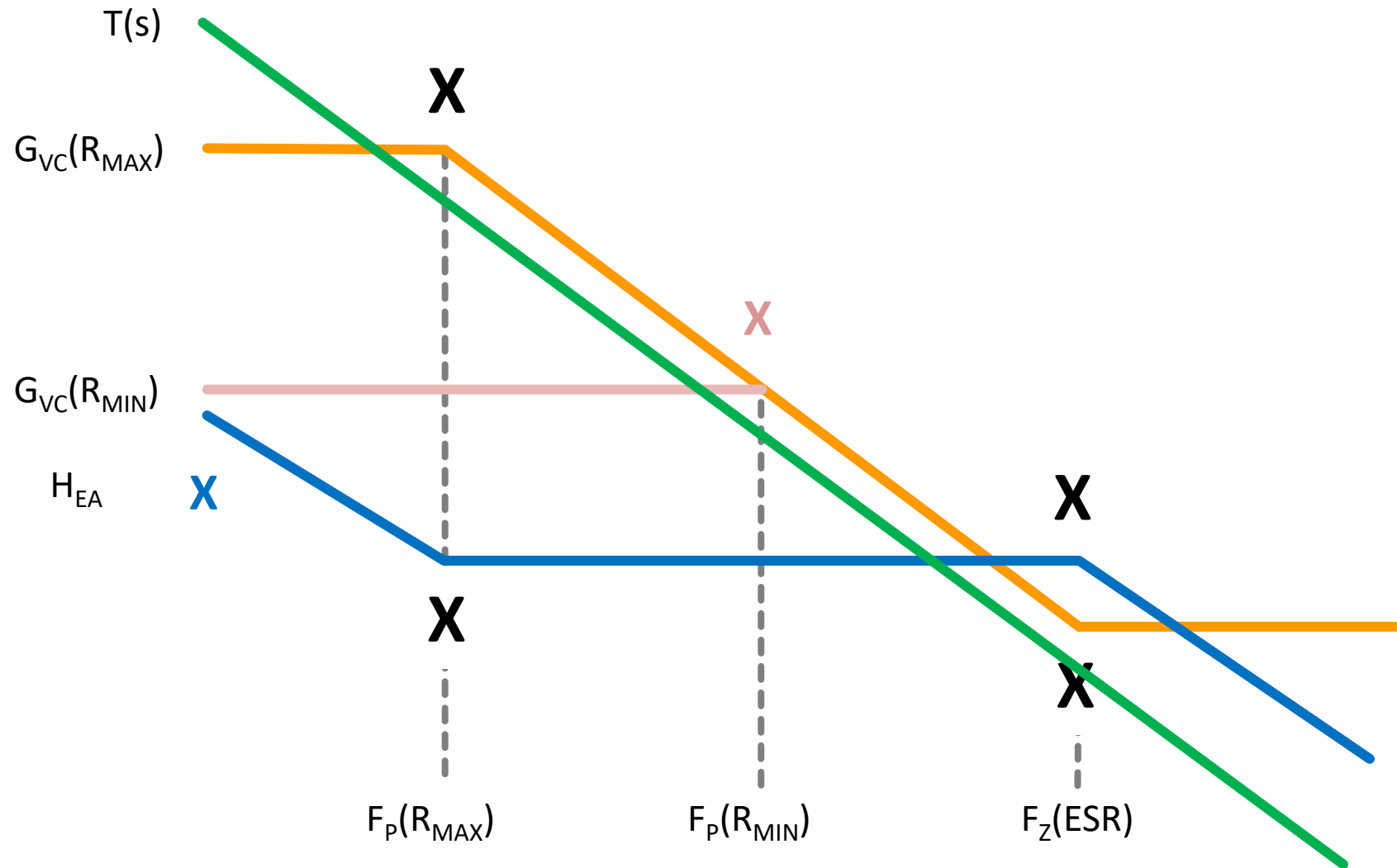


Loop Gain T(s)

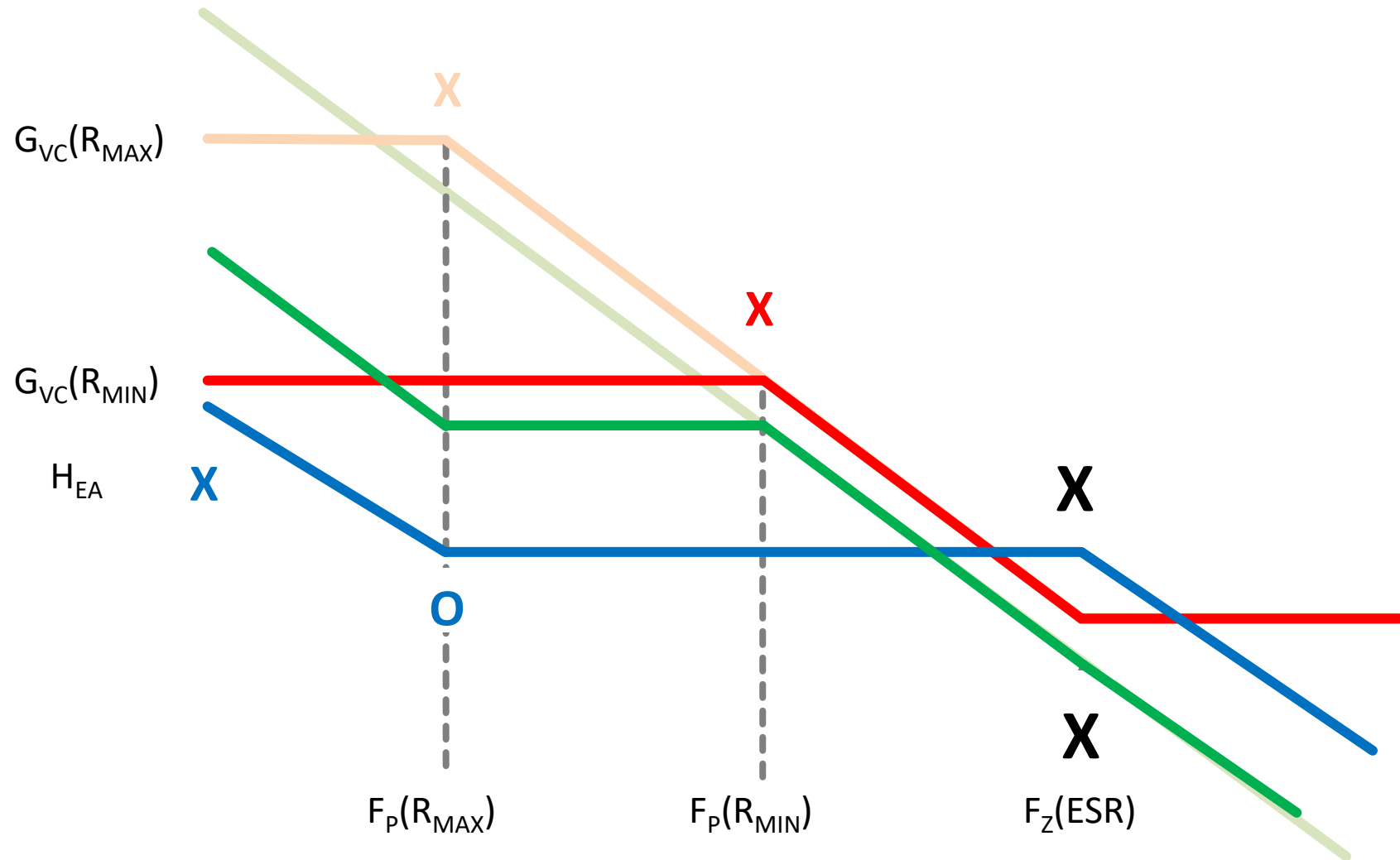

Loop Gain T

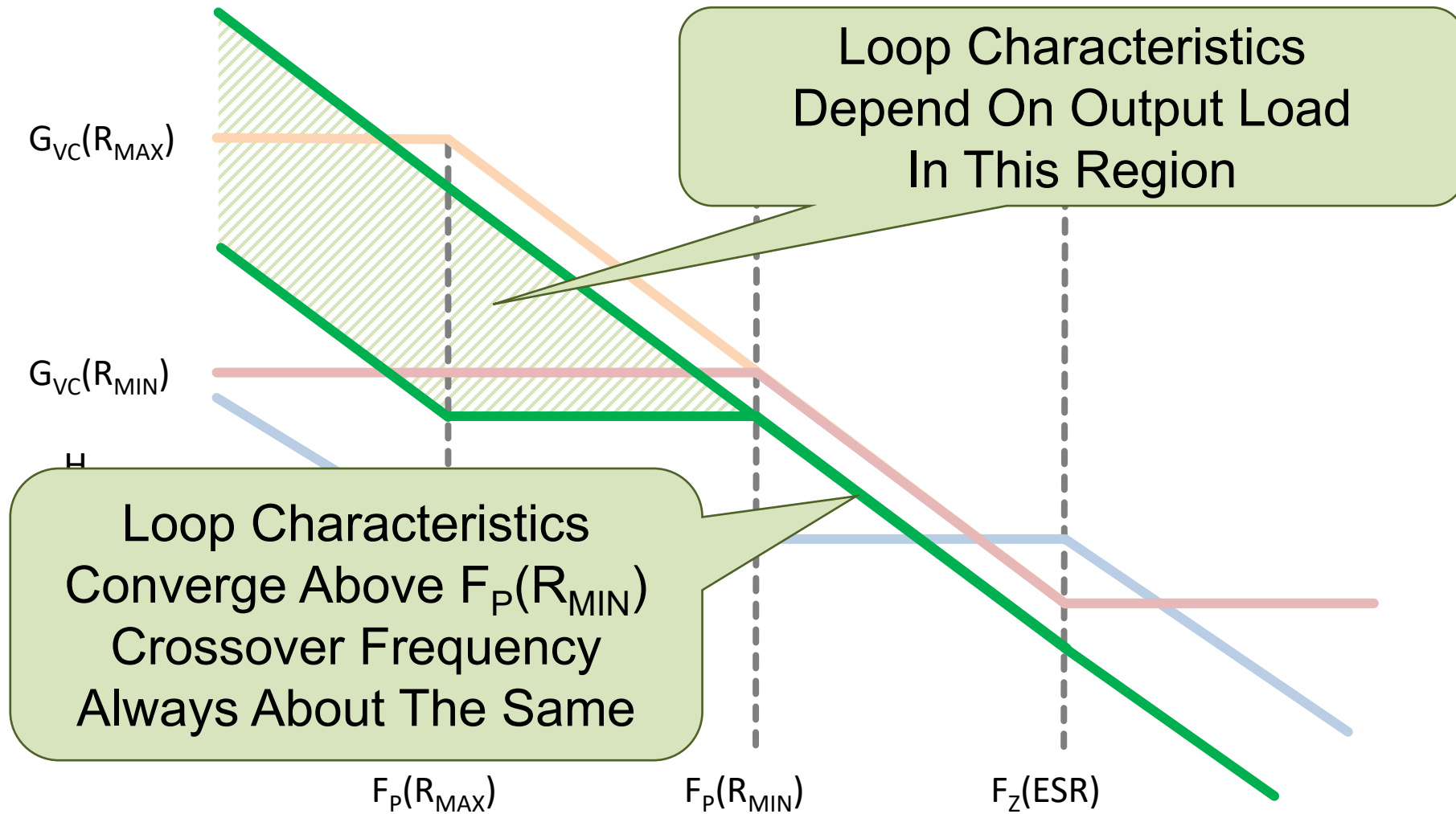

Type II Compensator

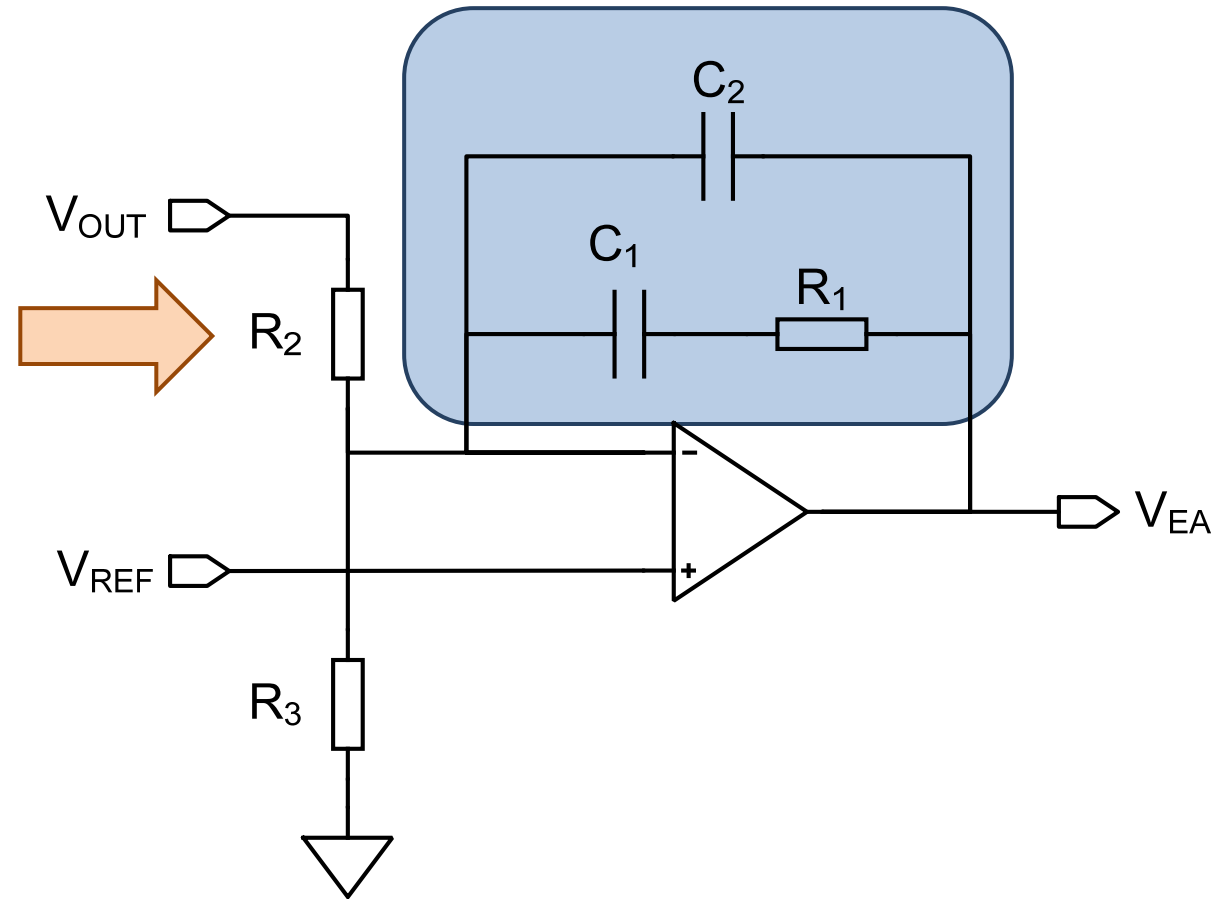

Type II Compensator

$$H_2(s) = -\frac{Z_F}{Z_S}$$


$$= -\frac{\frac{1}{s \cdot (C_1 + C_2)} \cdot \frac{1 + s \cdot R_1 \cdot C_1}{1 + s \cdot R_1 \cdot \frac{C_1 \cdot C_2}{C_1 + C_2}}}{R_2}$$

$$= -\frac{1}{s \cdot R_2 \cdot (C_1 + C_2)} \cdot \frac{1 + s \cdot R_1 \cdot C_1}{1 + s \cdot R_1 \cdot \frac{C_1 \cdot C_2}{C_1 + C_2}}$$

Integrator Pole

Zero

Second Pole

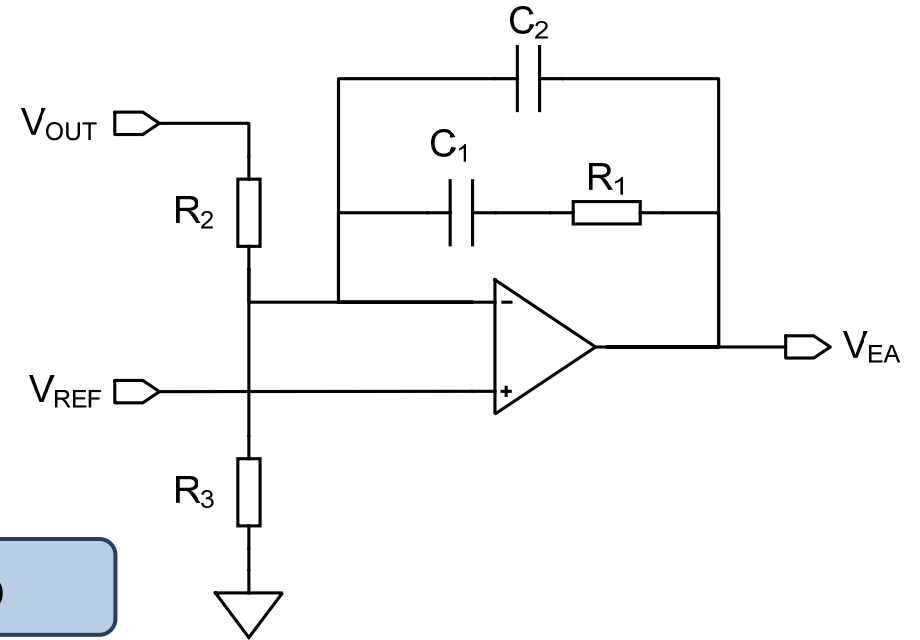

Compensator Frequencies

$$T(s) = \frac{\omega_c}{s} = H_{EA}(s) \cdot G_{VC}(s)$$

$$T(s) = \frac{\omega_c}{s} = \left(\frac{\omega_P}{s} \cdot \frac{1 + \frac{s}{\omega_{ZC}}}{1 + \frac{s}{\omega_{PC}}} \right) \cdot \left(G_O \cdot \frac{1 + \frac{s}{\omega_Z}}{1 + \frac{s}{\omega_P}} \right)$$

$$T(s) = \frac{\omega_c}{s} = \left(\frac{\omega_P}{s} \cdot \frac{1 + \frac{s}{\omega_{ZC}}}{1 + \frac{s}{\omega_{PC}}} \right) \cdot \left(K_I \cdot R_O \cdot \frac{1 + \frac{s}{\omega_Z}}{1 + \frac{s}{\omega_P}} \right)$$

Compensator Frequencies

$$T(s) = \frac{\omega_c}{s} = H_{EA}(s) \cdot G_{VC}(s)$$

$$T(s) = \frac{\omega_c}{s} = \left(\frac{\omega_P}{s} \cdot \frac{1 + \frac{s}{\omega_{ZC}}}{1 + \frac{s}{\omega_{PC}}} \right) \cdot \left(G_O \cdot \frac{1 + \frac{s}{\omega_Z}}{1 + \frac{s}{\omega_P}} \right)$$


$$T(s) = \frac{\omega_c}{s} = \left(\frac{\omega_P}{s} \cdot \frac{1 + \frac{s}{\omega_{ZC}}}{1 + \frac{s}{\omega_{PC}}} \right) \cdot \left(K_I \cdot R_O \cdot \frac{1 + \frac{s}{\omega_Z}}{1 + \frac{s}{\omega_P}} \right)$$

$$\omega_{ZC} = \omega_P \approx \frac{1}{R_O \cdot C}$$

$$\omega_{PC} = \omega_Z$$


$$\omega_P = \frac{\omega_c}{K_I \cdot R_O}$$

Sub-Harmonic Oscillation

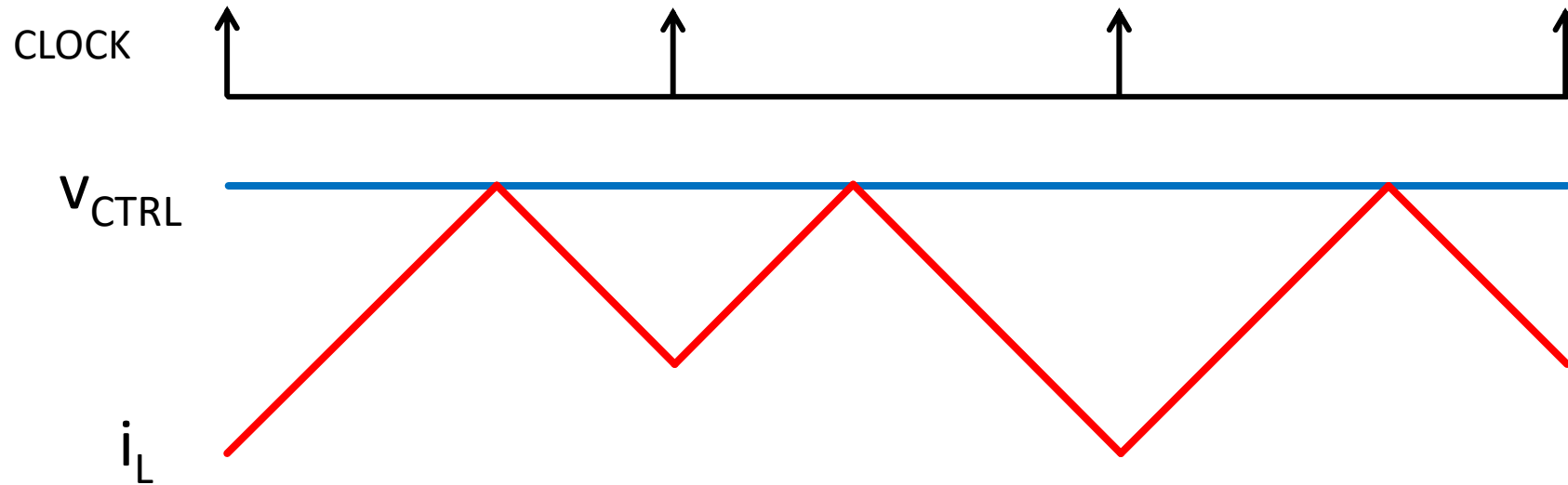


This Oscillation Happens For
Duty Cycles Greater Than 50%


Slope Compensation

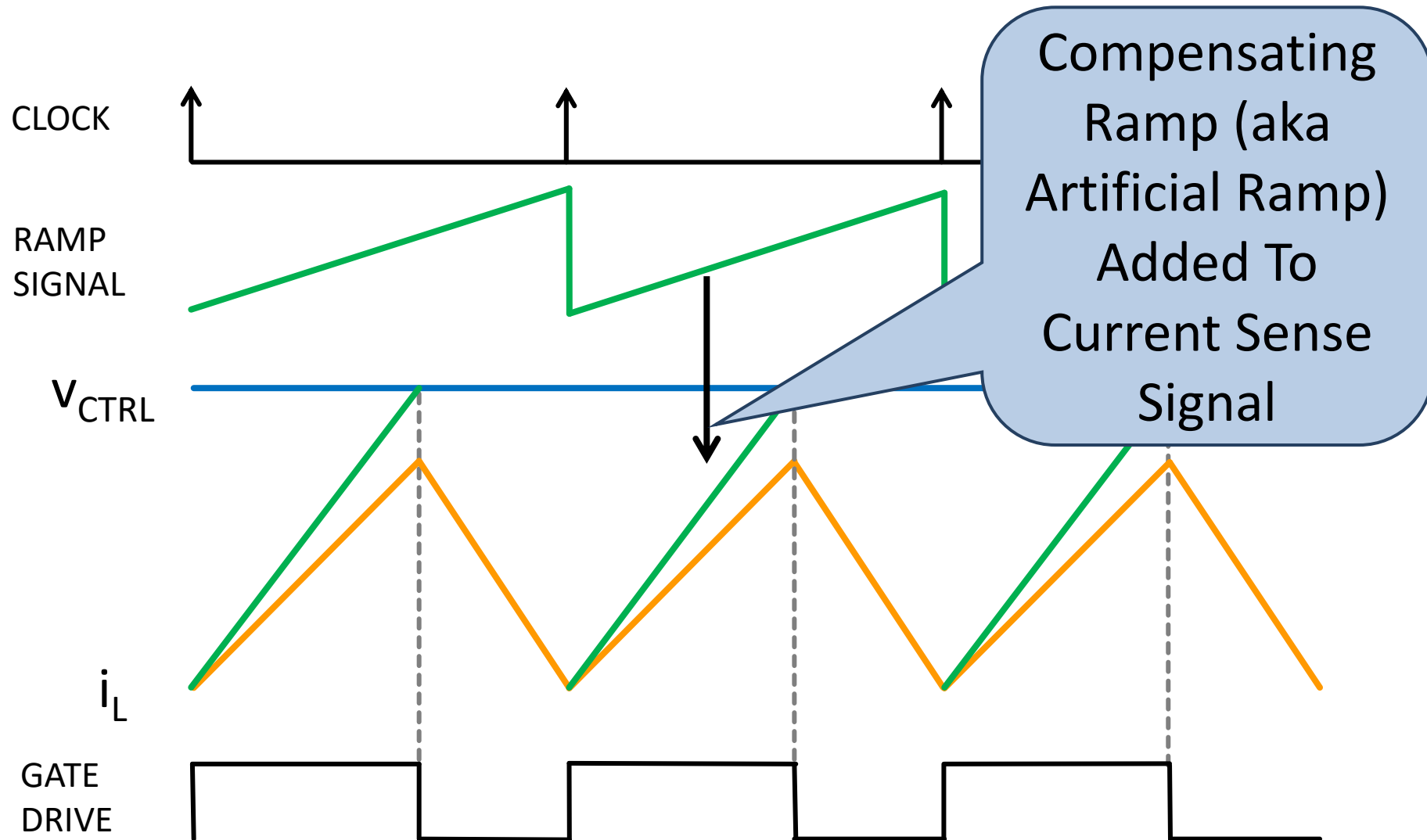

Slope Compensation

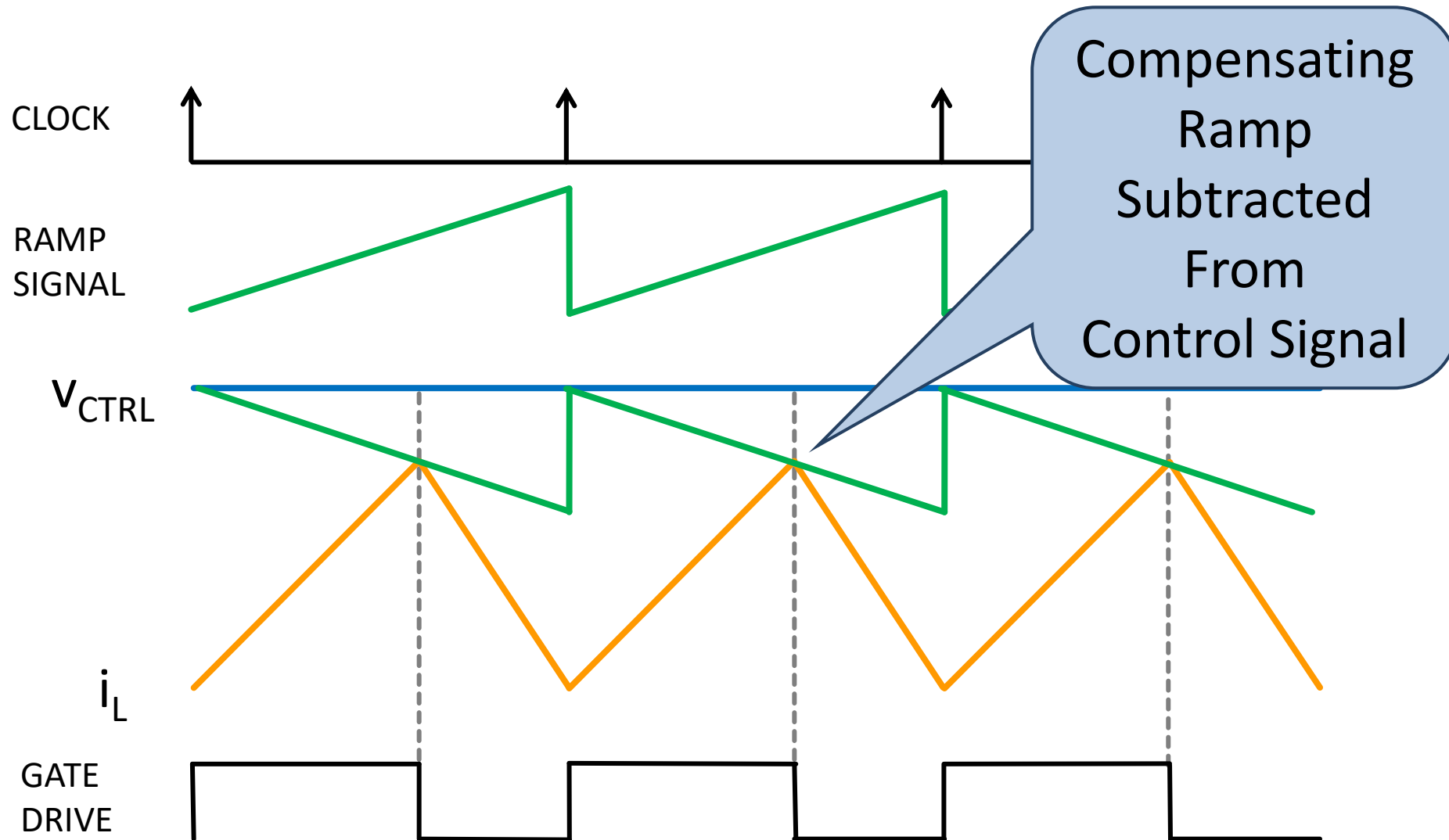

Slope Compensation

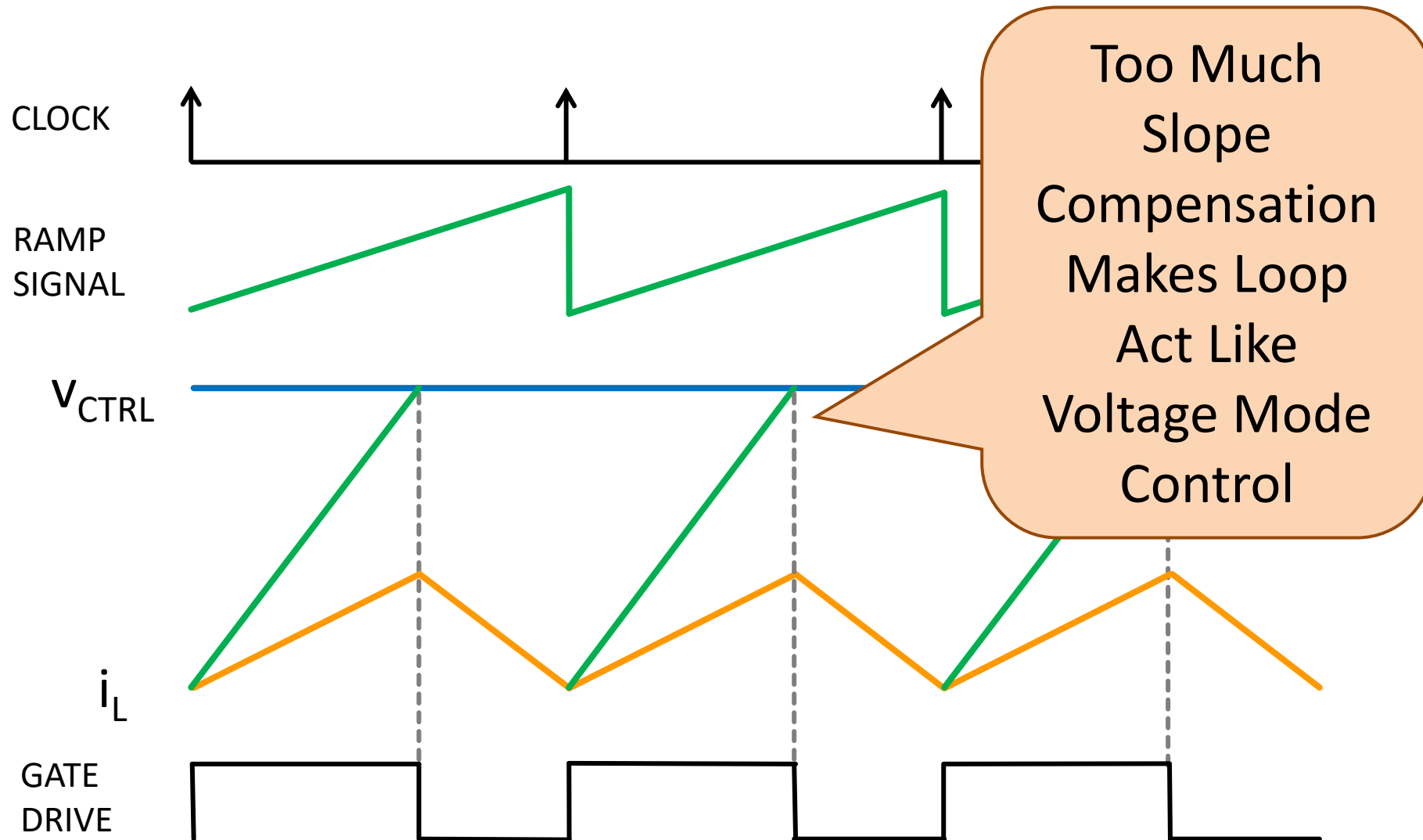

Why Peak Current Mode Control?

Advantages

- Faster Control Loop
- Feed Forward
- Simpler Compensator As Inductor Essentially Removed From Loop
- Build In Current Limiting

Disadvantages

- Must Sense The Current
- Noise Sensitivity
- “Slope Compensation”
 - Must Add Additional Ramp Signal To Current Sense Signal To Avoid Subharmonic Oscillations

Why Peak Current Mode Control?

Advantages

- Faster Control Loop
- Feed Forward
- Simpler Compensator As Inductor Essentially Removed From Loop
- Build In Current Limiting


Are Generally Heavily Outweighed
By These Advantages!

Disadvantages


- Must Sense The Current
- Noise Sensitivity
- “Slope Compensation”
 - Must Add Additional Ramp Signal To Current Sense Signal To Avoid Subharmonic Oscillations

These Disadvantages


Average Current Mode Control

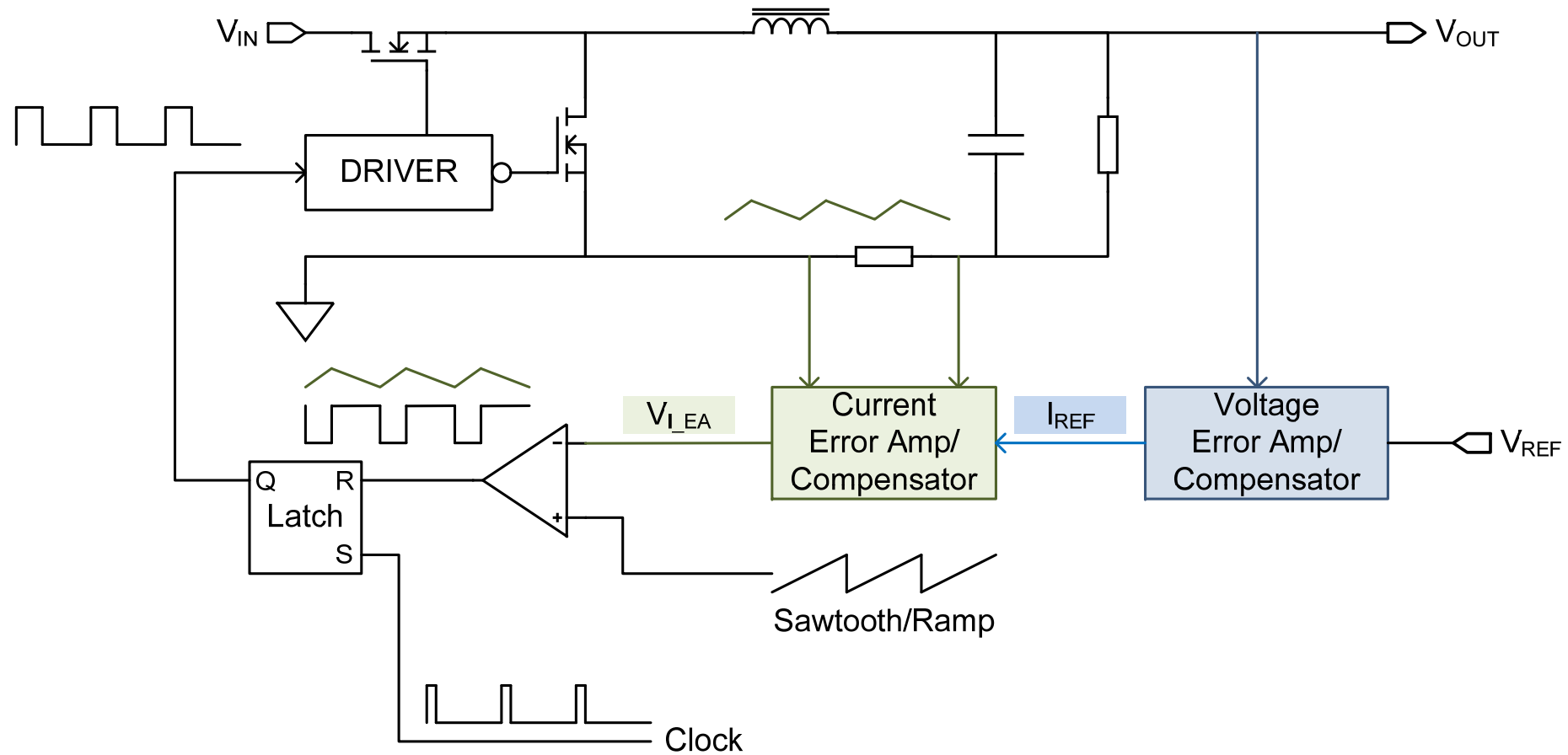


Average Current Mode Control

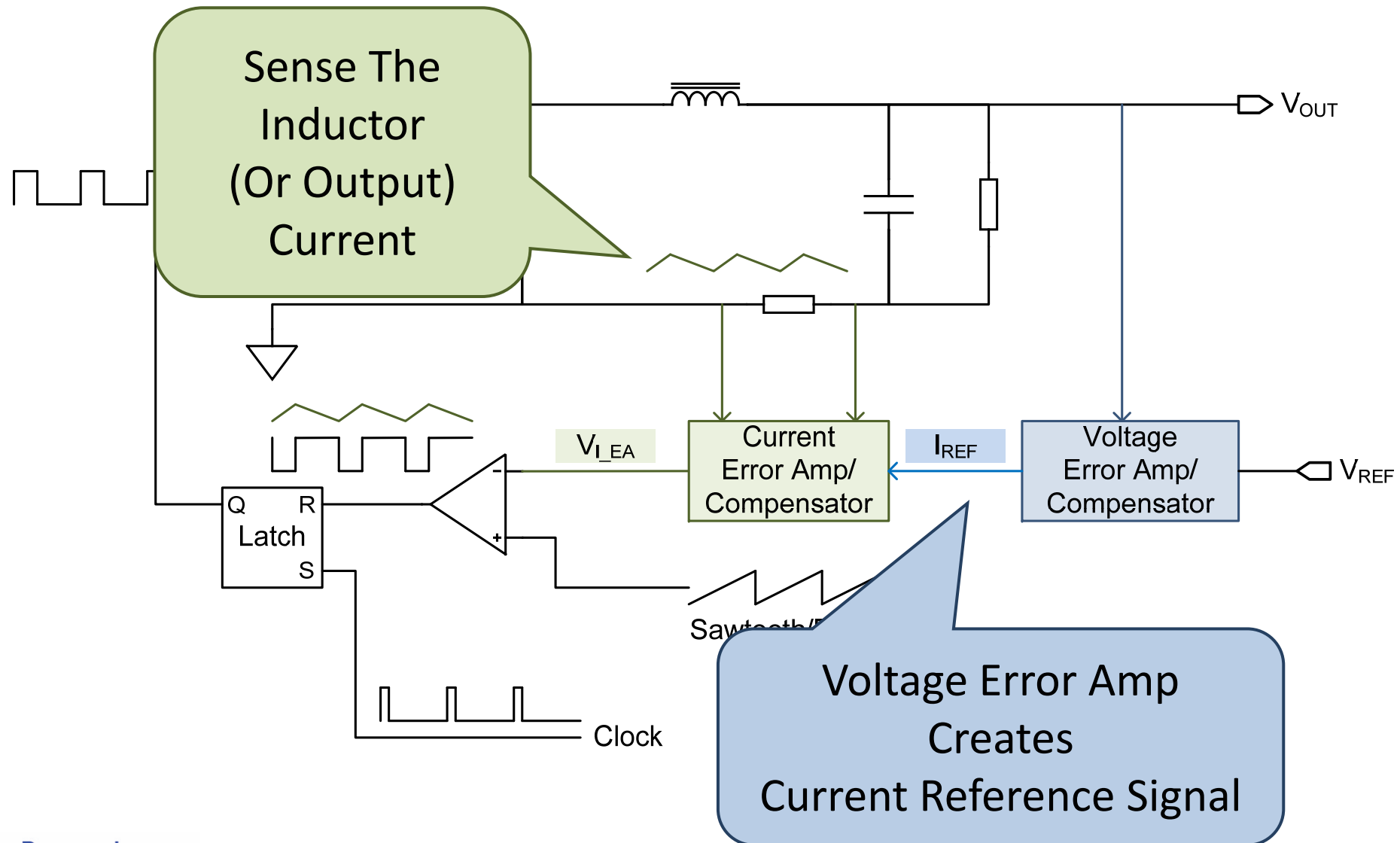

Average Current Mode Control

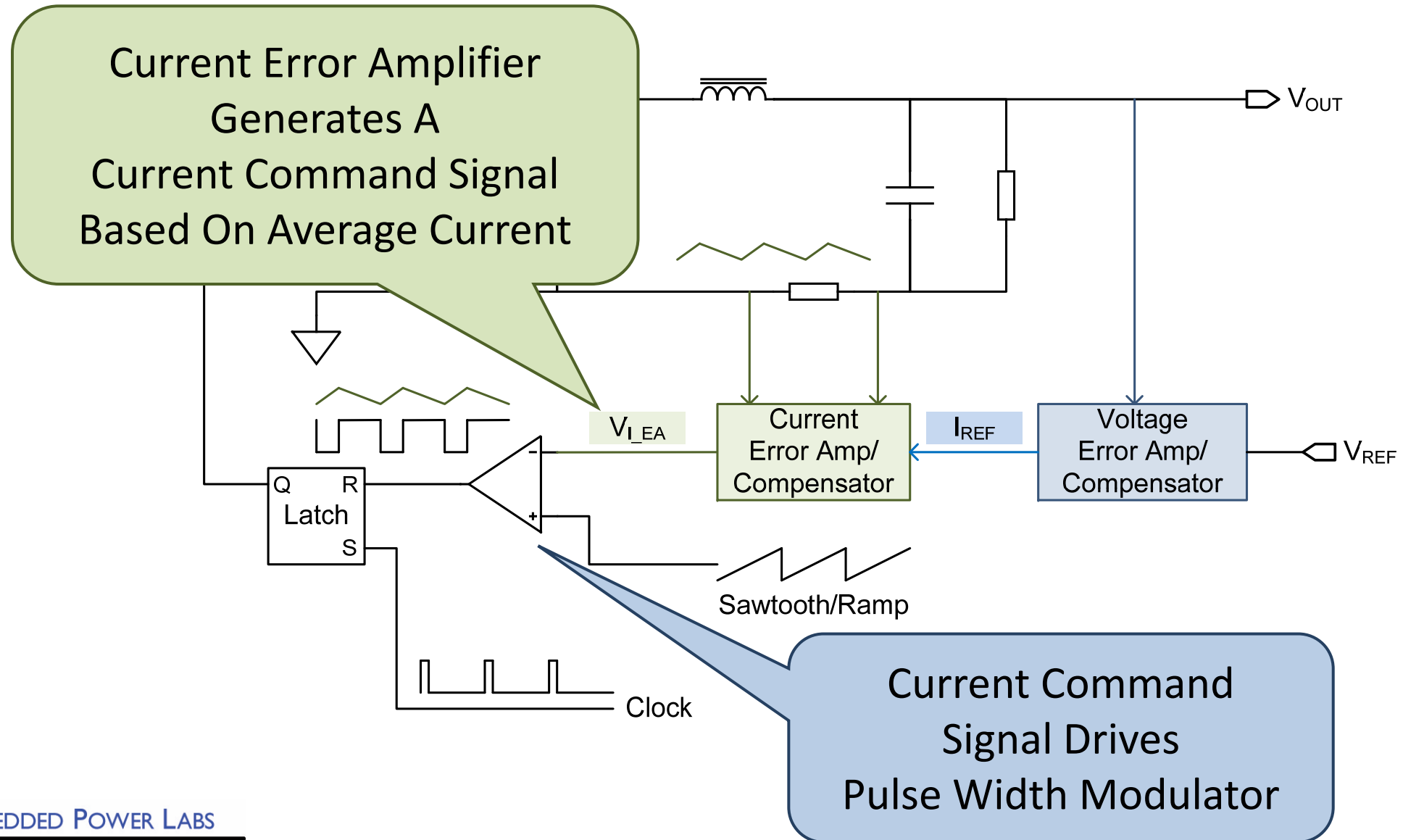

Average Current Mode Control

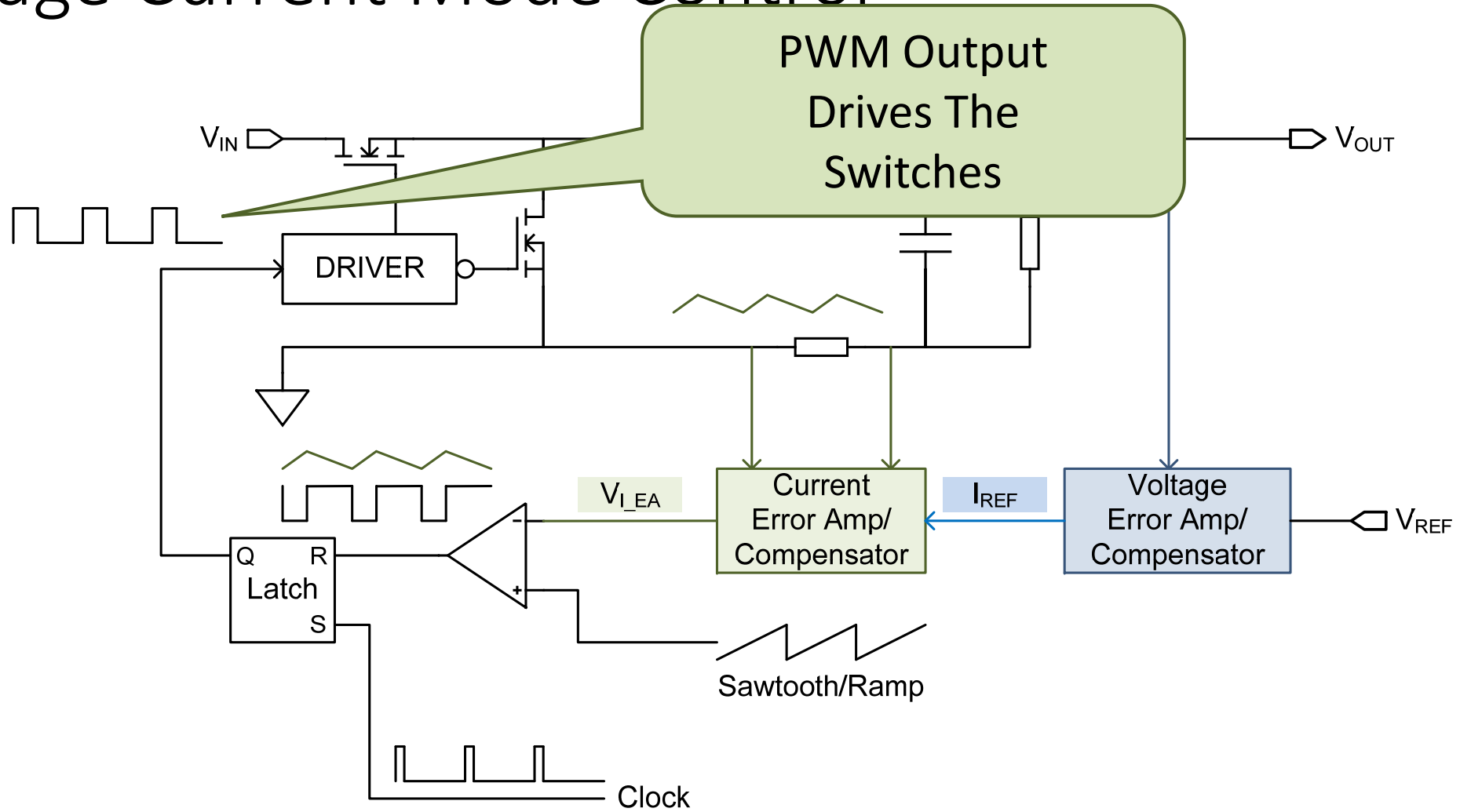

Why Average Current Mode Control?



Advantages

- Direct Control Of Average Output Current
- No Slope Compensation
- Excellent Noise Immunity

Disadvantages

- More Components

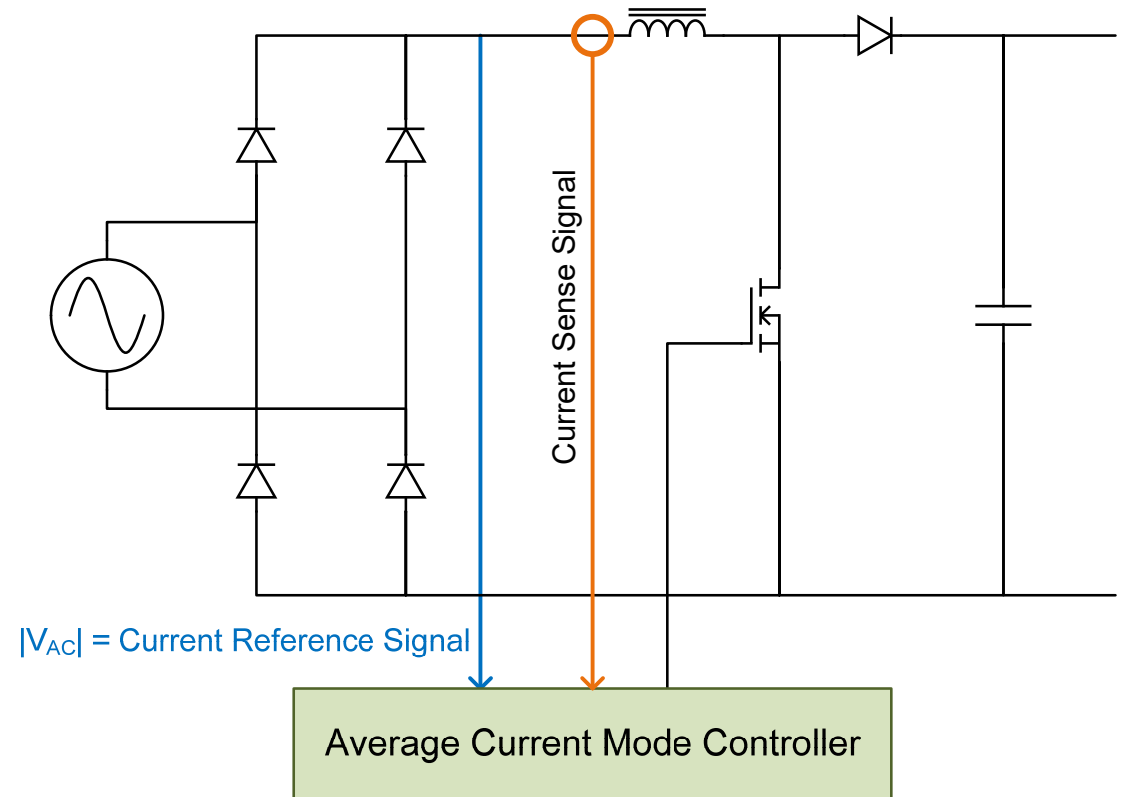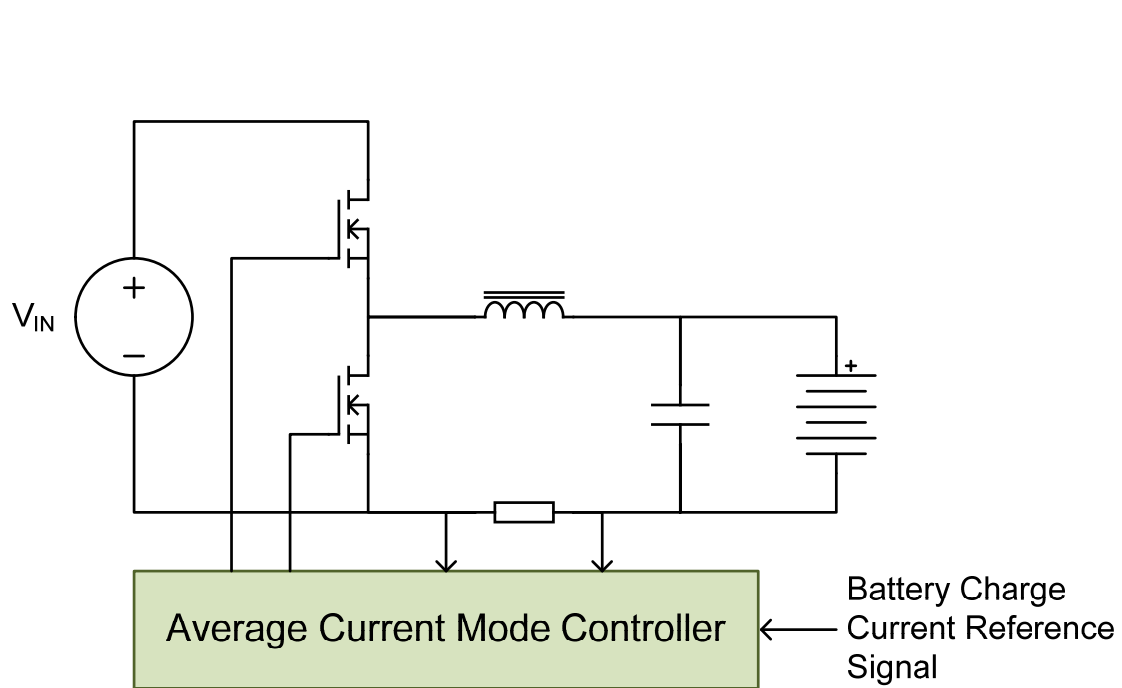Applications Of Average Current Mode Control



Summary

In Part II We Covered

- Basics Of Feedback Control
- Buck Converter Design Example
 - Determining The Transfer Function Of Each Block In The Control Loop
 - Solving For The Compensator
 - Designing The Compensator
 - K-Factor Method
- Overview Of Current Mode Control

Additional Resources

- Great Book For The Basics
“Fundamentals Of Power Supply Design”
Robert A. Mammano
- My Favorite Textbook
“Fundamentals Of Power Electronics”
2nd Edition, Erickson & Maksimovic
- For References Of Control To Output Transfer Functions
“Switch-Mode Power Supplies – SPICE Simulations And Practical Designs”
2nd Edition, 2014, Christophe P. Basso
- Best Paper On Modeling Current Mode Control
R. B. Ridley, "A new, continuous-time model for current-mode control," IEEE Transactions on Power Electronics, vol. 6, pp. 271-280, 1991

Additional Resources: Selected Tools

Commercial

SIMPLIS/SIMetrix

PSIM

MATLAB/Simulink/
Control Toolboxes

Mathcad

Pspice®

Free

SIMPLIS/SIMetrix Elements
Microchip Technology
MPLAB® MINDI™

Scilab/Xcos
GNU Octave

Smath Studio

LTspice

Survey Forms!

Questions?

About The Speaker

Bob White has over 40 years experience in power electronics. He has held managerial and individual contributor positions in product development, technology development, applications and systems engineering, and technical marketing. His areas of expertise include power systems for computing and telecommunications systems, digital power, and applications of wide bandgap power semiconductor devices. Bob is currently the president and chief engineer of Embedded Power Labs, a power electronics consulting company.

Bob has been very active in the IEEE Power Electronics Society and the APEC committees, including twice serving as the APEC General Chair.

He is a Fellow of the IEEE, has a BSEE from MIT, a MSEE from Worcester Polytechnic Institute and is currently pursuing a Ph.D. in power electronics at the University of Colorado-Boulder.

He can be reached by email at bob.white@embeddedpowerlabs.com




Appendices

- I. Non-Ideal Buck Converter
- II. Buck Converter Discontinuous Conduction Mode
- III. Isolated Buck Converters: Forward, Half-Bridge, Full-Bridge
- IV. Boost Converter Discontinuous Conduction And Critical Conduction Modes
- V. Non-Ideal Boost Converter
- VI. Buck-Boost Converter Analysis
- VII. More Realistic Flyback Converter Simulation
- VIII. Flyback Converter Continuous Conduction Mode
- IX. Four Switch Noninverting Buck-Boost
- X. Simple Pole And Zero Transfer Functions
- XI. Loop Gain And Tracking
- XII. Ideal Loop Calculations
- XIII. Analog Compensators

APPENDIX I.

Non-Ideal Buck Converter

Non-Ideal Buck Converter

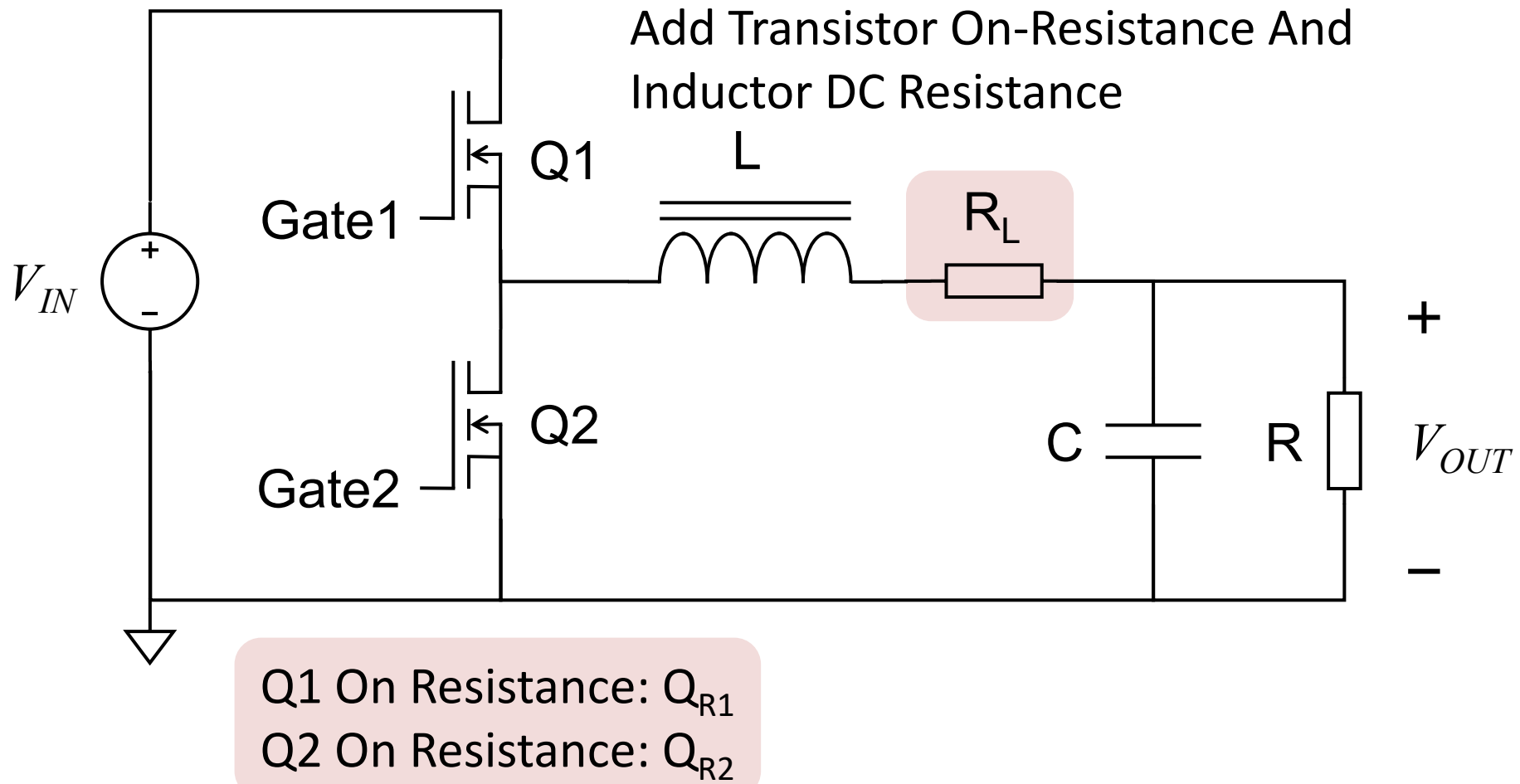

Conversion Ratio Derivation

$$V_L(T_{ON}) = V_{IN} - R_{Q1} \cdot I_L - R_L \cdot I_L - V_{OUT}$$

$$V_L(T_{OFF}) = -V_{OUT} - R_{Q2} \cdot I_L - R_L \cdot I_L$$

$$V_L(T_{ON}) \cdot T_{ON} + V_L(T_{OFF}) \cdot T_{OFF} = 0$$

$$\begin{aligned} & (V_{IN} - R_{Q1} \cdot I_L - R_L \cdot I_L - V_{OUT}) \cdot T_{ON} \\ & + (-V_{OUT} - R_{Q2} \cdot I_L - R_L \cdot I_L) \cdot T_{OFF} = 0 \end{aligned}$$

$$\begin{aligned} & (V_{IN} - R_{Q1} \cdot I_L - R_L \cdot I_L - V_{OUT}) \cdot D \cdot T_{SW} \\ & + (-V_{OUT} - R_{Q2} \cdot I_L - R_L \cdot I_L) \cdot (1 - D) \cdot T_{SW} = 0 \end{aligned}$$

$$\begin{aligned} & (V_{IN} - R_{Q1} \cdot I_L - R_L \cdot I_L - V_{OUT}) \cdot D \\ & + (-V_{OUT} - R_{Q2} \cdot I_L - R_L \cdot I_L) \cdot (1 - D) = 0 \end{aligned}$$

Conversion Ratio Derivation

$$\begin{aligned} & D \cdot V_{IN} - D \cdot R_{Q1} \cdot I_L - \cancel{D \cdot R_L \cdot I_L} - \cancel{D \cdot V_{OUT}} \\ & - V_{OUT} - R_{Q2} \cdot I_L - R_L \cdot I_L \\ & + \cancel{D \cdot V_{OUT}} + D \cdot R_{Q2} \cdot I_L + \cancel{D \cdot R_L \cdot I_L} = 0 \end{aligned}$$

$$D \cdot V_{IN} - D \cdot R_{Q1} \cdot I_L - V_{OUT} - R_{Q2} \cdot I_L - R_L \cdot I_L + D \cdot R_{Q2} \cdot I_L = 0$$

$$D \cdot V_{IN} - D \cdot R_{Q1} \cdot I_L - R_{Q2} \cdot I_L + D \cdot R_{Q2} \cdot I_L - R_L \cdot I_L - V_{OUT} = 0$$

$$D \cdot (V_{IN} - R_{Q1} \cdot I_L) - (1 - D) \cdot R_{Q2} \cdot I_L - R_L \cdot I_L - V_{OUT} = 0$$

$$V_{OUT} = D \cdot (V_{IN} - R_{Q1} \cdot I_L) - (1 - D) \cdot R_{Q2} \cdot I_L - R_L \cdot I_L$$

$$V_{OUT} = D \cdot V_{IN} - D \cdot R_{Q1} \cdot I_L - (1 - D) \cdot R_{Q2} \cdot I_L - R_L \cdot I_L$$

Conversion Ratio Derivation

Output Voltage Of An Ideal Buck Converter

These Terms Show The Effect Of The Non-Ideal Factors.

The Losses Subtract From The Ideal Output Voltage.

To Keep The Output Voltage Constant, The Controller Must Add Some Duty Cycle To Make Up For The Losses

$$V_{OUT} = D \cdot (V_{IN} - R_{Q1} \cdot I_L - (1 - D) \cdot R_{Q2} \cdot I_L - R_L \cdot I_L)$$

$$V_{OUT} = D \cdot V_{IN} - D \cdot R_{Q1} \cdot I_L - (1 - D) \cdot R_{Q2} \cdot I_L - R_L \cdot I_L$$

Duty Cycle As Function Of Load

$$D \cdot V_{IN} - D \cdot R_{Q1} \cdot I_L + D \cdot R_{Q2} \cdot I_L - R_{Q2} \cdot I_L - R_L \cdot I_L - V_{OUT} = 0$$


$$D \cdot V_{IN} - D \cdot R_{Q1} \cdot I_L + D \cdot R_{Q2} \cdot I_L = V_{OUT} + R_{Q2} \cdot I_L + R_L \cdot I_L$$

$$D \cdot (V_{IN} - R_{Q1} \cdot I_L + R_{Q2} \cdot I_L) = V_{OUT} + R_{Q2} \cdot I_L + R_L \cdot I_L$$


$$D = \frac{V_{OUT} + R_{Q2} \cdot I_L + R_L \cdot I_L}{V_{IN} - R_{Q1} \cdot I_L + R_{Q2} \cdot I_L}$$

Remember That The
Average Inductor Current
Equals The Load Current


Example

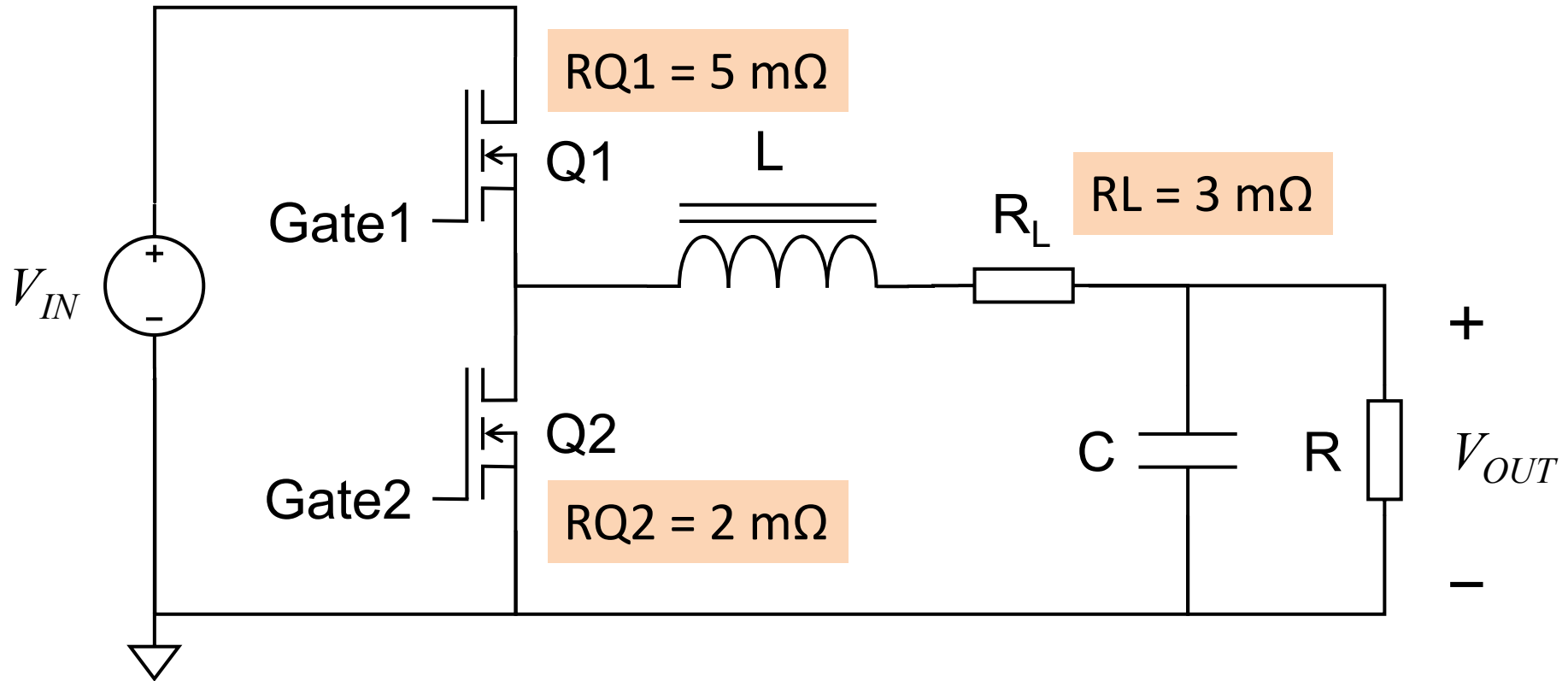


Duty Cycle Variation

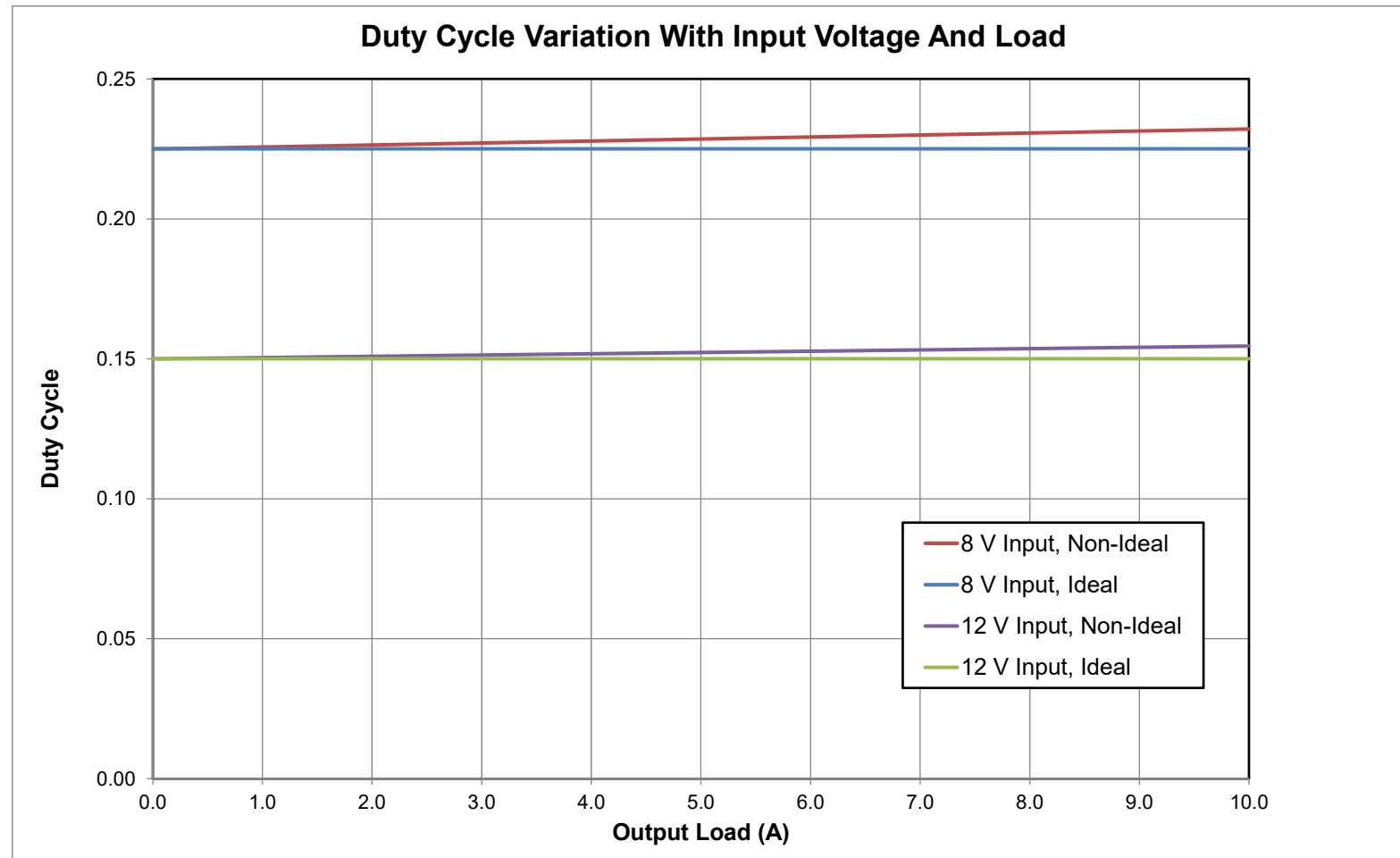

Duty Cycle Variation

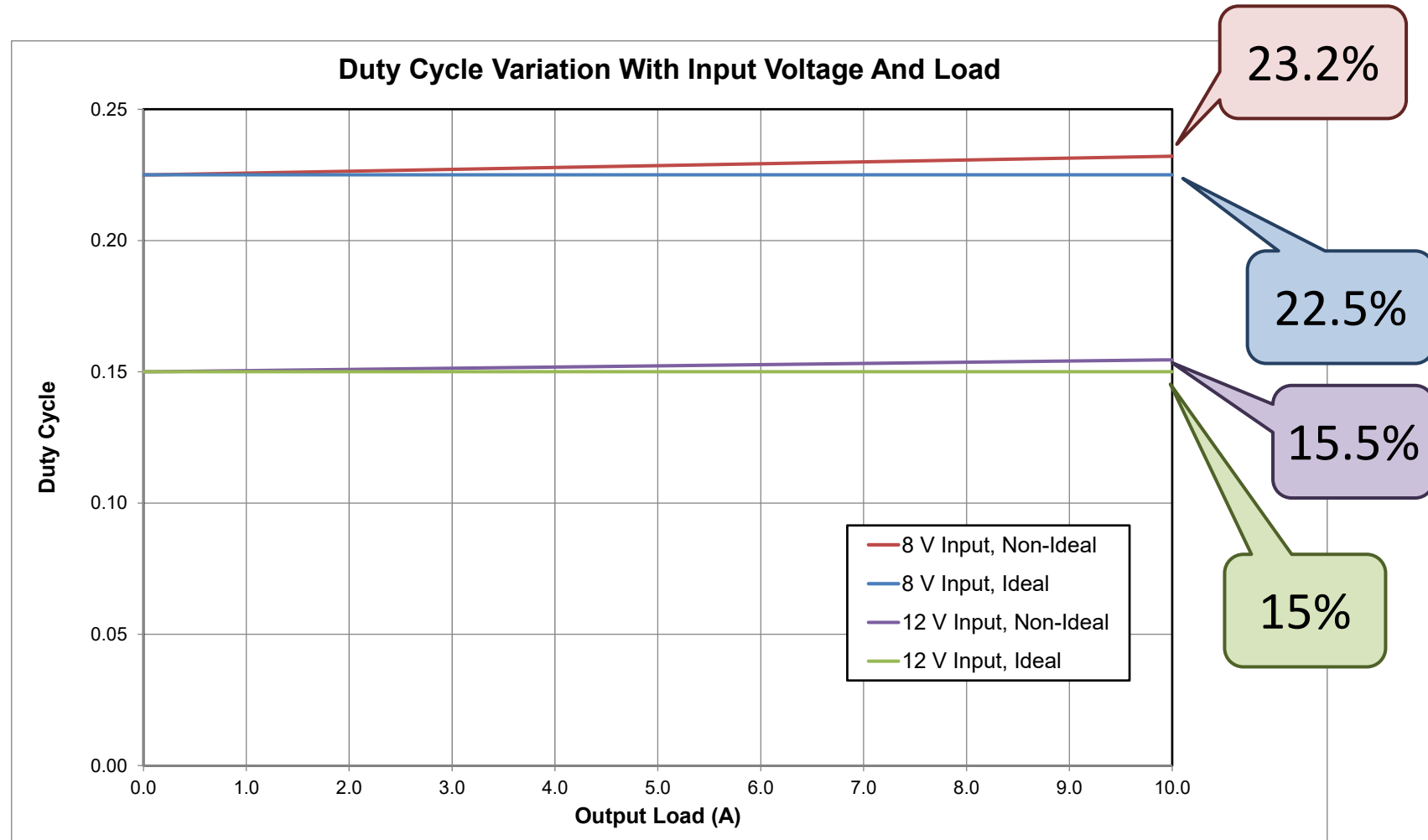

Duty Cycle Variation

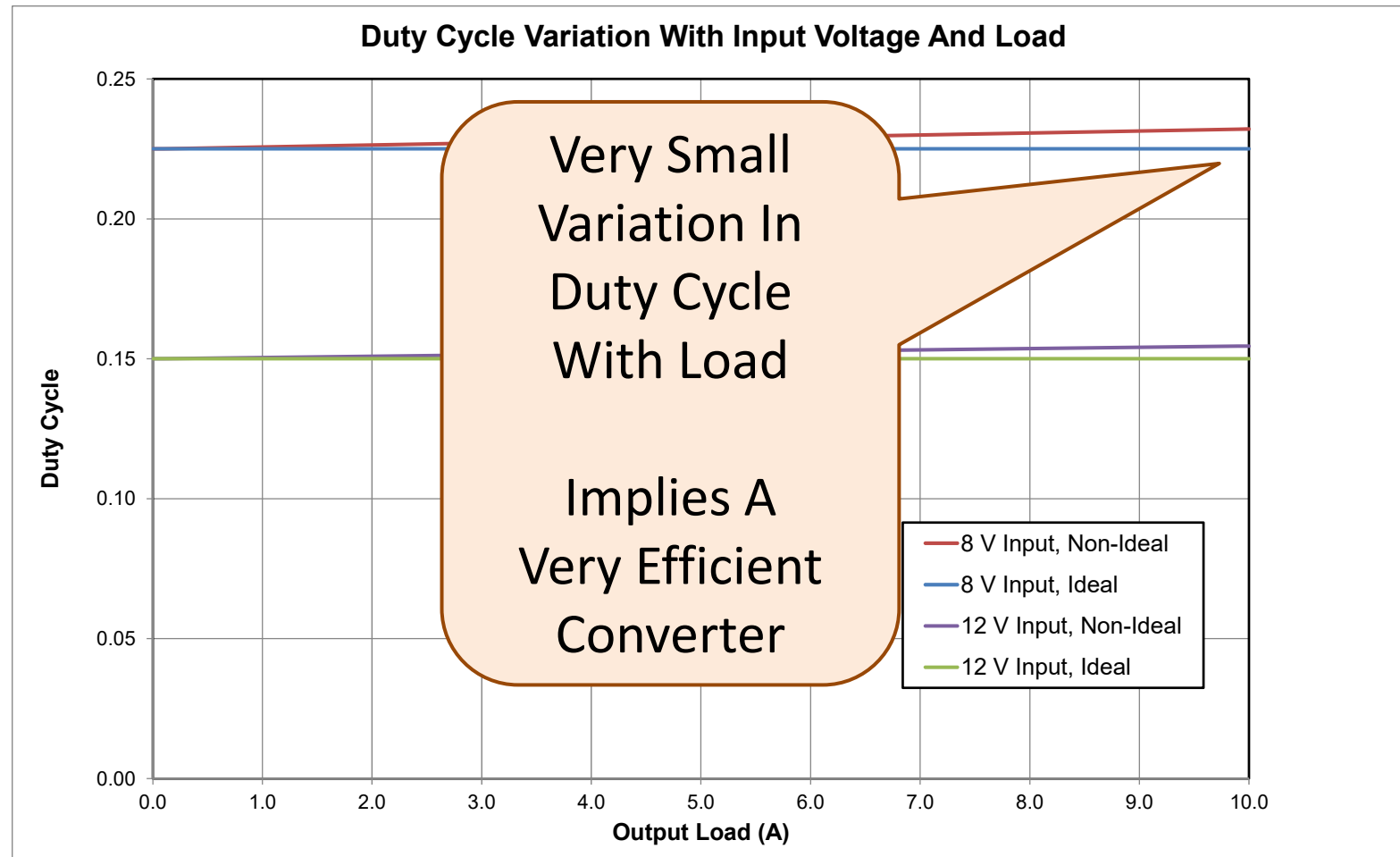

Duty Cycle Variation

Dutv Cvcle Variation With Input Voltage And Load

NOTE

This Is An Interesting And Informative Exercise. However, Note That Switching Losses Are Not Included And Make The Duty Cycle Needed For A Specified Output Voltage Is Larger Than Shown Here


Output Load (A)

APPENDIX II.


Buck Converter

Discontinuous Conduction Mode


Buck Converter

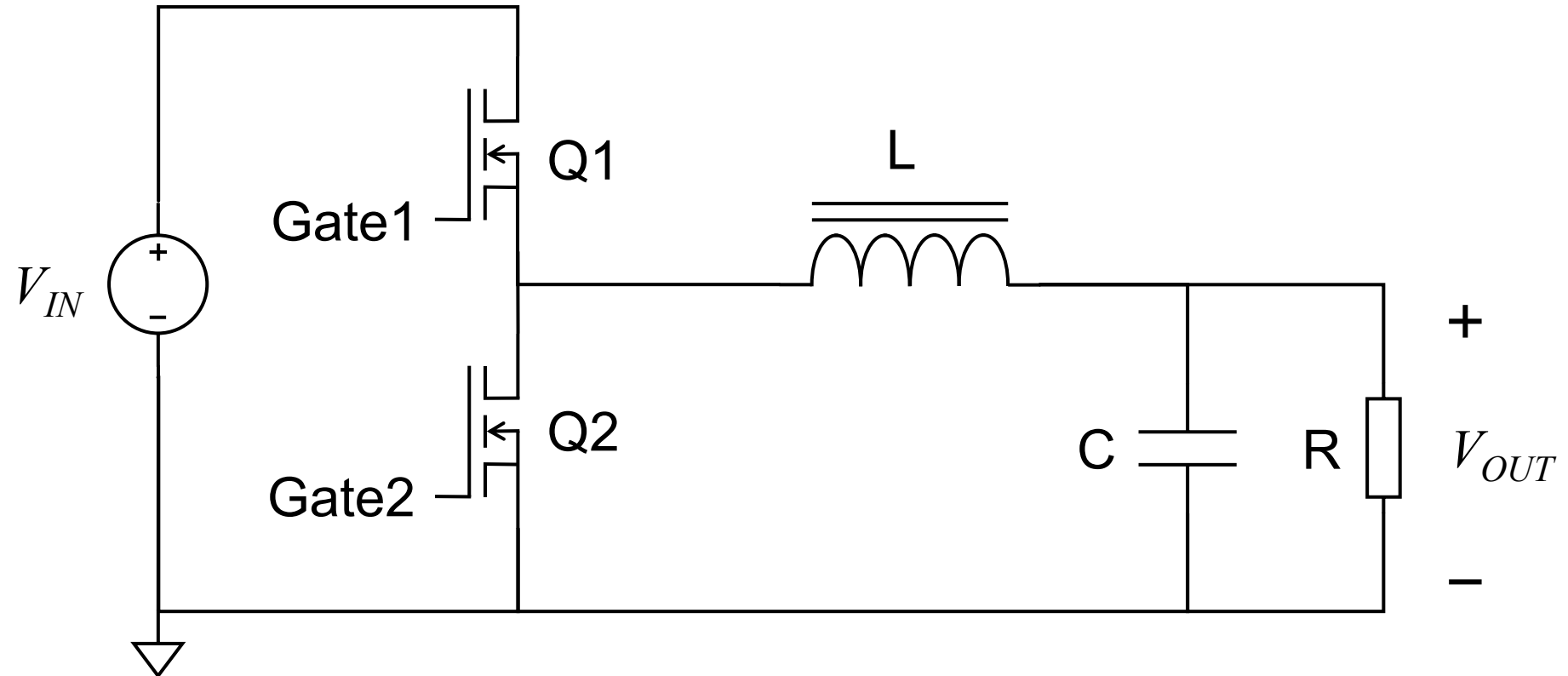

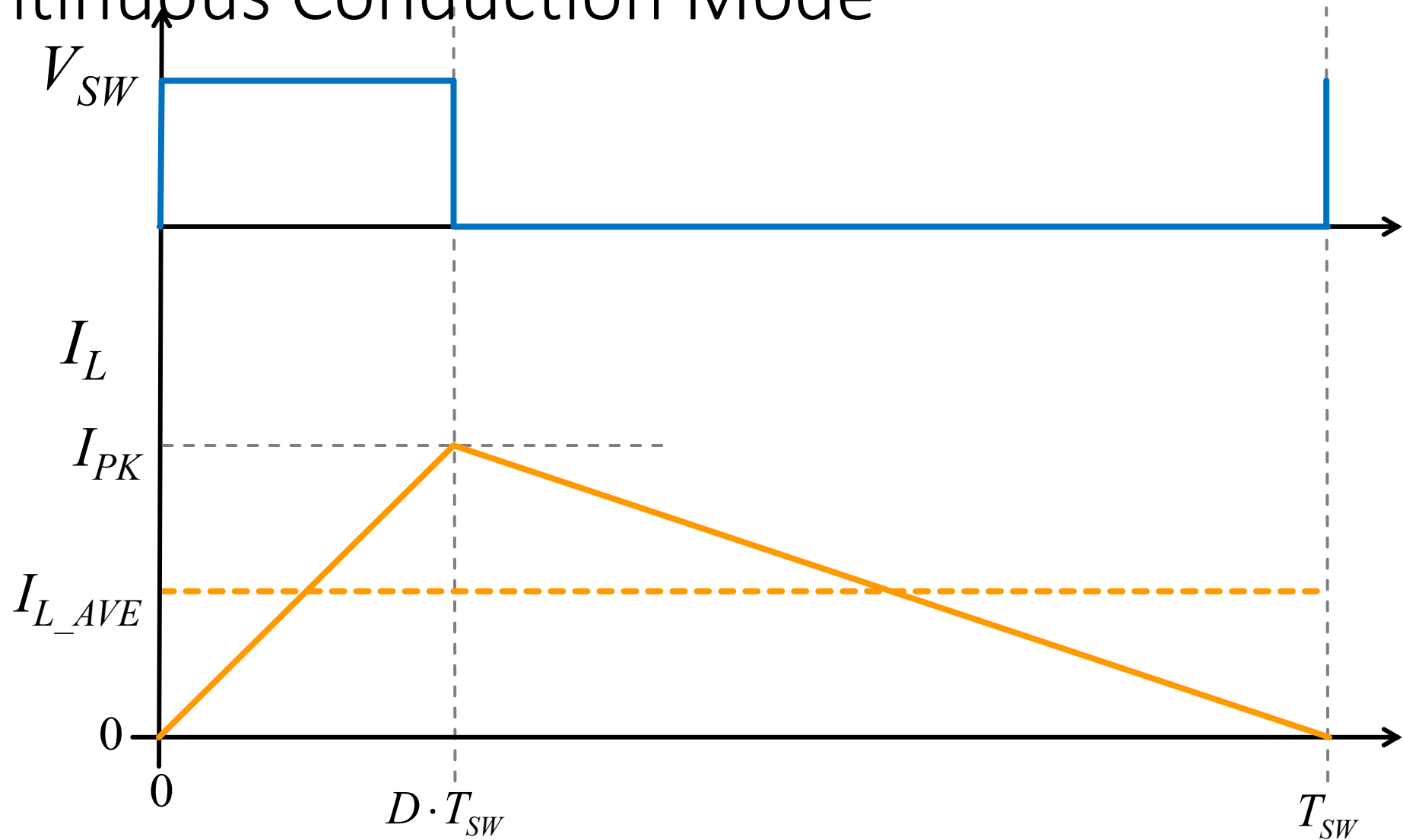Border Of Continuous And Discontinuous Conduction Mode



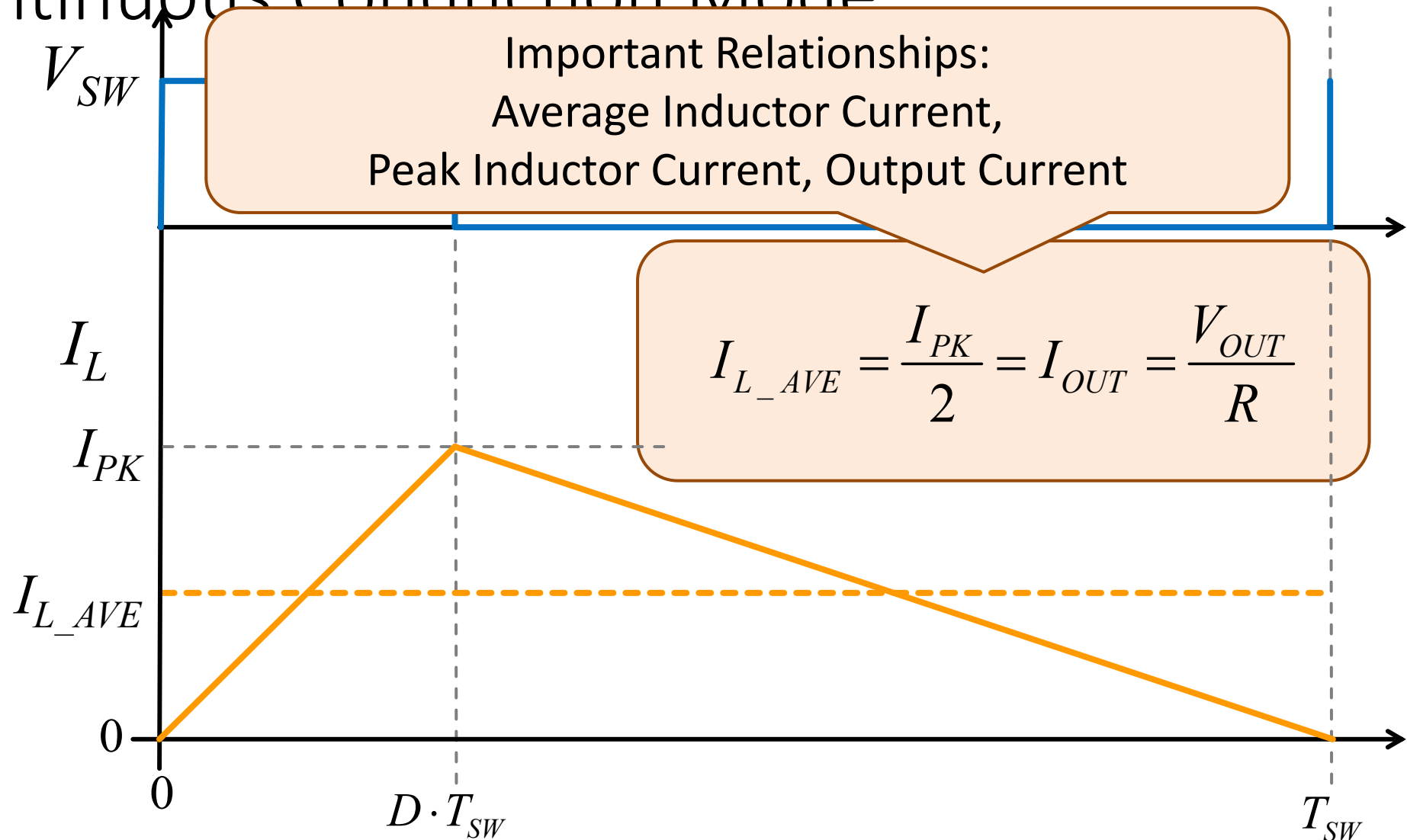Border Of Continuous And Discontinuous Conduction Mode



DCM And Output Inductor

Avoiding Discontinuous Mode At Light Load Often Specifies Minimum Value Of Output Inductor

$$I_{PK} = 2 \cdot I_{OUT}$$

$$I_{PK} = \frac{V_{IN} - V_{OUT}}{L_{MIN}} \cdot T_{ON}$$

$$L_{MIN} = \frac{V_{IN} - V_{OUT}}{I_{PK}} \cdot T_{ON}$$

$$T_{ON} = D \cdot T_{SW} = \frac{V_{OUT}}{V_{IN}} \cdot T_{SW}$$

$$L_{MIN} = \frac{V_{IN} - V_{OUT}}{2 \cdot I_{OUT}} \cdot \frac{V_{OUT}}{V_{IN}} \cdot T_{SW}$$

Minimum Criteria To Avoid Discontinuous Conduction Mode

Inductor Calculation Example

Circuit
Parameters

$$V_{IN} = 12 \text{ V}$$

$$V_{OUT} = 3.3 \text{ V}$$

$$I_{OUT} = 200 \text{ mA}$$

$$F_{SW} = 200 \text{ kHz}$$

$$T_{SW} = 5 \mu\text{s}$$

Inductance
Calculation

$$\begin{aligned} L_{MIN} &= \frac{V_{IN} - V_{OUT}}{2 \cdot I_{OUT}} \cdot \frac{V_{OUT}}{V_{IN}} \cdot T_{SW} \\ &= \frac{12 \text{ V} - 3.3 \text{ V}}{2 \cdot 200 \text{ mA}} \cdot \frac{3.3 \text{ V}}{12 \text{ V}} \cdot 5 \mu\text{s} \\ &= 29.9 \mu\text{H} \end{aligned}$$

Standard Value Of 30 μH Is Too Close.
Better To Choose 39 μH Or 47 μH

Inductor Calculation Example

Circuit

Parameters

$$V_{IN} = 12 \text{ V}$$

$$V_{OUT} = 3.3 \text{ V}$$

$$I_{OUT} = 200 \text{ mA}$$

$$R_{OUT} = \frac{3.3 \text{ V}}{200 \text{ mA}}$$

$$= 16.5 \Omega$$

$$F_{SW} = 200 \text{ kHz}$$

$$T_{SW} = 5 \mu\text{s}$$


$$L = 47 \mu\text{H}$$

How Small Can Output Current Be Before Inductor Current Becomes Discontinuous?


$$\begin{aligned} I_{PK} &= \frac{V_{IN} - V_{OUT}}{L} \cdot D \cdot T_{SW} \\ &= \frac{V_{IN} - V_{OUT}}{L} \cdot \frac{V_{OUT}}{V_{IN}} \cdot T_{SW} \\ &= \frac{12 \text{ V} - 3.3 \text{ V}}{47 \mu\text{H}} \cdot \frac{3.3 \text{ V}}{12 \text{ V}} \cdot 5 \mu\text{s} \\ &= 254.5 \text{ mA} \end{aligned}$$

$$I_{DCM} = \frac{I_{PK}}{2} = \frac{254.5 \text{ mA}}{2} = 127 \text{ mA}$$


Discontinuous Conduction Mode

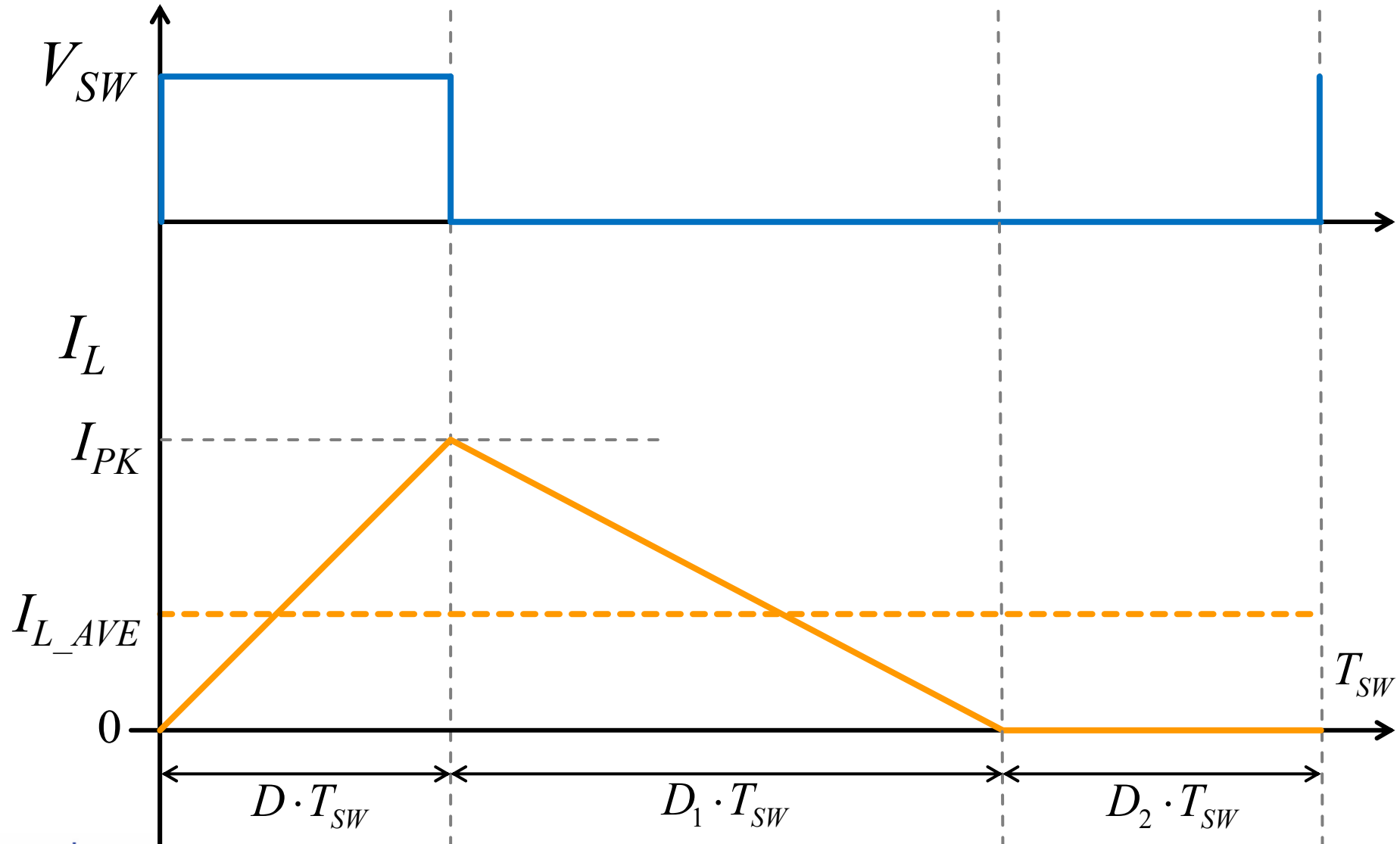

Discontinuous Conduction Mode

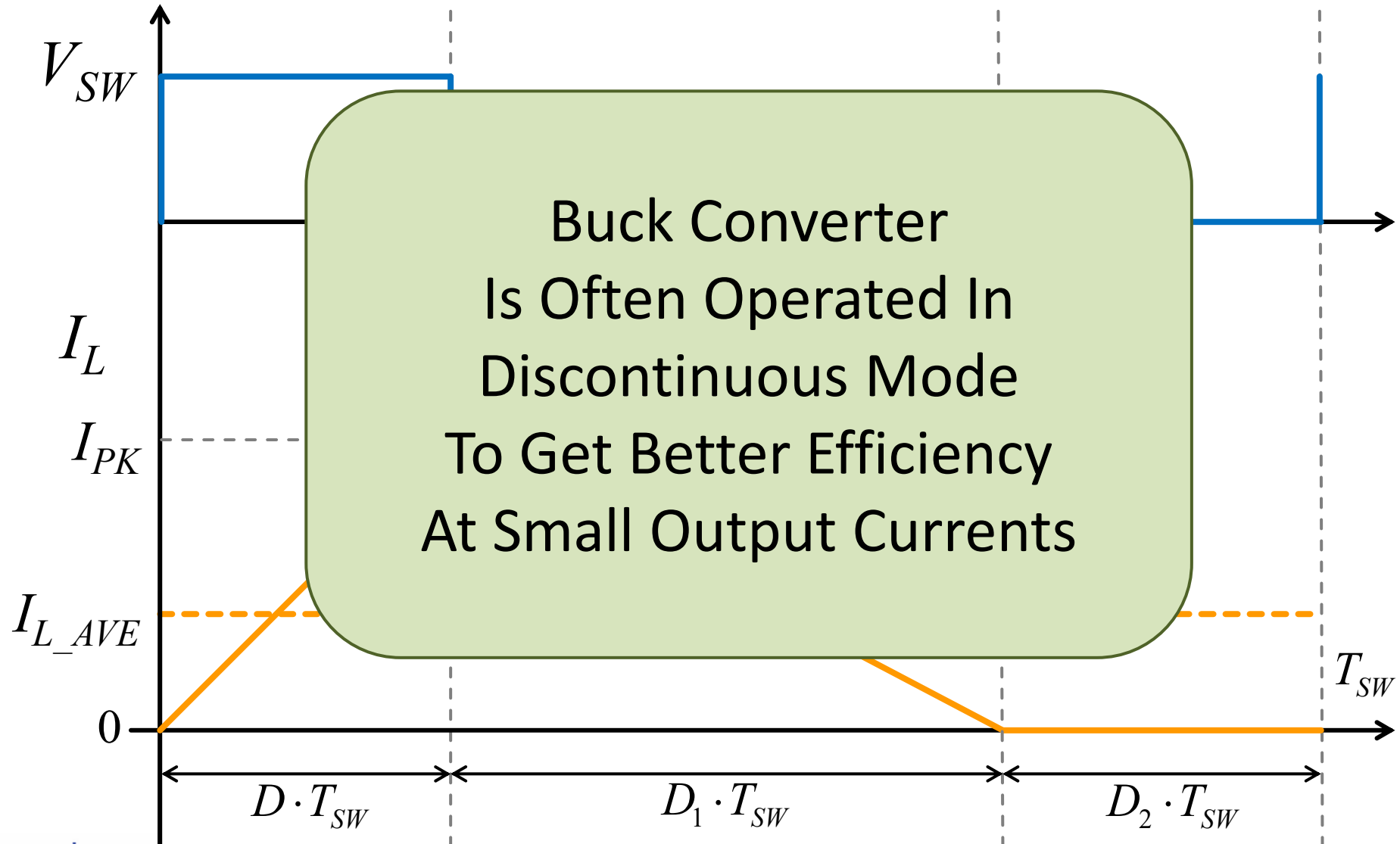

Discontinuous Conduction Mode

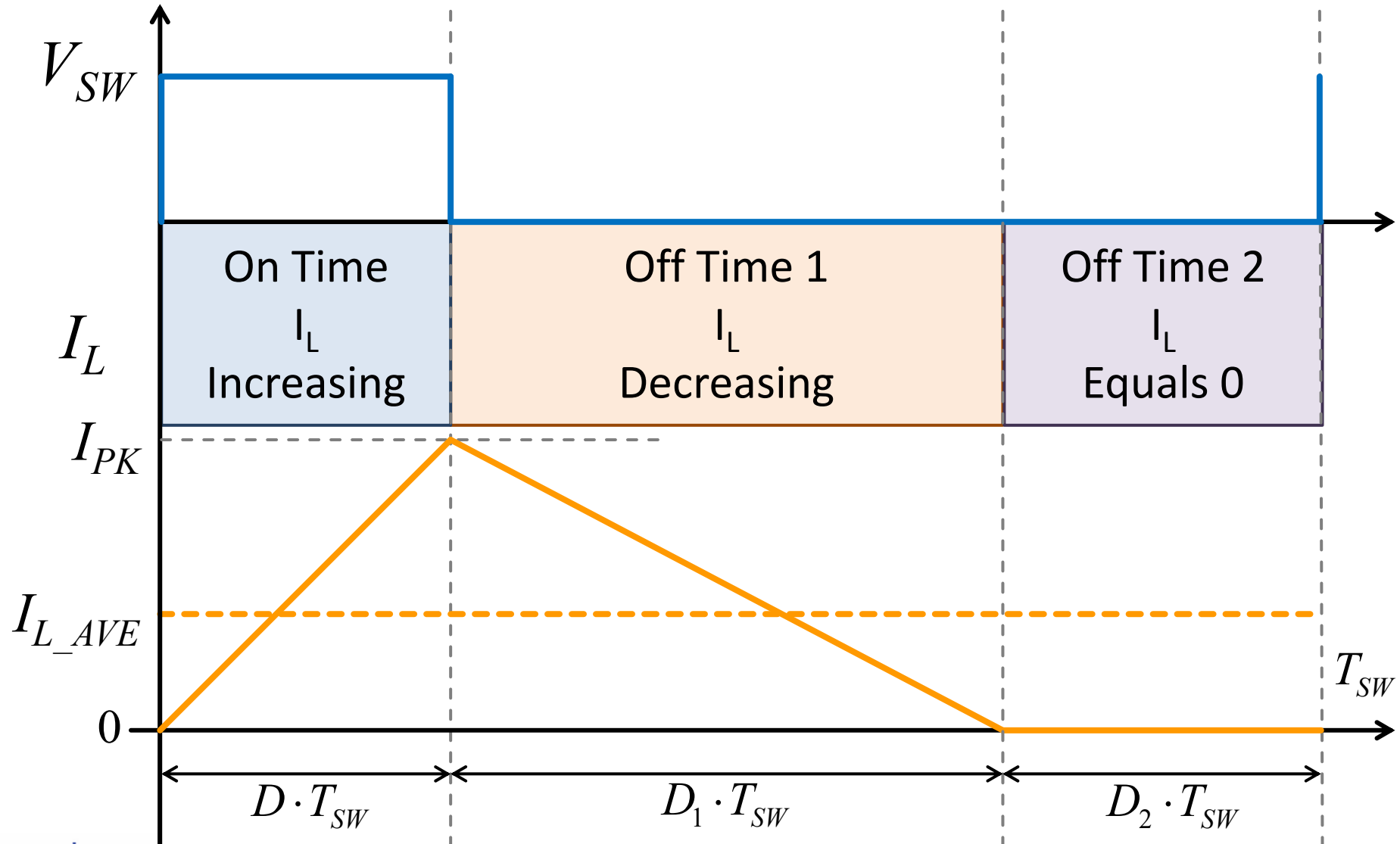

Conversion Ratio In DCM

Start With Inductor Voltages And Capacitor Currents In Each Of The Three Intervals

On Time

$$v_L(t) = V_{IN} - V_{OUT}$$

$$i_C(t) = i_L(t) - \frac{1}{R} \cdot V_{OUT}$$

Off Time 1

$$v_L(t) = -V_{OUT}$$

$$i_C(t) = i_L(t) - \frac{1}{R} \cdot V_{OUT}$$

Off Time 2

$$v_L(t) = 0$$

$$i_C(t) = -\frac{1}{R} \cdot V_{OUT}$$

Inductor Volt-Second Balance

$$v_L(T_{ON}) \cdot T_{ON} + v_L(T_{OFF1}) \cdot T_{OFF1} + v_L(T_{OFF2}) \cdot T_{OFF2} = 0$$

$$(V_{IN} - V_{OUT}) \cdot T_{ON} + (-V_{OUT}) \cdot T_{OFF1} + 0 \cdot T_{OFF2} = 0$$

$$(V_{IN} - V_{OUT}) \cdot D \cdot T_{SW} + (-V_{OUT}) \cdot D_1 \cdot T_{SW} = 0$$

$$(V_{IN} - V_{OUT}) \cdot D + (-V_{OUT}) \cdot D_1 = 0$$


$$D_1 \cdot V_{OUT} = (V_{IN} - V_{OUT}) \cdot D$$

$$V_{OUT} = \frac{D}{D + D_1} \cdot V_{IN}$$

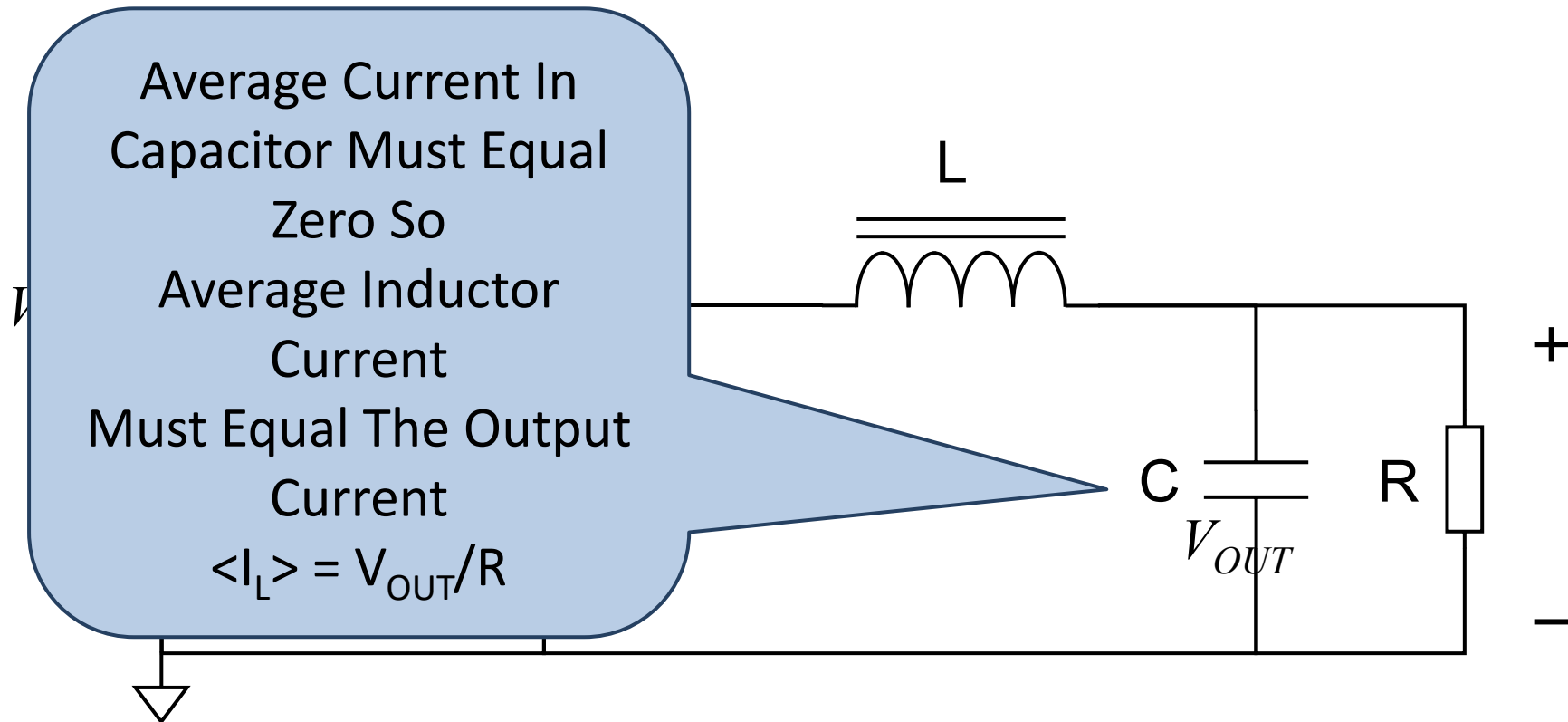
Problem: We Do Not
Know D_1 !

Capacitor Charge Balance

Time Consuming To Solve Analytically Because Inductor Current Is Not Constant. Use A Circuit Argument Instead.



Average Inductor Current Equals:

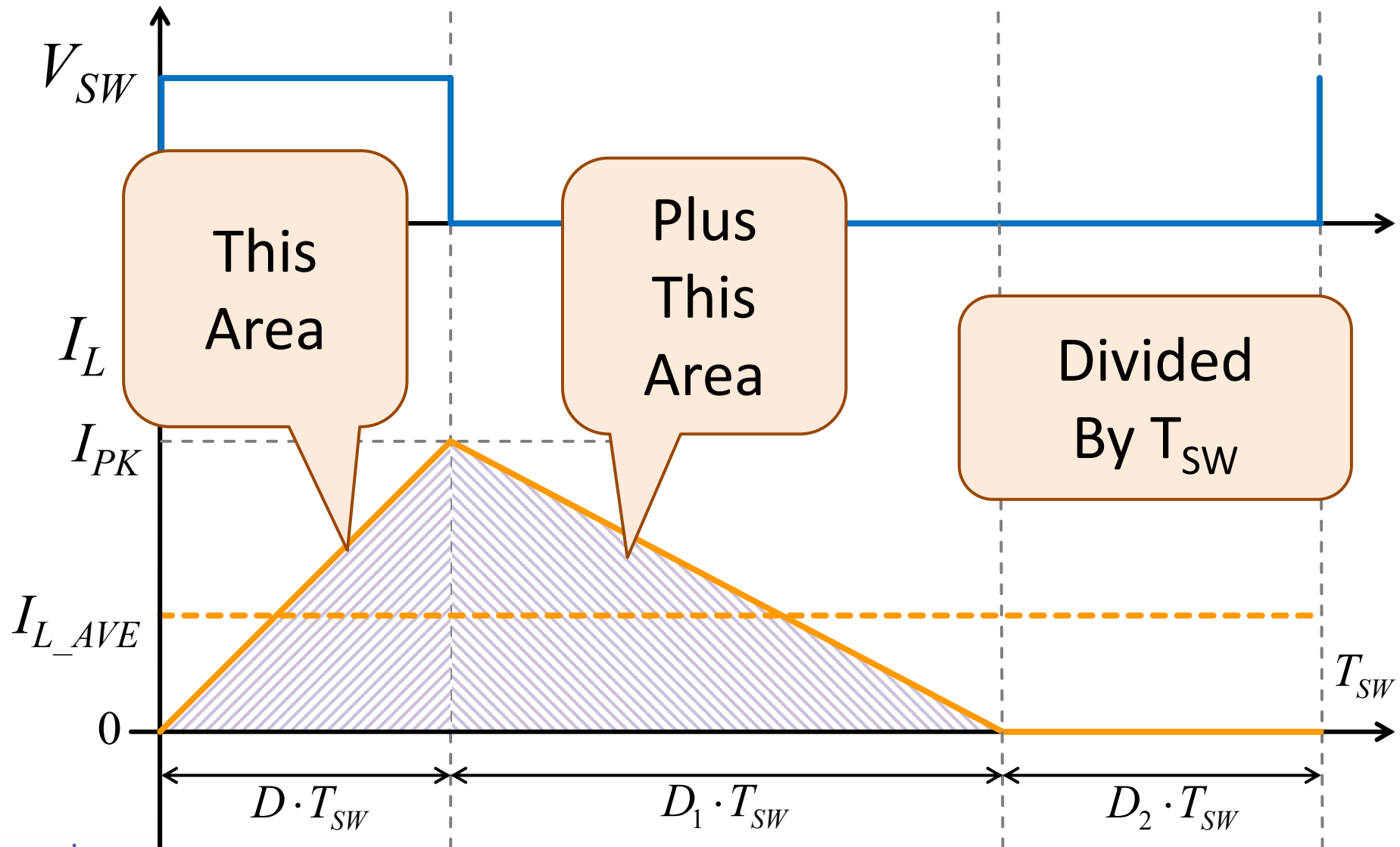

Average Inductor Current

$$I_{L_AVE} = \frac{\frac{1}{2} \cdot I_{PK} \cdot T_{ON} + \frac{1}{2} \cdot I_{PK} \cdot T_{OFF1}}{T_{SW}}$$
$$= \frac{1}{2} \cdot I_{PK} \cdot (D + D_1)$$

Calculating Average
By Geometry

$$I_{PK} = \frac{V_{IN} - V_{OUT}}{L} \cdot T_{ON} = \frac{V_{IN} - V_{OUT}}{L} \cdot D \cdot T_{SW}$$

We Need The
Peak Current

$$I_{L_AVE} = \frac{1}{2} \cdot \left(\frac{V_{IN} - V_{OUT}}{L} \cdot D \cdot T_{SW} \right) \cdot (D + D_1)$$
$$= \frac{D \cdot T_{SW}}{2 \cdot L} \cdot (V_{IN} - V_{OUT}) \cdot (D + D_1)$$

Substituting
Peak Current
Expression

DCM Conversion Ratio

$$I_{L_AVE} = \frac{1}{R} \cdot V_{OUT}$$

Result From Capacitor Charge Balance Analysis That the Average Inductor Current Must Equal The Output Current

$$\frac{1}{R} \cdot V_{OUT} = \frac{D \cdot T_{SW}}{2 \cdot L} \cdot (V_{IN} - V_{OUT}) \cdot (D + D_1)$$

Still Need D_1

$$V_{OUT} = \frac{D}{D + D_1} \cdot V_{IN}$$

Solve Expression for Output Voltage For D_1

$$D_1 = \frac{V_{IN} - V_{OUT}}{V_{OUT}} \cdot D$$

Substitute This Into The Expression Above

DCM Conversion Ratio

Now Solve This For V_{OUT}

$$\frac{1}{R} \cdot V_{OUT} = \frac{D \cdot T_{SW}}{2 \cdot L} \cdot (V_{IN} - V_{OUT}) \cdot \left(D + \left(\frac{V_{IN} - V_{OUT}}{V_{OUT}} \cdot D \right) \right)$$

$$V_{OUT} = \frac{D^2 \cdot R \cdot T_{SW}}{2 \cdot L} \cdot (V_{IN} - V_{OUT}) \cdot \left(1 + \frac{V_{IN} - V_{OUT}}{V_{OUT}} \right)$$

$$= \frac{D^2 \cdot R \cdot T_{SW}}{2 \cdot L} \cdot (V_{IN} - V_{OUT}) \cdot \left(\frac{V_{IN}}{V_{OUT}} \right)$$

$$V_{OUT}^2 = \frac{D^2 \cdot R \cdot T_{SW}}{2 \cdot L} \cdot (V_{IN} - V_{OUT}) \cdot V_{IN}$$

DCM Conversion Ratio

$$\alpha = \frac{D^2 \cdot R \cdot T_{SW}}{2 \cdot L}$$

To Make The Algebra Easier To Follow, Define Alpha

$$V_{OUT}^2 = \alpha \cdot V_{IN}^2 - \alpha \cdot V_{IN} \cdot V_{OUT}$$

Substituting Alpha

$$V_{OUT}^2 + \alpha \cdot V_{IN} \cdot V_{OUT} - \alpha \cdot V_{IN}^2 = 0$$

$$V_{OUT} = \frac{-\alpha \cdot V_{IN} \pm \sqrt{(\alpha \cdot V_{IN})^2 - 4 \cdot (-\alpha \cdot V_{IN}^2)}}{2}$$

Applying The Formula For The Solution To A Quadratic Equation

DCM Conversion Ratio

$$\begin{aligned} V_{OUT} &= \frac{-\alpha \cdot V_{IN} \pm \sqrt{(\alpha \cdot V_{IN})^2 + 4 \cdot \frac{(\alpha^2 \cdot V_{IN}^2)}{\alpha}}}{2} \\ &= \frac{-\alpha \cdot V_{IN} \pm \alpha \cdot V_{IN} \cdot \sqrt{1 + \frac{4}{\alpha}}}{2} \\ \frac{V_{OUT}}{V_{IN}} &= \alpha \cdot \frac{-1 + \sqrt{1 + \frac{4}{\alpha}}}{2} \cdot \frac{1 + \sqrt{1 + \frac{4}{\alpha}}}{1 + \sqrt{1 + \frac{4}{\alpha}}} \\ &= \frac{\alpha}{2} \cdot \frac{-1 - \sqrt{1 + \frac{4}{\alpha}} + \sqrt{1 + \frac{4}{\alpha}} + \sqrt{1 + \frac{4}{\alpha}} \cdot \sqrt{1 + \frac{4}{\alpha}}}{1 + \sqrt{1 + \frac{4}{\alpha}}} \end{aligned}$$

DCM Conversion Ratio

$$\frac{V_{OUT}}{V_{IN}} = \frac{\alpha}{2} \cdot \frac{-1 + \left(1 + \frac{4}{\alpha}\right)}{1 + \sqrt{1 + \frac{4}{\alpha}}} = \frac{\alpha}{2} \cdot \frac{\frac{4}{\alpha}}{1 + \sqrt{1 + \frac{4}{\alpha}}}$$

$$= \frac{2}{1 + \sqrt{1 + \frac{4}{\alpha}}}$$

$$= \frac{2}{1 + \sqrt{1 + \frac{4}{\frac{D^2 \cdot R \cdot T_{SW}}{2 \cdot L}}}}$$


$$= \frac{2}{1 + \sqrt{1 + \frac{4}{D^2} \cdot \frac{2 \cdot L}{R \cdot T_{SW}}}}$$

DCM Conversion Ratio Is Nonlinear And Depends On Load Resistance, Output Inductance, And Switching Frequency


APPENDIX III.

More Isolated Buck Converters: Forward Converters, Half And Full Bridge Converters


One Transistor Forward Converter

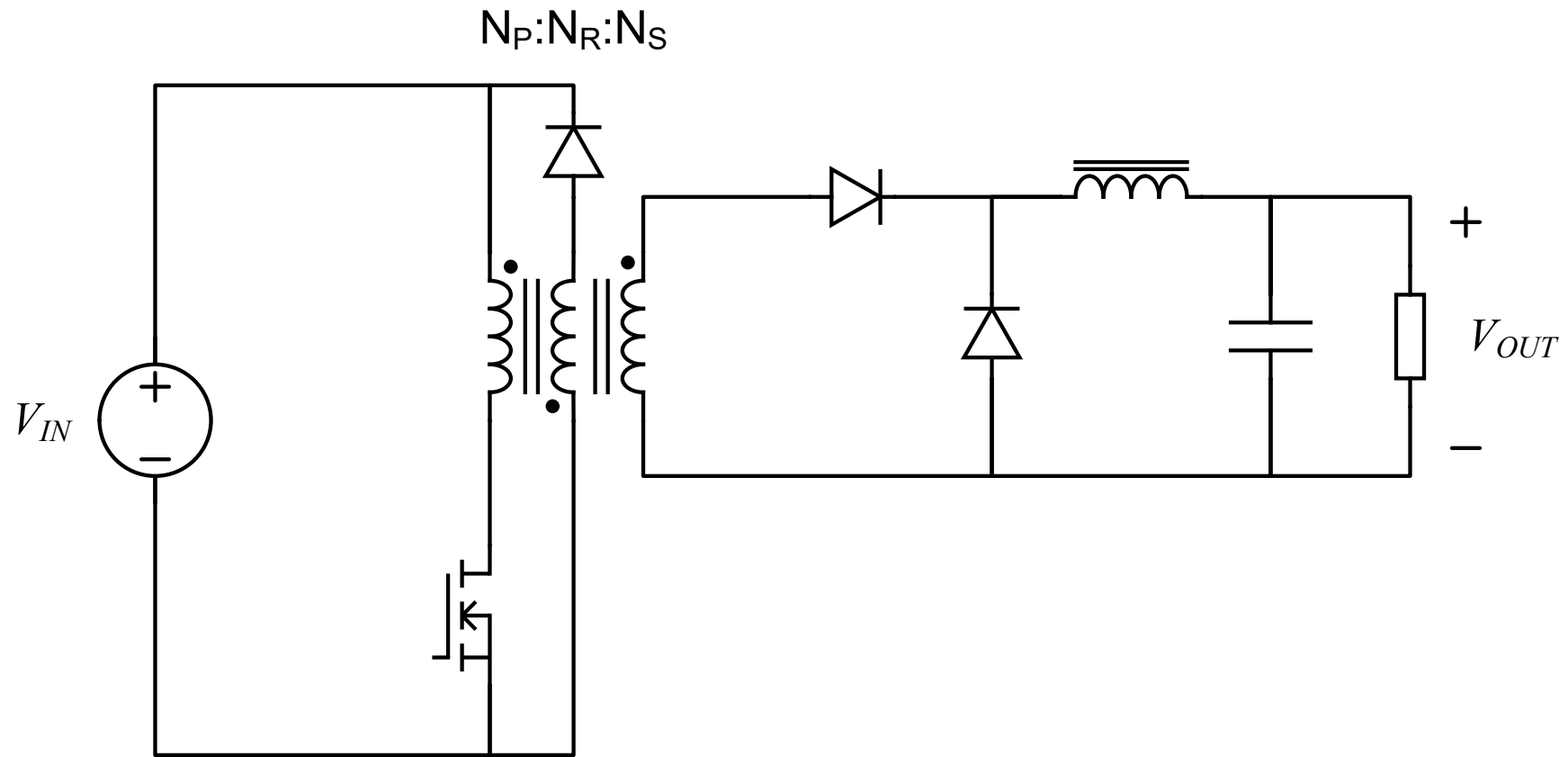

One Transistor Forward Converter

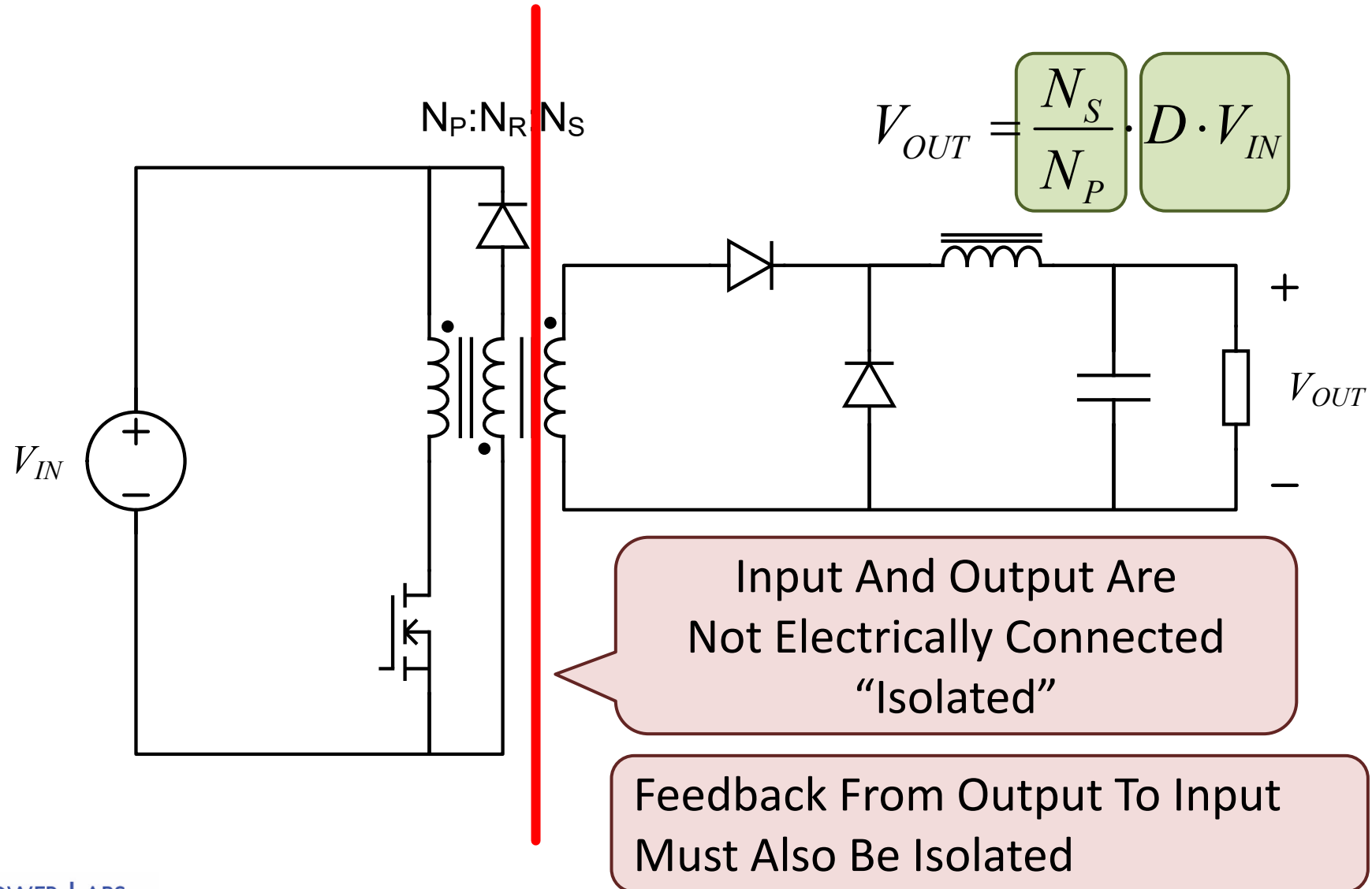


One Transistor Forward Converter On Time

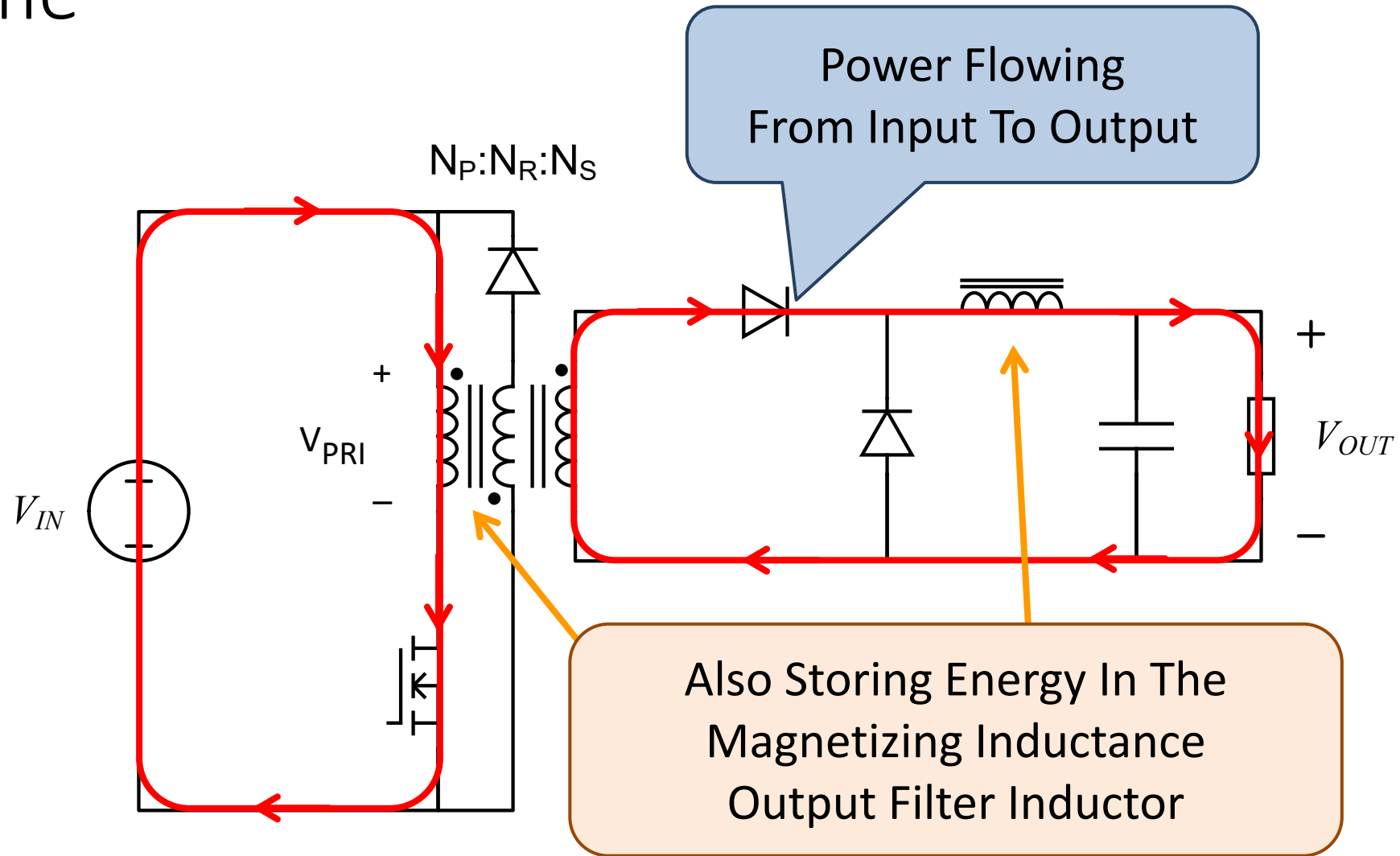


One Transistor Forward Converter

Reset Time

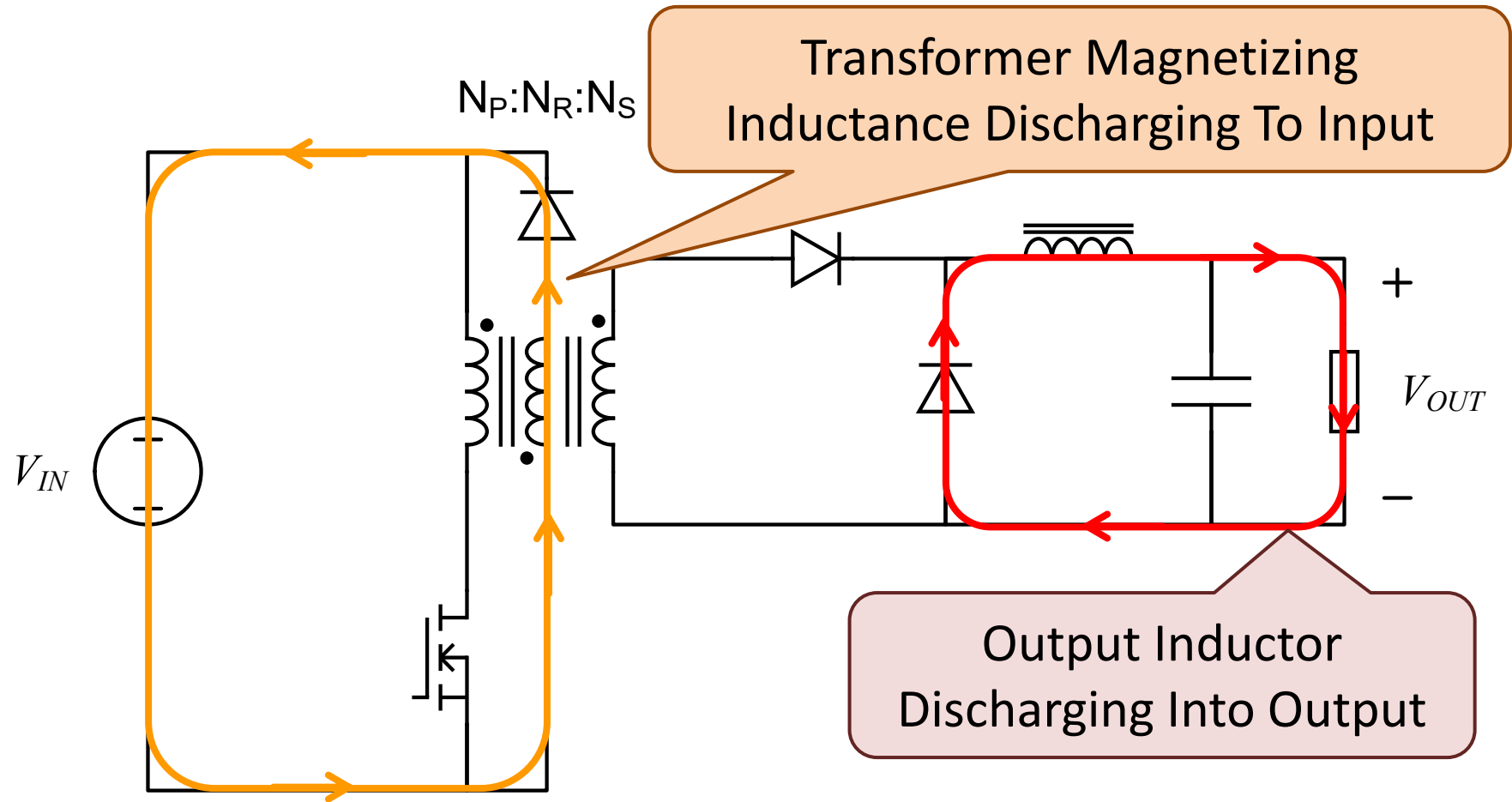


One Transistor Forward Converter

Reset Time

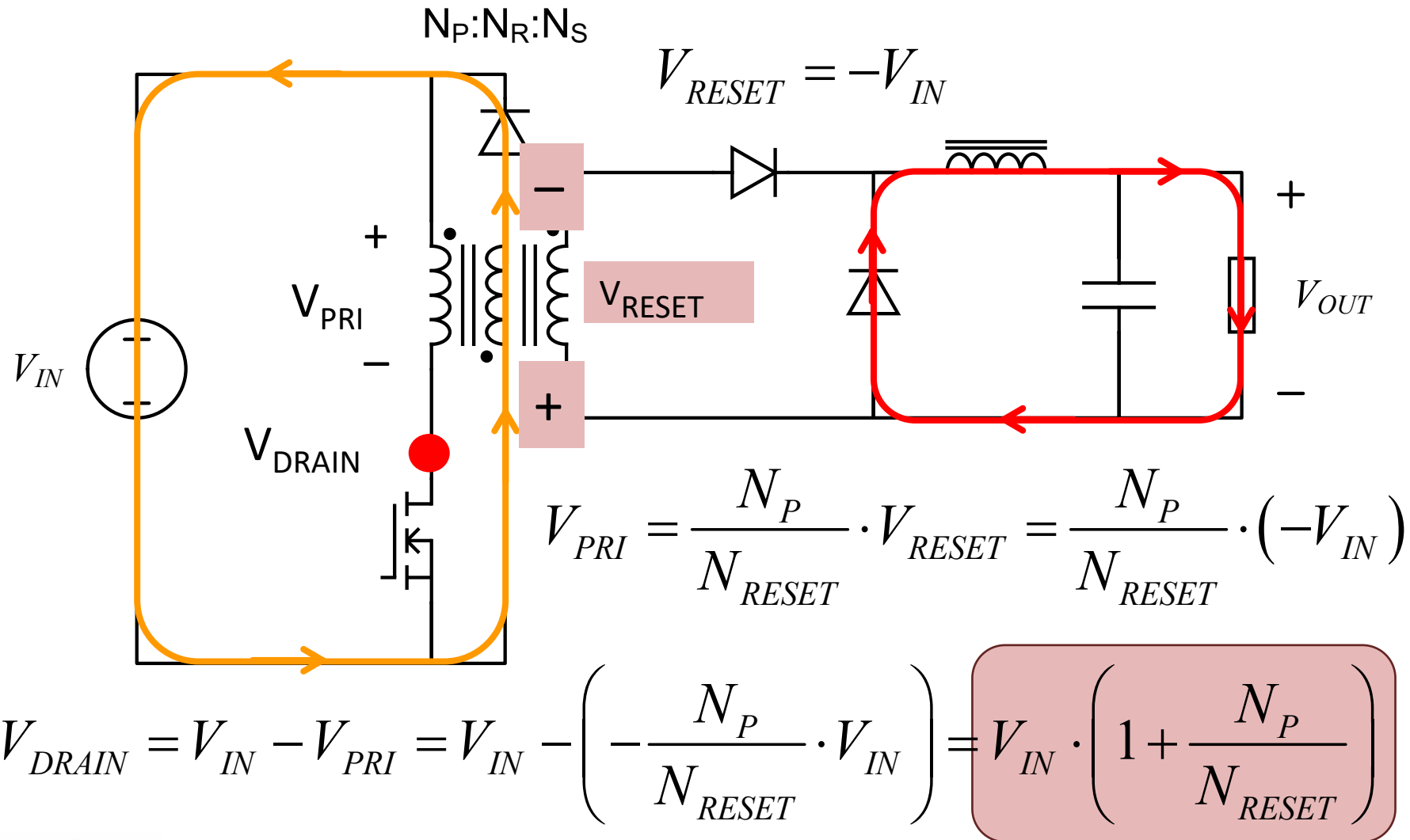

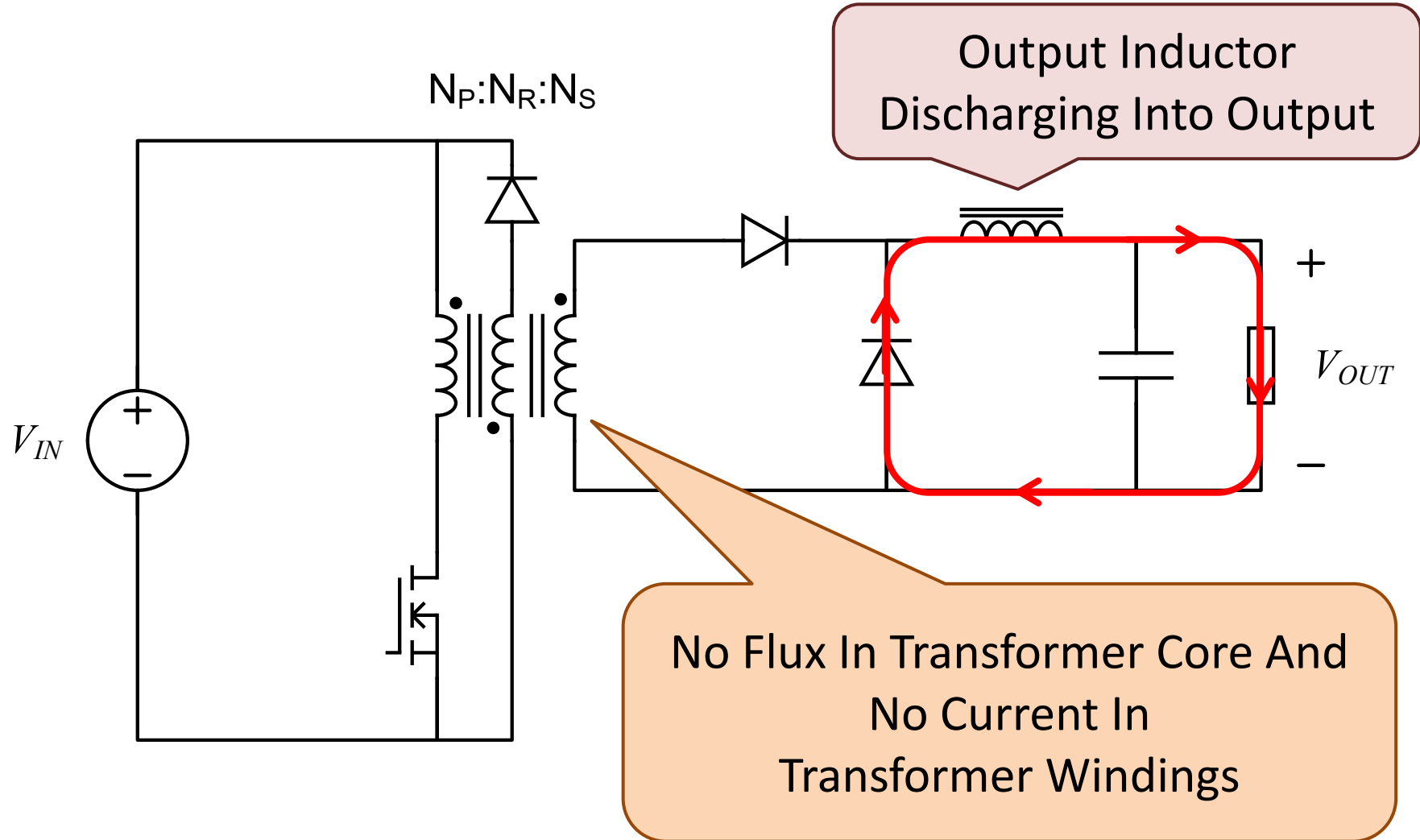One Transistor Forward Converter Idle Time



One Transistor Forward Converter Conversion Ratio

$$V_L(T_{ON}) \cdot T_{ON} + V_L(T_{RESET}) \cdot T_{RESET} + V_L(T_{IDLE}) \cdot T_{IDLE} = 0$$

Inductor Volt-Second Balance

$$\left(\frac{N_S}{N_P} \cdot V_{IN} - V_{OUT} \right) \cdot T_{ON} + (-V_{OUT}) \cdot T_{RESET} + (-V_{OUT}) \cdot T_{IDLE} = 0$$

$$\left(\frac{N_S}{N_P} \cdot V_{IN} - V_{OUT} \right) \cdot T_{ON} + (-V_{OUT}) \cdot (T_{RESET} + T_{IDLE}) = 0$$

$$\left(\frac{N_S}{N_P} \cdot V_{IN} - V_{OUT} \right) \cdot T_{ON} + (-V_{OUT}) \cdot T_{OFF} = 0$$

$$\left(\frac{N_S}{N_P} \cdot V_{IN} - V_{OUT} \right) \cdot D \cdot T_{SW} + (-V_{OUT}) \cdot (1-D) \cdot T_{SW} = 0$$

$$\left(\frac{N_S}{N_P} \cdot V_{IN} - V_{OUT} \right) \cdot D + (-V_{OUT}) \cdot (1-D) = 0$$

$$D \cdot \frac{N_S}{N_P} \cdot V_{IN} - D \cdot V_{OUT} - V_{OUT} + D \cdot V_{OUT} = 0$$


$$D \cdot \frac{N_S}{N_P} \cdot V_{IN} - V_{OUT} = 0$$

$$V_{OUT} = D \cdot \frac{N_S}{N_P} \cdot V_{IN}$$


During On Time Voltage At Input To Inductor Is the Input Voltage Multiplied By the Transformer Turns Ratio

Same As The Buck Converter Except For The Transformer Turns Ratio


Forward Converter Simulation Schematic

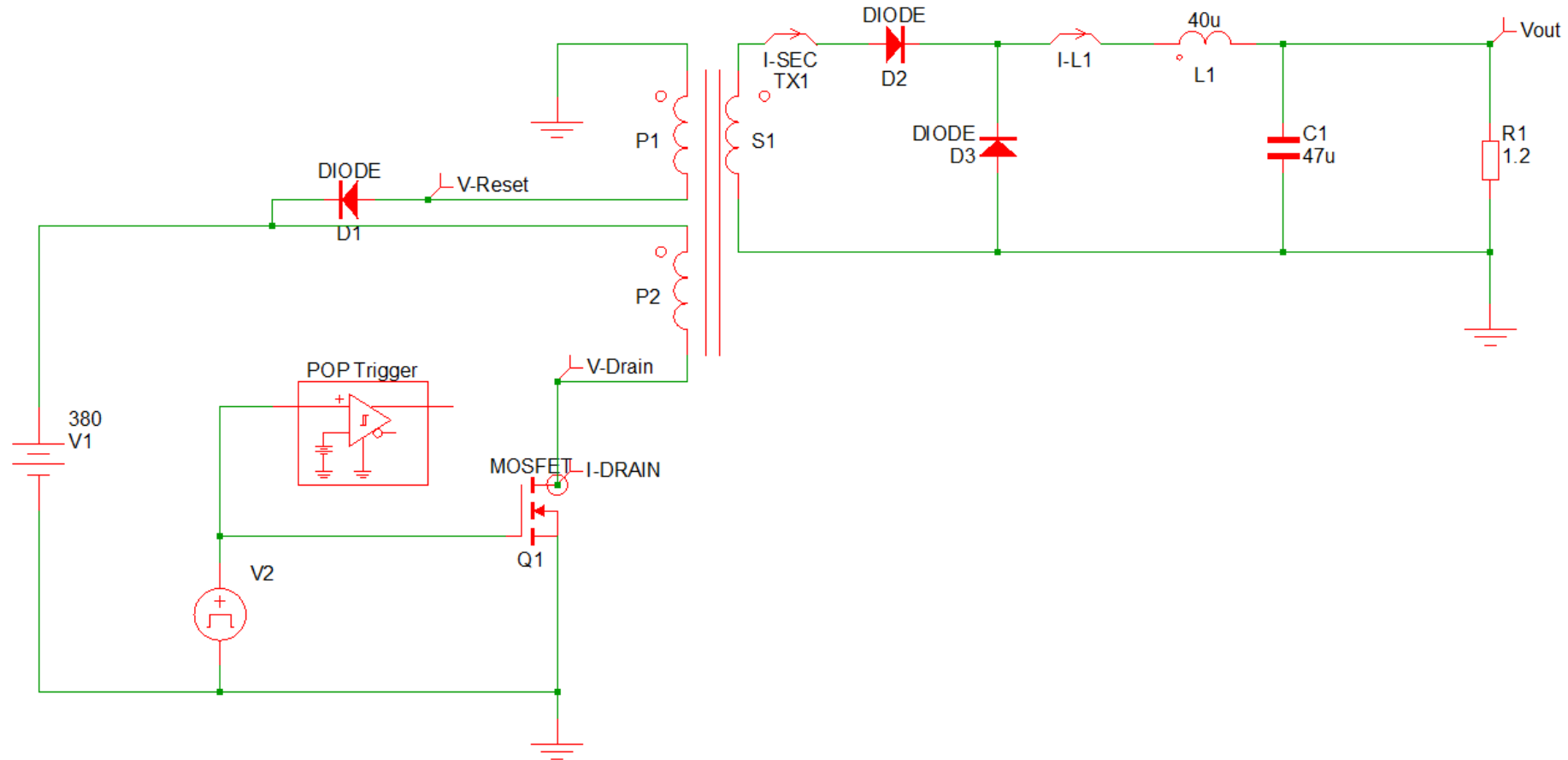

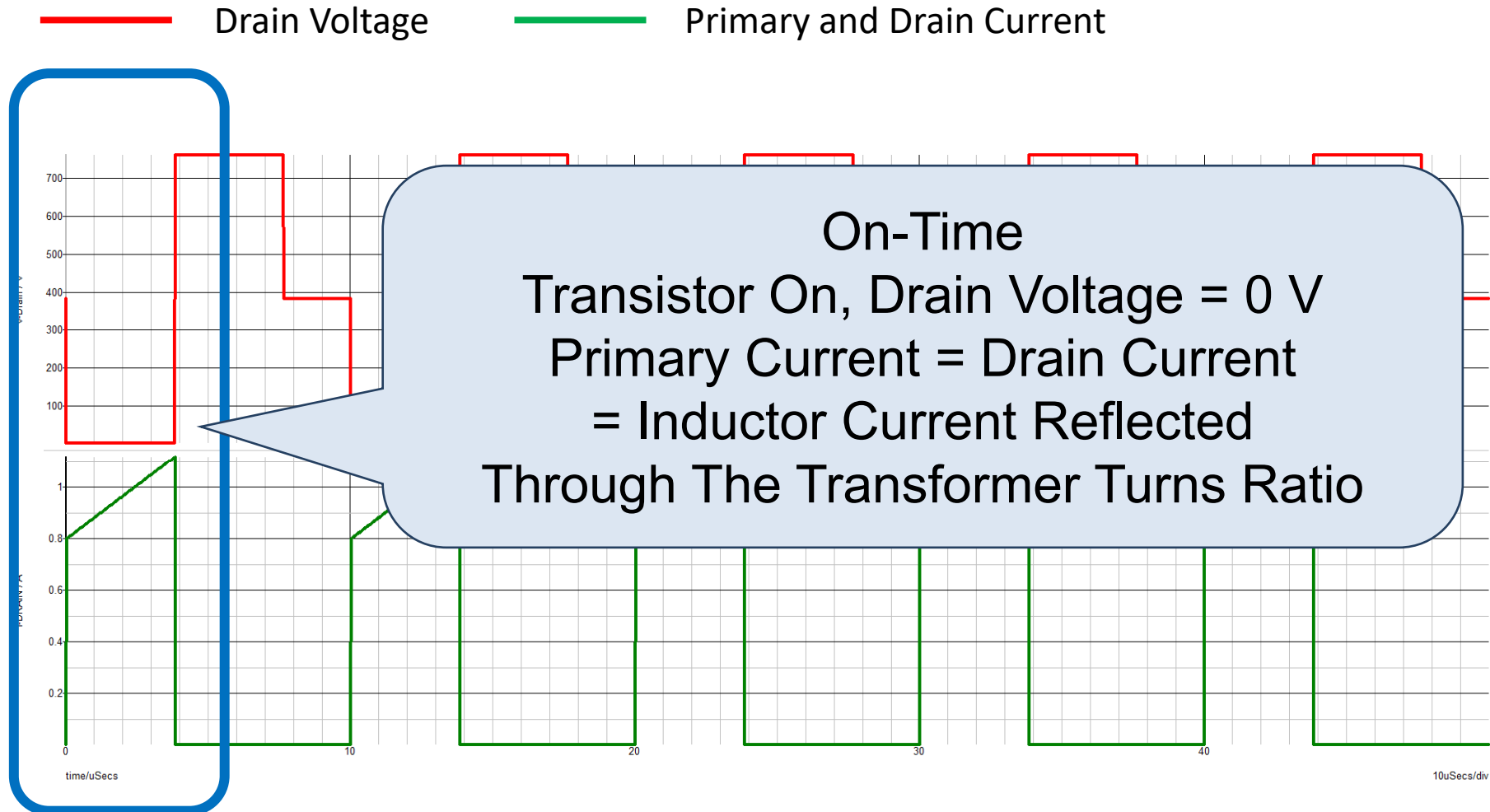
Forward Converter Simulation Primary Waveforms



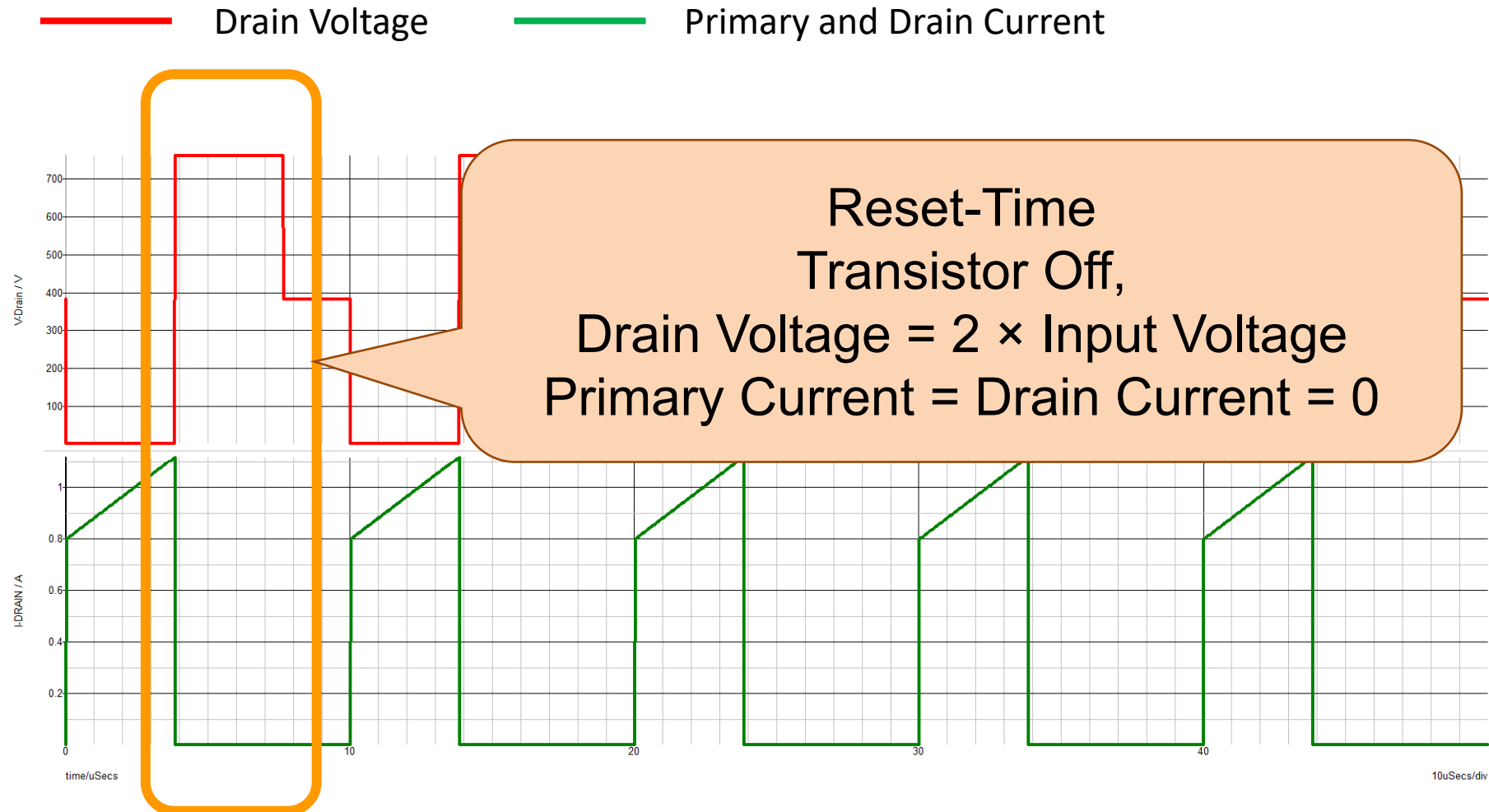Forward Converter Simulation Primary Waveforms



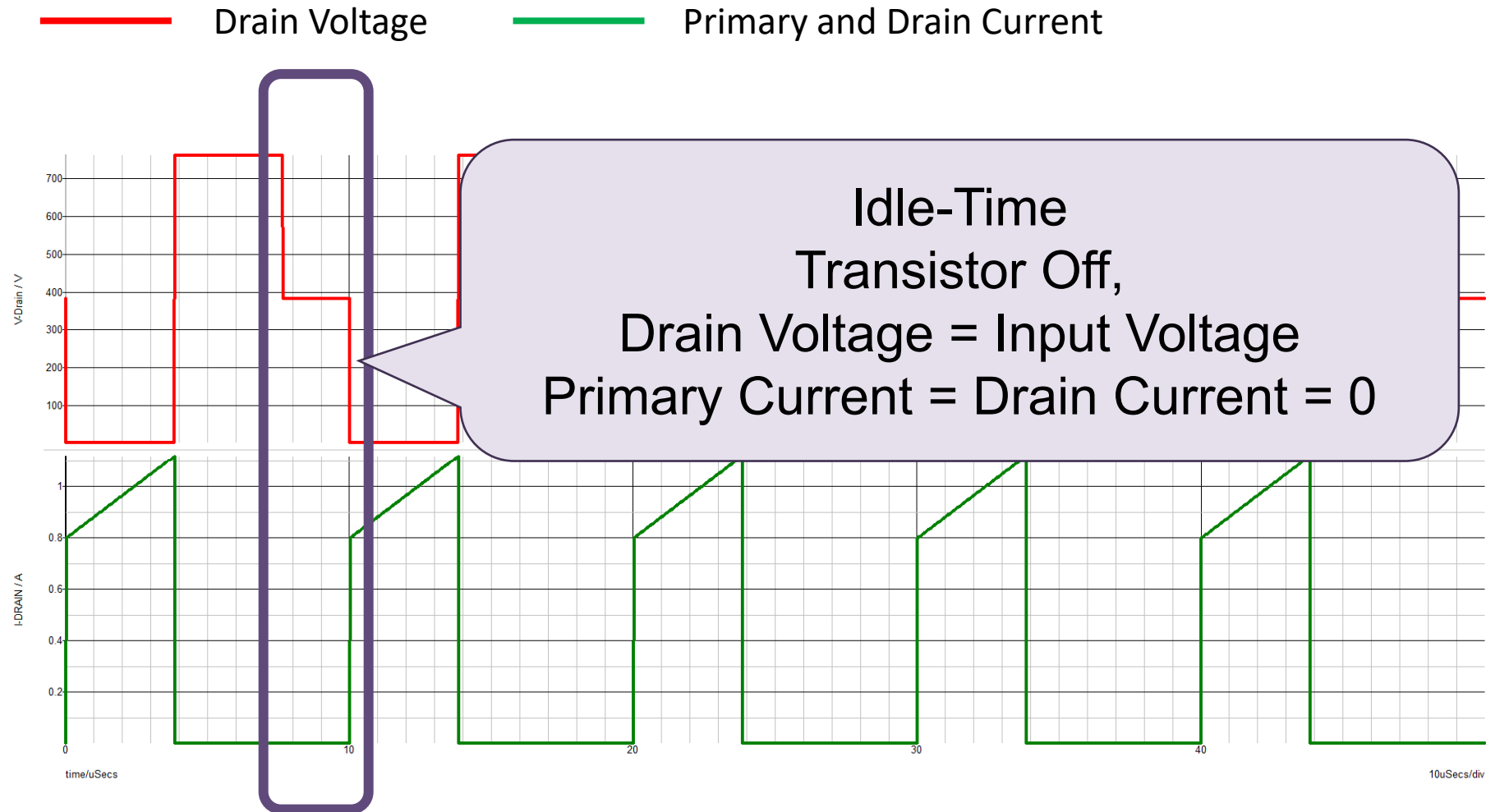
Forward Converter Simulation Primary Waveforms



Forward Converter Simulation


Secondary Waveforms

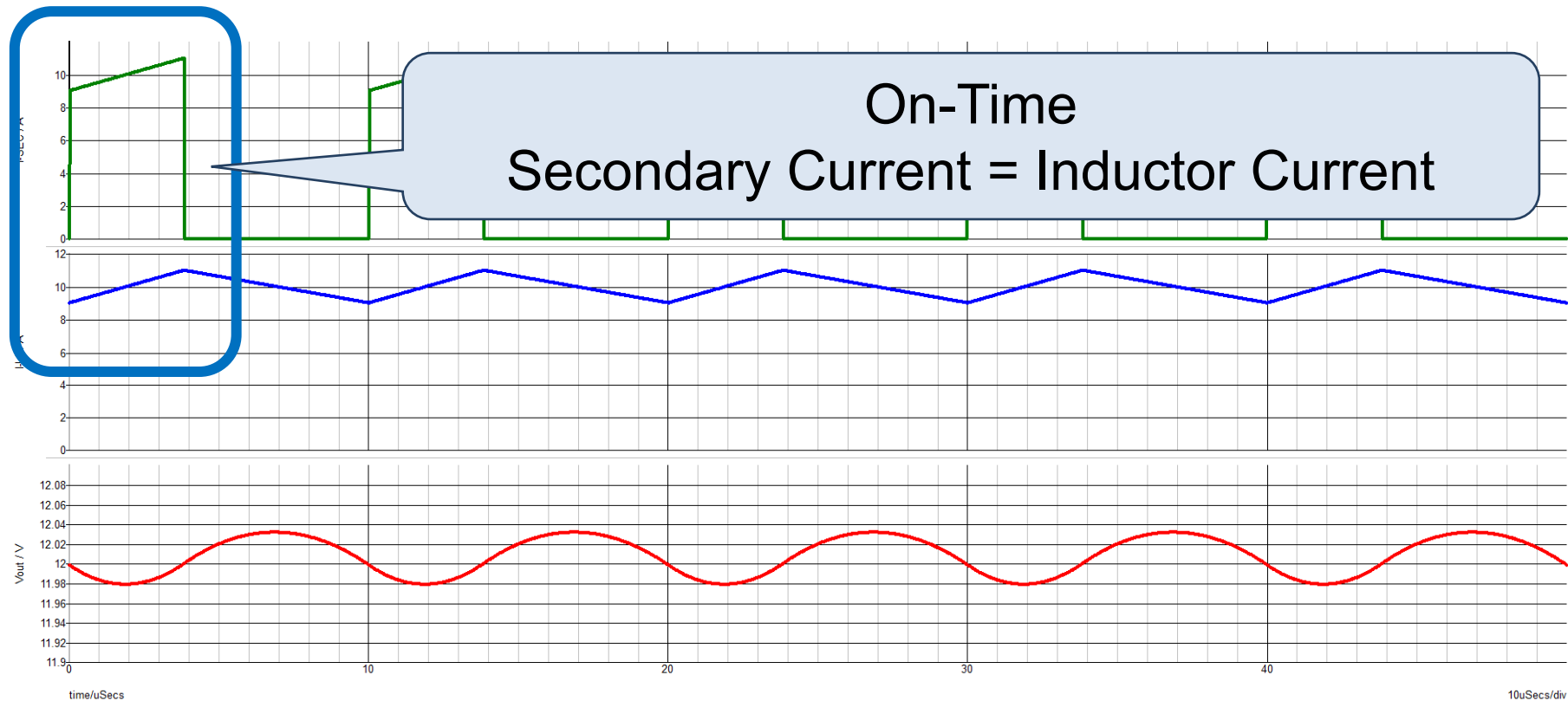— Secondary Current — Inductor Current
— Output Voltage (Scaled To Show Ripple Voltage)




Forward Converter Simulation Secondary Waveforms

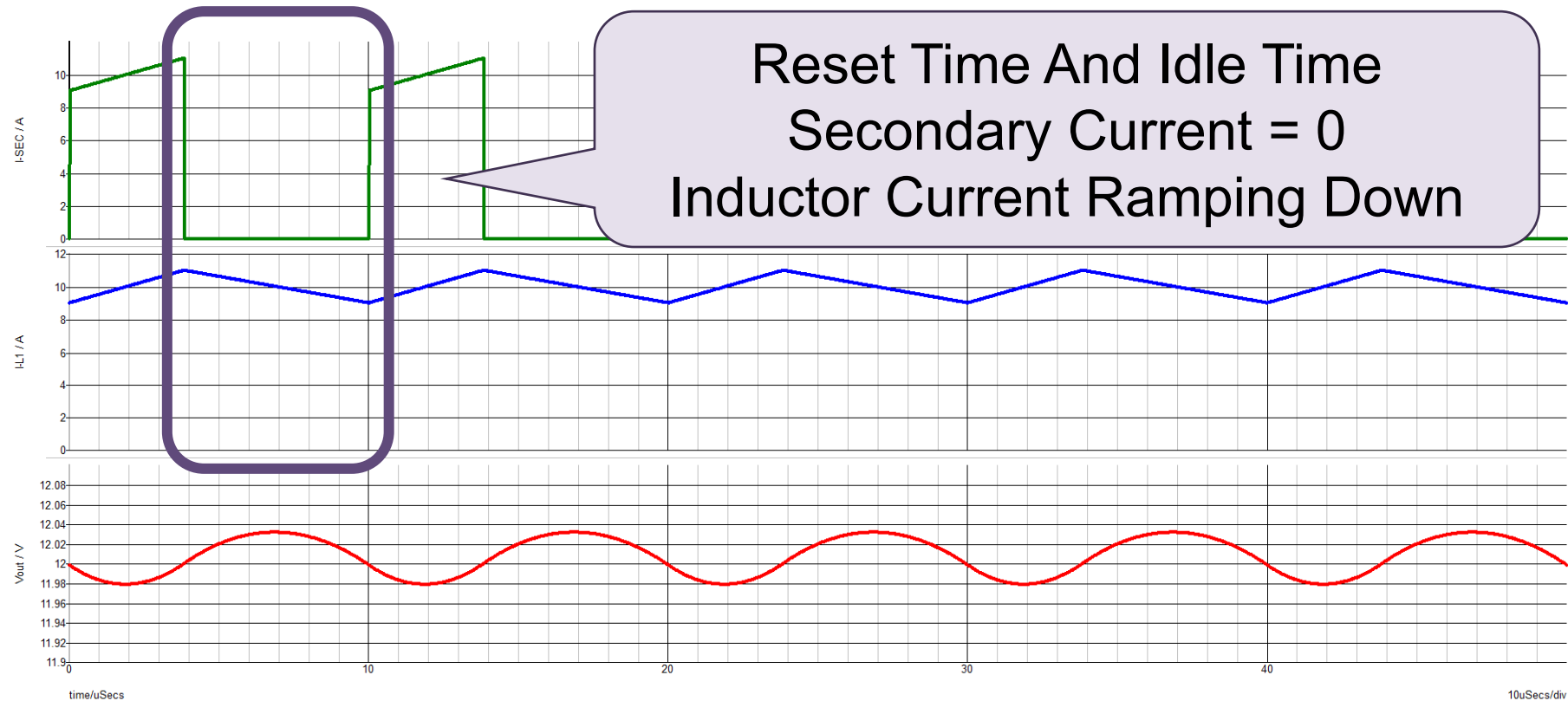— Secondary Current — Inductor Current
— Output Voltage (Scaled To Show Ripple Voltage)




Forward Converter Simulation Secondary Waveforms

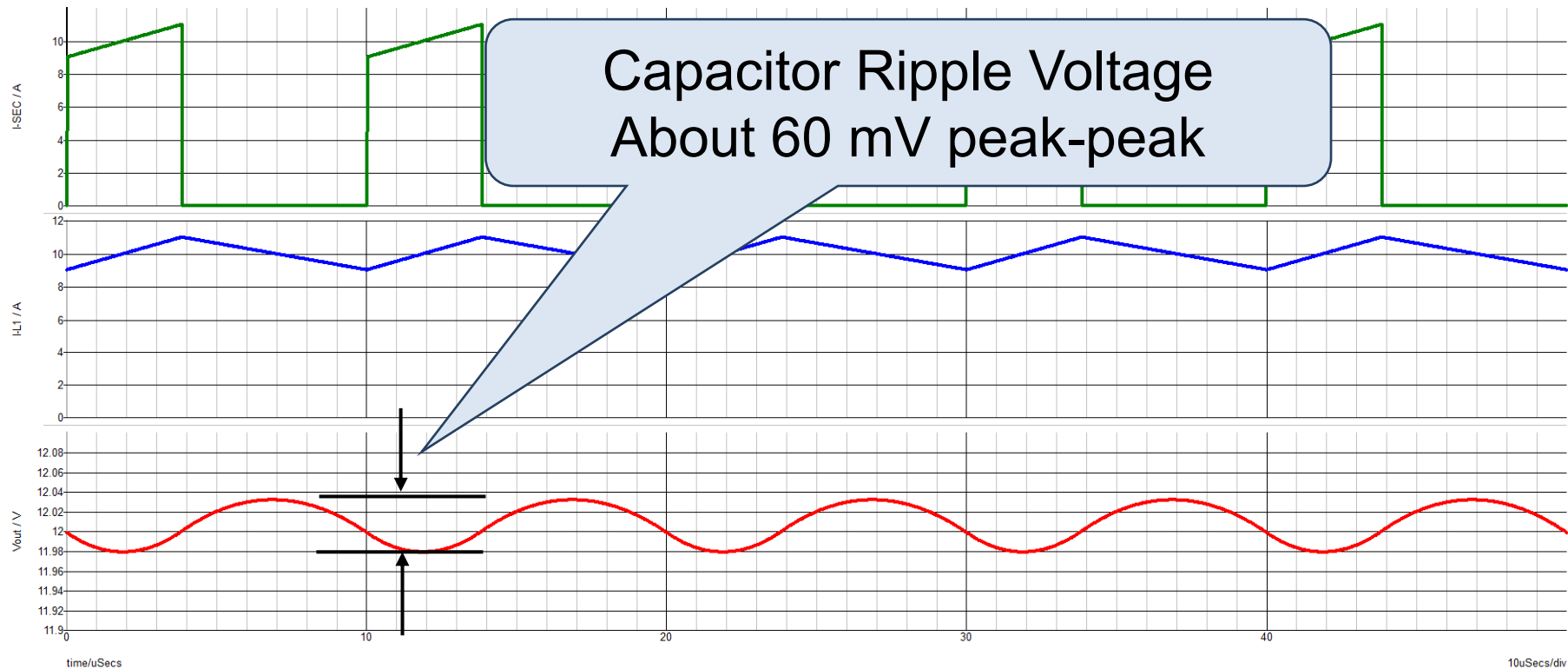— Secondary Current — Inductor Current
— Output Voltage (Scaled To Show Ripple Voltage)




Forward Converter Simulation Secondary Waveforms

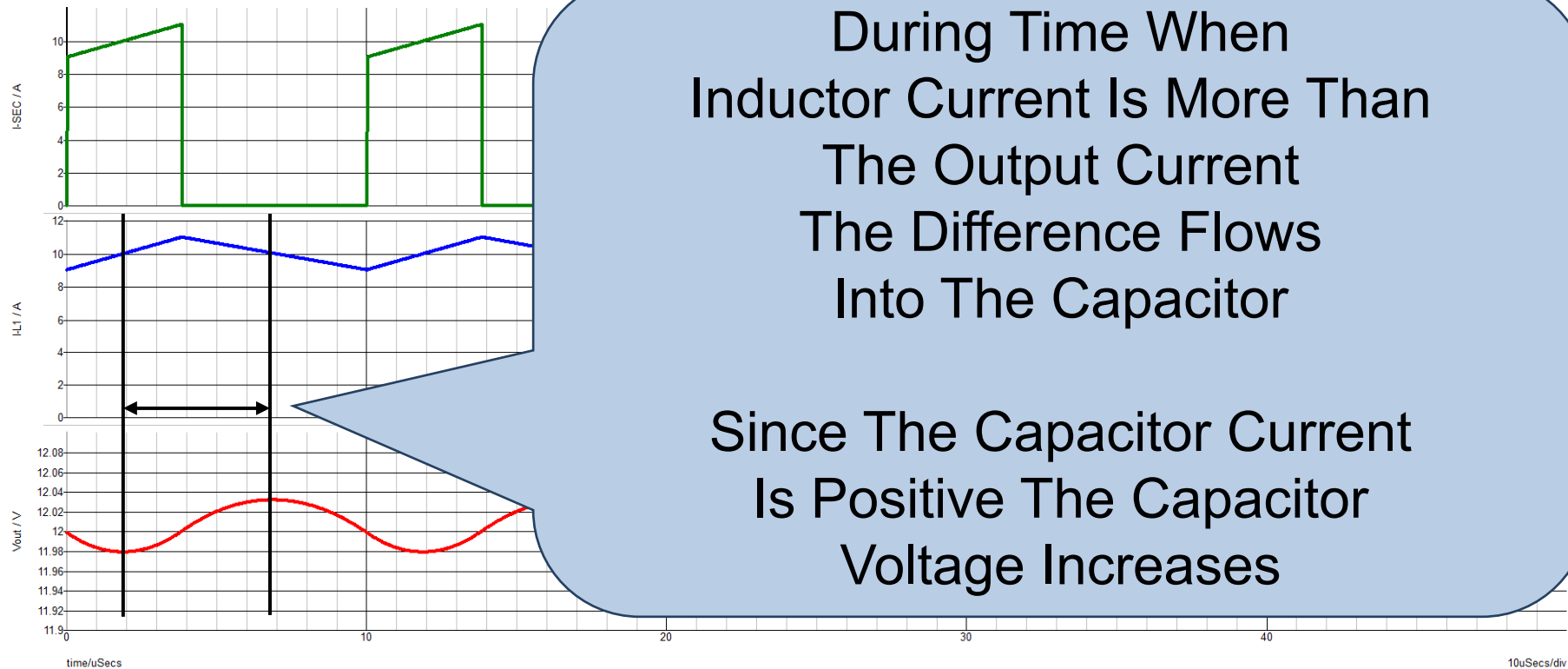— Secondary Current — Inductor Current
— Output Voltage (Scaled To Show Ripple Voltage)




Forward Converter Simulation Secondary Waveforms

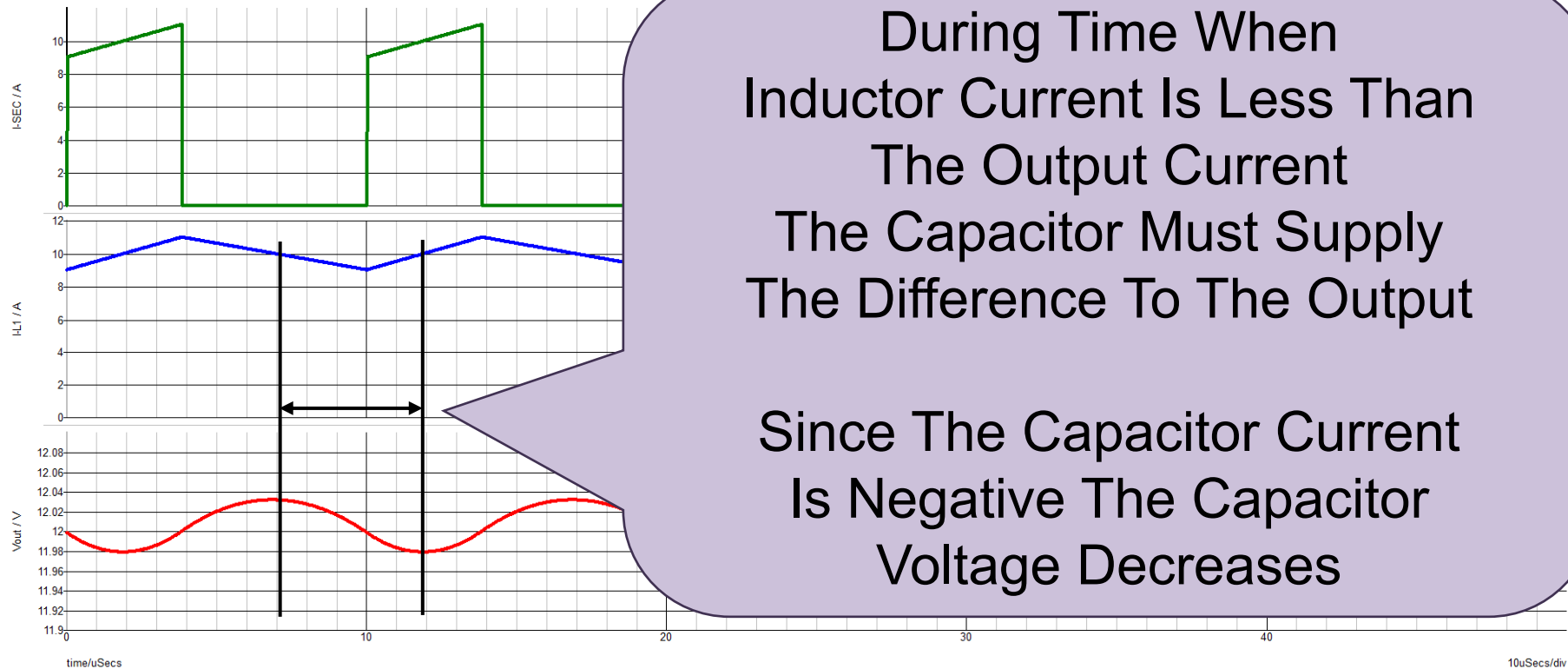— Secondary Current — Inductor Current
— Output Voltage (Scaled To Show Ripple Voltage)



Multiple Output Forward Converter

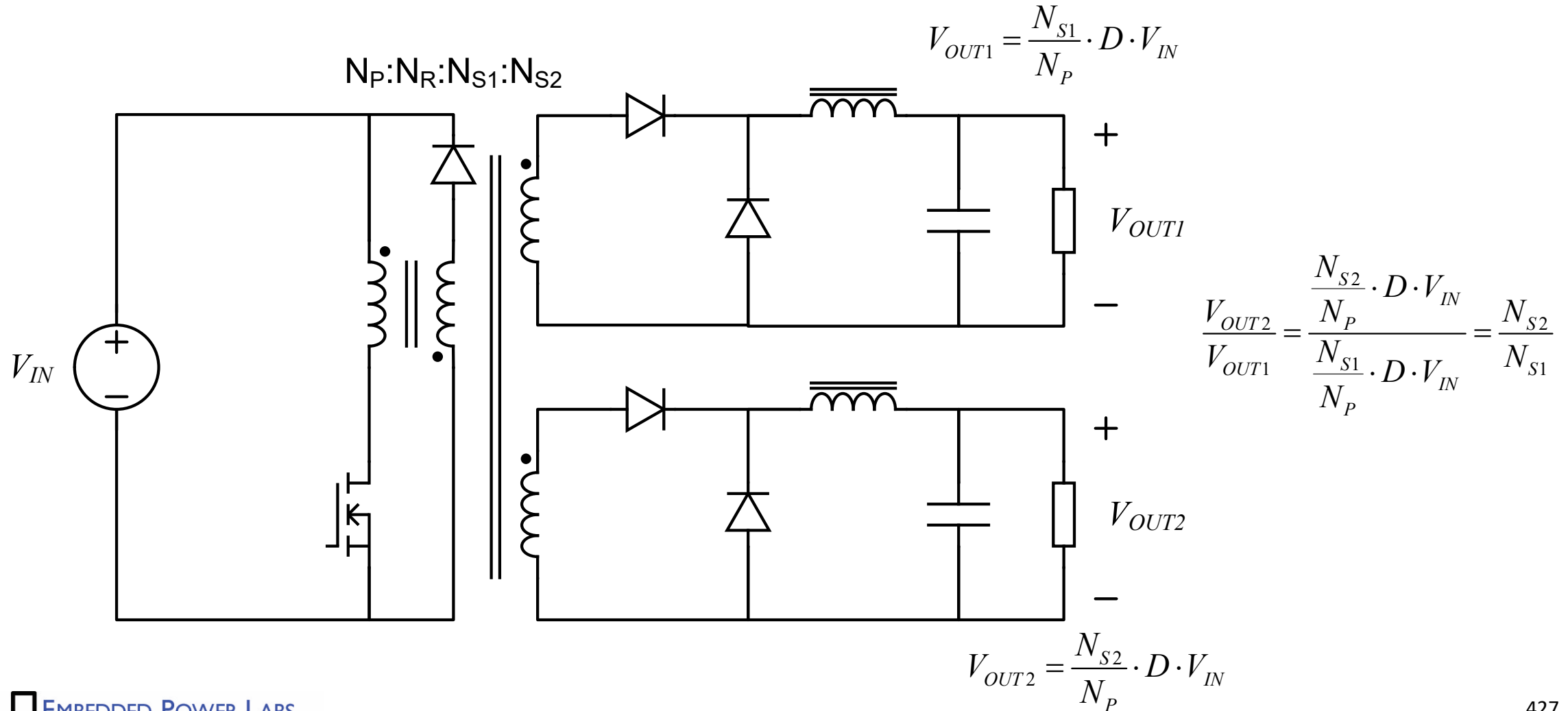

Forward Converter


Advantages

- Isolated
- Good For
50 W To 500 W
- Multiple Isolated Outputs
Possible
- Easy To Control


Disadvantages

- Transformer Needed
- High Voltage Stress On
Transistor And Diode


Two Transistor Forward Converter

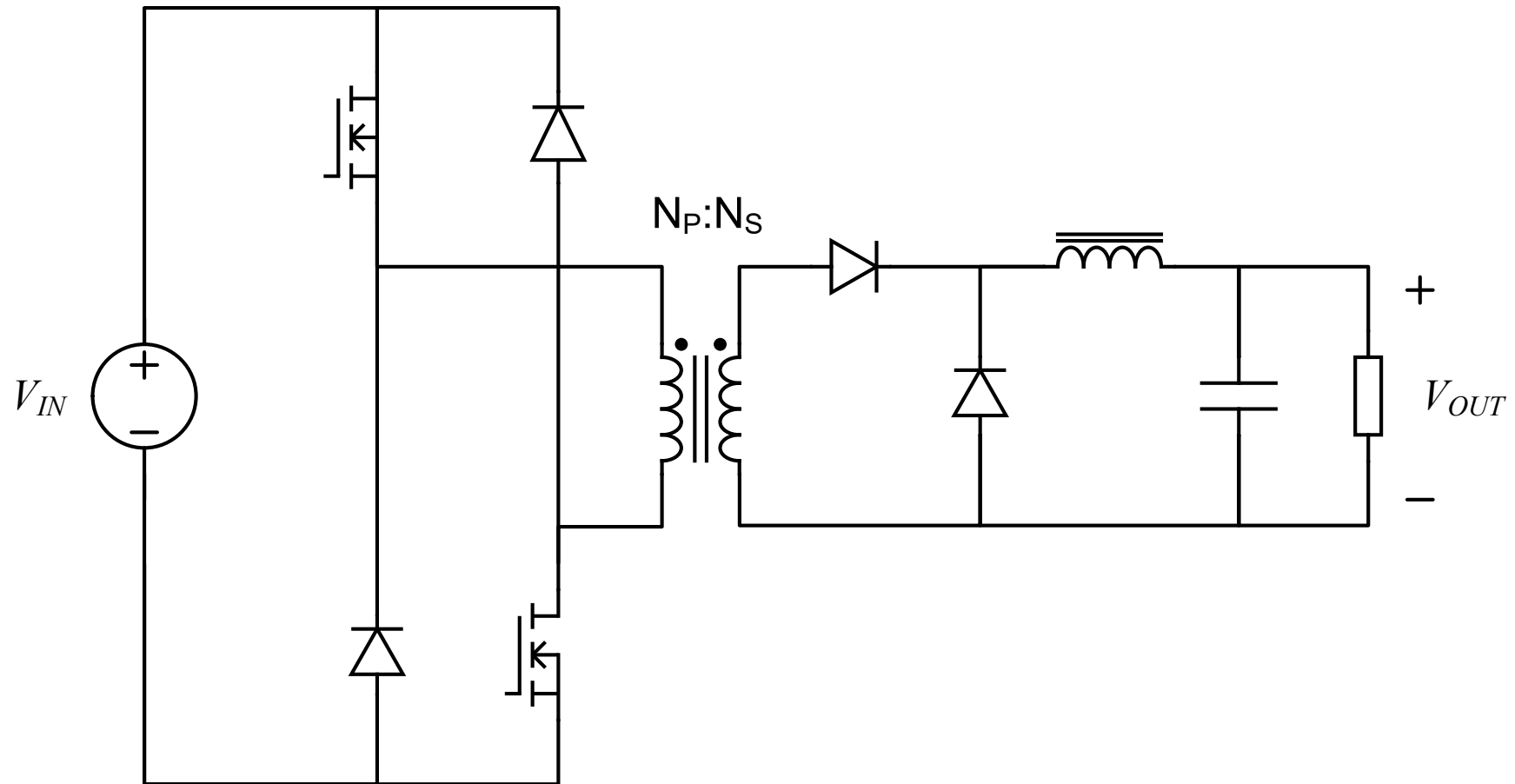


Two Transistor Forward Converter On-Time

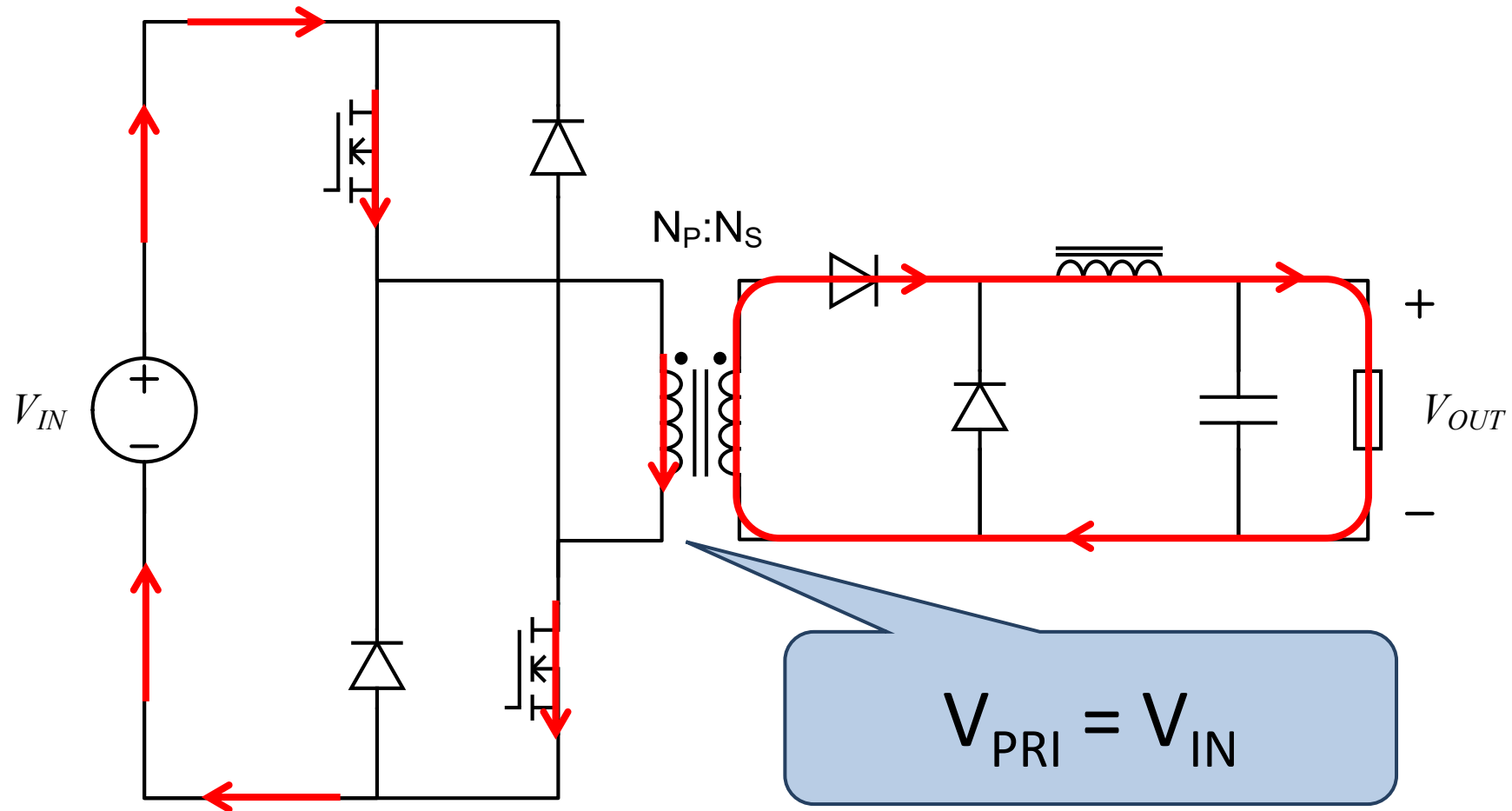

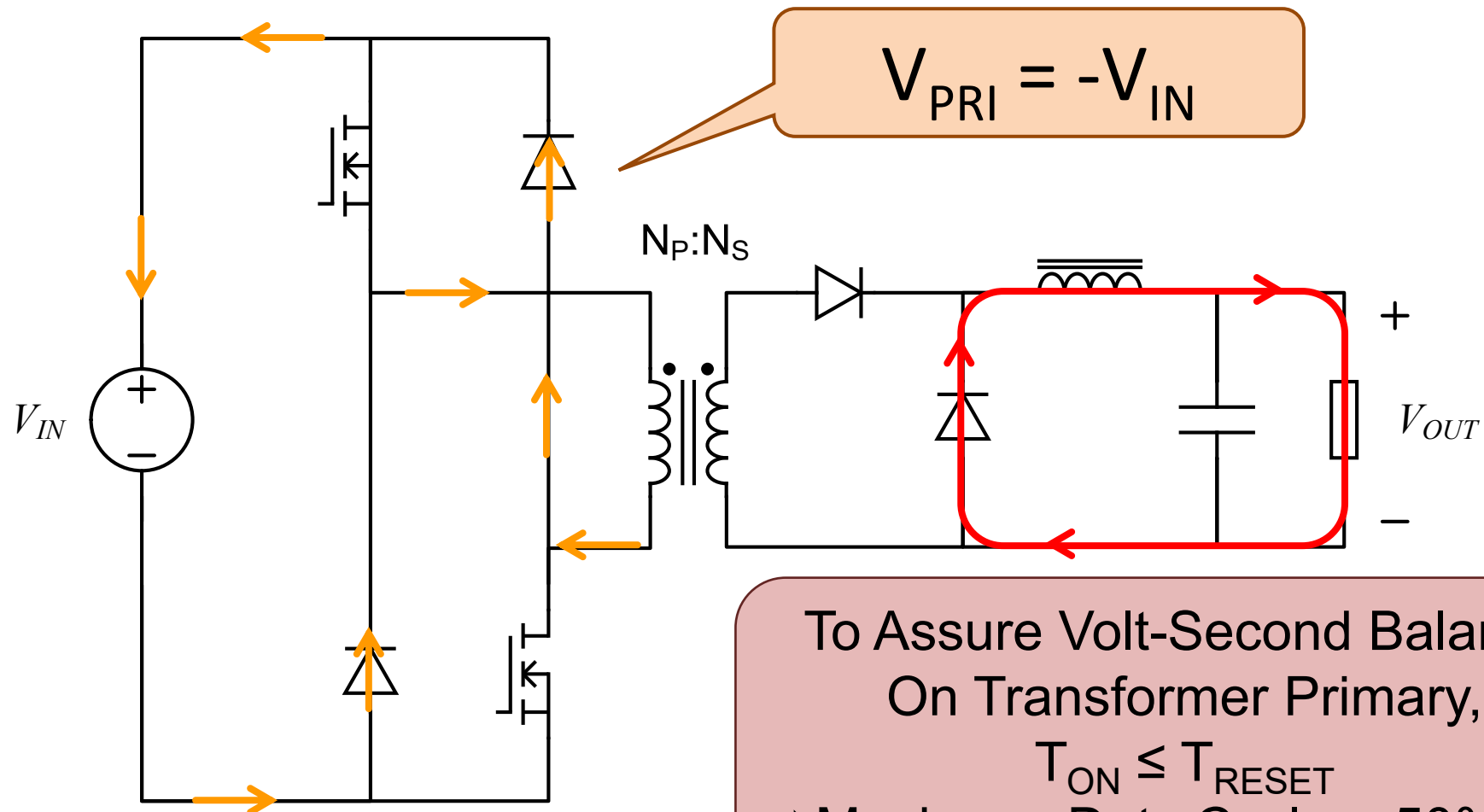
Two Transistor Forward Converter Reset-Time



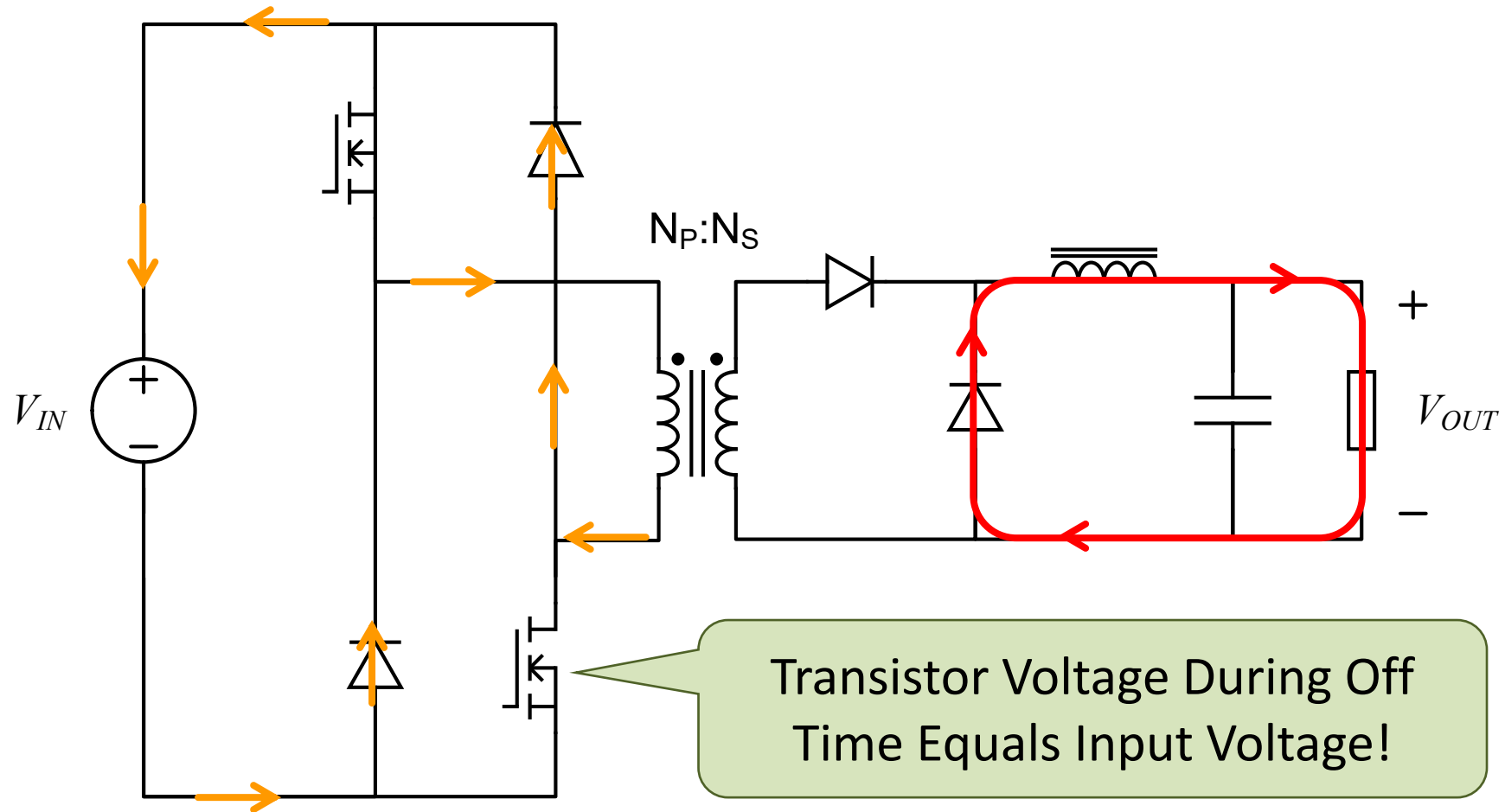Two Transistor Forward Converter Reset-Time



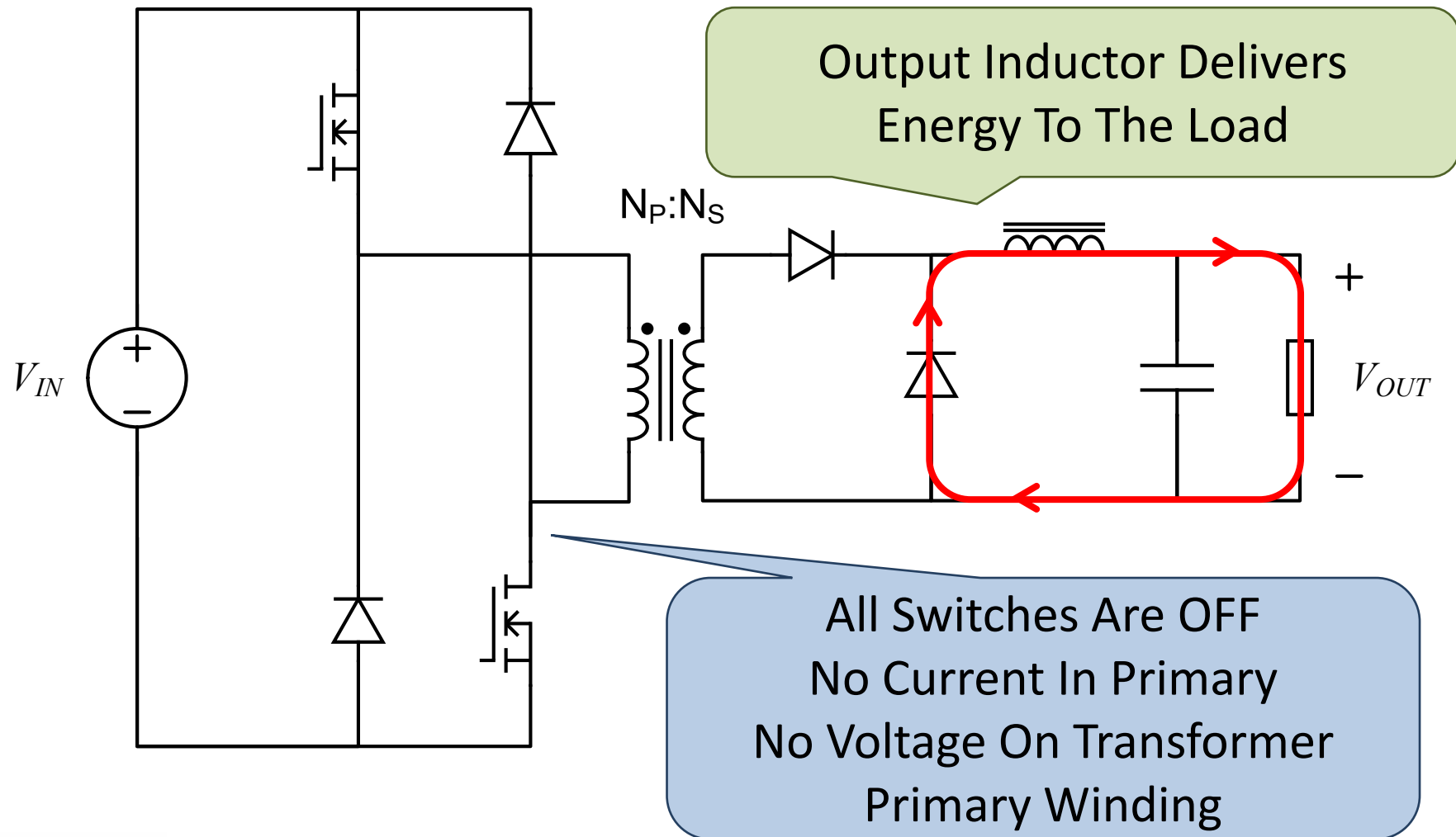Two Transistor Forward Converter Idle-Time



Two Transistor Forward Converter Conversion Ratio

$$V_L(T_{ON}) \cdot T_{ON} + V_L(T_{RESET}) \cdot T_{RESET} + V_L(T_{IDLE}) \cdot T_{IDLE} = 0$$

Inductor Volt-Second Balance

$$\left(\frac{N_S}{N_P} \cdot V_{IN} - V_{OUT}\right) \cdot T_{ON} + (-V_{OUT}) \cdot T_{RESET} + (-V_{OUT}) \cdot T_{IDLE} = 0$$

$$\left(\frac{N_S}{N_P} \cdot V_{IN} - V_{OUT}\right) \cdot T_{ON} + (-V_{OUT}) \cdot (T_{RESET} + T_{IDLE}) = 0$$

$$\left(\frac{N_S}{N_P} \cdot V_{IN} - V_{OUT}\right) \cdot T_{ON} + (-V_{OUT}) \cdot T_{OFF} = 0$$

$$\left(\frac{N_S}{N_P} \cdot V_{IN} - V_{OUT}\right) \cdot D \cdot T_{SW} + (-V_{OUT}) \cdot (1-D) \cdot T_{SW} = 0$$

$$\left(\frac{N_S}{N_P} \cdot V_{IN} - V_{OUT}\right) \cdot D + (-V_{OUT}) \cdot (1-D) = 0$$

$$D \cdot \frac{N_S}{N_P} \cdot V_{IN} - D \cdot V_{OUT} - V_{OUT} + D \cdot V_{OUT} = 0$$

$$D \cdot \frac{N_S}{N_P} \cdot V_{IN} - V_{OUT} = 0$$

$$V_{OUT} = D \cdot \frac{N_S}{N_P} \cdot V_{IN}$$

During On Time Voltage At Input To Inductor Is the Input Voltage Multiplied By the Transformer Turns Ratio

Same At The Buck Converter Except For The Transformer Turns Ratio

Two Transistor Forward Converter


Advantages

- Isolated
- Good For
50 W To 500 W
- Multiple Isolated Outputs
Possible
- Easy To Control
- Low Voltage Stress On
Switching Transistors


Disadvantages

- Transformer Needed
- Maximum Duty Cycle Limited
To 50%
- Gate Drive Transformer Or IC
Needed
- High Voltage Stress On
Output Diodes

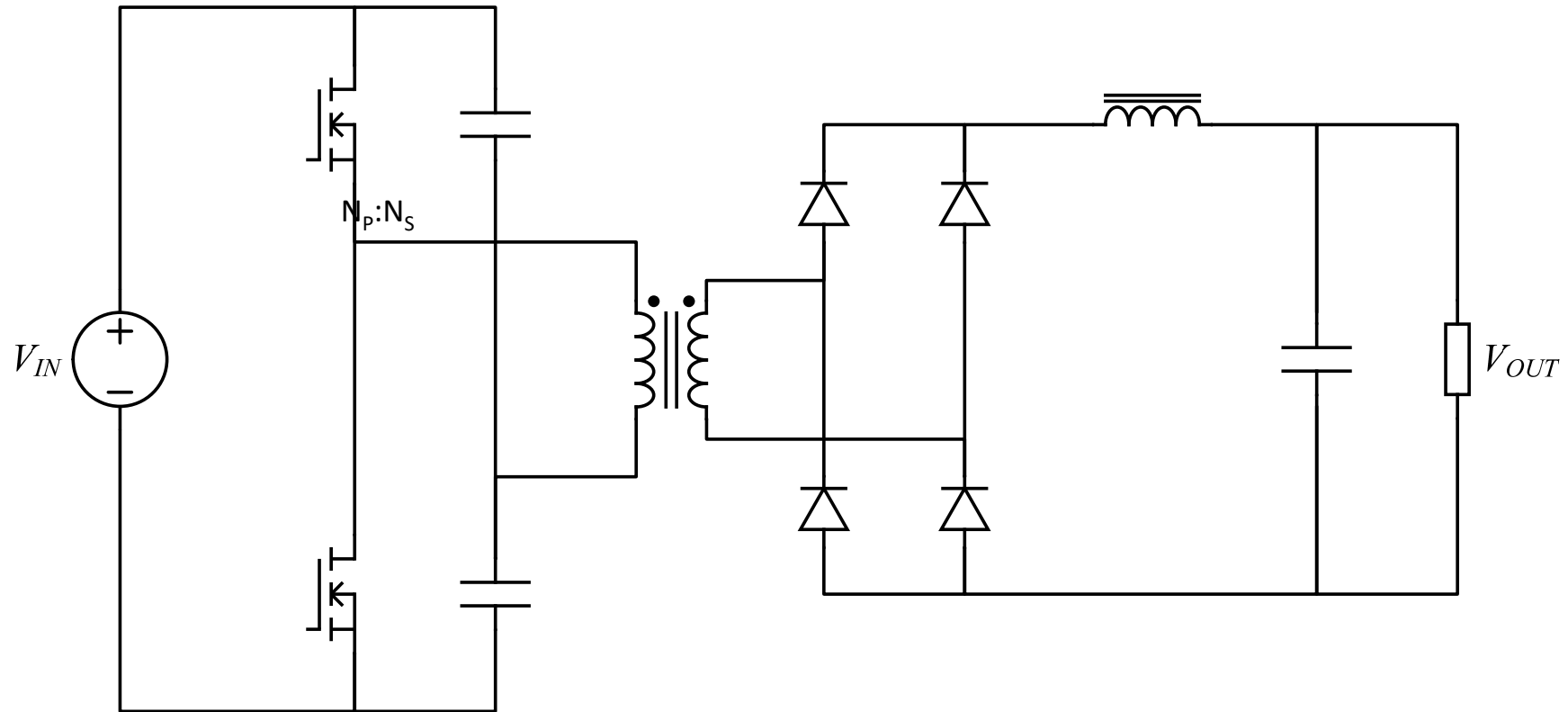
Half-Bridge Converter w/Full Wave Rectifier



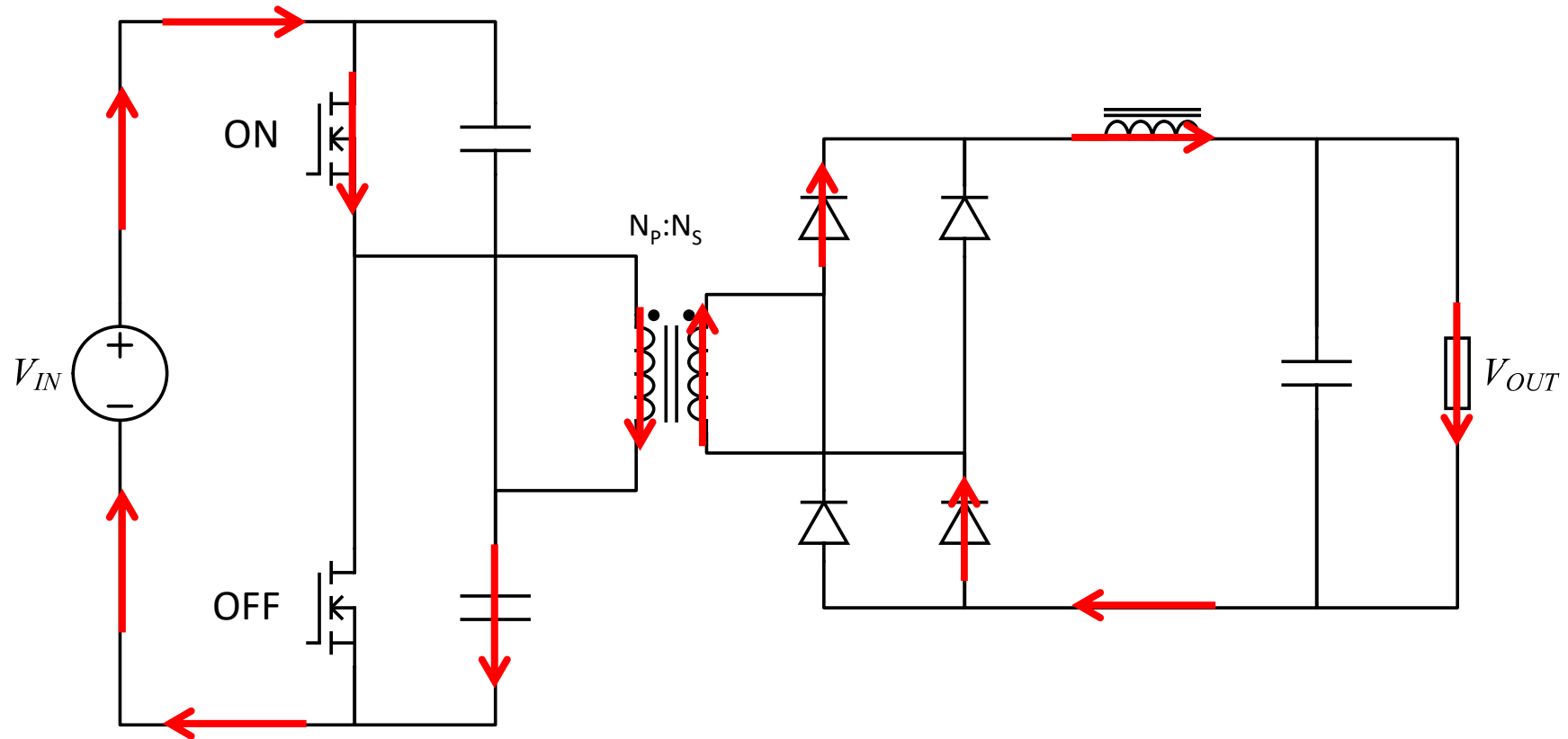
Half-Bridge Converter w/FW Rectifier On Time 1



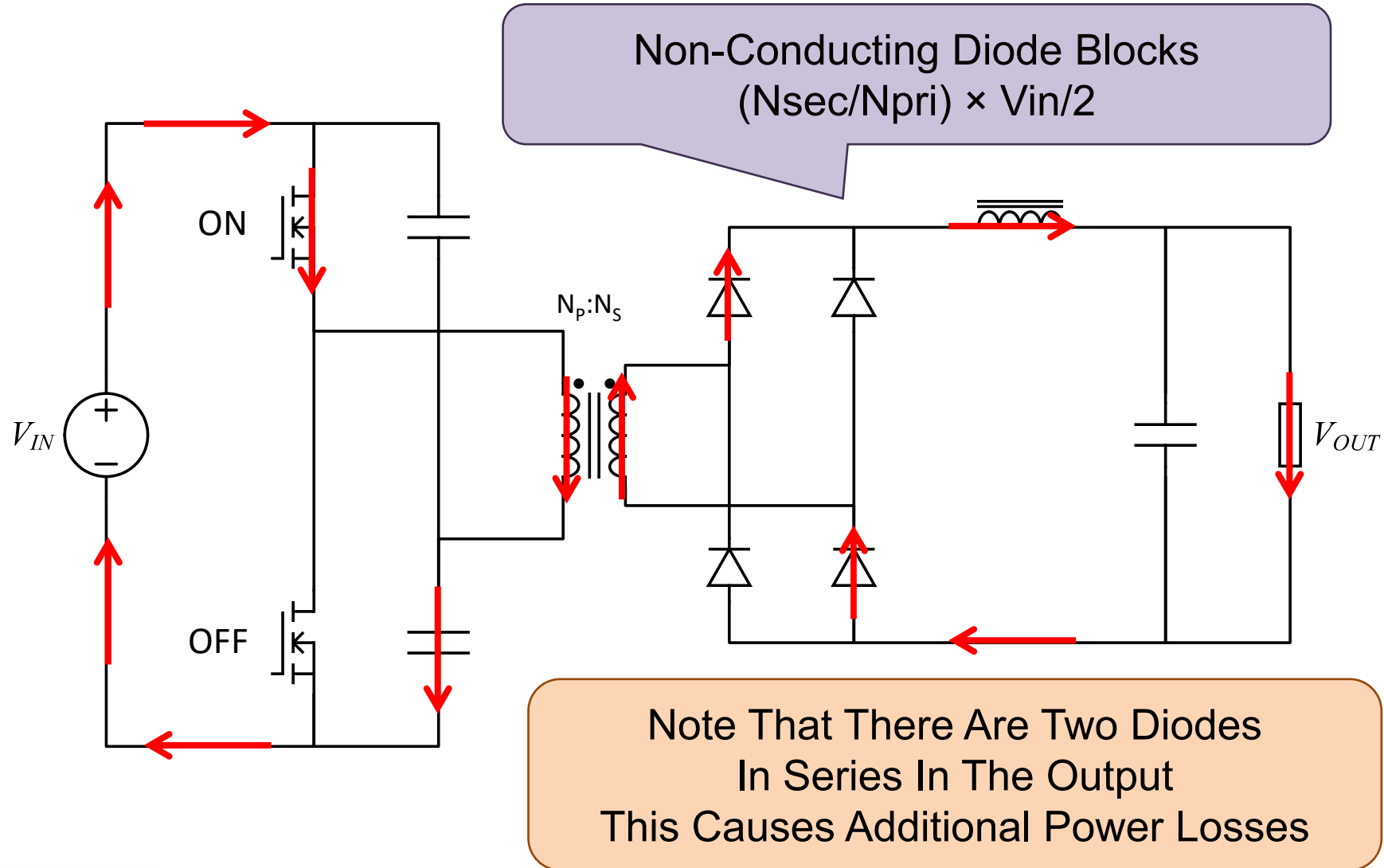
Half-Bridge Converter w/FW Rectifier On Time 1



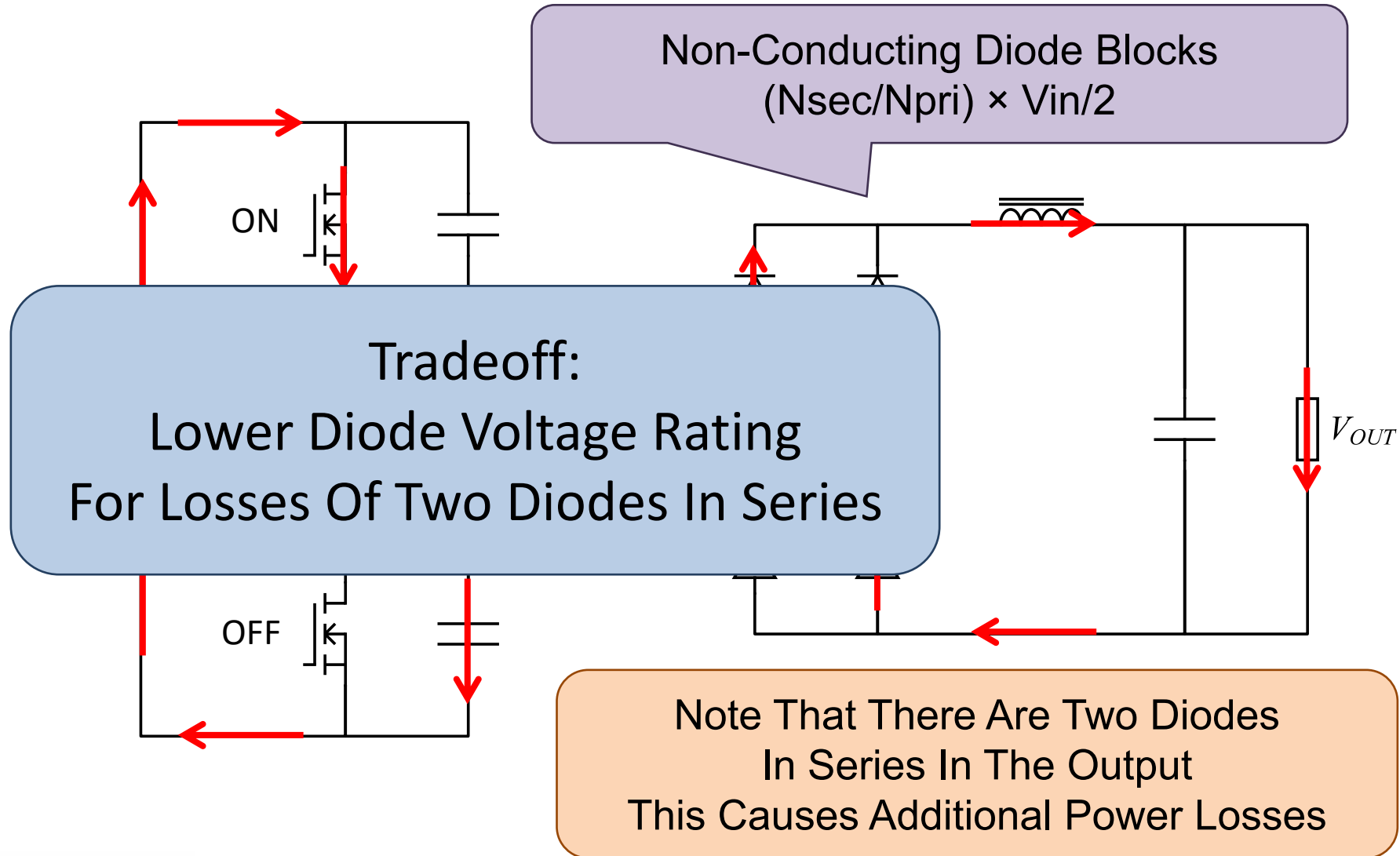Half-Bridge Converter w/FW Rectifier On Time 1




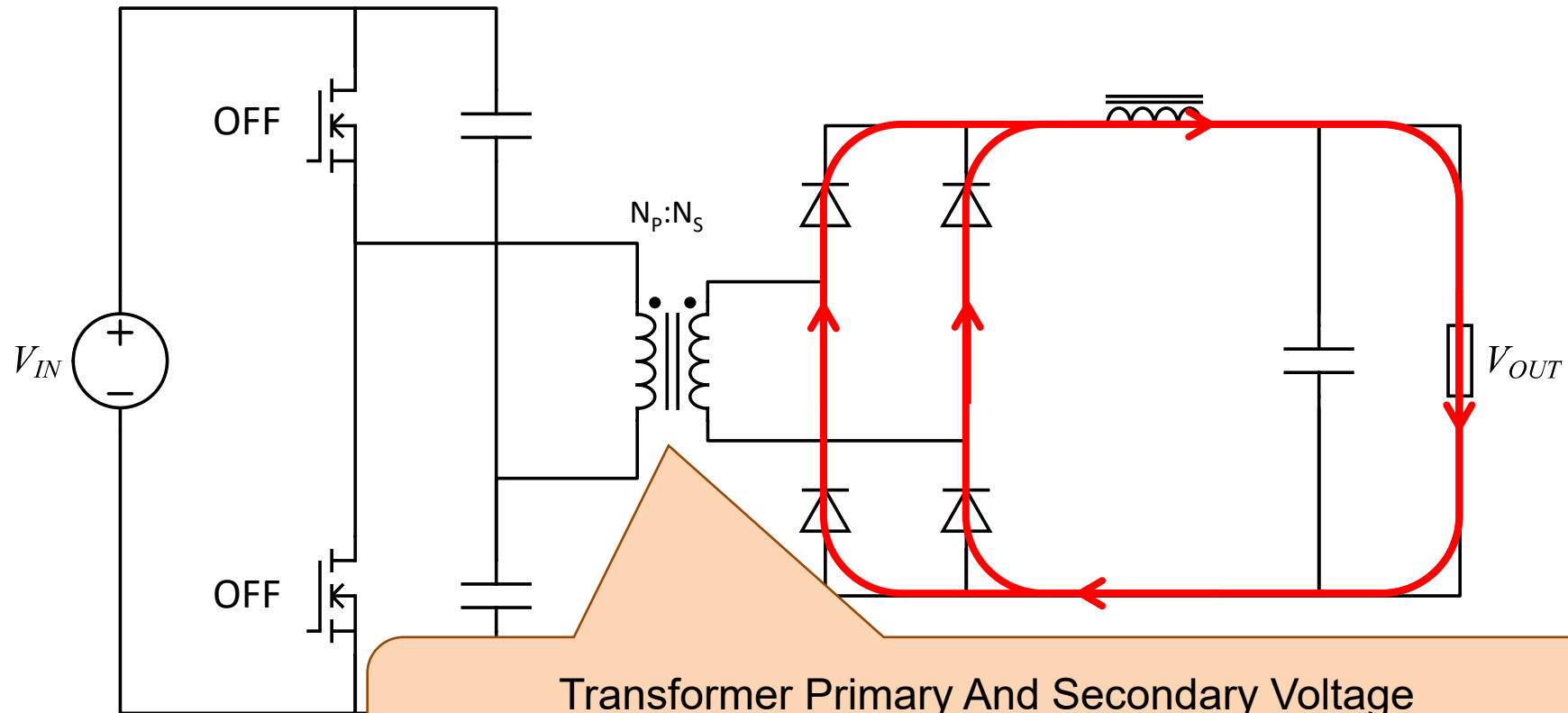Half-Bridge Converter w/FW Rectifier Off Time 1




Transformer Primary And Secondary Voltage
Are 0 V During Off Time Because The
Secondary Winding Is Shorted By The Conducting Diodes

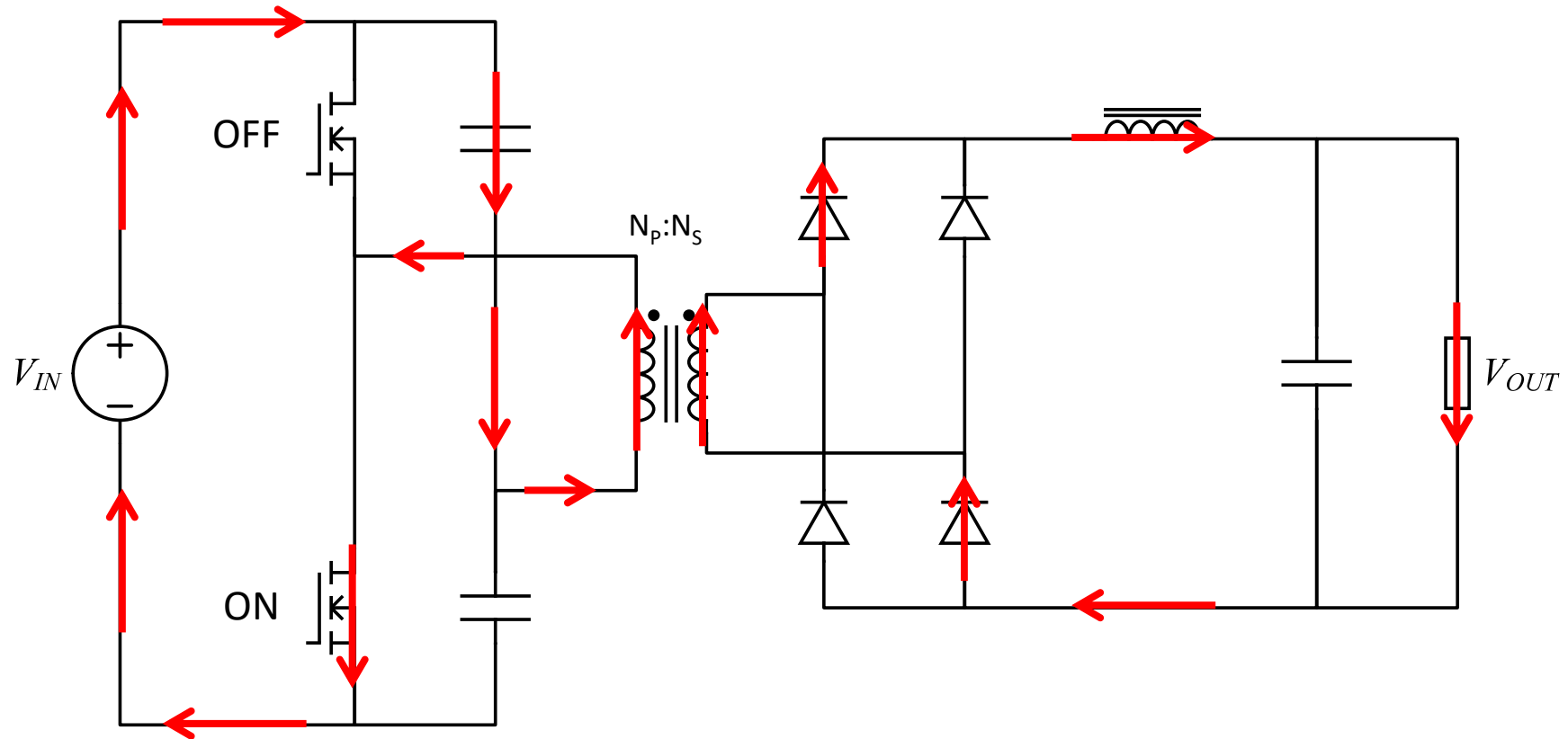
Half-Bridge Converter w/FW Rectifier On Time 2



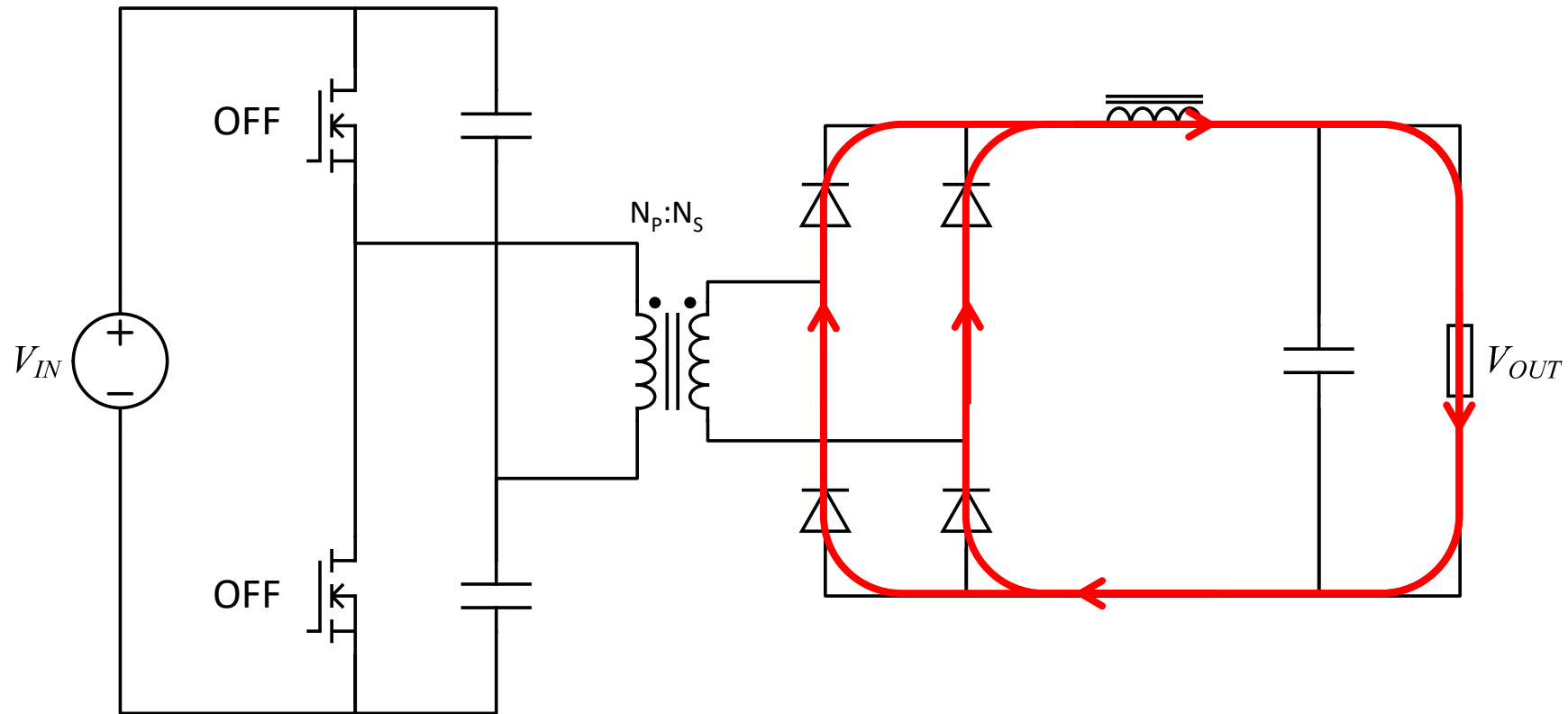
Half-Bridge Converter w/FW Rectifier Off Time 2



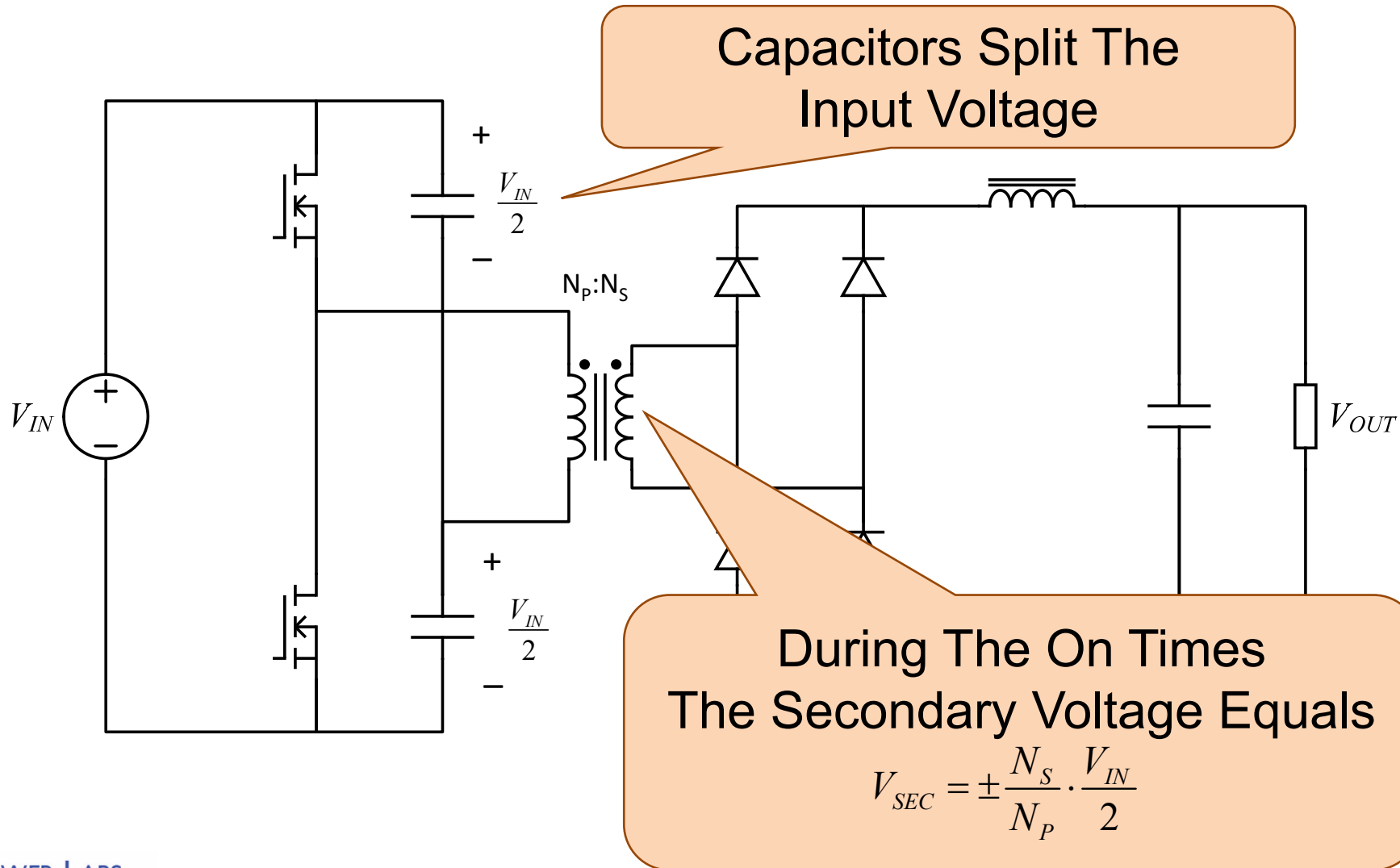
Half-Bridge Converter w/FW Rectifier Conversion Ratio



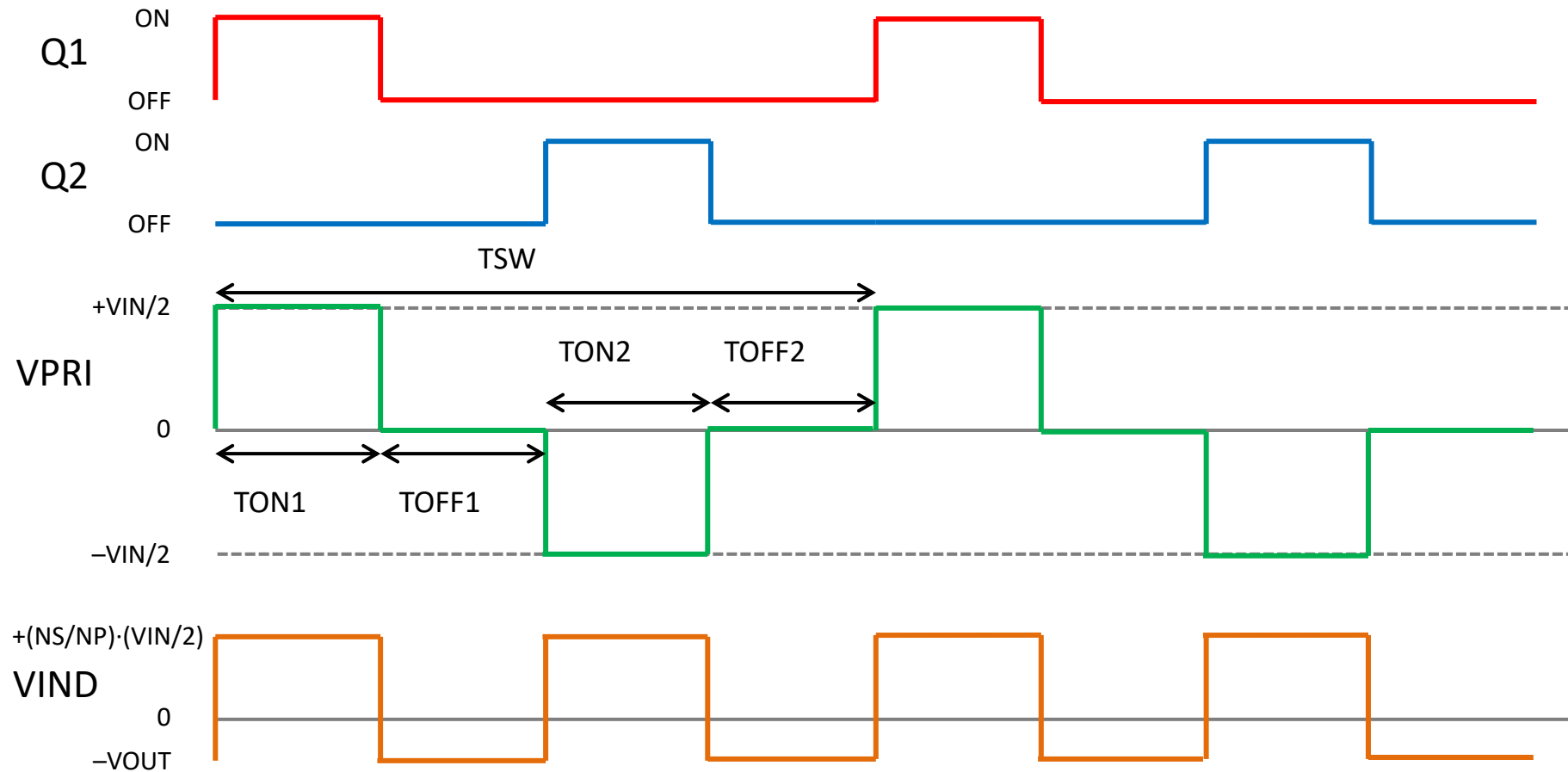Half-Bridge Converter w/FW Rectifier Conversion Ratio



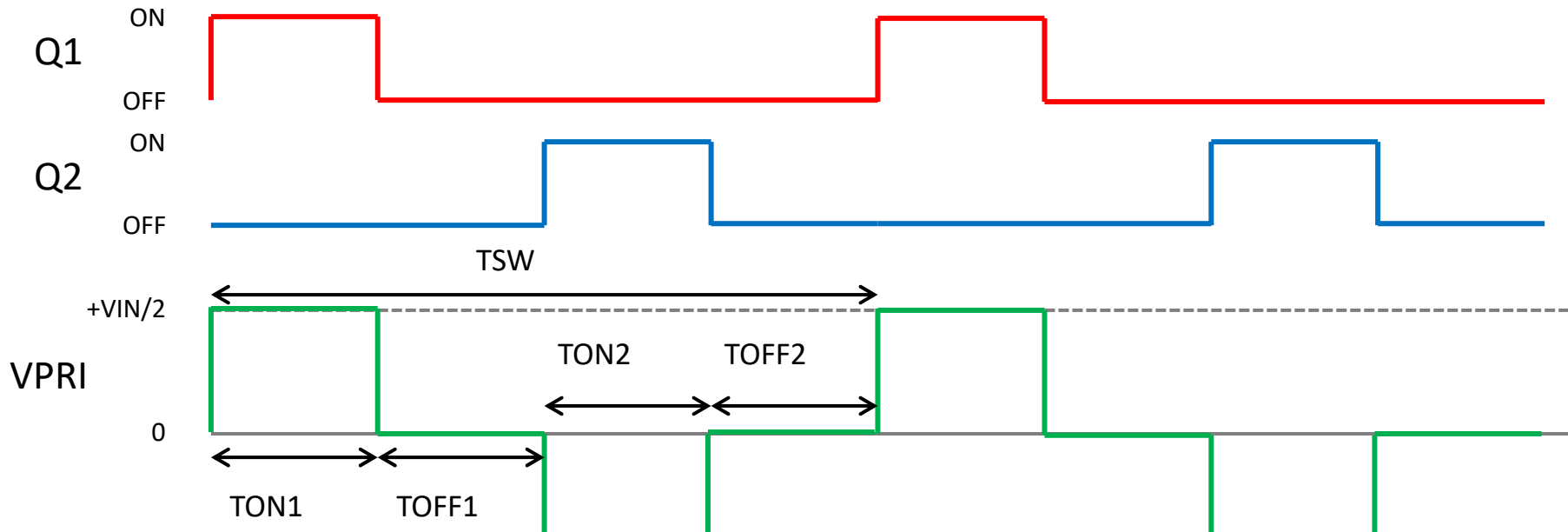Half-Bridge Converter w/FW Rectifier Conversion Ratio



$$T_{SW} = T_{ON1} + T_{OFF2} + T_{ON2} + T_{OFF2}$$

$$T_{ON1} = T_{ON2} = T_{ON}$$

$$T_{OFF1} = T_{OFF2} = T_{OFF}$$

$$D = \frac{T_{ON}}{T_{ON} + T_{OFF}}$$

$$= \frac{T_{ON1} + T_{ON2}}{T_{SW}} = \frac{2 \cdot T_{ON}}{T_{SW}}$$

Half-Bridge Converter w/FW Rectifier Conversion Ratio

$$V_L(T_{ON1}) \cdot T_{ON1} + V_L(T_{OFF1}) \cdot T_{OFF1} + V_L(T_{ON2}) \cdot T_{ON2} + V_L(T_{OFF2}) \cdot T_{OFF2} = 0$$

$$V_L(T_{ON}) \cdot T_{ON} + V_L(T_{OFF}) \cdot T_{OFF} + V_L(T_{ON}) \cdot T_{ON} + V_L(T_{OFF}) \cdot T_{OFF} = 0$$

$$V_L(T_{ON}) \cdot 2 \cdot T_{ON} + V_L(T_{OFF}) \cdot 2 \cdot T_{OFF} = 0$$

$$V_L(T_{ON}) \cdot \frac{2 \cdot T_{ON}}{T_{SW}} + V_L(T_{OFF}) \cdot \frac{T_{SW} - 2 \cdot T_{ON}}{T_{SW}} = 0$$

$$V_L(T_{ON}) \cdot D + V_L(T_{OFF}) \cdot (1 - D) = 0$$

$$\left(\frac{N_S}{N_P} \cdot \frac{V_{IN}}{2} - V_{OUT} \right) \cdot D + (-V_{OUT}) \cdot (1 - D) = 0$$

$$\frac{N_S}{N_P} \cdot \frac{V_{IN}}{2} \cdot D - V_{OUT} \cdot D - V_{OUT} + V_{OUT} \cdot D = 0$$


$$\frac{N_S}{N_P} \cdot \frac{V_{IN}}{2} \cdot D = V_{OUT}$$

$$V_{OUT} = D \cdot \frac{N_S}{N_P} \cdot \frac{V_{IN}}{2}$$


Inductor Volt-
Second
Balance

Same As Buck Converter Except:
- Transformer Turns Ratio
- Capacitor Split Input Voltage

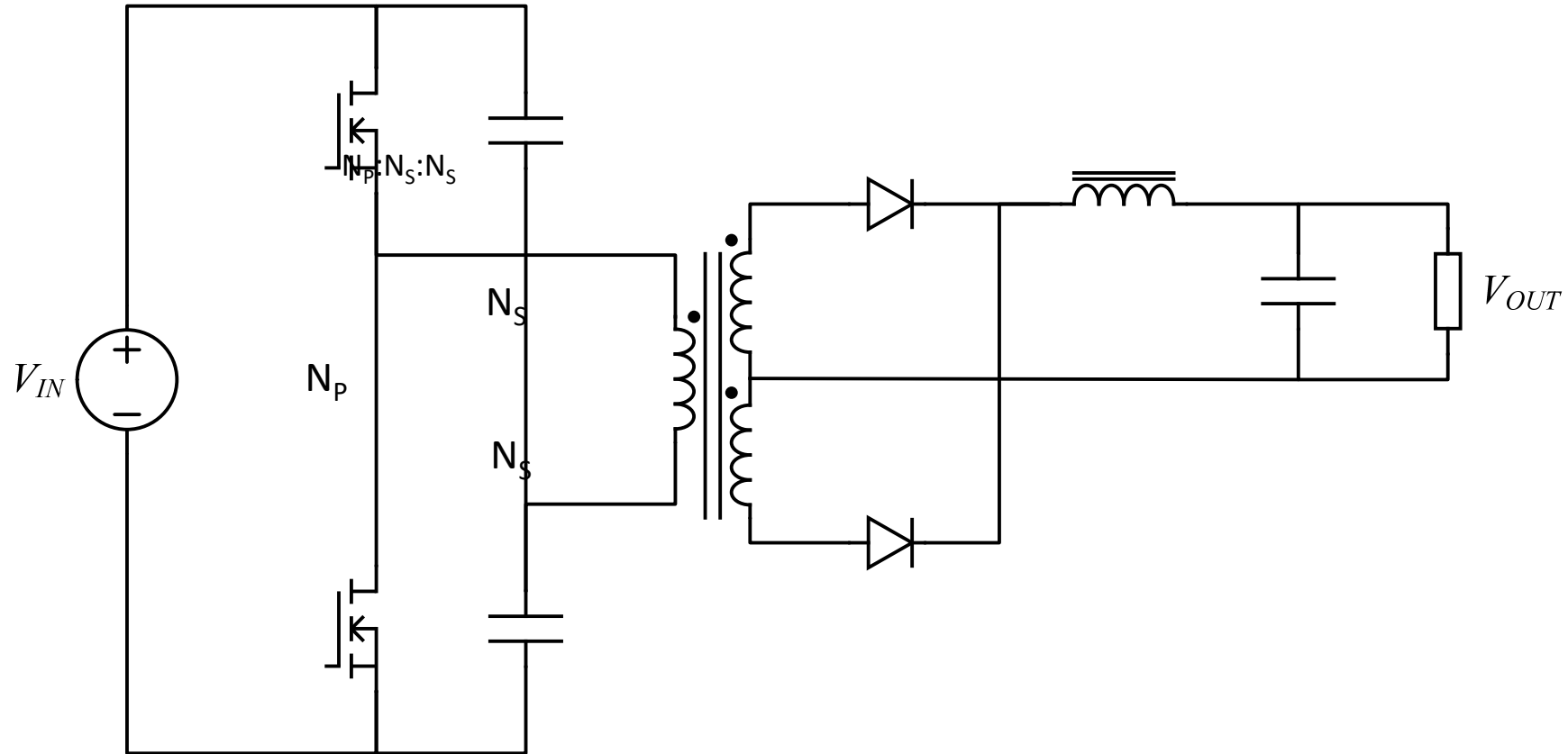
Half-Bridge Converter w/Center Tapped Rectifier



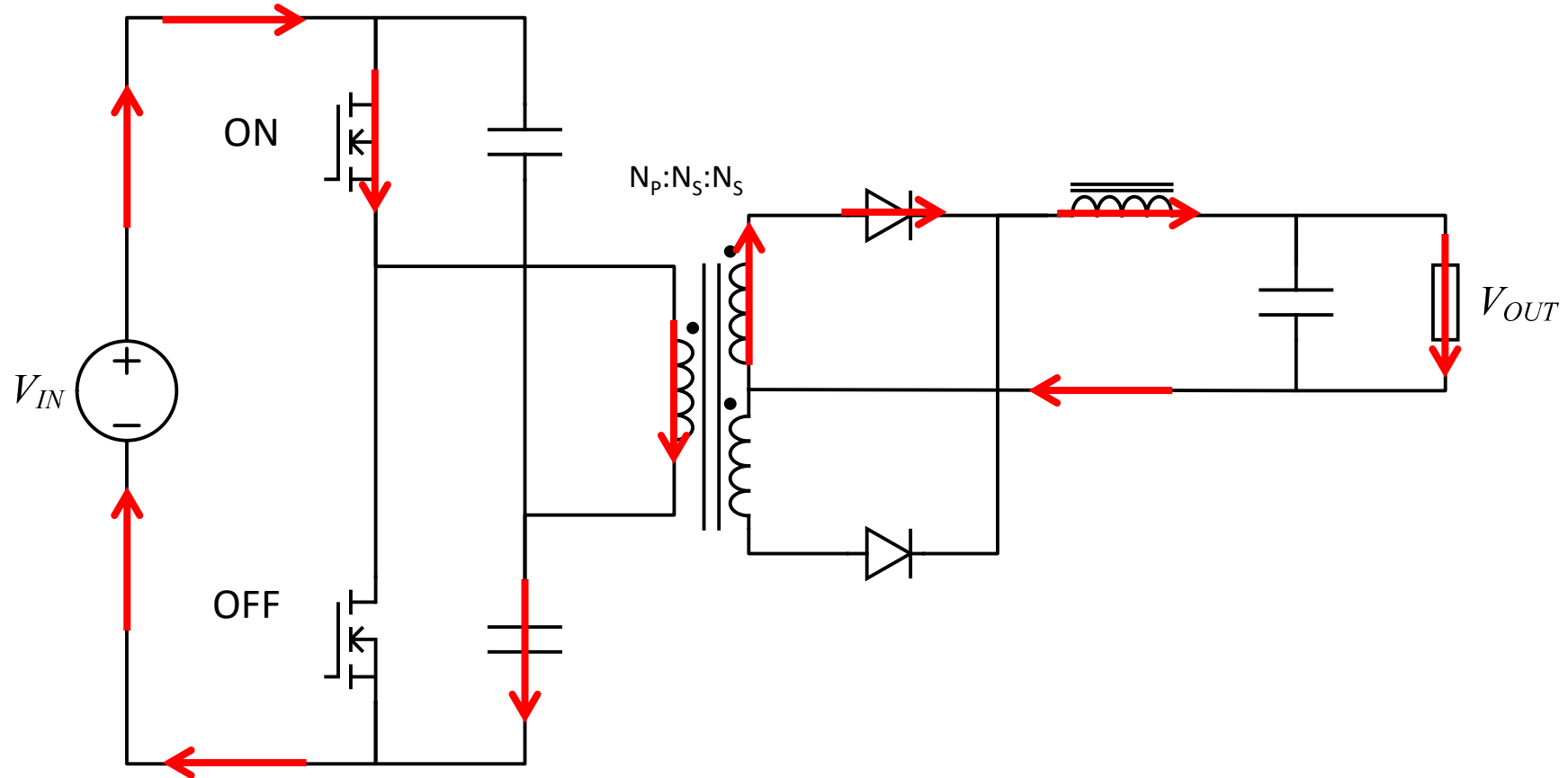
Half-Bridge Converter w/CT Rectifier On Time 1



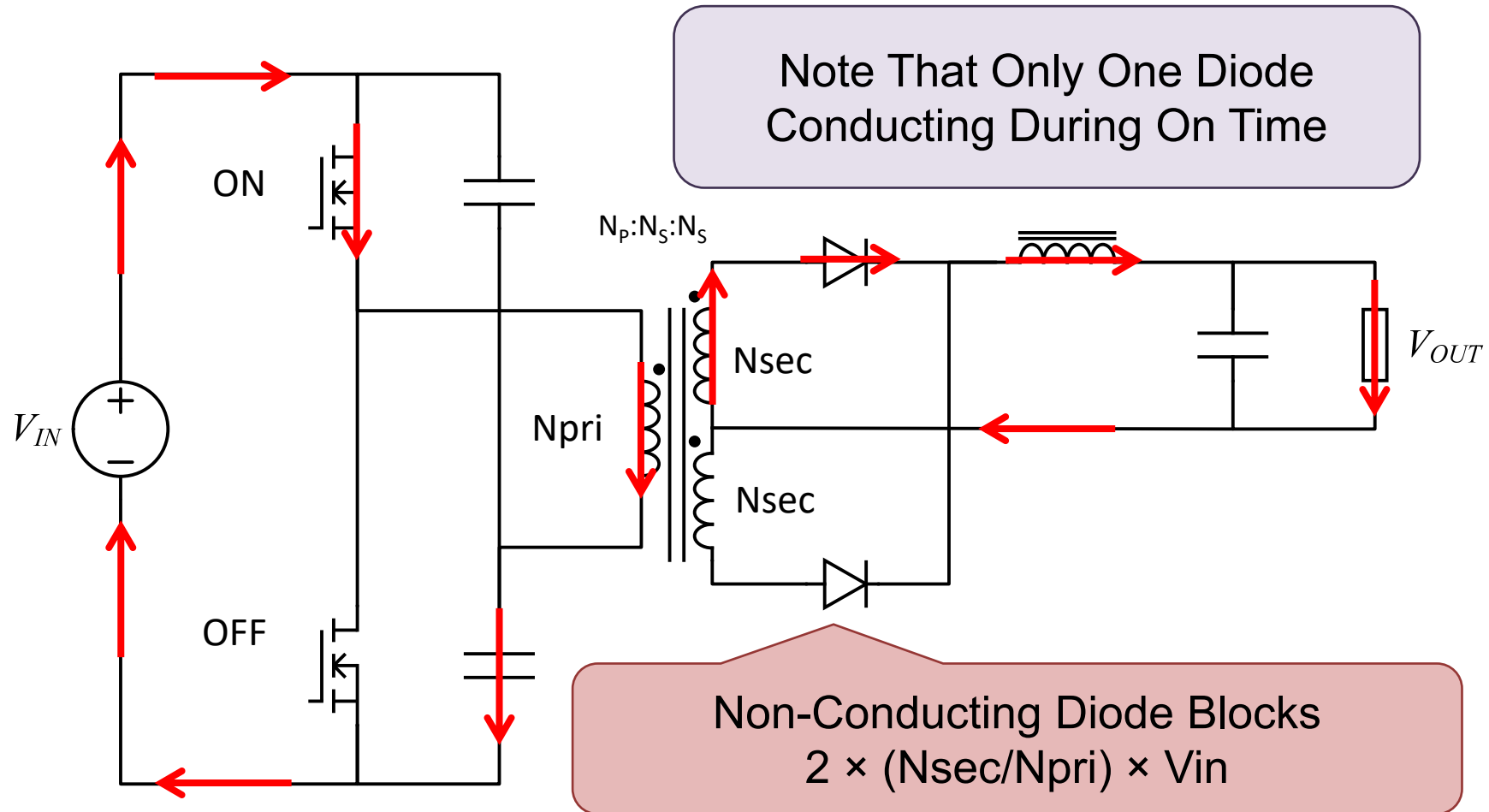Half-Bridge Converter w/CT Rectifier On Time 1




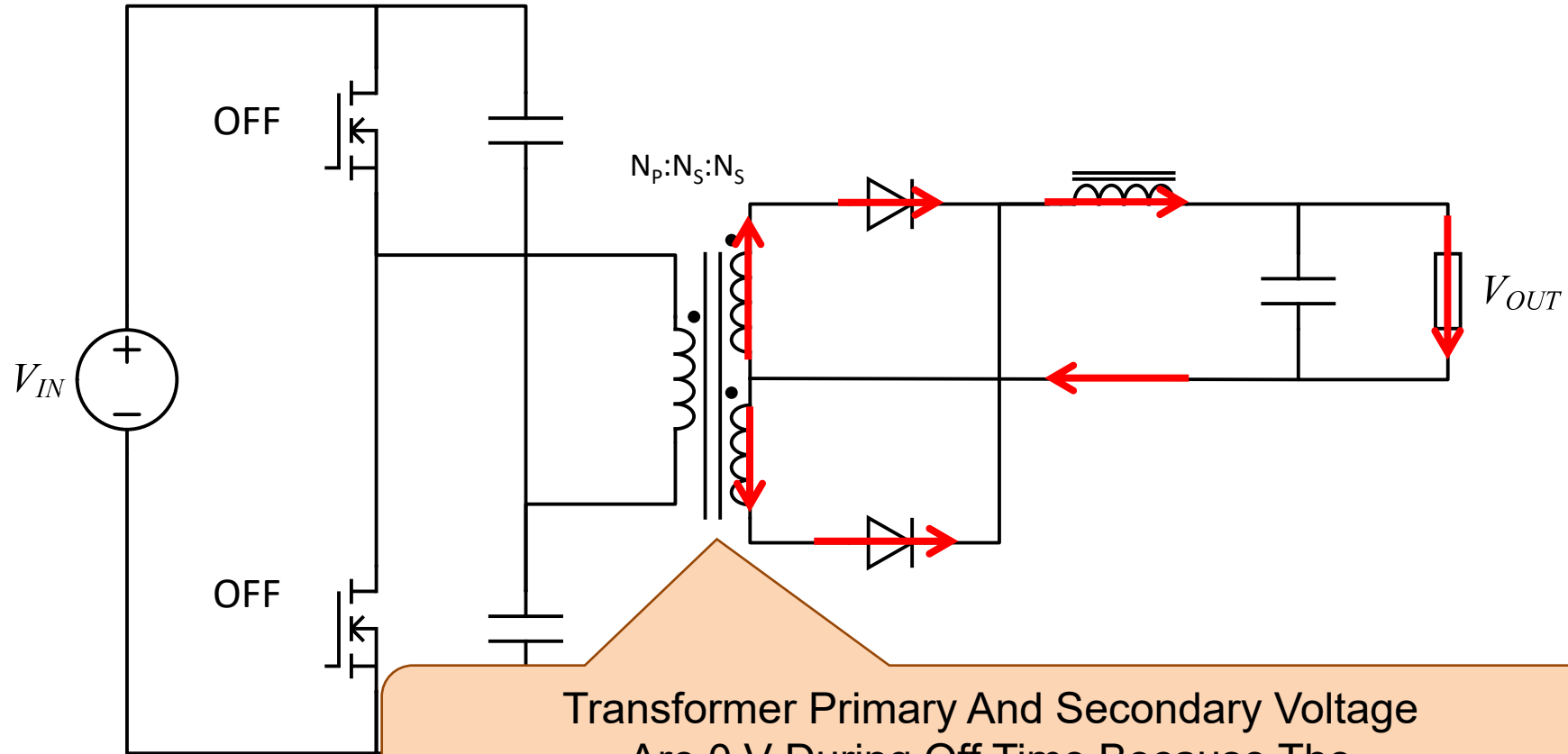Half-Bridge Converter w/CT Rectifier Off Time 1




Transformer Primary And Secondary Voltage
Are 0 V During Off Time Because The
Secondary Winding Is Shorted By The Conducting Diodes

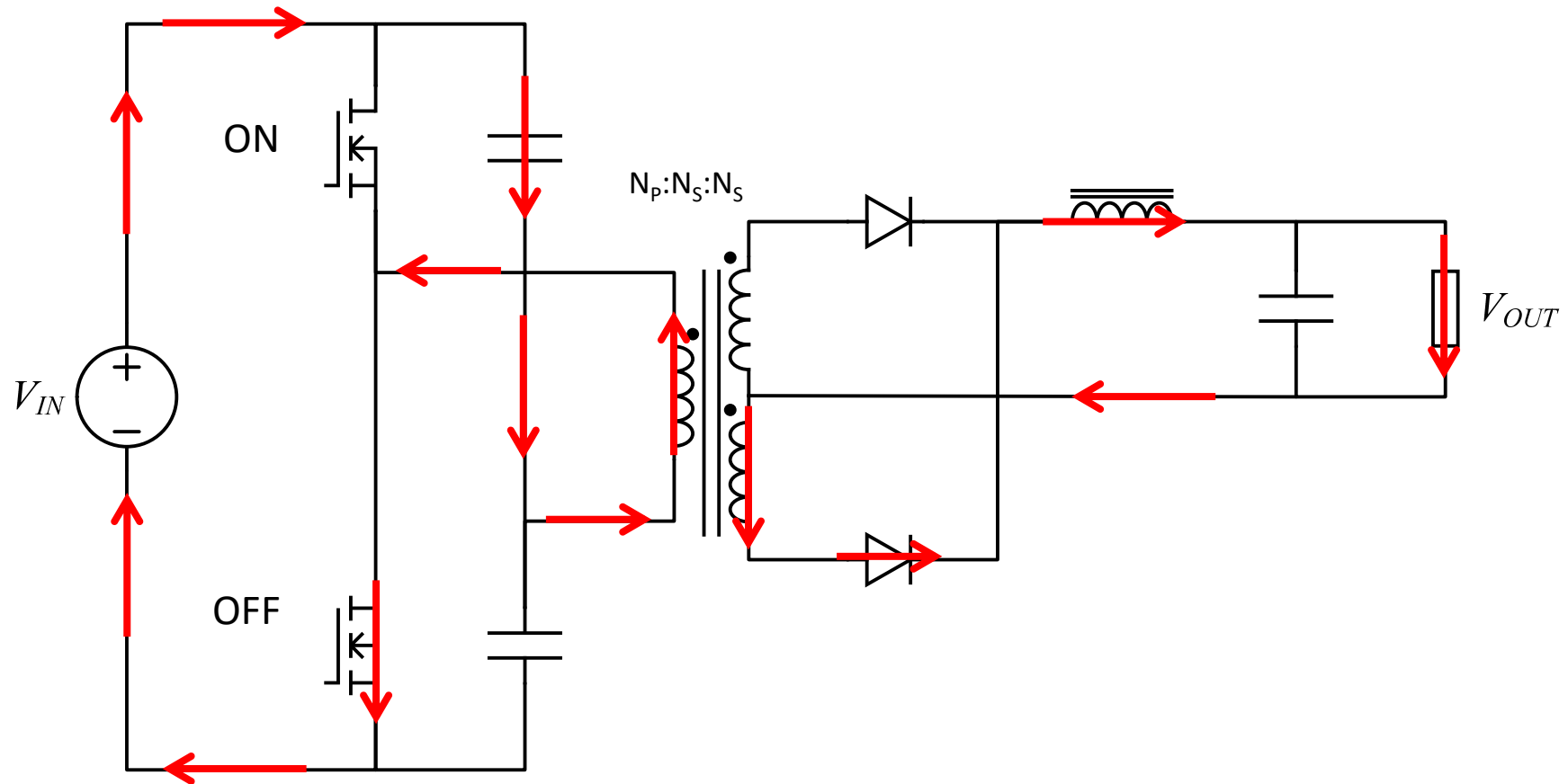
Half-Bridge Converter w/CT Rectifier On Time 2



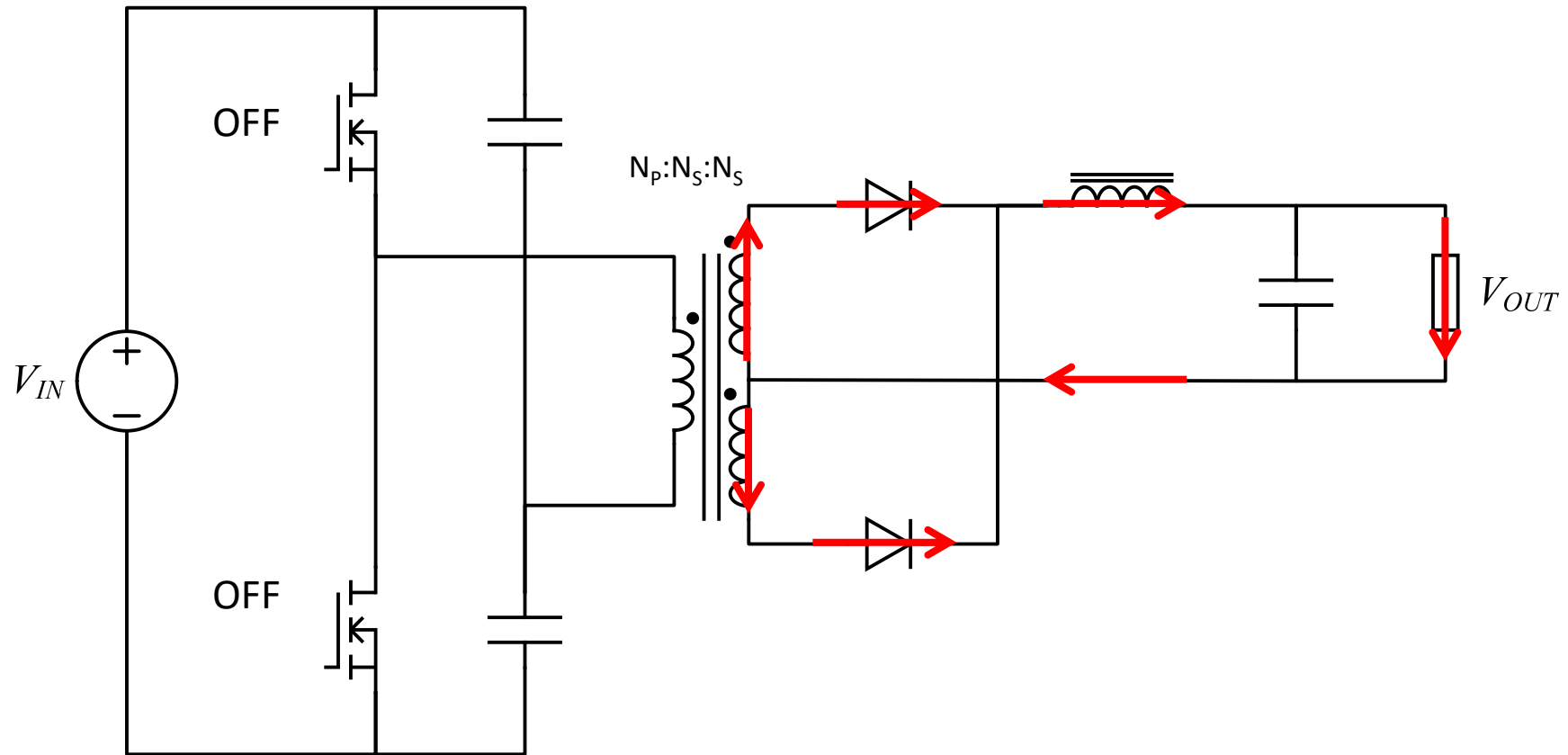Half-Bridge Converter w/CT Rectifier Off Time 2



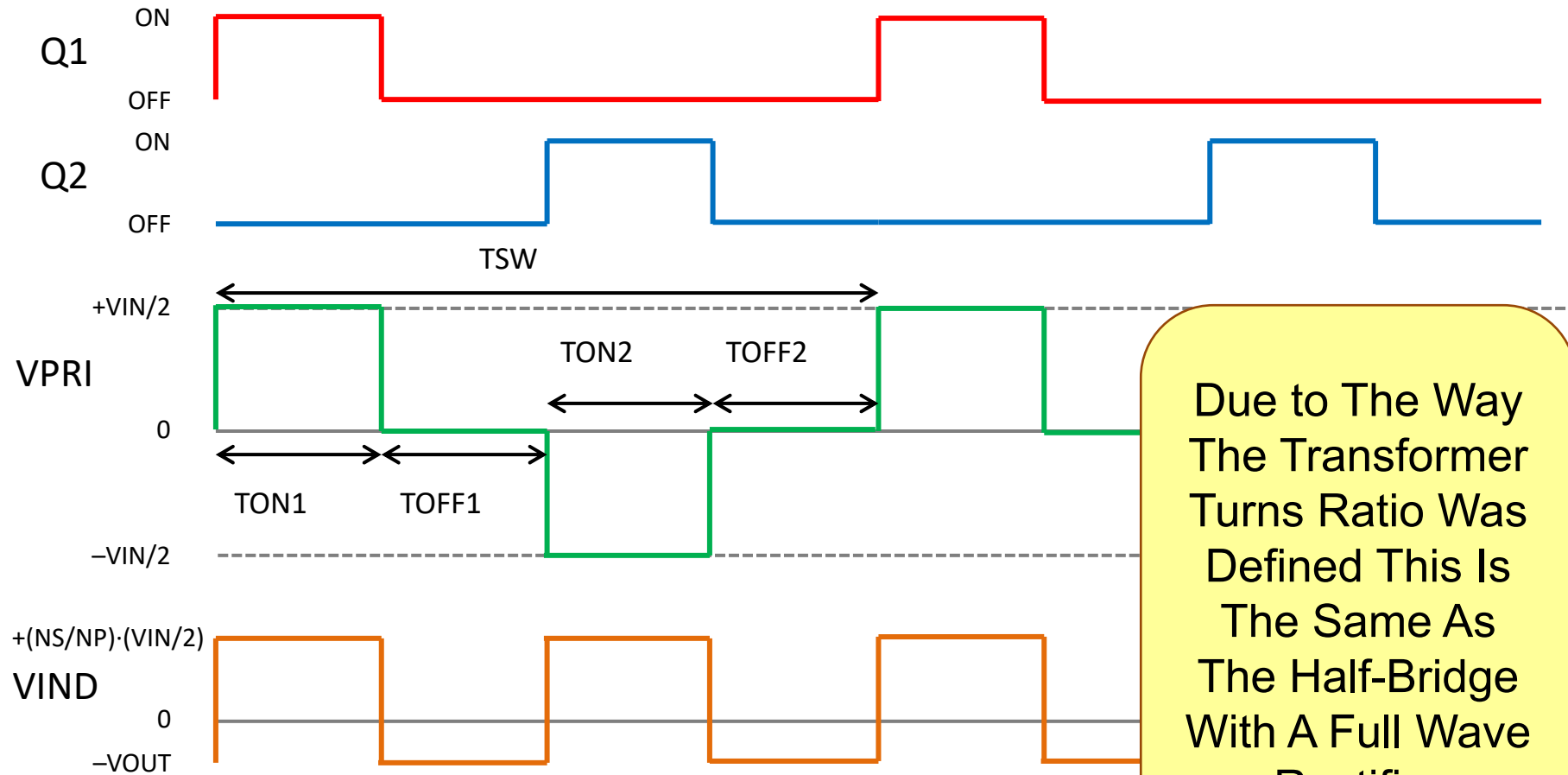
Half-Bridge Converter w/CT Rectifier Conversion Ratio



Due to The Way
The Transformer
Turns Ratio Was
Defined This Is
The Same As
The Half-Bridge
With A Full Wave
Rectifier

Half-Bridge Converter w/CT Rectifier

Conversion Ratio

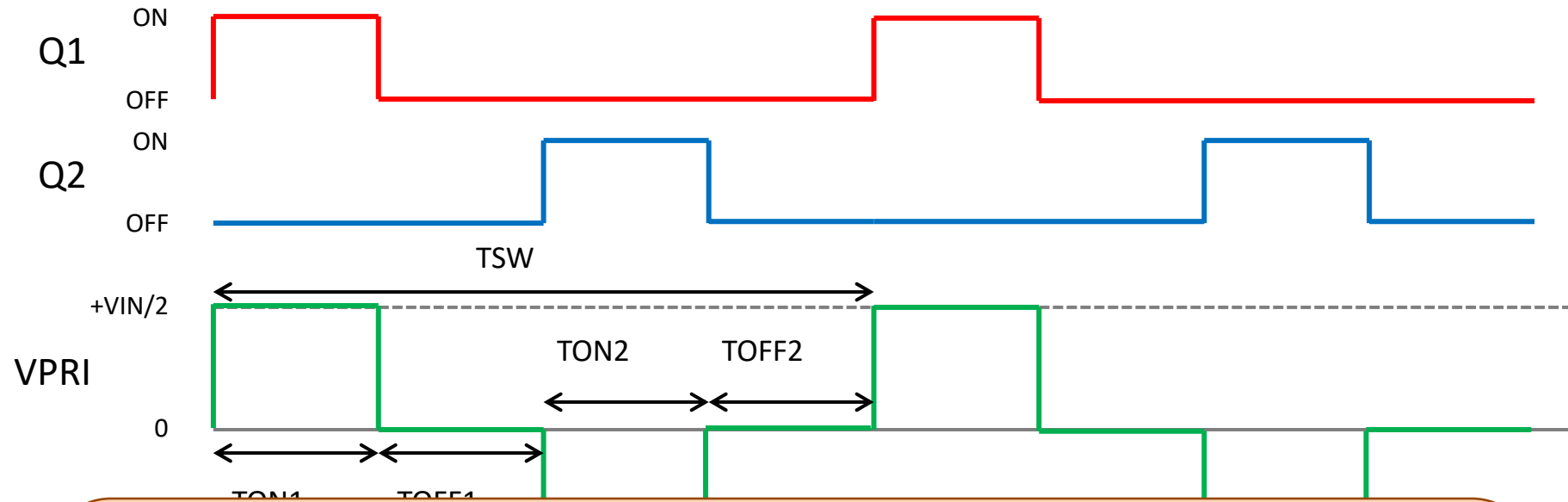

$$T_{SW} = T_{ON1} + T_{OFF2} + T_{ON2} + T_{OFF2}$$

$$T_{ON1} = T_{ON2} = T_{ON}$$

$$T_{OFF1} = T_{OFF2} = T_{OFF}$$

$$D = \frac{T_{ON}}{T_{ON} + T_{OFF}}$$

$$= \frac{T_{ON1} + T_{ON2}}{T_{SW}} = \frac{2 \cdot T_{ON}}{T_{SW}}$$

Half-Bridge Converter w/CT Rectifier Conversion Ratio

$$V_L(T_{ON1}) \cdot T_{ON1} + V_L(T_{OFF1}) \cdot T_{OFF1} + V_L(T_{ON2}) \cdot T_{ON2} + V_L(T_{OFF2}) \cdot T_{OFF2} = 0$$

$$V_L(T_{ON}) \cdot T_{ON} + V_L(T_{OFF}) \cdot T_{OFF} + V_L(T_{ON}) \cdot T_{ON} + V_L(T_{OFF}) \cdot T_{OFF} = 0$$

$$V_L(T_{ON}) \cdot 2 \cdot T_{ON} + V_L(T_{OFF}) \cdot 2 \cdot T_{OFF} = 0$$

$$V_L(T_{ON}) \cdot \frac{2 \cdot T_{ON}}{T_{SW}} + V_L(T_{OFF}) \cdot \frac{T_{SW} - 2 \cdot T_{ON}}{T_{SW}} = 0$$

$$V_L(T_{ON}) \cdot D + V_L(T_{OFF}) \cdot (1 - D) = 0$$

$$\left(\frac{N_S}{N_P} \cdot \frac{V_{IN}}{2} - V_{OUT} \right) \cdot D + (-V_{OUT}) \cdot (1 - D) = 0$$

$$\frac{N_S}{N_P} \cdot \frac{V_{IN}}{2} \cdot D - V_{OUT} \cdot D - V_{OUT} + V_{OUT} \cdot D = 0$$

$$\frac{N_S}{N_P} \cdot \frac{V_{IN}}{2} \cdot D = V_{OUT}$$

$$V_{OUT} = D \cdot \frac{N_S}{N_P} \cdot \frac{V_{IN}}{2}$$

Inductor Volt-
Second
Balance

Due to The Way The Transformer
Turns Ratio Was Defined This Is
The Same As The Half-Bridge With
A Full Wave Rectifier

Same As Buck Converter Except:
- Transformer Turns Ratio
- Capacitor Split Input Voltage

Half Bridge Converter


Advantages

- Isolated
- Good For
250 W To 1000 W
- Multiple Isolated Outputs
Possible
- Easy To Control
- Good Use Of Transformer Core
- Low Voltage Stress On
Switching Transistors

Disadvantages


- Transformer Needed
- Must Have Way TO Prevent
Transformer Saturation
- Center Tap Output: High
Voltage Stress On Output
Diodes
- Full Wave Output:
More Diodes And Diode Loss

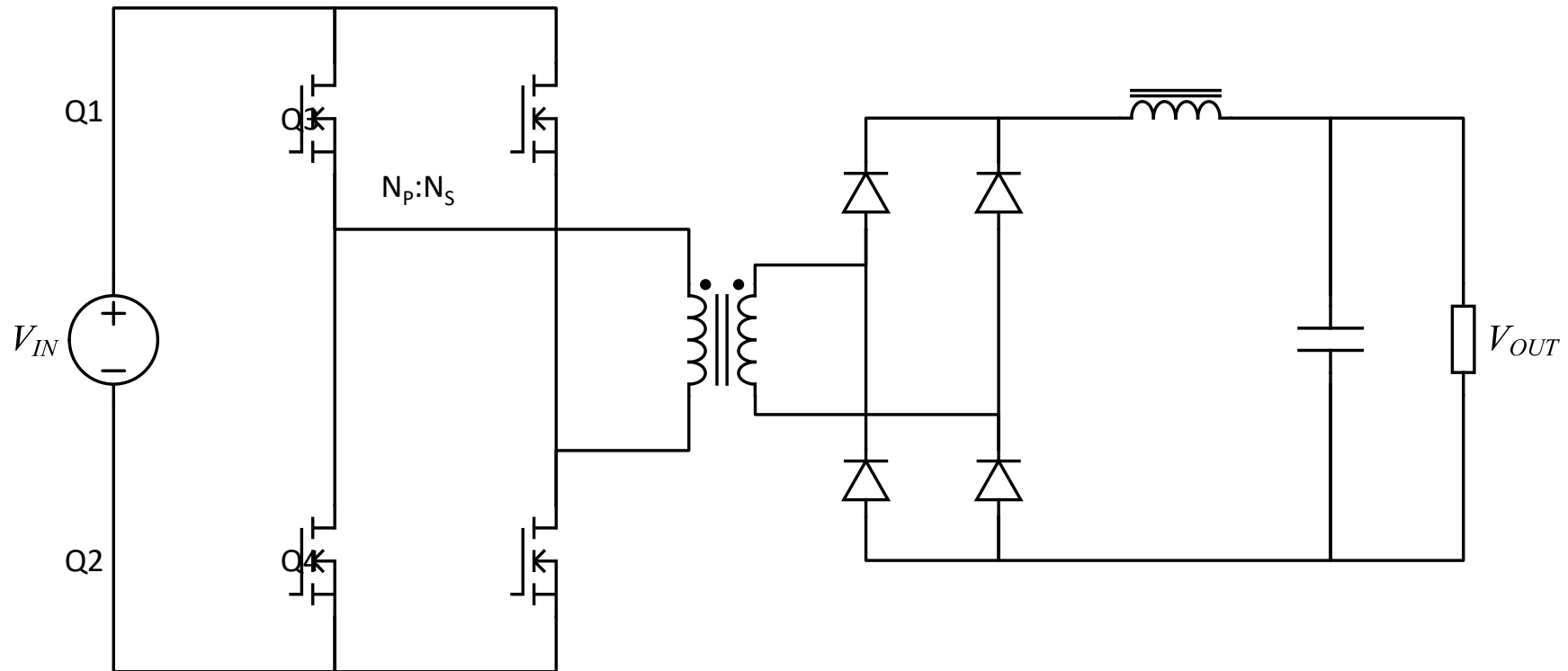Full-Bridge Converter w/Full Wave Rectifier




Full-Bridge Converter w/FW Rectifier

On Time 1

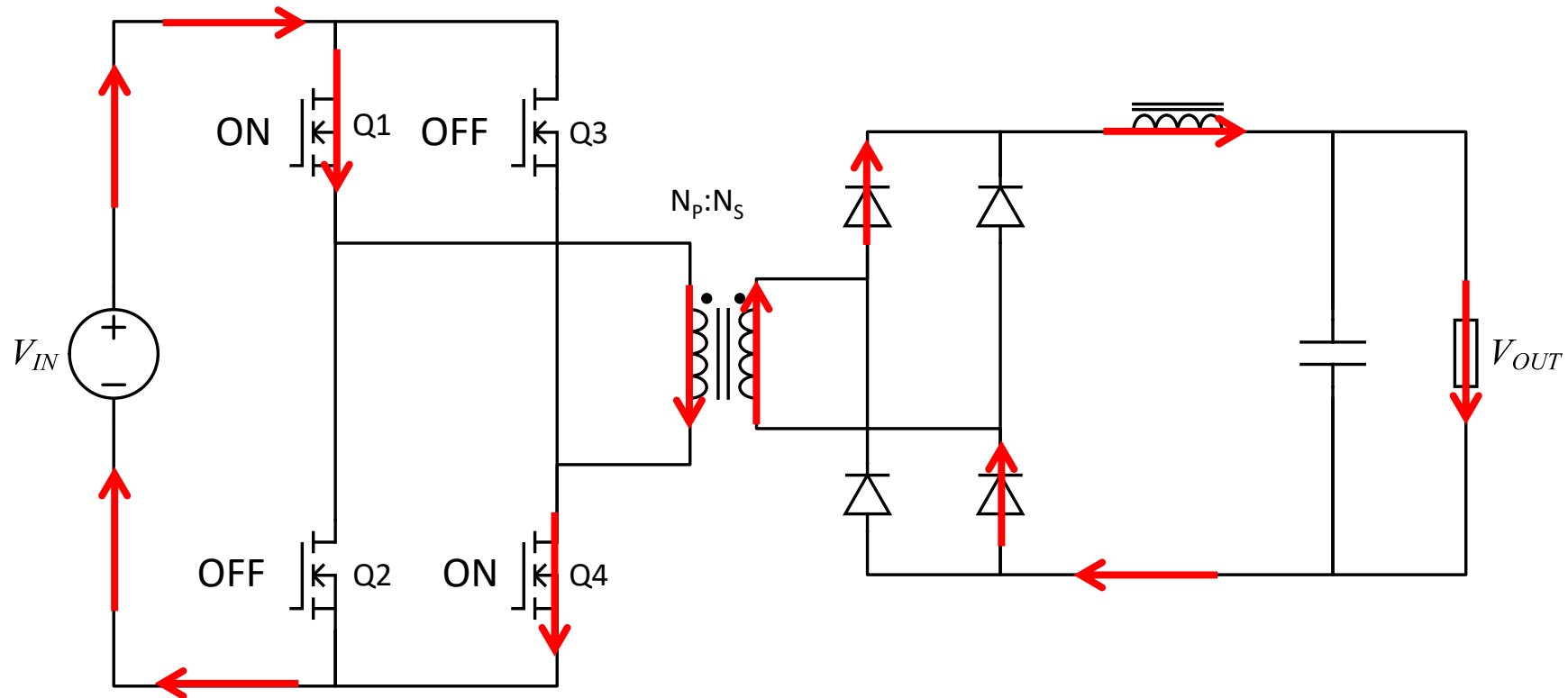


Full-Bridge Converter w/FW Rectifier

On Time 1

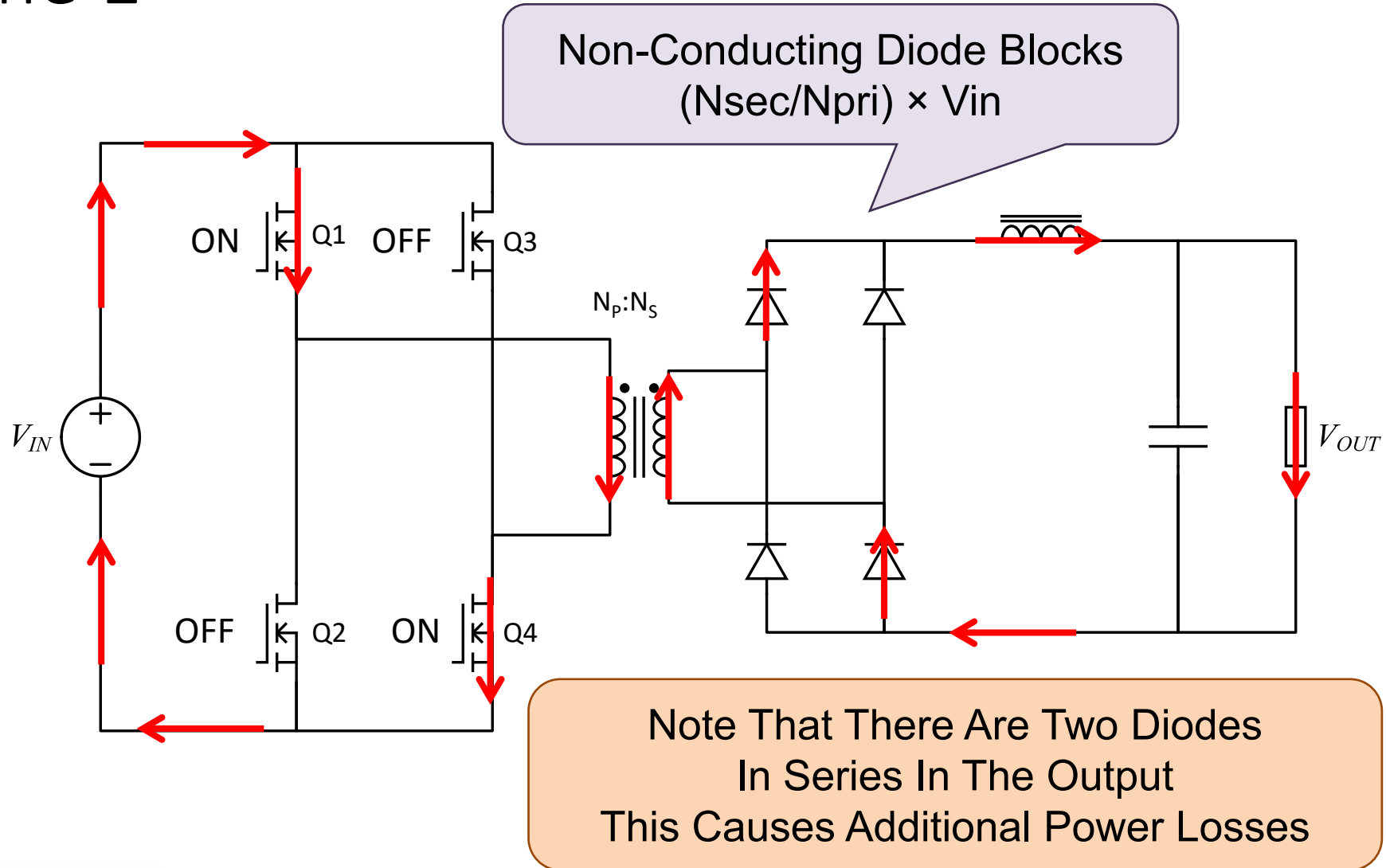

Full-Bridge Converter w/FW Rectifier


Off Time 1

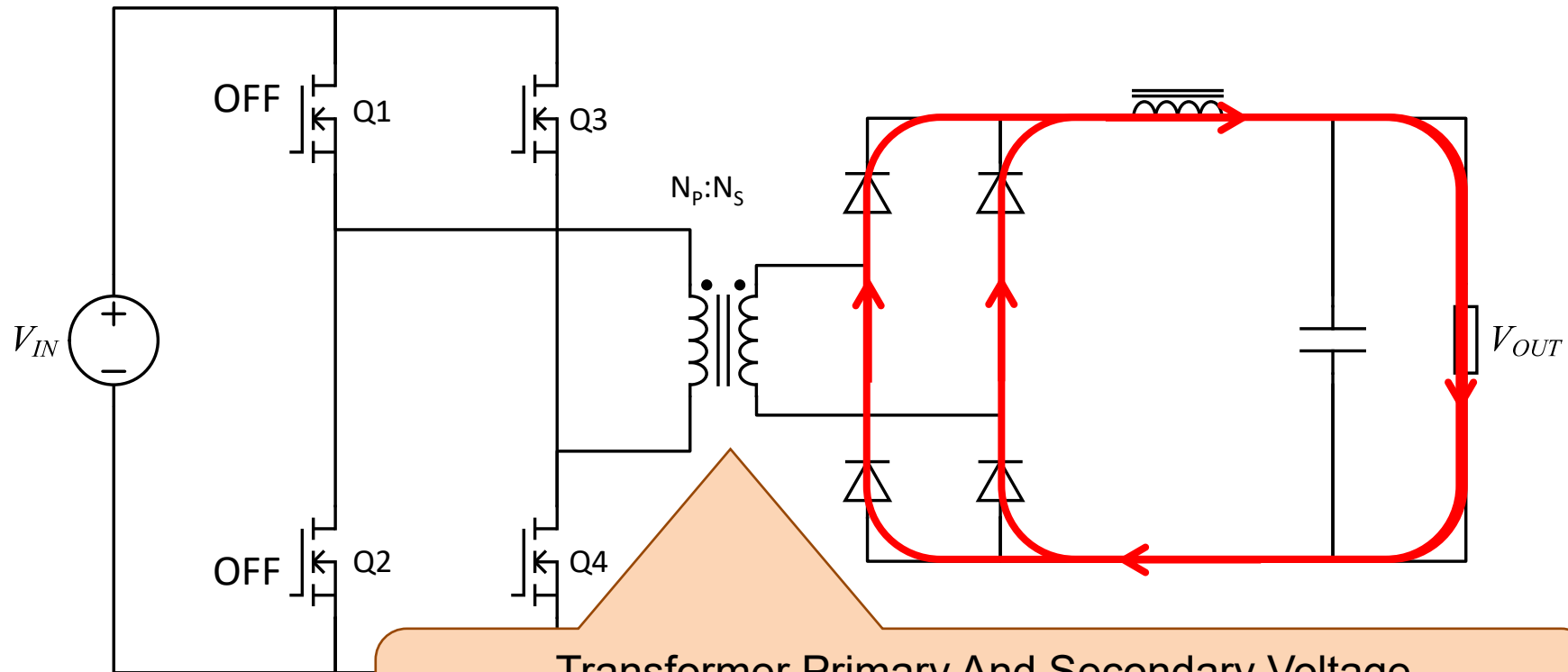

Transformer Primary And Secondary Voltage
Are 0 V During Off Time Because The
Secondary Winding Is Shorted By The Conducting Diodes


Full-Bridge Converter w/FW Rectifier

On Time 2

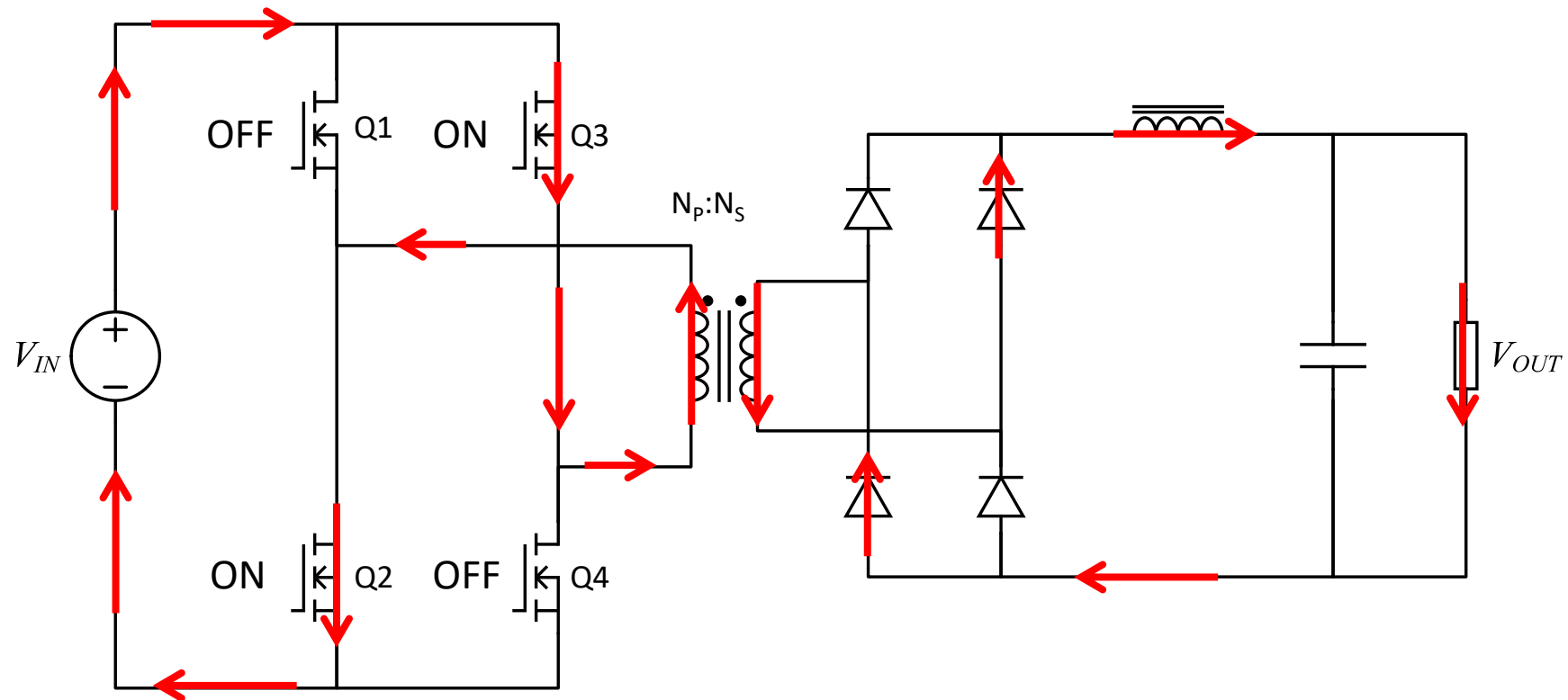


Full-Bridge Converter w/FW Rectifier

Off Time 2

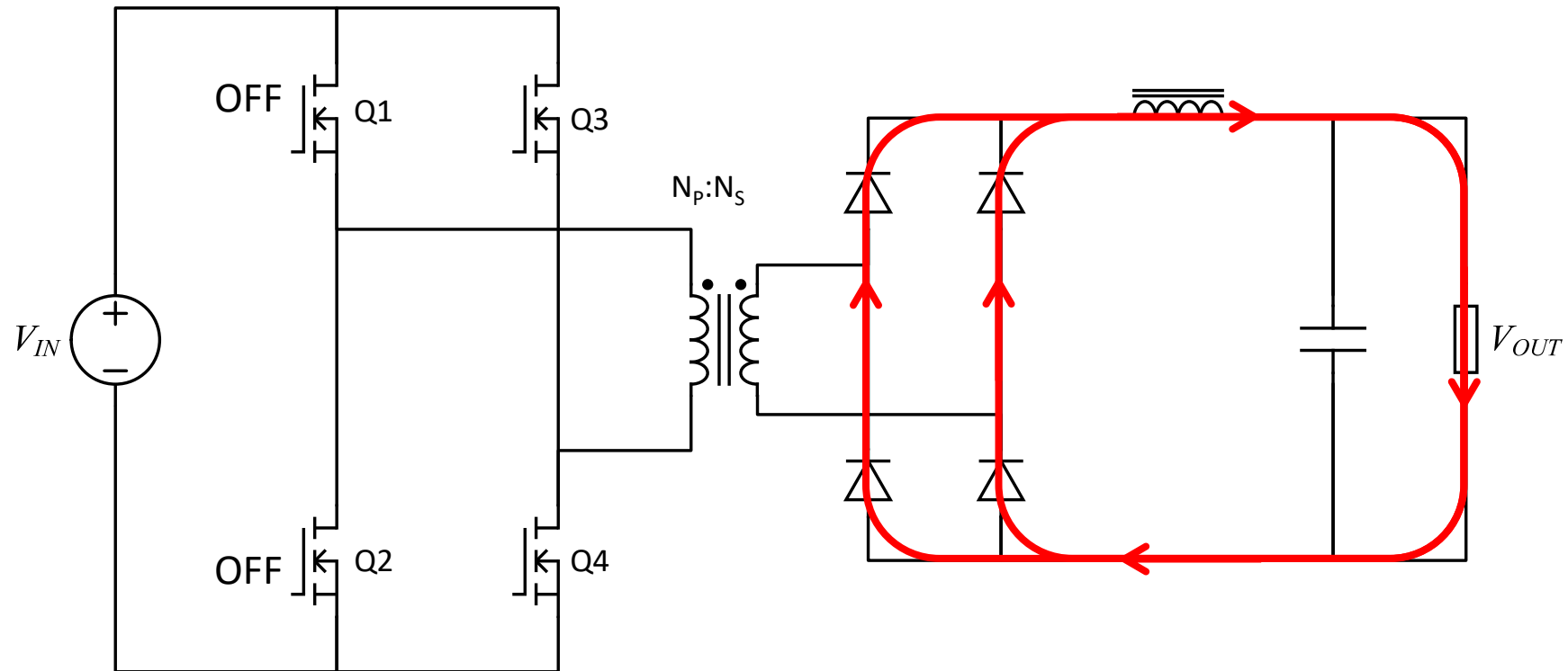


Full-Bridge Converter w/FW Rectifier

Conversion Ratio

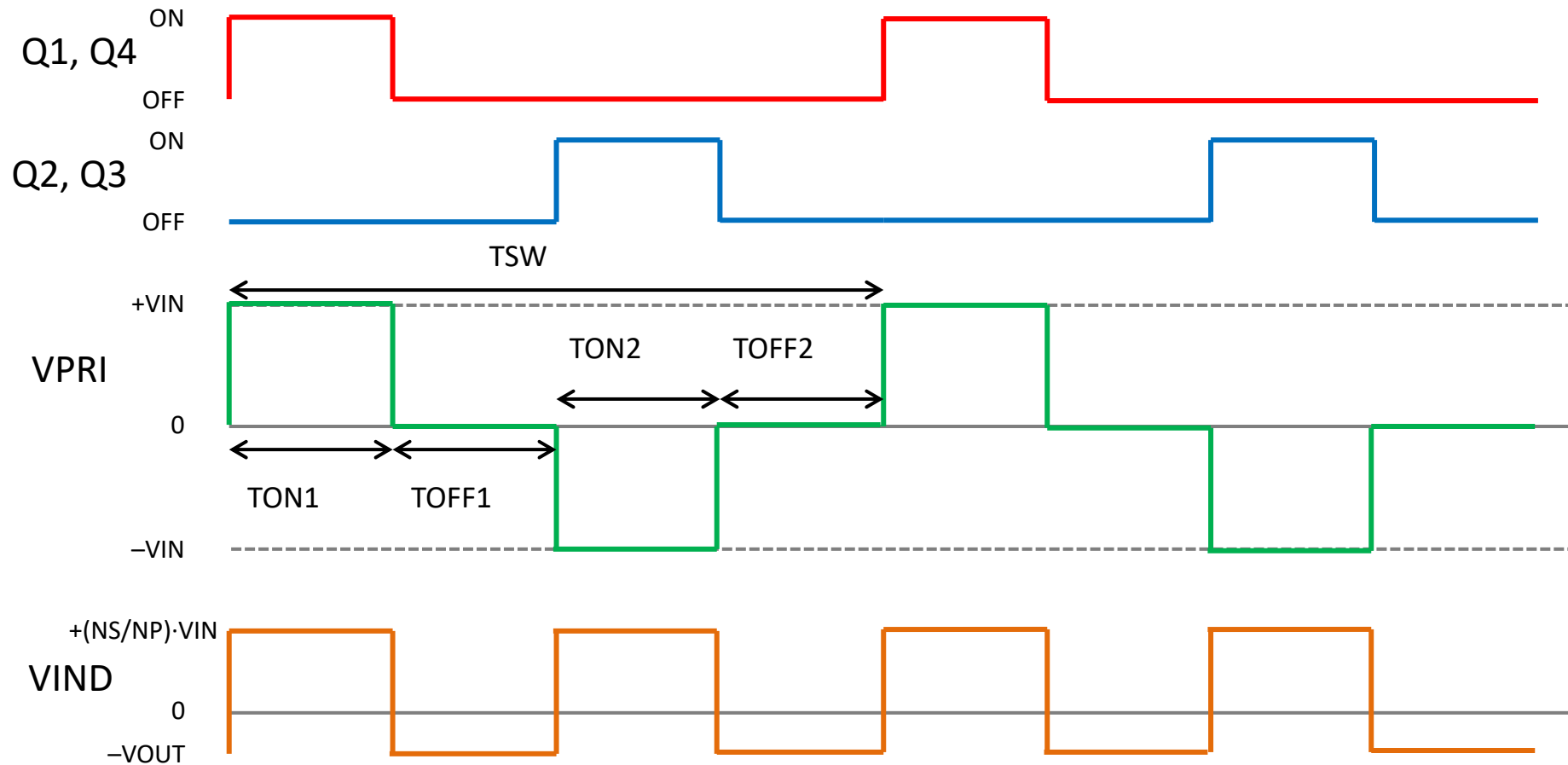

Full-Bridge Converter w/FW Rectifier

Conversion Ratio

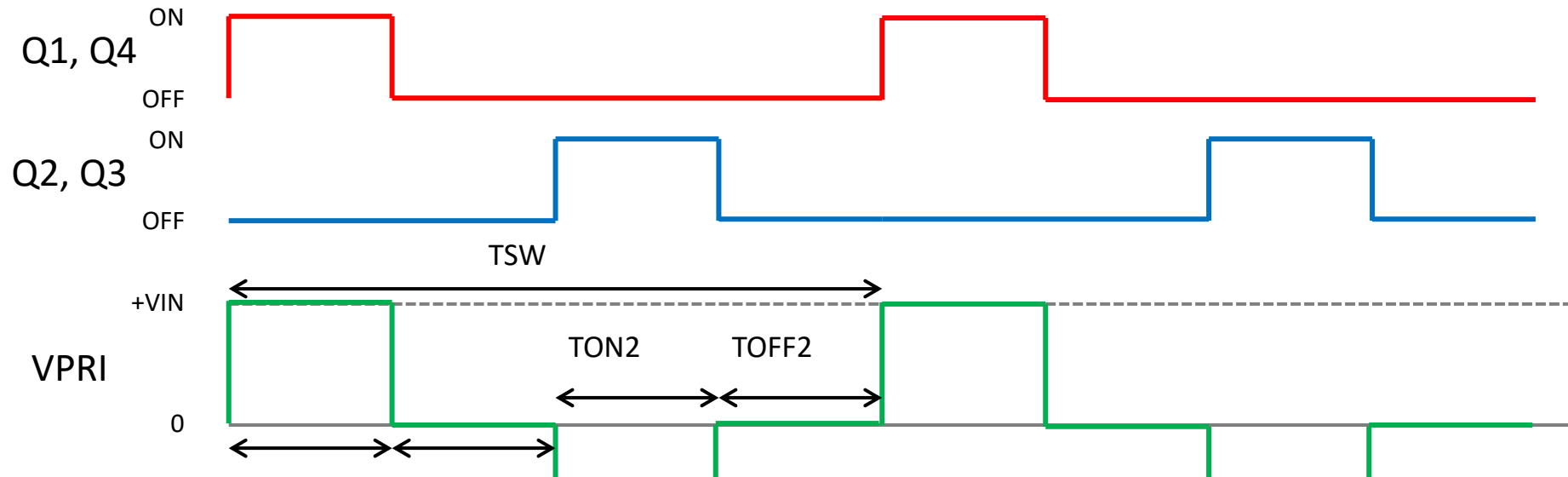

$$T_{SW} = T_{ON1} + T_{OFF2} + T_{ON2} + T_{OFF2}$$

$$D = \frac{T_{ON}}{T_{ON} + T_{OFF}}$$

$$T_{ON1} = T_{ON2} = T_{ON}$$

$$T_{OFF1} = T_{OFF2} = T_{OFF}$$

$$= \frac{T_{ON1} + T_{ON2}}{T_{SW}} = \frac{2 \cdot T_{ON}}{T_{SW}}$$

Full-Bridge Converter w/FW Rectifier

Conversion Ratio

$$V_L(T_{ON1}) \cdot T_{ON1} + V_L(T_{OFF1}) \cdot T_{OFF1} + V_L(T_{ON2}) \cdot T_{ON2} + V_L(T_{OFF2}) \cdot T_{OFF2} = 0$$

$$V_L(T_{ON}) \cdot T_{ON} + V_L(T_{OFF}) \cdot T_{OFF} + V_L(T_{ON}) \cdot T_{ON} + V_L(T_{OFF}) \cdot T_{OFF} = 0$$

$$V_L(T_{ON}) \cdot 2 \cdot T_{ON} + V_L(T_{OFF}) \cdot 2 \cdot T_{OFF} = 0$$

$$V_L(T_{ON}) \cdot \frac{2 \cdot T_{ON}}{T_{SW}} + V_L(T_{OFF}) \cdot \frac{T_{SW} - 2 \cdot T_{ON}}{T_{SW}} = 0$$

$$V_L(T_{ON}) \cdot D + V_L(T_{OFF}) \cdot (1 - D) = 0$$

$$\left(\frac{N_S}{N_P} \cdot V_{IN} - V_{OUT} \right) \cdot D + (-V_{OUT}) \cdot (1 - D) = 0$$

$$\frac{N_S}{N_P} \cdot V_{IN} \cdot D - V_{OUT} \cdot D - V_{OUT} + V_{OUT} \cdot D = 0$$


$$\frac{N_S}{N_P} \cdot V_{IN} \cdot D = V_{OUT}$$

$$V_{OUT} = D \cdot \frac{N_S}{N_P} \cdot V_{IN}$$

Inductor Volt-
Second
Balance


Same As Buck Converter Except:
- Transformer Turns Ratio

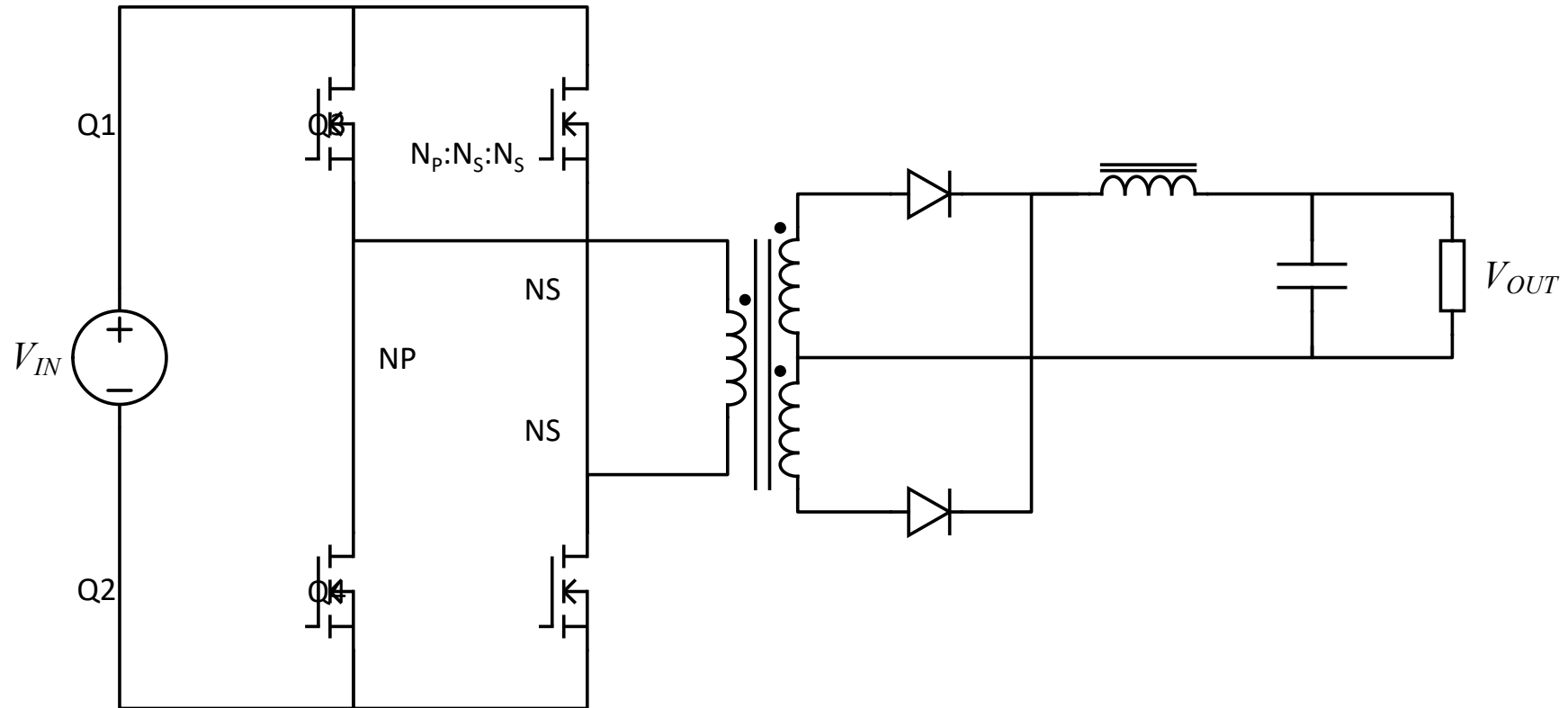Full-Bridge Converter w/Center Tapped Rectifier




Full-Bridge Converter w/CT Rectifier

On Time 1

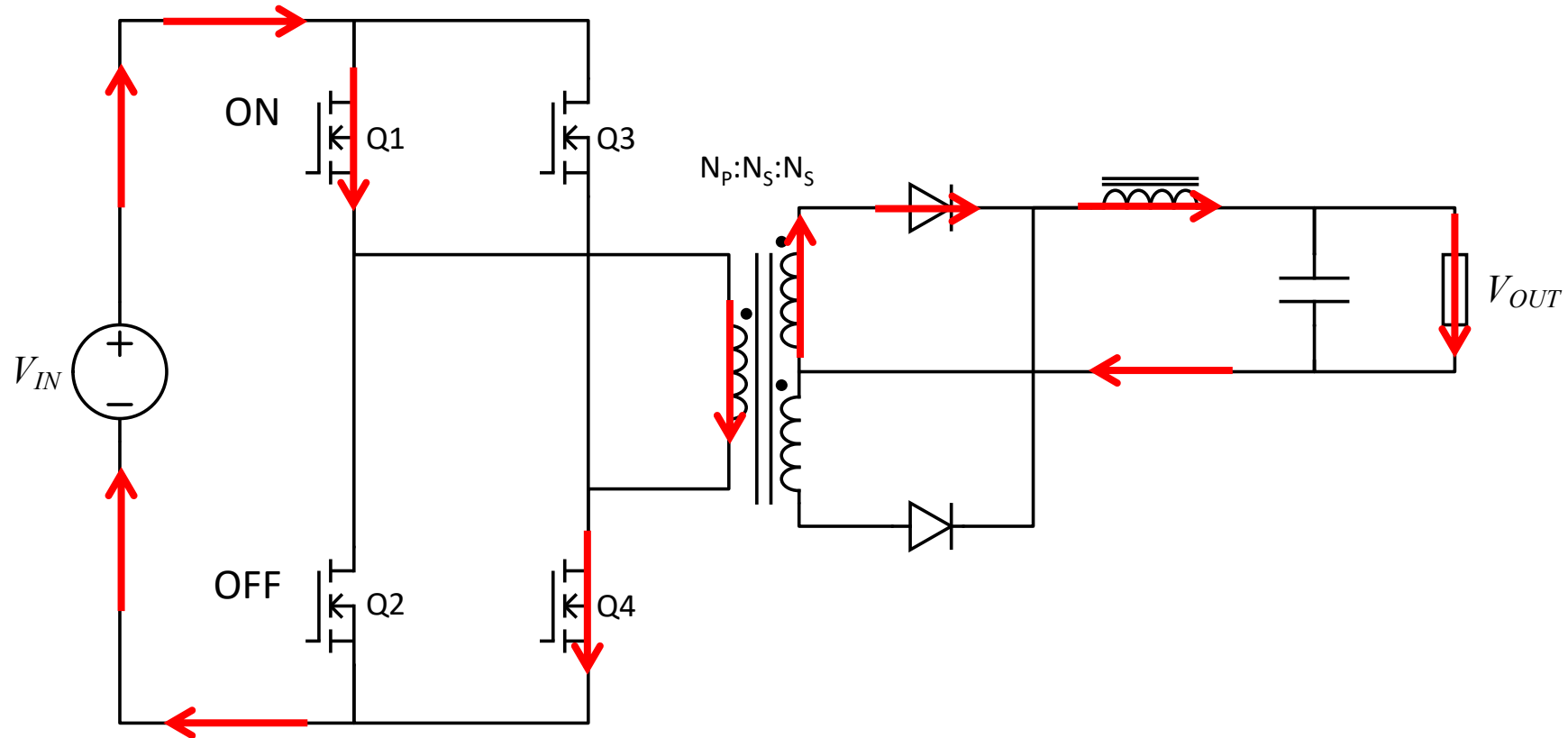


Full-Bridge Converter w/CT Rectifier

On Time 1

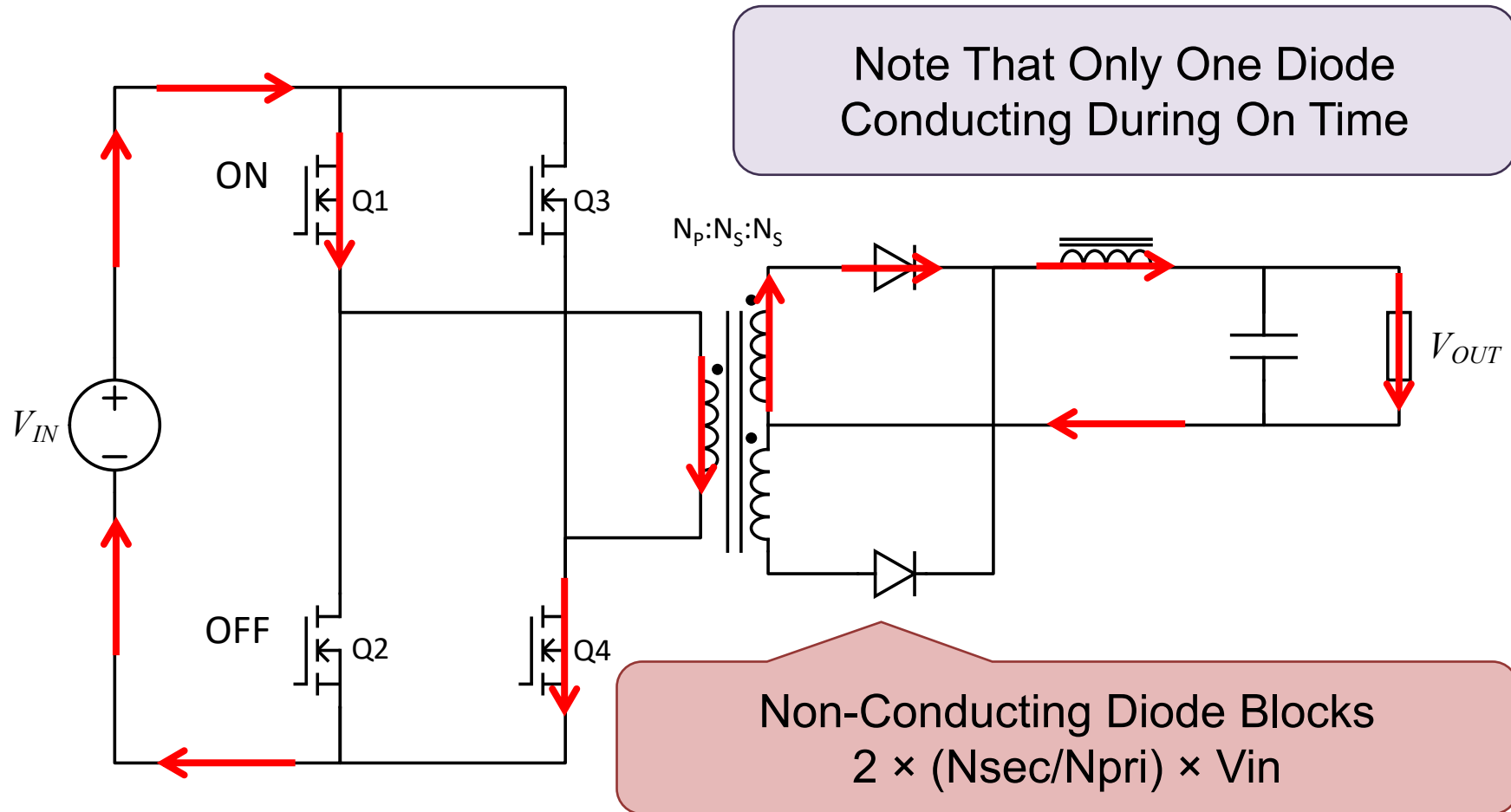

Full-Bridge Converter w/CT Rectifier


Off Time 1

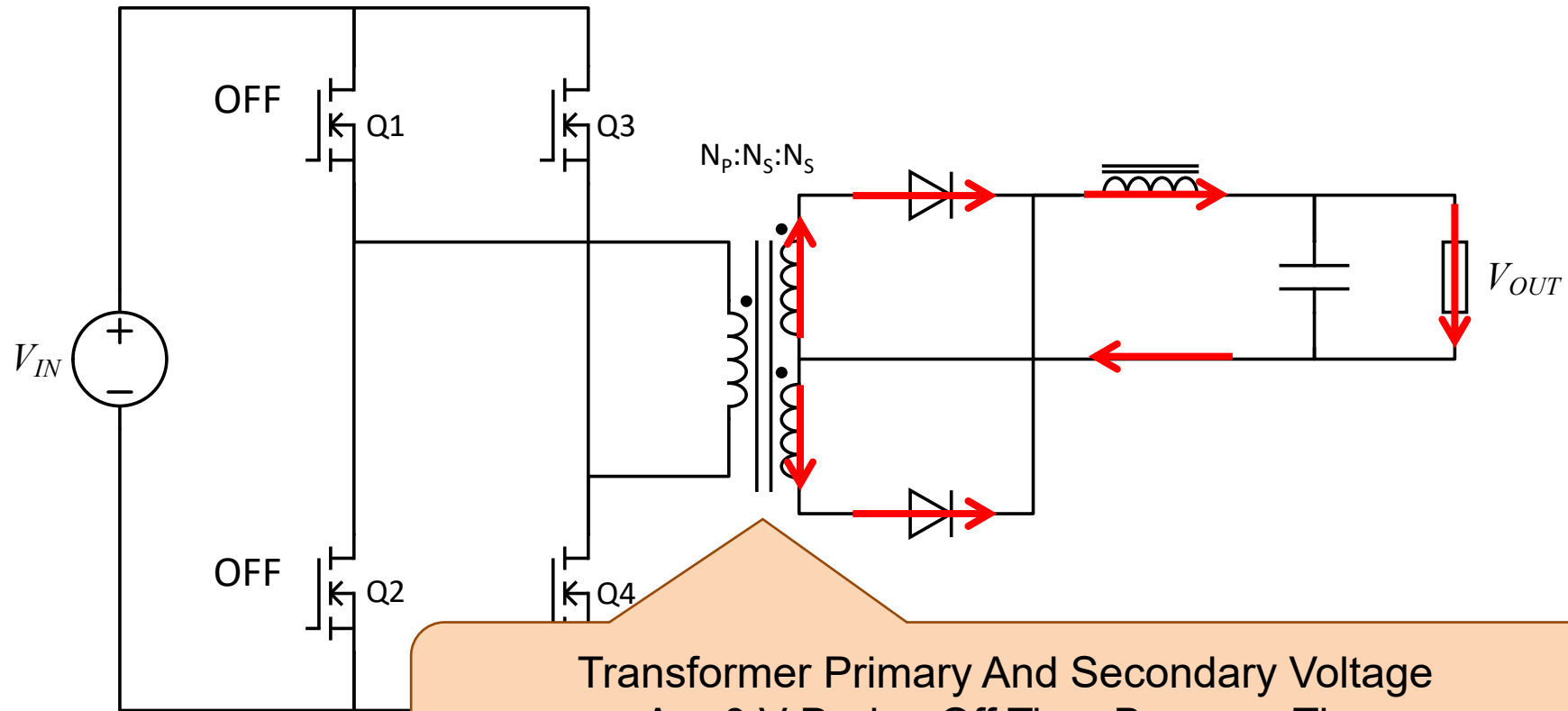

Transformer Primary And Secondary Voltage Are 0 V During Off Time Because The Secondary Winding Is Shorted By The Conducting Diodes


Full-Bridge Converter w/CT Rectifier

On Time 2

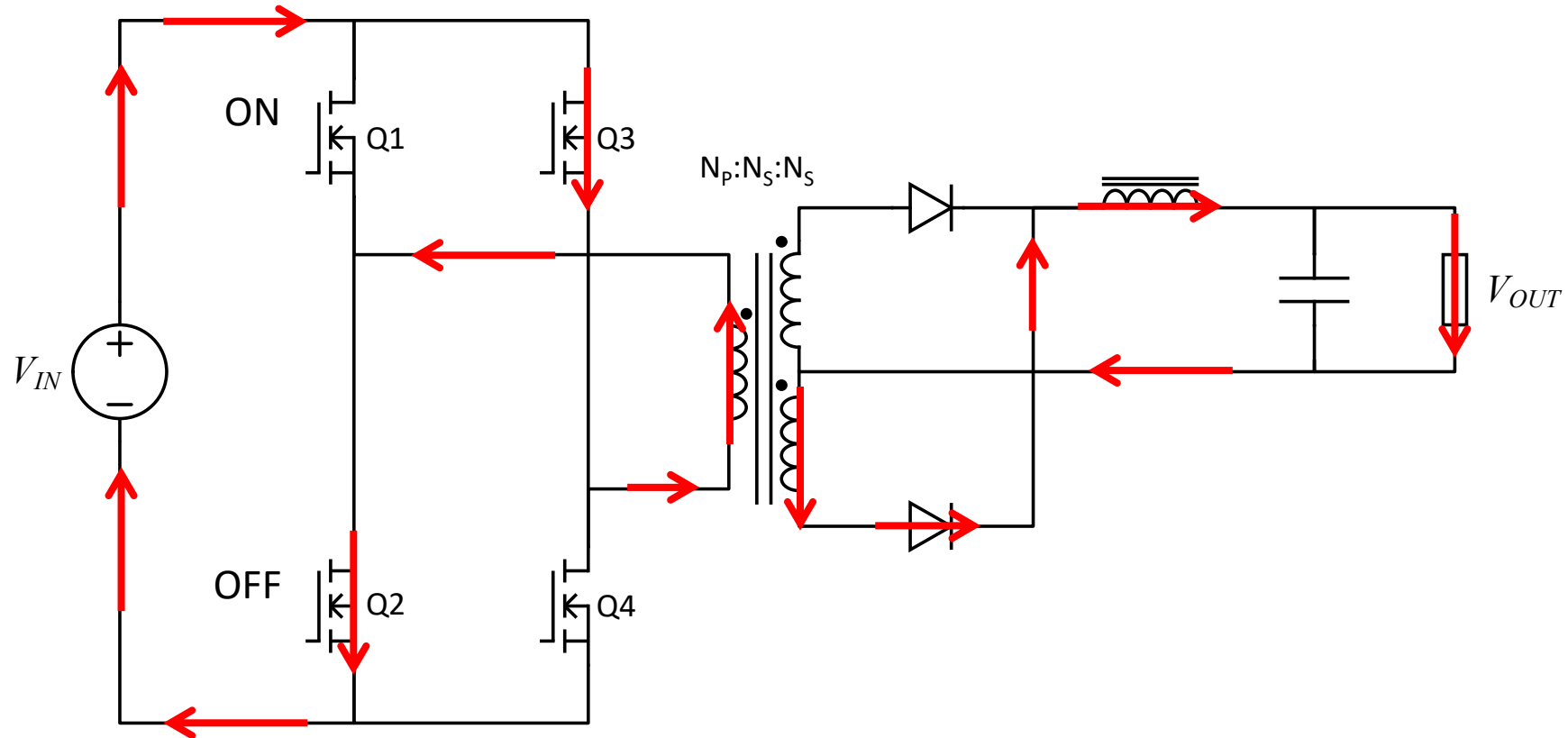


Full-Bridge Converter w/CT Rectifier

Off Time 2

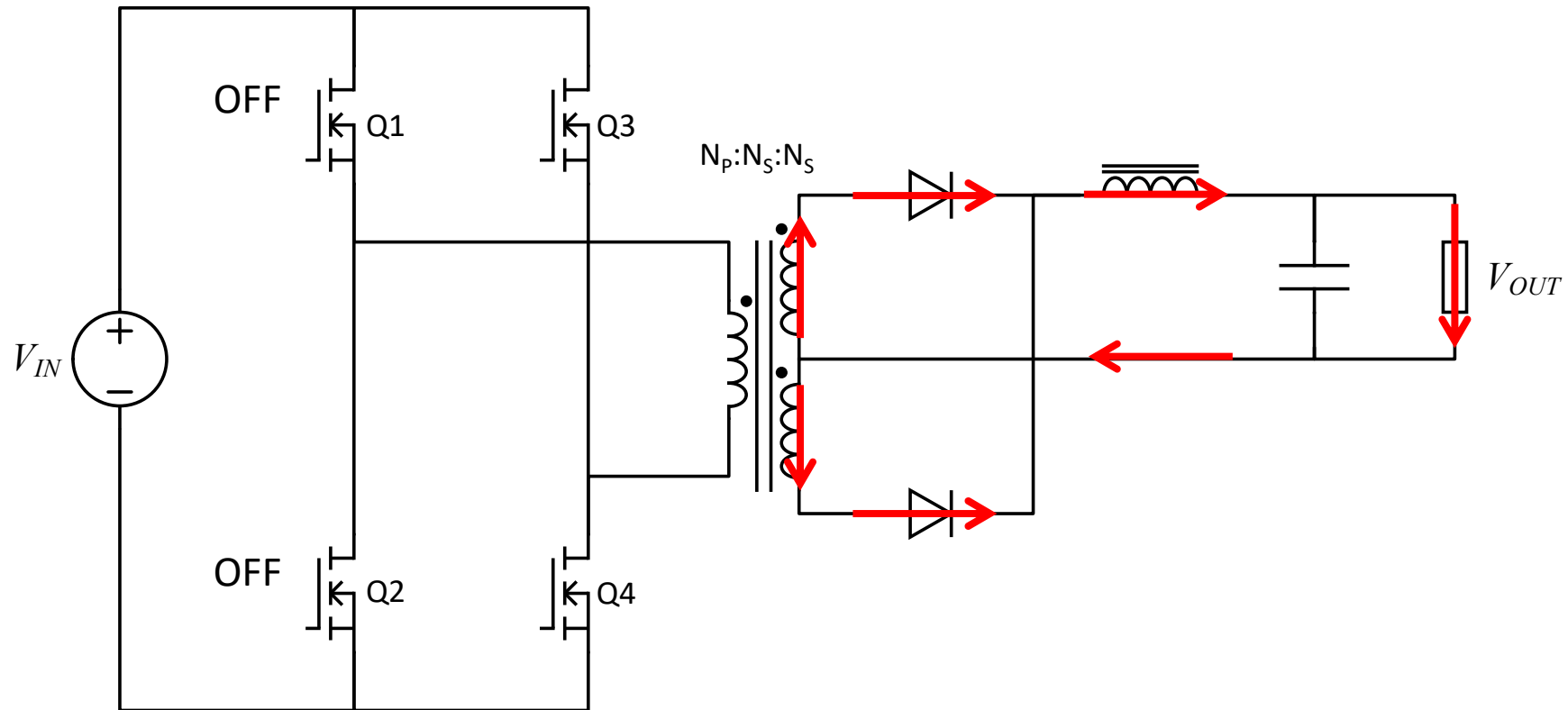

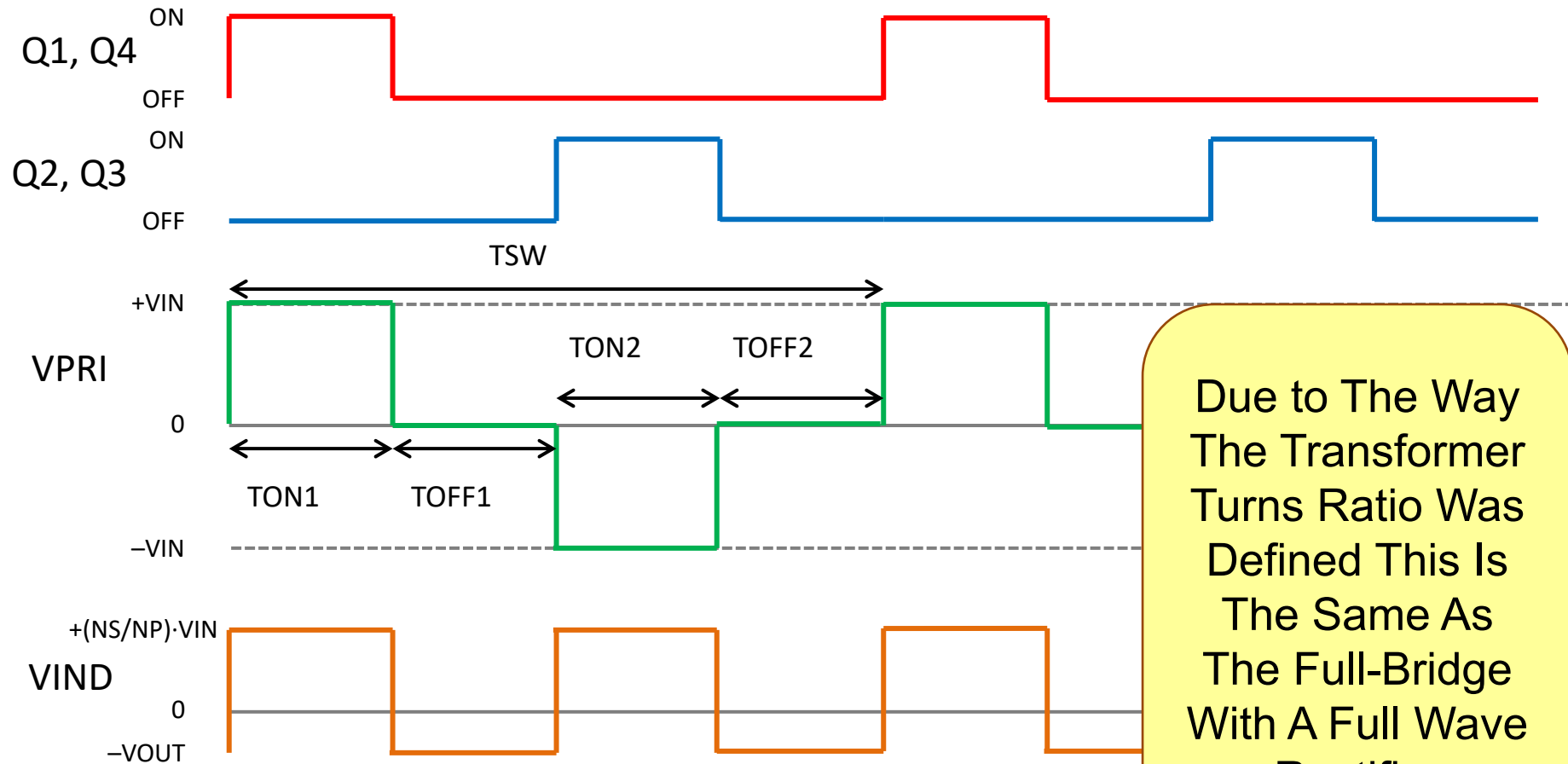
Full-Bridge Converter w/CT Rectifier Conversion Ratio



Due to The Way The Transformer Turns Ratio Was Defined This Is The Same As The Full-Bridge With A Full Wave Rectifier

Full-Bridge Converter w/CT Rectifier

Conversion Ratio

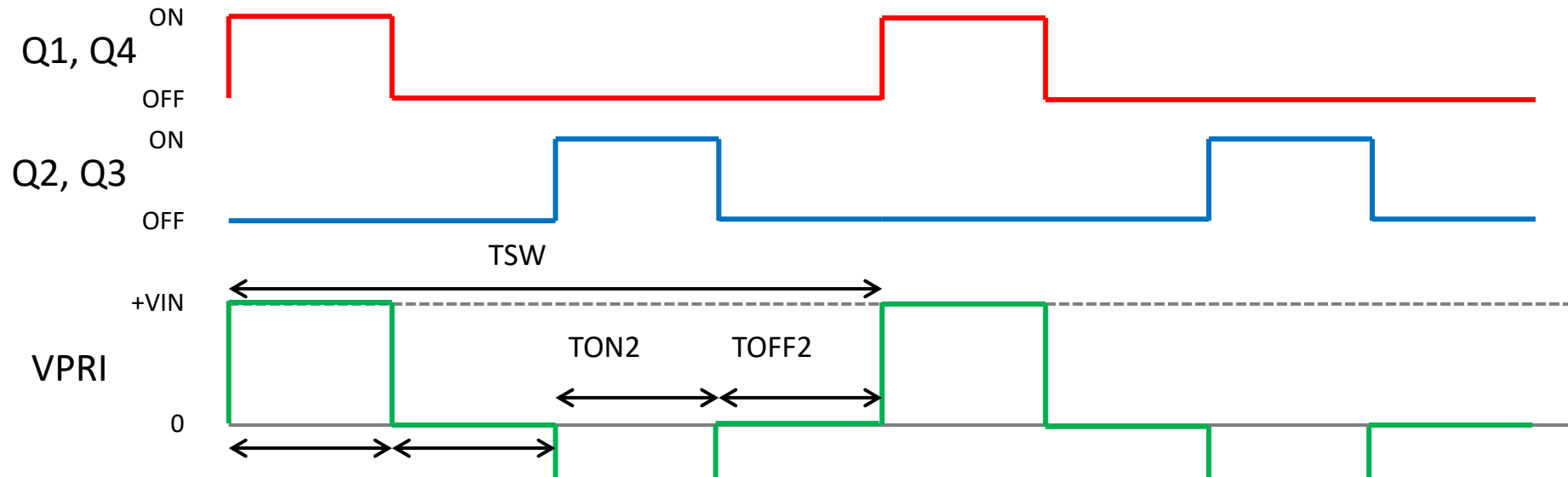

$$T_{SW} = T_{ON1} + T_{OFF2} + T_{ON2} + T_{OFF2}$$

$$D = \frac{T_{ON}}{T_{ON} + T_{OFF}}$$

$$T_{ON1} = T_{ON2} = T_{ON}$$

$$T_{OFF1} = T_{OFF2} = T_{OFF}$$

$$= \frac{T_{ON1} + T_{ON2}}{T_{SW}} = \frac{2 \cdot T_{ON}}{T_{SW}}$$

Full-Bridge Converter w/CT Rectifier

Conversion Ratio

$$V_L(T_{ON1}) \cdot T_{ON1} + V_L(T_{OFF1}) \cdot T_{OFF1} + V_L(T_{ON2}) \cdot T_{ON2} + V_L(T_{OFF2}) \cdot T_{OFF2} = 0$$

$$V_L(T_{ON}) \cdot T_{ON} + V_L(T_{OFF}) \cdot T_{OFF} + V_L(T_{ON}) \cdot T_{ON} + V_L(T_{OFF}) \cdot T_{OFF} = 0$$

$$V_L(T_{ON}) \cdot 2 \cdot T_{ON} + V_L(T_{OFF}) \cdot 2 \cdot T_{OFF} = 0$$

$$V_L(T_{ON}) \cdot \frac{2 \cdot T_{ON}}{T_{SW}} + V_L(T_{OFF}) \cdot \frac{T_{SW} - 2 \cdot T_{ON}}{T_{SW}} = 0$$

$$V_L(T_{ON}) \cdot D + V_L(T_{OFF}) \cdot (1 - D) = 0$$

$$\left(\frac{N_S}{N_P} \cdot V_{IN} - V_{OUT} \right) \cdot D + (-V_{OUT}) \cdot (1 - D) = 0$$

$$\frac{N_S}{N_P} \cdot V_{IN} \cdot D - V_{OUT} \cdot D - V_{OUT} + V_{OUT} \cdot D = 0$$

$$\frac{N_S}{N_P} \cdot V_{IN} \cdot D = V_{OUT}$$

$$V_{OUT} = D \cdot \frac{N_S}{N_P} \cdot V_{IN}$$

Inductor Volt-
Second
Balance

Due to The Way The Transformer
Turns Ratio Was Defined This Is
The Same As The Full-Bridge With
A Full Wave Rectifier

Same As Buck Converter Except:
- Transformer Turns Ratio

Full Bridge Converter

Advantages


- Isolated
- Good For 500 W And Up
- Multiple Isolated Outputs Possible
- Easy To Control
- Good Use Of Transformer Core
- Low Voltage Stress On Switching Transistors

Disadvantages


- Transformer Needed
- Four Switches And Associated Drive Circuits
- Must Have Way To Prevent Transformer Saturation
- Center Tap Output: High Voltage Stress On Output Diodes
- Full Wave Output: More Diodes And Diode Loss

APPENDIX IV.
Boost Converter
Discontinuous Conduction
And Critical Conduction Modes


Boost Converter

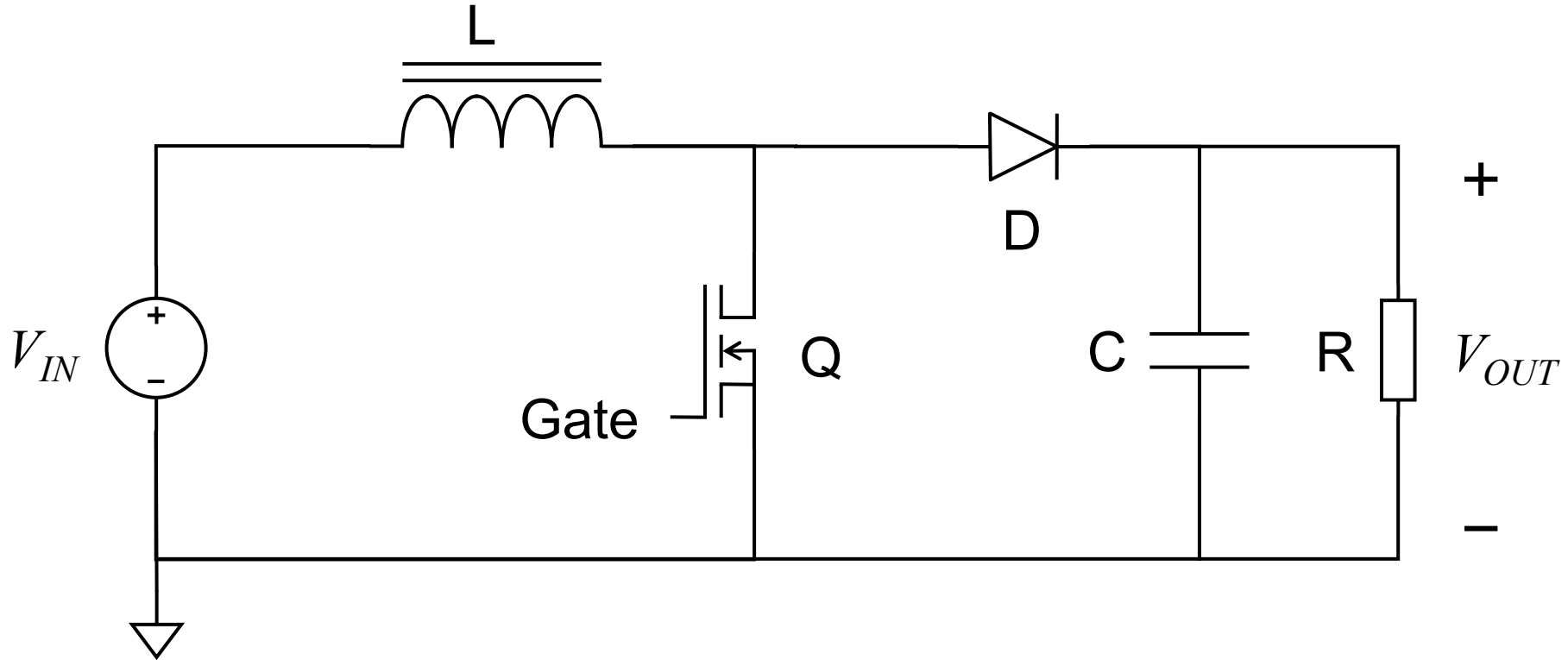

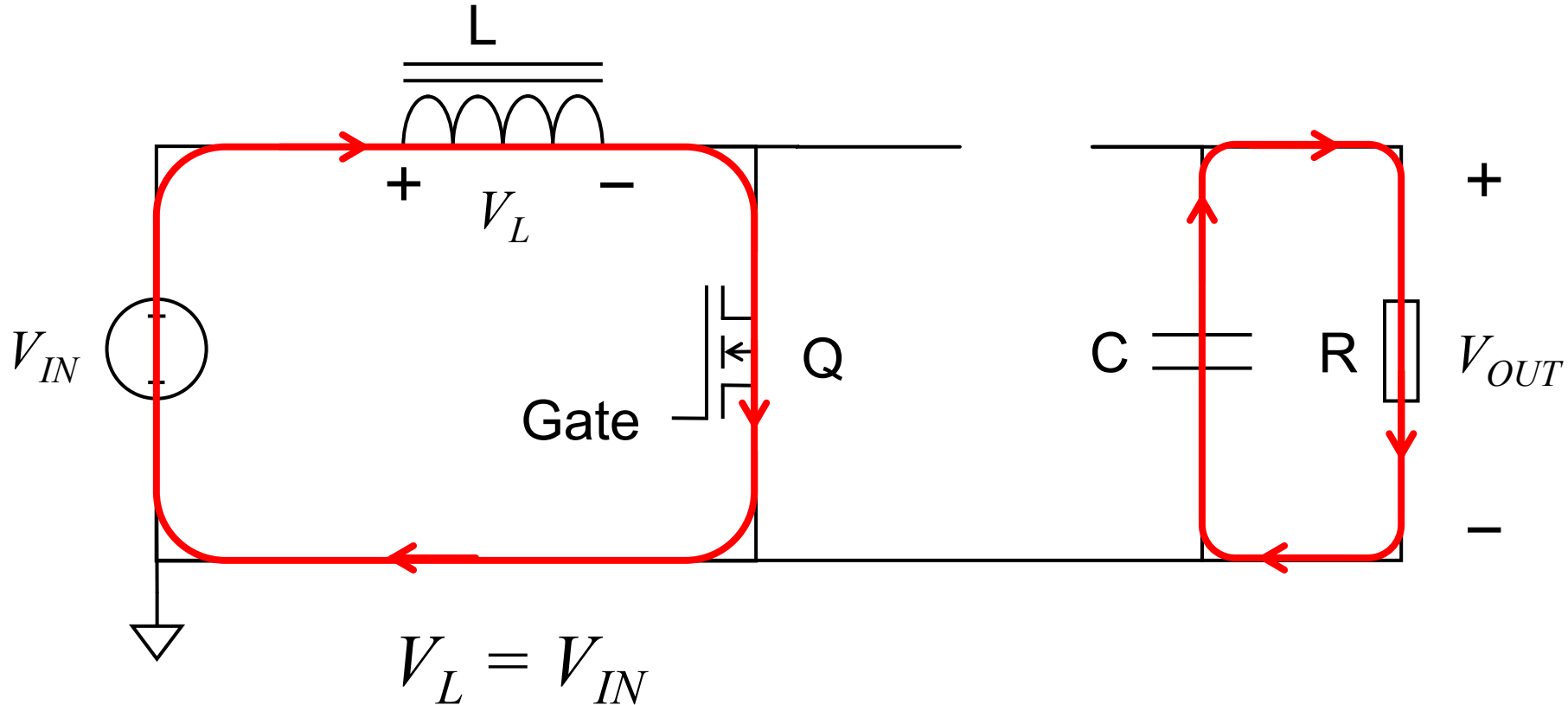
Boost Converter Discontinuous Conduction Mode: On Time



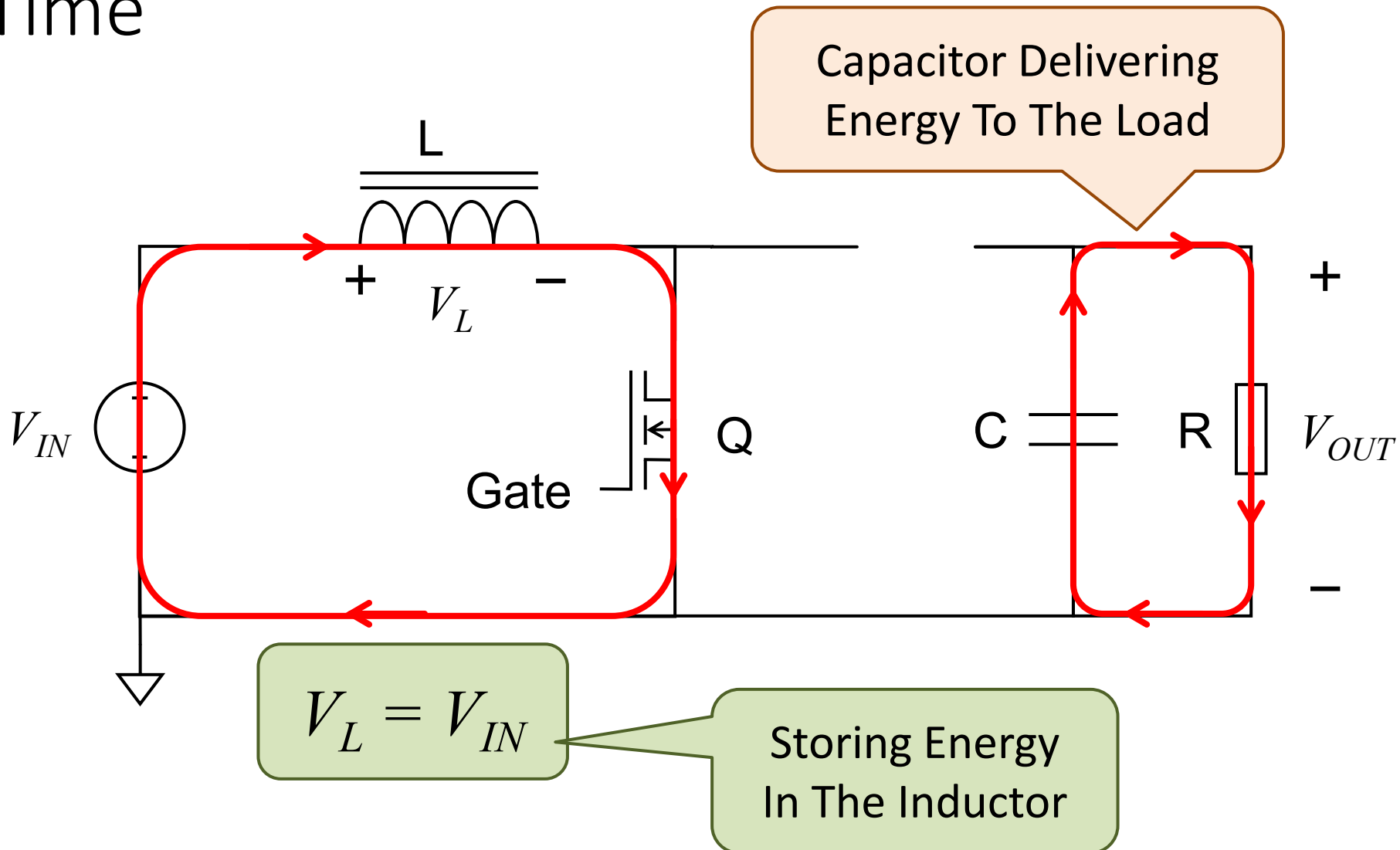
Boost Converter Discontinuous Conduction Mode: On Time



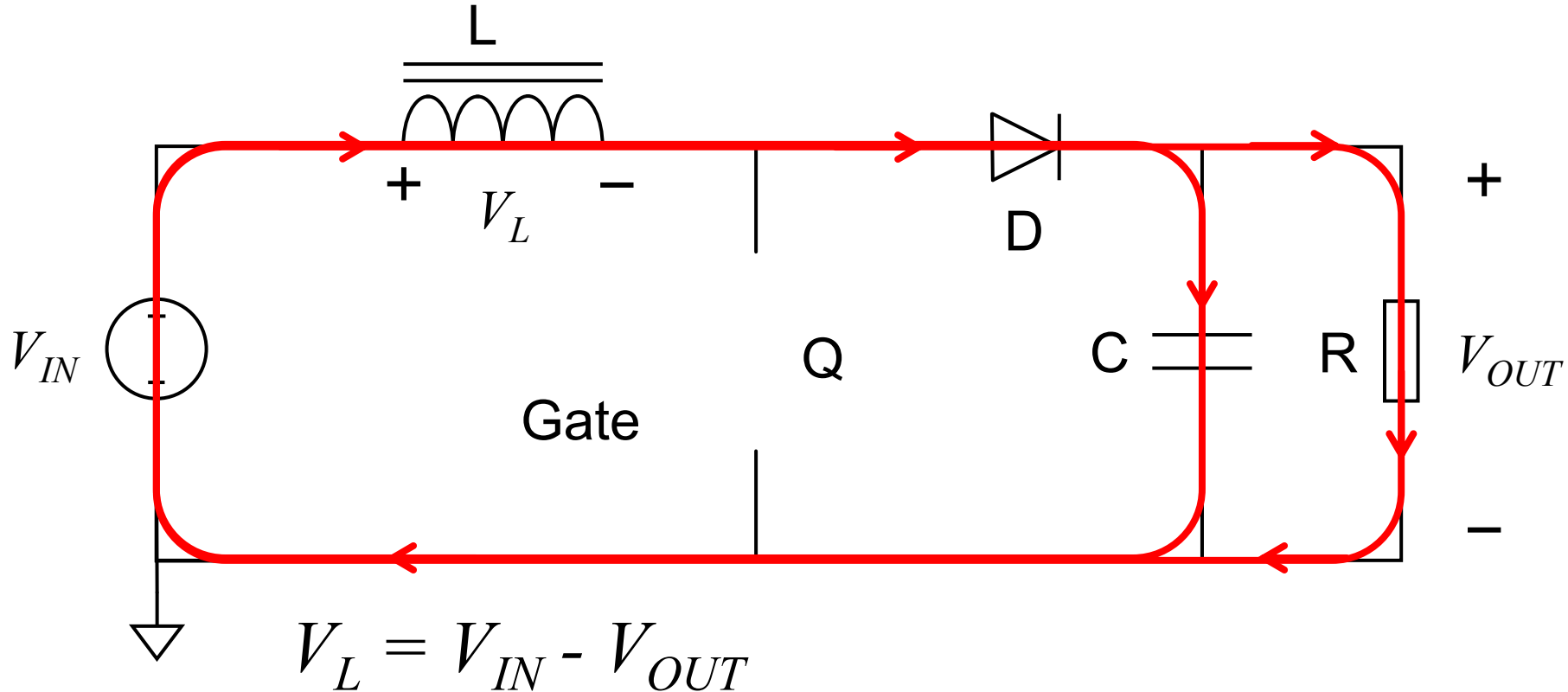
Boost Converter Discontinuous Conduction Mode: Off Time 1



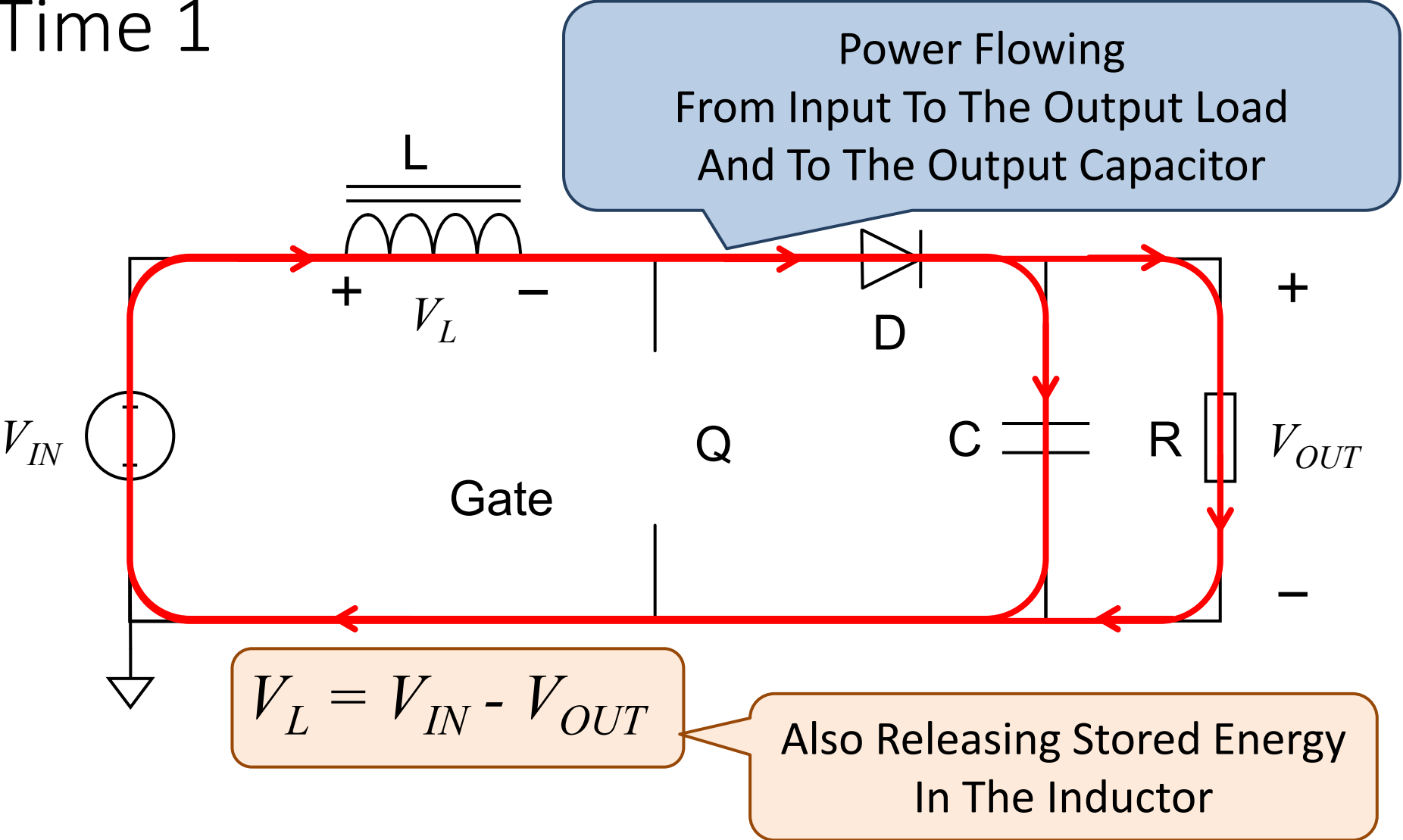
Boost Converter Discontinuous Conduction Mode: Off Time 1



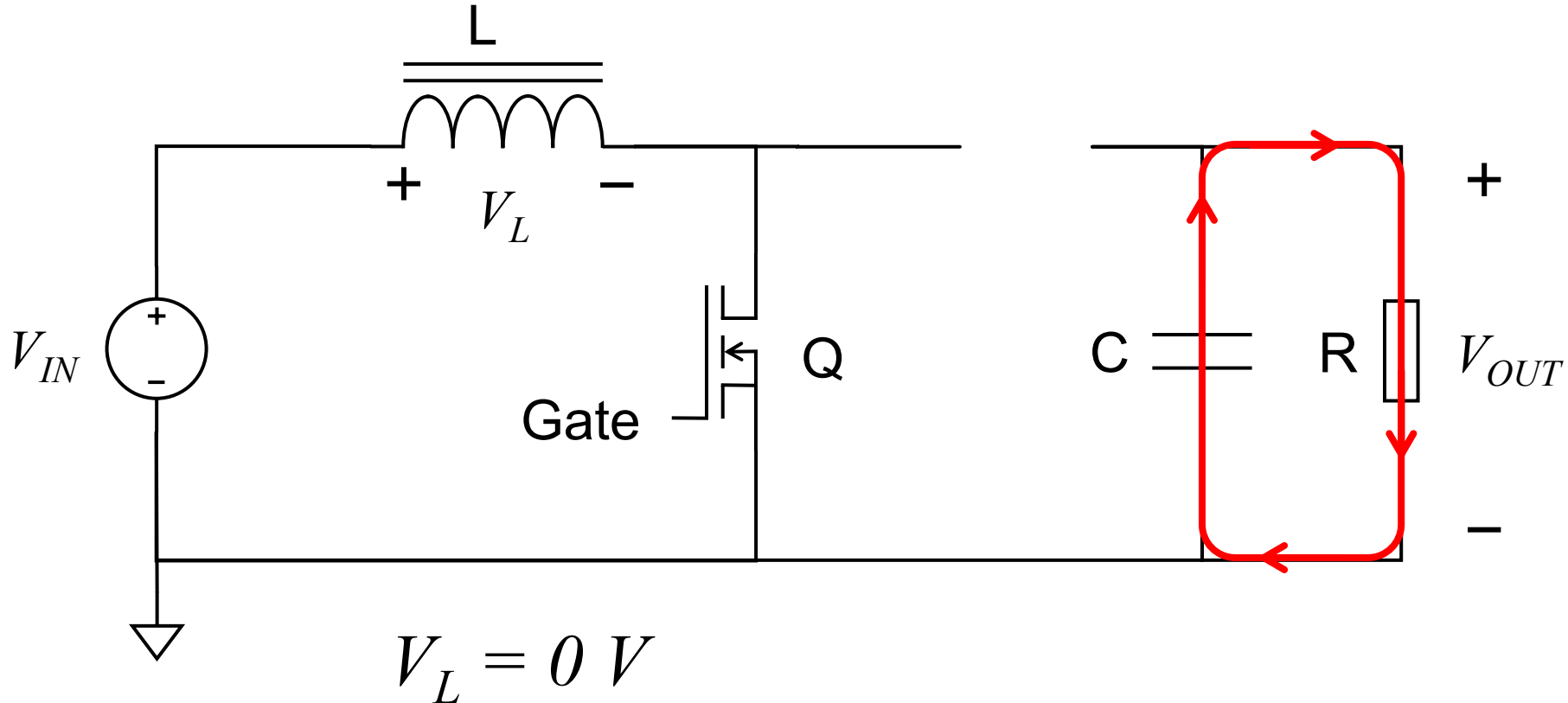
Boost Converter Discontinuous Conduction Mode: Off Time 2



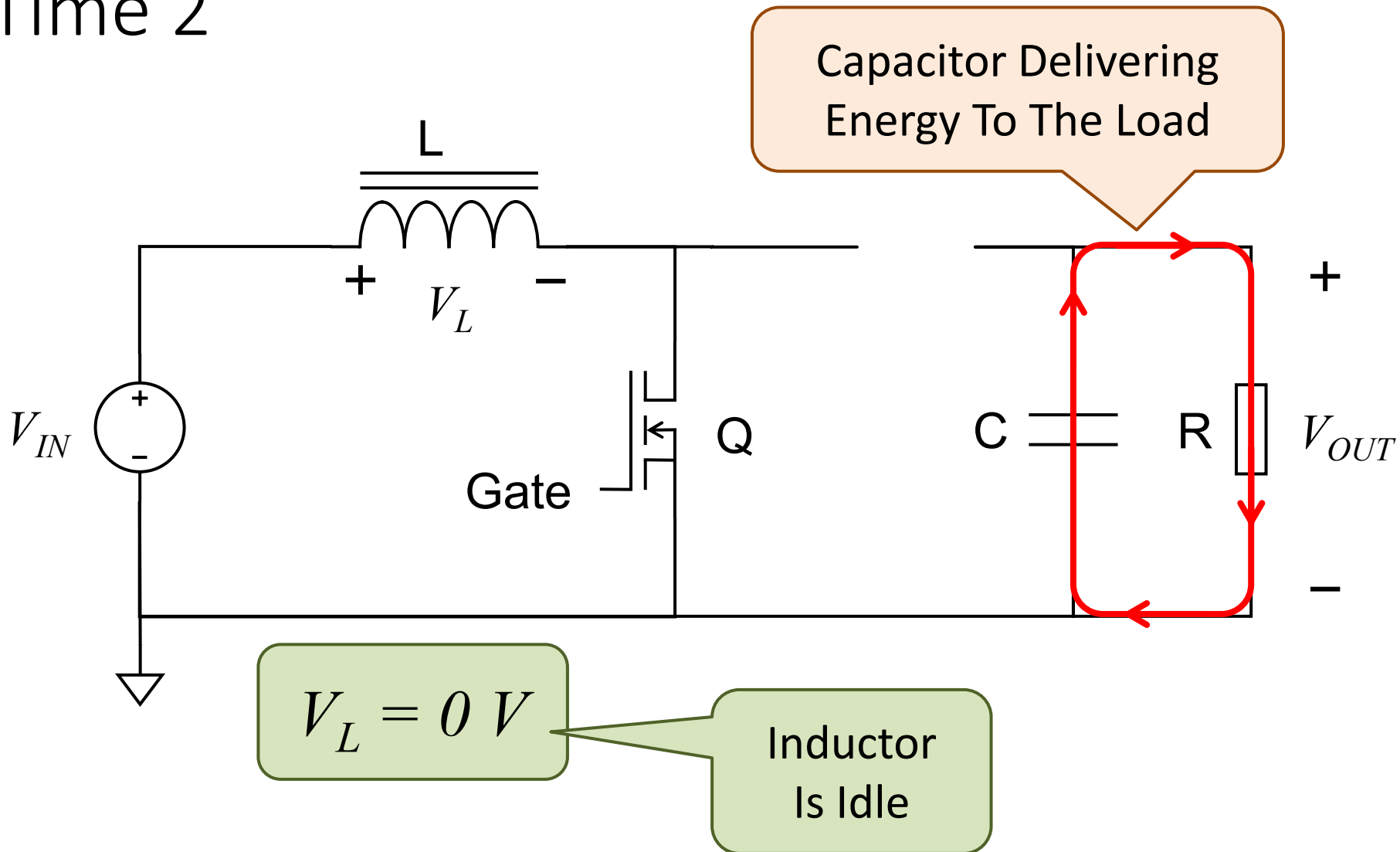
Boost Converter Discontinuous Conduction Mode: Off Time 2




Discontinuous Conduction Mode

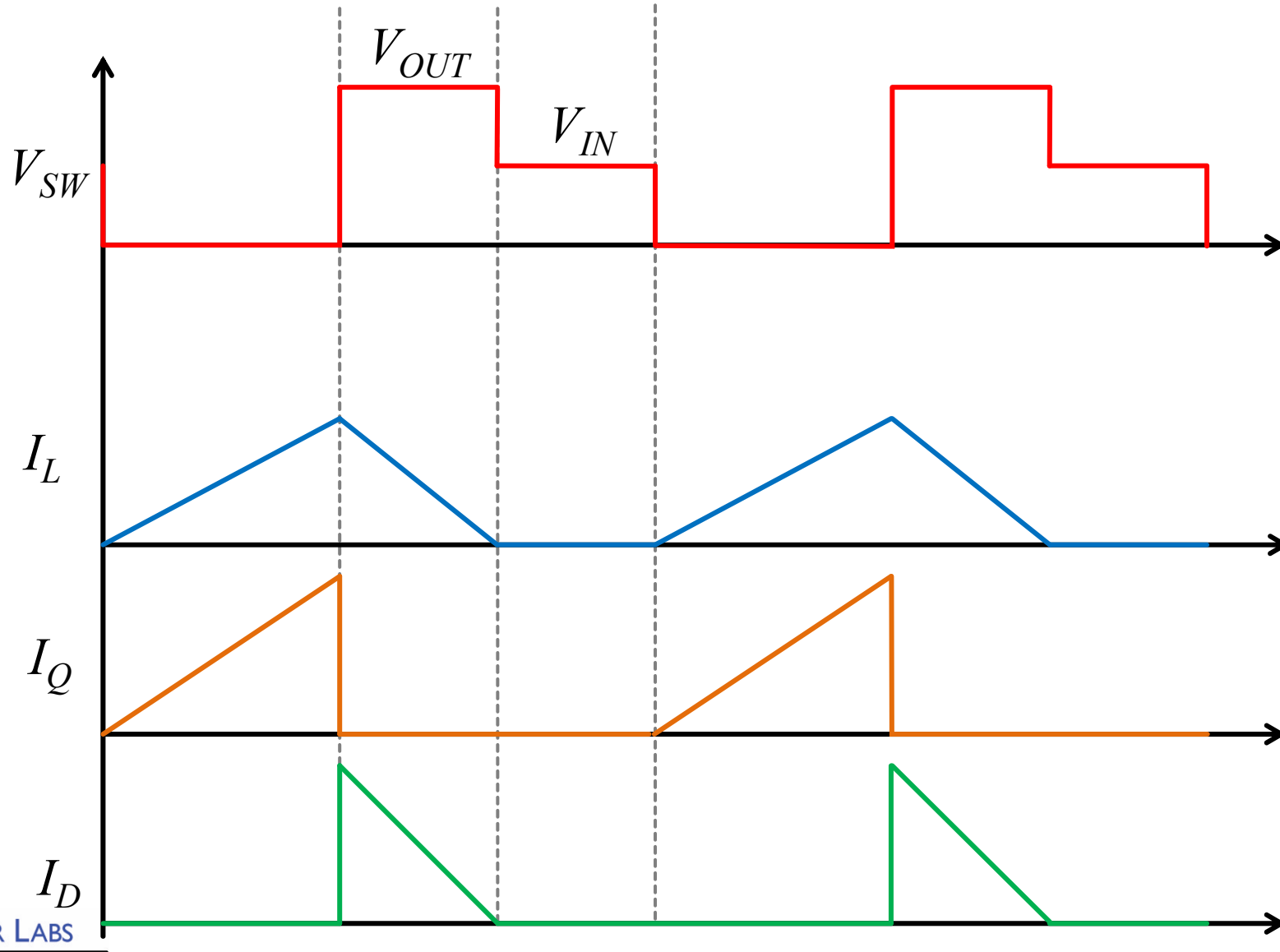


Discontinuous Conduction Mode

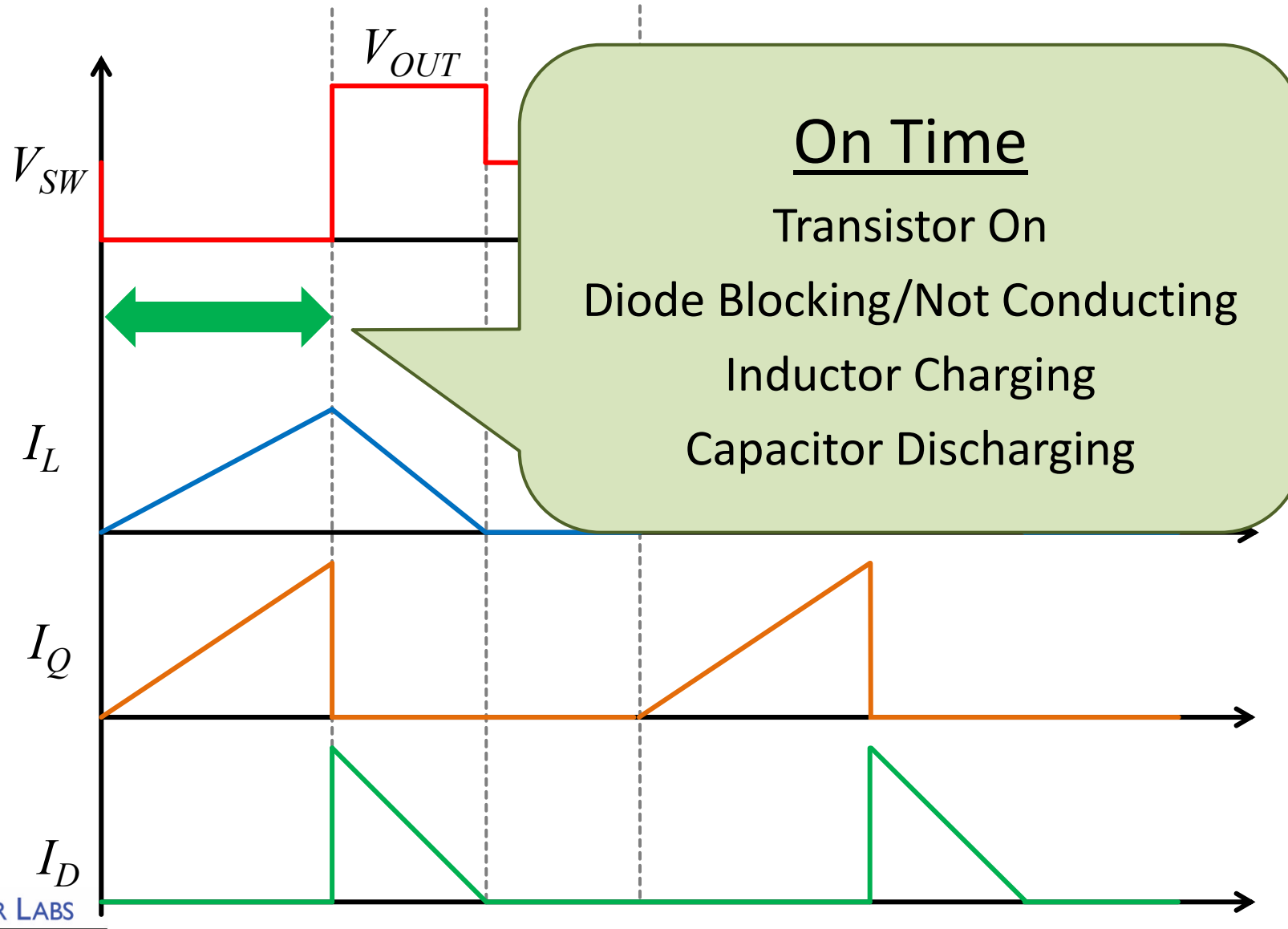

Discontinuous Conduction Mode

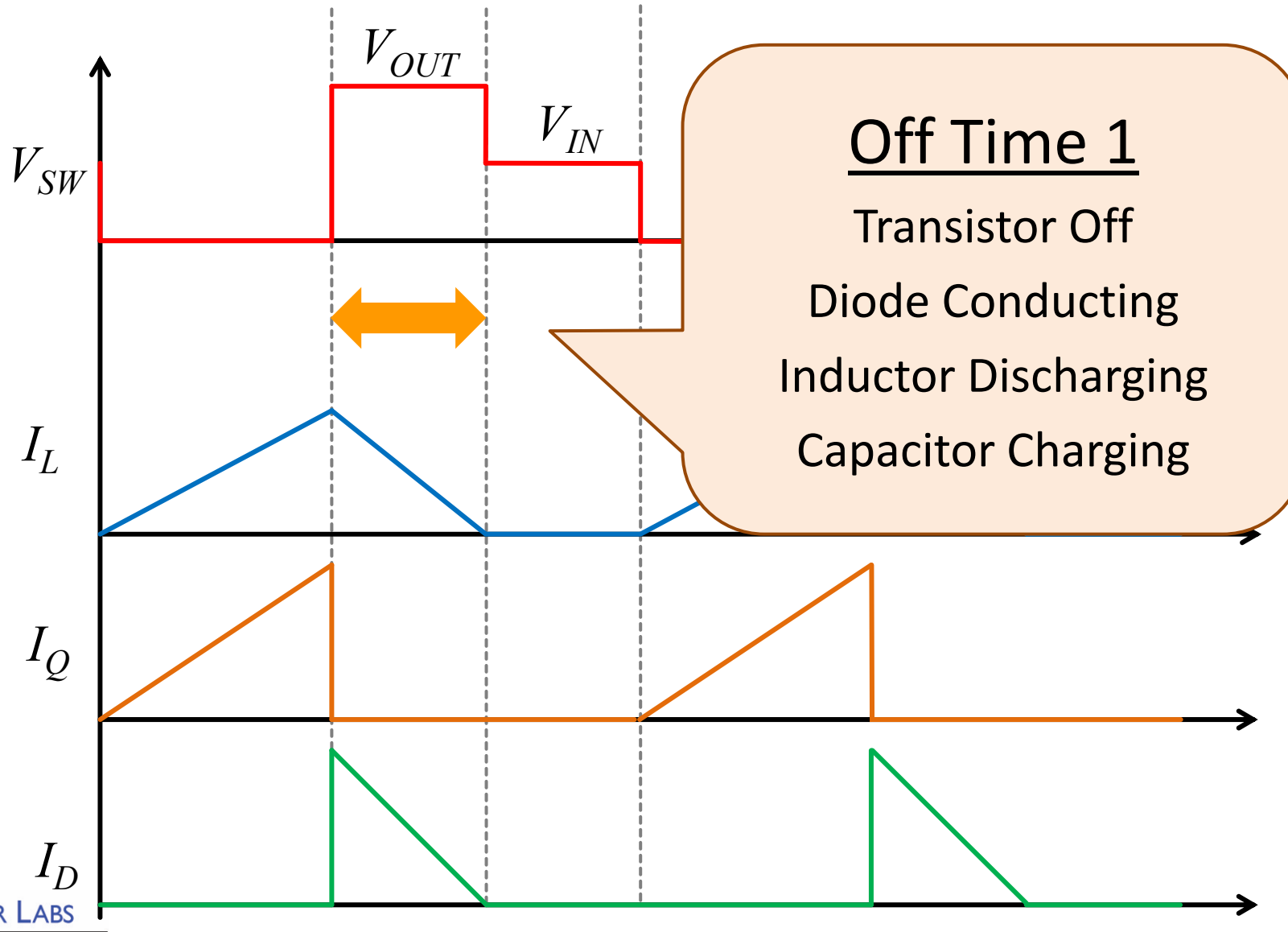

Discontinuous Conduction Mode

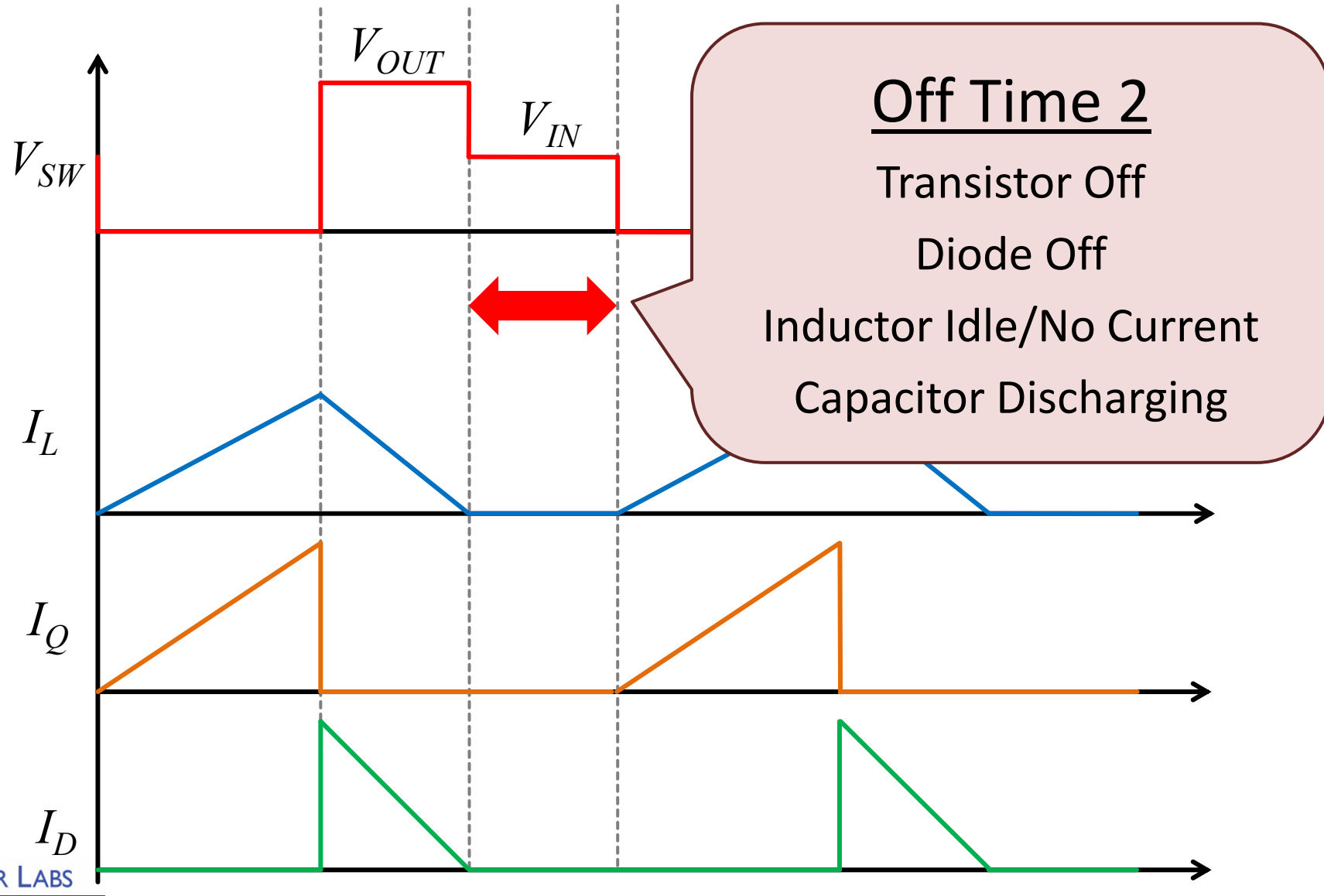

DCM Conversion Ratio


$$\frac{V_{OUT}}{V_{IN}} = \frac{1 + \sqrt{1 + 4 \cdot D^2 \cdot \frac{R \cdot T_{SW}}{2 \cdot L}}}{2}$$

- Nonlinear
- Depends On Load Resistance, Inductor, Switching Frequency
- Becomes Continuous Conduction Mode When:

$$\frac{2 \cdot L}{R \cdot T_{SW}} \geq D \cdot (1 - D)^2$$

Video Lab 11

Boost Converter In Discontinuous Mode

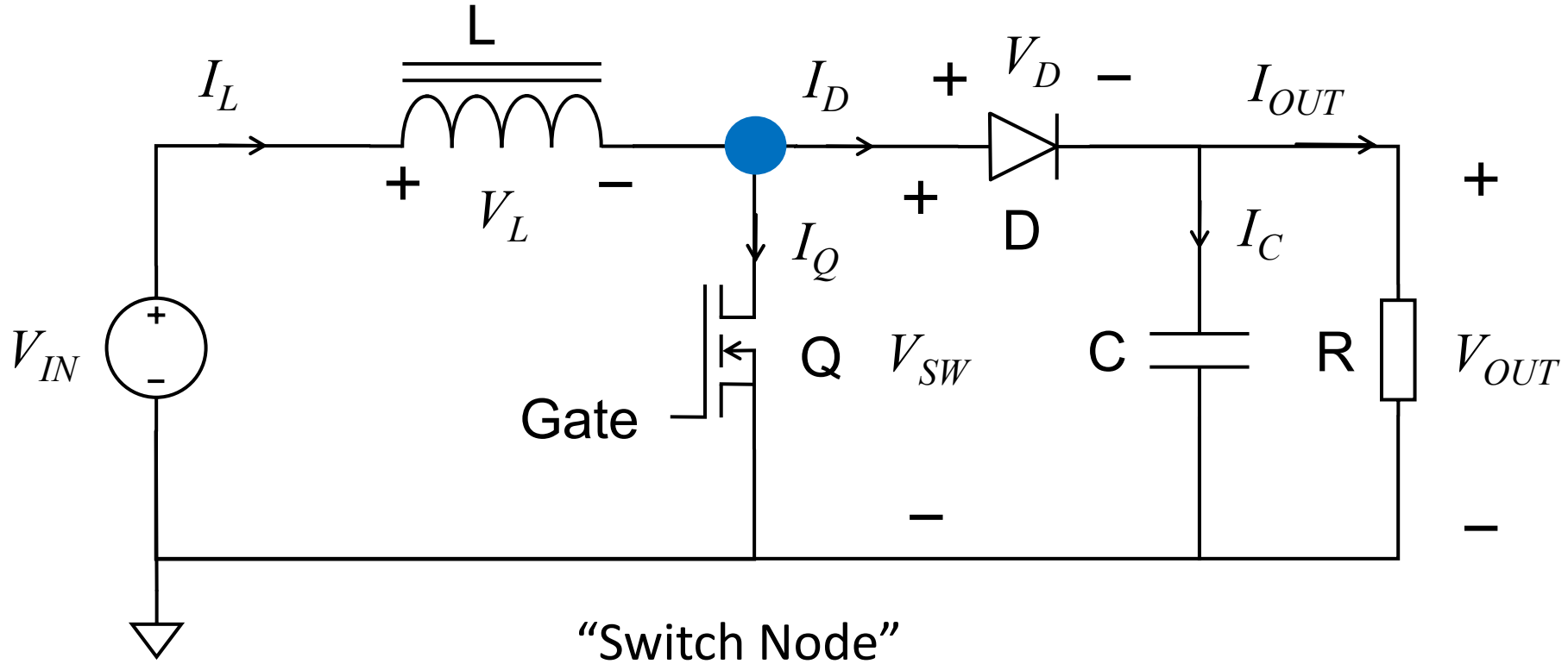

Video Lab 11

Boost Converter In Discontinuous Mode

- Switch Node
- Output Voltage
- Input Voltage
- Inductor Current



Video Lab 11

Boost Converter In Discontinuous Mode

We See Here
The Switch
Node Voltage
Oscillating As
The Inductor
Rings With the
Output
Capacitance
Of The
MOSFET

Can Also See
The Current In
The Inductor
Oscillating/
Ringing



Video Lab 11

Boost Converter In Discontinuous Mode

In The Video,
Note That The
Output Voltage
Increases As
The Load
Current Is
Decreased.

Why Do You
Think that
Happens?



Boost Discontinuous Mode


Advantages

- Easy To Design The Controller
- No Losses From Diode Reverse Recovery


Disadvantages

- High Peak Currents In Transistor, Diode, Inductor Means Significant I^2R Losses
- Large Output Capacitor


Critical Conduction Mode

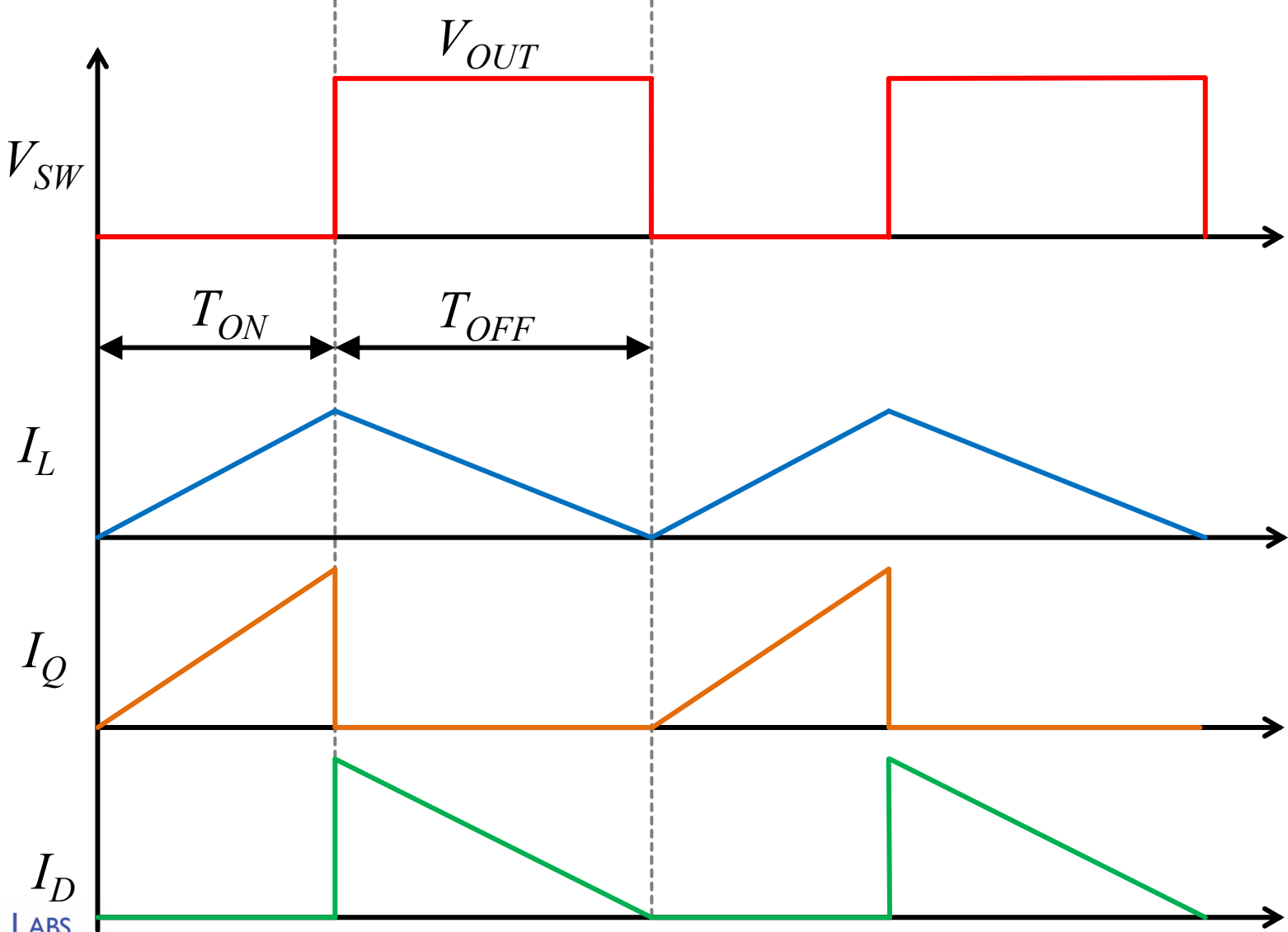


Critical Conduction Mode

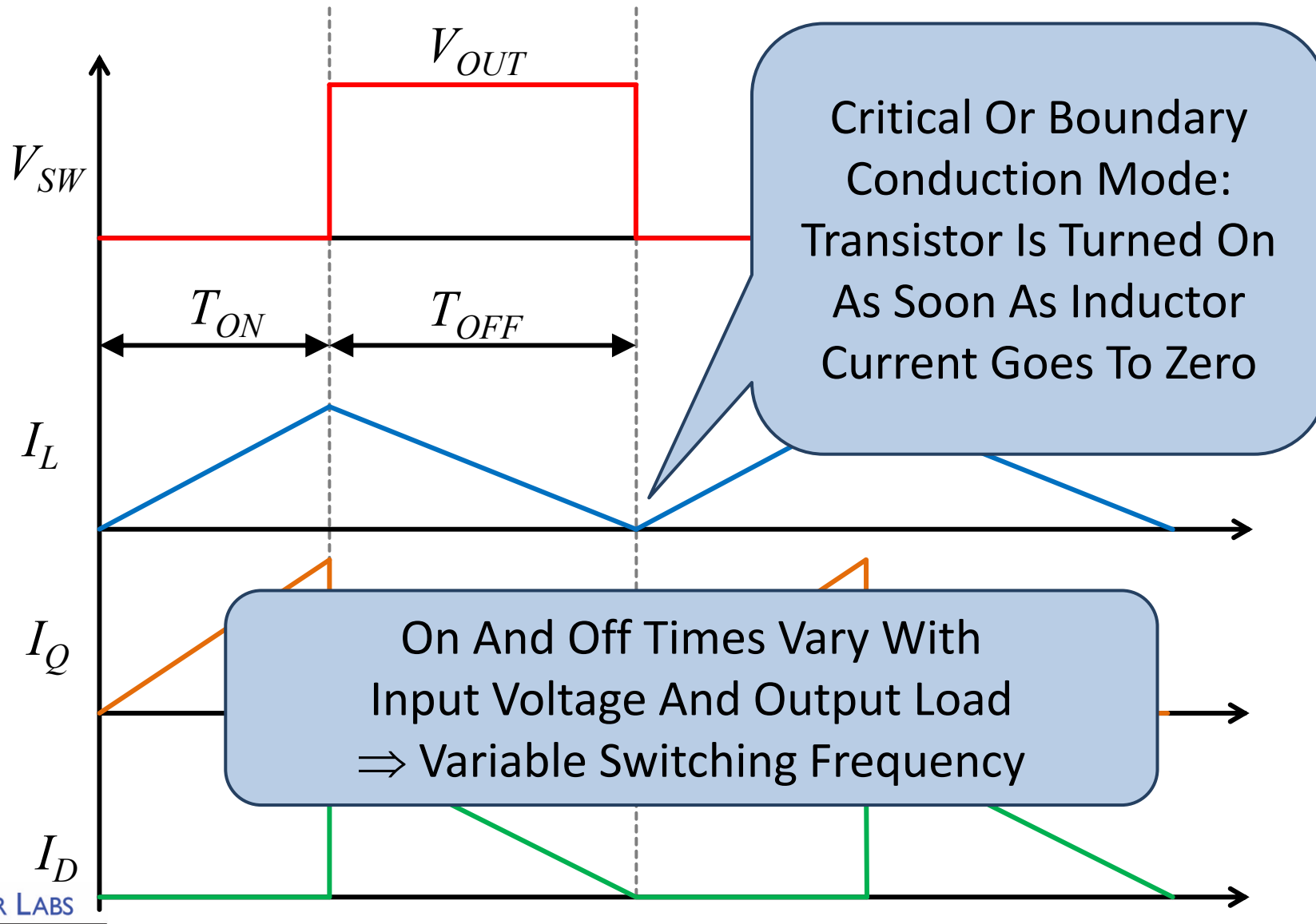

Critical Conduction Mode

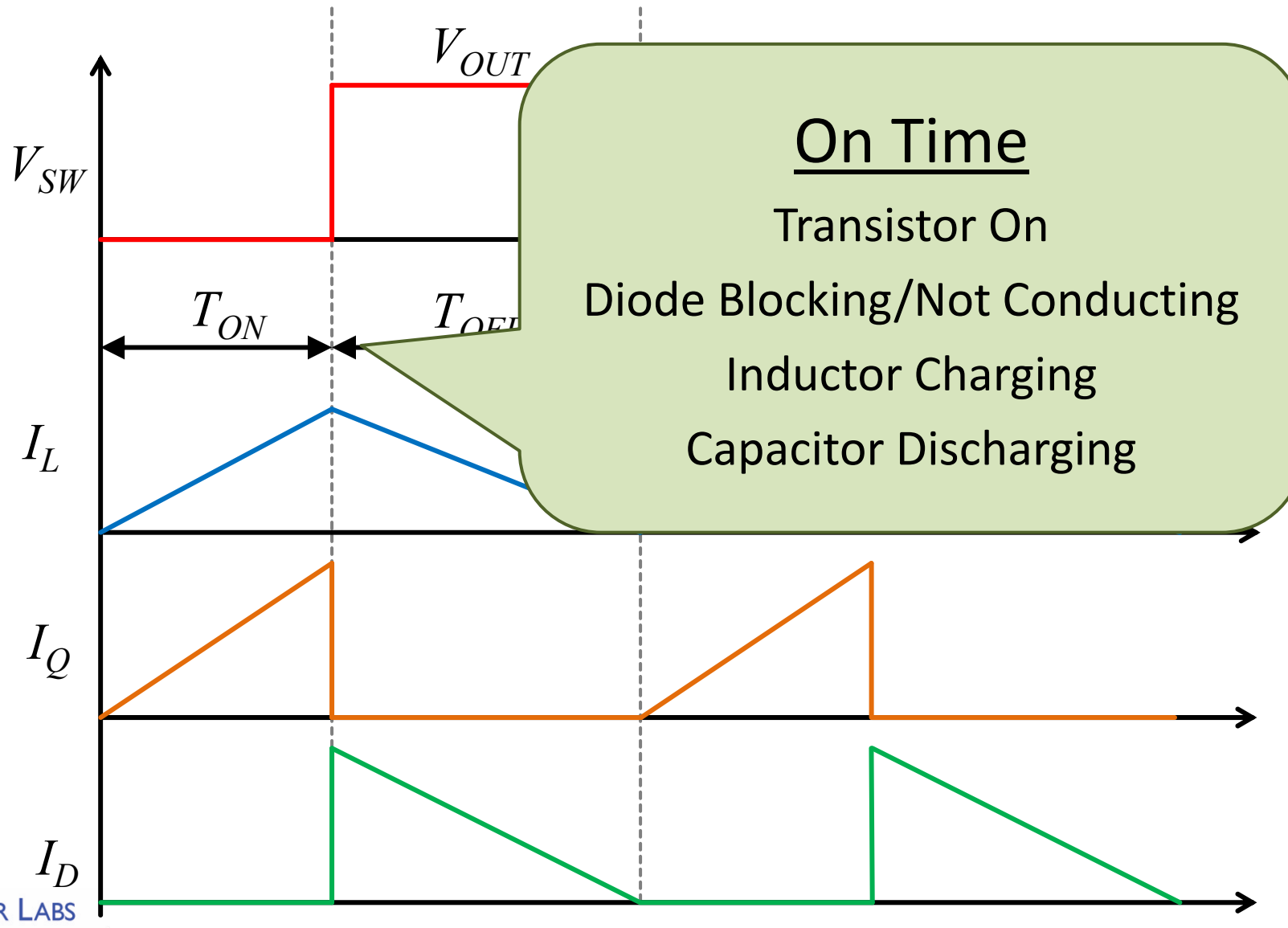

Critical Conduction Mode

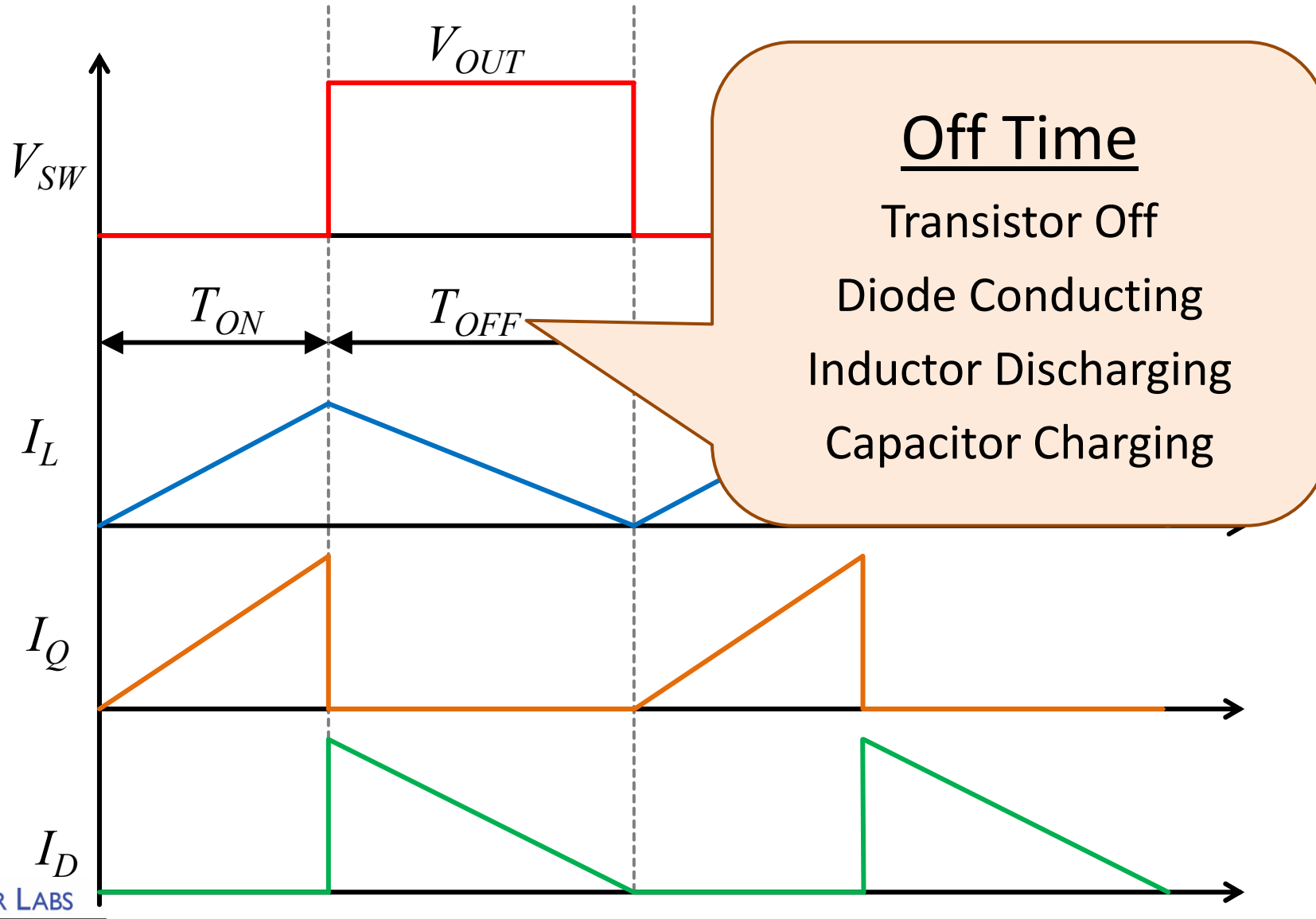

Boost Critical Conduction Mode

Advantages

- No Losses From Diode Reverse Recovery
- Smaller Peak Currents Than Discontinuous Mode

Disadvantages


- Specialized Controller
- Variable Frequency Operation
- Large Output Capacitor

This Mode Of Operation Is Popular When A Boost Converter Is Used To Make An Active Rectifier (Power Factor Correction, PFC) In An AC-DC Power Supply Because The Lack Of Diode Reverse Recovery Improves Efficiency

APPENDIX V.


Non-Ideal Boost Converter

Non-Ideal Boost Converter

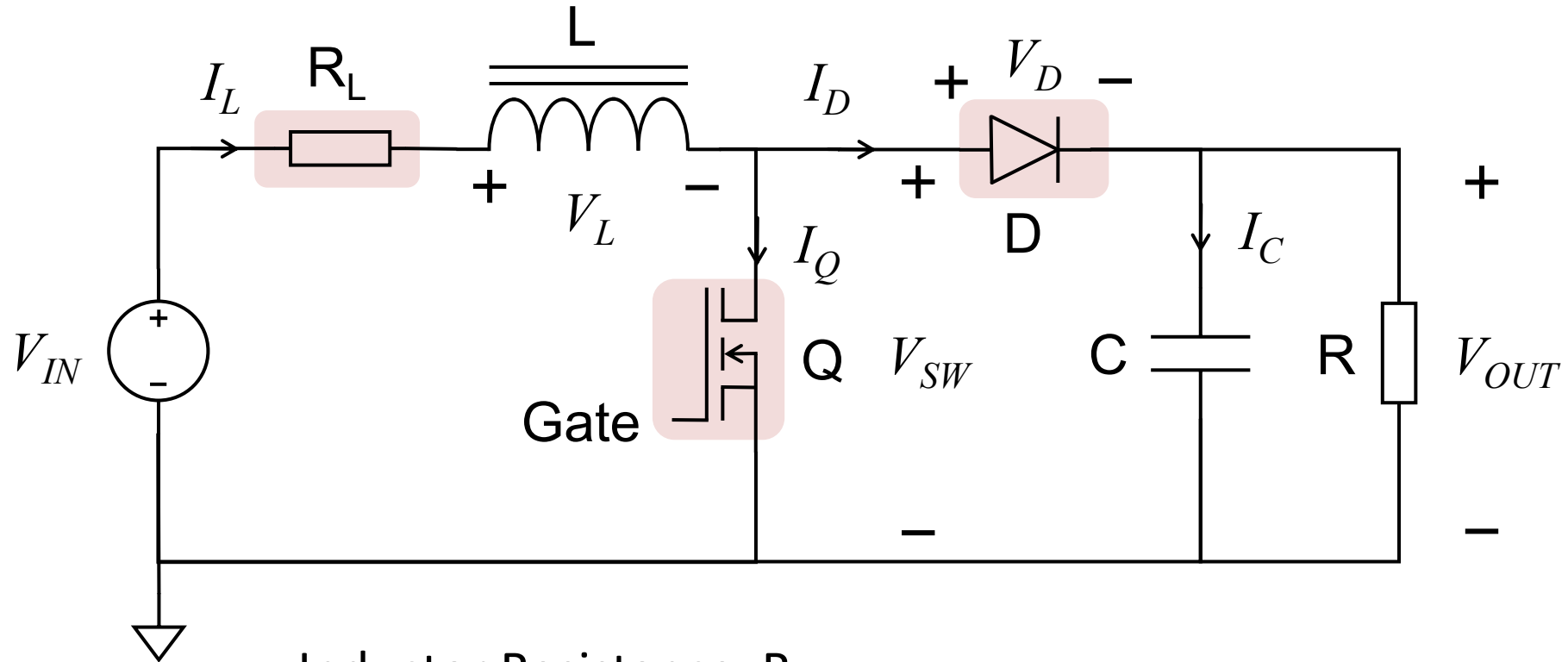

Inductor Resistance, R_L
Transistor On-Resistance, R_Q
Diode Forward Voltage, V_D

Non-Ideal Boost Converter

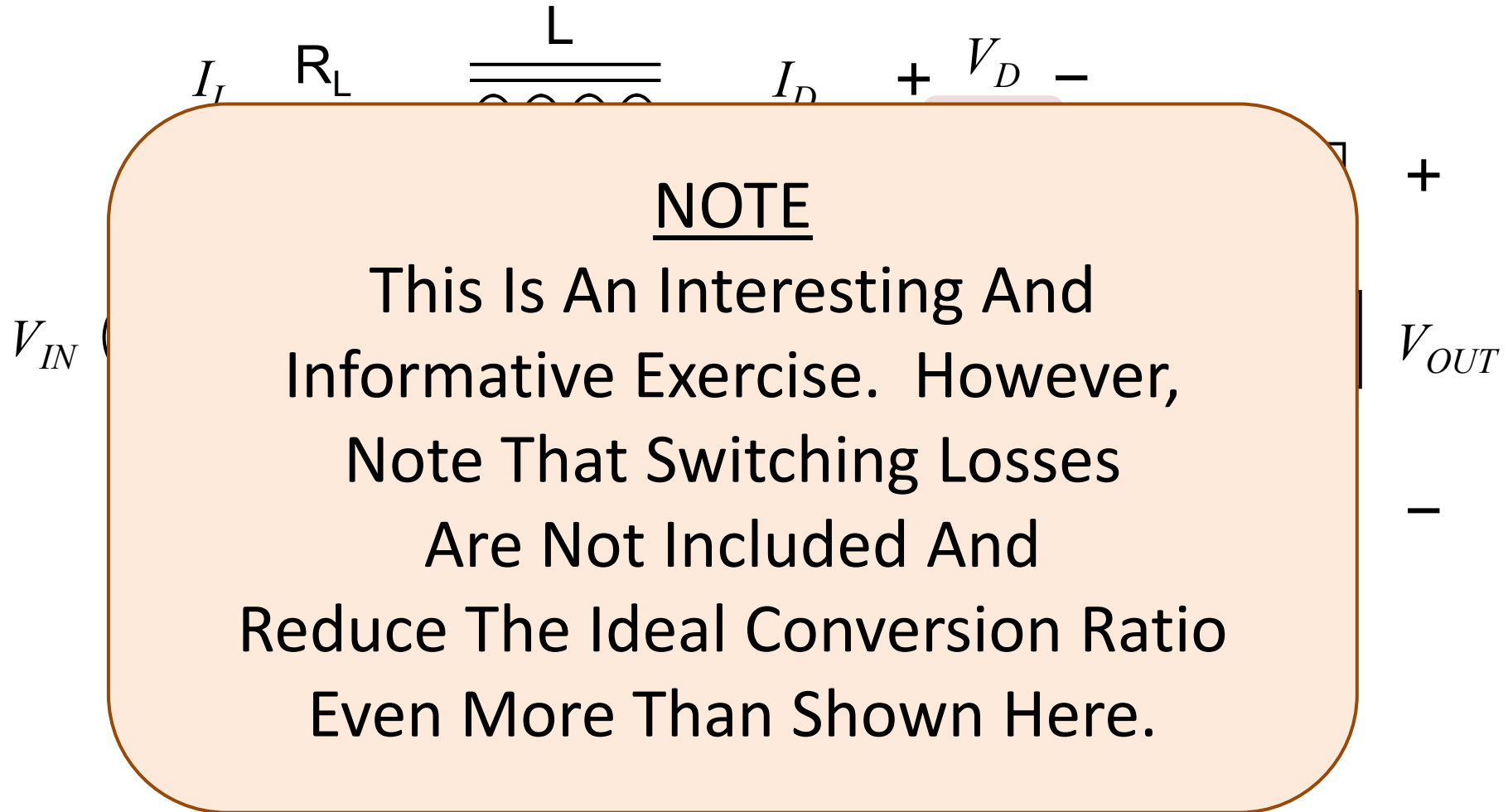

Boost Converter Input Current

$$I_C(T_{ON}) \cdot T_{ON} + I_C(T_{OFF}) \cdot T_{OFF} = 0$$

$$I_C(T_{ON}) = -\frac{V_{OUT}}{R}$$

$$I_C(T_{OFF}) = I_L - \frac{V_{OUT}}{R}$$

$$\left(-\frac{V_{OUT}}{R}\right) \cdot T_{ON} + \left(I_L - \frac{V_{OUT}}{R}\right) \cdot T_{OFF} = 0$$

$$\left(-\frac{V_{OUT}}{R}\right) \cdot D \cdot T_{SW} + \left(I_L - \frac{V_{OUT}}{R}\right) \cdot (1-D) \cdot T_{SW} = 0$$

$$\left(-\frac{V_{OUT}}{R}\right) \cdot D + \left(I_L - \frac{V_{OUT}}{R}\right) \cdot (1-D) = 0$$

$$-D \cdot \frac{V_{OUT}}{R} + I_L - D \cdot I_L - \frac{V_{OUT}}{R} + D \cdot \frac{V_{OUT}}{R} = 0$$

$$I_L - D \cdot I_L - \frac{V_{OUT}}{R} = 0$$

$$(1-D) \cdot I_L = \frac{V_{OUT}}{R}$$

$$I_L = I_{IN} = \frac{1}{1-D} \cdot \frac{V_{OUT}}{R}$$



$$D \rightarrow 1 \Rightarrow I_{IN} \rightarrow \infty$$

Inductor Voltages

$$V_L(T_{ON}) = V_{IN} - R_L \cdot I_L - R_Q \cdot I_L$$

$$V_L(T_{OFF}) = V_{IN} - R_L \cdot I_L - V_D - V_{OUT}$$

Both Expressions Use The Inductor Current. We Use The Expression For The Inductor Current We Just Derived

$$I_L = \frac{1}{D'} \cdot \frac{V_{OUT}}{R}$$

Inductor Volt-Second Balance

$$\begin{aligned}V_L(T_{ON}) &= V_{IN} - R_L \cdot \frac{1}{D'} \cdot \frac{V_{OUT}}{R} - R_Q \cdot \frac{1}{D'} \cdot \frac{V_{OUT}}{R} \\ &= V_{IN} - \frac{(R_L + R_Q)}{D'} \cdot \frac{V_{OUT}}{R}\end{aligned}$$

$$\begin{aligned}V_L(T_{OFF}) &= V_{IN} - R_L \cdot \frac{1}{D'} \cdot \frac{V_{OUT}}{R} - V_D - V_{OUT} \\ &= V_{IN} - V_D - V_{OUT} - R_L \cdot \frac{1}{D'} \cdot \frac{V_{OUT}}{R} \\ &= V_{IN} - V_D - V_{OUT} \cdot \left(1 + R_L \cdot \frac{1}{D'} \cdot \frac{1}{R}\right) \\ &= V_{IN} - V_D - V_{OUT} \cdot \left(1 + \frac{1}{D'} \cdot \frac{R_L}{R}\right) \\ &= V_{IN} - V_D - \frac{V_{OUT}}{R} \cdot \left(\frac{D' \cdot R + R_L}{D'}\right)\end{aligned}$$

$$\begin{aligned}0 &= V_L(T_{ON}) \cdot T_{ON} + V_L(T_{OFF}) \cdot T_{OFF} \\ &= V_L(T_{ON}) \cdot D + V_L(T_{OFF}) \cdot D' \\ &= \left(V_{IN} - \frac{(R_L + R_Q)}{D'} \cdot \frac{V_{OUT}}{R} \right) \cdot D \\ &\quad + \left(V_{IN} - V_D - \frac{V_{OUT}}{R} \cdot \left(\frac{D' \cdot R + R_L}{D'} \right) \right) \cdot D' \\ &= D \cdot V_{IN} - D \cdot \frac{(R_L + R_Q)}{D'} \cdot \frac{V_{OUT}}{R} \\ &\quad + D' \cdot V_{IN} - D' \cdot V_D - D' \cdot \frac{V_{OUT}}{R} \cdot \left(\frac{D' \cdot R + R_L}{D'} \right)\end{aligned}$$

Inductor Volt-Second Balance

$$\begin{aligned}
 0 &= D \cdot V_{IN} + D' \cdot V_{IN} - D' \cdot V_D \\
 &\quad - D \cdot \left(\frac{R_L + R_Q}{D'} \right) \cdot \frac{V_{OUT}}{R} - D' \cdot \left(\frac{D' \cdot R + R_L}{D'} \right) \cdot \frac{V_{OUT}}{R} \\
 &= (D + D') V_{IN} - D' \cdot V_D \\
 &\quad - D \cdot \left(\frac{R_L + R_Q}{D'} \right) \cdot \frac{V_{OUT}}{R} - (D' \cdot R + R_L) \cdot \frac{V_{OUT}}{R} \\
 &= V_{IN} - D' \cdot V_D \\
 &\quad - \frac{D}{D'} \cdot R_L \cdot \frac{V_{OUT}}{R} - R_L \cdot \frac{V_{OUT}}{R} - \frac{D}{D'} \cdot R_Q \cdot \frac{V_{OUT}}{R} - D' \cdot R \cdot \frac{V_{OUT}}{R}
 \end{aligned}$$


$$\begin{aligned}
 0 &= V_{IN} - D' \cdot V_D \\
 &\quad - \left(1 + \frac{D}{D'} \right) R_L \cdot \frac{V_{OUT}}{R} - \frac{D}{D'} \cdot R_Q \cdot \frac{V_{OUT}}{R} - D' \cdot V_{OUT} \\
 &= V_{IN} - D' \cdot V_D \\
 &\quad - \left(\frac{1-D}{D'} + \frac{D}{D'} \right) R_L \cdot \frac{V_{OUT}}{R} - \frac{D}{D'} \cdot R_Q \cdot \frac{V_{OUT}}{R} - D' \cdot V_{OUT} \\
 &= V_{IN} - D' \cdot V_D \\
 &\quad - \frac{1}{D'} R_L \cdot \frac{V_{OUT}}{R} - \frac{D}{D'} \cdot R_Q \cdot \frac{V_{OUT}}{R} - D' \cdot V_{OUT} \\
 &= V_{IN} - D' \cdot V_D \\
 &\quad - \left(\frac{1}{D'} R_L \cdot \frac{1}{R} + \frac{D}{D'} \cdot R_Q \cdot \frac{1}{R} + D' \right) \cdot V_{OUT}
 \end{aligned}$$

Non-Ideal Conversion Ratio

$$\left(D' + \frac{1}{D'} \frac{R_L}{R} + \frac{D}{D'} \cdot \frac{R_Q}{R} \right) \cdot V_{OUT} = V_{IN} - D' \cdot V_D$$

$$\begin{aligned} V_{OUT} &= \frac{V_{IN} - D' \cdot V_D}{D' + \frac{1}{D'} \frac{R_L}{R} + \frac{D}{D'} \cdot \frac{R_Q}{R}} \\ &= \frac{V_{IN}}{D'} \cdot \frac{1 - D' \cdot \frac{V_D}{V_{IN}}}{1 + \frac{1}{D'^2} \cdot \frac{R_L}{R} + \frac{D}{D'^2} \frac{R_Q}{R}} \end{aligned}$$

Non-Ideal Conversion Ratio

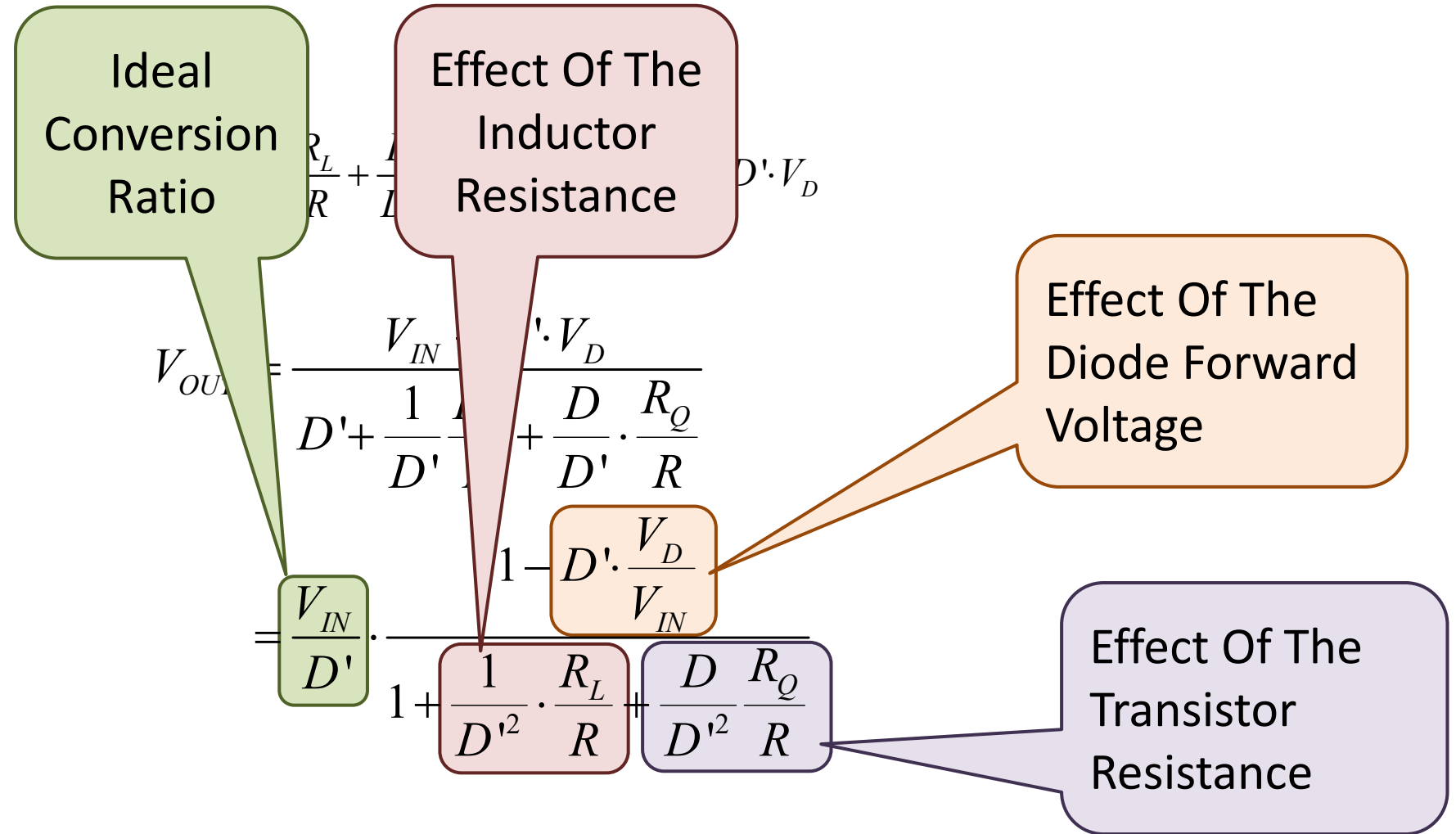

Non-Ideal Conversion Ratio

$$\left(D' + \frac{1}{D'} \frac{R_L}{R} + \frac{D}{D'} \cdot \frac{R_Q}{R} \right) \cdot V_{OUT} = V_{IN} - D' \cdot V_D$$


$$\begin{aligned} V_{OUT} &= \frac{V_{IN} - D' \cdot V_D}{D' + \frac{1}{D'} \frac{R_L}{R} + \frac{D}{D'} \cdot \frac{R_Q}{R}} \\ &= \frac{V_{IN}}{D'} \cdot \frac{1 - D' \cdot \frac{V_D}{V_{IN}}}{1 + \frac{1}{D'^2} \cdot \frac{R_L}{R} + \frac{D}{D'^2} \frac{R_Q}{R}} \end{aligned}$$

In This Form, It Is Easy To See That If:
 $V_D = 0$, $R_L = 0$,
And $R_Q = 0$,
We Get The Ideal Conversion Ratio

Example Calculation

- $V_{IN} = 3.3 \text{ V}$
- $R_{OUT} = 12 \Omega$
 - Nominally 12 V @ 1 A
- $R_L = 20 \text{ m}\Omega$
- $R_Q = 20 \text{ m}\Omega$
- $V_D = 0.4 \text{ V}$ (Schottky)


Conversion Ratio Plot

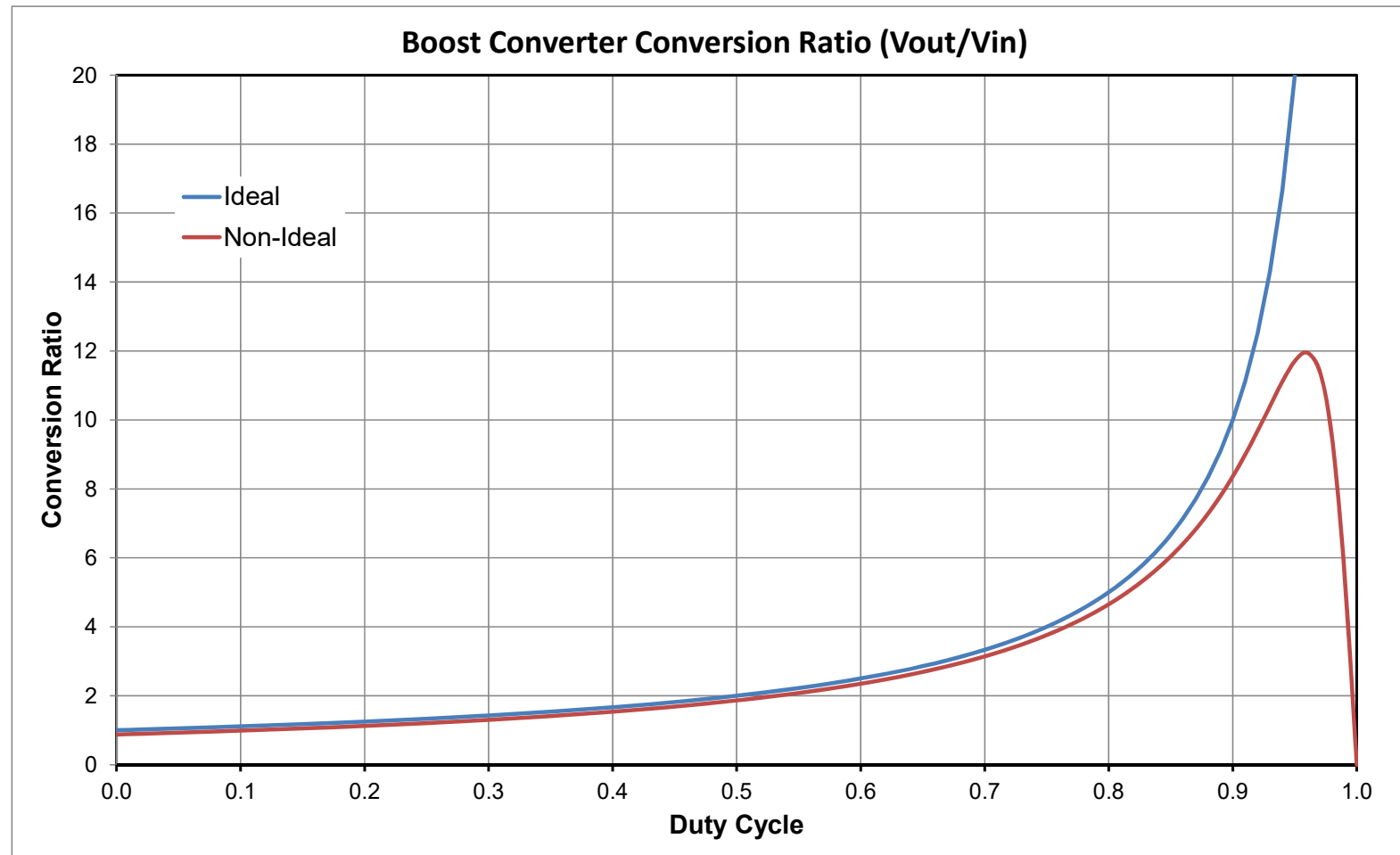

APPENDIX VI.

Buck-Boost Converter Analysis

Buck-Boost Converter

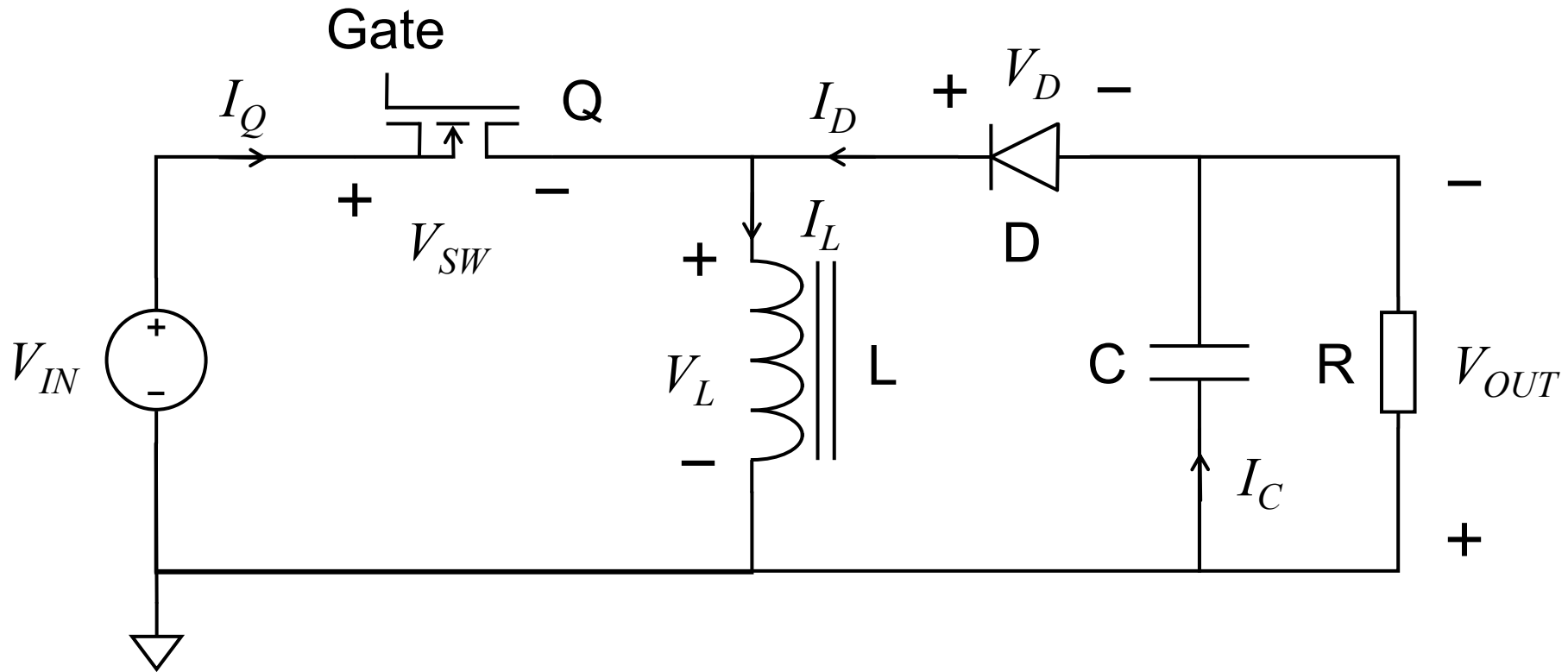

Conversion Ratio

$$V_L(T_{ON}) \cdot T_{ON} + V_L(T_{OFF}) \cdot T_{OFF} = 0$$


$$V_{IN} \cdot T_{ON} + V_{OUT} \cdot T_{OFF} = 0$$

$$D \cdot V_{IN} \cdot T_{SW} + V_{OUT} \cdot (1 - D) \cdot T_{SW} = 0$$

$$D \cdot V_{IN} + (1 - D) \cdot V_{OUT} = 0$$

$$(1 - D) \cdot V_{OUT} = -D \cdot V_{IN}$$
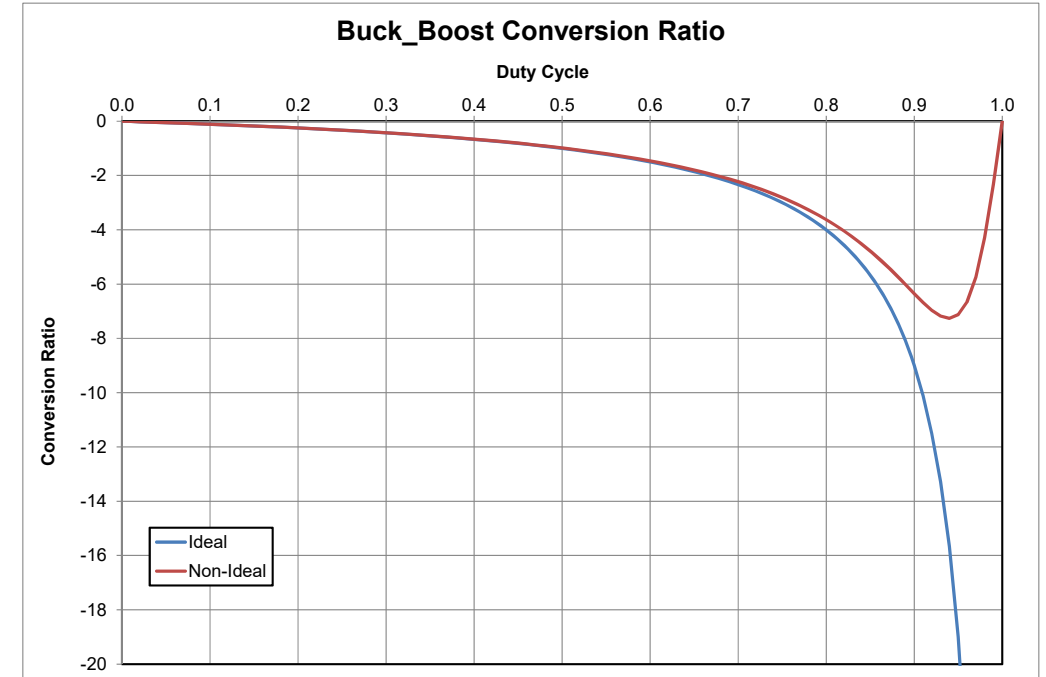
$$V_{OUT} = -\frac{D}{1 - D} \cdot V_{IN} = -\frac{D}{D'} \cdot V_{IN}$$



Conversion Ratio

$$V_L(T_{ON}) \cdot T_{ON} + V_L(T_{OFF}) \cdot T_{OFF} = 0$$

$$V_{IN} \cdot T_{ON} + V_{OUT} \cdot T_{OFF} = 0$$


$$D \cdot V_{IN} \cdot T_{SW} + V_{OUT} \cdot (1 - D) \cdot T_{SW} = 0$$

$$D \cdot V_{IN} + (1 - D) \cdot V_{OUT} = 0$$

$$(1 - D) \cdot V_{OUT} = -D \cdot V_{IN}$$

$$V_{OUT} = -\frac{D}{1 - D} \cdot V_{IN} = -\frac{D}{D'} \cdot V_{IN}$$

Buck-Boost Has The Same Loss Limiting On The Maximum Boost Ratio As The Boost Converter

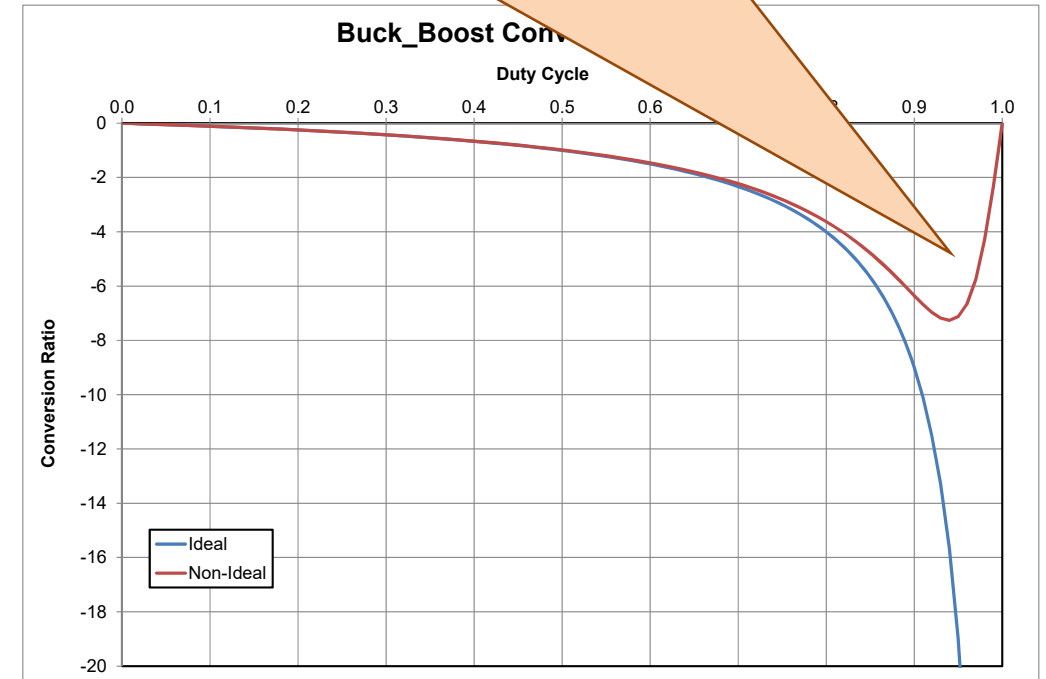


APPENDIX VII.

DCM Flyback Converter Deeper Dive


DCM Flyback Deeper Dive

- If You Are Going To Use The Flyback Converter, Important To Understand Effect Of:
 - Leakage Inductance
 - Stray Capacitances
- Leakage Inductance Effects:
 - Loss Of Efficiency
 - Needs A Clamp Circuit
 - Higher Switch Transistor Voltage Rating


Flyback Converter

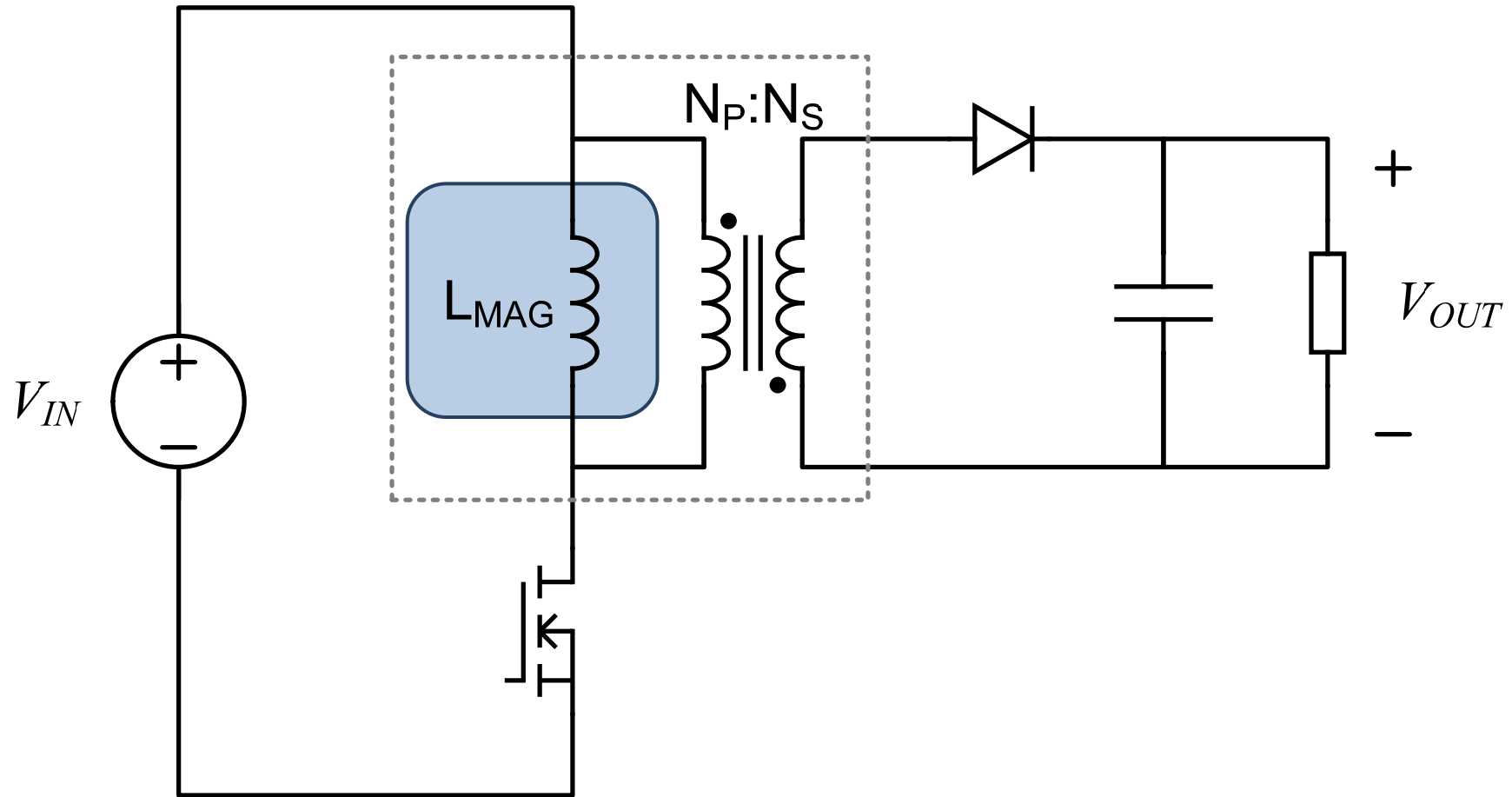

Leakage Inductance

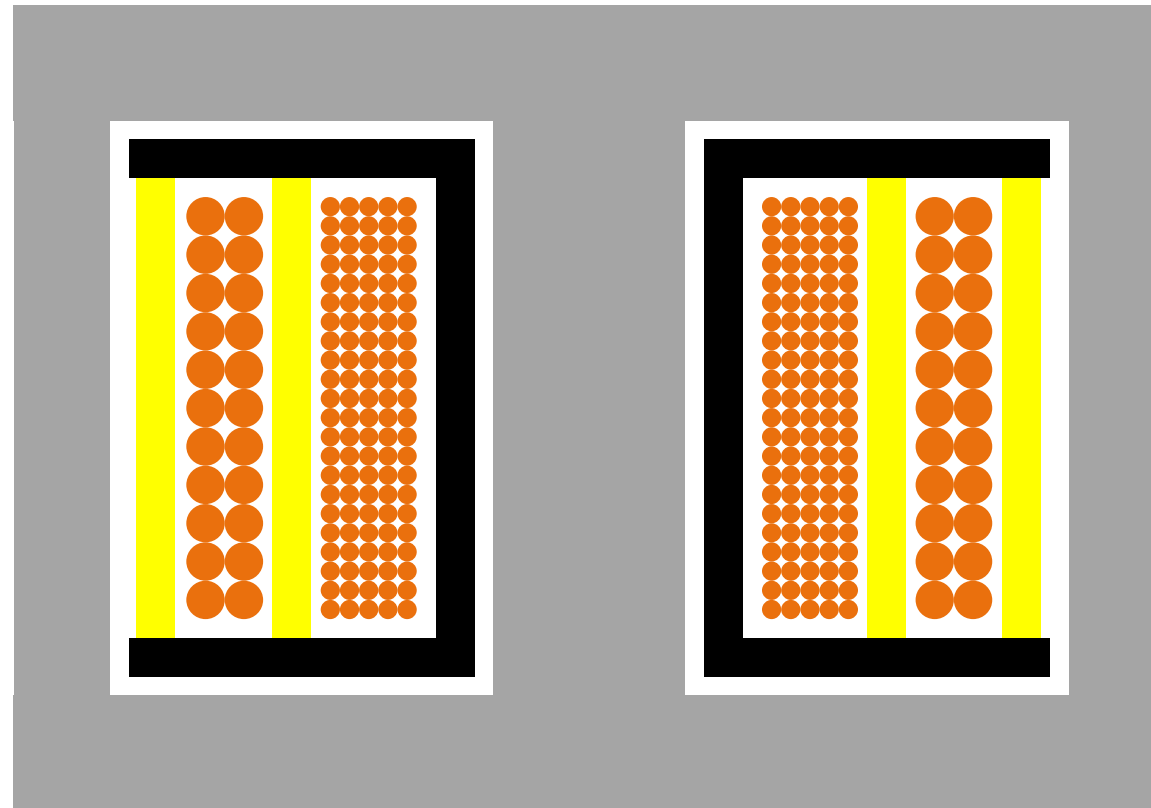


Leakage Inductance

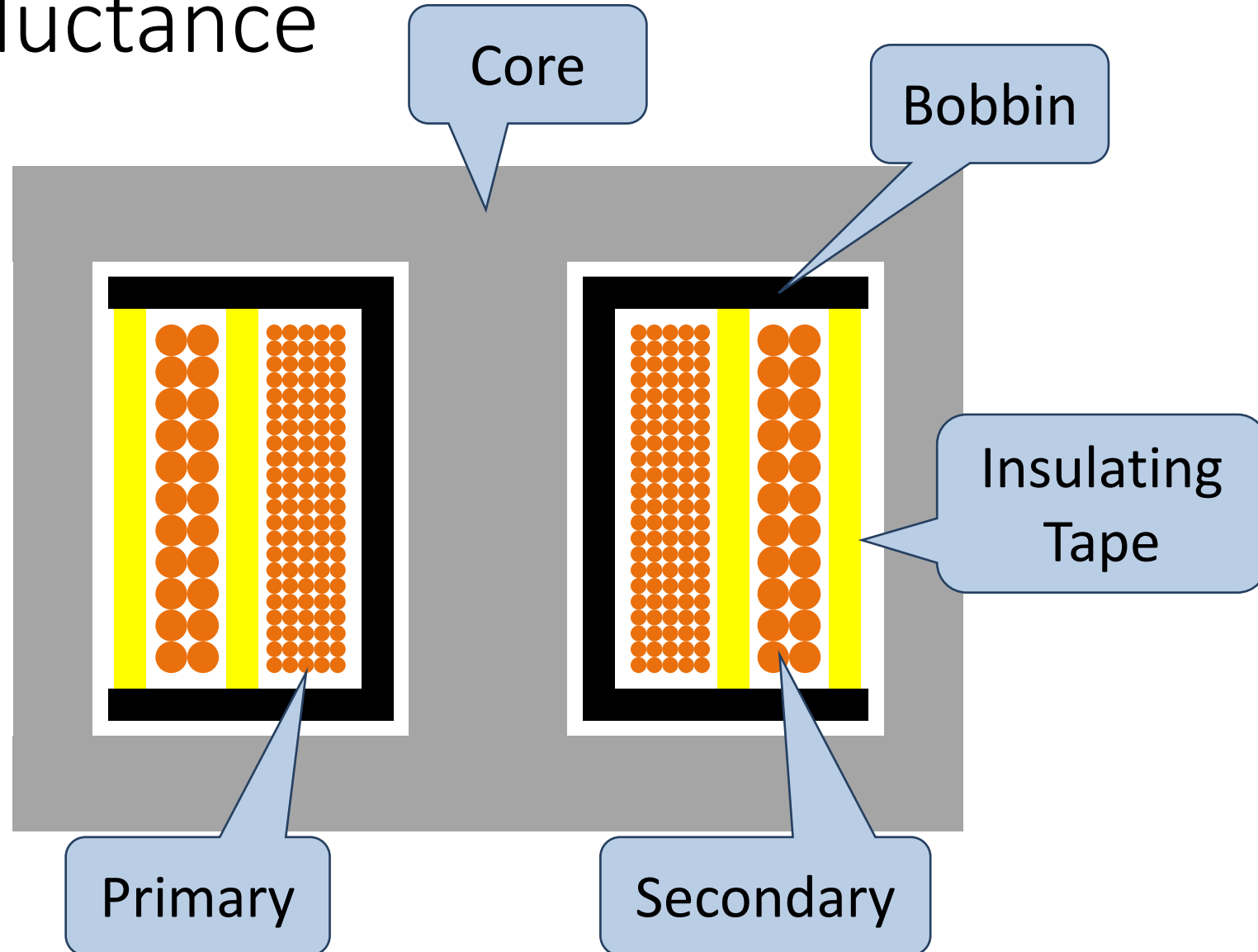


Leakage Inductance

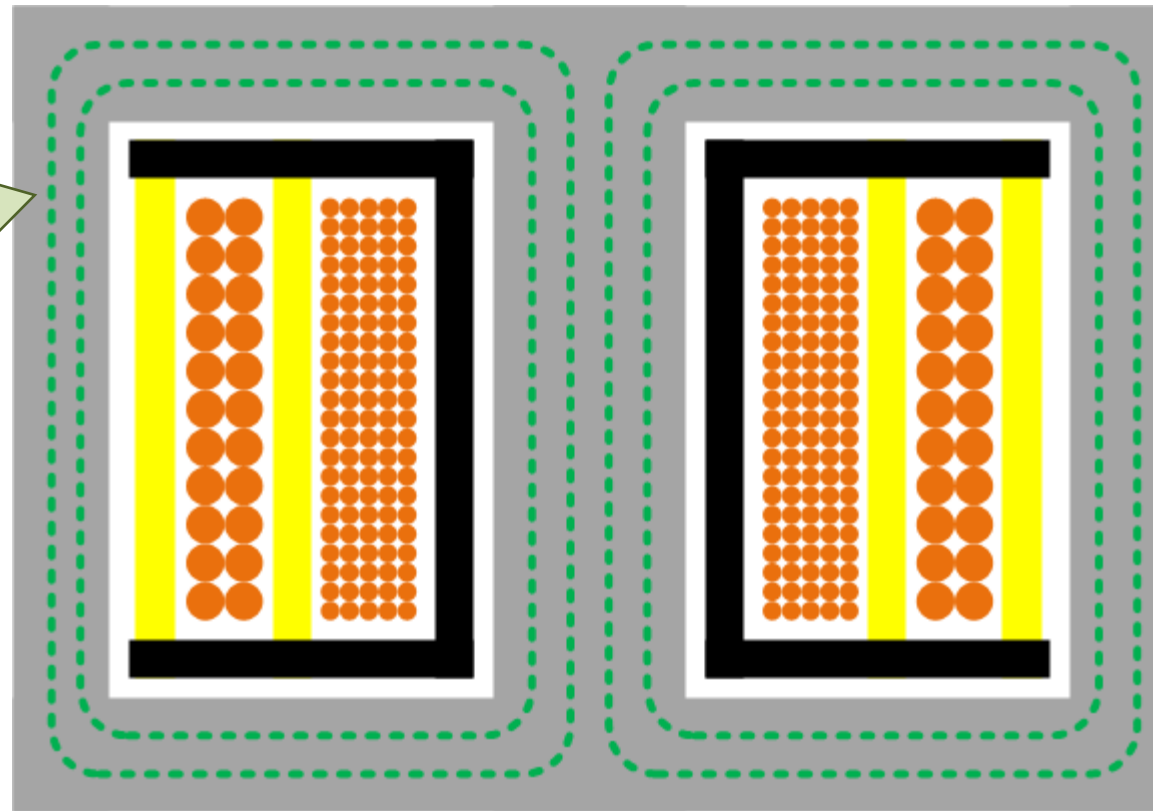Magnetic Flux In the Core Coupling Both Windings




Leakage Inductance

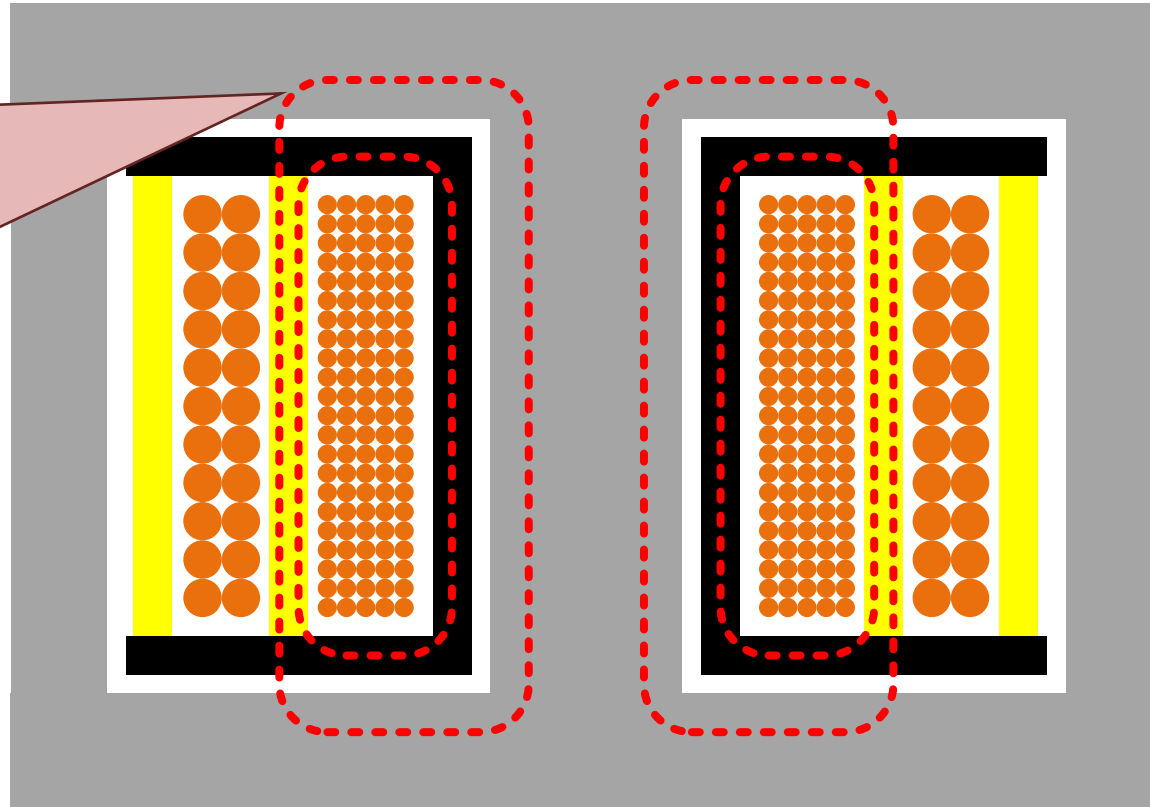Magnetic Flux In the Core Coupled Only To The Primary Winding




This “Leakage Flux” Results In The “Leakage Inductance”

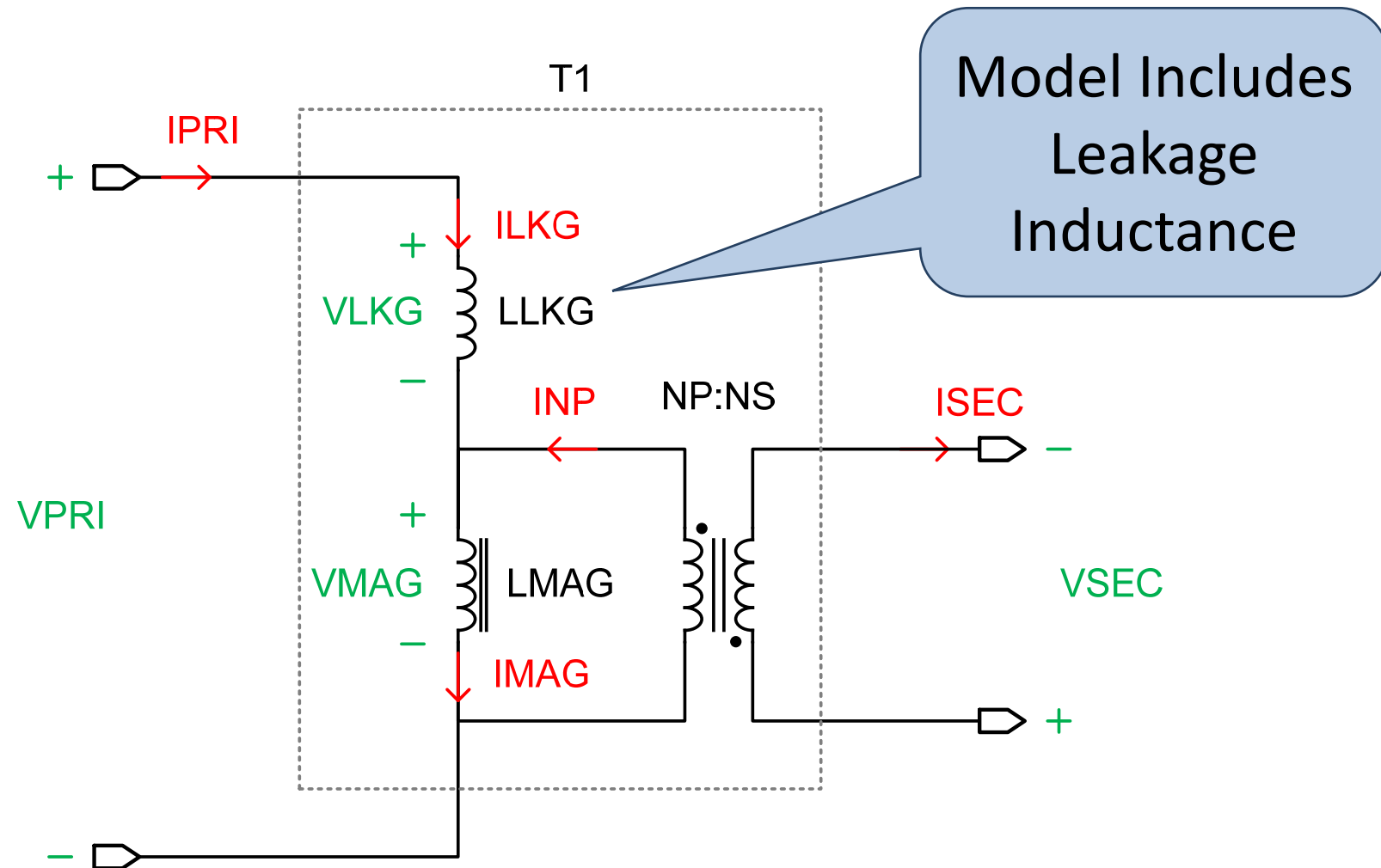
Transformer With Leakage Inductance Model



Flyback With Leakage Inductance

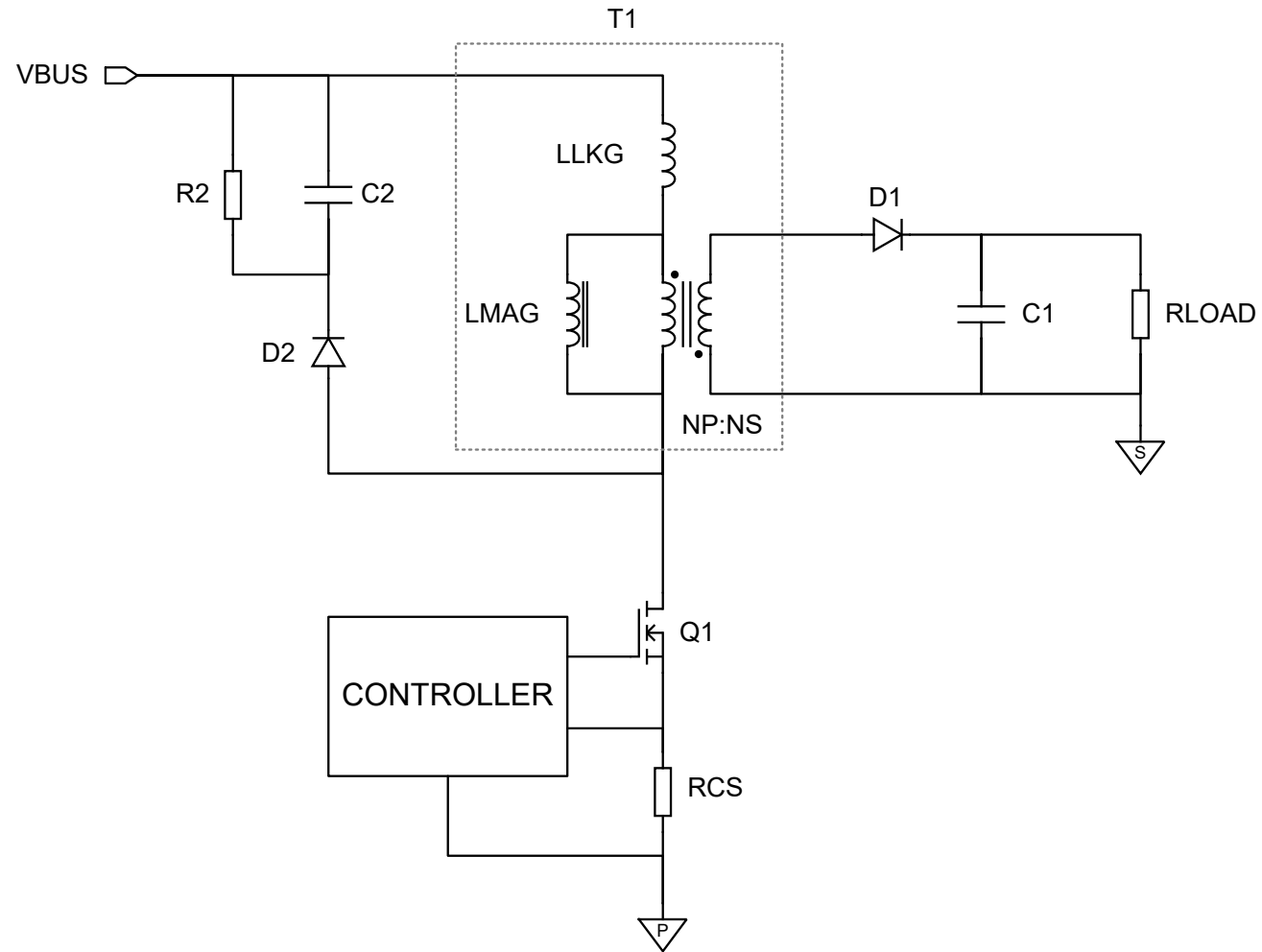


Flyback With Leakage Inductance

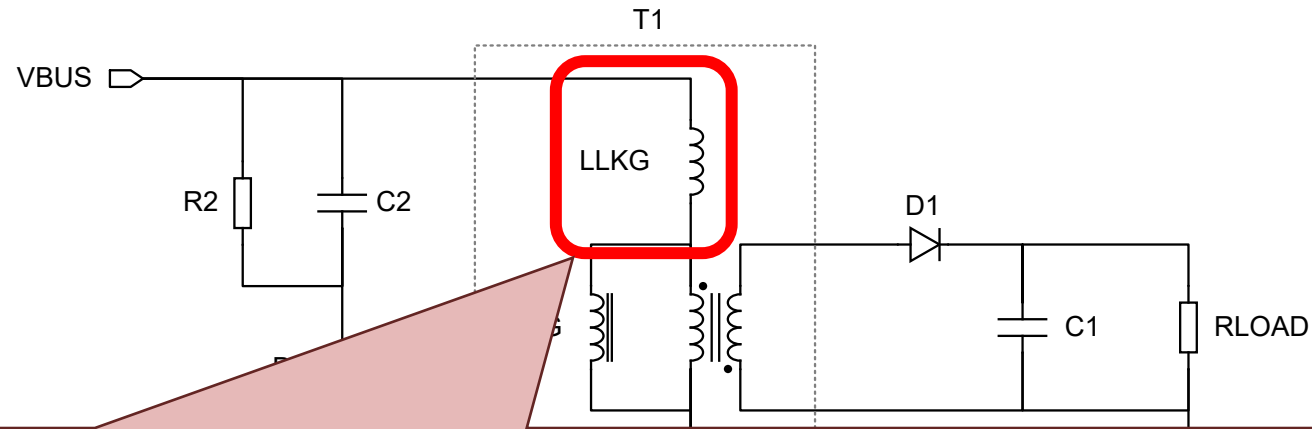


The Leakage Inductance Causes Many Problems In A Flyback Converter Including:

- Significant Loss Of Power/Efficiency
- Need For Clamping Circuit To Absorb The Energy Stored In The Leakage Inductance
- Much Higher Peak Voltage On Switching Transistor

Basic Flyback Circuit With RCD Clamp

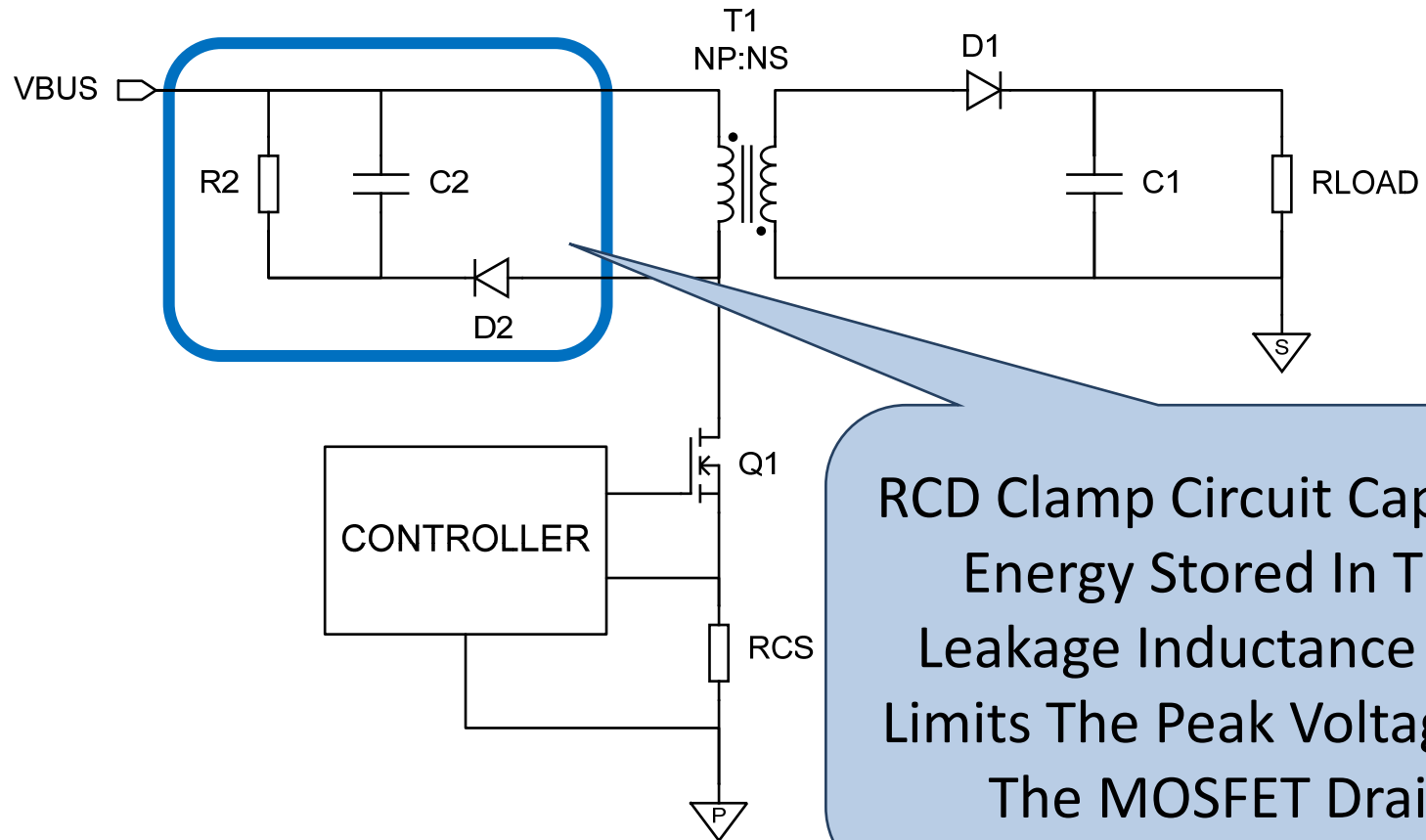


Flyback With Leakage Inductance

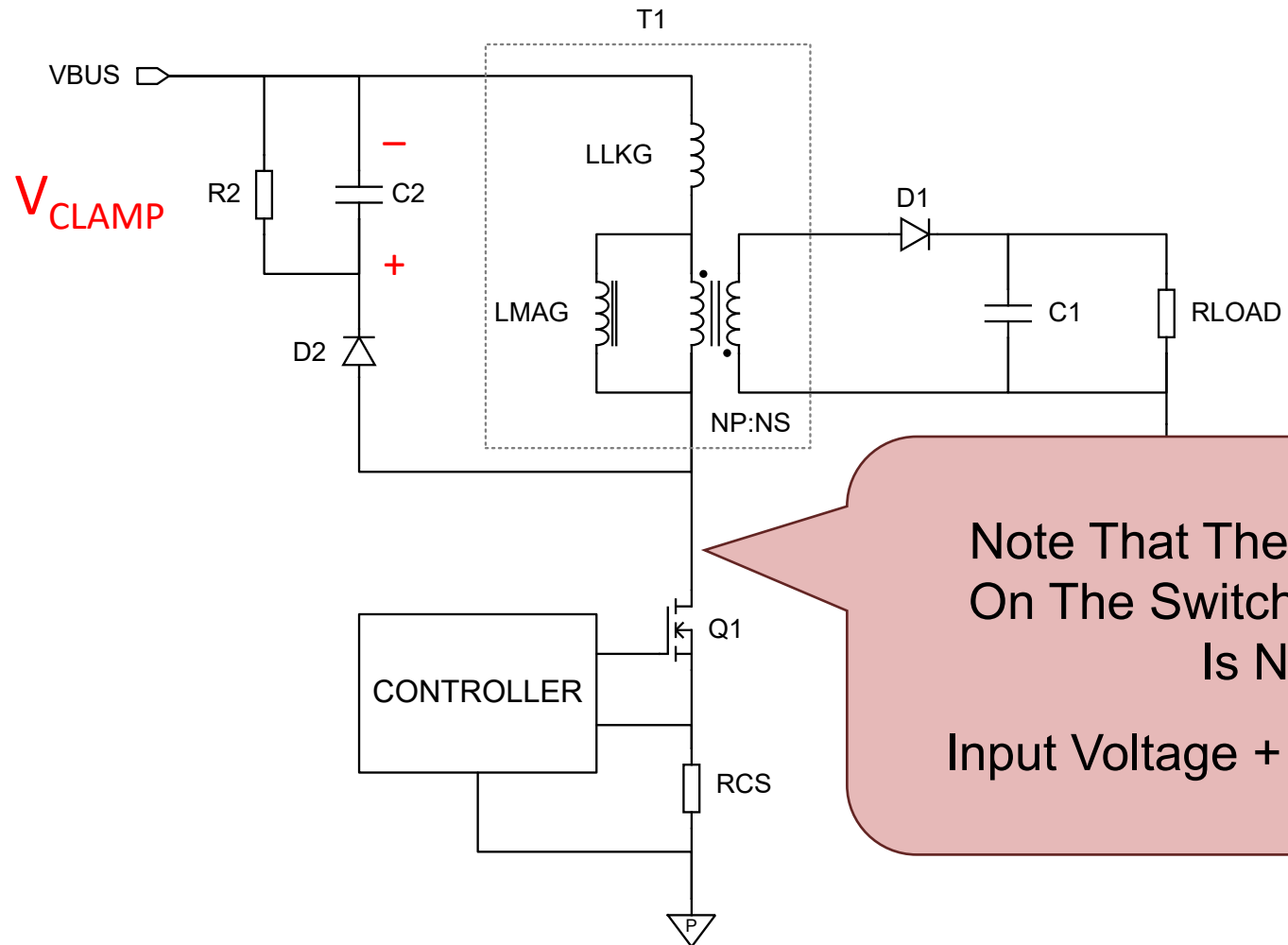


Note That The Peak Voltage
On The Switching Transistor
Is Now:
Input Voltage + Clamp Voltage

Flyback With Leakage Inductance

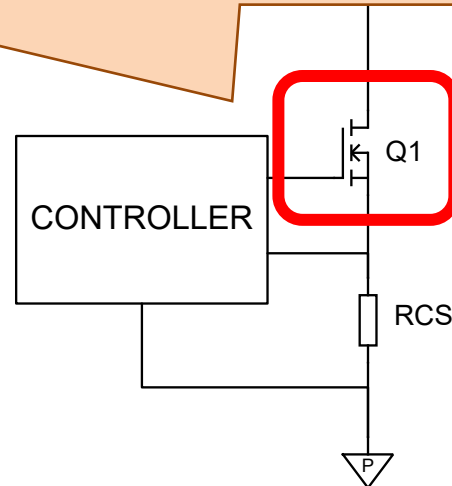Semiconductor Capacitances, Such As The Output Capacitance Of The Switching Transistor (C_{OSS}) And The Inter-Winding Capacitance Of The Flyback Inductor, Allow Significant Ringing With The Leakage And Magnetizing Inductance. This Can Be A Major Source Of EMI.




Flyback With Leakage Inductance

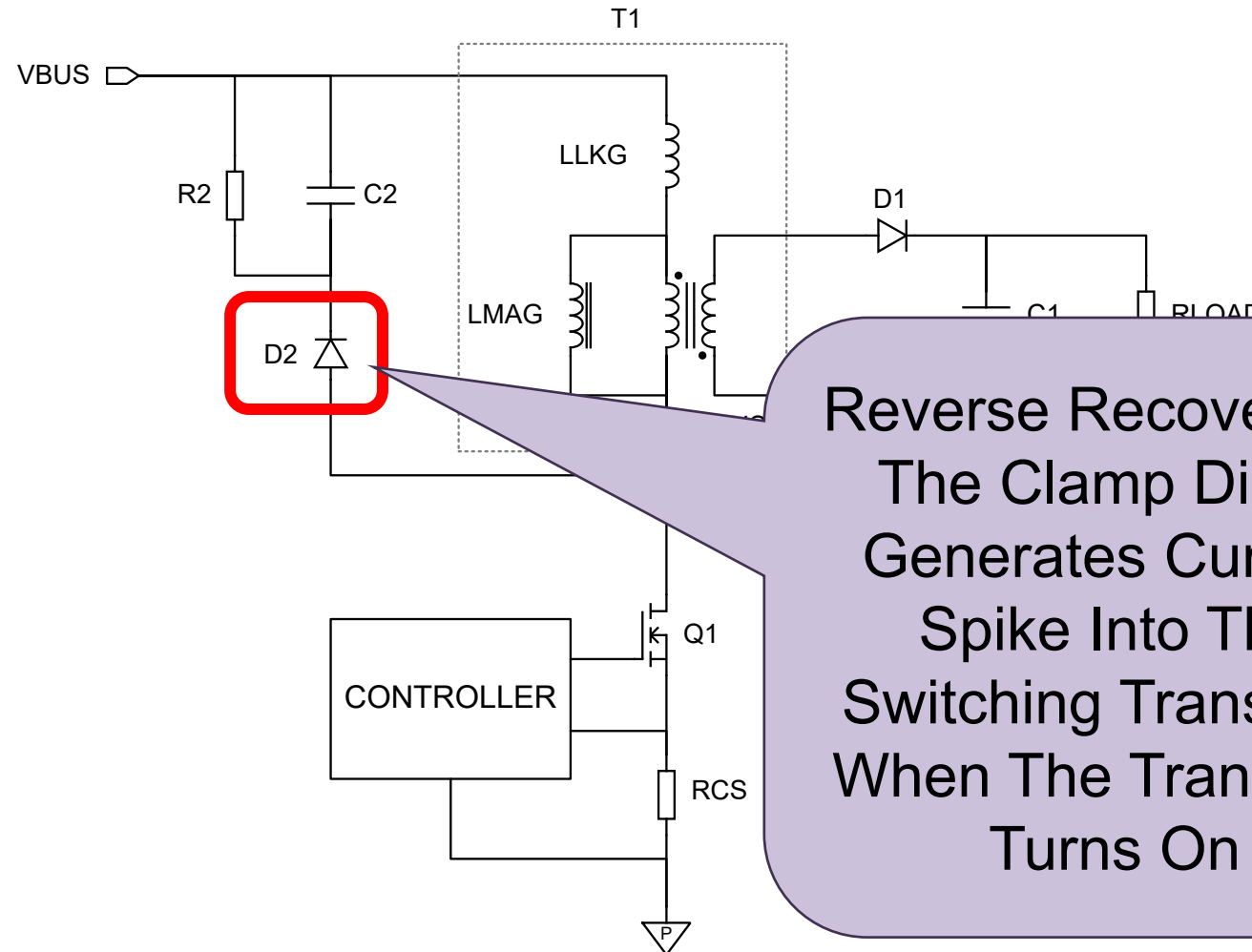


Reverse Recovery Of
The Clamp Diode
Generates Current
Spike Into The
Switching Transistor
When The Transistor
Turns On


Basic Flyback Circuit With RCD Clamp

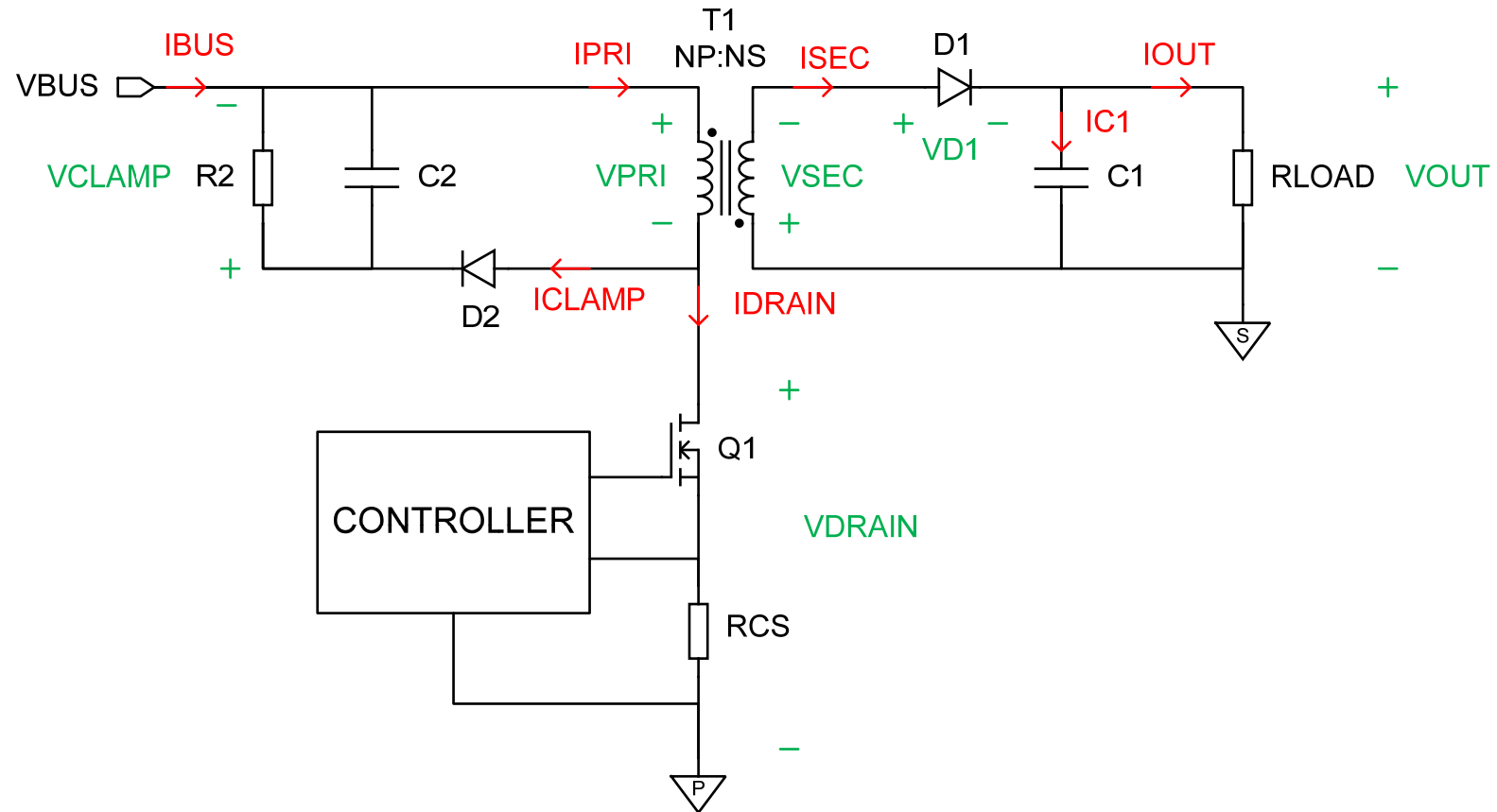


Flyback With Leakage Inductance

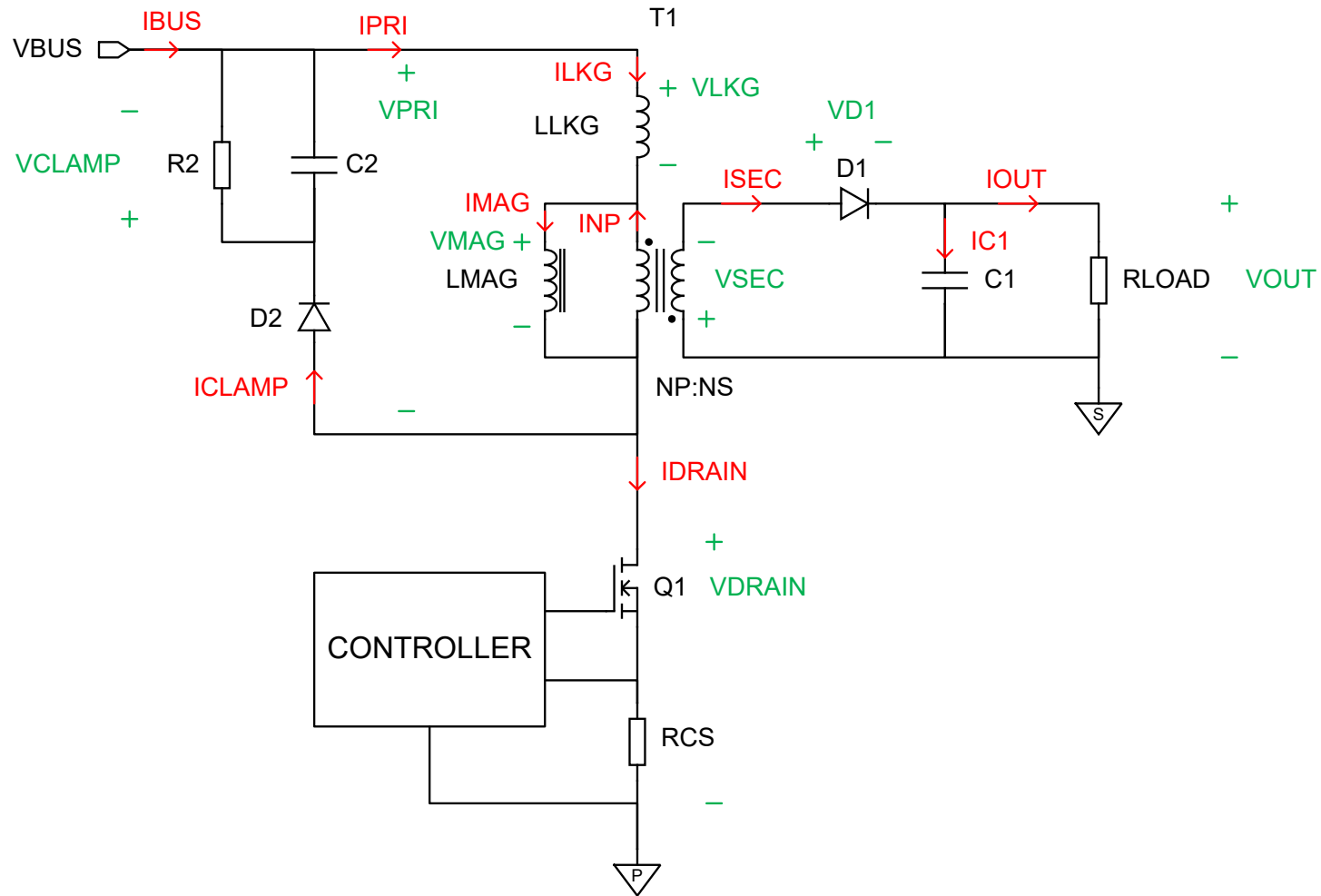


Discontinuous Conduction Mode

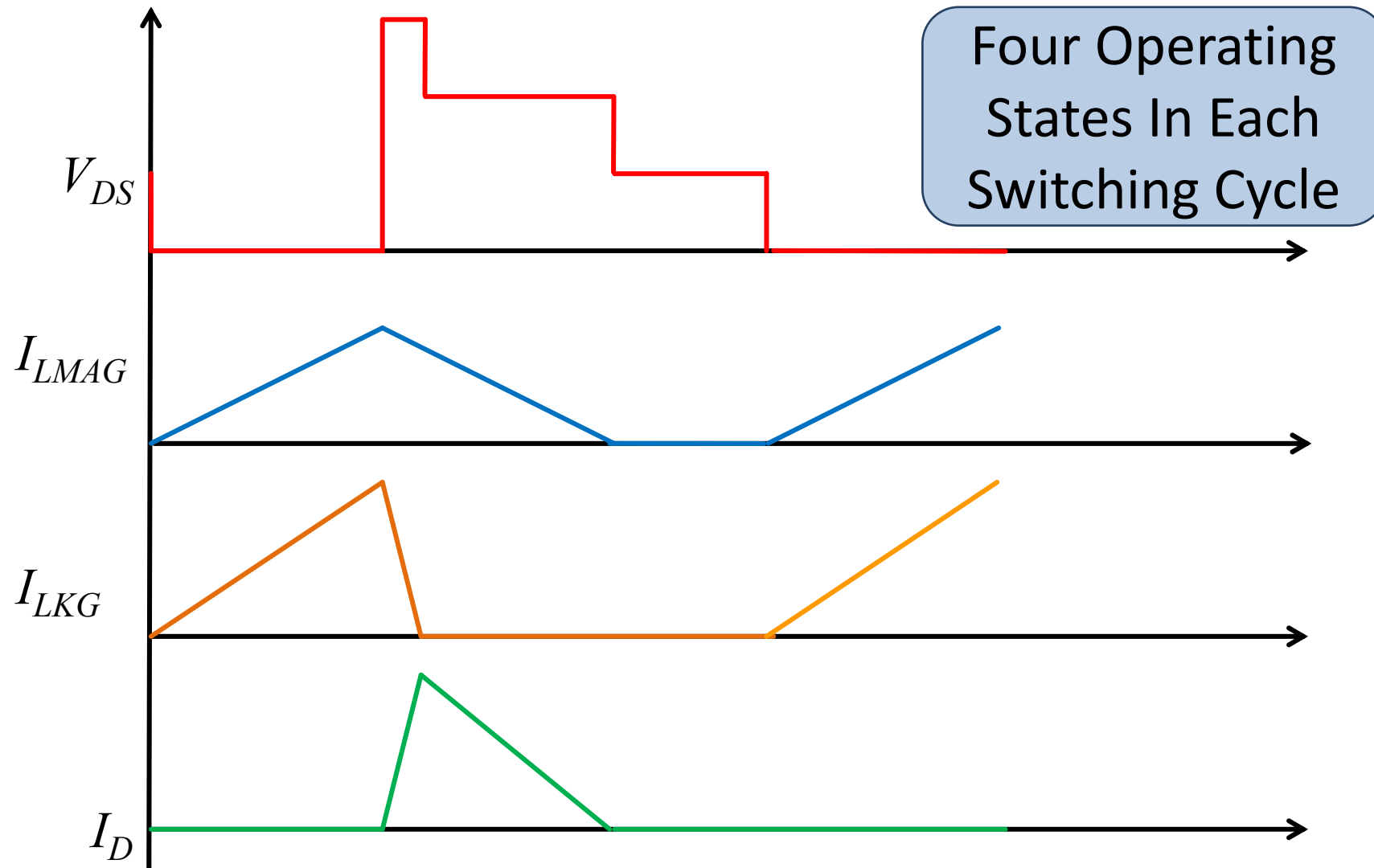


Discontinuous Conduction Mode

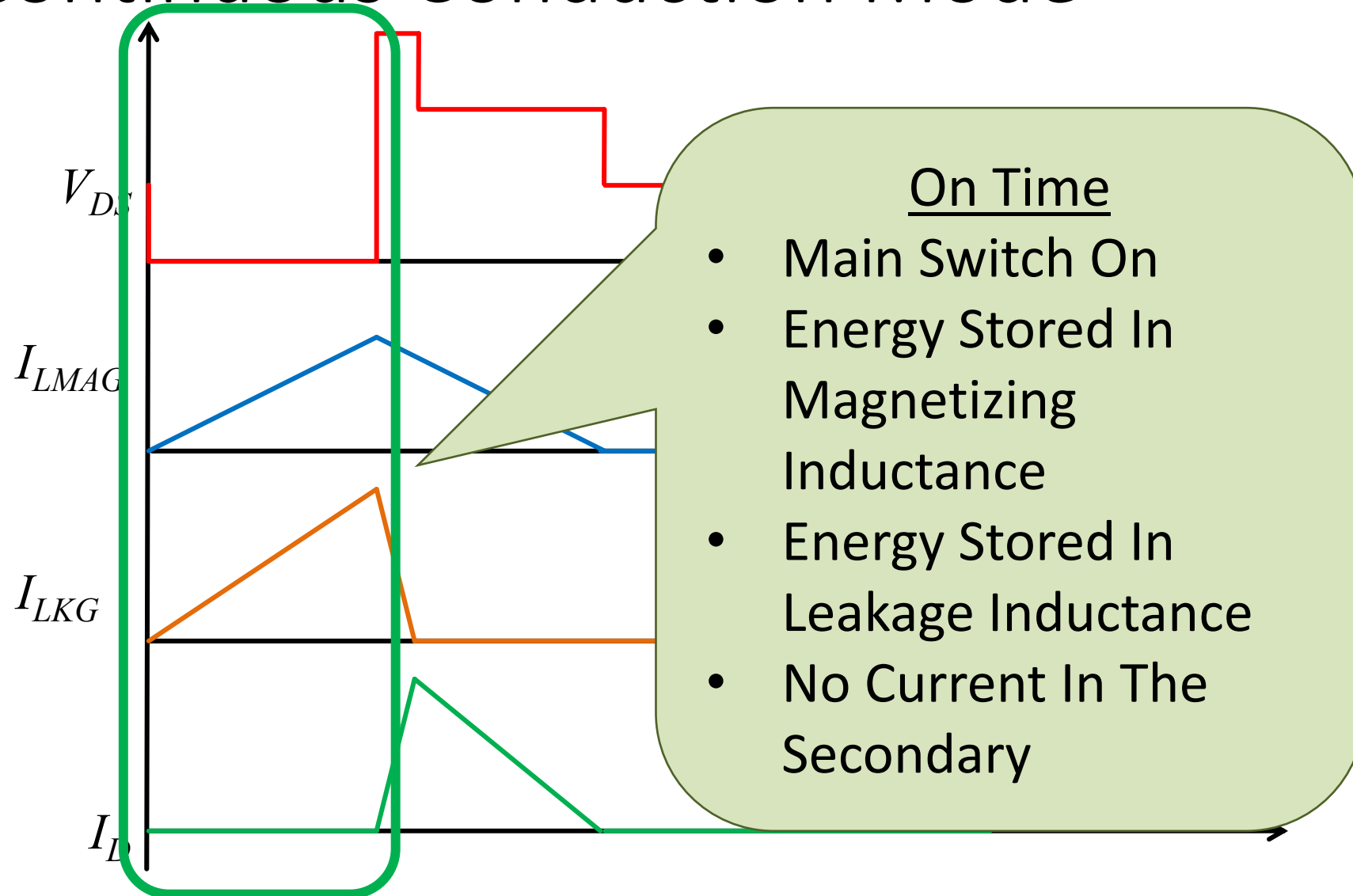


Discontinuous Conduction Mode

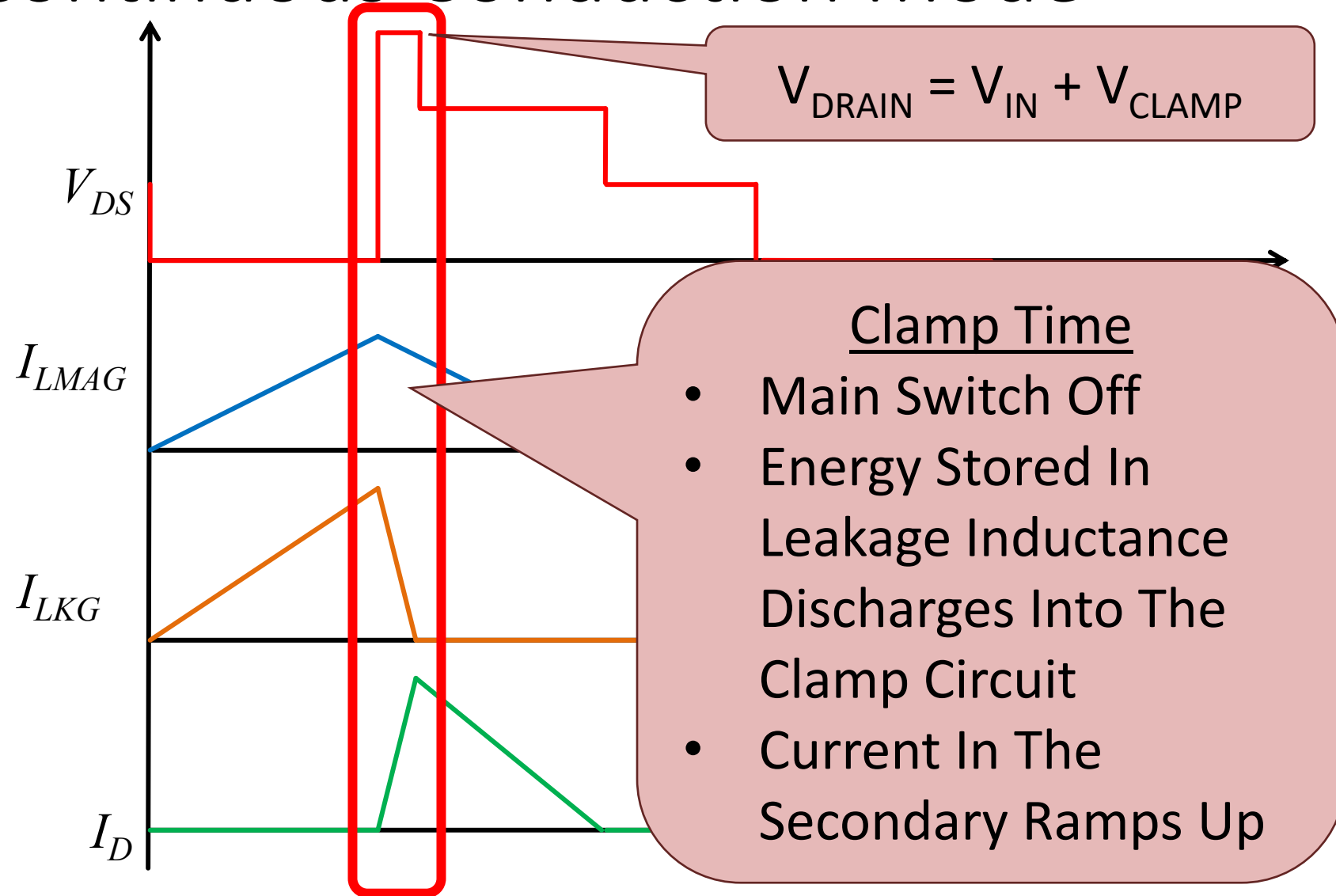


Discontinuous Conduction Mode

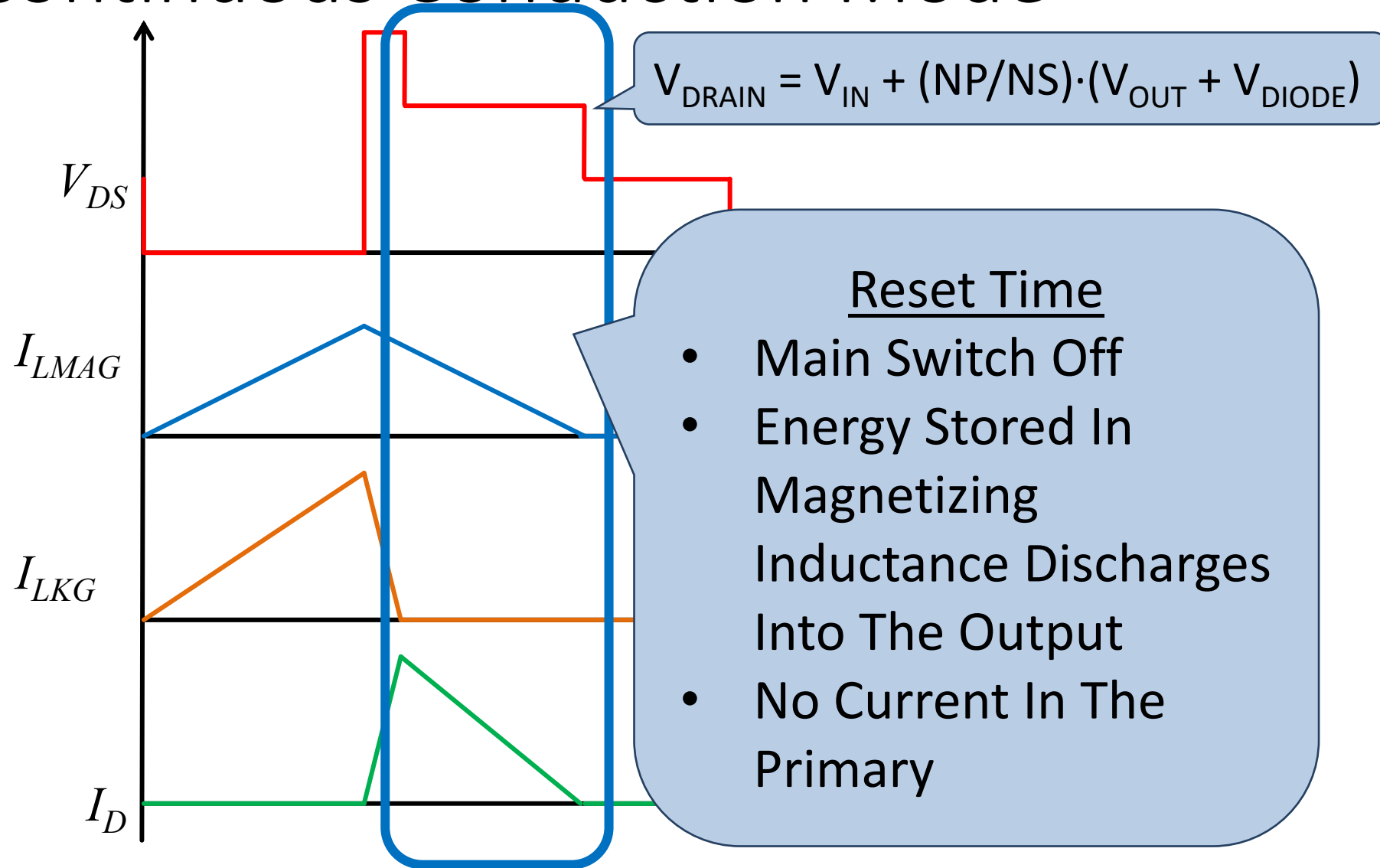


Discontinuous Conduction Mode

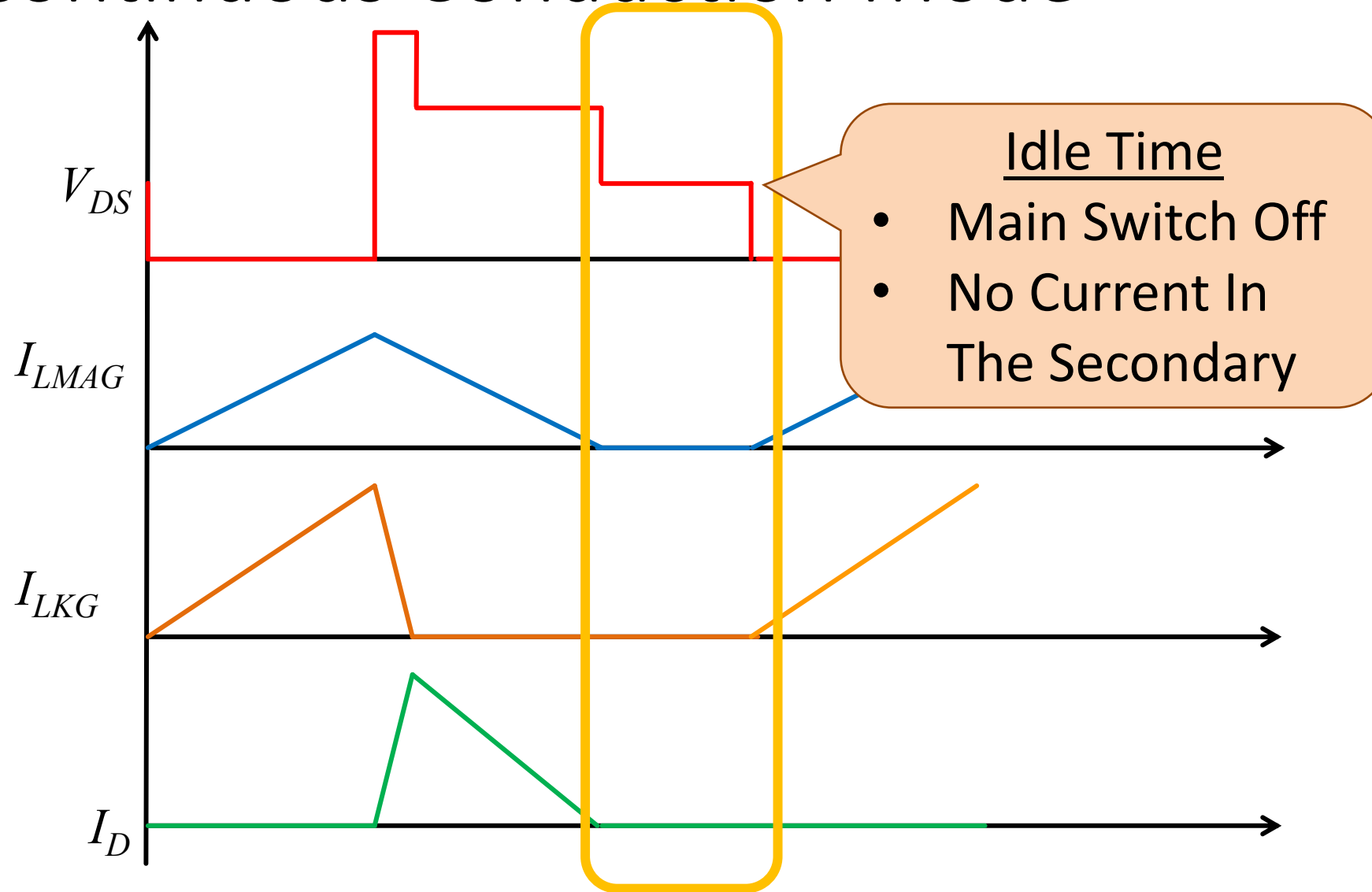

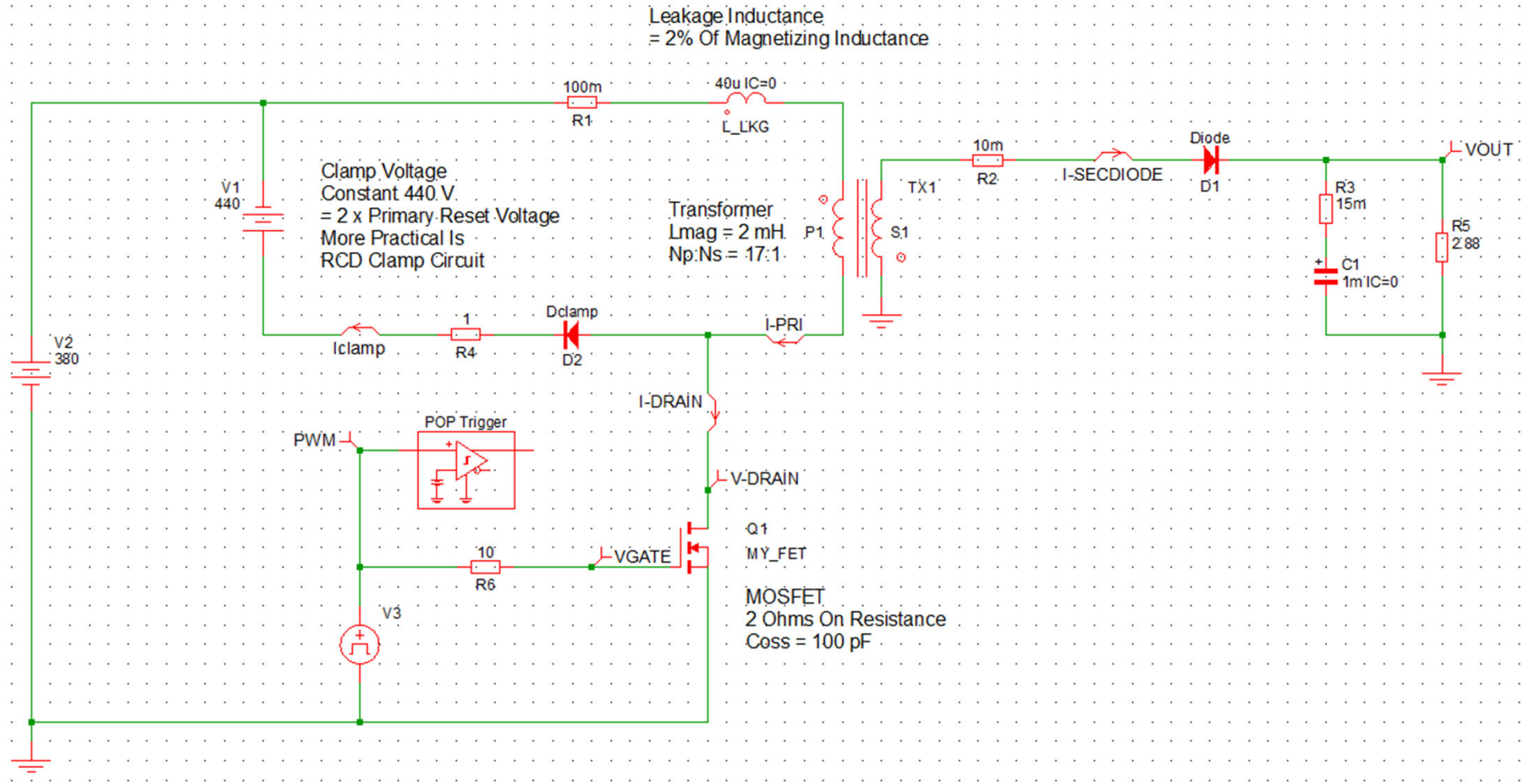Discontinuous Conduction Mode More Realistic Flyback Simulation




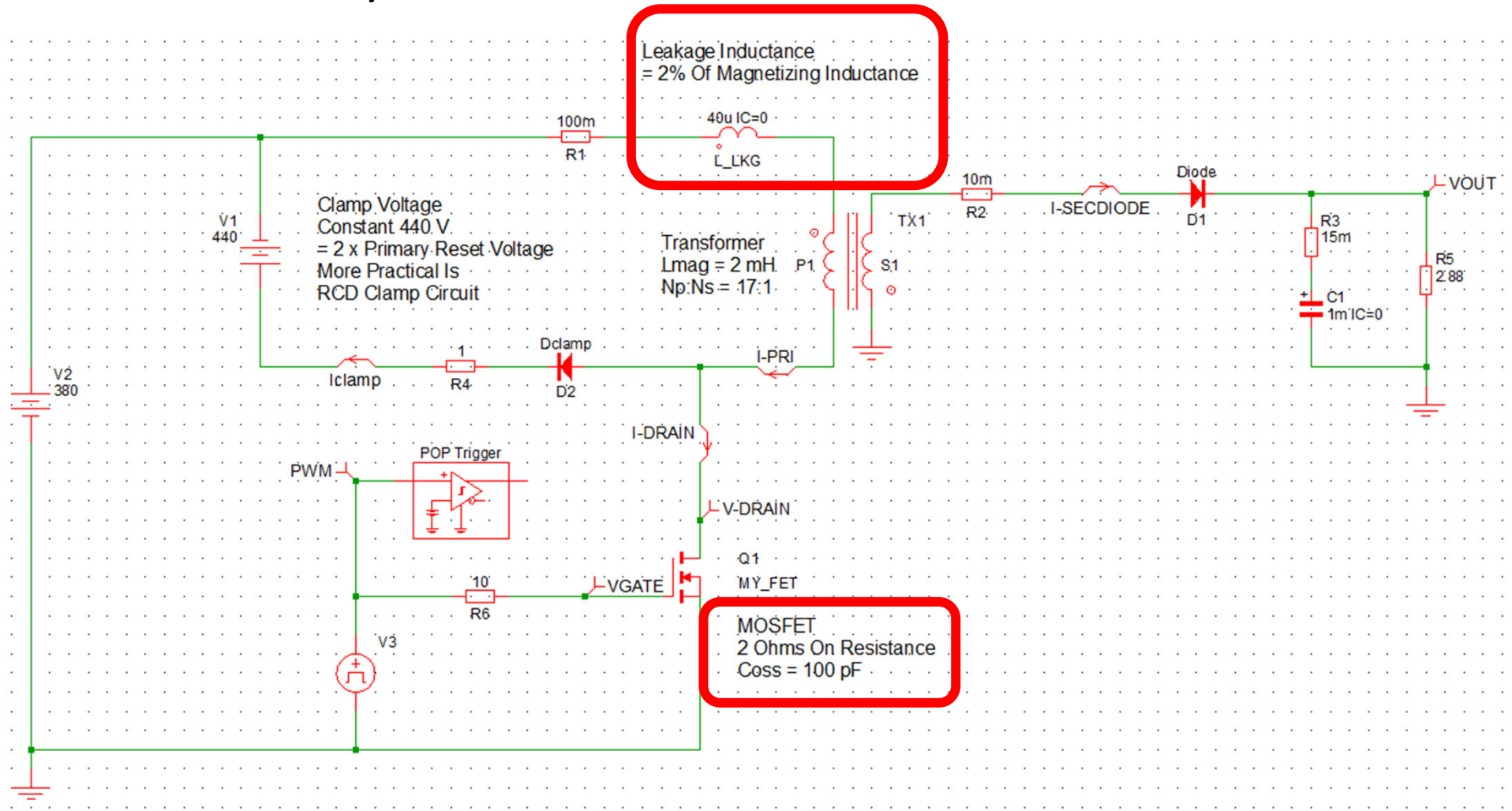Discontinuous Conduction Mode More Realistic Flyback Simulation




DCM On Time


DCM: On Time

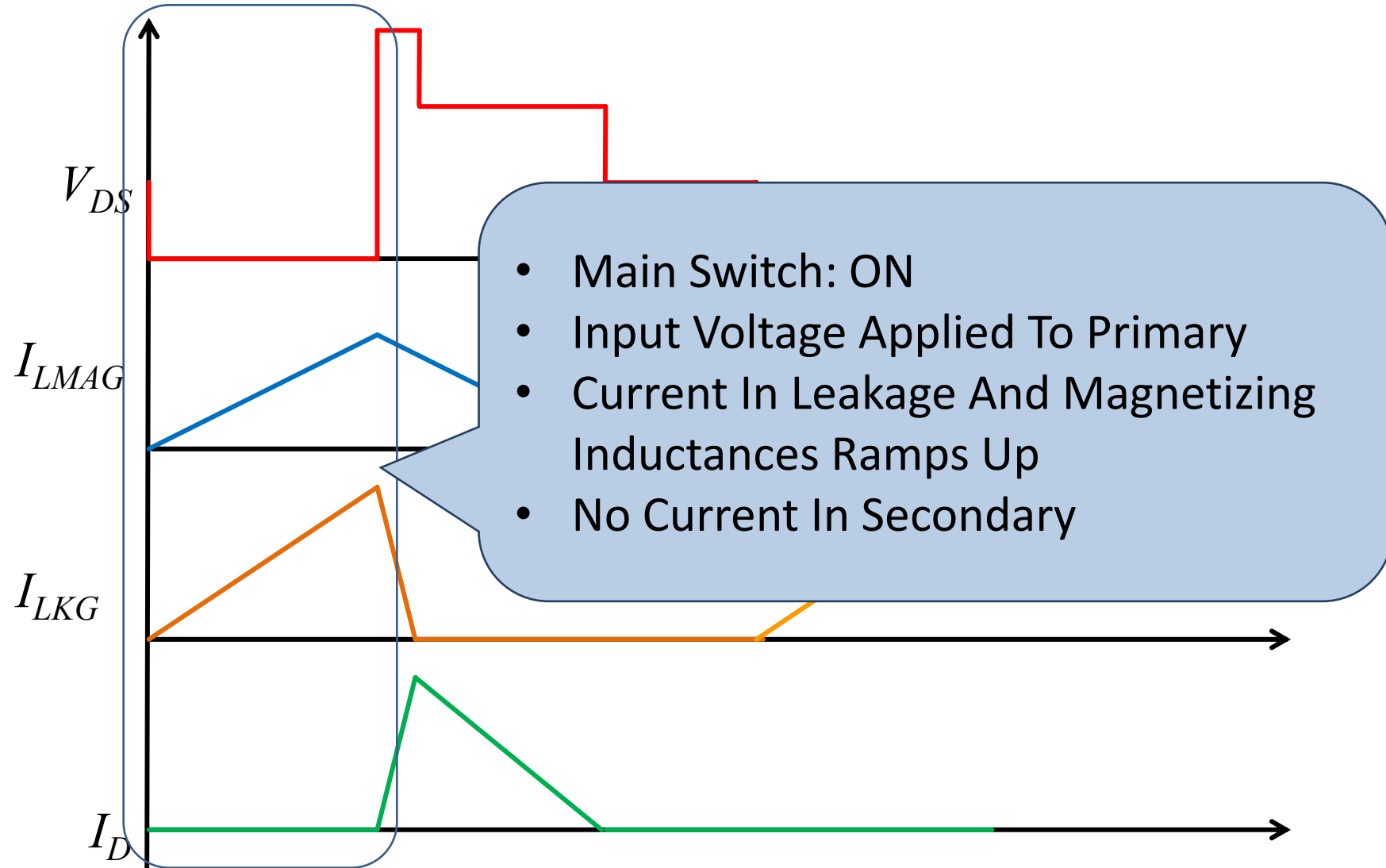

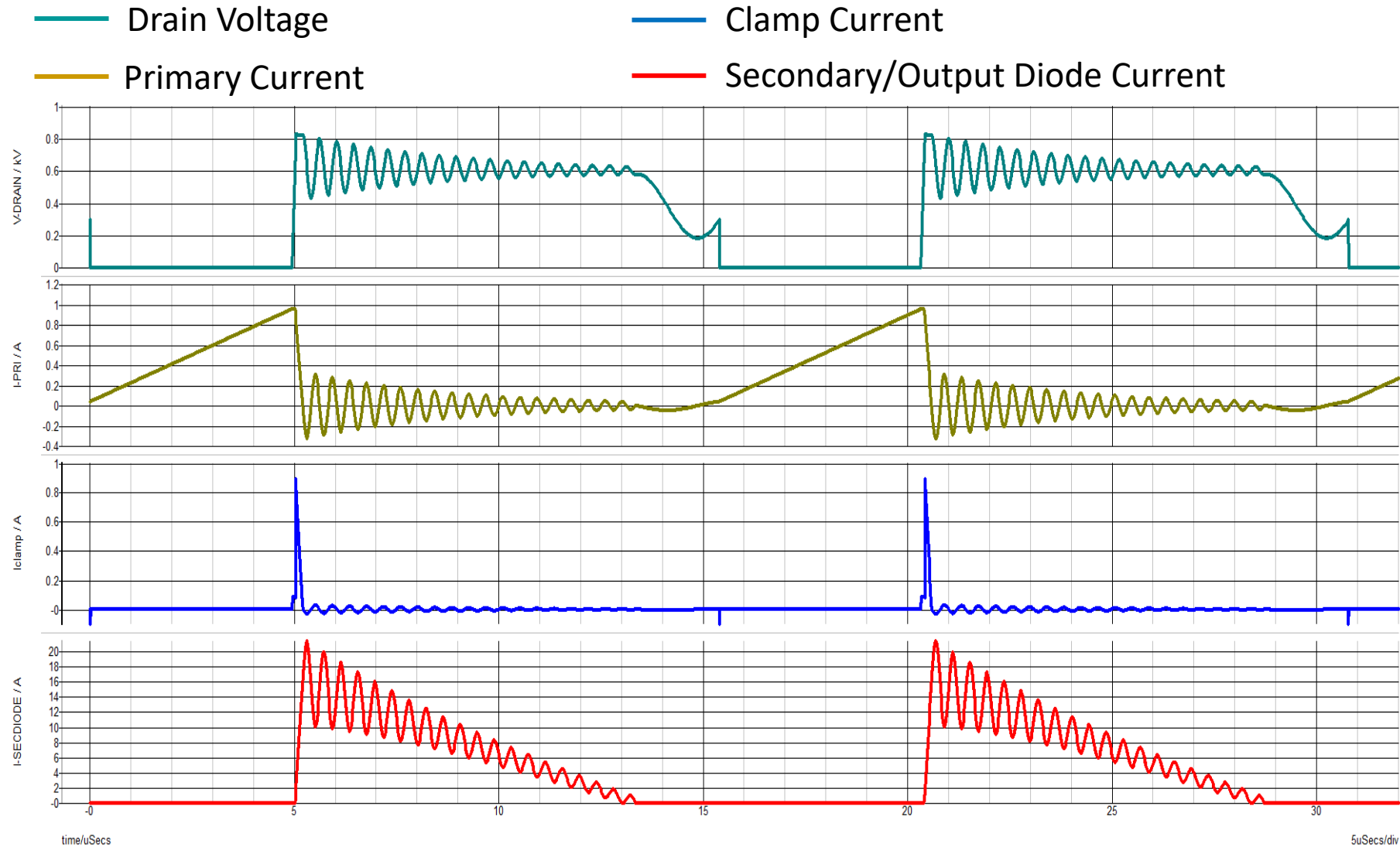Discontinuous Conduction Mode More Realistic Flyback Simulation




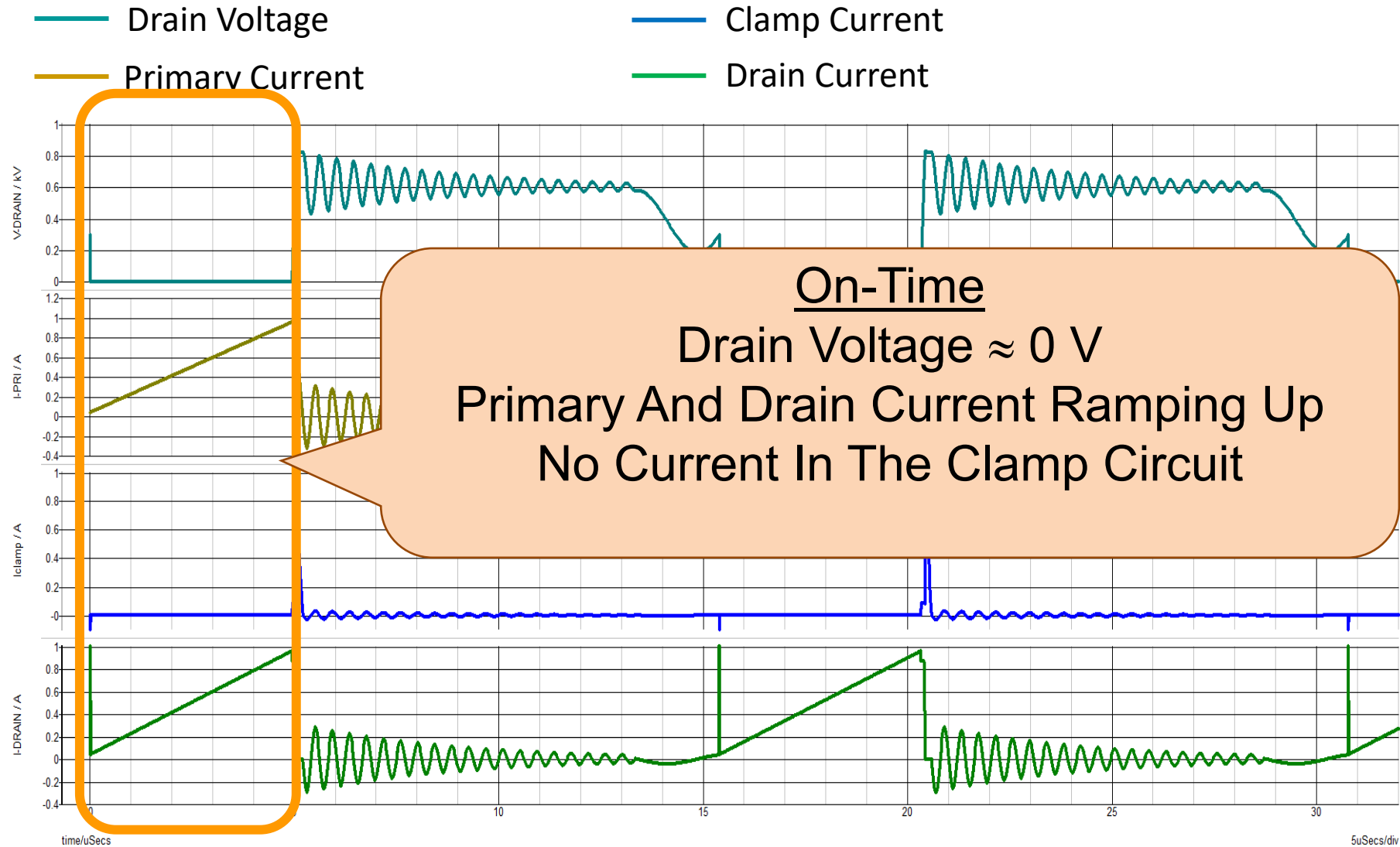Discontinuous Conduction Mode More Realistic Flyback Simulation



DCM Clamping Interval


Just Before MOSFET Turns Off

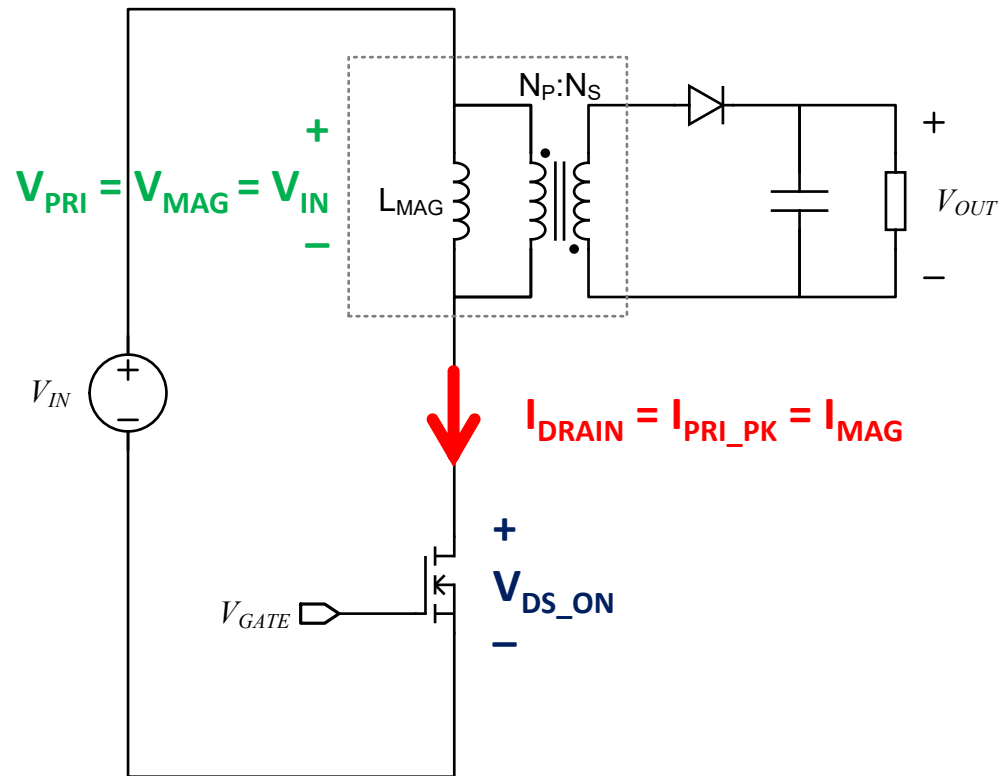

How Does This Circuit Model Change When The MOSFET Is Turned Off?


Ignoring L_{LKG} For The Moment...

Just After MOSFET Turned Off

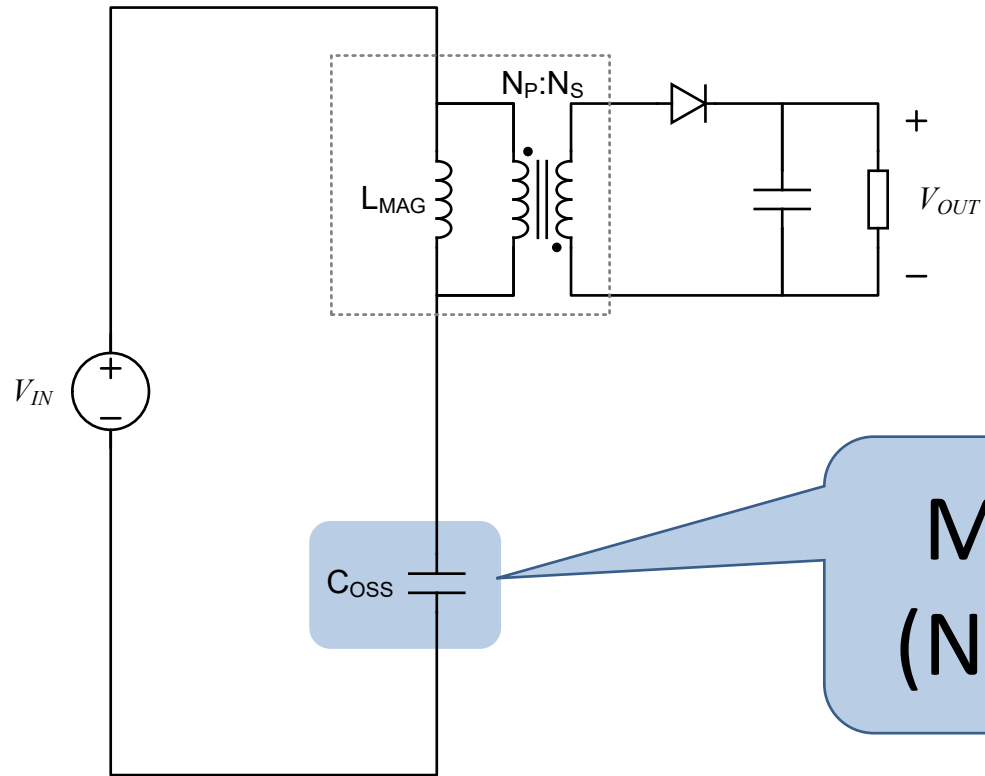


MOSFET Becomes A
(Nonlinear) Capacitor

Just After MOSFET Turned Off

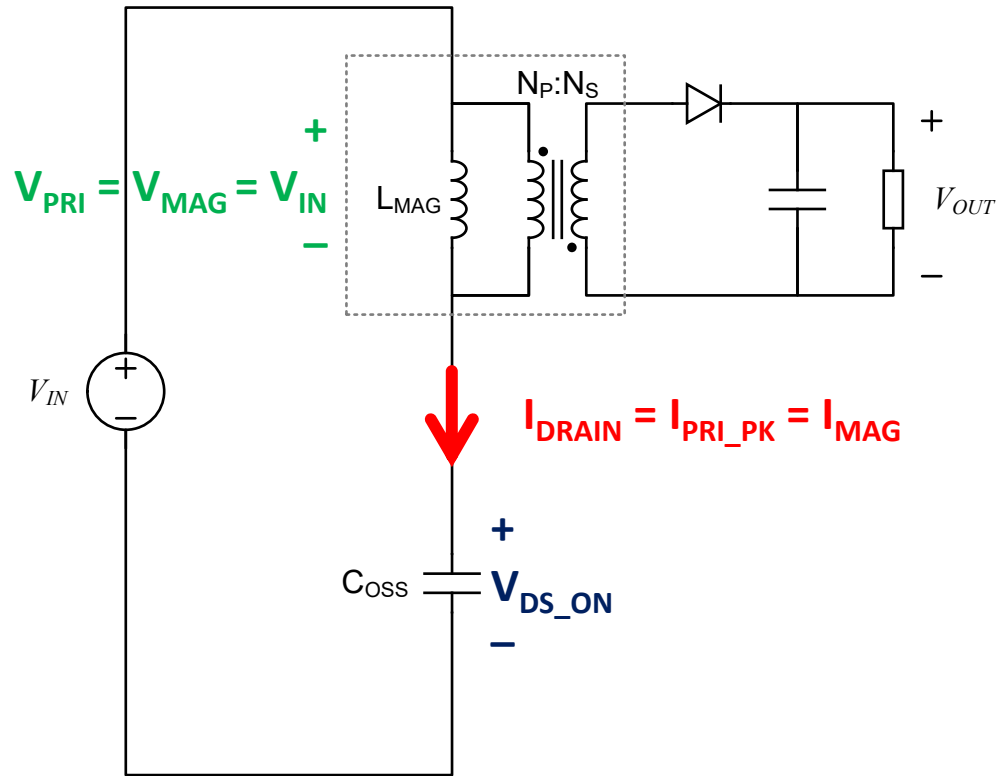


L_{MAG} Rings
With C_{OSS}

Just After MOSFET Turned Off

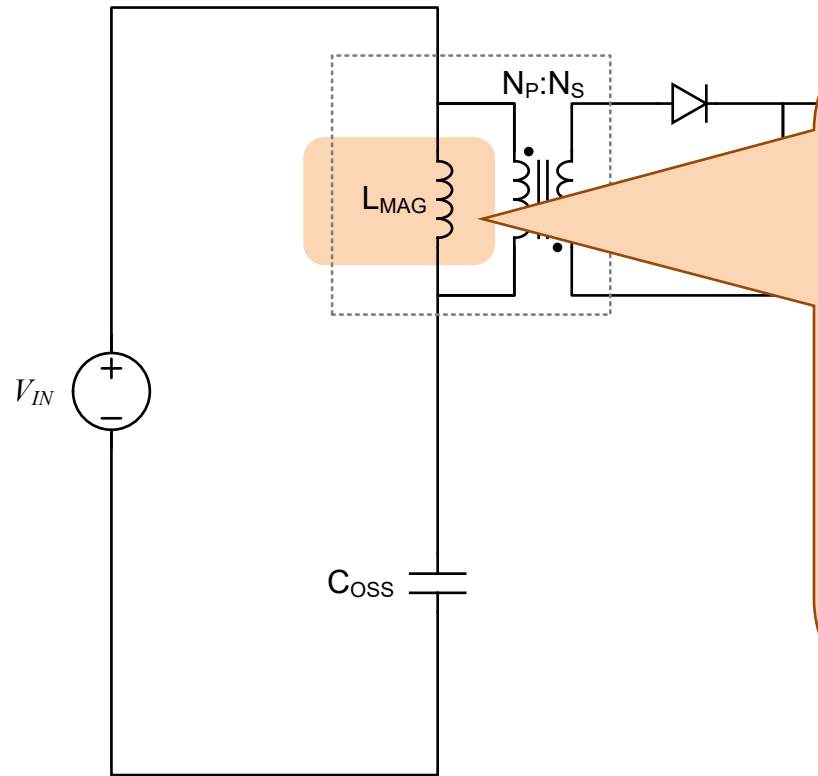


During Time Interval
Of Interest I_{MAG} Does
Not Change Much.
We Model It As A
Constant Current
Source


Just After MOSFET Turned Off

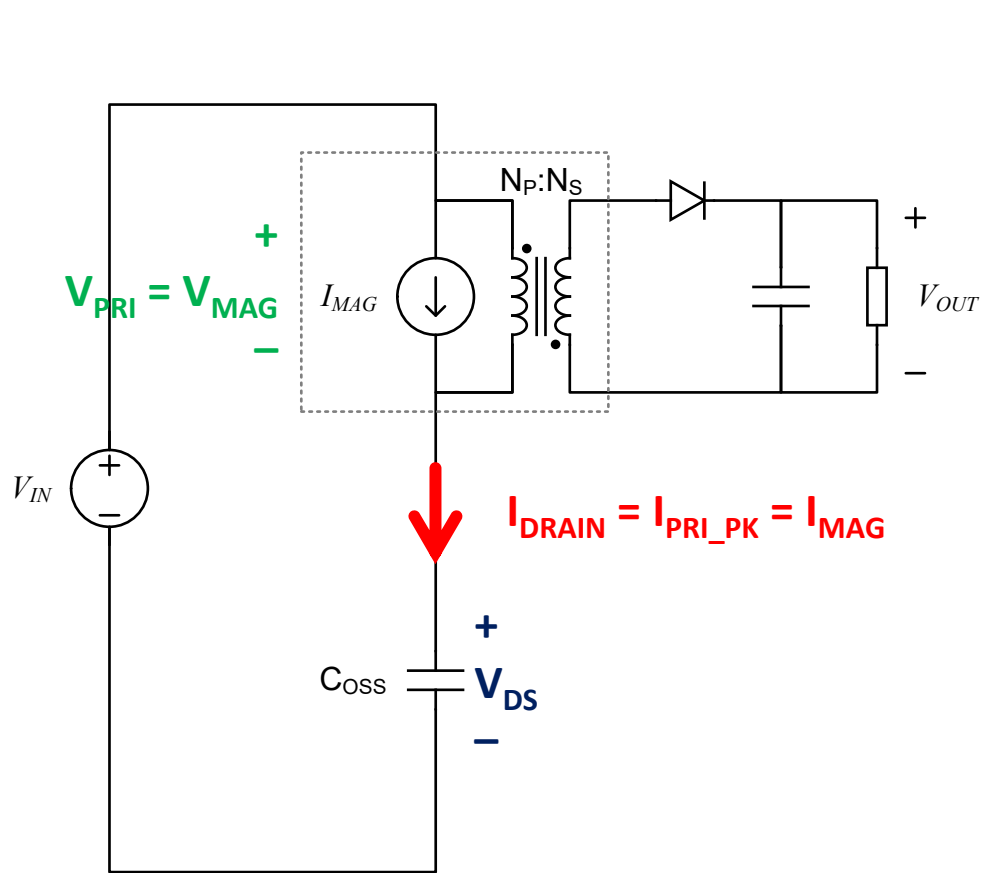


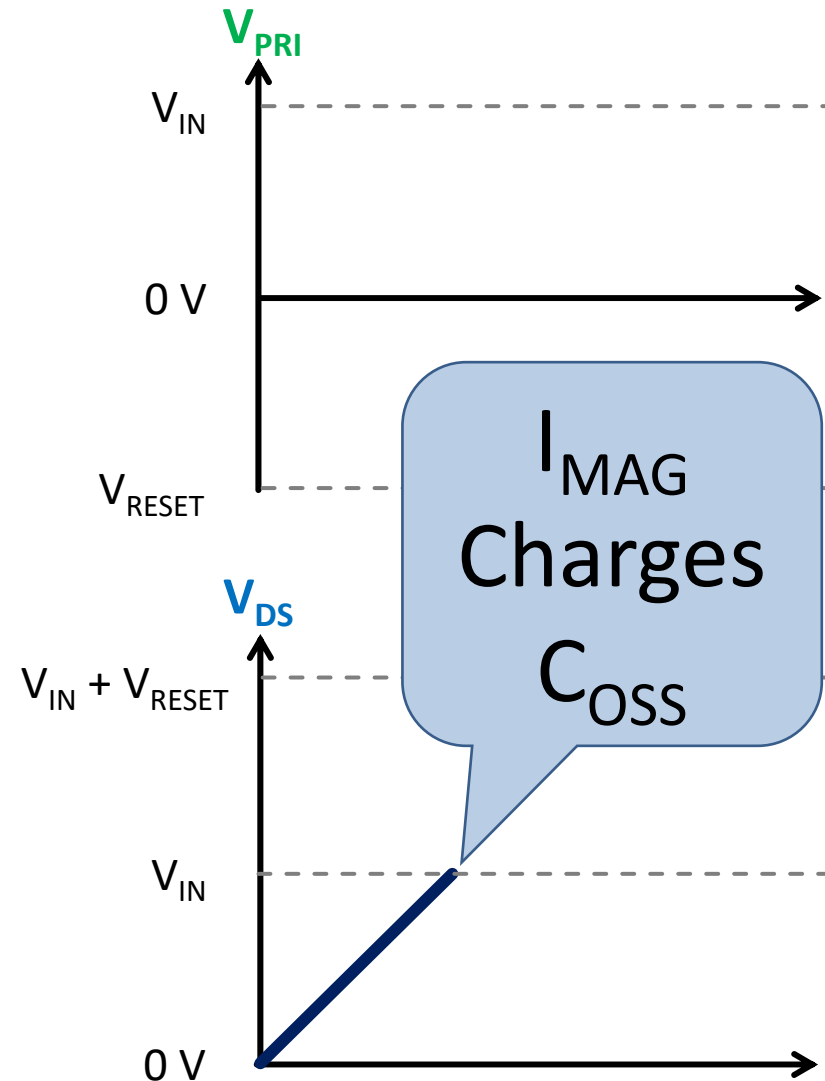
$$V_{RESET} = (N_P/N_S) \cdot (V_{OUT} + V_{DIODE})$$






Just After MOSFET Turned Off

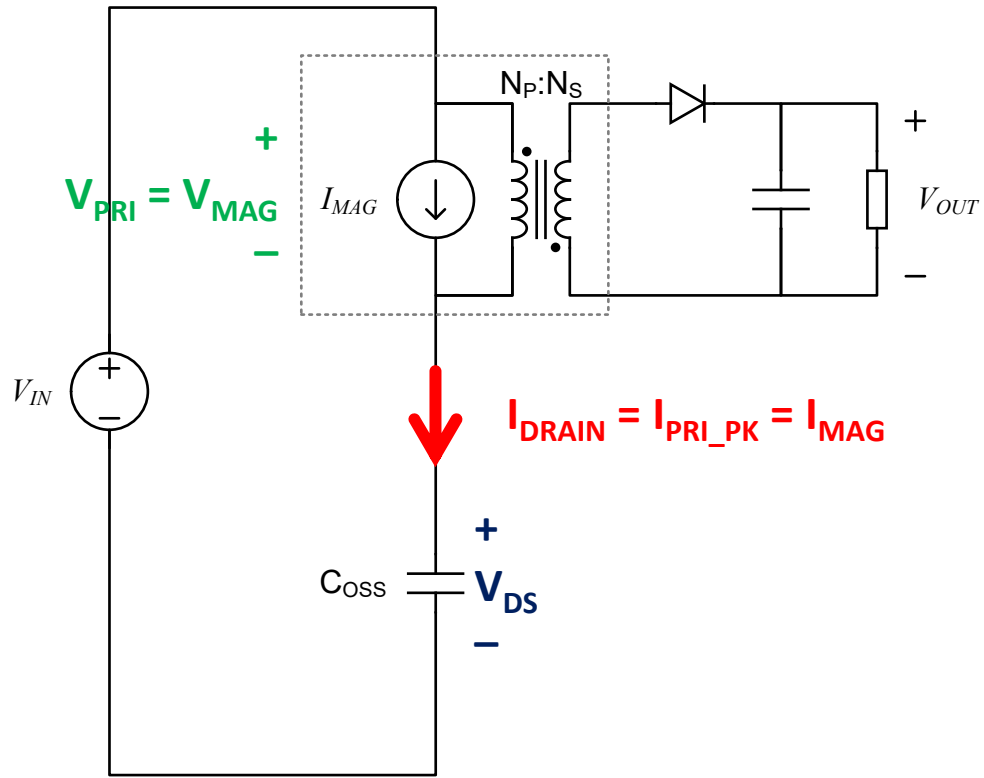
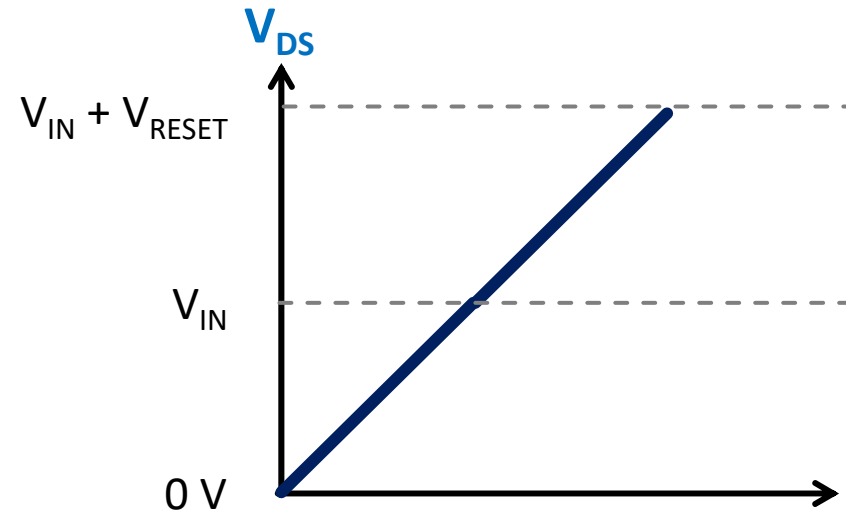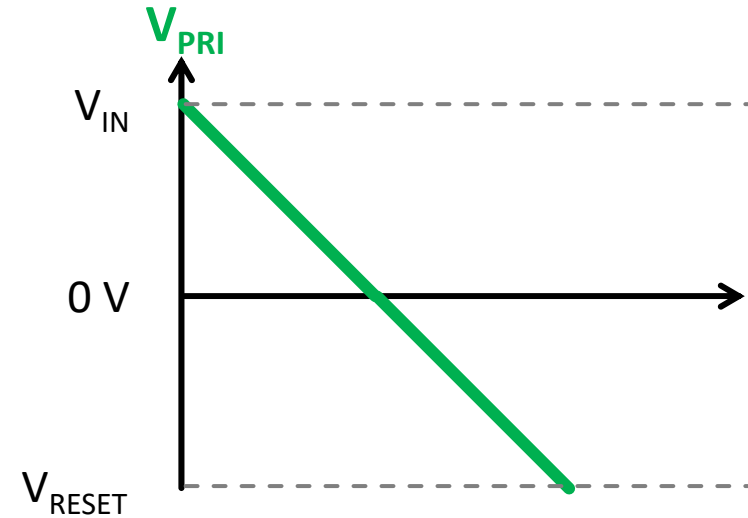
$$V_{RESET} = (N_P/N_S) \cdot (V_{OUT} + V_{DIODE})$$




Just After MOSFET Turned Off

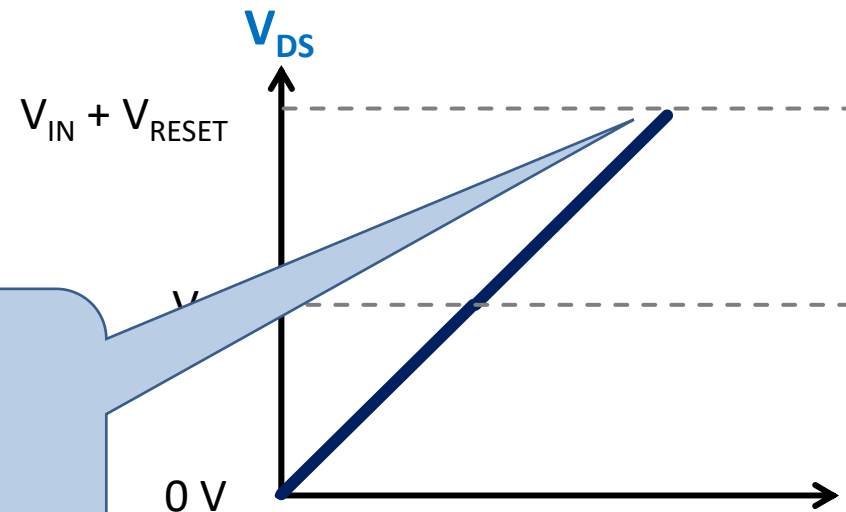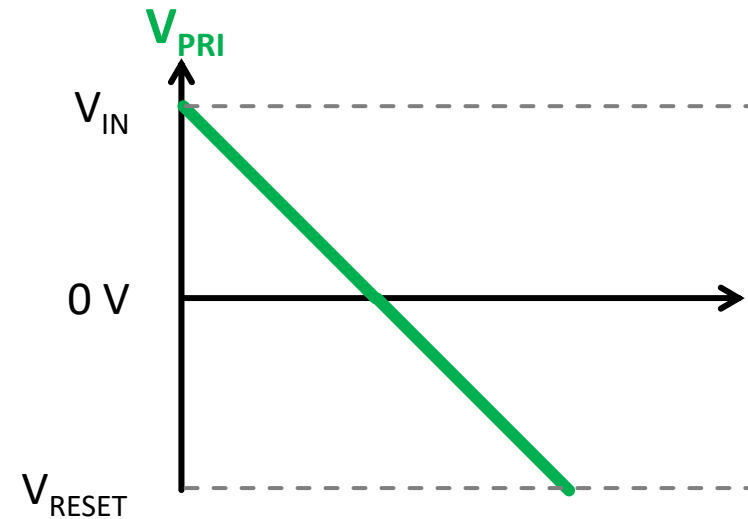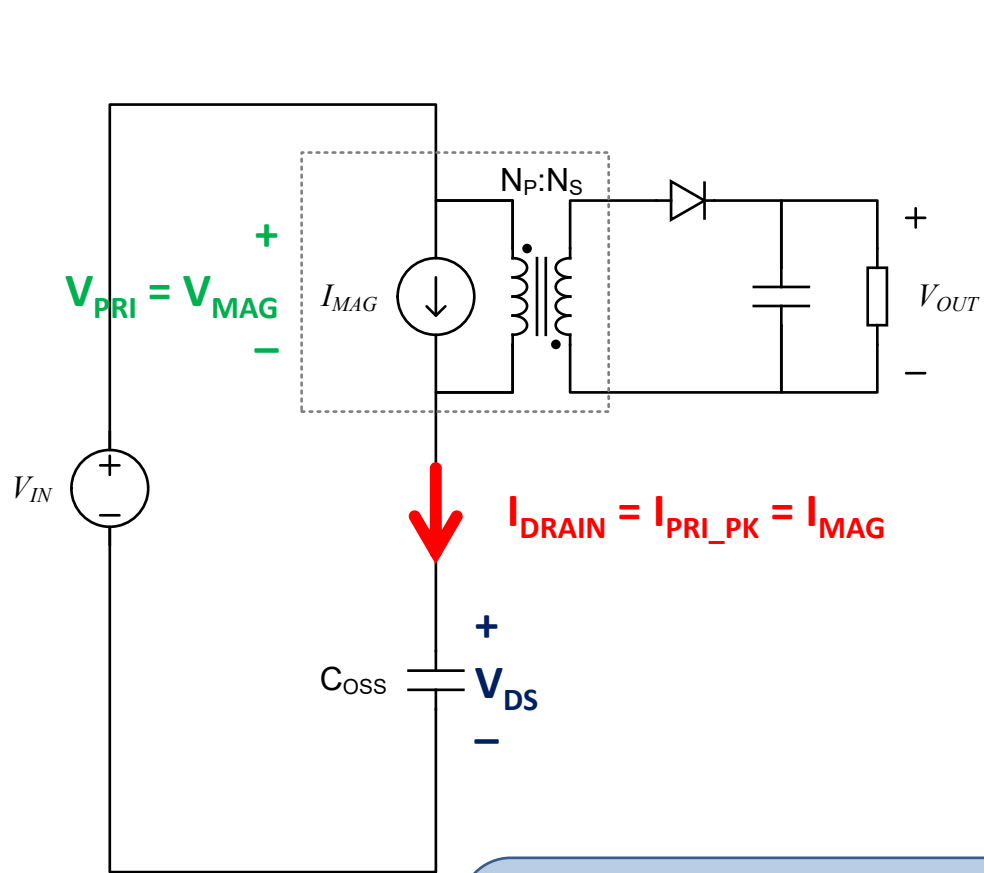

Now What Happens?

$$V_{RESET} = (N_P/N_S) \cdot (V_{IN} + V_{DS})$$

Just After MOSFET Turned Off

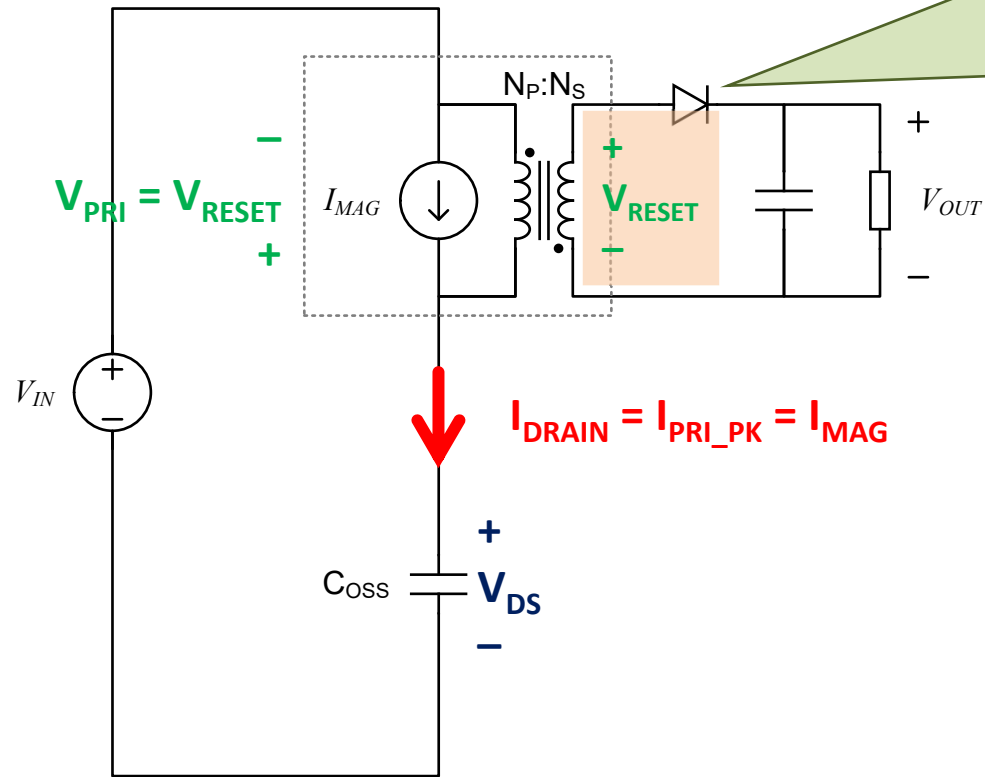

$$V_{RESET} = (N_P/N_S) \cdot (V_{OUT} + V_{DIODE})$$


Diode
Becomes
Forward
Biased

V_{RESET}

Primary Voltage Now
Clamped To Reflected
Output Voltage, V_{RESET}

0V


Just After MOSFET Turned Off

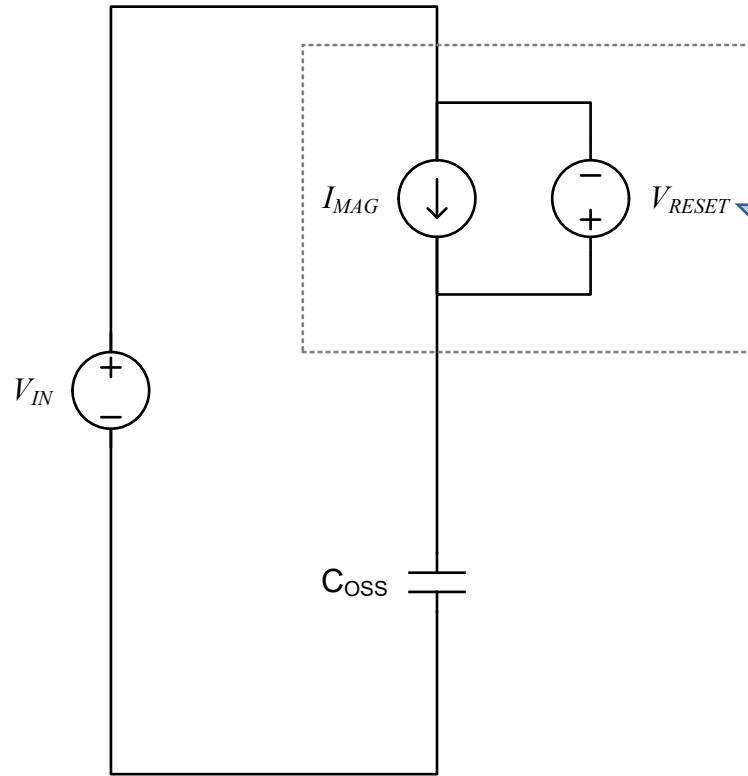

Modeling Voltage
Reflected From
Secondary As
Constant

But Wait!
There's
More!


Just After MOSFET Turned Off

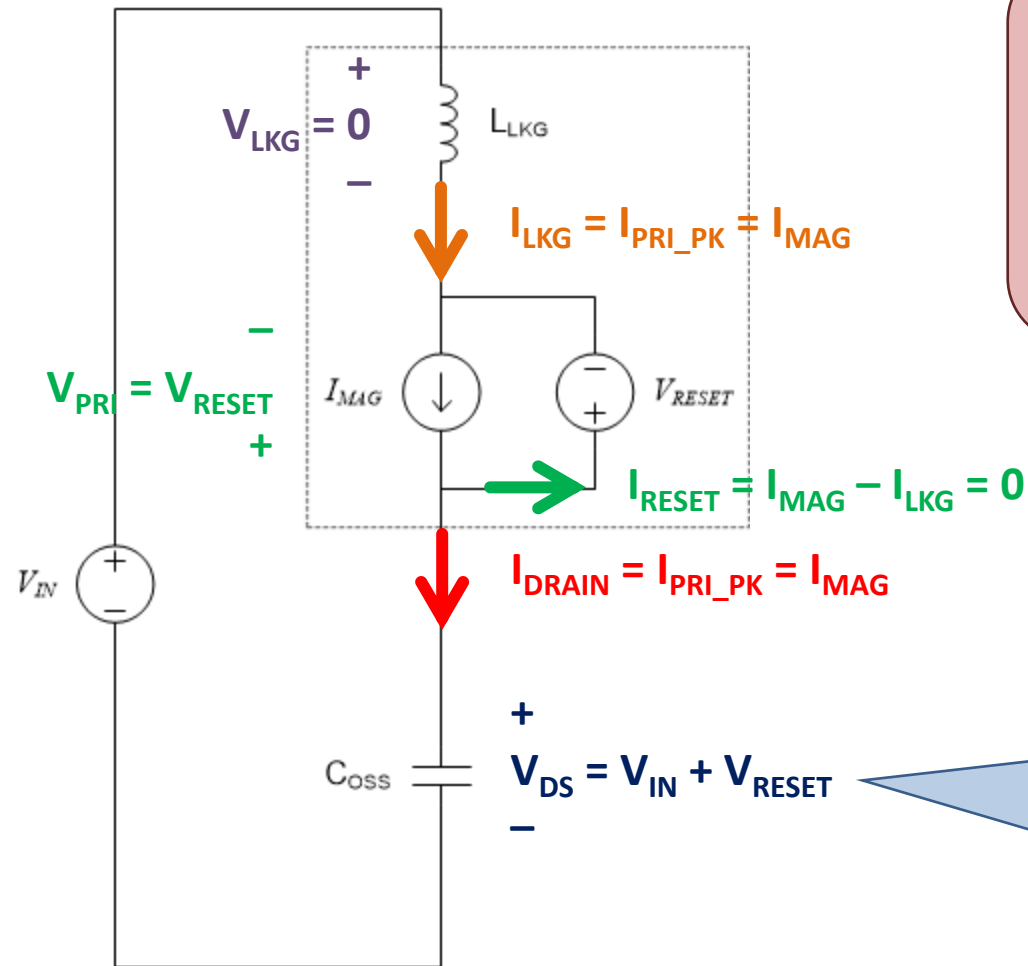


What Limits
The Maximum
Drain Voltage?

C_{OSS} Continues
To Charge

Voltage Clamp

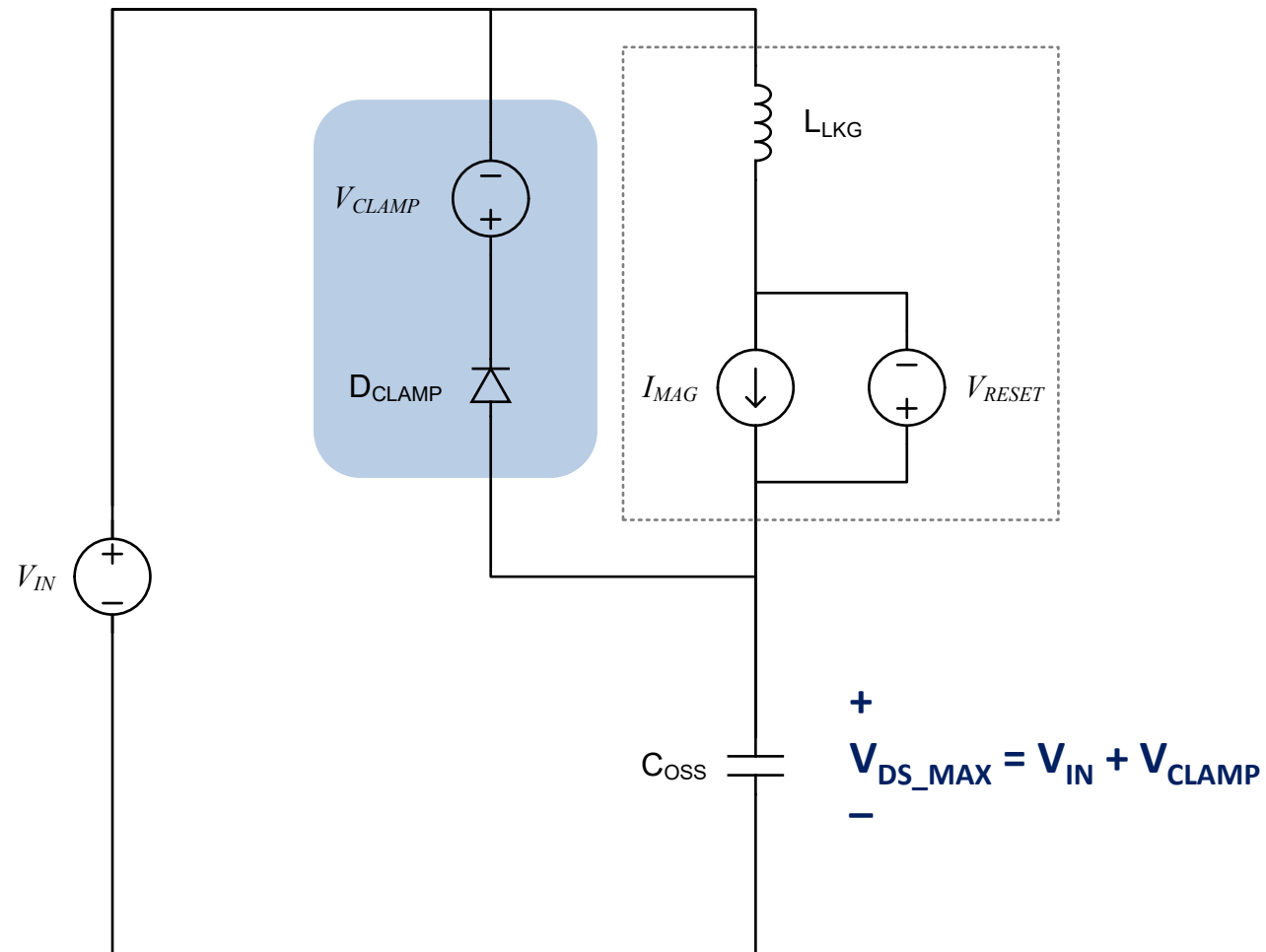


RCD Voltage Clamp

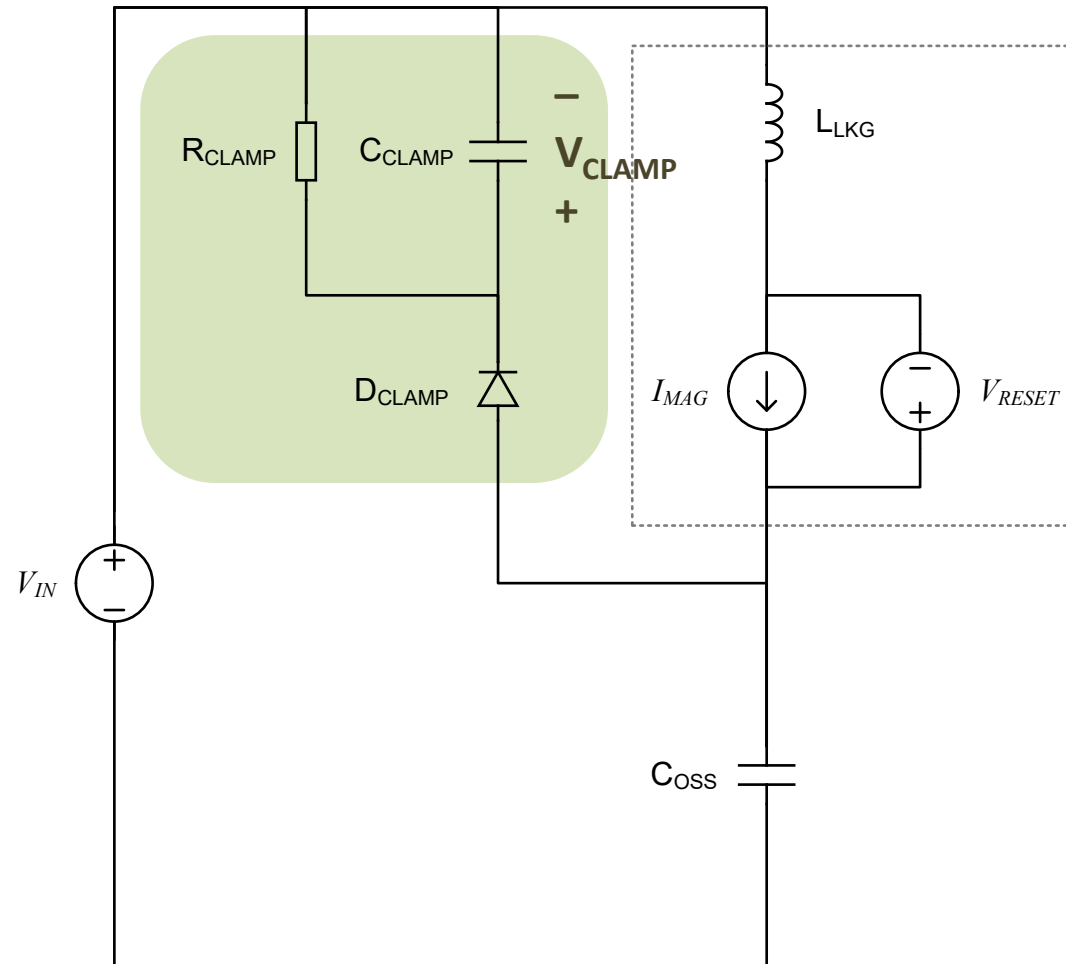


Shown Later
 C_{CLAMP} Is Large
Enough That
 V_{CLAMP} Can Be
Considered
Constant

Clamp Interval

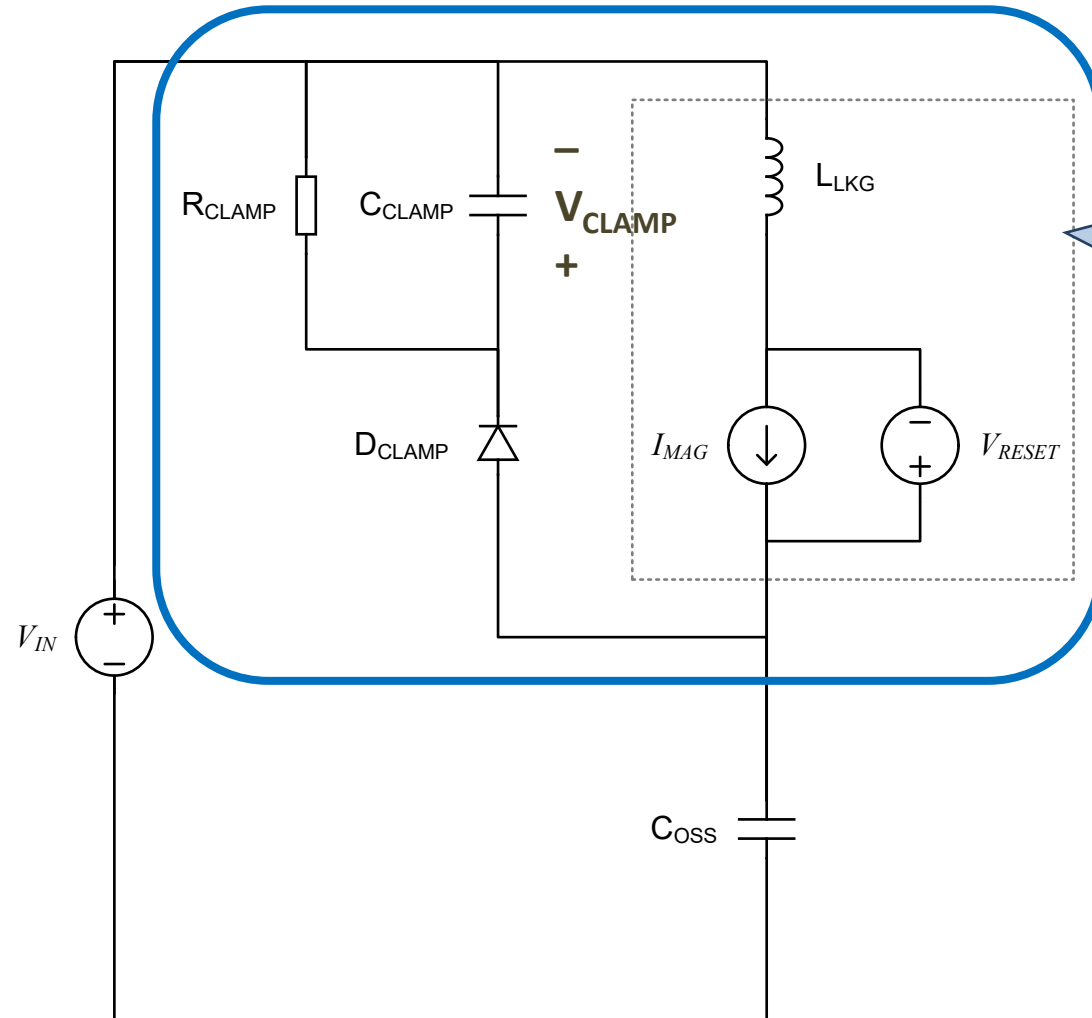


Focus Just On
This Part Of
The Circuit To
Analyze What
Happens
During The
Clamp Interval

DCM: Clamp Interval

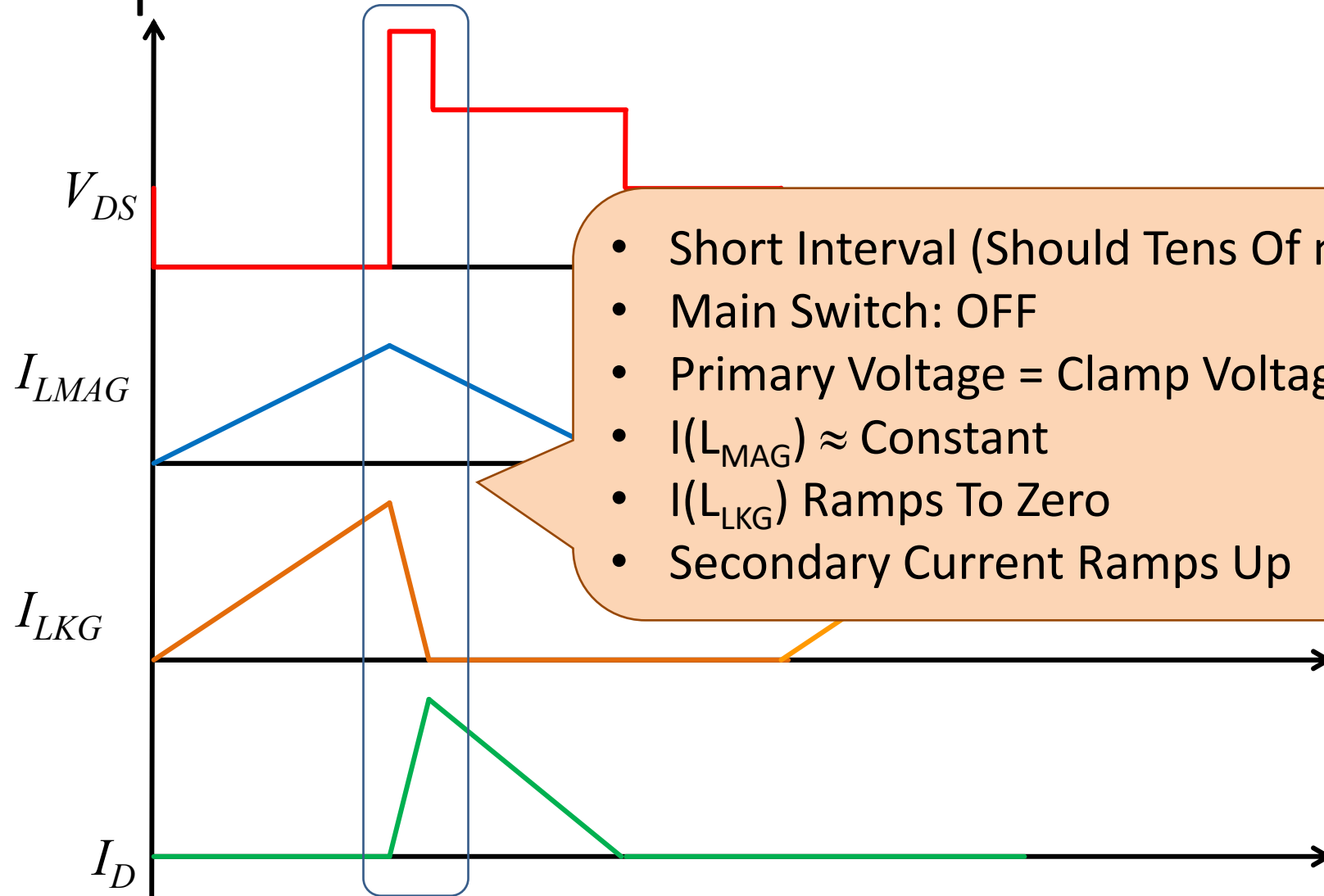


- Short Interval (Should Tens Of ns)
- Main Switch: OFF
- Primary Voltage = Clamp Voltage
- $I(L_{MAG}) \approx \text{Constant}$
- $I(L_{LKG})$ Ramps To Zero
- Secondary Current Ramps Up

Clamp Interval Circuit Model

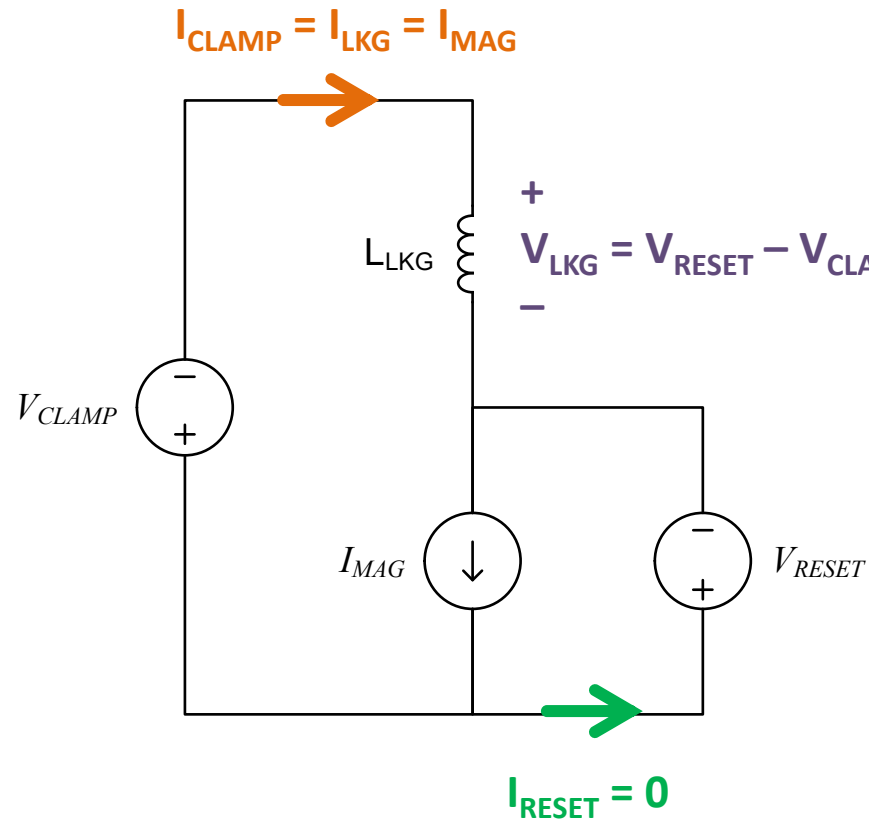


Initial Conditions

Clamp Interval Current

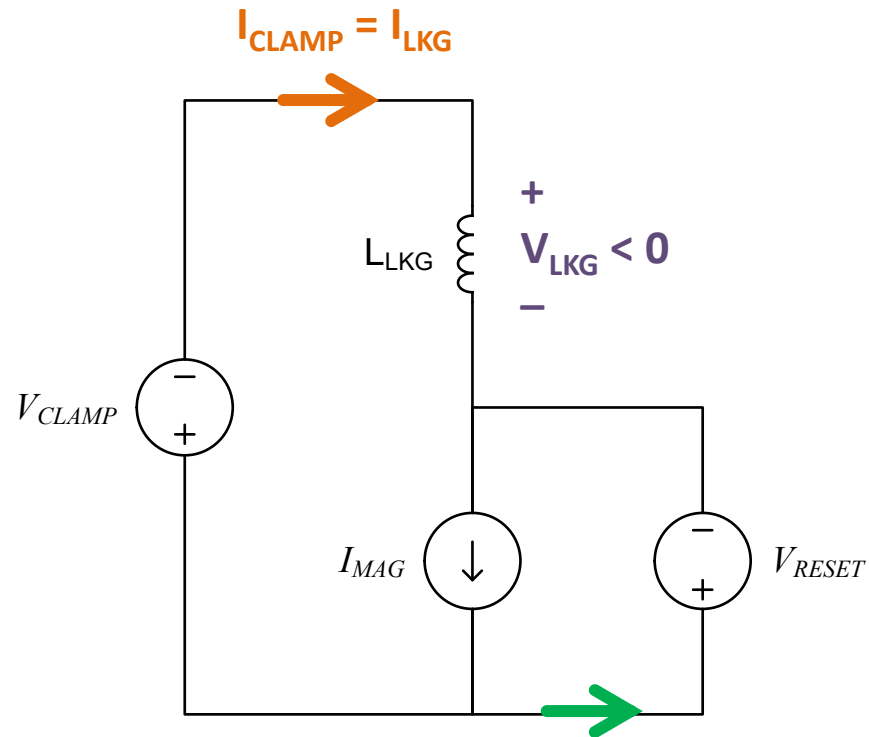


$$I_{RESET} = I_{MAG} - I_{LKG}$$

$$I_{SEC} = (N_P/N_S) \cdot I_{RESET}$$

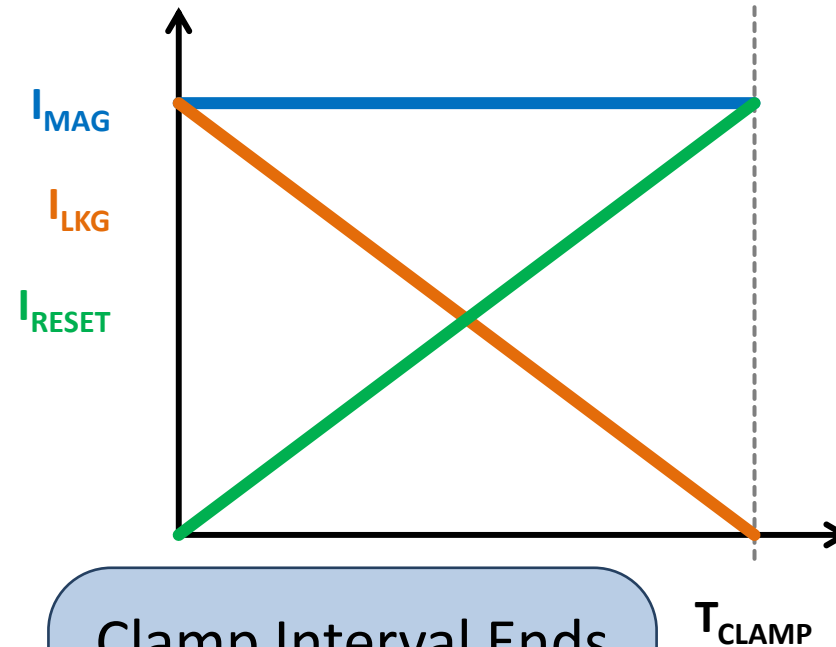


Clamp Interval Ends
When Current In
Leakage Inductance
Goes To Zero

DCM: Clamp Interval

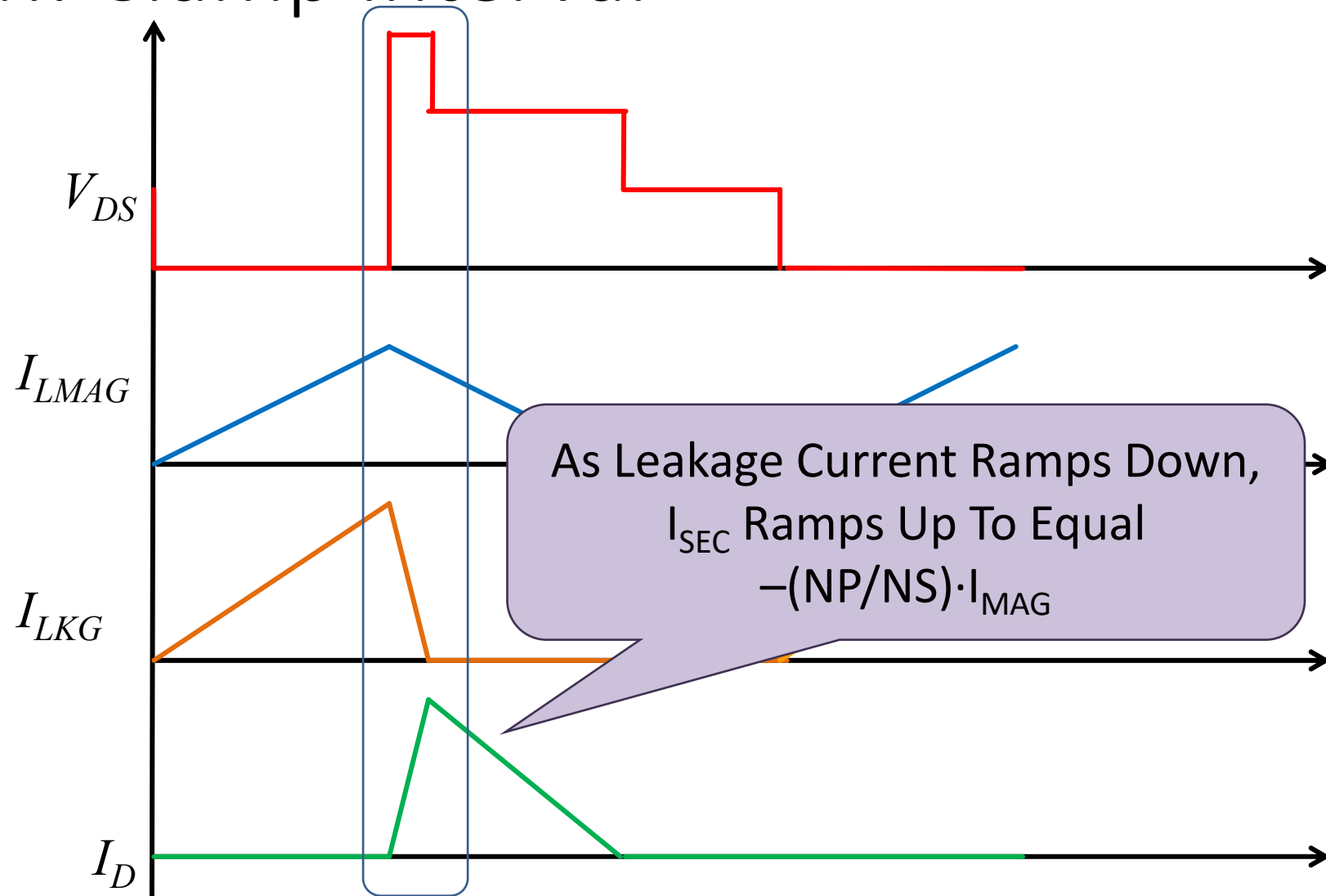


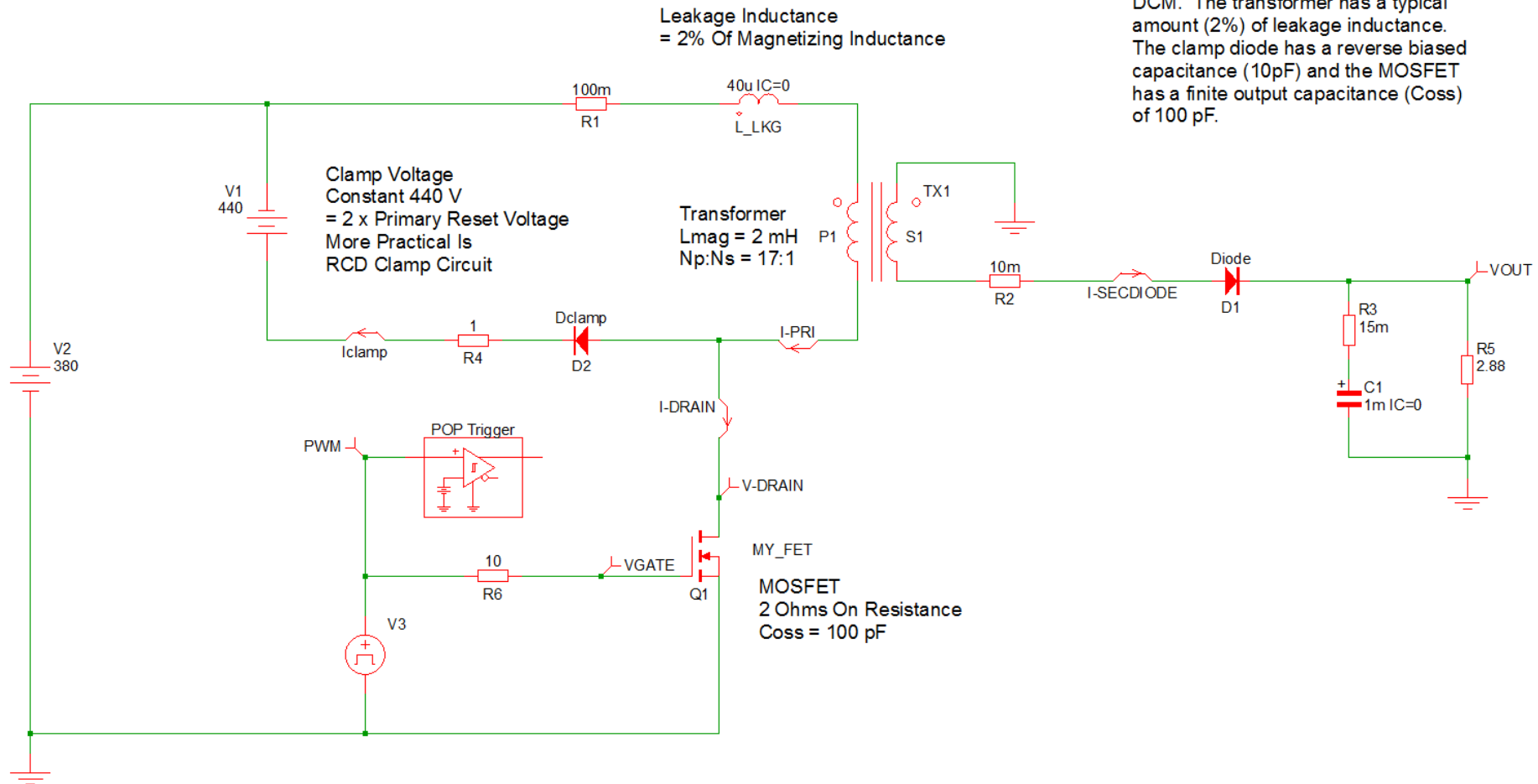Discontinuous Conduction Mode More Realistic Flyback Simulation



This is a more realistic simulation of a flyback converter operating in DCM. The transformer has a typical amount (2%) of leakage inductance. The clamp diode has a reverse biased capacitance (10pF) and the MOSFET has a finite output capacitance (Coss) of 100 pF.

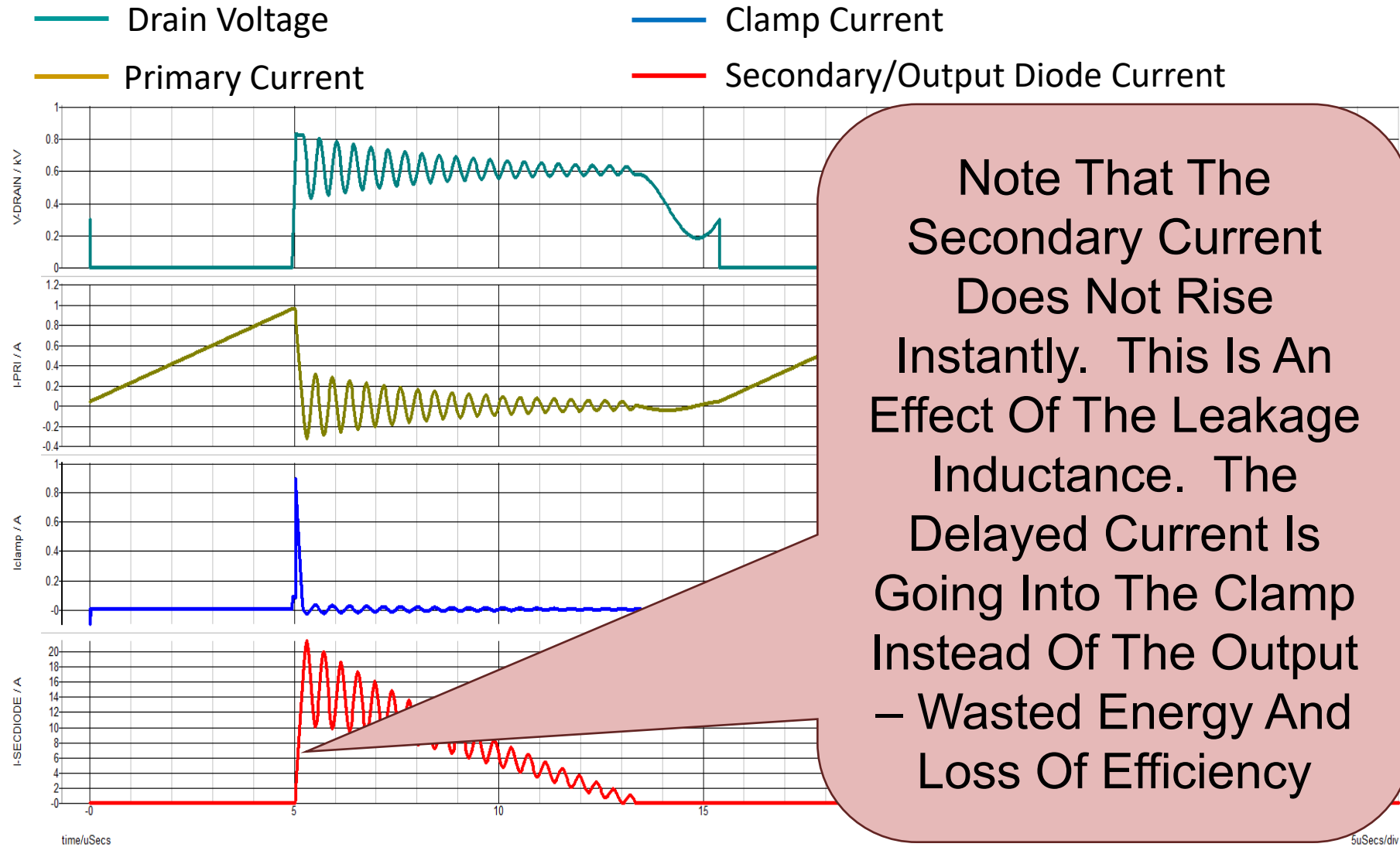Discontinuous Conduction Mode More Realistic Flyback Simulation




Note That The Secondary Current Does Not Rise Instantly. This Is An Effect Of The Leakage Inductance. The Delayed Current Is Going Into The Clamp Instead Of The Output – Wasted Energy And Loss Of Efficiency

Discontinuous Conduction Mode


Details Of The Clamp Time

— Drain Voltage
— Primary Current
— Clamp Current
— Secondary/Output Diode Current

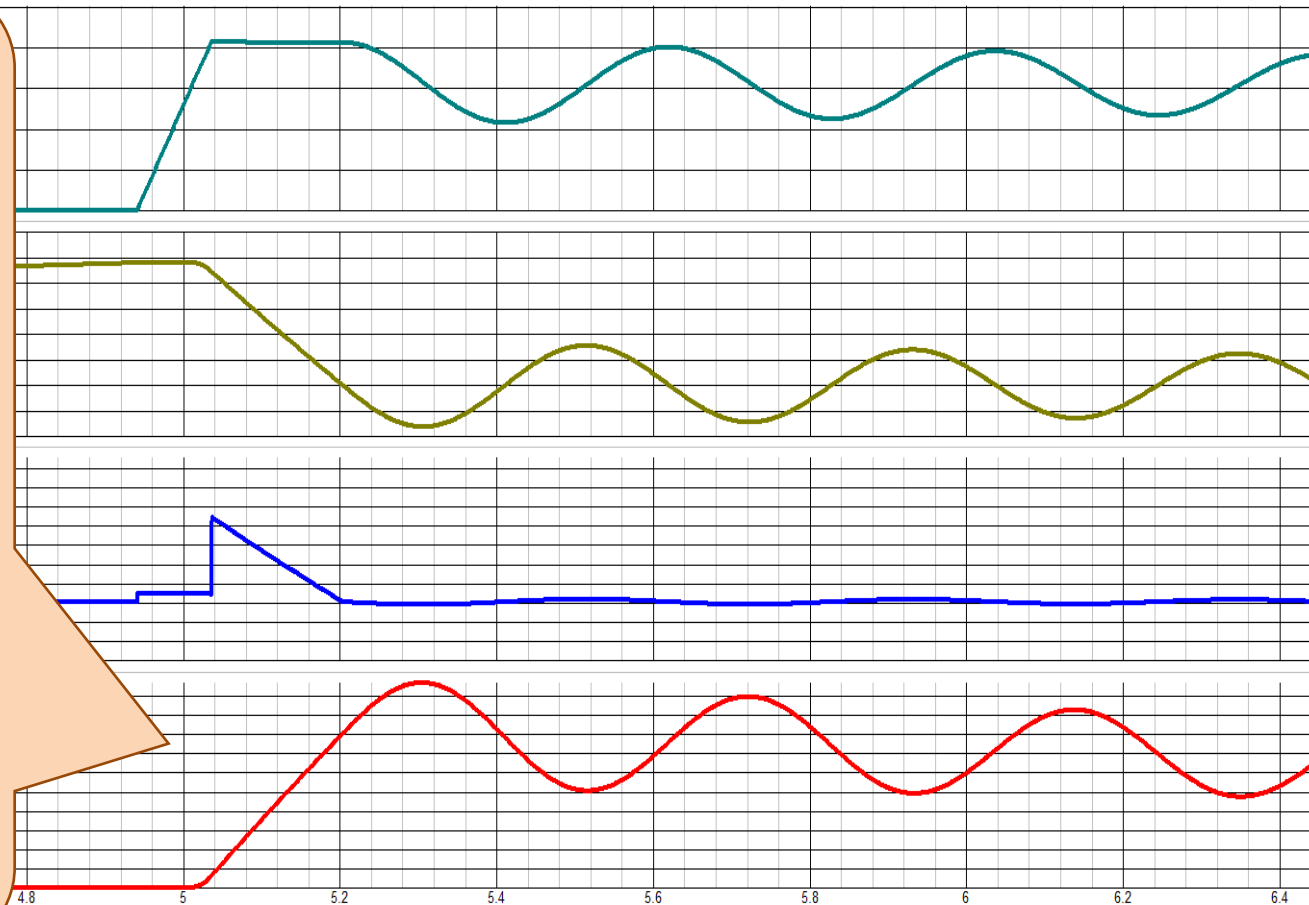
Note That The Secondary Current Is Not Fully Established Until The Leakage Inductance /Clamp Current Goes To Zero



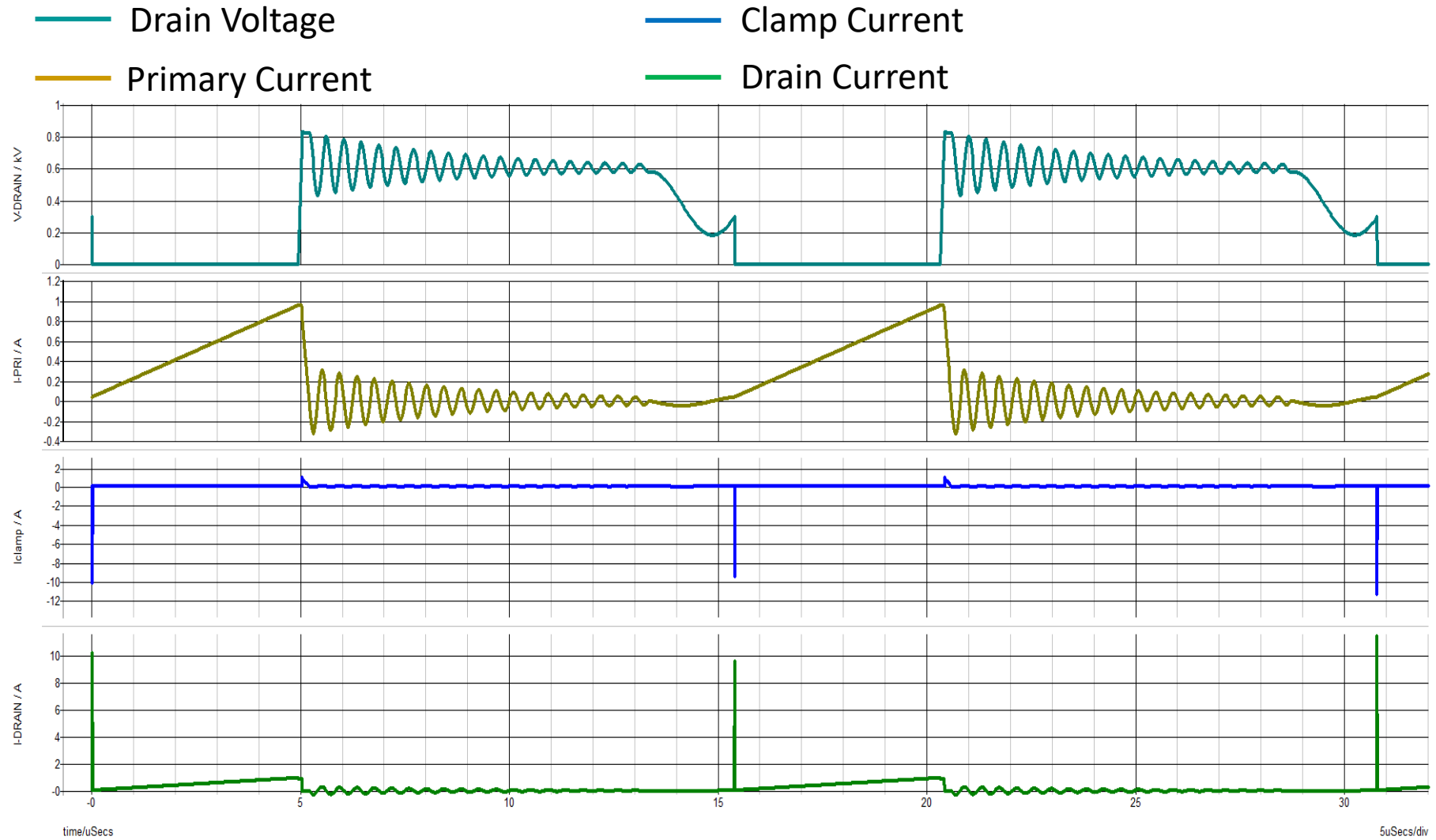
Discontinuous Conduction Mode More Realistic Flyback Simulation



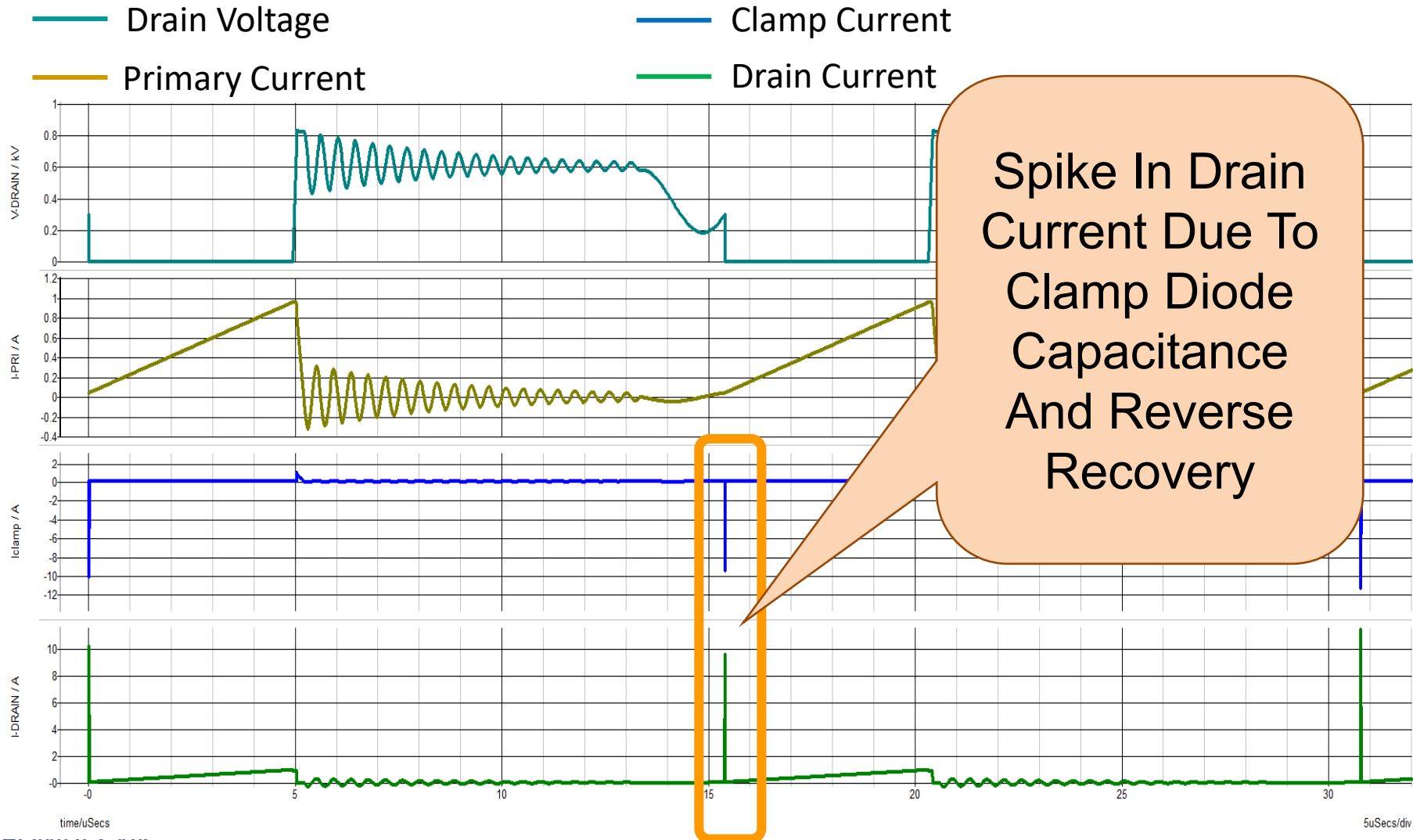
Discontinuous Conduction Mode More Realistic Flyback Simulation



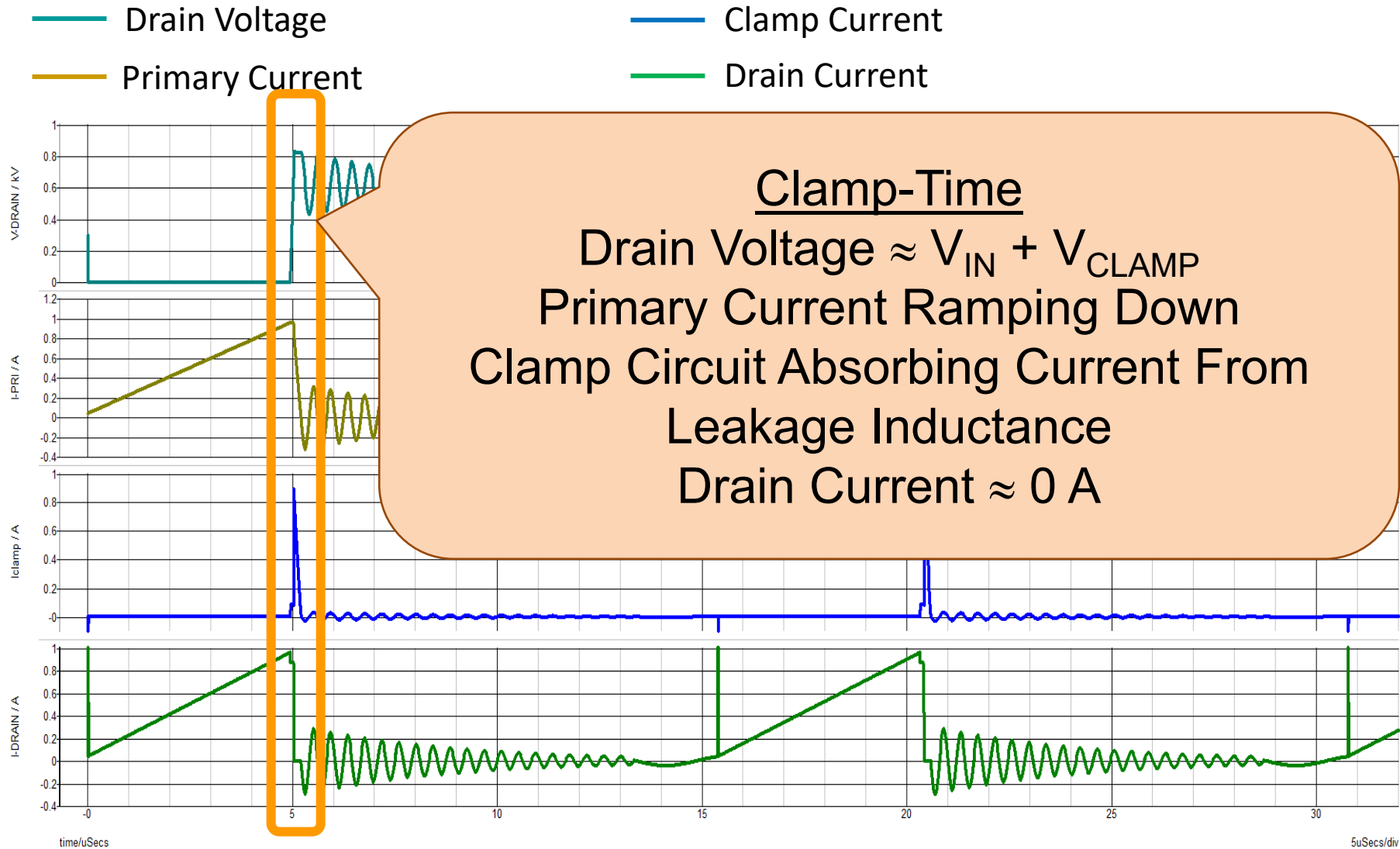
Discontinuous Conduction Mode More Realistic Flyback Simulation




DCM: Clamp Interval

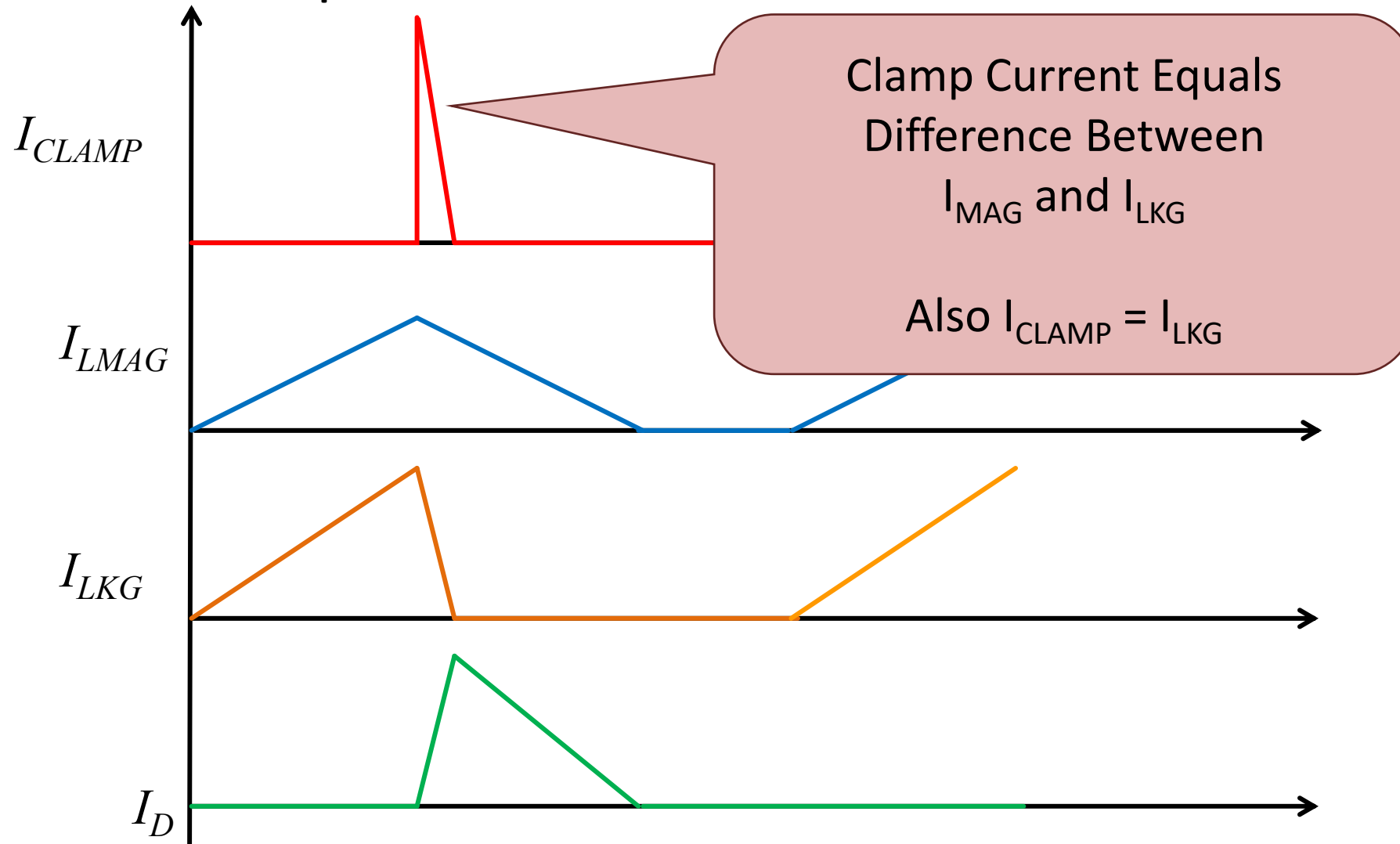


DCM: Clamp Interval

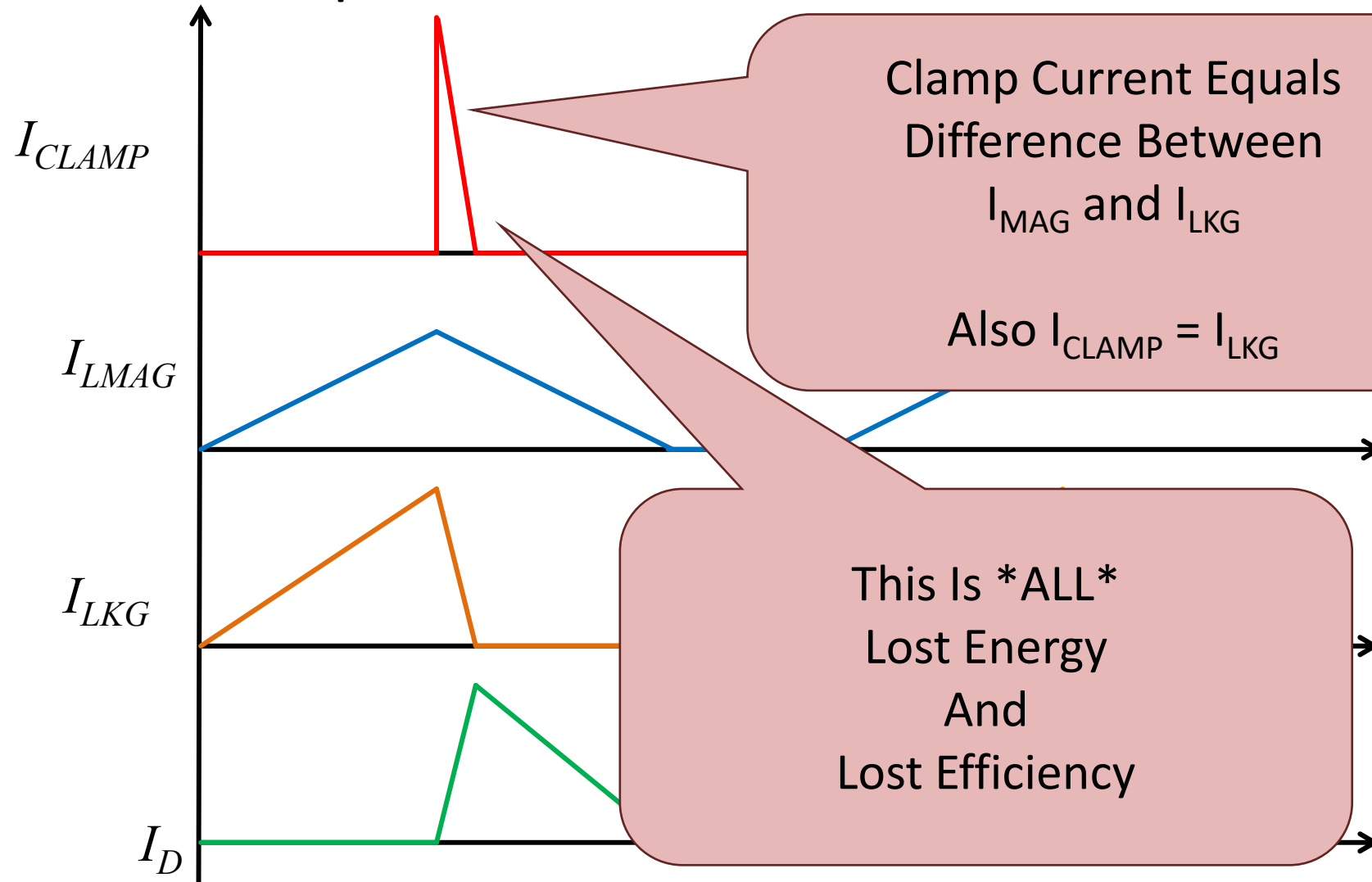


Leakage Loss

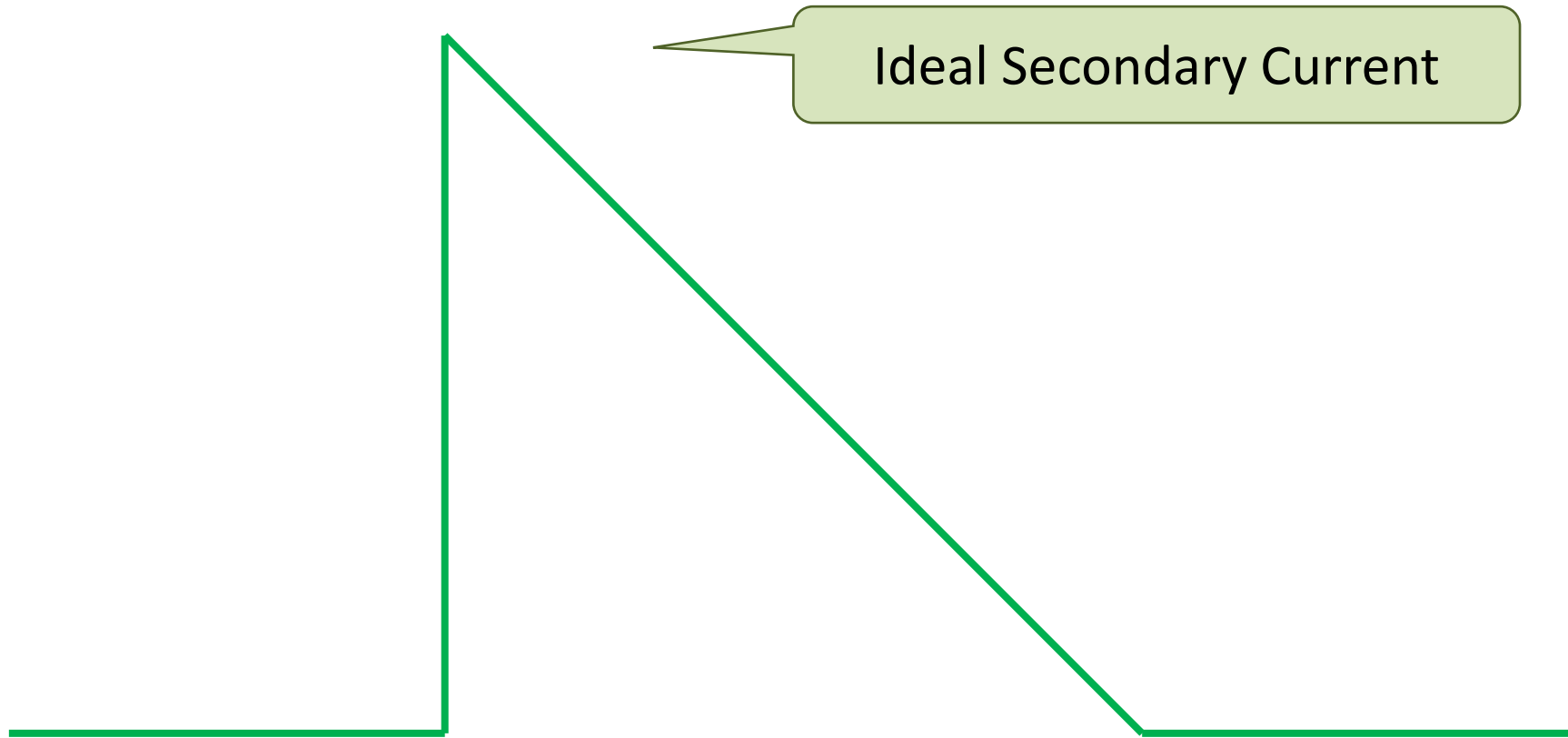


Leakage Loss

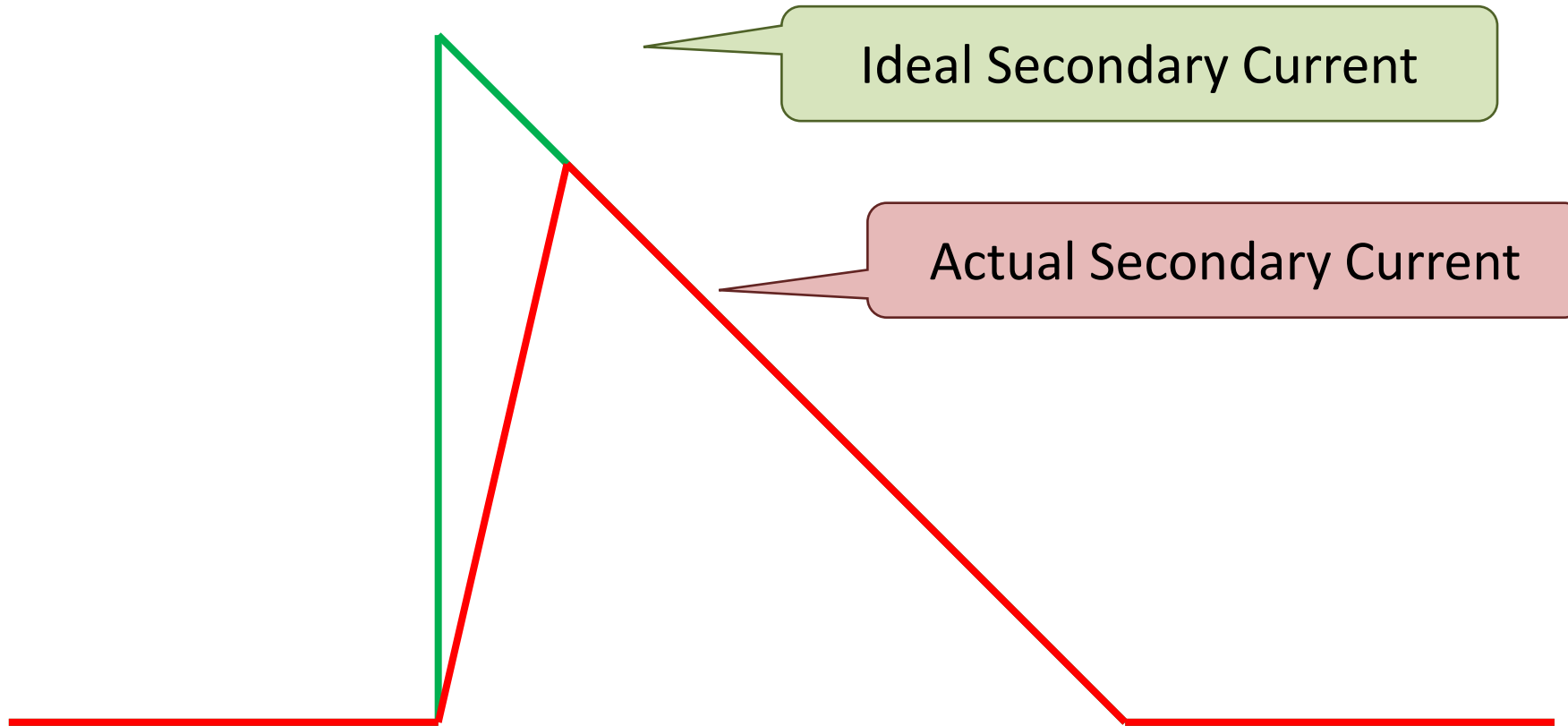

Leakage Loss

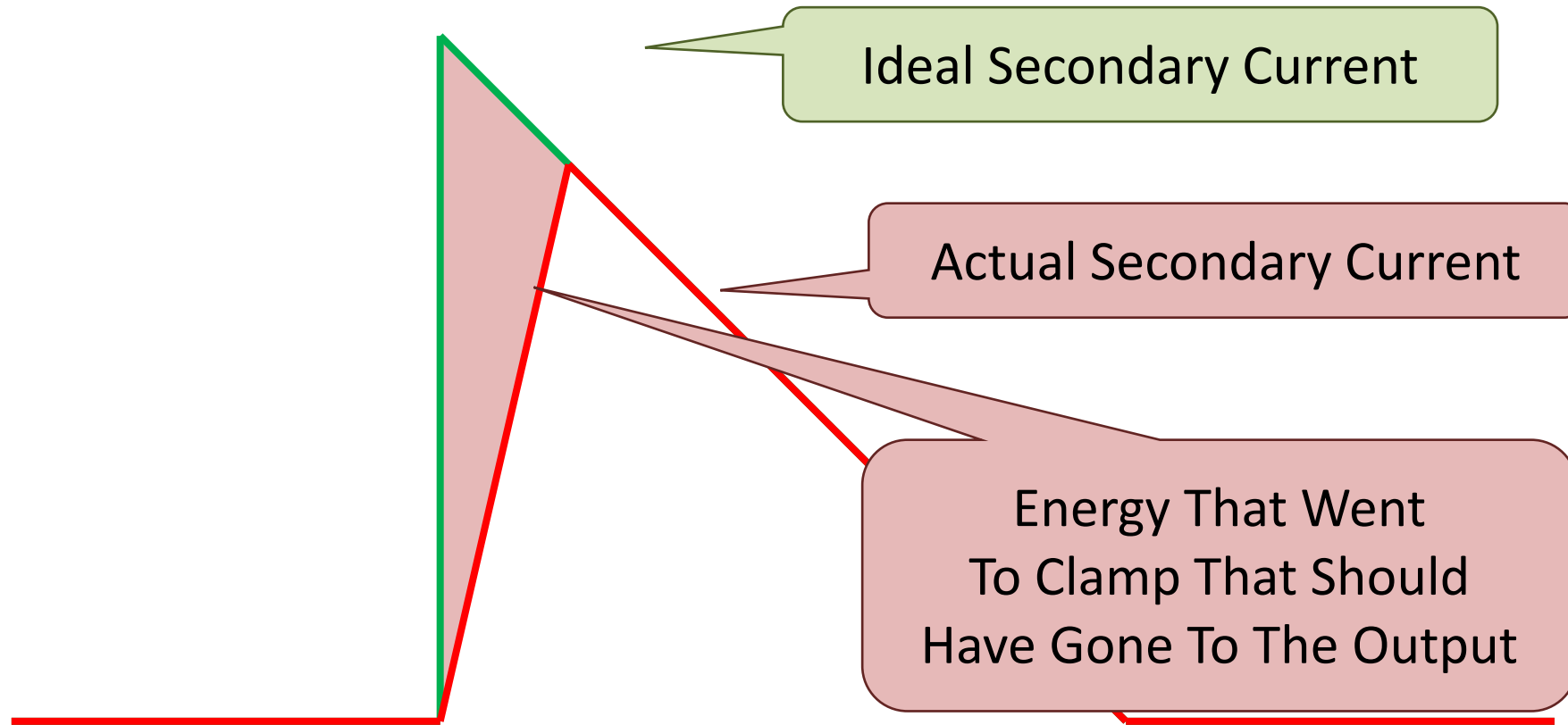

Leakage Loss

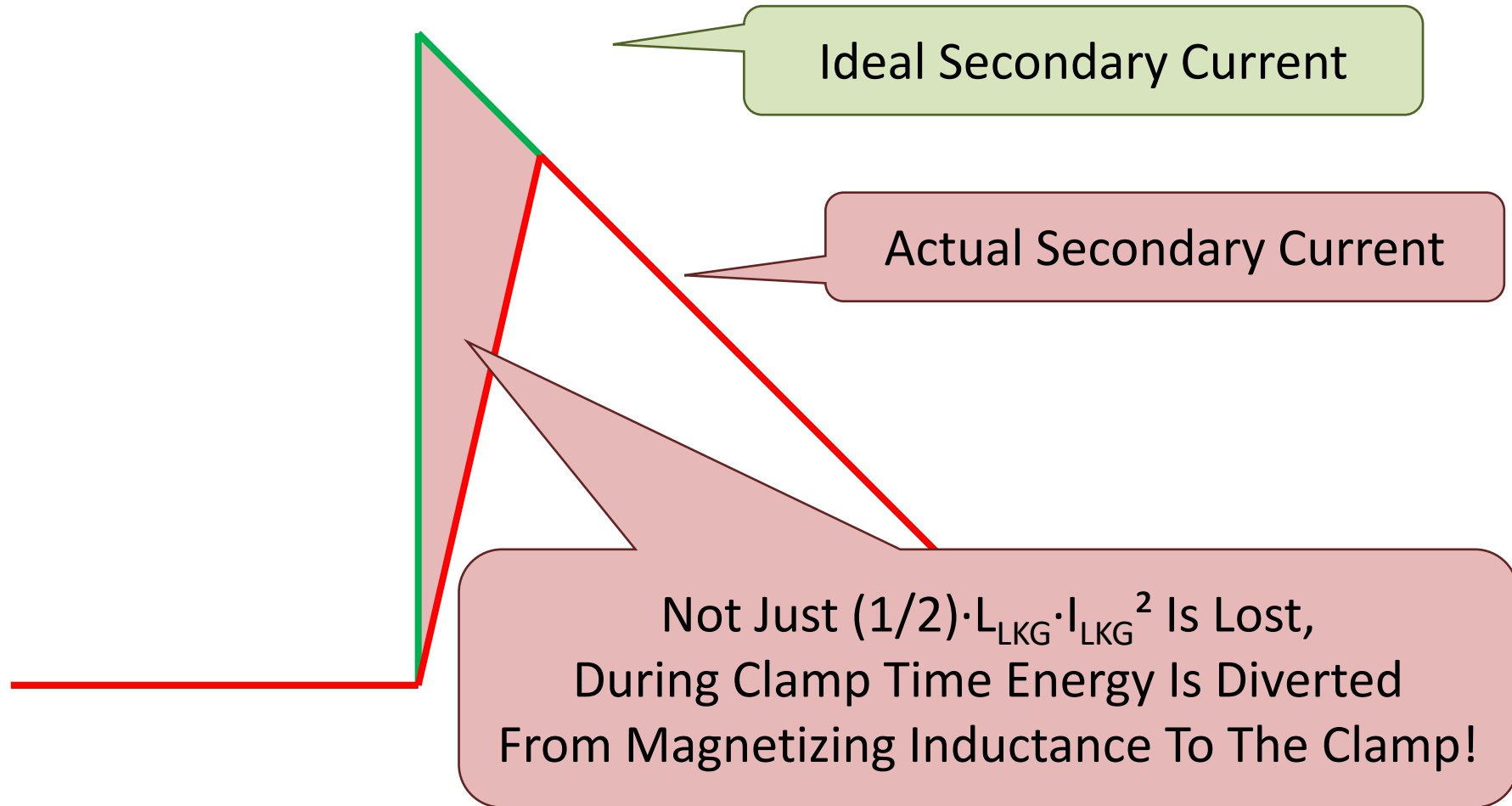

Clamp Loss

$$i_{LKG}(t=0) = i_{MAG}(t=0) = I_{PK}$$

$$\frac{di_{LKG}(t)}{dt} = \frac{V_{CLAMP} - V_{RESET}}{L_{LKG}} \quad V_{RESET} = \frac{N_P}{N_S} \cdot (V_{OUT} + V_{DIODE})$$

$$i_{LKG}(t) = I_{PK} - \left(\frac{V_{CLAMP} - V_{RESET}}{L_{LKG}} \right) \cdot t$$

Clamp Loss

$$i_{LKG}(T_{LKG}) = 0$$

At End Of Clamp Interval,
Leakage Inductance Current = 0

$$I_{PK} - \left(\frac{V_{CLAMP} - V_{RESET}}{L_{LKG}} \right) \cdot T_{LKG} = 0$$

$$T_{LKG} = \frac{I_{PK}}{\frac{V_{CLAMP} - V_{RESET}}{L_{LKG}}} = \frac{L_{LKG} \cdot I_{PK}}{V_{CLAMP} - V_{RESET}}$$

Clamp Loss

$$i_{CLAMP}(t) = i_{LKG}(t)$$

$$p_{CLAMP}(t) = v_{CLAMP}(t) \cdot i_{CLAMP}(t) \approx V_{CLAMP} \cdot i_{CLAMP}(t)$$

$$\begin{aligned} P_{CLAMP} &= \frac{1}{T_{SW}} \cdot \int_0^{T_{SW}} p_{CLAMP}(t) dt = \frac{1}{T_{SW}} \cdot \int_0^{T_{LKG}} p_{CLAMP}(t) dt \\ &= \frac{1}{T_{SW}} \cdot \int_0^{T_{LKG}} (V_{CLAMP} \cdot i_{CLAMP}(t)) dt = \frac{V_{CLAMP}}{T_{SW}} \cdot \int_0^{T_{LKG}} i_{CLAMP}(t) dt \end{aligned}$$

Clamp Loss

$$\begin{aligned} P_{CLAMP} &= \frac{V_{CLAMP}}{T_{SW}} \cdot \int_0^{T_{LKG}} \left(I_{PK} - \left(\frac{V_{CLAMP} - V_{RESET}}{L_{LKG}} \right) \cdot t \right) dt \\ &= \frac{V_{CLAMP} \cdot I_{PK} \cdot T_{LKG}}{T_{SW}} - \frac{V_{CLAMP}}{T_{SW}} \cdot \int_0^{T_{LKG}} \left(\frac{V_{CLAMP} - V_{RESET}}{L_{LKG}} \right) \cdot t dt \\ &= \frac{V_{CLAMP} \cdot I_{PK} \cdot T_{LKG}}{T_{SW}} - \frac{V_{CLAMP}}{T_{SW}} \cdot \left(\frac{V_{CLAMP} - V_{RESET}}{L_{LKG}} \right) \cdot \int_0^{T_{LKG}} t dt \\ &= \frac{V_{CLAMP} \cdot I_{PK} \cdot T_{LKG}}{T_{SW}} - \frac{V_{CLAMP}}{T_{SW}} \cdot \left(\frac{V_{CLAMP} - V_{RESET}}{L_{LKG}} \right) \cdot \frac{T_{LKG}^2}{2} \end{aligned}$$

Clamp Loss

$$\begin{aligned}
 P_{CLAMP} &= \frac{V_{CLAMP} \cdot I_{PK} \cdot T_{LKG}}{T_{SW}} - \frac{1}{2} \cdot \frac{V_{CLAMP}}{T_{SW}} \cdot \left(\frac{V_{CLAMP} - V_{RESET}}{L_{LKG}} \right) \cdot \left(\frac{L_{LKG} \cdot I_{PK}}{V_{CLAMP} - V_{RESET}} \right)^2 \\
 &= \frac{V_{CLAMP} \cdot I_{PK}}{T_{SW}} \cdot \frac{L_{LKG} \cdot I_{PK}}{V_{CLAMP} - V_{RESET}} - \frac{1}{2} \cdot \frac{V_{CLAMP}}{T_{SW}} \cdot \frac{L_{LKG} \cdot I_{PK}^2}{V_{CLAMP} - V_{RESET}} \\
 &= \frac{V_{CLAMP}}{T_{SW}} \cdot \frac{L_{LKG} \cdot I_{PK}^2}{V_{CLAMP} - V_{RESET}} - \frac{1}{2} \cdot \frac{V_{CLAMP}}{T_{SW}} \cdot \frac{L_{LKG} \cdot I_{PK}^2}{V_{CLAMP} - V_{RESET}} \\
 &= \frac{1}{2} \cdot \frac{V_{CLAMP}}{T_{SW}} \cdot \frac{L_{LKG} \cdot I_{PK}^2}{V_{CLAMP} - V_{RESET}} \\
 P_{CLAMP} &= \frac{V_{CLAMP}}{V_{CLAMP} - V_{RESET}} \cdot \frac{1}{2} \cdot L_{LKG} \cdot I_{PK}^2 \cdot F_{SW}
 \end{aligned}$$

Clamp Loss

$$P_{CLAMP} = \frac{V_{CLAMP}}{V_{CLAMP} - V_{RESET}} \cdot \frac{1}{2} \cdot L_{LKG} \cdot I_{PK}^2 \cdot F_{SW}$$
$$= \frac{V_{CLAMP}}{V_{CLAMP} - V_{RESET}} \cdot E_{LKG} \cdot F_{SW}$$

Energy
Stored In
Leakage Inductance


Clamp Loss

$$P_{CLAMP} = \frac{V_{CLAMP}}{V_{CLAMP} - V_{RESET}} \cdot \frac{1}{2} \cdot L_{LKG} \cdot I_{PK}^2 \cdot F_{SW}$$
$$= \frac{V_{CLAMP}}{V_{CLAMP} - V_{RESET}} \cdot E_{LKG} \cdot F_{SW}$$


Loss
Multiplier!

Energy
Stored In The
Leakage Inductance


Clamp Loss

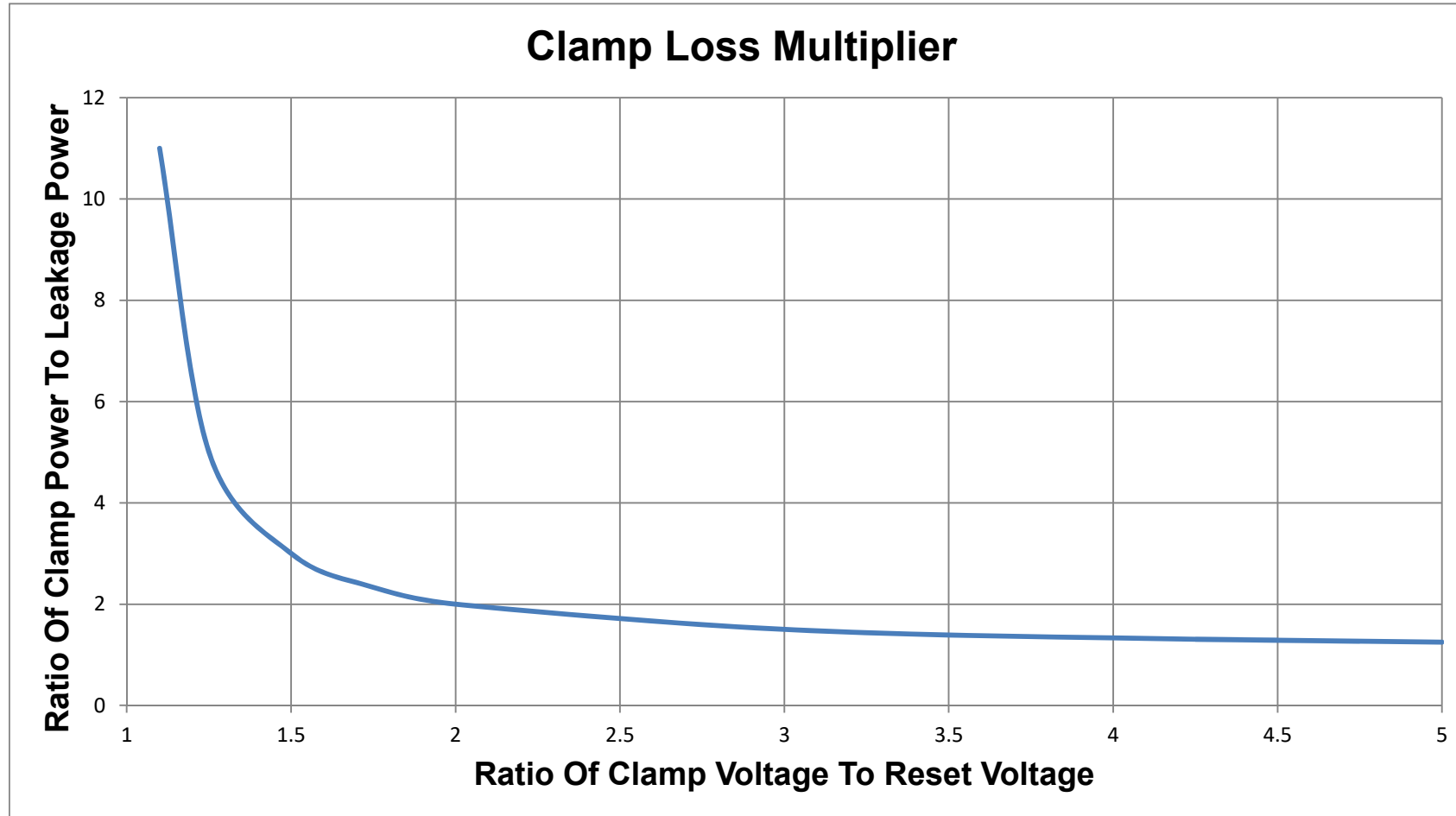

Clamp Loss

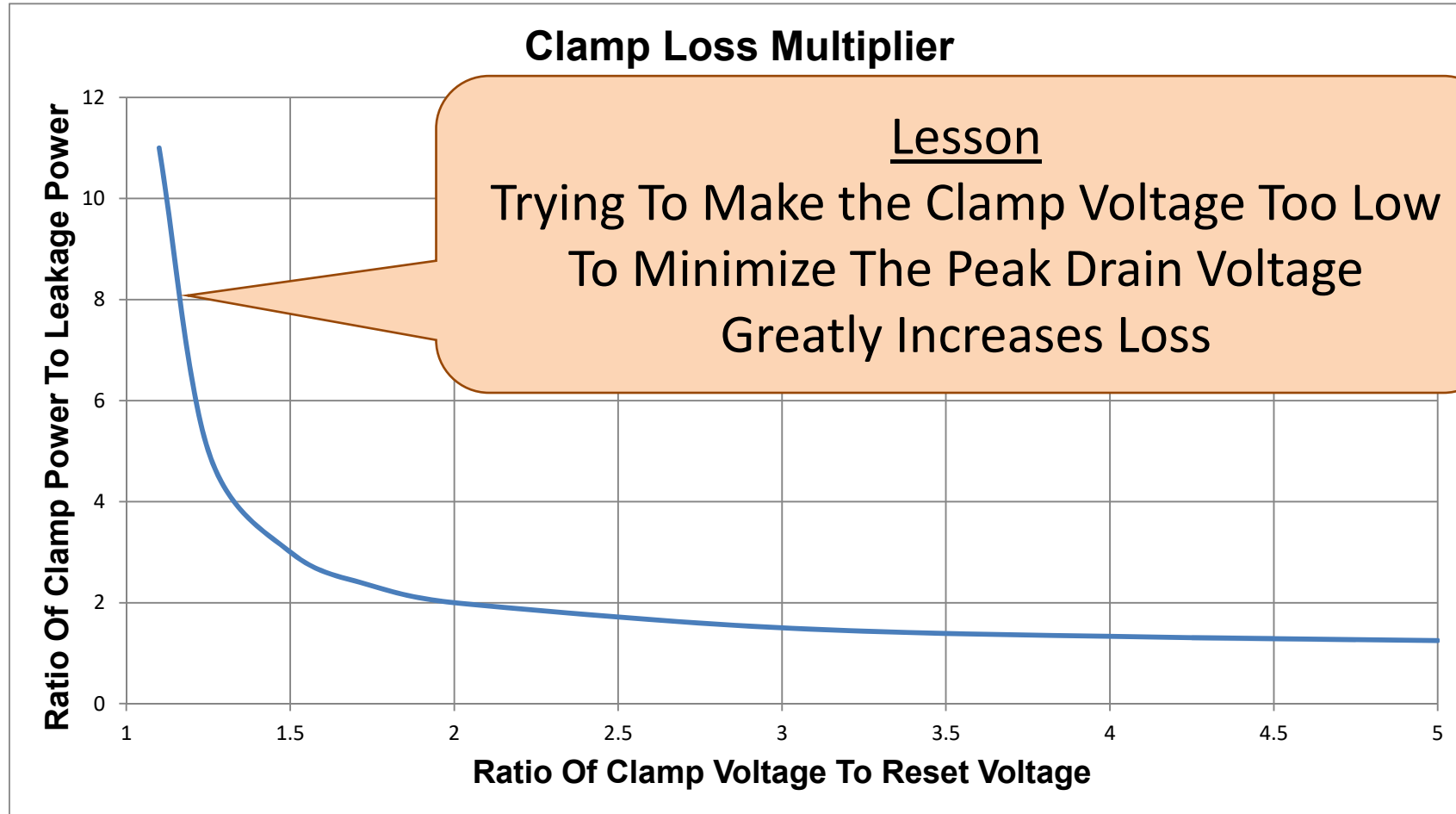


Clamp Diode Forward Recovery

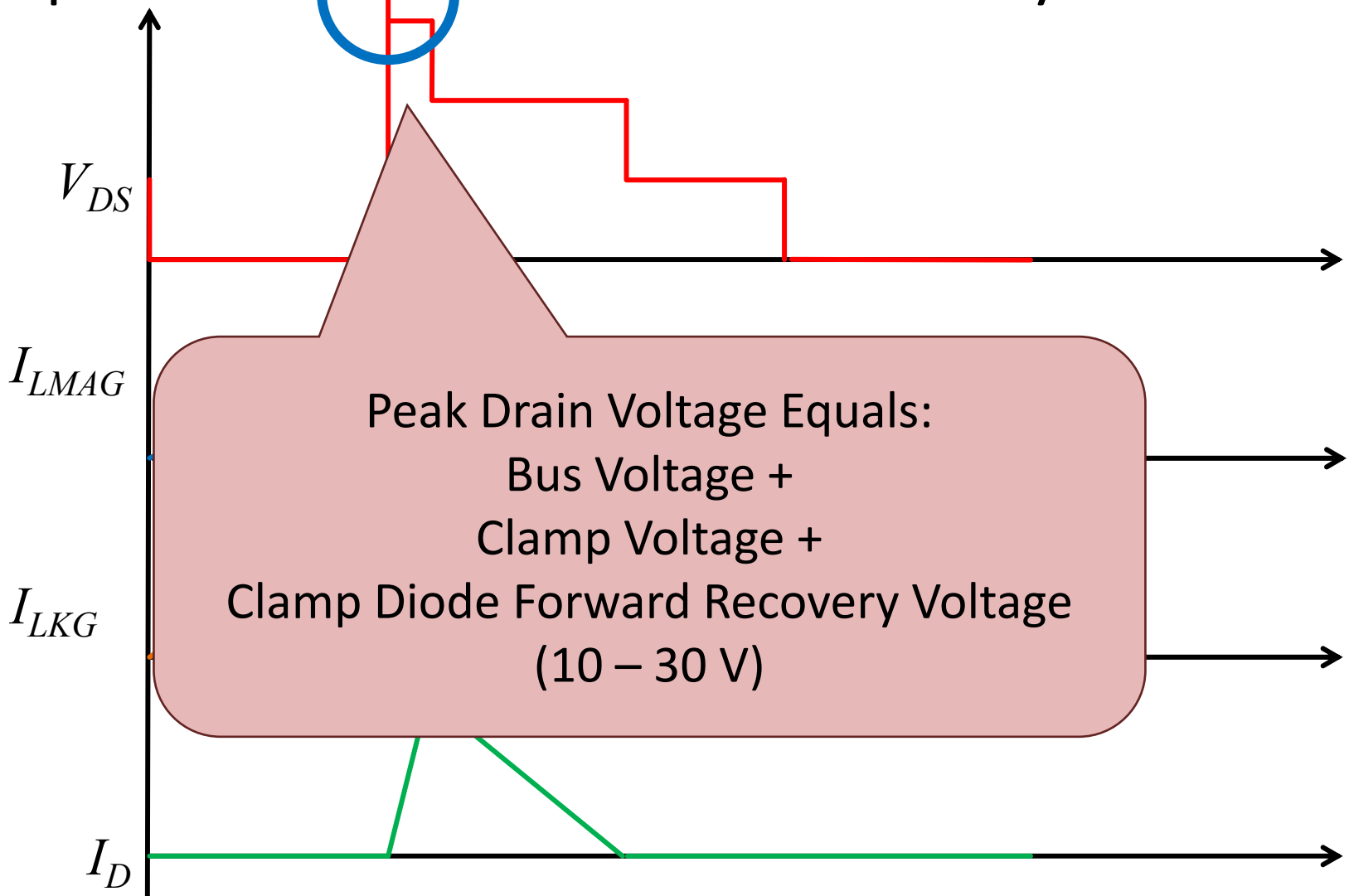


DCM Reset Time

DCM Reset Time

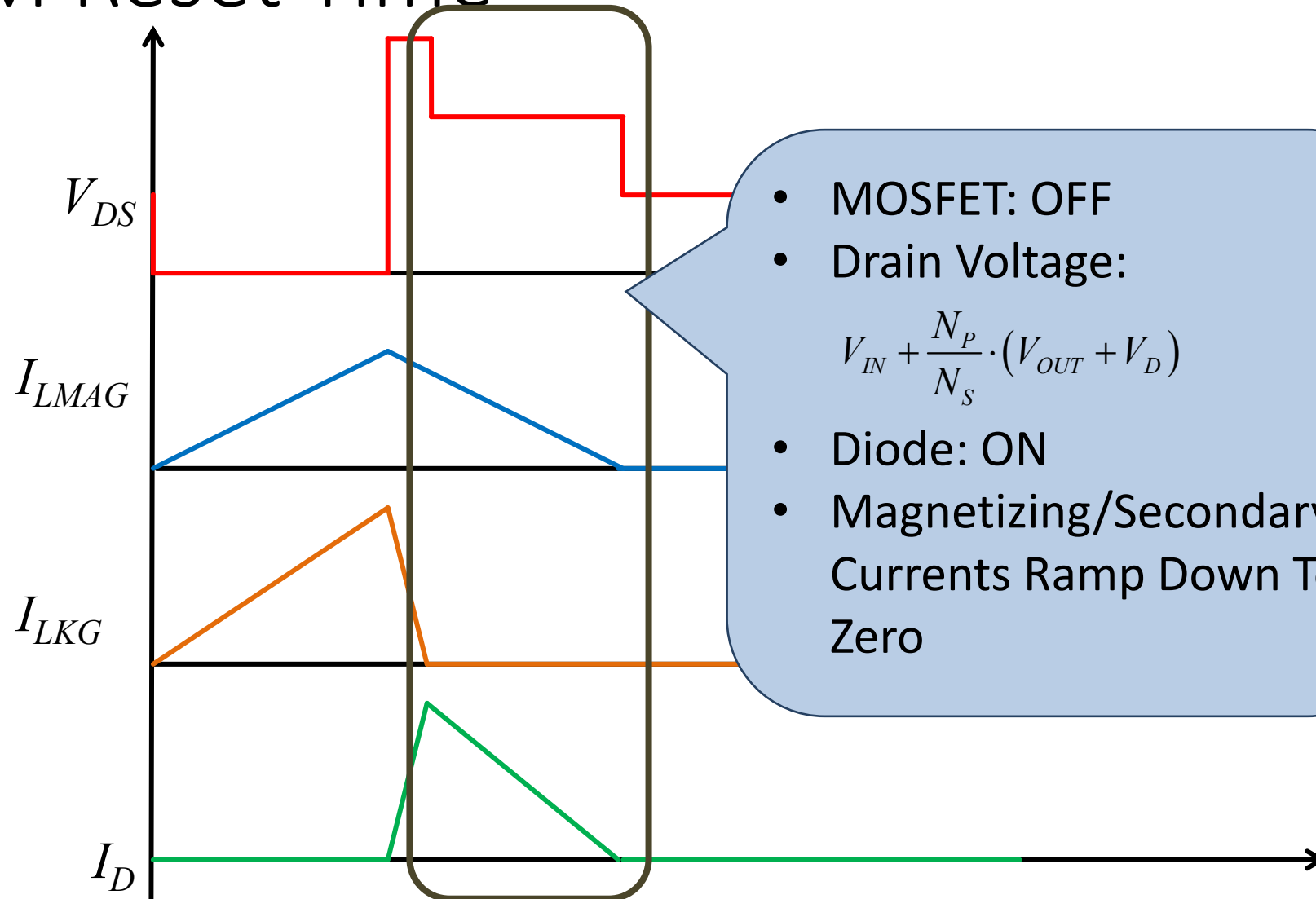


- MOSFET: OFF
- Drain Voltage:
$$V_{IN} + \frac{N_P}{N_S} \cdot (V_{OUT} + V_D)$$
- Diode: ON
- Magnetizing/Secondary Currents Ramp Down To Zero

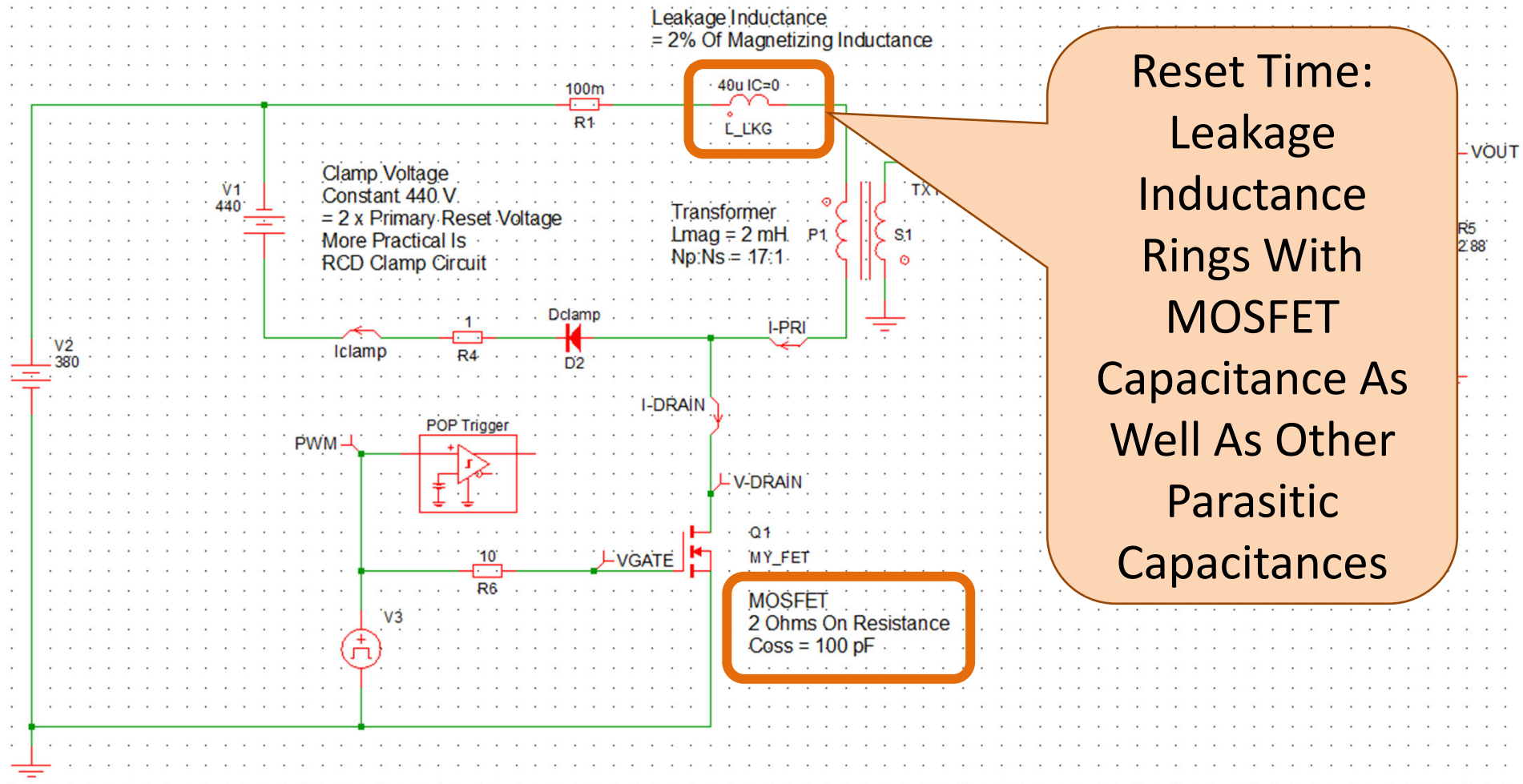Discontinuous Conduction Mode More Realistic Flyback Simulation




Reset Time:
Leakage
Inductance
Rings With
MOSFET
Capacitance As
Well As Other
Parasitic
Capacitances

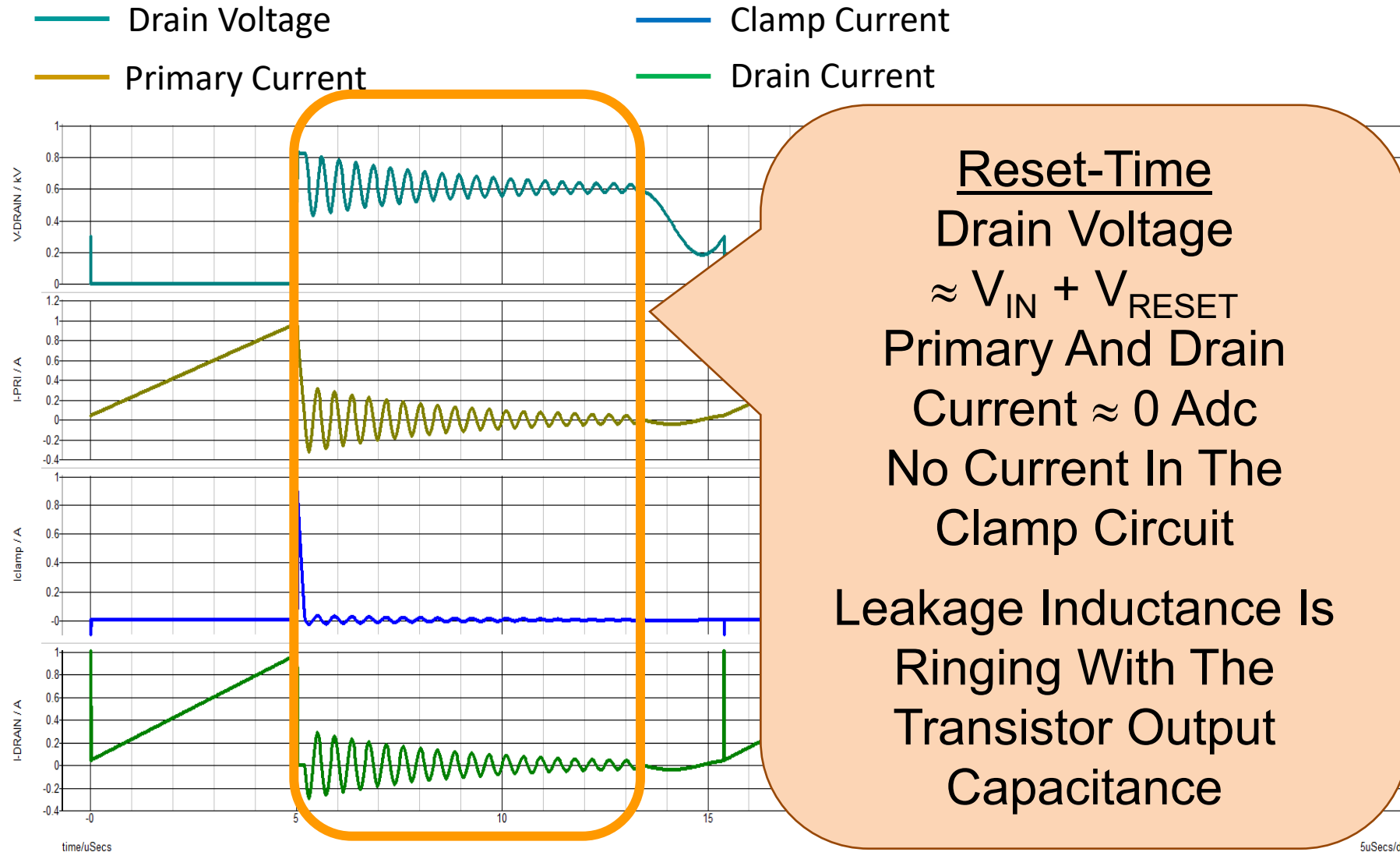Discontinuous Conduction Mode More Realistic Flyback Simulation




DCM Idle Time

DCM Idle Time

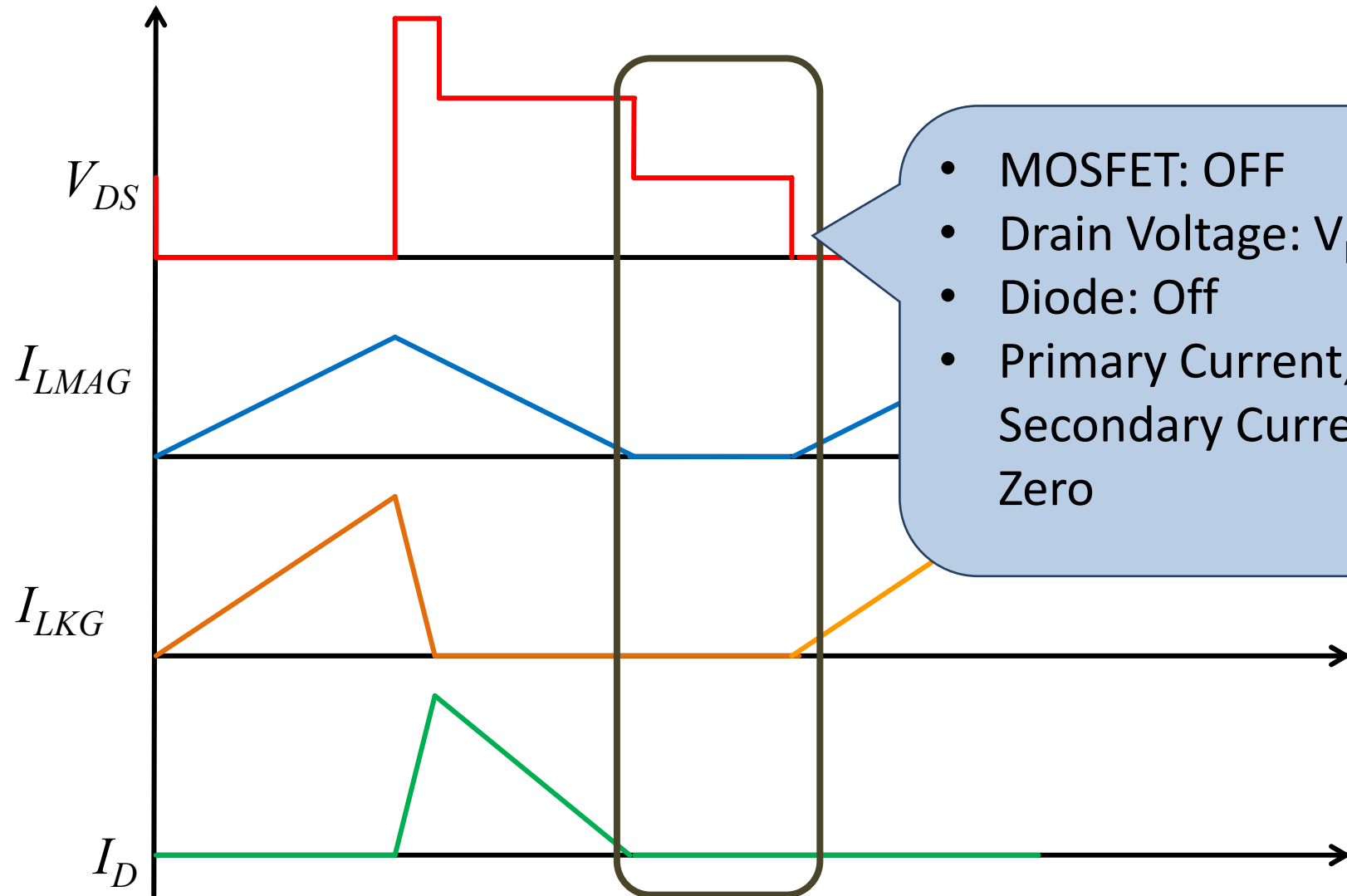


- MOSFET: OFF
- Drain Voltage: V_{IN}
- Diode: Off
- Primary Current, Secondary Current: Zero

DCM Idle Time

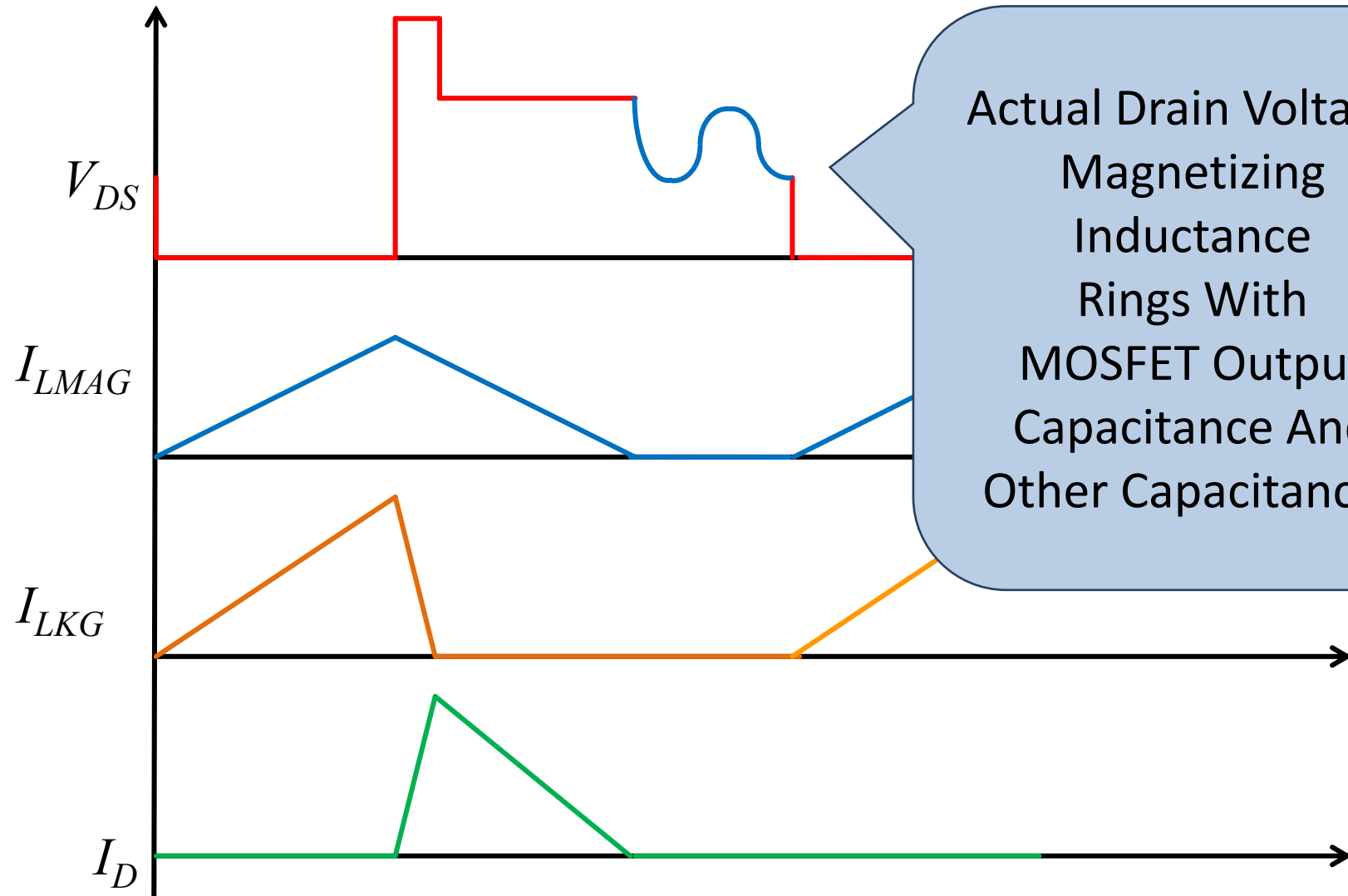


Actual Drain Voltage:
Magnetizing
Inductance
Rings With
MOSFET Output
Capacitance And
Other Capacitances

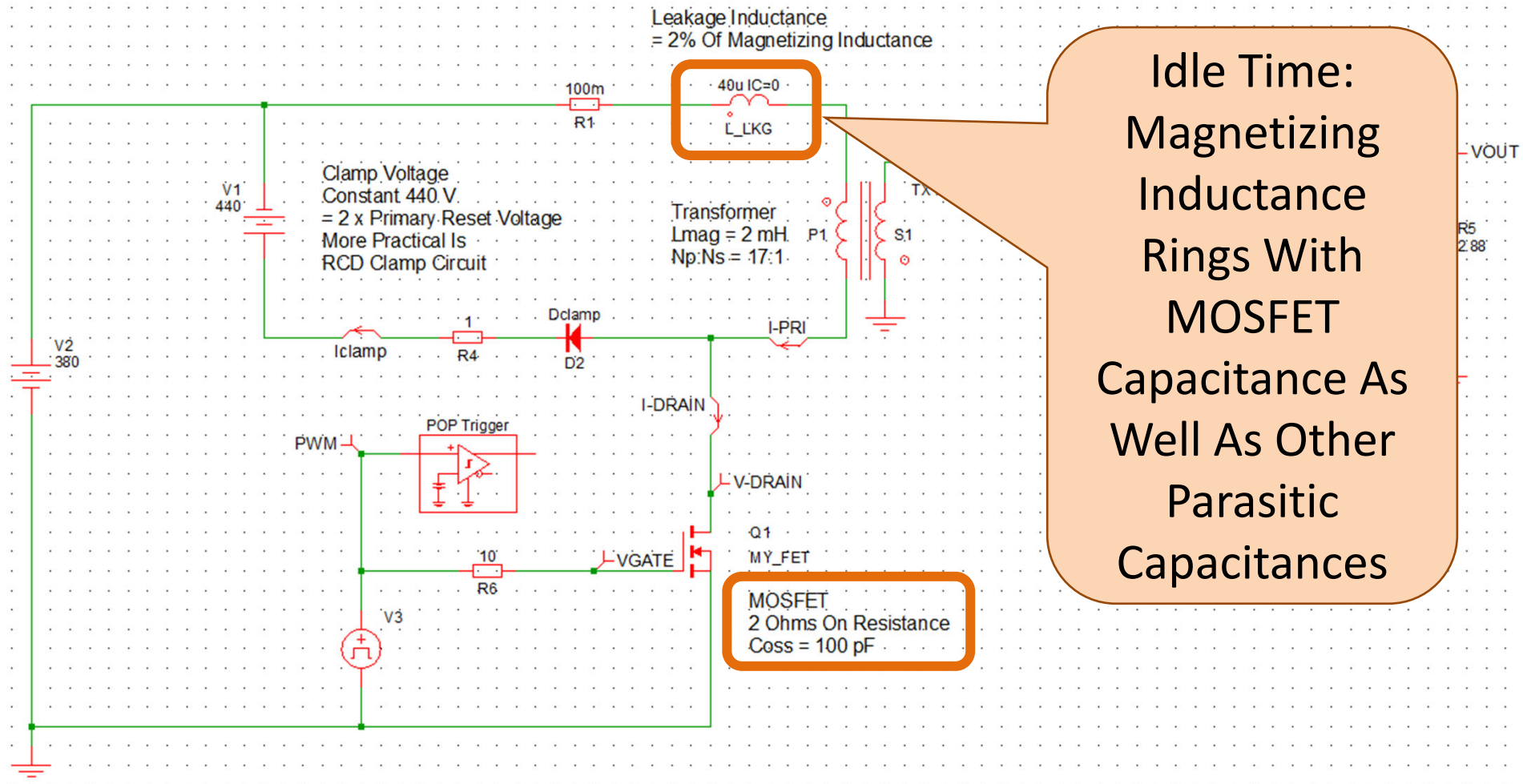Discontinuous Conduction Mode More Realistic Flyback Simulation



Idle Time:
Magnetizing
Inductance
Rings With
MOSFET
Capacitance As
Well As Other
Parasitic
Capacitances

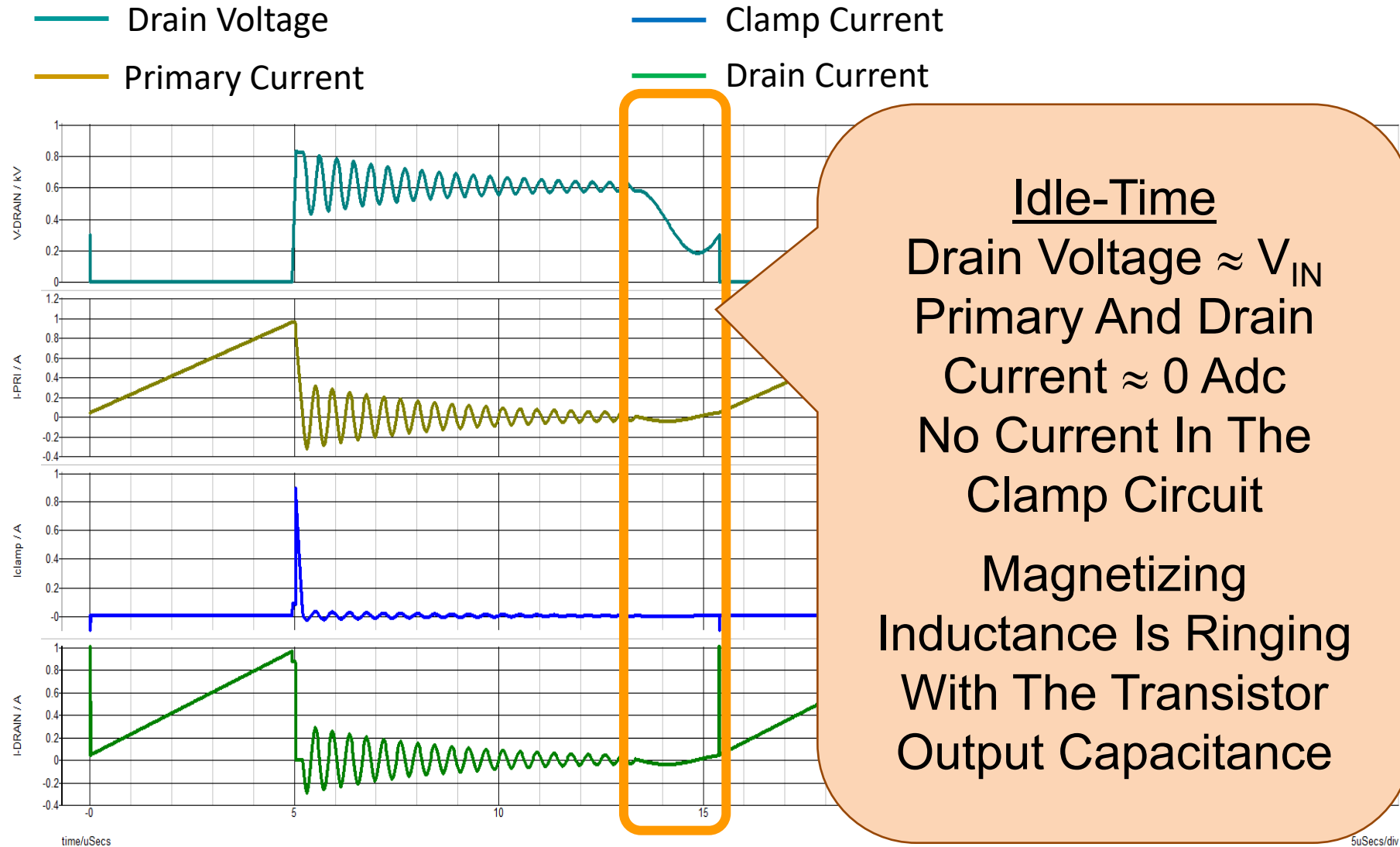Discontinuous Conduction Mode More Realistic Flyback Simulation



DM Flyback Deeper Dive Summary


- Leakage Inductance Can Be Minimized But Not Eliminated
- Leakage Inductance Has A Profound Affect On DCM Flyback
 - High Frequency Ringing Causing EMI Problems
 - High Voltage On The Main Switch
 - Increased Losses
- Clamp Circuits Generally Used To Limit Voltage
- Choice Of Clamp Voltage Has Large Affect On Clamp Losses

APPENDIX VIII.


Flyback Converter

Continuous Conduction Mode


Flyback Converter

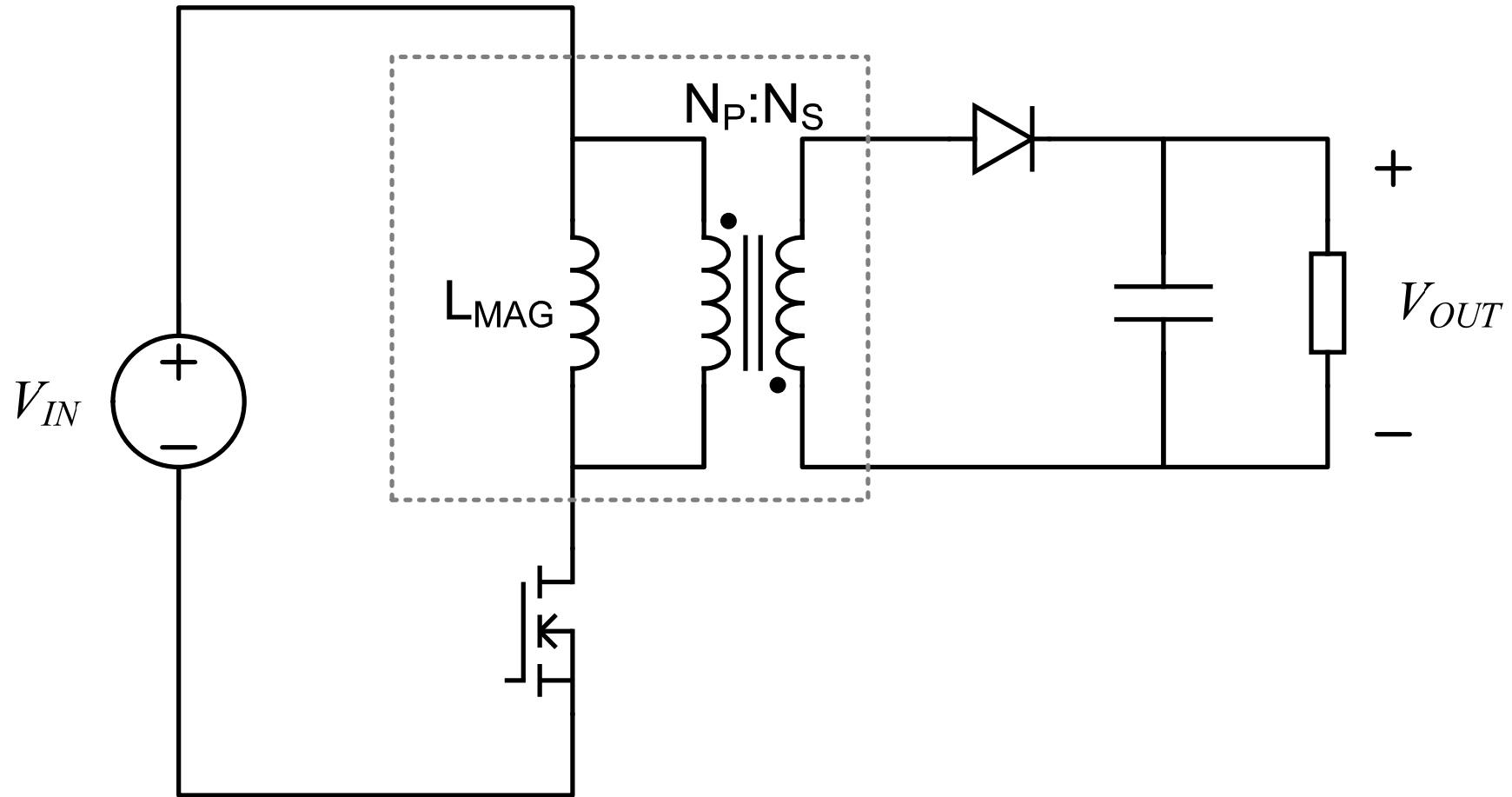


Flyback Converter On Time

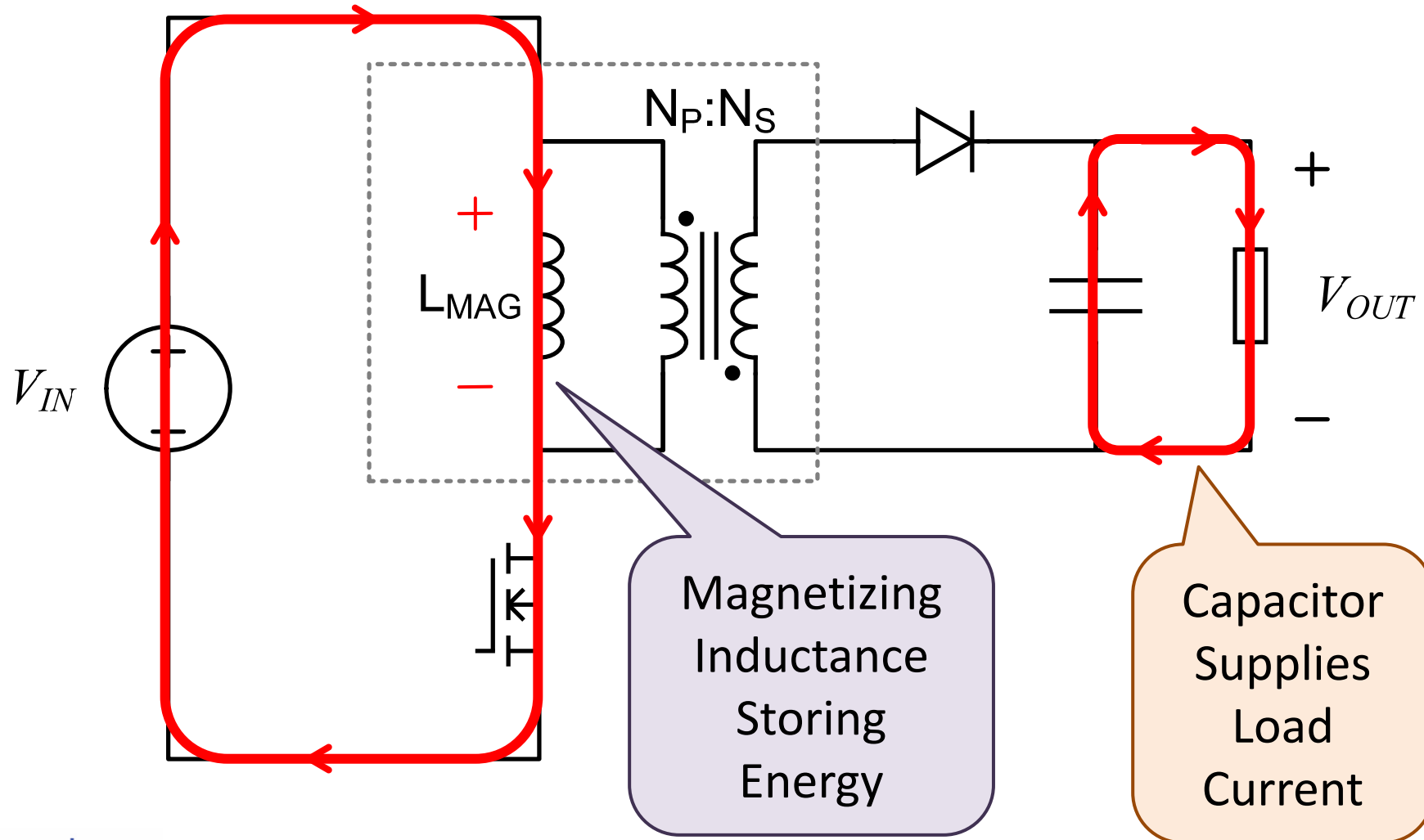

Flyback Converter Off Time

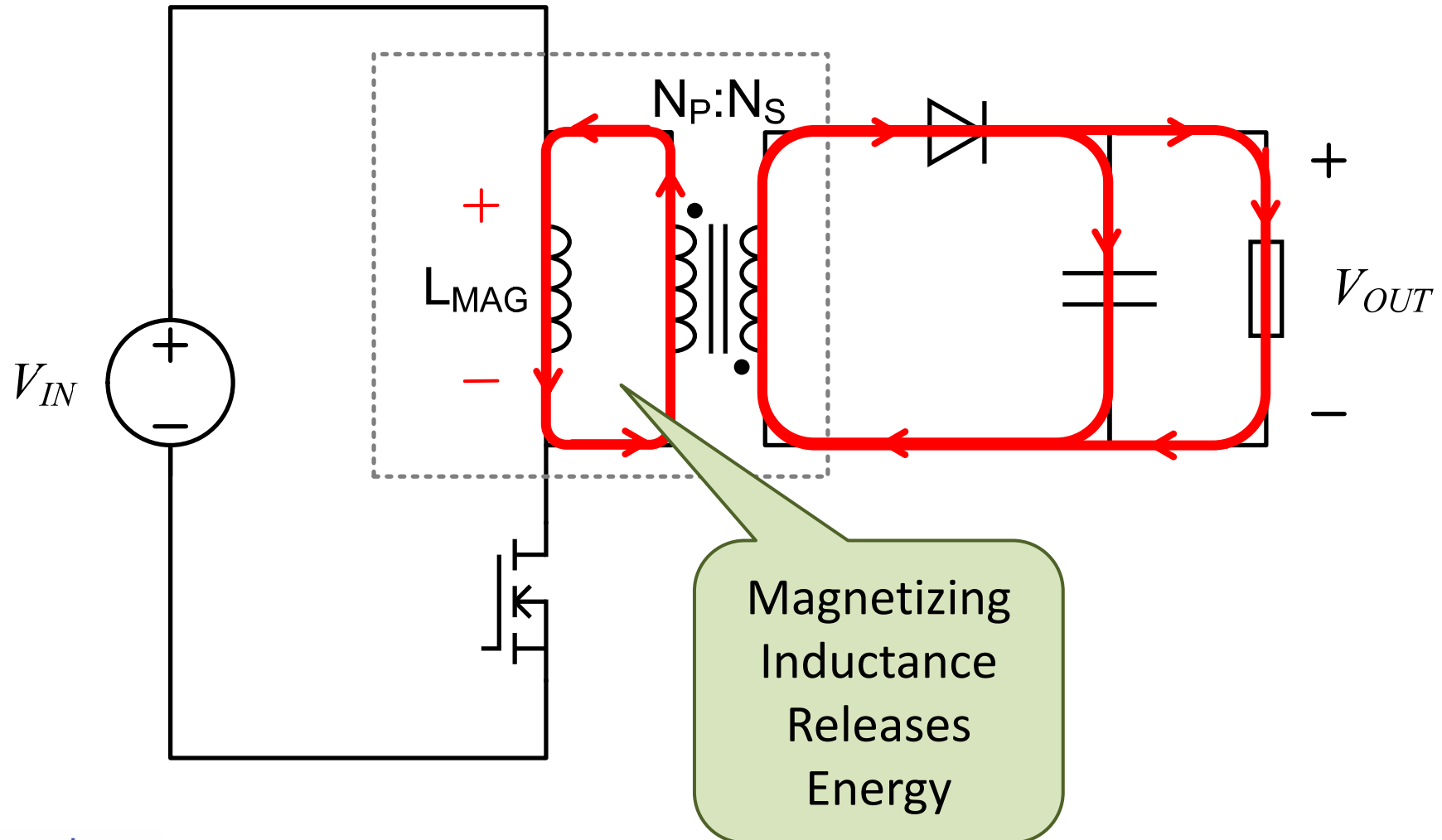

Flyback Converter Waveforms

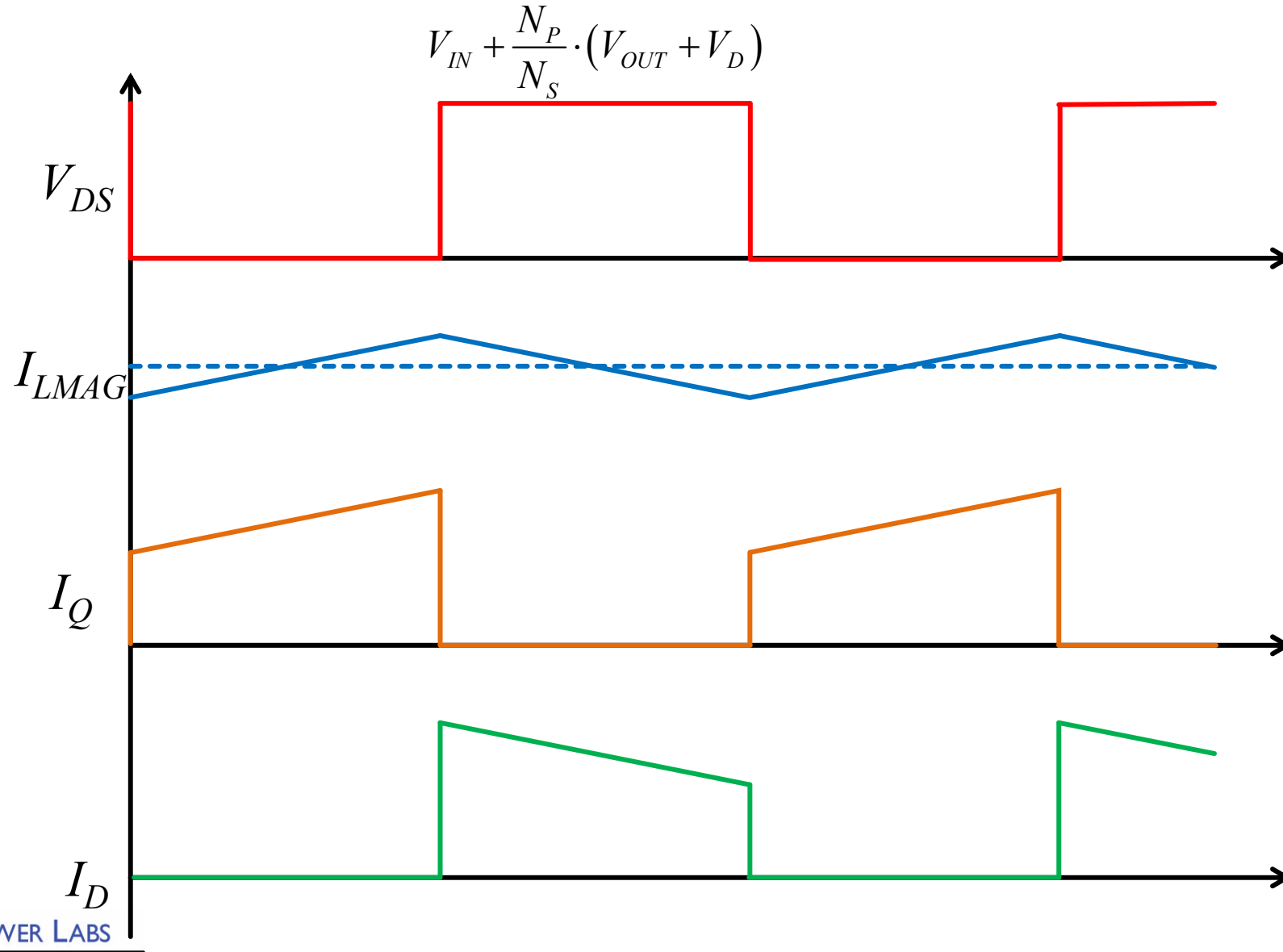

Flyback Conversion Ratio

$$V_{LMAG}(T_{ON}) \cdot T_{ON} + V_{LMAG}(T_{OFF}) \cdot T_{OFF} = 0$$

$$V_{IN} \cdot D + \left(-\frac{N_P}{N_S} \cdot (V_{OUT} + V_D) \right) \cdot D' = 0$$

$$D \cdot V_{IN} - D' \cdot \frac{N_P}{N_S} \cdot V_{OUT} - D' \cdot \frac{N_P}{N_S} \cdot V_D = 0$$

$$D' \cdot \frac{N_P}{N_S} \cdot V_{OUT} = D \cdot V_{IN} - D' \cdot \frac{N_P}{N_S} \cdot V_D$$

$$V_{OUT} = \frac{1}{D'} \cdot \frac{N_S}{N_P} \cdot \left(D \cdot V_{IN} - D' \cdot \frac{N_P}{N_S} \cdot V_D \right)$$

$$V_{OUT} = \frac{N_S}{N_P} \cdot \frac{D}{D'} \cdot V_{IN} - V_D$$

Not Quite
Ideal,
Diode
Voltage
Included

Flyback Conversion Ratio

$$V_{LMAG}(T_{ON}) \cdot T_{ON} + V_{LMAG}(T_{OFF}) \cdot T_{OFF} = 0$$

$$V_{IN} \cdot D + \left(-\frac{N_P}{N_S} \cdot (V_{OUT} + V_D) \right) \cdot D' = 0$$

$$D \cdot V_{IN} - D' \cdot \frac{N_P}{N_S} \cdot V_{OUT} - D' \cdot \frac{N_P}{N_S} \cdot V_D = 0$$

Standard Buck-Boost D/D' Conversion Ratio

Transformer Turns Ratio

$$V_{OUT} = \frac{N_S}{N_P} \cdot \left(\frac{D}{D'} \cdot V_{IN} - V_D \right)$$

$$V_{OUT} = \frac{N_S}{N_P} \cdot \frac{D}{D'} \cdot V_{IN} - V_D$$

Diode Voltage

Continuous Conduction Mode Flyback

Advantages

- Simpler Topology Than Forward Converter
- Can Process More Power Than DCM Flyback
- 100-250 W Possible

Disadvantages


- Control Characteristics Make It Hard To Stabilize And Get Good Transient Response
- Load Dependent “Right Half Plane” Zero In Control-To-Output Transfer Function

Appendix IX

Four Switch Noninverting Buck Boost Converter


Noninverting Buck-Boost Converter

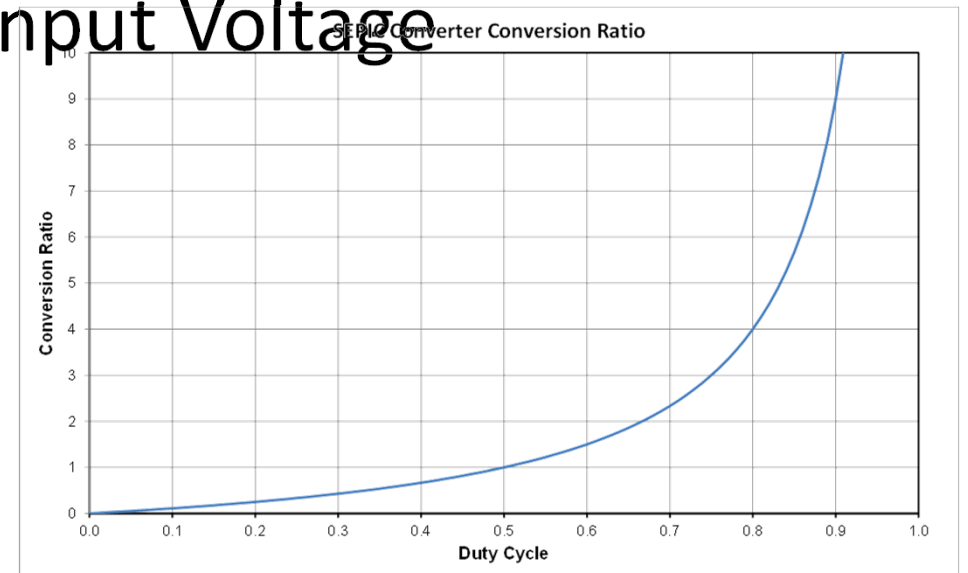- The SEPIC Is A Noninverting Boost Converter
 - Input And Output Voltage Both Positive
- The $D/(1 - D)$ Conversion Ratio Allows A Smooth And Continuous Variation Of The Output Voltage From Less Than To Greater Than The Input Voltage
- Another Noninverting Buck-Boost Converter Is The Four Switch Buck-Boost



Four-Switch Buck Boost

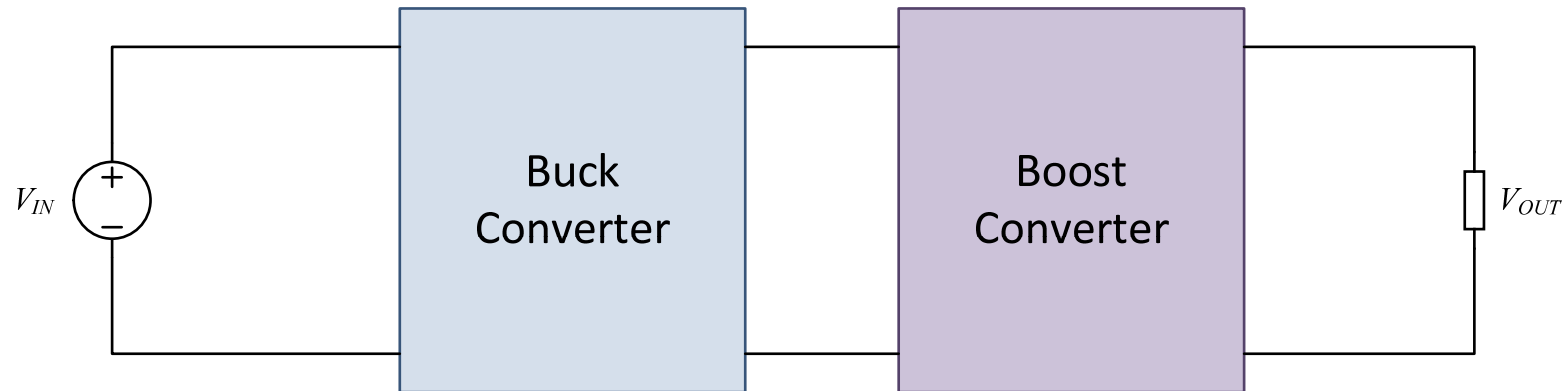
Consider The Cascade Of A Buck Converter And A Boost Converter




Conversion Ratio Is The Desired Noninverting Buck-Boost: $V_{OUT} = \frac{1}{1-D} \cdot D \cdot V_{IN}$

Four-Switch Buck Boost


Cascade Of Buck And Boost Converters

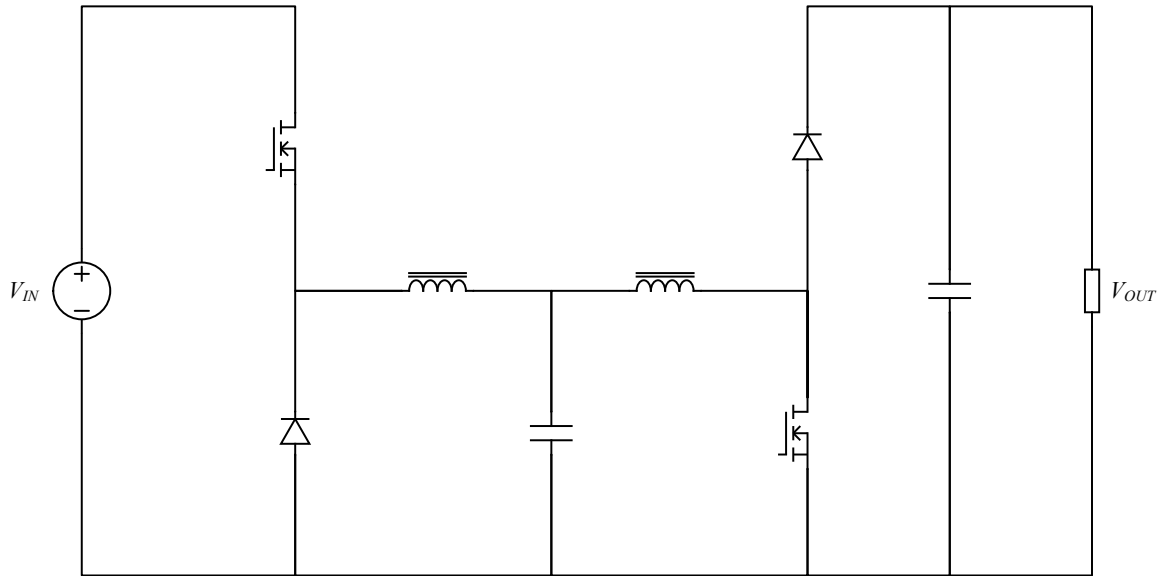

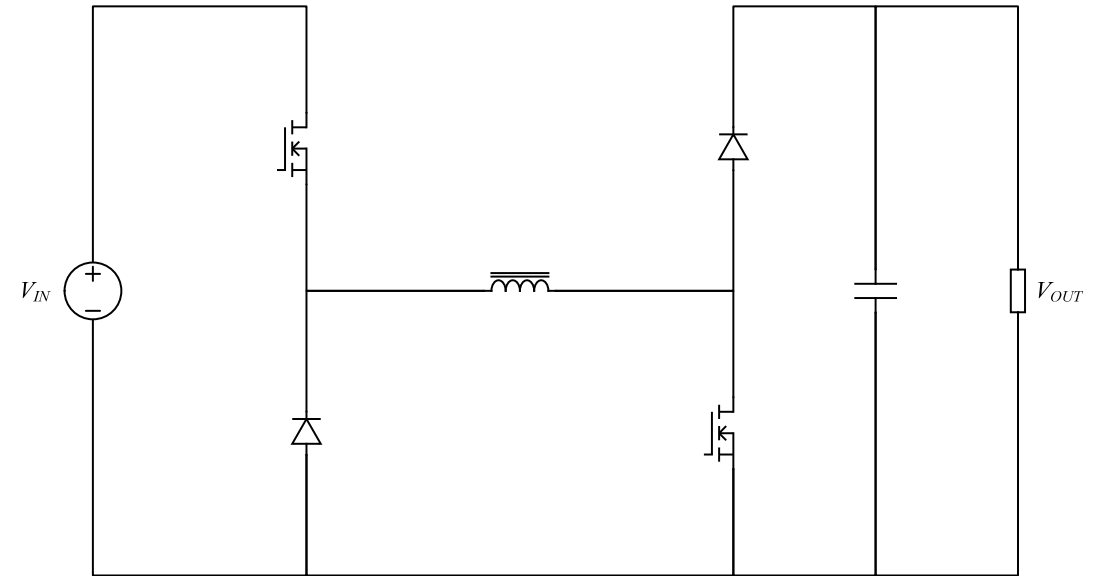
Simplify By Eliminating Common Capacitor
And One Inductor



Synchronous Four Switch Buck Boost

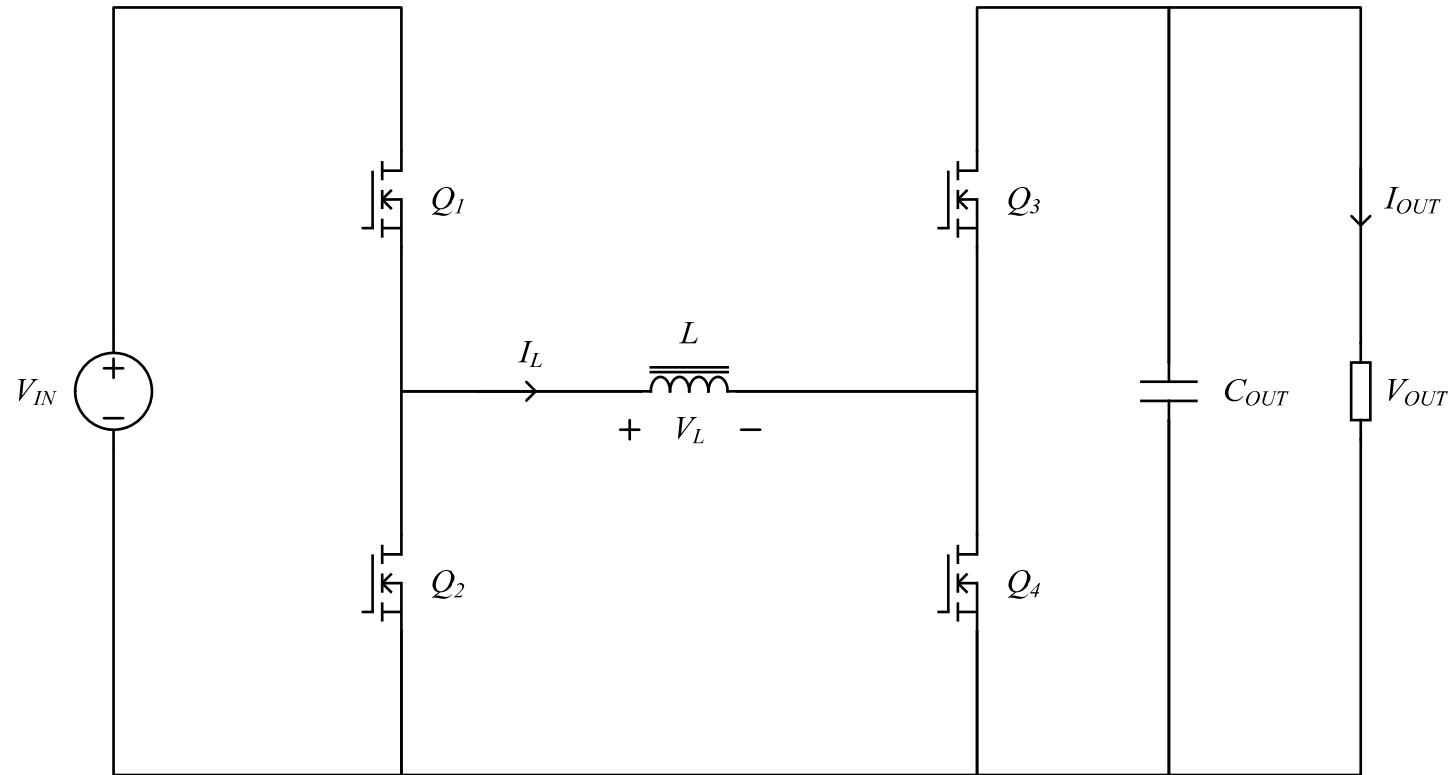


Synchronous Four Switch Buck Boost

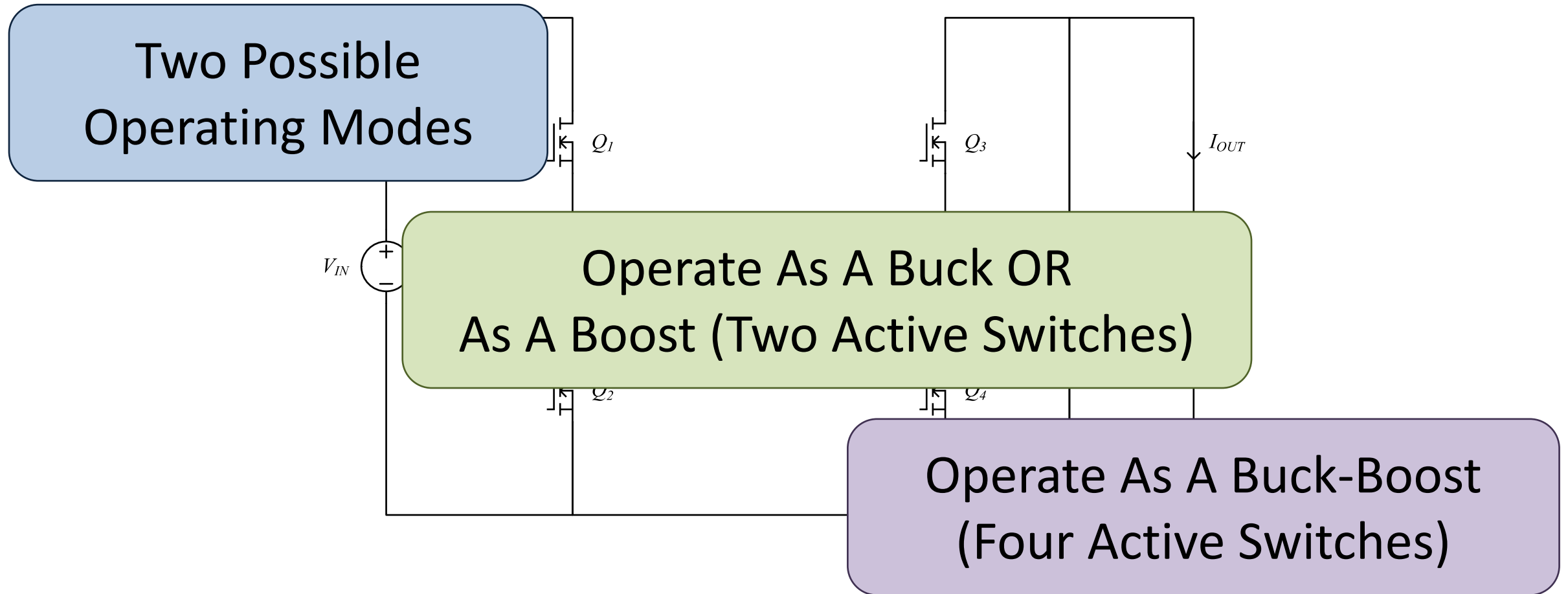


Synchronous Four Switch Buck-Boost

Operate As Either Buck OR Boost With Only Two Switches Active

Buck Mode

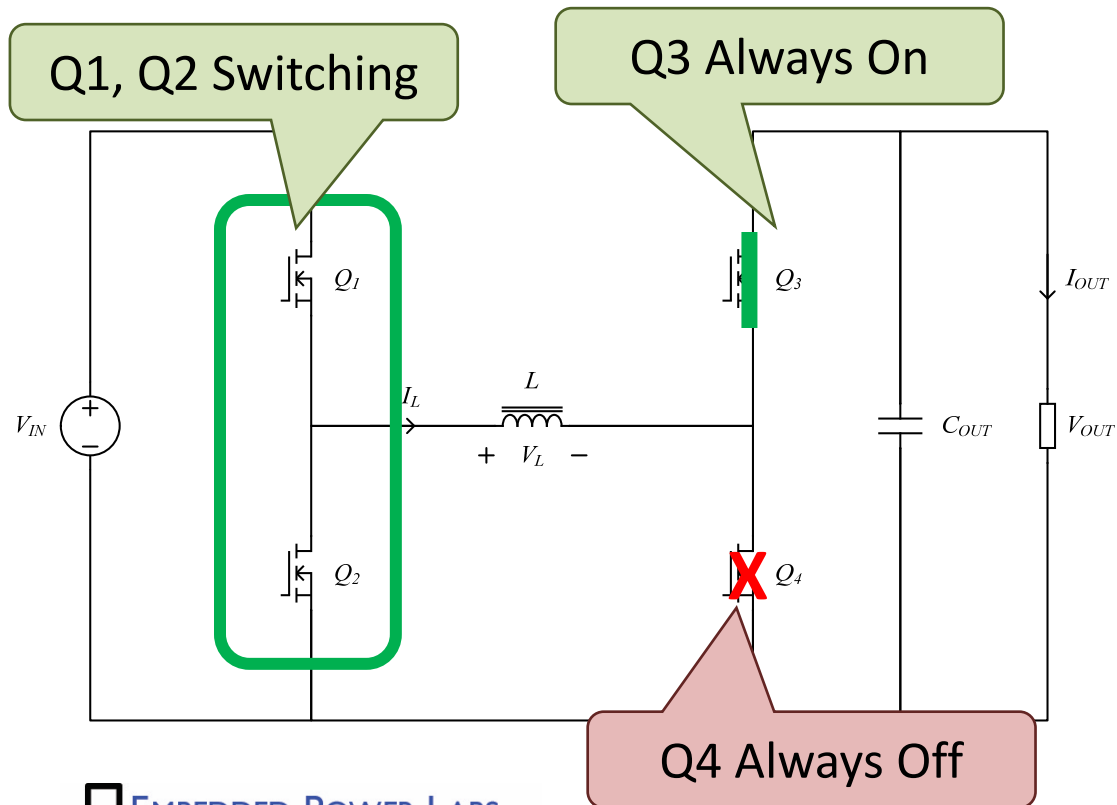


Boost Mode

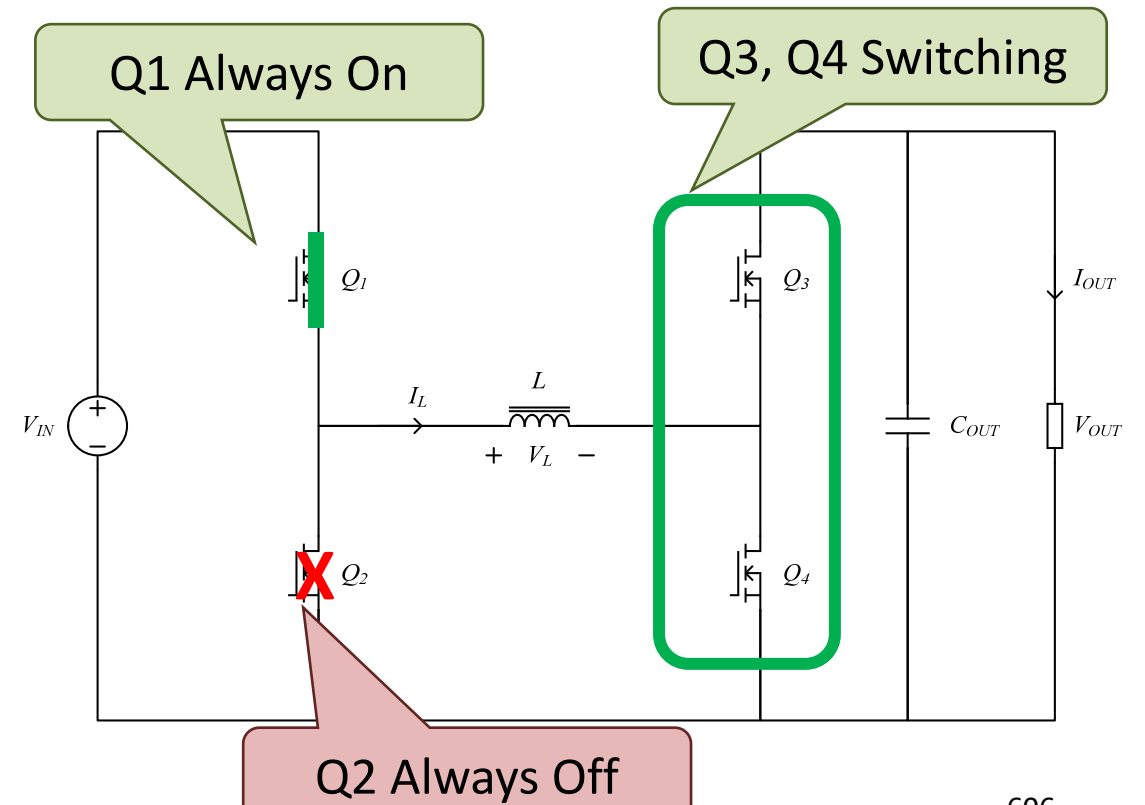

Four Active Switches Mode – On Time

Q1, Q4: On
Q2, Q3: Off

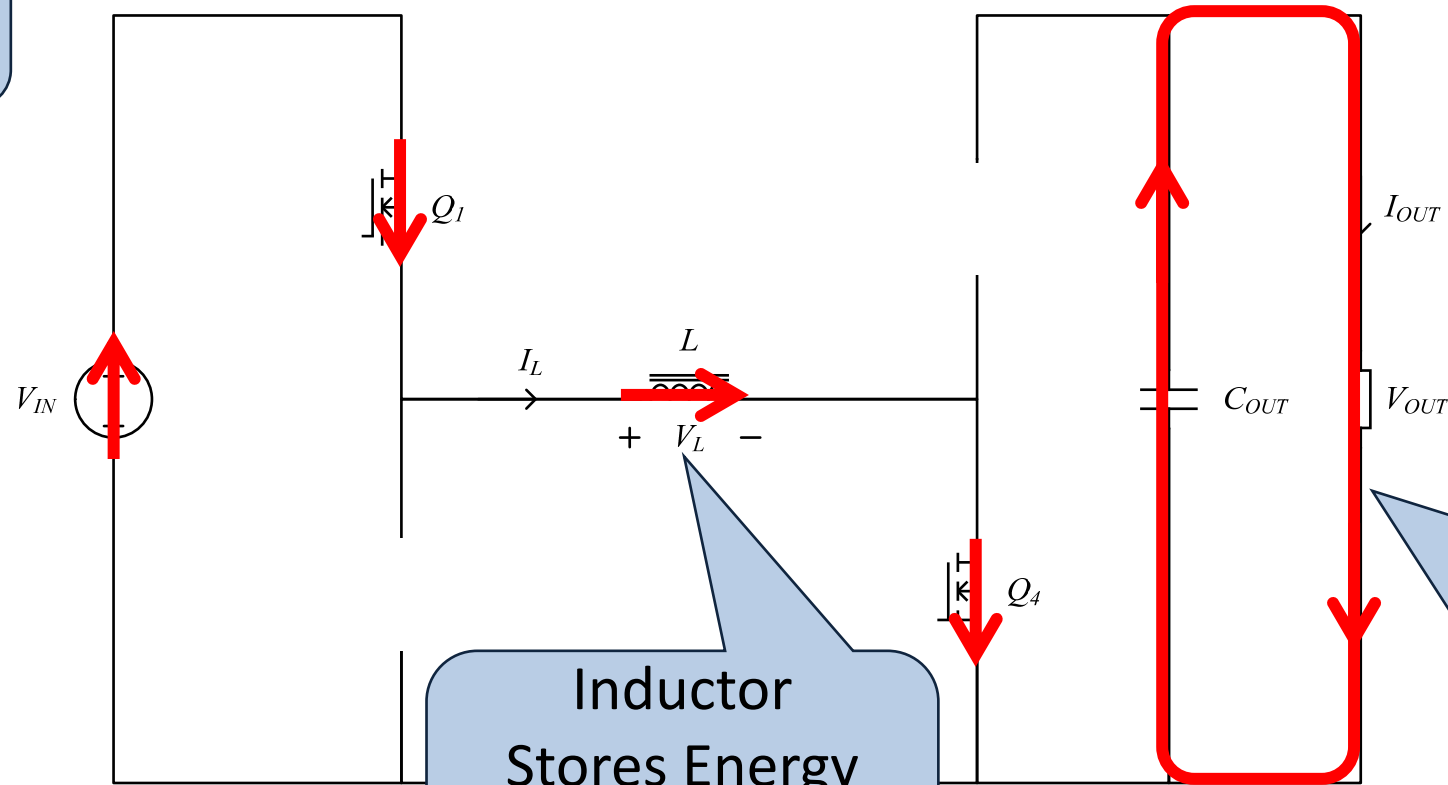


Inductor
Stores Energy
From Input
Supply

Capacitor
Supplies
Energy To
The Output

Four Active Switches Mode – Off Time


Q1, Q4: Off
Q2, Q3: On

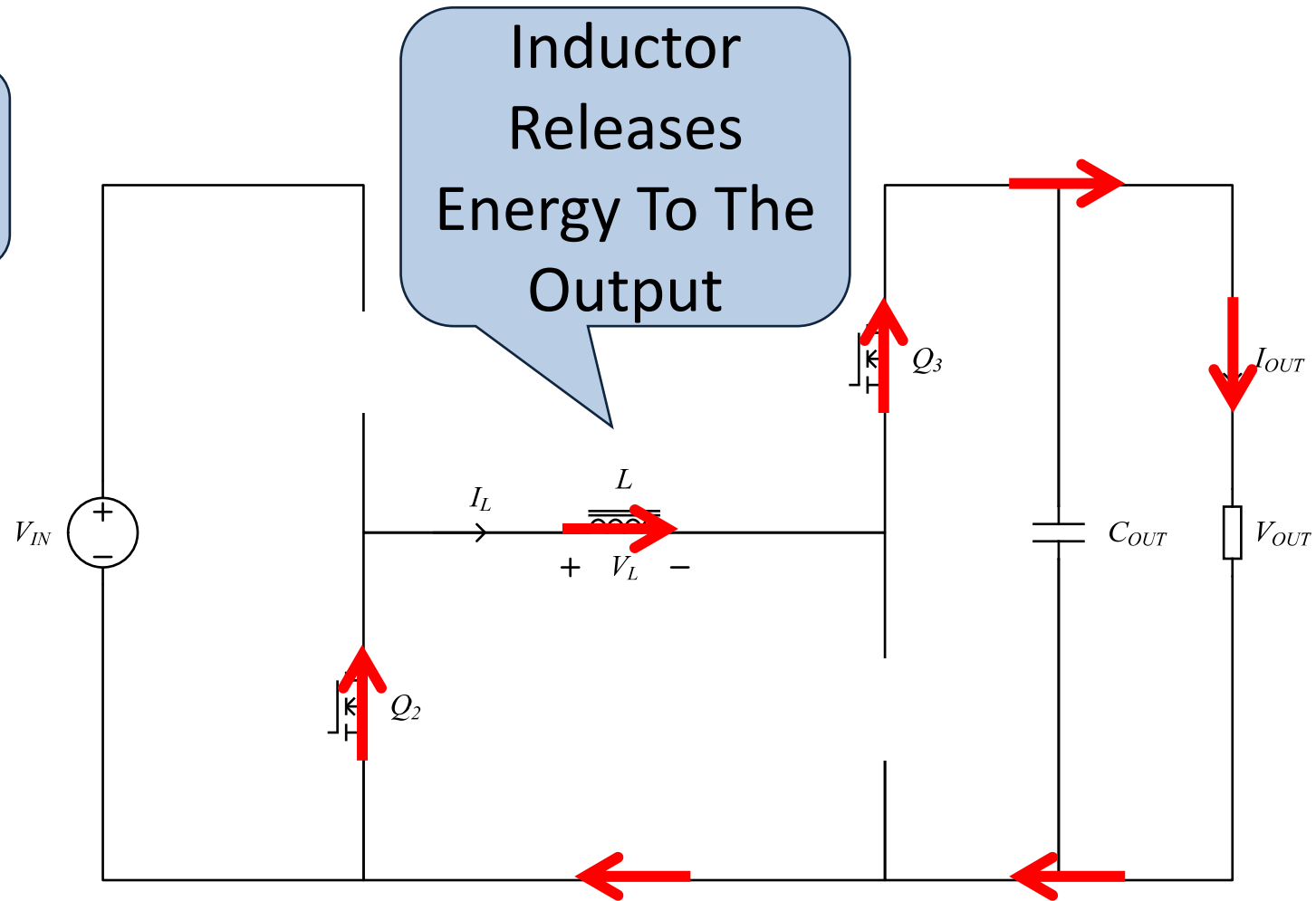

Four Active Switches Mode – Off Time


Q1, Q4: Off
Q2, Q3: On

Inductor
Releases
Energy To The
Output

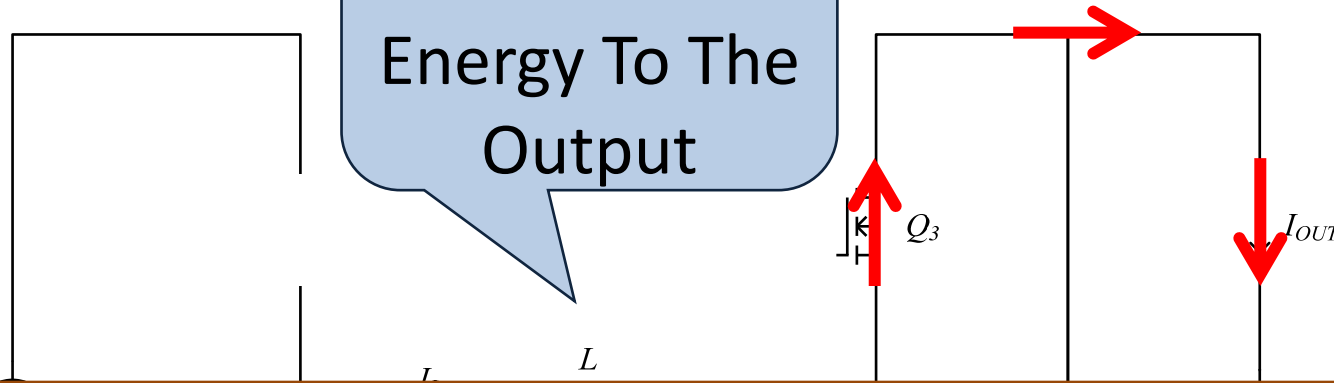

Note That Like The Inverting Buck-Boost
No Energy Is Transferred Directly From The Input To
Output During Either The On-Time Or Off-Time

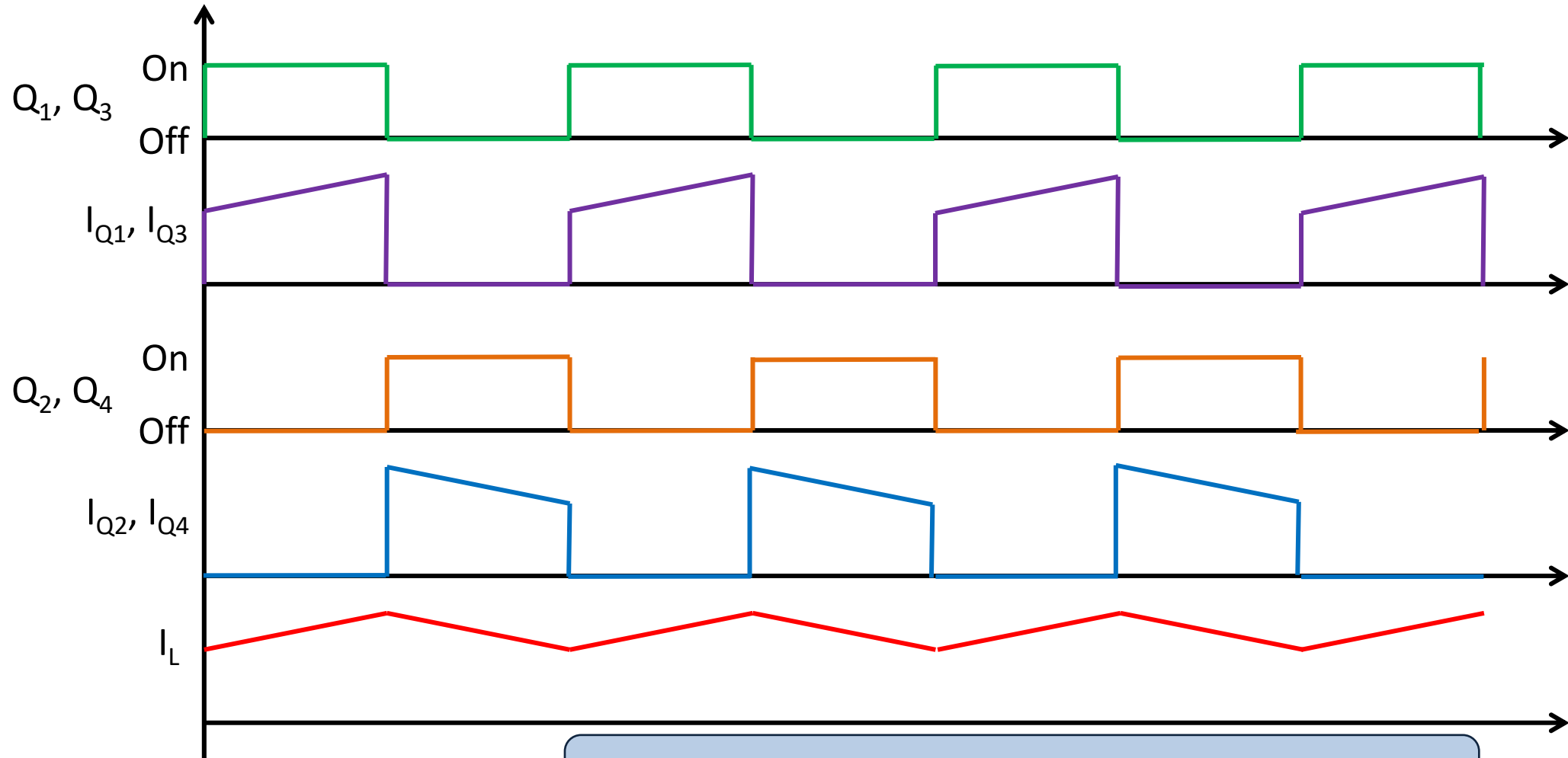Four Active Switches Mode Waveforms - CCM



$D = 0.5 \quad V_{OUT} = V_{IN} \quad I_{L_AVE} = 2 \cdot I_{OUT}$

Four Active Switches Mode Conversion Ratio

Output Voltage Conversion Ratio

Inductor
Volt-Second Balance

$$V_{IN} \cdot T_{ON} + (-V_{OUT}) \cdot T_{OFF} = 0$$

$$V_{IN} \cdot D \cdot T_{SW} - V_{OUT} \cdot (1-D) \cdot T_{SW} = 0$$

$$V_{IN} \cdot D - V_{OUT} \cdot (1-D) = 0$$

$$V_{OUT} \cdot (1-D) = V_{IN} \cdot D$$

$$V_{OUT} = \frac{D}{1-D} \cdot V_{IN} = \frac{D}{D'} \cdot V_{IN}$$

Noninverting Buck-Boost
Conversion Ratio

Average Inductor Current

$$-I_{OUT} \cdot T_{ON} + (I_L - I_{OUT}) \cdot T_{OFF} = 0$$

$$-I_{OUT} \cdot D \cdot T_{SW} + (I_L - I_{OUT}) \cdot (1-D) \cdot T_{SW} = 0$$

$$-I_{OUT} \cdot D + (I_L - I_{OUT}) \cdot (1-D) = 0$$

$$-I_{OUT} \cdot D + I_L \cdot (1-D) - I_{OUT} \cdot (1-D) = 0$$

$$-I_{OUT} + I_L \cdot (1-D) = 0$$

$$I_L = \frac{1}{1-D} \cdot I_{OUT}$$

Capacitor
Charge Balance

Operating Mode Comparison

Buck Or Boost

- Highest Efficiency As Only Two Active Switches
- Hard To Control Transition As Output Voltage Increases Or Decreases Past The Input Voltage

- Consider Cases When

$$V_{OUT} = 0.99 \cdot V_{IN} \text{ Or}$$

$$V_{OUT} = 1.01 \cdot V_{IN}$$

Four Active Switches Mode

- Smooth And Easy Control As Output Voltage Increases Or Decreases Past The Input Voltage
- Lower Efficiency With Four Active Switches

Four Switch Buck-Boost Summary/SEPIC Comparison

Four Switch Buck Boost

- Topology
 - Four Switches
 - One Simple Inductor
- More Complex Switch Drive
 - Two Or Four Controlled Switches
- Input-To-Output Shoot-Through Failure Mode
- Simpler Control Characteristic


SEPIC

- Topology
 - One Controlled Switch
 - Two Inductors Or One Coupled Inductor
- Simple Single Switch Drive
- No Input-To-Output Shoot-Through Failure Mode
- Complex Control Characteristic

Appendix X

Simple Pole And Zero Transfer Functions

Simple Pole Transfer Function $H_P(s)$

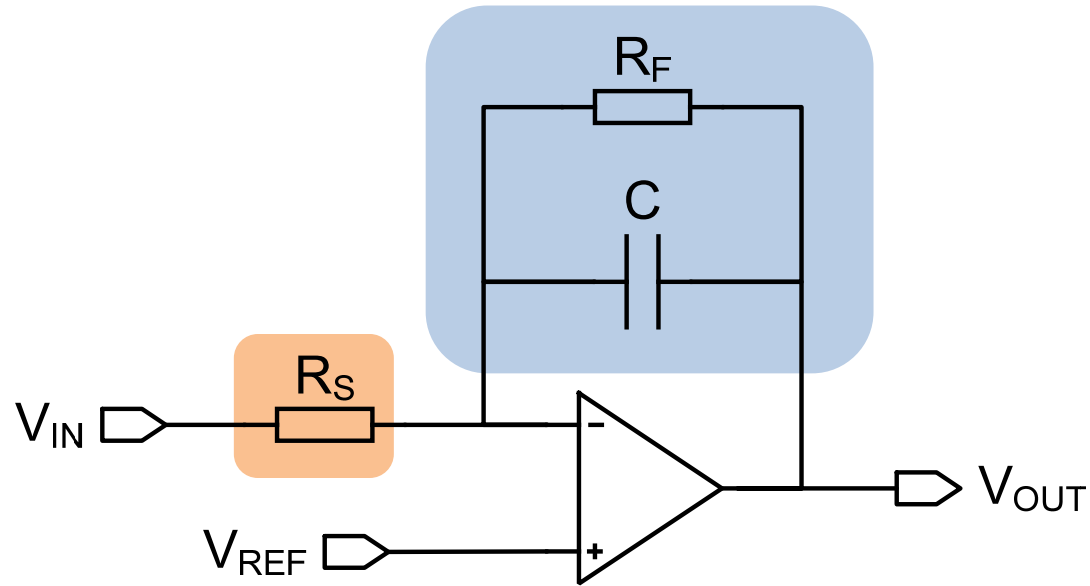

$$H_P(s) = -\frac{Z_F}{Z_S}$$

$$\begin{aligned} Z_F &= R_F \parallel \frac{1}{s \cdot C} \\ &= \frac{R_F \cdot \frac{1}{s \cdot C}}{R_F + \frac{1}{s \cdot C}} \cdot \frac{s \cdot C}{s \cdot C} \\ &= \frac{R_F}{1 + s \cdot R_F \cdot C} \end{aligned}$$

$$Z_S = R_S$$

Simple Pole Transfer Function

$$H_P(s) = -\frac{Z_F}{Z_S}$$

$$H_P(s) = -\frac{R_F}{R_S} \cdot \frac{1}{1 + s \cdot R_F \cdot C}$$
$$= -\frac{R_F}{R_S} \cdot \frac{1}{1 + s \cdot R_F \cdot C}$$

$$H_P(s) = G_0 \cdot \frac{1}{1 + \frac{s}{\omega_P}}$$

Standard Form
With DC Gain Term
And Frequency
Dependent Term

$$G_0 = -\frac{R_F}{R_S}$$

DC Gain

$$\omega_P = 2 \cdot \pi \cdot f_P = \frac{1}{R_F \cdot C}$$

$$f_P = \frac{1}{2 \cdot \pi \cdot R_F \cdot C}$$

Pole
Frequency

Simple Pole Transfer Function: Magnitude

$$\begin{aligned} |H_P(j \cdot \omega)|^2 &= H_P(j \cdot \omega) \cdot H_P^*(j \cdot \omega) \\ &= H_P(j \cdot \omega) \cdot H_P(-j \cdot \omega) \\ &= \left(G_0 \cdot \frac{1}{1 + \frac{j \cdot \omega}{\omega_P}} \right) \cdot \left(G_0 \cdot \frac{1}{1 + \frac{-j \cdot \omega}{\omega_P}} \right) \\ &= G_0^2 \cdot \frac{1}{1 + \frac{j \cdot \omega}{\omega_P}} \cdot \frac{1}{1 - \frac{j \cdot \omega}{\omega_P}} \\ &= G_0^2 \cdot \frac{1}{1 + \left(\frac{\omega}{\omega_P} \right)^2} \end{aligned}$$

$$\begin{aligned} |H_P(j \cdot \omega)| &= G_0 \cdot \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_P} \right)^2}} \\ &= G_0 \cdot \frac{1}{\sqrt{1 + \left(\frac{f}{f_P} \right)^2}} \end{aligned}$$

Consider The Case When $f = f_P$

$$\begin{aligned} |H_P(j \cdot \omega_P)| &= G_0 \cdot \frac{1}{\sqrt{1 + \left(\frac{f_P}{f_P} \right)^2}} = G_0 \cdot \frac{1}{\sqrt{1 + 1^2}} \\ &= G_0 \cdot \frac{1}{\sqrt{2}} = G_0 \cdot \frac{\sqrt{2}}{2} = -3 \text{ dB} \end{aligned}$$

Simple Pole Transfer Function: Phase

$$\angle H_P(j \cdot \omega) = \tan^{-1} \left(\frac{\text{Im}(H_P(j \cdot \omega))}{\text{Re}(H_P(j \cdot \omega))} \right)$$

$$\begin{aligned} \text{Im}(H_P(j \cdot \omega)) &= \text{Im} \left(G_0 \cdot \frac{1}{1 + \frac{j \cdot \omega}{\omega_P}} \right) = \text{Im} \left(G_0 \cdot \frac{1}{1 + \frac{j \cdot \omega}{\omega_P}} \cdot \frac{1 - \frac{j \cdot \omega}{\omega_P}}{1 - \frac{j \cdot \omega}{\omega_P}} \right) & \text{Re}(H_P(j \cdot \omega)) &= \text{Re} \left(G_0 \cdot \frac{1}{1 + \frac{j \cdot \omega}{\omega_P}} \right) = \text{Re} \left(G_0 \cdot \frac{1}{1 + \frac{j \cdot \omega}{\omega_P}} \cdot \frac{1 - \frac{j \cdot \omega}{\omega_P}}{1 - \frac{j \cdot \omega}{\omega_P}} \right) \\ &= \text{Im} \left(G_0 \cdot \frac{1 - \frac{j \cdot \omega}{\omega_P}}{1 + \left(\frac{\omega}{\omega_P} \right)^2} \right) & &= \text{Re} \left(G_0 \cdot \frac{1 - \frac{j \cdot \omega}{\omega_P}}{1 + \left(\frac{\omega}{\omega_P} \right)^2} \right) \\ &= G_0 \cdot \frac{-\frac{\omega}{\omega_P}}{1 + \left(\frac{\omega}{\omega_P} \right)^2} & &= G_0 \cdot \frac{1}{1 + \left(\frac{\omega}{\omega_P} \right)^2} \end{aligned}$$


Simple Pole Transfer Function: Phase

$$\begin{aligned}\angle H(j \cdot \omega) &= \tan^{-1} \left(\frac{\text{Im}(H(j \cdot \omega))}{\text{Re}(H(j \cdot \omega))} \right) \\ &= \tan^{-1} \left(\frac{G_0 \cdot \frac{-\omega}{\omega_P} \cdot \frac{1}{1 + \left(\frac{\omega}{\omega_P}\right)^2}}{G_0 \cdot \frac{1}{1 + \left(\frac{\omega}{\omega_P}\right)^2}} \right) \\ &= \tan^{-1} \left(-\frac{\omega}{\omega_P} \right) = \tan^{-1} \left(-\frac{f}{f_P} \right)\end{aligned}$$


Consider The Case When $f = f_P$

$$\begin{aligned}\angle H(j \cdot \omega_P) &= \tan^{-1} \left(-\frac{f_P}{f_P} \right) \\ &= \tan^{-1}(-1) \\ &= -\frac{\pi}{4} = -45^\circ\end{aligned}$$


Simple Pole Bode Plot

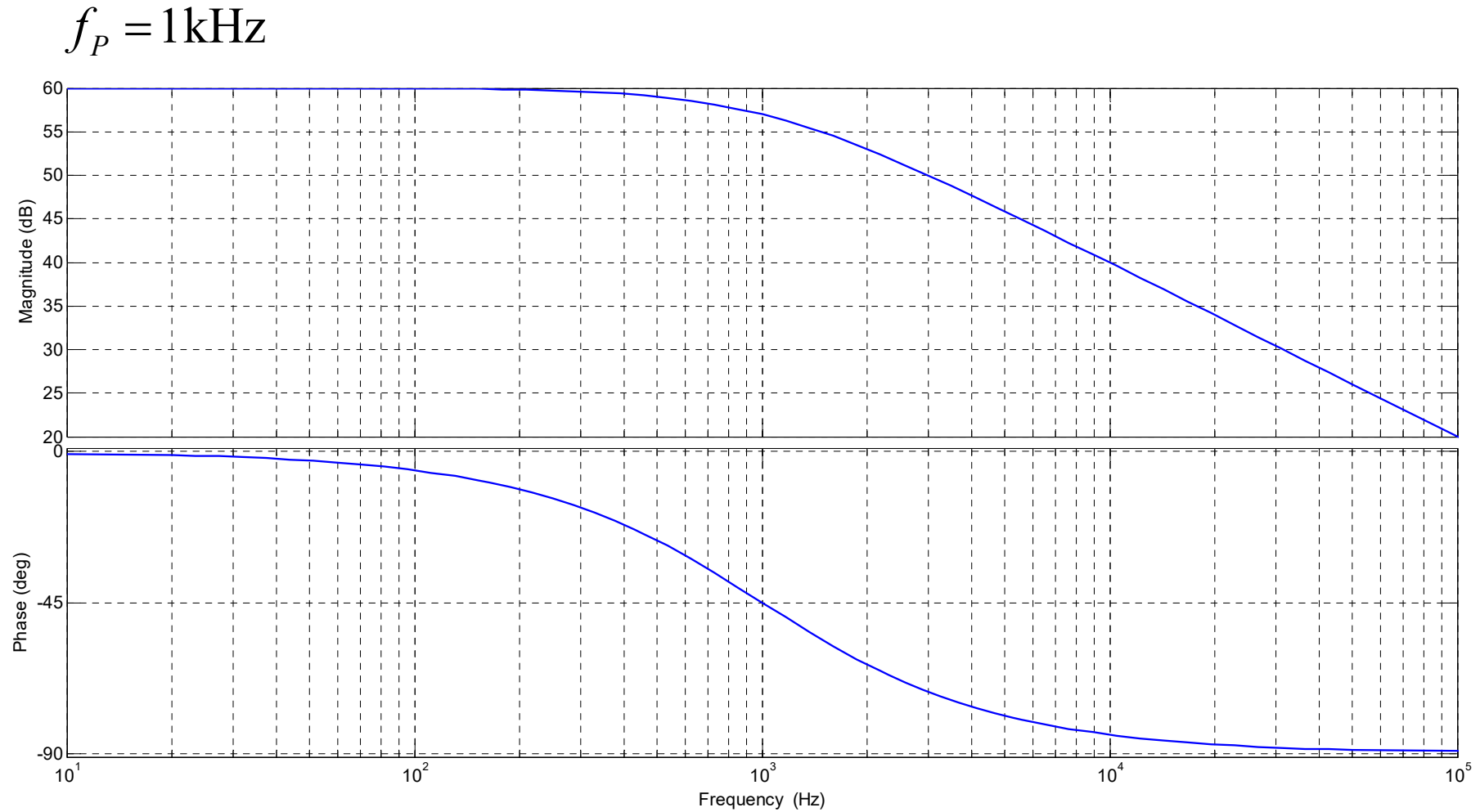

Simple Pole Bode Plot

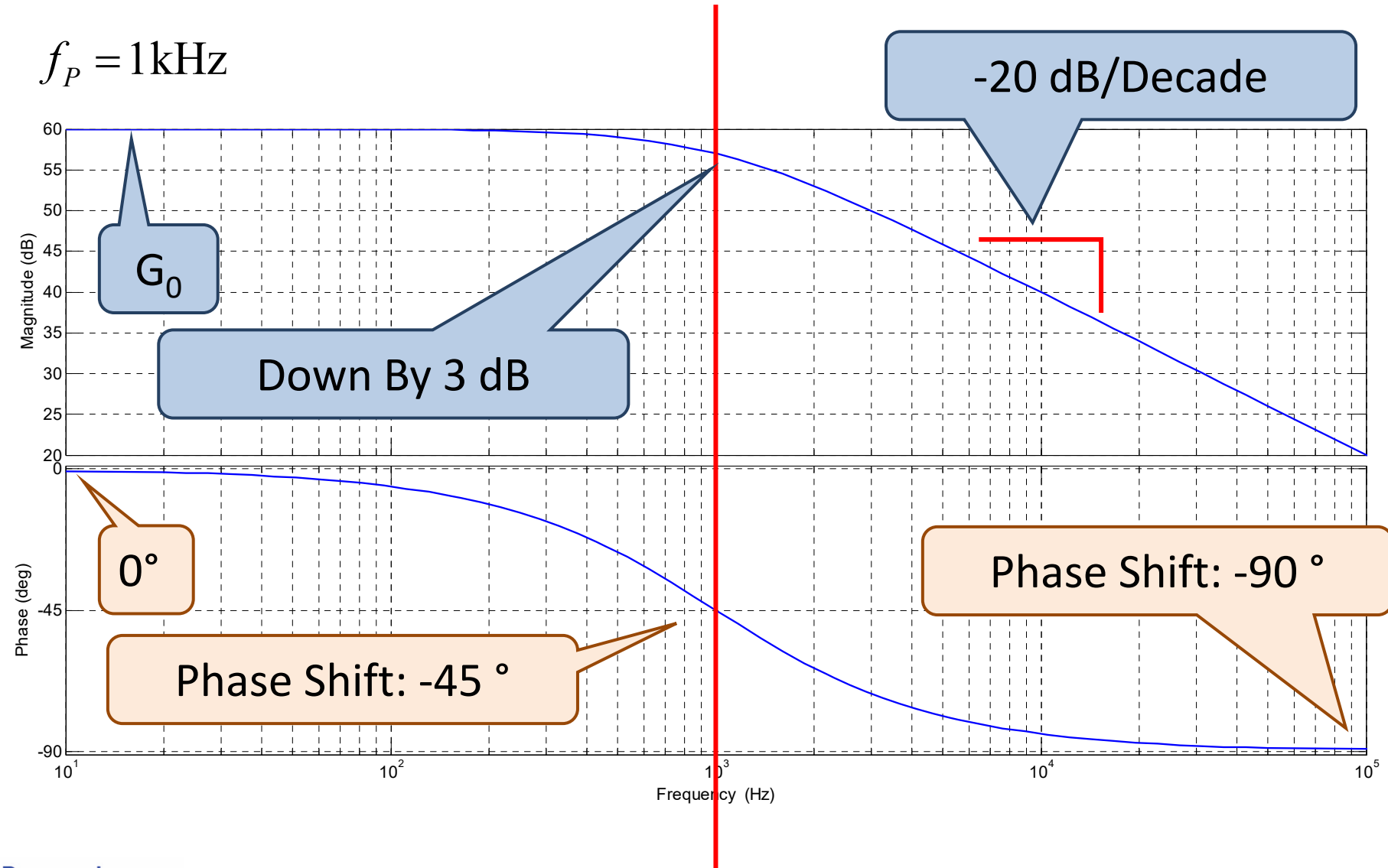

Simple Zero Transfer Function $H_Z(s)$

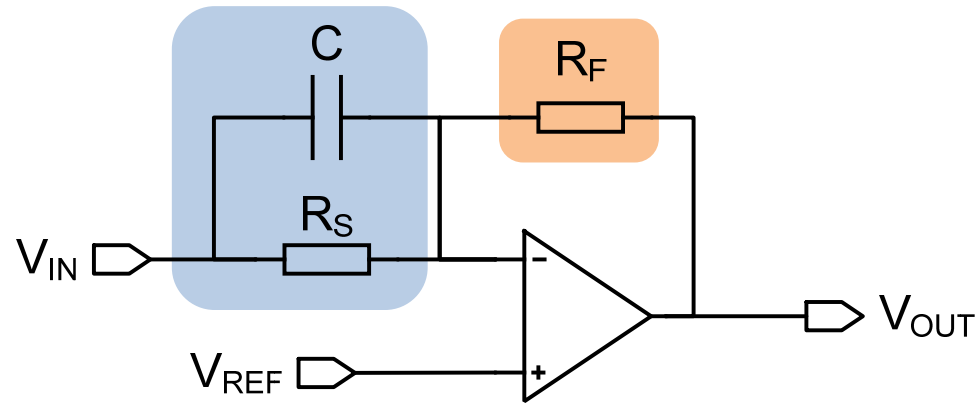

$$H_Z(s) = -\frac{Z_F}{Z_S}$$

$$\begin{aligned} Z_S &= R_S \parallel \frac{1}{s \cdot C} \\ &= \frac{R_S \cdot \frac{1}{s \cdot C}}{R_S + \frac{1}{s \cdot C}} \cdot \frac{s \cdot C}{s \cdot C} \\ &= \frac{R_S}{1 + s \cdot R_S \cdot C} \end{aligned}$$

$$Z_F = R_F$$

Simple Zero Transfer Function

$$\begin{aligned}H_Z(s) &= -\frac{Z_F}{Z_S} \\ &= -\frac{R_F}{\frac{R_S}{1 + s \cdot R_S \cdot C}} \\ &= -\frac{R_F}{R_S} \cdot (1 + s \cdot R_S \cdot C)\end{aligned}$$

$$\begin{aligned}H_Z(s) &= G_0 \cdot \left(1 + \frac{s}{\omega_Z}\right) \\ G_0 &= -\frac{R_F}{R_S} \\ \omega_Z &= 2 \cdot \pi \cdot f_Z = \frac{1}{R_S \cdot C} \\ f_Z &= \frac{1}{2 \cdot \pi \cdot R_S \cdot C}\end{aligned}$$

Simple Zero Transfer Function: Magnitude

$$\begin{aligned} |H_Z(j \cdot \omega)|^2 &= H_Z(j \cdot \omega) \cdot H_Z^*(j \cdot \omega) \\ &= H_Z(j \cdot \omega) \cdot H_Z(-j \cdot \omega) \\ &= G_0 \cdot \left(1 + \frac{j \cdot \omega}{\omega_Z}\right) \cdot G_0 \cdot \left(1 + \frac{-j \cdot \omega}{\omega_Z}\right) \\ &= G_0^2 \cdot \left(1 + \left(\frac{\omega}{\omega_Z}\right)^2\right) \end{aligned}$$

$$\begin{aligned} |H_Z(j \cdot \omega)| &= G_0 \cdot \sqrt{1 + \left(\frac{\omega}{\omega_Z}\right)^2} \\ &= G_0 \cdot \sqrt{1 + \left(\frac{f}{f_Z}\right)^2} \end{aligned}$$

Consider The Case When $f = f_Z$

$$\begin{aligned} |H_Z(j \cdot \omega_Z)| &= G_0 \cdot \sqrt{1 + \left(\frac{f_Z}{f_Z}\right)^2} \\ &= G_0 \cdot \sqrt{1 + 1^2} \\ &= G_0 \cdot \sqrt{2} \Rightarrow +3\text{dB} \end{aligned}$$

Simple Zero Transfer Function: Phase

$$\angle H(j \cdot \omega) = \tan^{-1} \left(\frac{\text{Im}(H(j \cdot \omega))}{\text{Re}(H(j \cdot \omega))} \right)$$

$$\begin{aligned} \text{Im}(H(j \cdot \omega)) &= \text{Im} \left(G_0 \cdot \left(1 + \frac{j \cdot \omega}{\omega_Z} \right) \right) \\ &= G_0 \cdot \frac{\omega}{\omega_Z} \end{aligned}$$

$$\begin{aligned} \text{Re}(H(j \cdot \omega)) &= \text{Re} \left(G_0 \cdot \left(1 + \frac{j \cdot \omega}{\omega_Z} \right) \right) \\ &= G_0 \end{aligned}$$


$$\begin{aligned} \angle H(j \cdot \omega) &= \tan^{-1} \left(\frac{G_0 \cdot \frac{\omega}{\omega_Z}}{G_0} \right) \\ &= \tan^{-1} \left(\frac{\omega}{\omega_Z} \right) = \tan^{-1} \left(\frac{f}{f_Z} \right) \end{aligned}$$

Consider The Case When $f = f_Z$


$$\begin{aligned} \angle H(j \cdot \omega_Z) &= \tan^{-1} \left(\frac{f_Z}{f_Z} \right) = \tan^{-1}(1) \\ &= \frac{\pi}{4} = 45^\circ \end{aligned}$$

Simple Zero Bode Plot

$$f_z = 1\text{kHz}$$

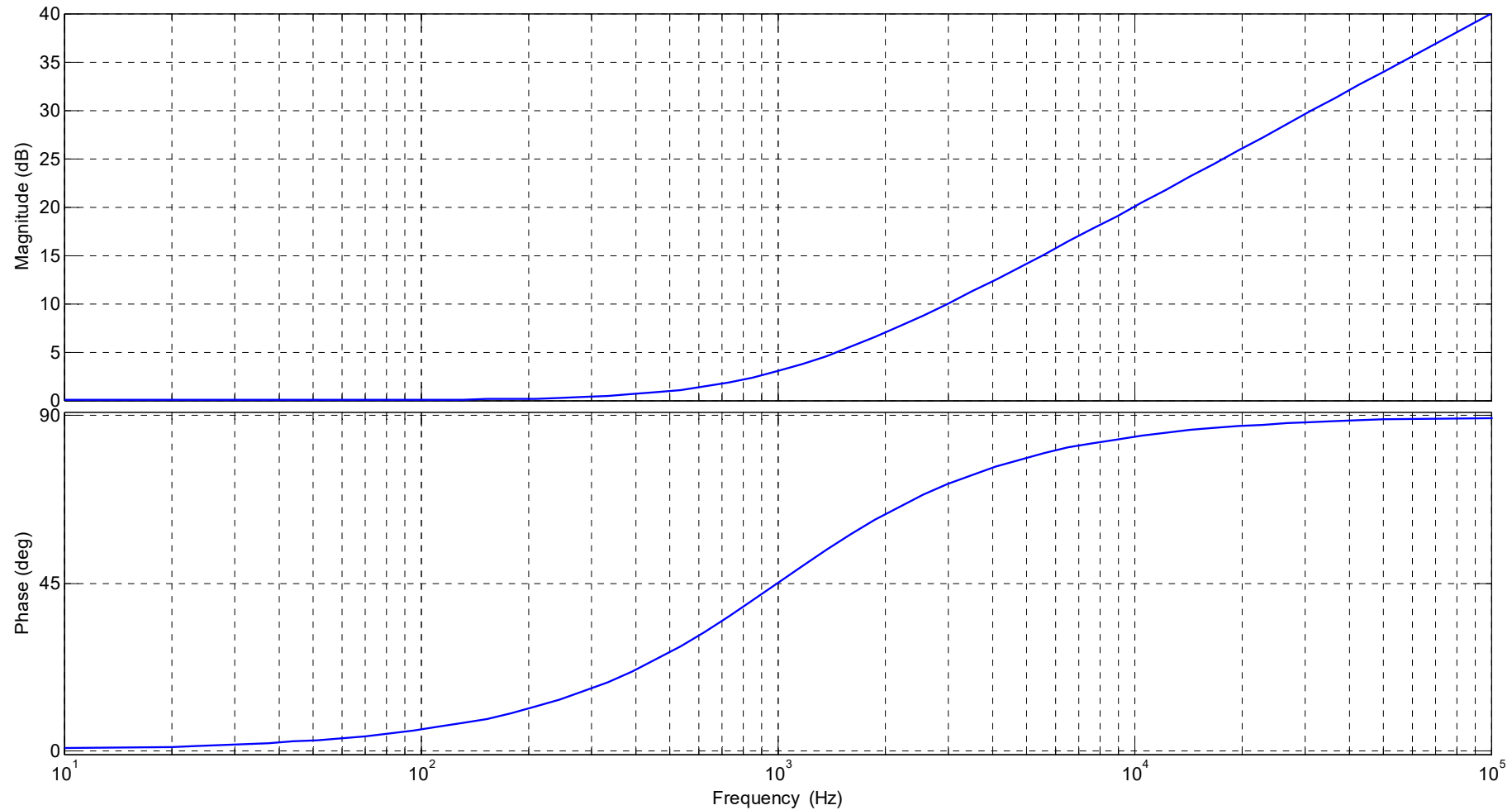


Simple Zero Bode Plot

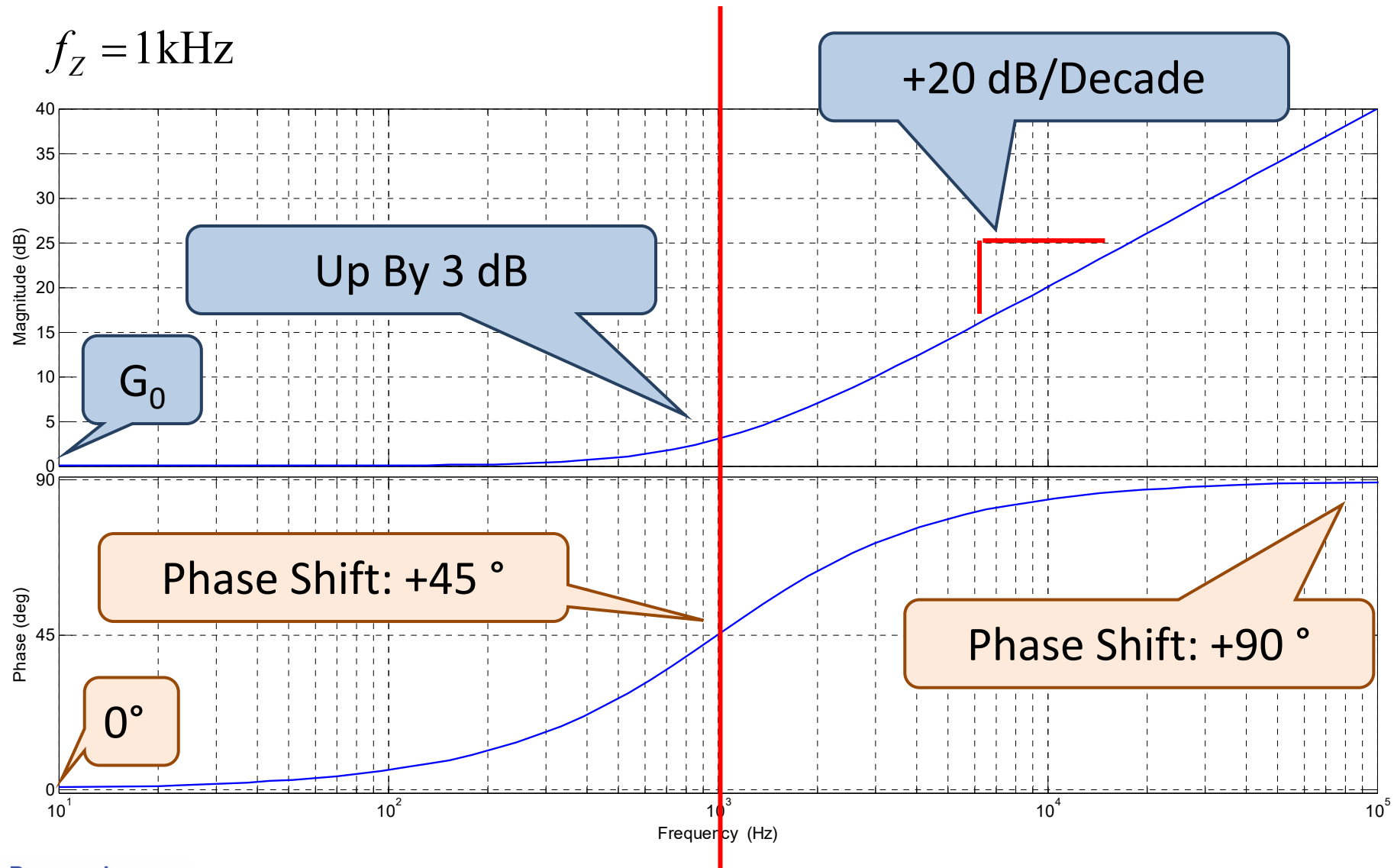

Appendix XI

Loop Gain And Tracking

Op-Amp Buffer/Follower

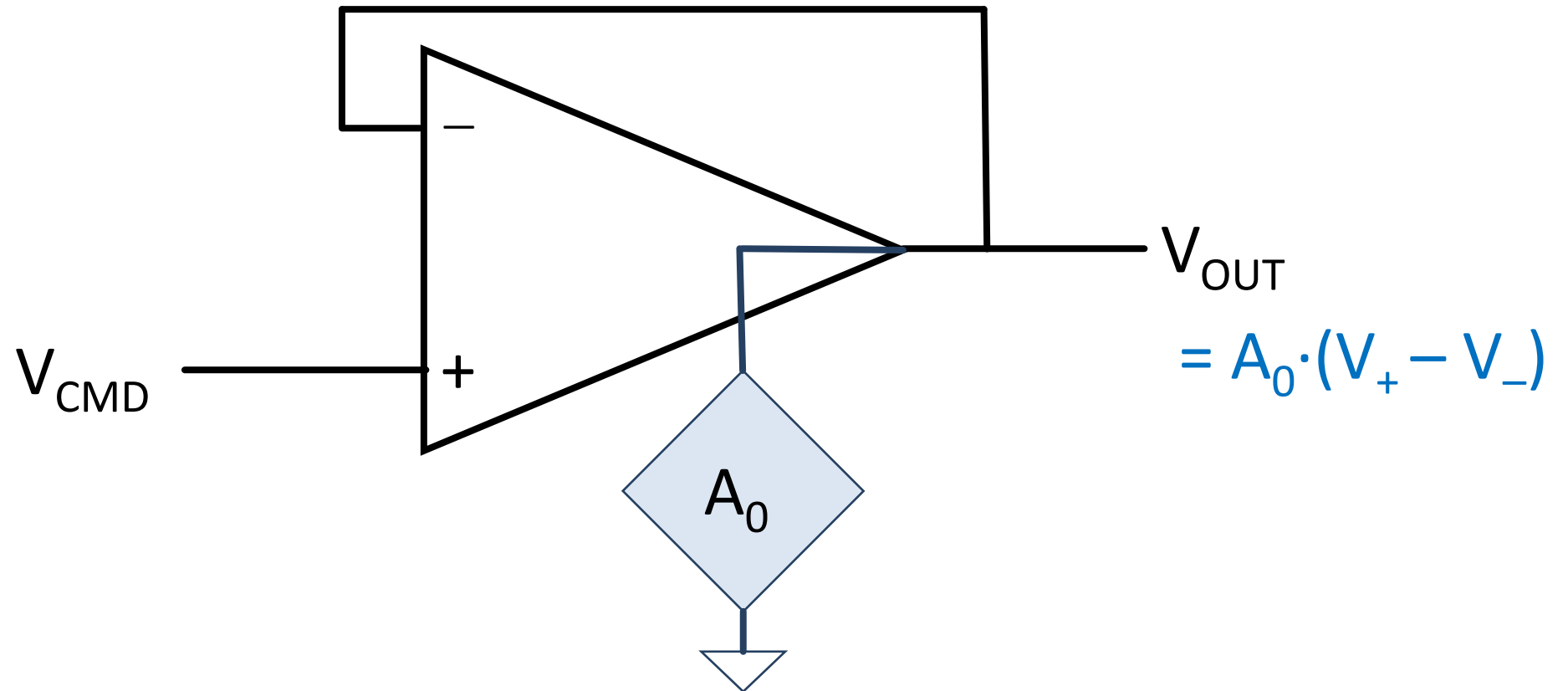

Op-Amp Buffer/Follower

$$v_{out}(s) = A(s) \cdot (v_+(s) - v_-(s))$$

$$v_-(s) = v_{out}(s)$$

$$v_+(s) = v_{cmd}(s)$$

$$\begin{aligned} v_{out}(s) &= A(s) \cdot (v_{cmd}(s) - v_{out}(s)) \\ &= A(s) \cdot v_{cmd}(s) - A(s) \cdot v_{out}(s) \end{aligned}$$

$$v_{out}(s) + A(s) \cdot v_{out}(s) = A(s) \cdot v_{cmd}(s)$$

$$v_{out}(s) = \frac{A(s)}{1 + A(s)} \cdot v_{cmd}(s)$$

$$|A(s)| \gg 1$$

$$v_{out}(s) \approx \frac{A(s)}{1 + A(s)} \cdot v_{cmd}(s)$$


$$\approx \frac{A(s)}{A(s)} \cdot v_{cmd}(s)$$

$$v_{out}(s) \approx v_{cmd}(s)$$

Let The
Op-amp Gain
Be Very Large

With Very Large Op-amp Gain
The Output Tracks The
Command Voltage

Loop Gain And Tracking

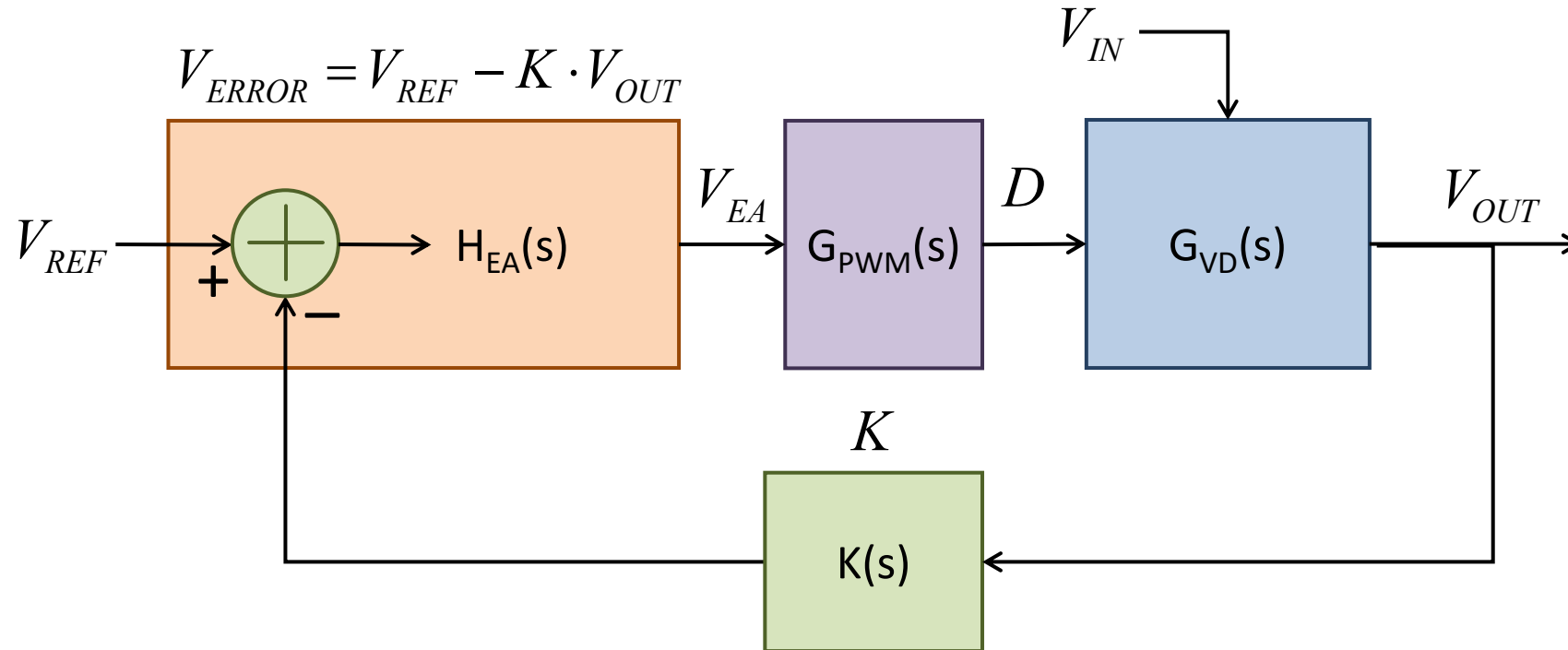

Loop Gain And Tracking

$$V_{OUT}(s) = G_{VD}(s) \cdot D(s) = G_{VD}(s) \cdot G_{PWM}(s) \cdot V_{EA}(s)$$

$$V_{EA}(s) = H_{EA}(s) \cdot (V_{REF} - K(s) \cdot V_{OUT}(s))$$

$$\begin{aligned} V_{OUT}(s) &= G_{VD}(s) \cdot G_{PWM}(s) \cdot H_{EA}(s) \cdot (V_{REF} - K(s) \cdot V_{OUT}(s)) \\ &= G_{VD}(s) \cdot G_{PWM}(s) \cdot H_{EA}(s) \cdot V_{REF} \\ &\quad - K(s) \cdot G_{VD}(s) \cdot G_{PWM}(s) \cdot H_{EA}(s) \cdot V_{OUT}(s) \end{aligned}$$

$$V_{OUT}(s) + K(s) \cdot G_{VD}(s) \cdot G_{PWM}(s) \cdot H_{EA}(s) \cdot V_{OUT}(s) = G_{VD}(s) \cdot G_{PWM}(s) \cdot H_{EA}(s) \cdot V_{REF}$$

$$\begin{aligned} V_{OUT}(s) &= \frac{G_{VD}(s) \cdot G_{PWM}(s) \cdot H_{EA}(s)}{1 + K(s) \cdot G_{VD}(s) \cdot G_{PWM}(s) \cdot H_{EA}(s)} \cdot V_{REF} \\ &= \frac{1}{K(s)} \cdot \frac{K(s) \cdot G_{VD}(s) \cdot G_{PWM}(s) \cdot H_{EA}(s)}{1 + K(s) \cdot G_{VD}(s) \cdot G_{PWM}(s) \cdot H_{EA}(s)} \cdot V_{REF} \end{aligned}$$

$$V_{OUT}(s) = \frac{1}{K(s)} \cdot \frac{T(s)}{1 + T(s)} \cdot V_{REF}$$

Loop Gain And Tracking

$$V_{OUT}(s) = \frac{1}{K(s)} \cdot \frac{T(s)}{1+T(s)} \cdot V_{REF}$$

$$|T(s)| \gg 1$$

Let The Loop Gain
Be Large

$$V_{OUT}(s) \approx \frac{1}{K(s)} \cdot \frac{T(s)}{1+T(s)} V_{REF}$$

$$\approx \frac{1}{K(s)} \cdot \frac{T(s)}{T(s)} \cdot V_{REF}$$

$$V_{OUT}(s) \approx \frac{1}{K(s)} \cdot V_{REF}$$

$$K(s) = K$$

Feedback Divider
Usually Constant
(Just Resistors)


$$V_{OUT}(s) \approx \frac{1}{K} \cdot V_{REF}$$

With Large Loop Gain
Output Voltage Tracks
The Reference Voltage/Input

Appendix XII

Ideal Loop Calculations

Better T(s)

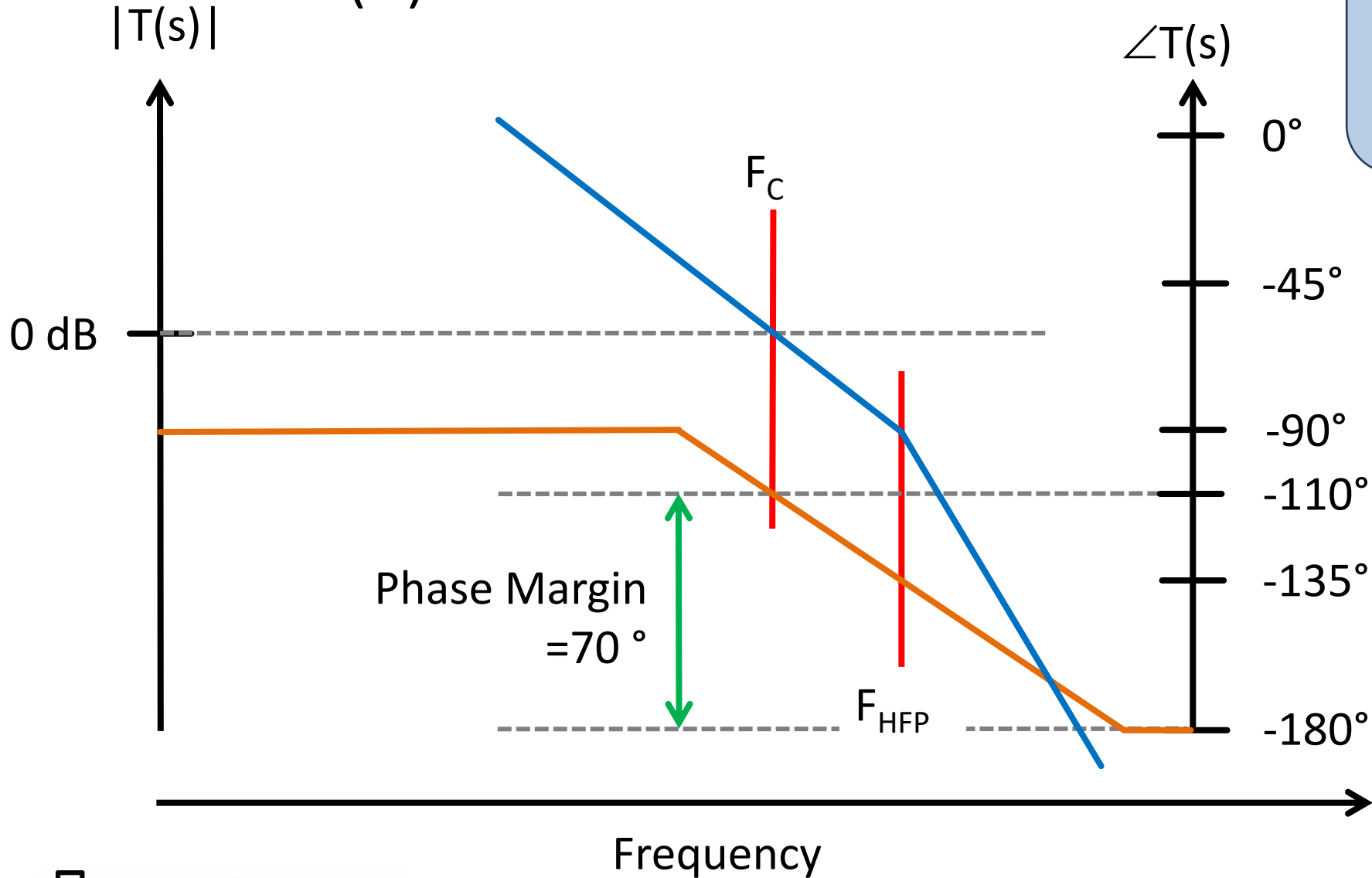

$$T(s) = \frac{\omega_0}{s} \cdot \frac{1}{1 + \frac{s}{\omega_{HFP}}}$$

To Have The Desired Phase Margin, What Is The High Frequency Pole (F_{HFP}) Frequency?

Calculating F_{HFP}

- Given Desired Phase Margin: PM
- Total Loop Phase Lag At Crossover Equals:
Phase_Lag = $-180^\circ + \text{PM}$
 - e.g. PM = 70° , Phase_Lag = $-180^\circ + 70^\circ = -110^\circ$
- Integrator Pole Contributes -90° Phase Shift
- Phase Lag At Crossover Due To High Frequency Pole (FHFP):
 - Phase_Lag_HFP = $-180^\circ - (-90^\circ) + \text{PM}$
= $-90^\circ + \text{PM}$
 - Example: PM = 70°
Phase_Lag_HFP = $-90^\circ + 70^\circ = -20^\circ$

Calculating F_{HFP}

- Phase Shift As A Function Of Frequency For a Simple Pole (See Previous Example):

$$\angle H_p(j \cdot \omega) = \tan^{-1} \left(-\frac{\omega}{\omega_p} \right)$$

$$\angle H_p(j \cdot 2 \cdot \pi \cdot f) = \tan^{-1} \left(-\frac{f}{f_p} \right)$$

- Solving For F_{HFP}

$$Phase_Lag_HFP(F_C) = \tan^{-1} \left(-\frac{F_C}{F_{HFP}} \right)$$

$$-\frac{F_C}{F_{HFP}} = \tan(Phase_Lag_HFP(F_C))$$

$$F_{HFP} = -\frac{F_C}{\tan(Phase_Lag_HFP(F_C))}$$

- Example

$$Phase_Lag_HFP(F_C) = -20^\circ$$

$$F_{HFP} = -\frac{F_C}{\tan(-20^\circ)} = 2.75 \cdot F_C$$

Calculating ω_0

- Ideal Loop Transfer Function

$$T(s) = \frac{\omega_0}{s} \cdot \frac{1}{1 + \frac{s}{\omega_{HFP}}}$$

- At Crossover We Want:

$$|T(j \cdot \omega_c)| = 1$$

- Using Identity For Square Of The Magnitude:

$$|T(j \cdot \omega_c)|^2 = \left(\frac{\omega_0}{j \cdot \omega_c} \cdot \frac{1}{1 + \frac{j \cdot \omega_c}{\omega_{HFP}}} \right) \cdot \left(\frac{\omega_0}{-j \cdot \omega_c} \cdot \frac{1}{1 - \frac{j \cdot \omega_c}{\omega_{HFP}}} \right)$$

Calculating ω_0

$$\begin{aligned} |T(j \cdot \omega_C)|^2 &= \left(\frac{\omega_0}{j \cdot \omega_C} \cdot \frac{1}{1 + \frac{j \cdot \omega_C}{\omega_{HFP}}} \right) \cdot \left(\frac{\omega_0}{-j \cdot \omega_C} \cdot \frac{1}{1 - \frac{j \cdot \omega_C}{\omega_{HFP}}} \right) \\ &= \left(\frac{\omega_0}{\omega_C} \right)^2 \cdot \frac{1}{1 + \left(\frac{\omega_C}{\omega_{HFP}} \right)^2} = 1 \end{aligned}$$

$$\left(\frac{\omega_0}{\omega_C} \right)^2 = 1 + \left(\frac{\omega_C}{\omega_{HFP}} \right)^2$$


$$\frac{\omega_0}{\omega_C} = \sqrt{1 + \left(\frac{\omega_C}{\omega_{HFP}} \right)^2}$$

$$\omega_0 = \omega_C \cdot \sqrt{1 + \left(\frac{\omega_C}{\omega_{HFP}} \right)^2}$$

Appendix XIII


Analog Compensators

Type I Compensator

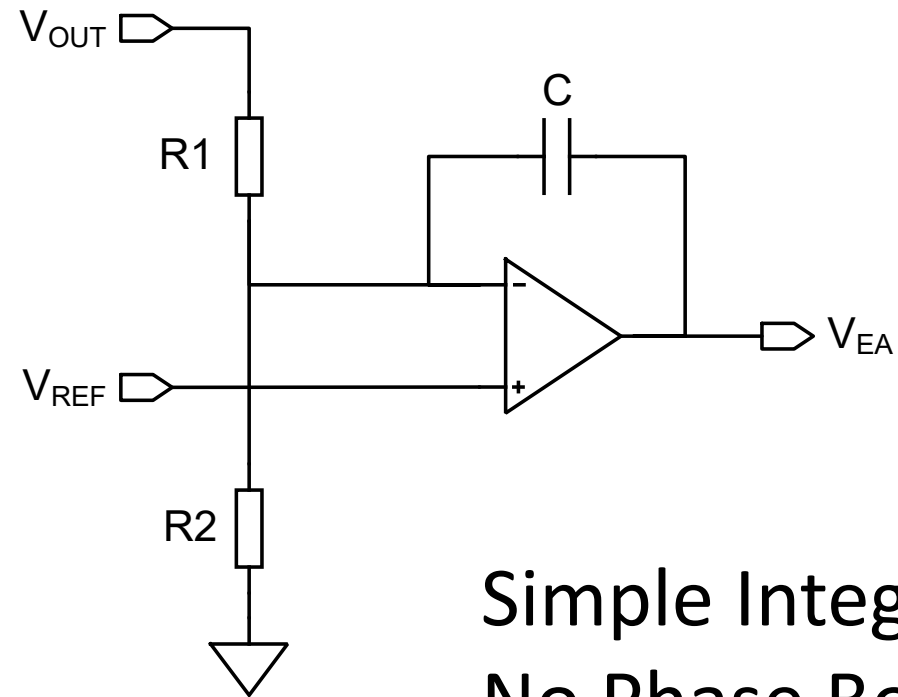


Simple Integrator
No Phase Boost

Type I Compensator

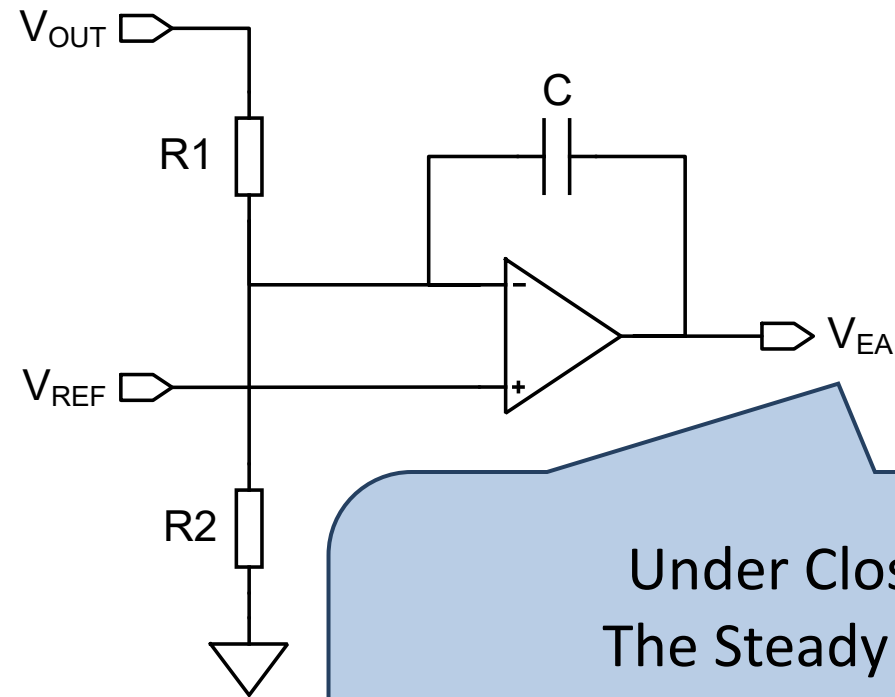

Under Closed Loop Control.
The Steady State Value Of V_{EA}
Will Be Whatever Value Is Needed To Drive
 V_{OUT} Such That The Op-Amp Differential Input
Voltage ($V_+ - V_-$) Is Essentially Zero

Type I Compensator

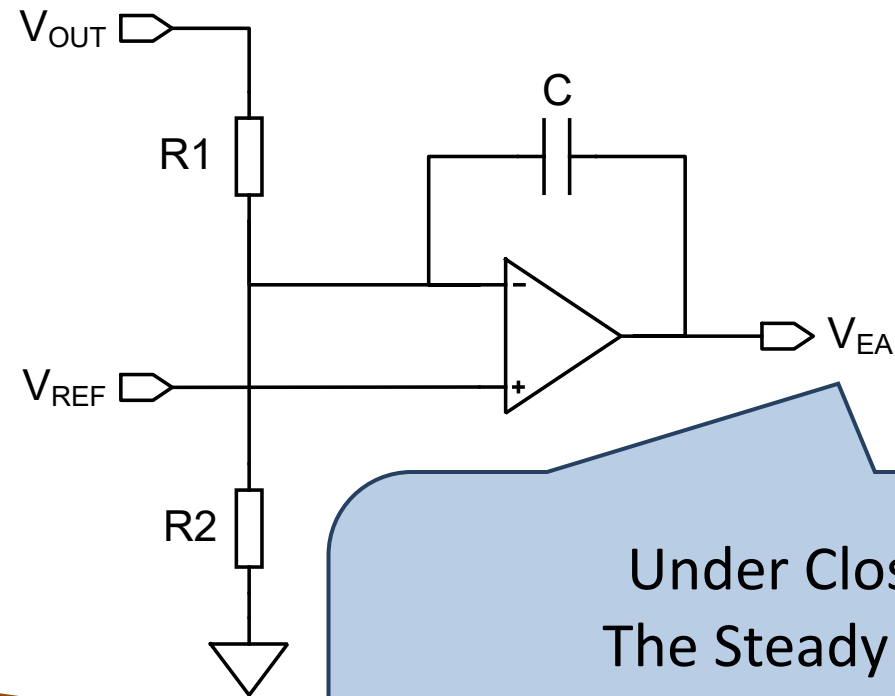

True For All
Compensators
That Include
An Integrator

Under Closed Loop Control.
The Steady State Value Of V_{EA}
Will Be Whatever Value Is Needed To Drive
 V_{OUT} Such That The Op-Amp Differential Input
Voltage ($V_+ - V_-$) Is Essentially Zero

Type I Compensator: DC

$$V_{EA} = A_{OL} \cdot (V_+ - V_-)$$

$$V_- = V_+ - \frac{1}{A_{OL}} \cdot V_{EA}$$

$$V_+ = V_{REF}$$

$$V_- = V_{REF} - \frac{1}{A_{OL}} \cdot V_{EA}$$

$$A_{OL} \approx 10^4 \Rightarrow \frac{1}{A_{OL}} \cdot V_{EA} \approx 50 \mu\text{V}$$

$$V_- = V_{REF} - 50 \mu\text{V} \approx V_{REF}$$

Op-Amp Output Voltage At DC
Is The Differential Input Voltage ($V_+ - V_-$)
Times The DC Open Loop Gain (A_{OL})

Typical Op-Amp Open Loop Gain Is 40 dB (10,000)
And Assuming Error Amp Output At 5V

Type I Compensator: DC

$$I(R_1) = I(R_2) + I(V_-) \approx I(R_2)$$

$$\frac{V_{OUT} - V_-}{R_1} = \frac{V_{OUT} - V_{REF}}{R_1} = \frac{V_-}{R_2} = \frac{V_{REF}}{R_2}$$


$$\frac{V_{OUT} - V_{REF}}{R_1} = \frac{V_{REF}}{R_2}$$

$$\frac{V_{OUT}}{R_1} = \frac{V_{REF}}{R_2} + \frac{V_{REF}}{R_1} = \frac{R_1 + R_2}{R_1 \cdot R_2} \cdot V_{REF}$$

$$V_{OUT} = \frac{R_1 + R_2}{R_2} \cdot V_{REF}$$

This Relationship Is True For All Compensators With An Integrator

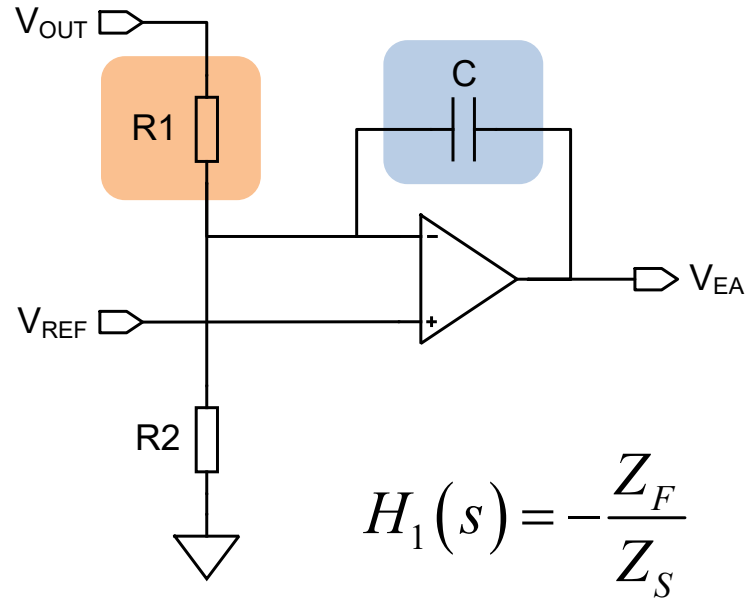Type I Compensator Transfer Function $H_1(s)$



$$H_1(s) = -\frac{Z_F}{Z_S}$$

$$Z_F = \frac{1}{s \cdot C}$$

$$Z_S = R$$

$$\begin{aligned} H_1(s) &= -\frac{Z_F}{Z_S} \\ &= -\frac{1}{s \cdot C} \cdot \frac{1}{R} \\ &= -\frac{1}{s \cdot R \cdot C} \end{aligned}$$

$$\begin{aligned} H_1(s) &= -\frac{1}{s} \\ &= -\frac{1}{\omega_P} \end{aligned}$$

$$\omega_P = 2 \cdot \pi \cdot f_P = \frac{1}{R \cdot C}$$

$$f_P = \frac{1}{2 \cdot \pi \cdot R \cdot C}$$

Type I Compensator Transfer Function

$$\begin{aligned} |H_1(j \cdot \omega)| &= \left| -\frac{\omega_P}{j \cdot \omega} \right| \\ &= \sqrt{\operatorname{Re}(H(j \cdot \omega))^2 + \operatorname{Im}(H(j \cdot \omega))^2} \\ &= \sqrt{0^2 + \left(-\frac{\omega_P}{\omega} \right)^2} \\ &= \frac{\omega_P}{\omega} = \frac{2 \cdot \pi \cdot f_P}{2 \cdot \pi \cdot f} \\ &= \frac{f_P}{f} \end{aligned}$$


Gain = 1 (0 dB)
When $f = f_p$

$$\begin{aligned} \angle H_1(j \cdot \omega) &= \tan^{-1} \left(\frac{\operatorname{Im}(H(j \cdot \omega))}{\operatorname{Re}(H(j \cdot \omega))} \right) \\ &= \tan^{-1} \left(\frac{-\frac{\omega_P}{\omega}}{0} \right) = \tan^{-1}(-\infty) \\ &= -\frac{\pi}{2} = -90^\circ \end{aligned}$$

Constant -90°
Phase Shift Independent
Of Frequency


Type I Compensator Bode Plot

$$f_P = 10\text{Hz}$$

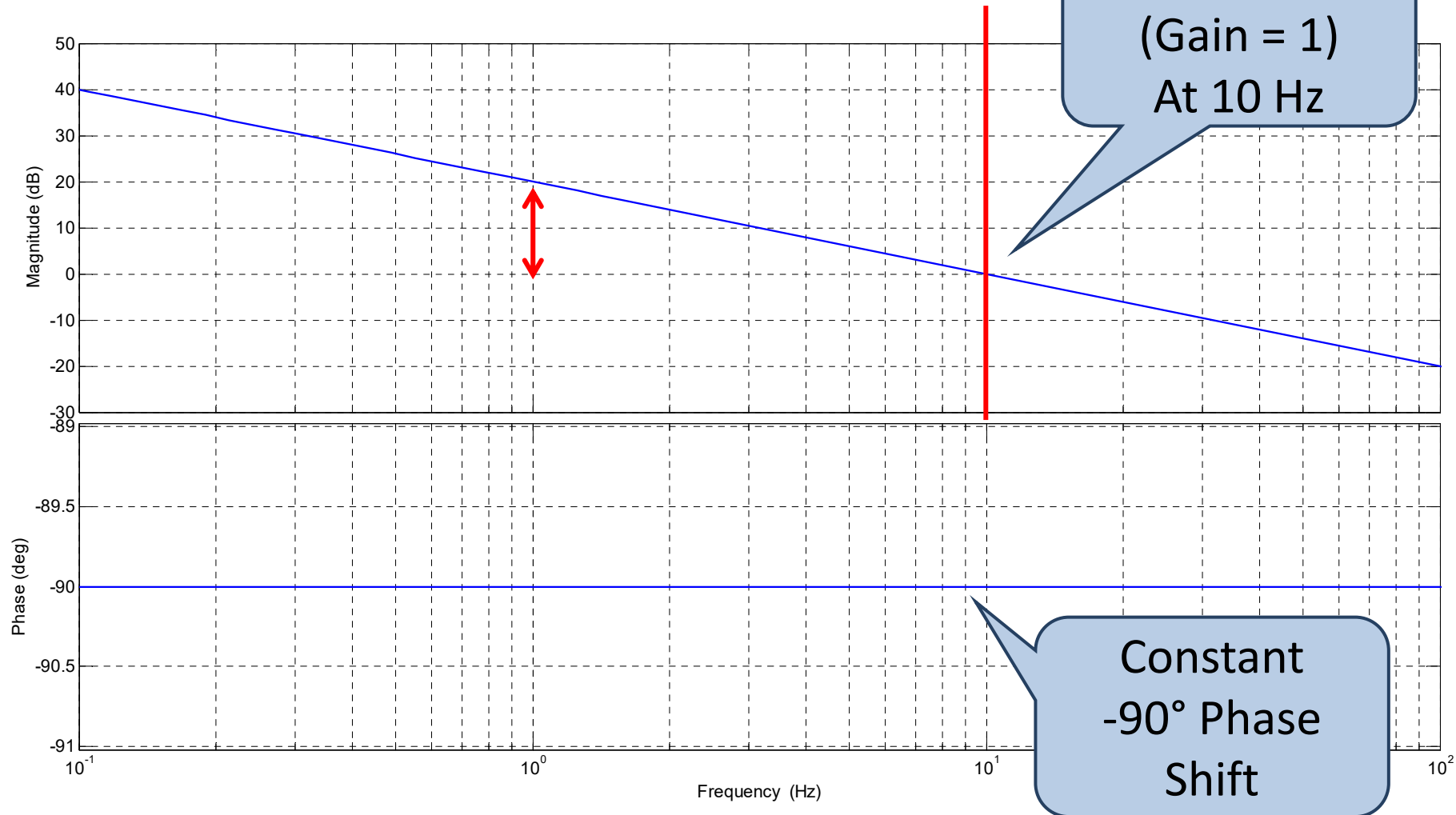


Type I Compensator Bode Plot

$$f_P = 10\text{Hz}$$

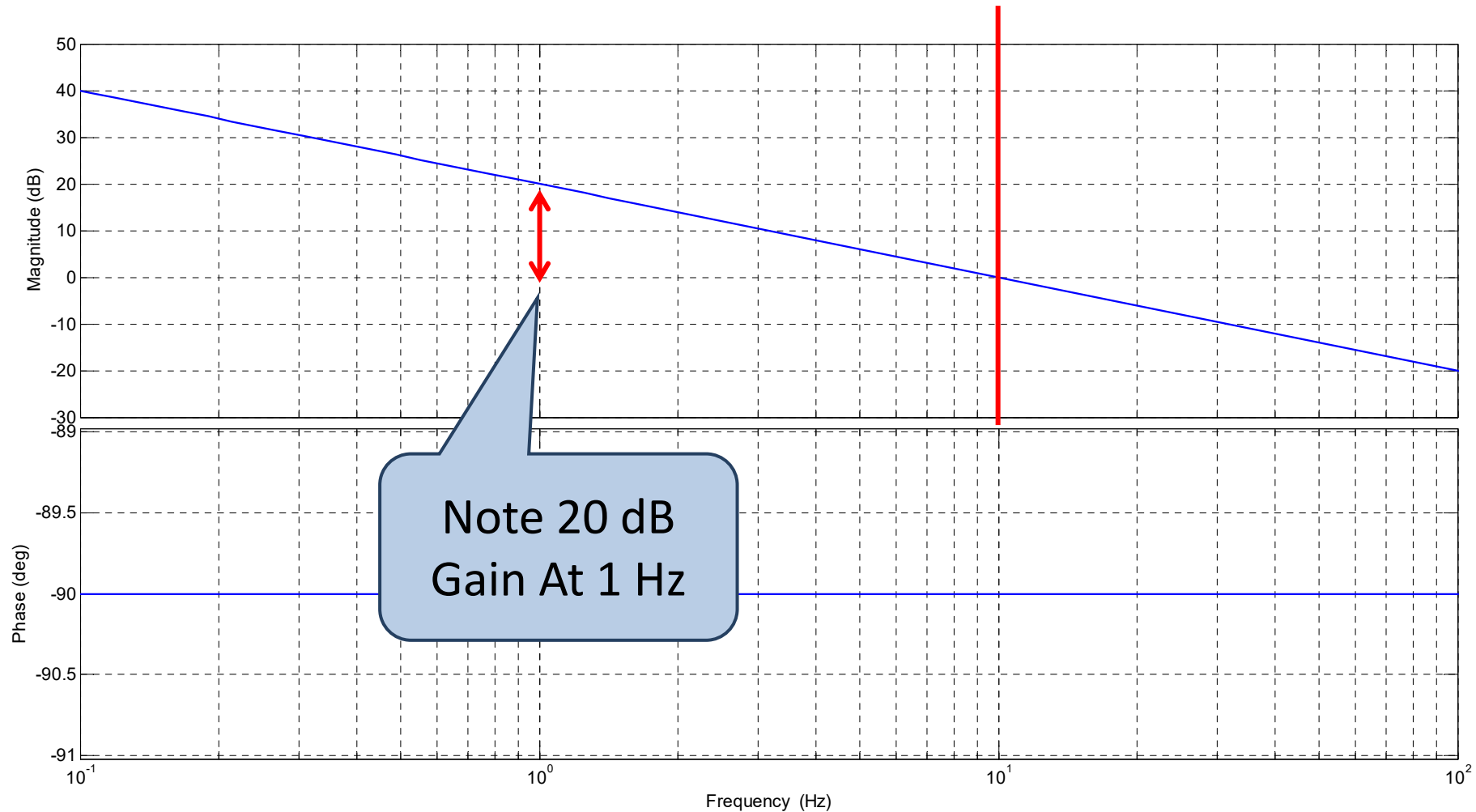

Type I Compensator Bode Plot


$$f_p = 1\text{kHz}$$

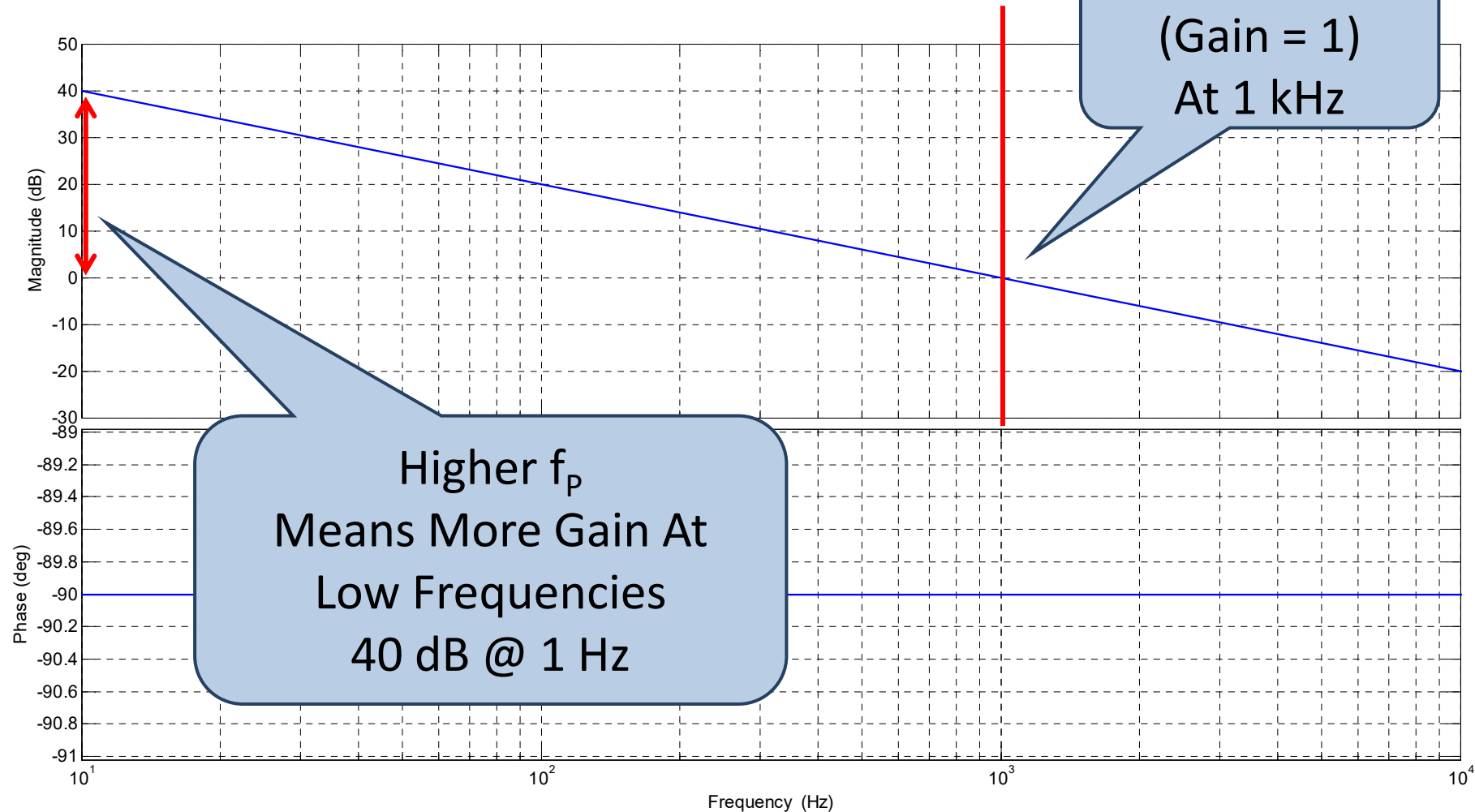

Type I For Debugging

- If Having Problems With Stability, Change Compensator To Type I
- Set Compensator Pole Frequency To No More Than 1/10th Of The Output Filter Frequency
 - 1/100th (2 Decades Lower) Is Better
- Loop Should Be Stable So You Can Debug
- Transient Response Will Be Poor
 - Input Ripple Rejection May Also Be Poor

Type II Compensator

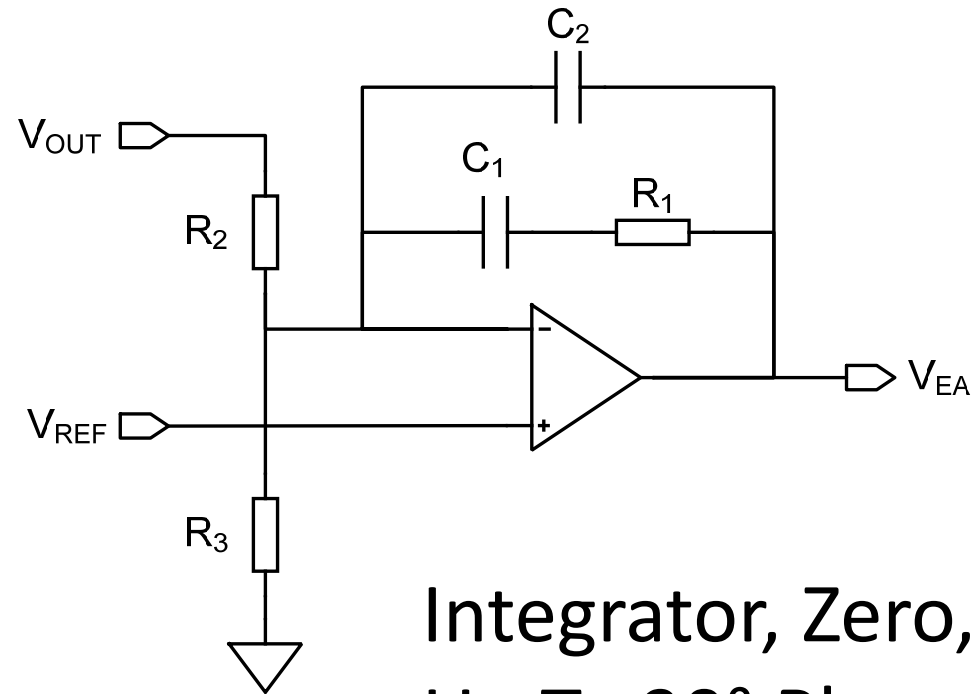


Integrator, Zero, Pole
Up To 90° Phase Boost

Type II Compensator

- Type II Compensator Used With Power Stages That Have Only -90° Phase Shift
 - Current Mode Control
 - Converters Operating In Discontinuous Mode

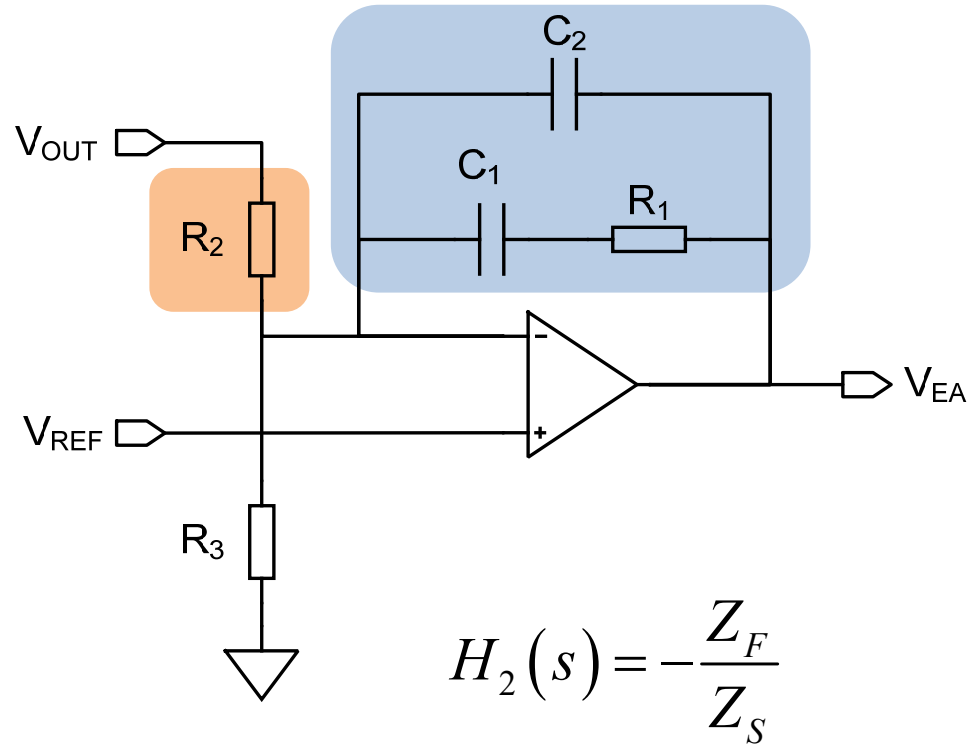Type II Compensator Transfer Function $H_2(s)$



$$\begin{aligned}
 Z_F &= \frac{1}{s \cdot C_2} \parallel \left(R_1 + \frac{1}{s \cdot C_1} \right) = \frac{1}{s \cdot C_2} \parallel \frac{1 + s \cdot R_1 \cdot C_1}{s \cdot C_1} \\
 &= \frac{1}{s \cdot C_2} \cdot \frac{1 + s \cdot R_1 \cdot C_1}{s \cdot C_1} \\
 &= \frac{s \cdot C_2}{1 + s \cdot R_1 \cdot C_1} \cdot \frac{s \cdot C_1}{s \cdot C_1} \cdot \frac{s \cdot C_2}{s \cdot C_2} \\
 &= \frac{1}{s \cdot C_2} + \frac{1 + s \cdot R_1 \cdot C_1}{s \cdot C_1} \\
 &= \frac{1 + s \cdot R_1 \cdot C_1}{s \cdot C_1 + s \cdot C_2 \cdot (1 + s \cdot R_1 \cdot C_1)}
 \end{aligned}$$

$$Z_S = R_2$$

Type II Compensator Transfer Function $H_2(s)$

$$H_2(s) = -\frac{Z_F}{Z_S}$$

$$= -\frac{\frac{1}{s \cdot (C_1 + C_2)} \cdot \frac{1 + s \cdot R_1 \cdot C_1}{1 + s \cdot R_1 \cdot \frac{C_1 \cdot C_2}{C_1 + C_2}}}{R_2}$$

$$= -\frac{1}{s \cdot R_2 \cdot (C_1 + C_2)} \cdot \frac{1 + s \cdot R_1 \cdot C_1}{1 + s \cdot R_1 \cdot \frac{C_1 \cdot C_2}{C_1 + C_2}}$$

Integrator Pole

$1 + s \cdot R_1 \cdot C_1$

Zero

$1 + s \cdot R_1 \cdot \frac{C_1 \cdot C_2}{C_1 + C_2}$

Second Pole

Type II Compensator Transfer Function $H_2(s)$

$$H_2(s) = -\frac{1}{\omega_{P0}} \frac{1 + \frac{s}{\omega_Z}}{s \left(1 + \frac{s}{\omega_{P1}}\right)}$$
$$= -\frac{\omega_{P0}}{s} \frac{1 + \frac{s}{\omega_Z}}{1 + \frac{s}{\omega_{P1}}}$$

$$\omega_{P0} = 2 \cdot \pi \cdot f_{P0} = \frac{1}{R_2 \cdot (C_1 + C_2)}$$

$$f_{P0} = \frac{1}{2 \cdot \pi \cdot R_2 \cdot (C_1 + C_2)}$$

$$\omega_Z = 2 \cdot \pi \cdot f_Z = \frac{1}{R_1 \cdot C_1}$$

$$f_Z = \frac{1}{2 \cdot \pi \cdot R_1 \cdot C_1}$$

$$\omega_{P1} = 2 \cdot \pi \cdot f_{P1} = \frac{1}{R_1 \cdot \frac{C_1 \cdot C_2}{C_1 + C_2}}$$


$$f_{P1} = \frac{1}{2 \cdot \pi \cdot R_1 \cdot \frac{C_1 \cdot C_2}{C_1 + C_2}}$$

Type II Compensator Bode Plot

$$f_{P0} = 100\text{ Hz}$$

$$f_Z = 100\text{ Hz}$$

$$f_{P1} = 10\text{ kHz}$$

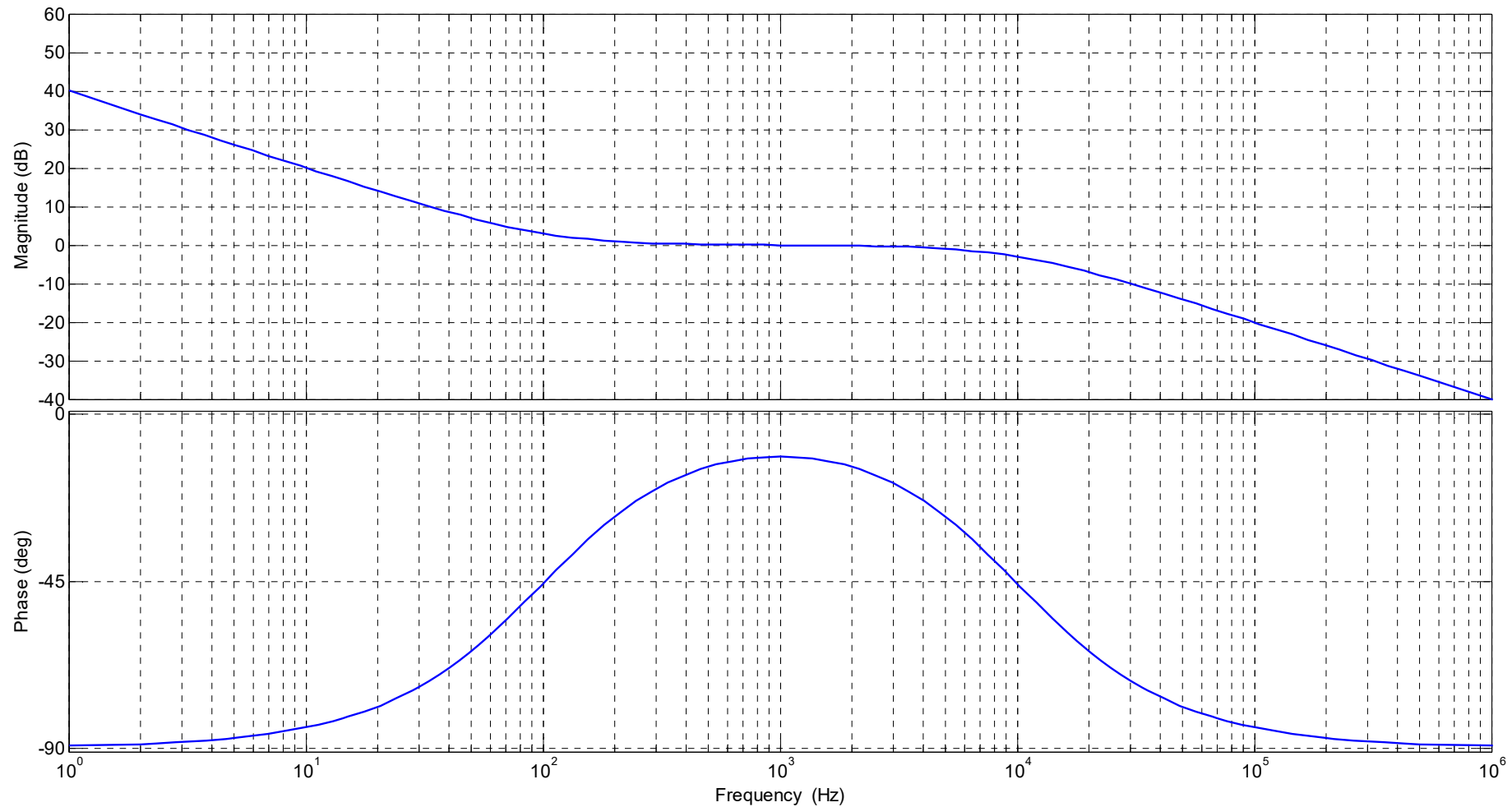


Type II Compensator Bode Plot

$$f_{P0} = 100 \text{ Hz}$$

$$f_Z = 100 \text{ Hz}$$

$$f_{P1} = 10 \text{ kHz}$$

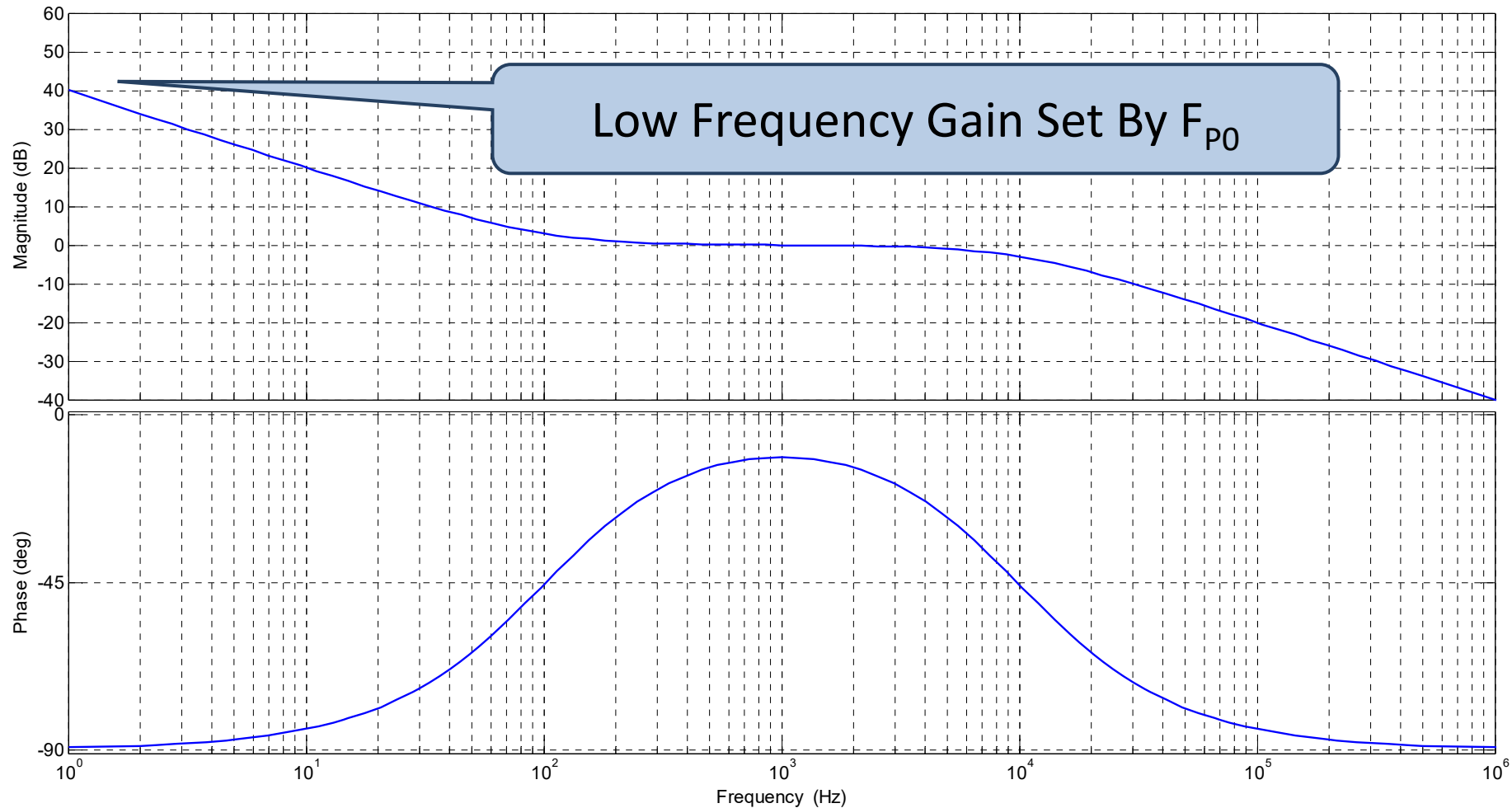


Type II Compensator Bode Plot

$$f_{P0} = 100 \text{ Hz}$$

$$f_Z = 100 \text{ Hz}$$

$$f_{P1} = 10 \text{ kHz}$$

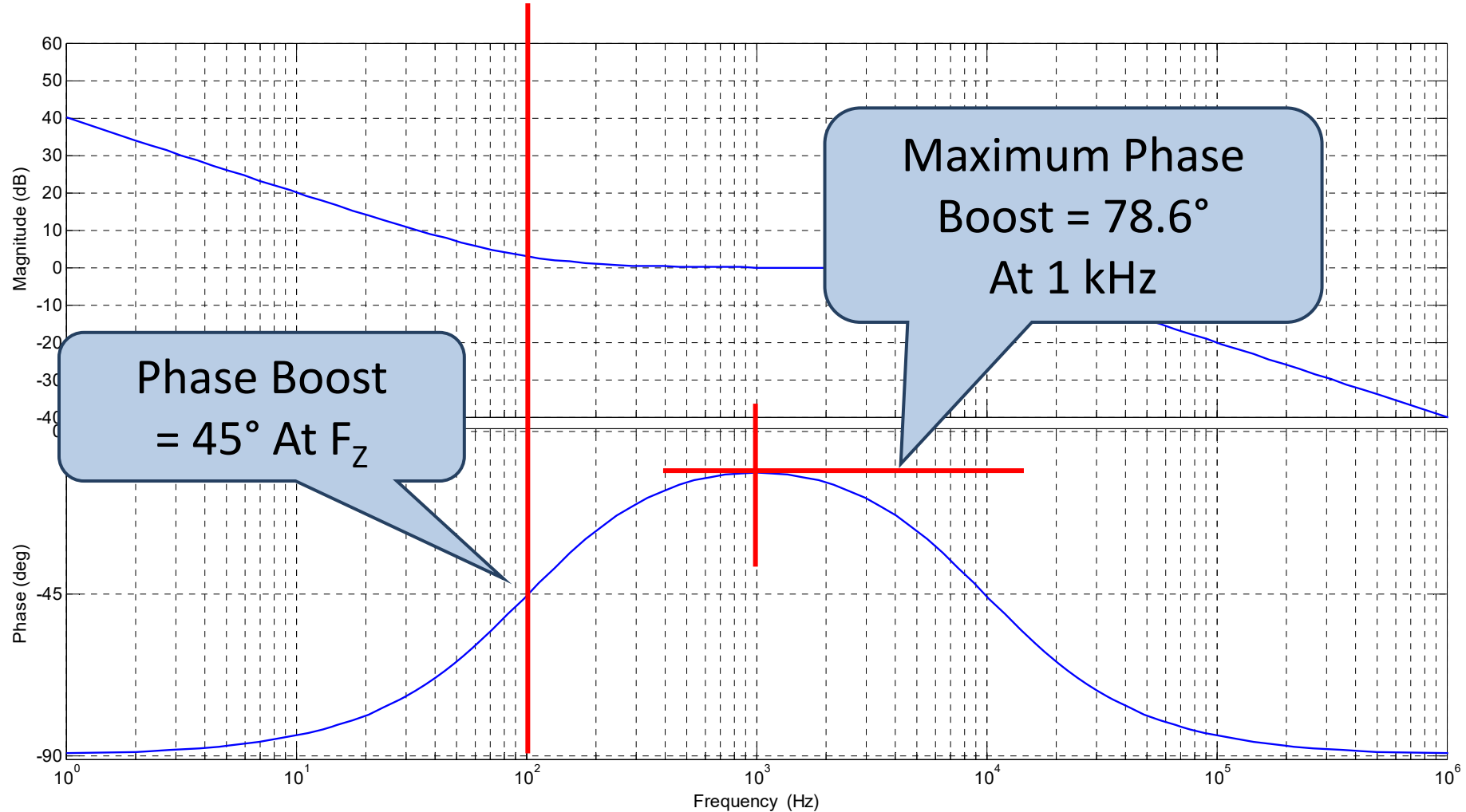


Calculating Component Values

- If $V_{OUT} > V_{REF}$ Choose Current (I_{BIAS}) Through R2 And R3
 - 100 μ A – 1 mA Typical

$$R_3 = \frac{V_{REF}}{I_{BIAS}}$$
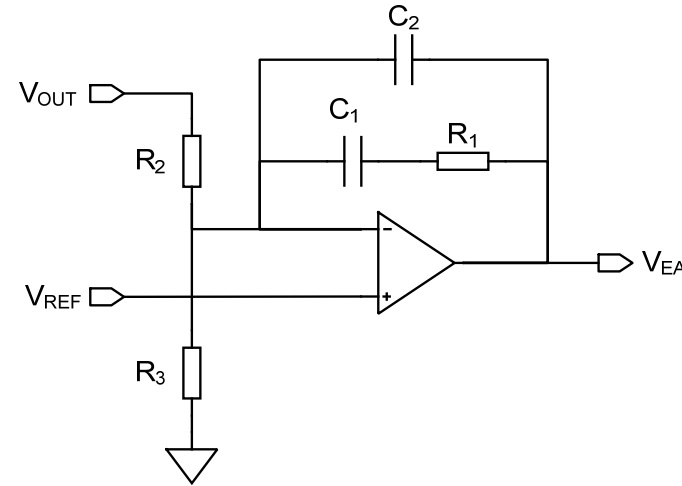
$$R_2 = \frac{V_{OUT} - V_{REF}}{V_{REF}} \cdot R_3$$




- If $V_{OUT} = V_{REF}$:
 - R3 Not Used
 - Choose Convenient Value For R2 (10 k Ω)

Calculating Component Values


Knowing The Desired Pole And Zero Frequencies Of The Compensator
The Individual Component Values Can Easily Be Calculated

$$C_2 = \frac{f_Z}{2 \cdot \pi \cdot R_2 \cdot f_{P1} \cdot f_{P0}} \quad R_1 = \frac{1}{2 \cdot \pi \cdot f_Z \cdot C_1}$$
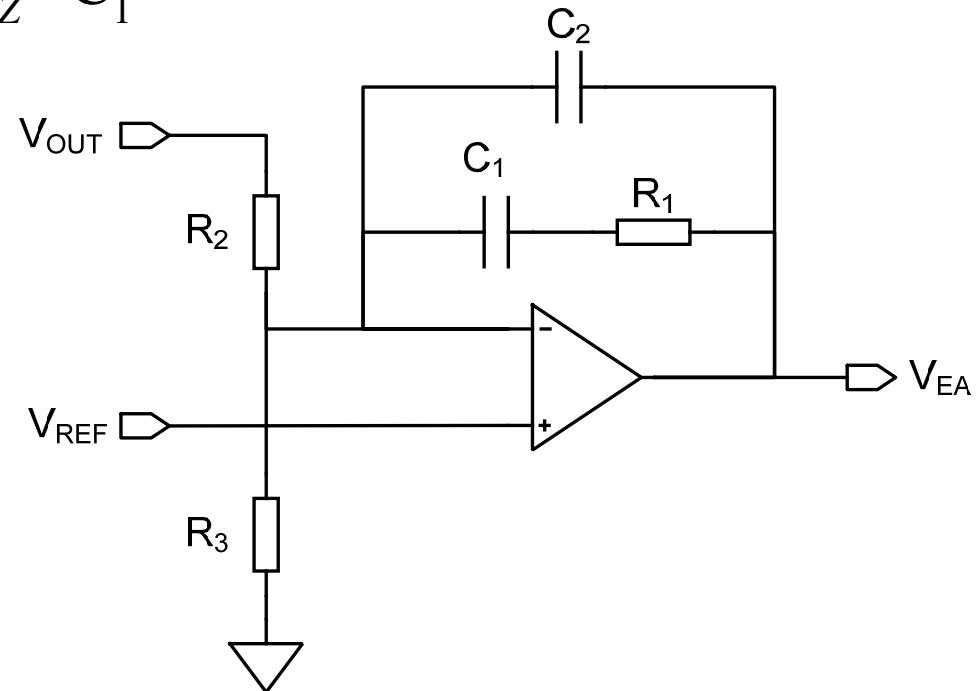
$$C_1 = \frac{1}{2 \cdot \pi \cdot R_2 \cdot f_{P0}} - C_2$$
$$= \frac{1}{2 \cdot \pi \cdot R_2 \cdot f_{P0}} \cdot \left(1 - \frac{f_Z}{f_{P1}} \right)$$




Type III Compensator

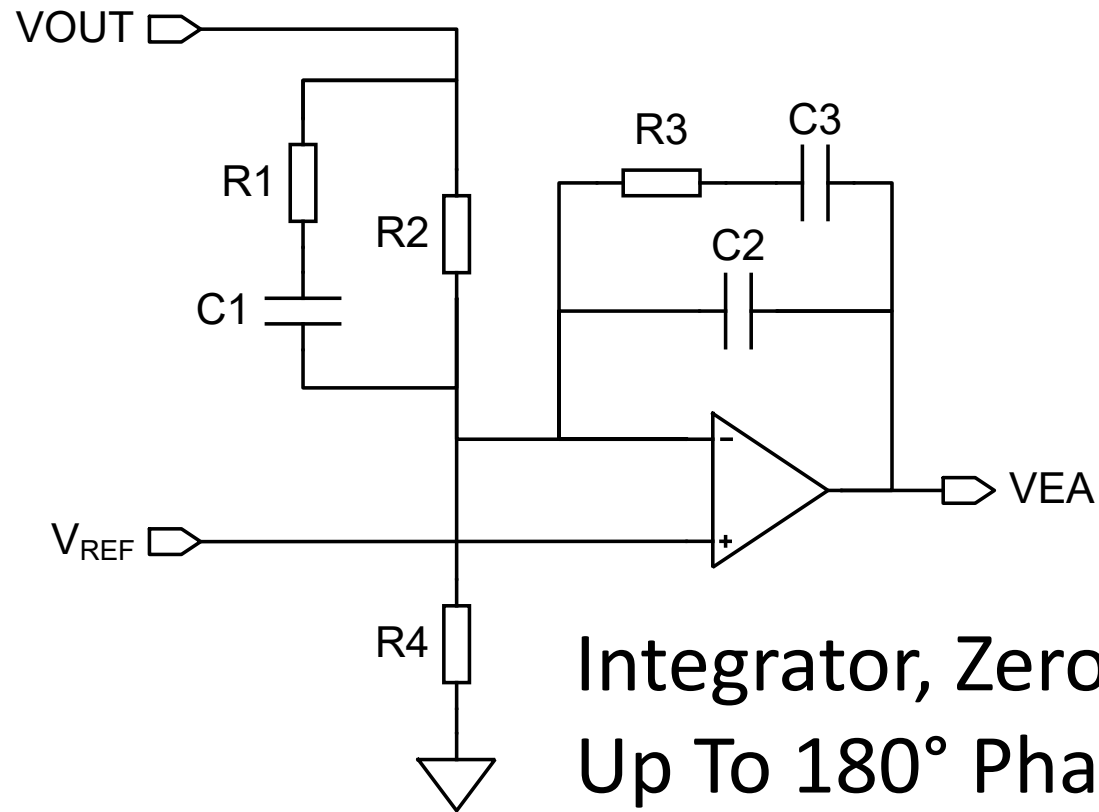

Type III Compensator


- Type III Compensator Used With Power Stages That Have More Than -90° Phase Shift
 - e.g. Buck Converter With Voltage Mode Control

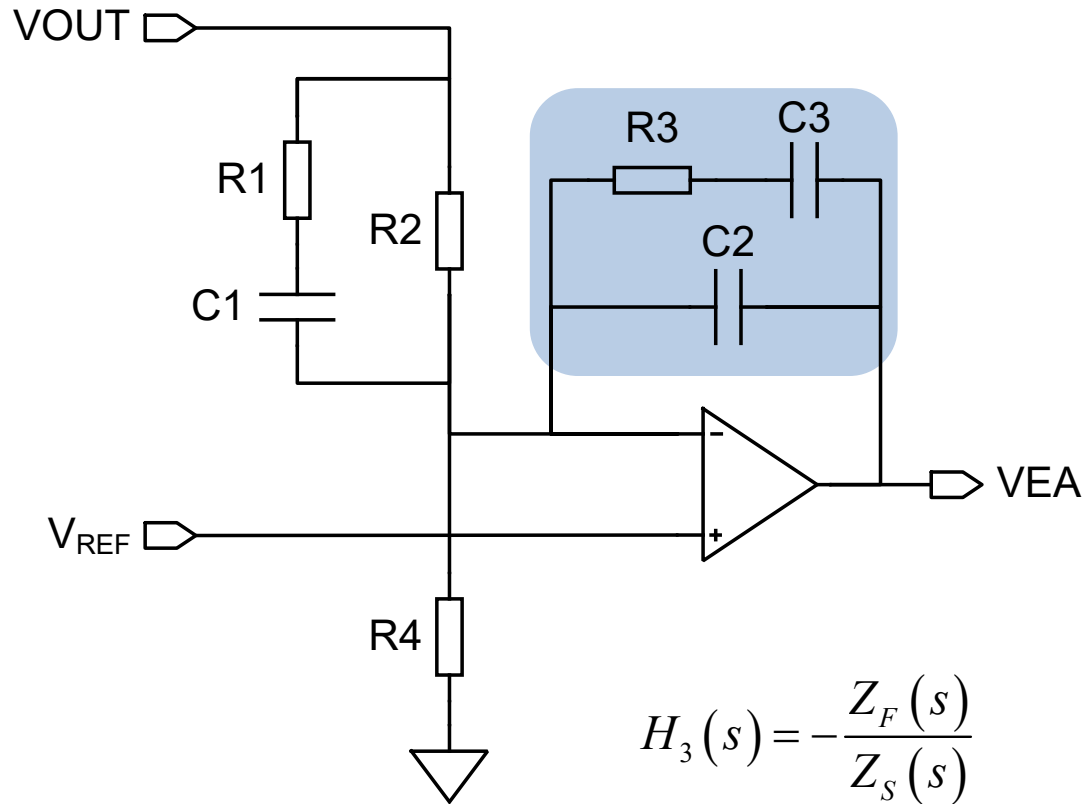Type III Compensator Transfer Function $H_3(s)$




$$\begin{aligned}
 Z_F(s) &= \frac{1}{s \cdot C_2} \parallel \left(R_3 + \frac{1}{s \cdot C_3} \right) = \frac{1}{s \cdot C_2} \parallel \left(\frac{1 + s \cdot R_3 \cdot C_3}{s \cdot C_3} \right) \\
 &= \frac{1}{s \cdot C_2} \cdot \frac{1 + s \cdot R_3 \cdot C_3}{s \cdot C_3} \\
 &= \frac{1}{s \cdot C_2 + \frac{1 + s \cdot R_3 \cdot C_3}{s \cdot C_3}} \cdot \frac{s \cdot C_2}{s \cdot C_2} \cdot \frac{s \cdot C_3}{s \cdot C_3} \\
 &= \frac{1 + s \cdot R_3 \cdot C_3}{s \cdot C_3 + s \cdot C_2 \cdot (1 + s \cdot R_3 \cdot C_3)} \\
 Z_F(s) &= \frac{1}{s} \cdot \frac{1 + s \cdot R_3 \cdot C_3}{C_3 + C_2 \cdot (1 + s \cdot R_3 \cdot C_3)}
 \end{aligned}$$

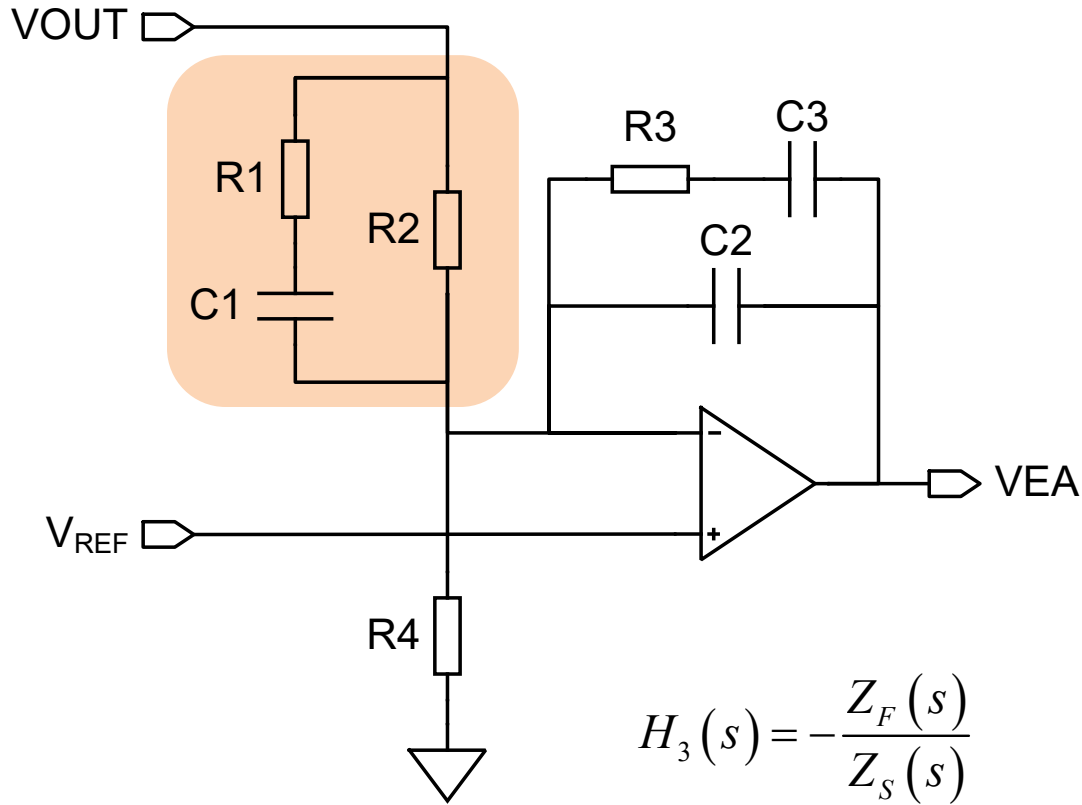Type III Compensator Transfer Function $H_3(s)$



$$\begin{aligned}
 Z_S(s) &= R_2 \parallel \left(R_1 + \frac{1}{s \cdot C_1} \right) = R_2 \parallel \frac{1 + s \cdot R_1 \cdot C_1}{s \cdot C_1} \\
 &= \frac{R_2 \cdot \left(\frac{1 + s \cdot R_1 \cdot C_1}{s \cdot C_1} \right)}{R_2 + \left(\frac{1 + s \cdot R_1 \cdot C_1}{s \cdot C_1} \right)} = R_2 \cdot \frac{1 + s \cdot R_1 \cdot C_1}{1 + s \cdot R_1 \cdot C_1 + s \cdot R_2 \cdot C_1} \\
 &= R_2 \cdot \frac{1 + s \cdot R_1 \cdot C_1}{1 + s \cdot (R_1 + R_2) \cdot C_1}
 \end{aligned}$$

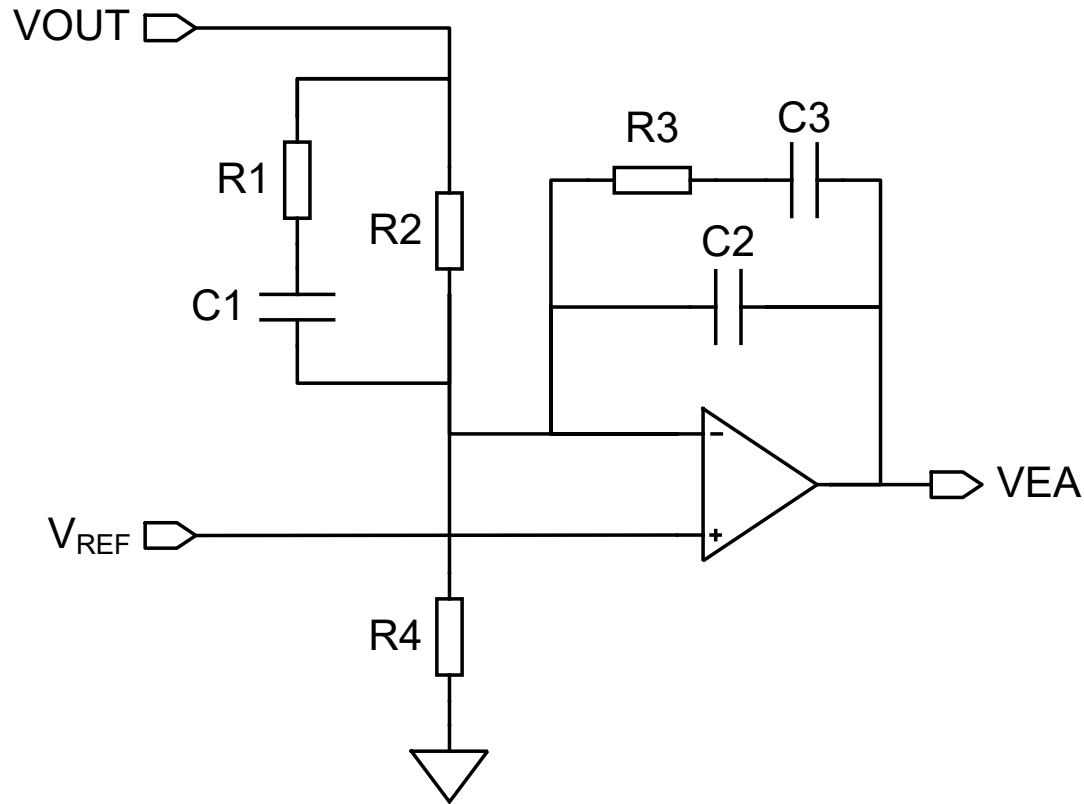Type III Compensator Transfer Function $H_3(s)$



$$H_3(s) = -\frac{Z_F(s)}{Z_S(s)}$$

$$= -\frac{\frac{1}{s \cdot (C_2 + C_3)} \cdot \frac{1 + s \cdot R_3 \cdot C_3}{1 + s \cdot R_3 \cdot \frac{C_2 \cdot C_3}{C_2 + C_3}}}{R_2 \cdot \frac{1 + s \cdot R_1 \cdot C_1}{1 + s \cdot (R_1 + R_2) \cdot C_1}}$$

$$H_3(s) = -\frac{1}{s \cdot R_2 \cdot (C_2 + C_3)} \cdot \frac{1 + s \cdot R_3 \cdot C_3}{1 + s \cdot R_1 \cdot C_1} \cdot \frac{1 + s \cdot (R_1 + R_2) \cdot C_1}{1 + s \cdot R_3 \cdot \frac{C_2 \cdot C_3}{C_2 + C_3}}$$

Type III Compensator Transfer Function $H_3(s)$

$$H_3(s) = -\frac{\omega_{P0}}{\omega} \cdot \frac{\left(1 + \frac{\omega}{\omega_{Z1}}\right) \cdot \left(1 + \frac{\omega}{\omega_{Z2}}\right)}{\left(1 + \frac{\omega}{\omega_{P1}}\right) \cdot \left(1 + \frac{\omega}{\omega_{P2}}\right)}$$

$$\omega_{P0} = \frac{1}{R_2 \cdot (C_2 + C_3)}$$

$$f_{P0} = \frac{1}{2 \cdot \pi \cdot R_2 \cdot (C_2 + C_3)}$$

$$\omega_{Z1} = \frac{1}{R_3 \cdot C_3}$$

$$f_{Z1} = \frac{1}{2 \cdot \pi \cdot R_3 \cdot C_3}$$

$$\omega_{Z2} = \frac{1}{(R_1 + R_2) \cdot C_1}$$

$$f_{Z2} = \frac{1}{2 \cdot \pi \cdot (R_1 + R_2) \cdot C_1}$$

$$\omega_{P1} = \frac{1}{R_1 \cdot C_1}$$


$$f_{P1} = \frac{1}{2 \cdot \pi \cdot R_1 \cdot C_1}$$

$$\omega_{P2} = \frac{1}{R_3 \cdot \frac{C_2 \cdot C_3}{C_2 + C_3}}$$

$$f_{P2} = \frac{1}{2 \cdot \pi \cdot R_3 \cdot \frac{C_2 \cdot C_3}{C_2 + C_3}}$$


Type III Bode Plot
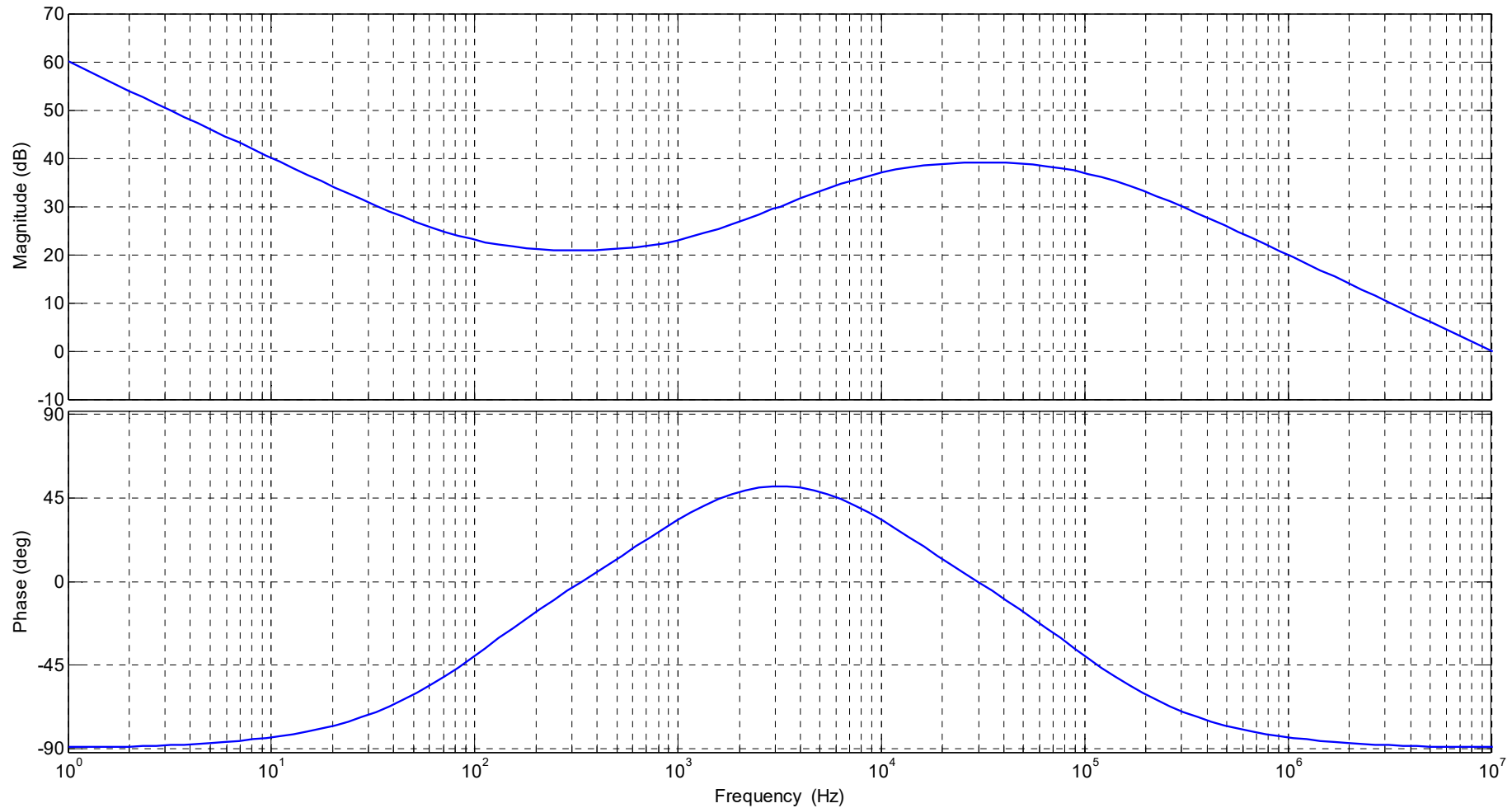
$$f_{P0} = 1000\text{Hz} \quad f_{Z1} = 100\text{Hz} \quad f_{Z2} = 1000\text{Hz} \quad f_{P1} = 10\text{kHz} \quad f_{P2} = 100\text{kHz}$$




Type III Bode Plot
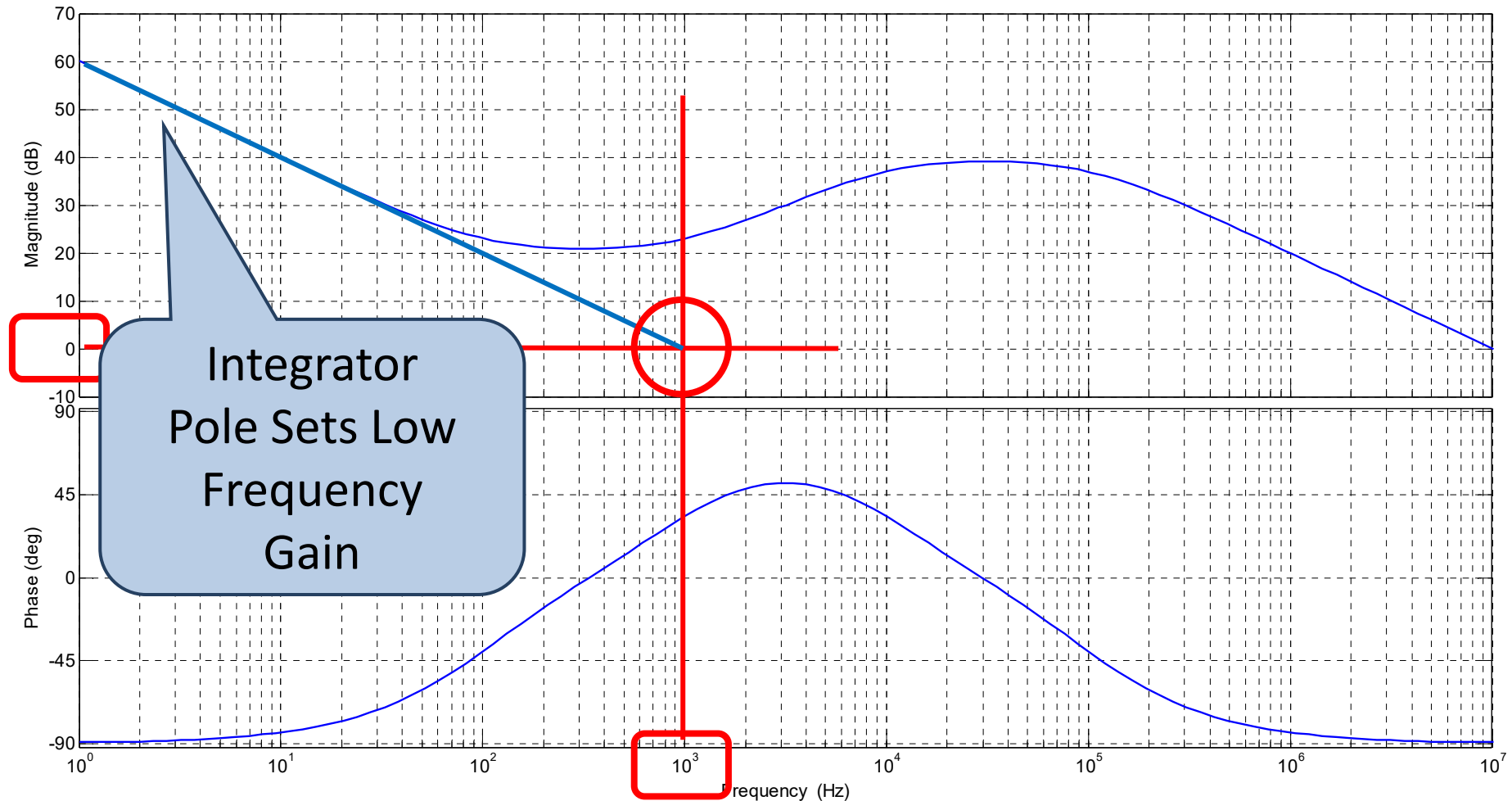
$$f_{P0} = 1000\text{ Hz} \quad f_{Z1} = 100\text{ Hz} \quad f_{Z2} = 1000\text{ Hz} \quad f_{P1} = 10\text{ kHz} \quad f_{P2} = 100\text{ kHz}$$




Type III Bode Plot
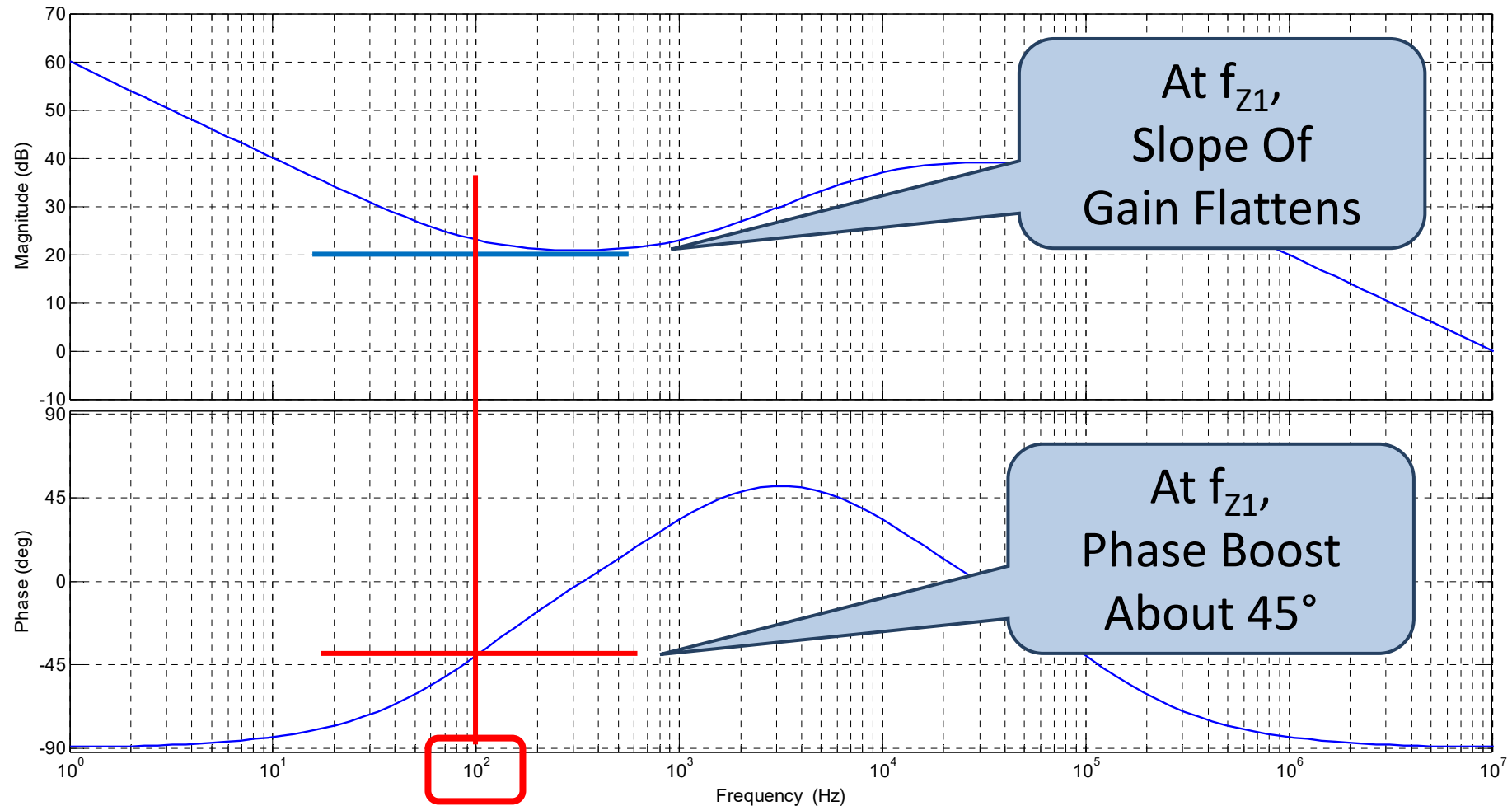
$$f_{P0} = 1000\text{Hz} \quad f_{Z1} = 100\text{Hz} \quad f_{Z2} = 1000\text{Hz} \quad f_{P1} = 10\text{kHz} \quad f_{P2} = 100\text{kHz}$$




Type III Bode Plot
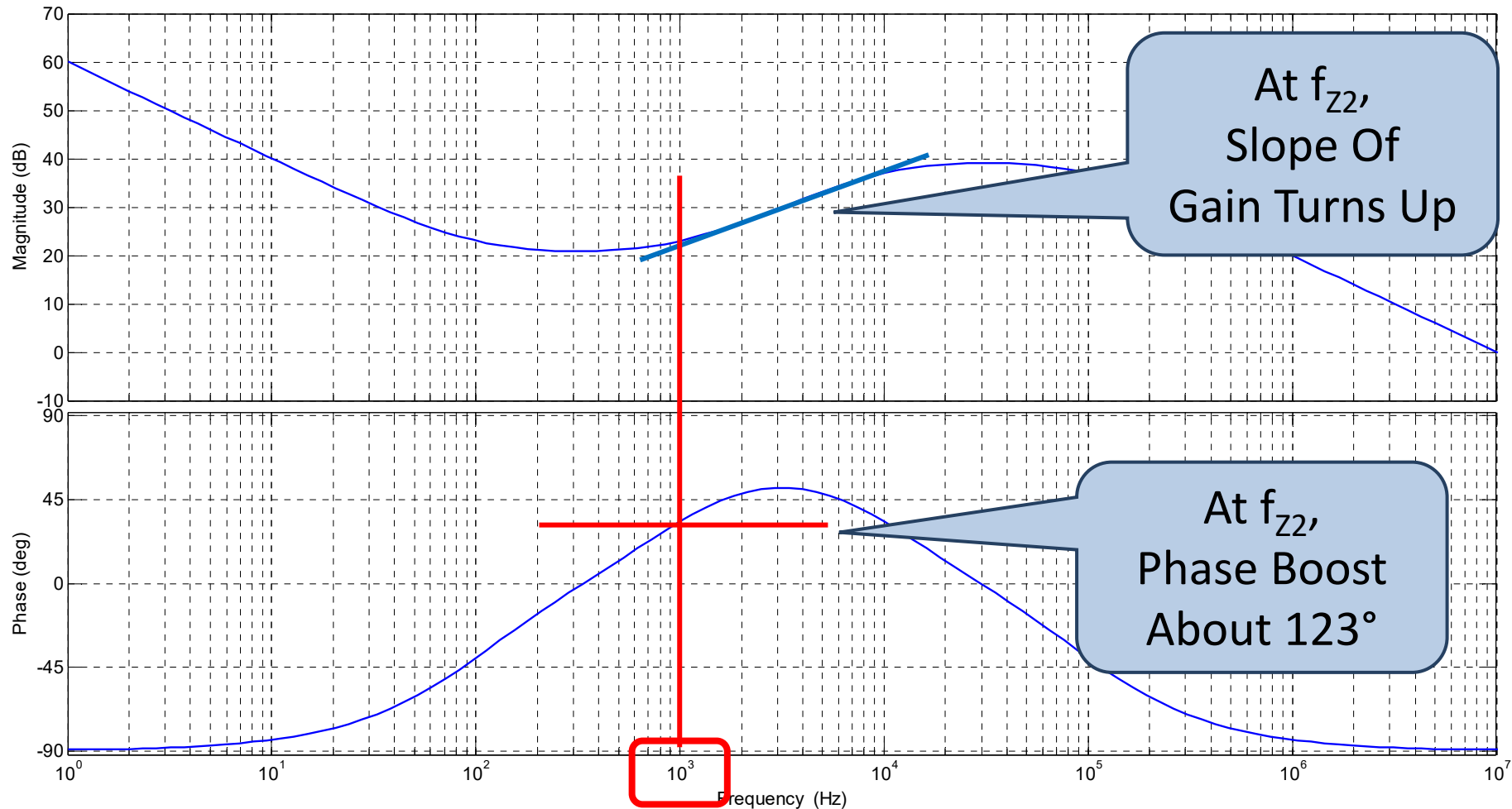
$$f_{P0} = 1000\text{Hz} \quad f_{Z1} = 100\text{Hz} \quad f_{Z2} = 1000\text{Hz} \quad f_{P1} = 10\text{kHz} \quad f_{P2} = 100\text{kHz}$$




Type III Bode Plot
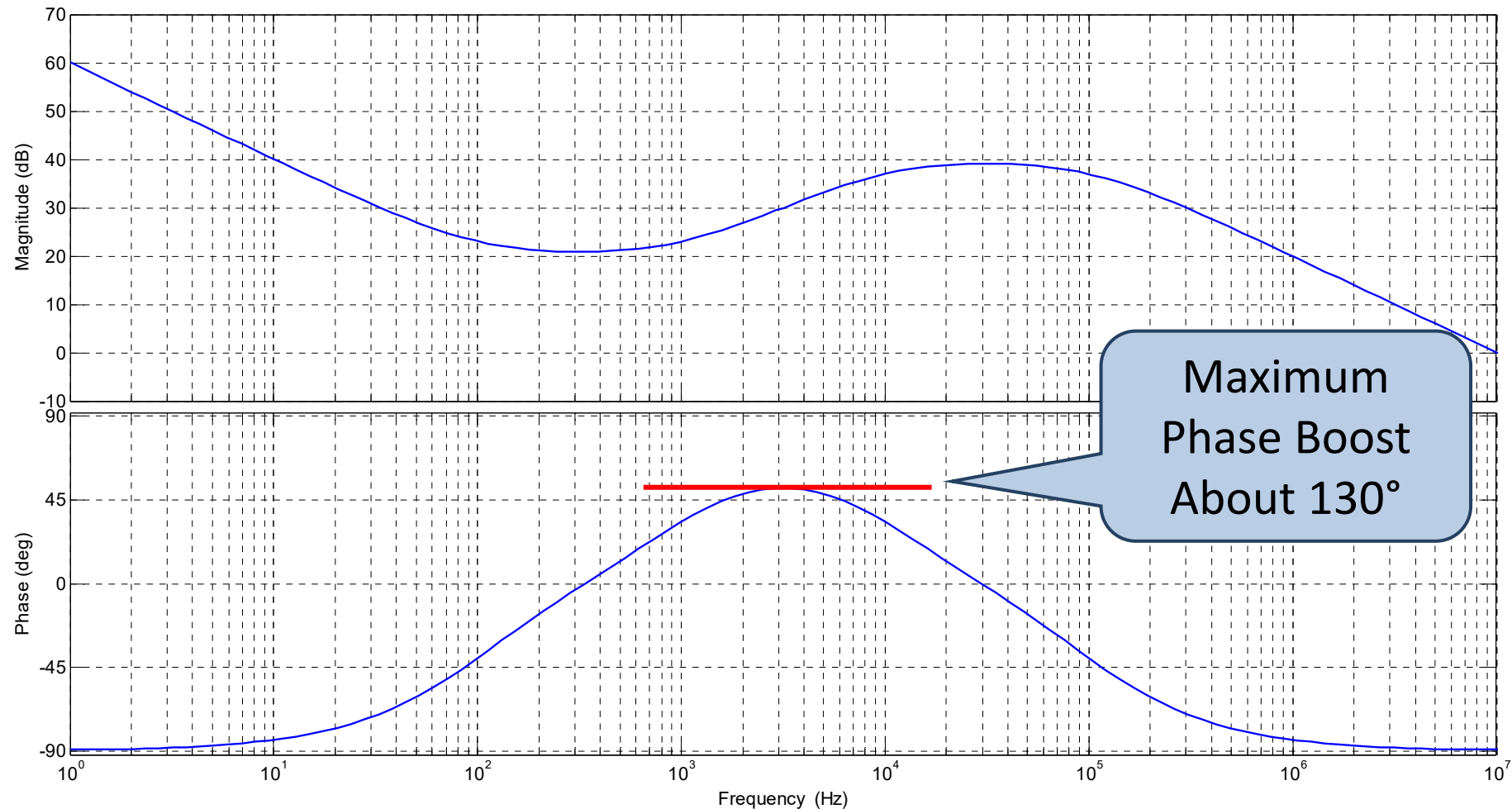
$$f_{P0} = 1000\text{Hz} \quad f_{Z1} = 100\text{Hz} \quad f_{Z2} = 1000\text{Hz} \quad f_{P1} = 10\text{kHz} \quad f_{P2} = 100\text{kHz}$$




Type III Bode Plot
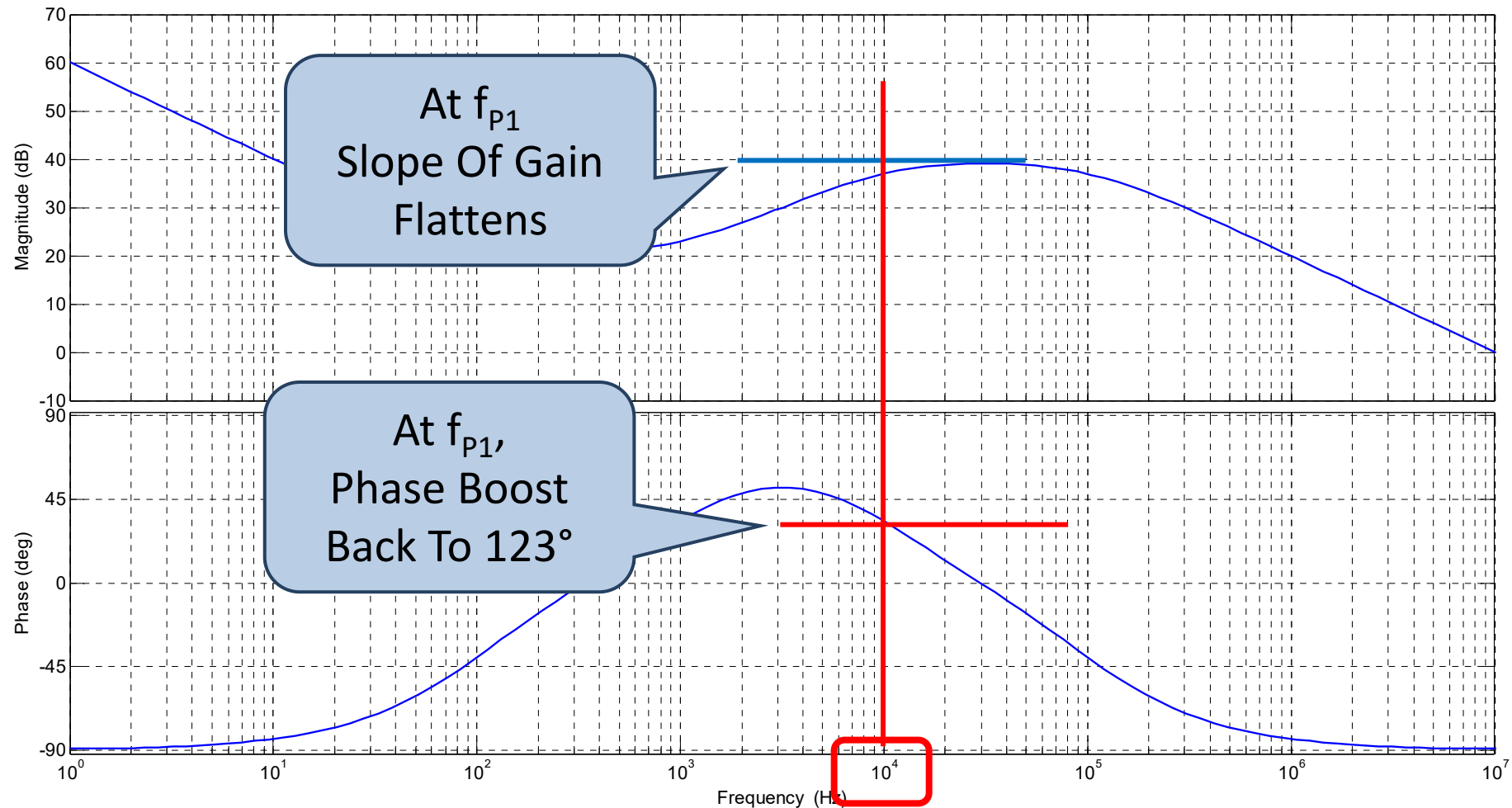
$$f_{P0} = 1000\text{Hz} \quad f_{Z1} = 100\text{Hz} \quad f_{Z2} = 1000\text{Hz} \quad \boxed{f_{P1} = 10\text{kHz}} \quad f_{P2} = 100\text{kHz}$$



Type III Bode Plot
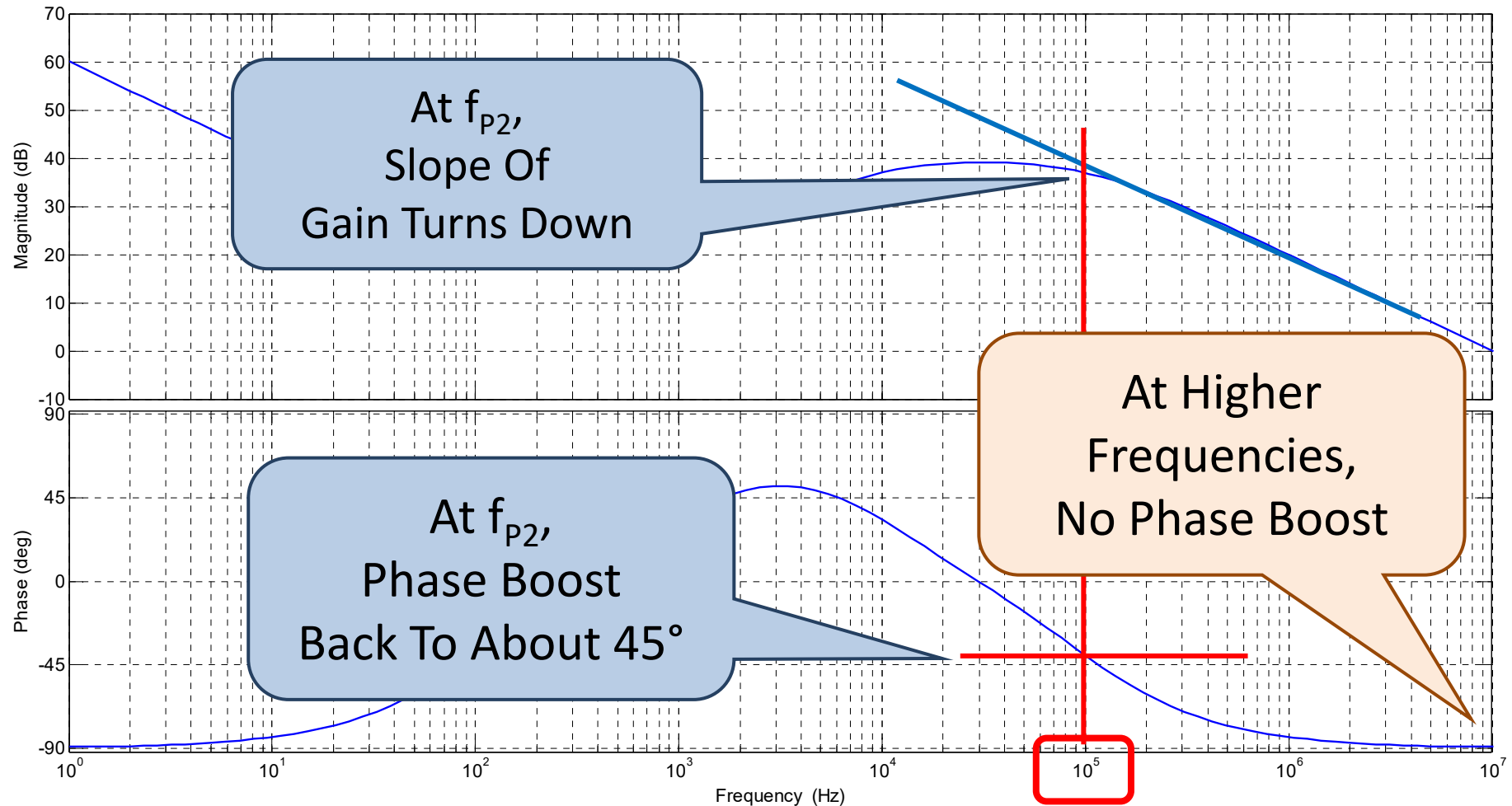
$$f_{P0} = 1000\text{Hz} \quad f_{Z1} = 100\text{Hz} \quad f_{Z2} = 1000\text{Hz} \quad f_{P1} = 10\text{kHz} \quad f_{P2} = 100\text{kHz}$$



Choosing Compensator Poles And Zeroes

Given

- F_{SW}
- F_{LC}

- F_{ESR}
- 70° Phase Margin

Choose

- $F_C = F_{SW}/10$
- $F_{Z1} = F_{LC}$
- $F_{Z2} = 0.75 \times F_{LC}$
- $F_{Z_ESR} = F_{ESR}$
- $F_{HFP} = 2.7 \times F_C$


This Will Give You A Good Starting Point
With Confidence Loop Will Be Stable

Calculating Component Values

- If $V_{OUT} > V_{REF}$ Choose Current (I_{BIAS}) Through R2 And R4
 - 100 μ A - 1 mA Typical

$$R_4 = \frac{V_{REF}}{I_{BIAS}}$$
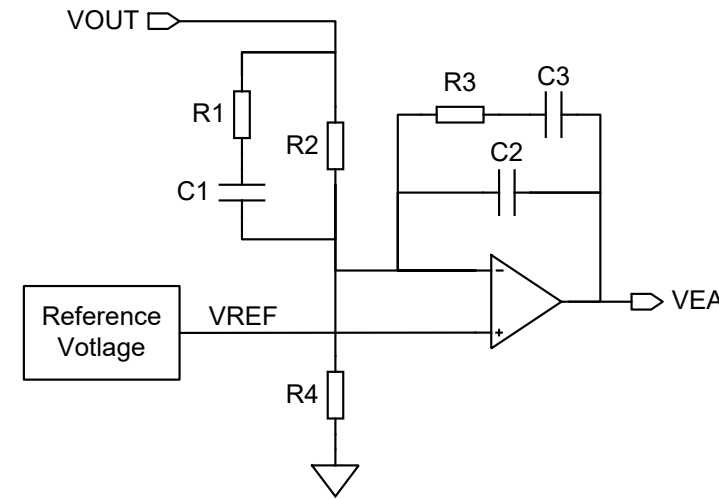
$$R_2 = \frac{V_{OUT} - V_{REF}}{V_{REF}} \cdot R_4$$



- If $V_{OUT} = V_{REF}$:
 - R4 Not Used
 - Choose Convenient Value For R2 (10 k Ω)

Calculating Component Values

Knowing The Desired Pole And Zero Frequencies Of The Compensator
The Individual Component Values Can Easily Be Calculated

$$R_1 = \frac{f_{Z2}}{f_{P1} - f_{Z2}} \cdot R_2$$

$$C_3 = \frac{1}{2 \cdot \pi \cdot f_{P0} \cdot R_2} - C_2$$

$$C_1 = \frac{1}{2 \cdot \pi \cdot f_{P1} \cdot R_1}$$

$$R_3 = \frac{1}{2 \cdot \pi \cdot f_{Z1} \cdot C_3}$$

$$C_2 = \frac{f_{Z1}}{2 \cdot \pi \cdot f_{P2} \cdot f_{P0} \cdot R_2}$$

